



تقدم لجنة EICoM الاكاديمية

دفتر لمادة:

الالكترونيات (2)

من شرح:


د. هادي العيثاوي

جزيل الشكر للطالب:


عدنان حورانبي



Chapter (6) = Basic (BJT) Amplifiers :-

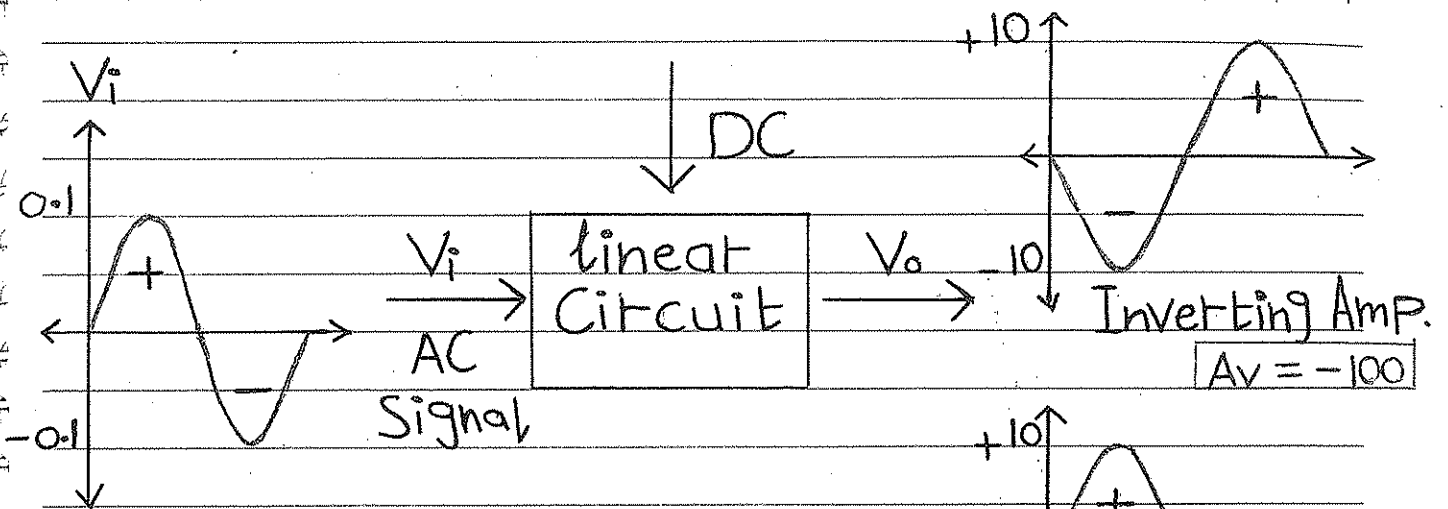

$$V_o = A_v \cdot V_i$$

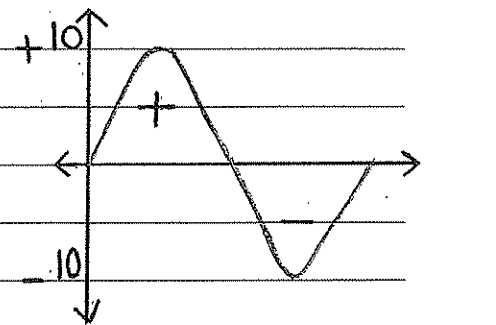

Non-Inverting Amp.

$$A_v = 100$$

$$A_v = \text{Voltage gain} = \frac{V_o}{V_i}$$

$$V_o = A_v \cdot V_i$$

Amplifier : Linear electronic Circuit

Contains :

- Active devices : (BJT, MOSFET, JFET, OP-Amp), to Amplify the AC i/P Signal.
- DC Sources : Biasing Active Devices in the required mode.


◆ Resistors : Voltage-divider, limiting Resistor, load.

◆ Capacitors : Coupling for AC Signal

$$(X_c = \frac{1}{2\pi fC} \approx 0)$$

Blocking for DC Signal

$$(X_c = \frac{1}{2\pi fC} = \infty)$$

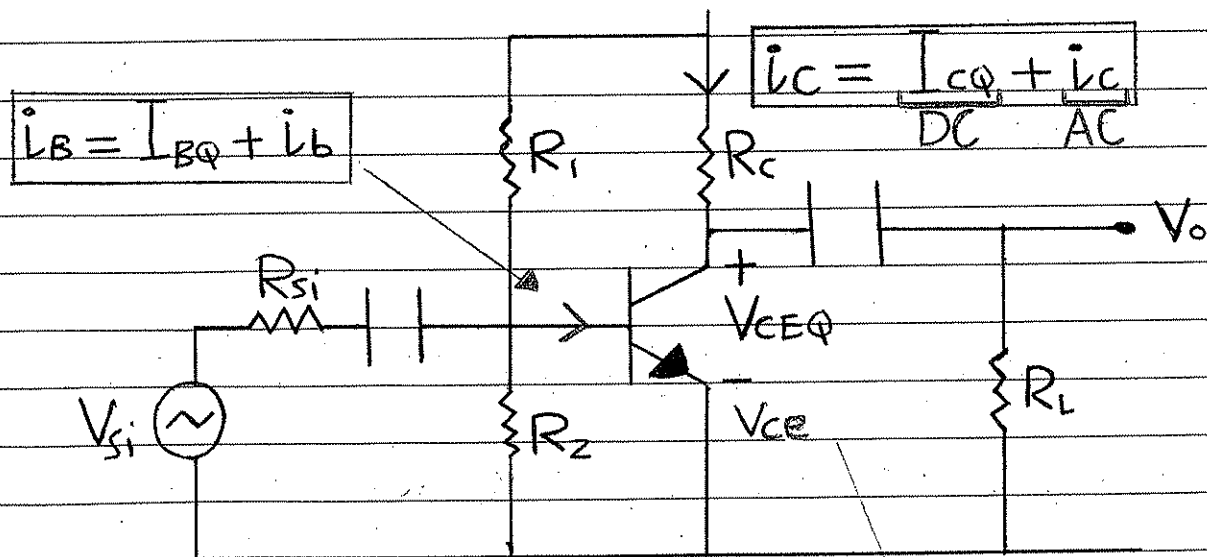

$$V_{ce} = V_{ceq} + V_{ce}$$

Since the Amp. is linear CCT. So


Superposition can be Applied ;

i.e the total response is the D.C response
+ AC response.


1) For D.C : [All Cap.s are open and
AC Source. = 0]

The DC Source will bias the BJT in
Forward Active mode at a certain

Q-Pt. ; I_{BQ} , I_{CQ} , V_{CEQ} .

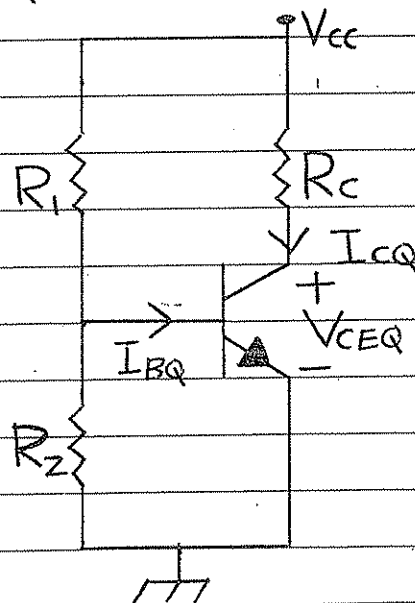


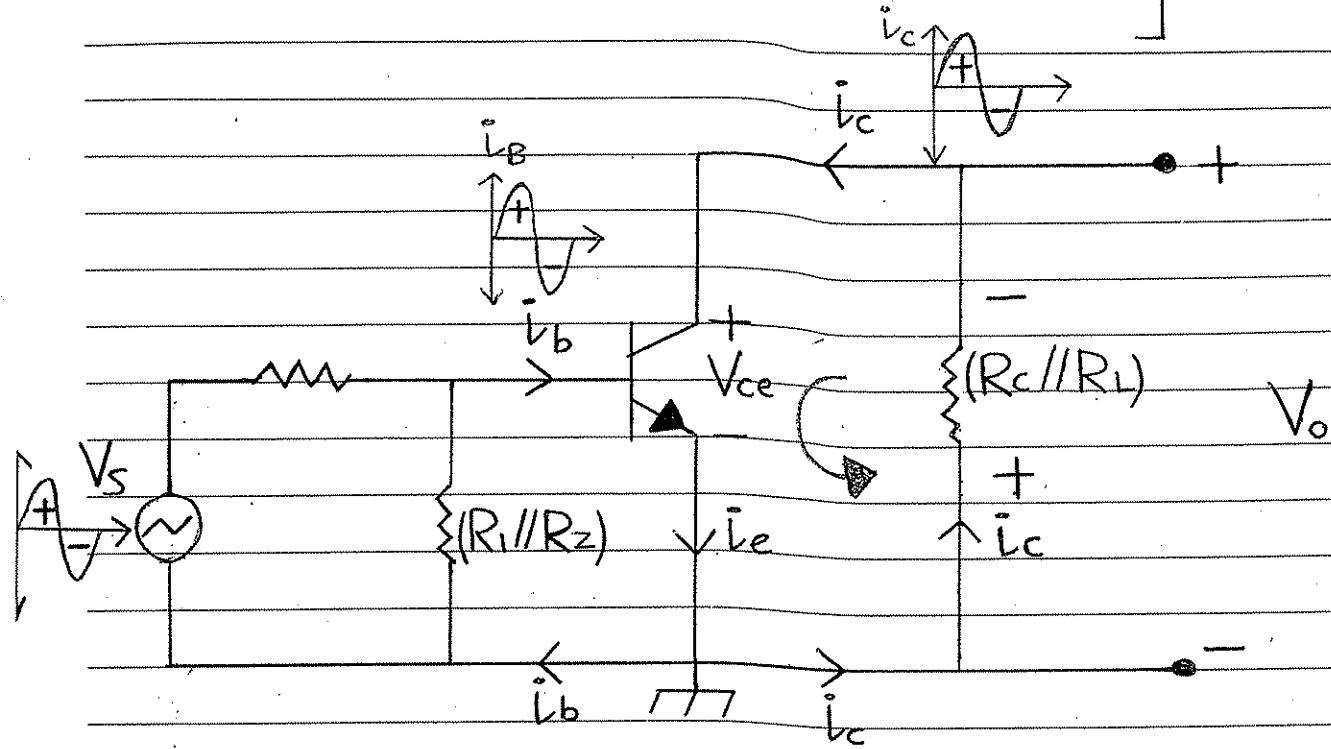2) For AC : [All Cap.s are Short cct,
and DC Source \rightarrow Short cct.]



$$V_{ce} + i_c (R_c // R_L) = 0$$

$$V_{ce} = -i_c (R_c // R_L)$$

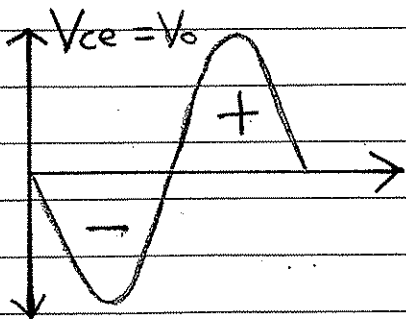

$$V_o = -i_c (R_c // R_L)$$

The AC i/p signal will drive an (a.c base current (i_b)) which will cause an (a.c collector current ($i_c = \beta i_b$)).

i_c will flow through (R_c or $R_c // R_L$) causing an a.c o/p voltage :

$$V_o = V_{ce} = -i_c (R_c // R_L)$$

#

3) Since the Amp. contains DC & AC sources and it is linear CCT., So according to Superposition the total response is :

$$i_B = I_{BQ} + i_b$$

$$i_C = I_{CQ} + i_c$$




$$V_{CE} = V_{CEQ} + v_{ce}$$

#

For $I_{BQ} = 10 \mu A$, $I_{CQ} = 0.5 \text{ mA}$,

$V_{CEQ} = 5 \text{ V}$; $i_b = 5 \sin \omega t \mu A$,

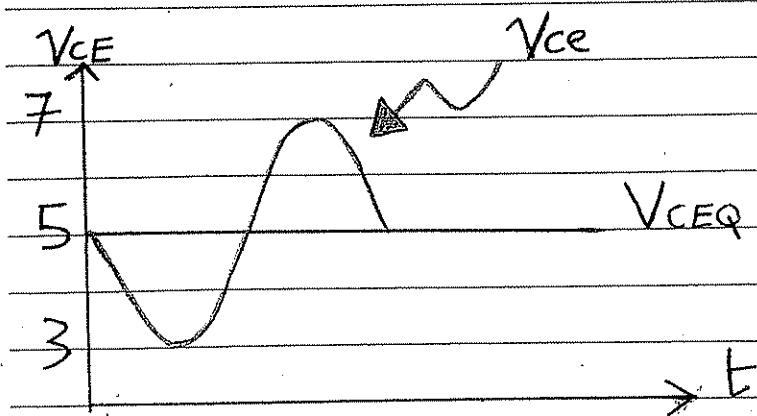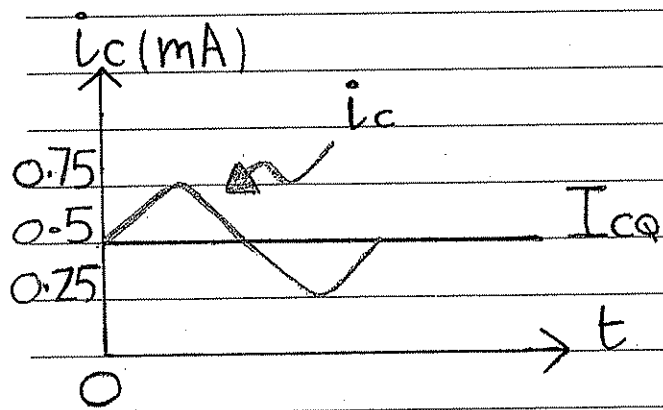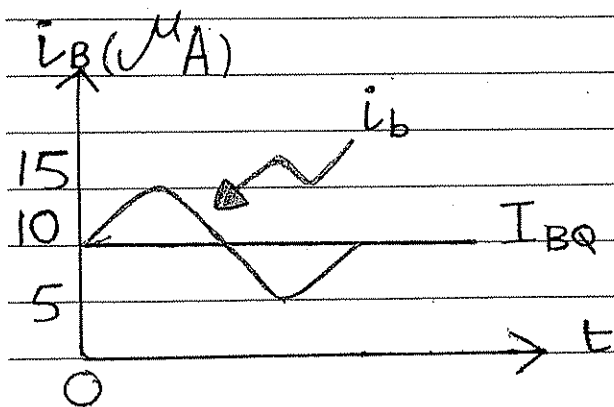
$i_c = 0.25 \sin \omega t \text{ mA}$, $V_{ce} = -2 \sin \omega t \text{ V}$



* For Amp., the BJT must be biased in Forward Active mode.

BJT Amp. :-

1] Common - Emitter Amp. :-

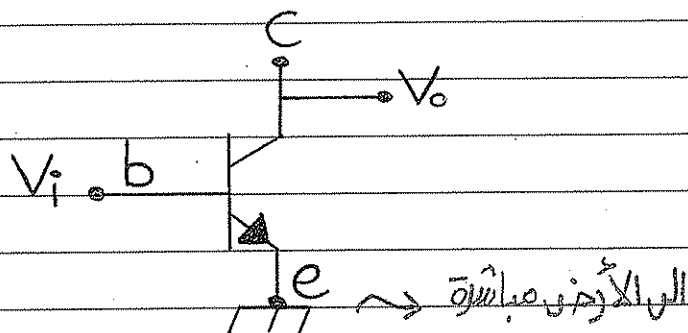


(i) Basic C-E Amp.


E \rightarrow Common-terminal.

Input to base.

Output from Collector.

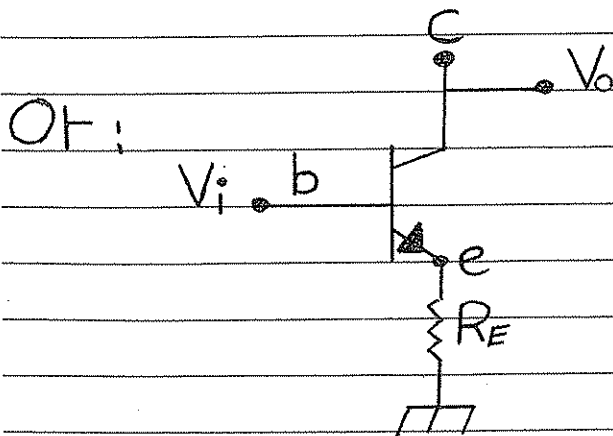


(ii) C-E with R_E .

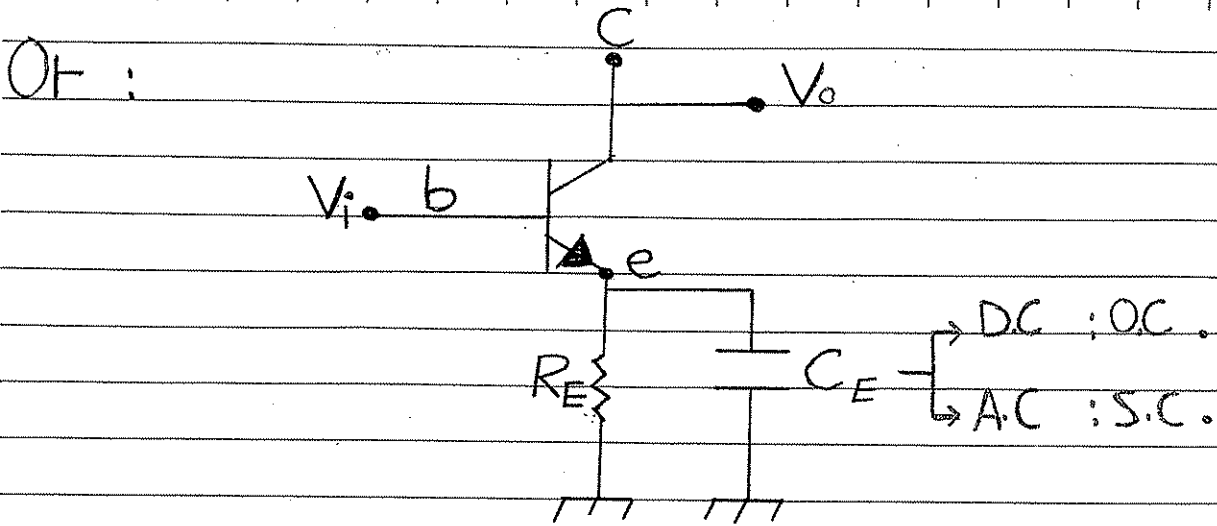

(iii) C-E with bypass Cap. (C_E)

i Basic C-E Amp. :-

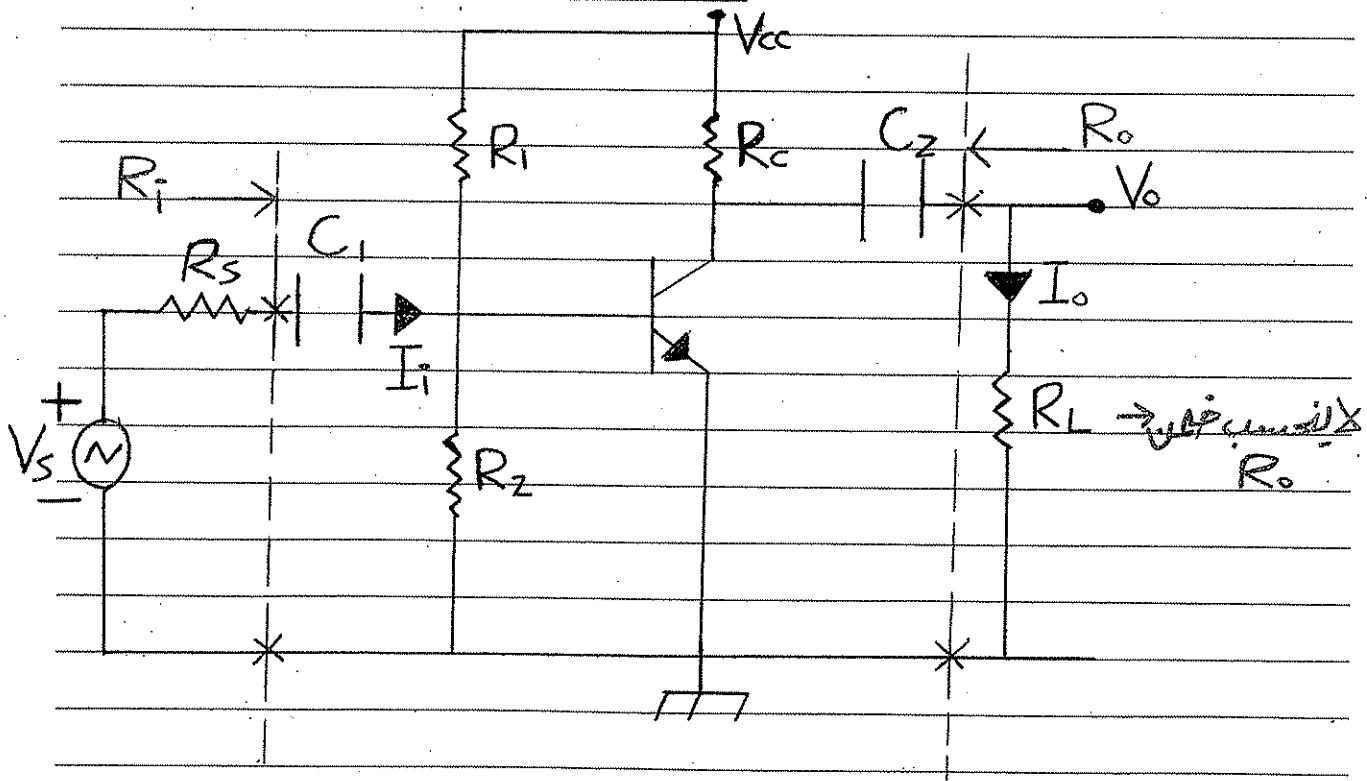

Voltage-gain = $A_v = \frac{V_o}{V_s}$


Current-gain = $A_I = \frac{I_o}{I_i}$

Input Resistance : R_i

Output Resistance : R_o

R_i seen by Signal Voltage generator = $R_i + R_s$

EXA. :-

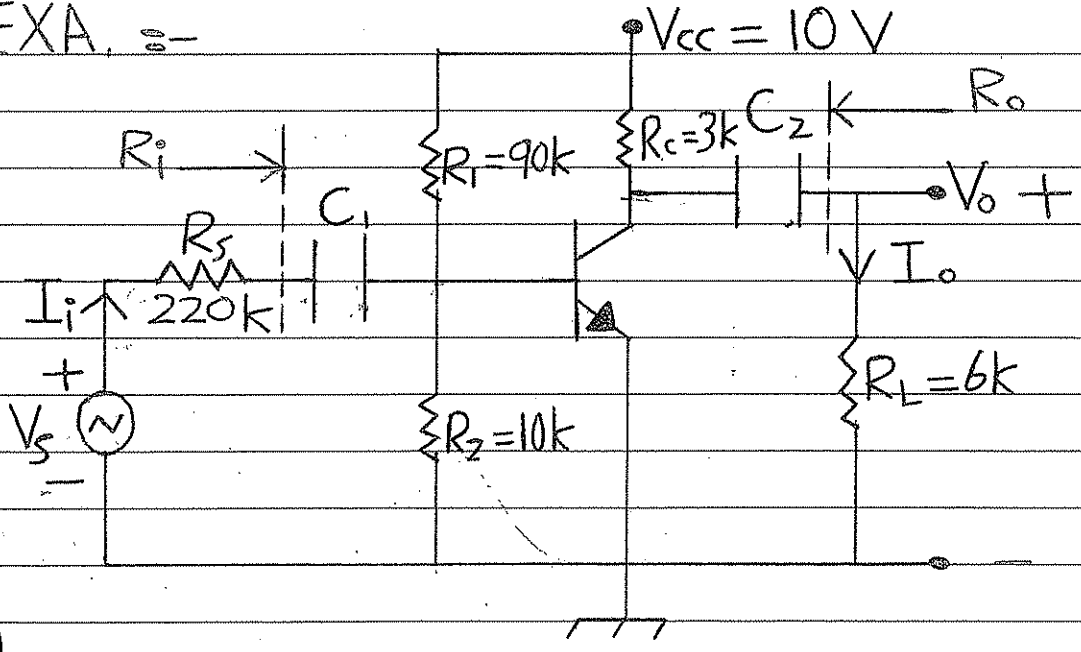

1)

Given $\beta = 50$, $V_{BE} = 0.7V$, $V_A = 160V$

Calculate I_{BQ} , I_{CQ} , V_{CEQ} .

2) Draw Small-Signal Equivalent cct. of the Amp. and find :

a) Voltage-gain. $A_v = \frac{V_o}{V_i}$

b) Current-gain. $A_I = \frac{I_o}{I_i}$

c) Input Resistance. R_i

d) Output Resistance. R_o


Sol.

① For DC Analysis :-

All Caps are Open CCT. :-

$$R_{Th} = R_1 // R_2 \\ = 9 \text{ k}\Omega$$
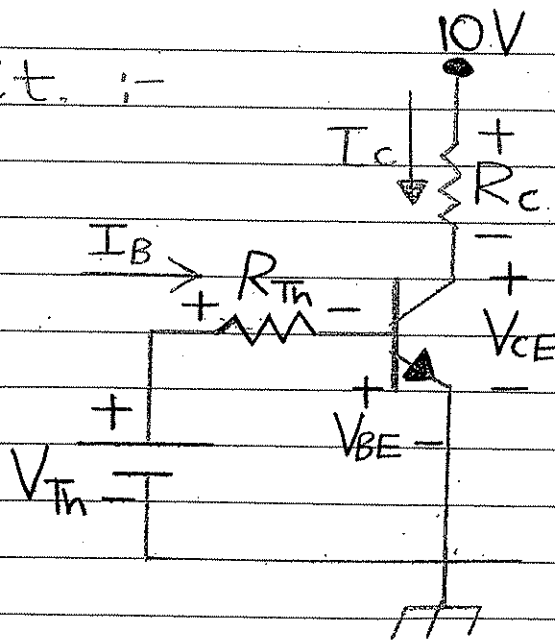
$$V_{Th} = \frac{10 * 10}{100} = 1 \text{ V}$$



KVL for BE loop :

$$-V_{Th} + R_{Th} I_B + V_{BE} = 0$$

$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th}} = \frac{1 - 0.7}{9} = 0.3 = 0.033 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 50 * 0.033 = 1.67 \text{ mA} = I_{BQ}$$

KVL for CE loop :


$$-V_{CC} + I_C R_C + V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$


$$= 10 - 1.67 * 3 = 10 - 5 = 5 \text{ V}$$

The BJT in F.A.M.

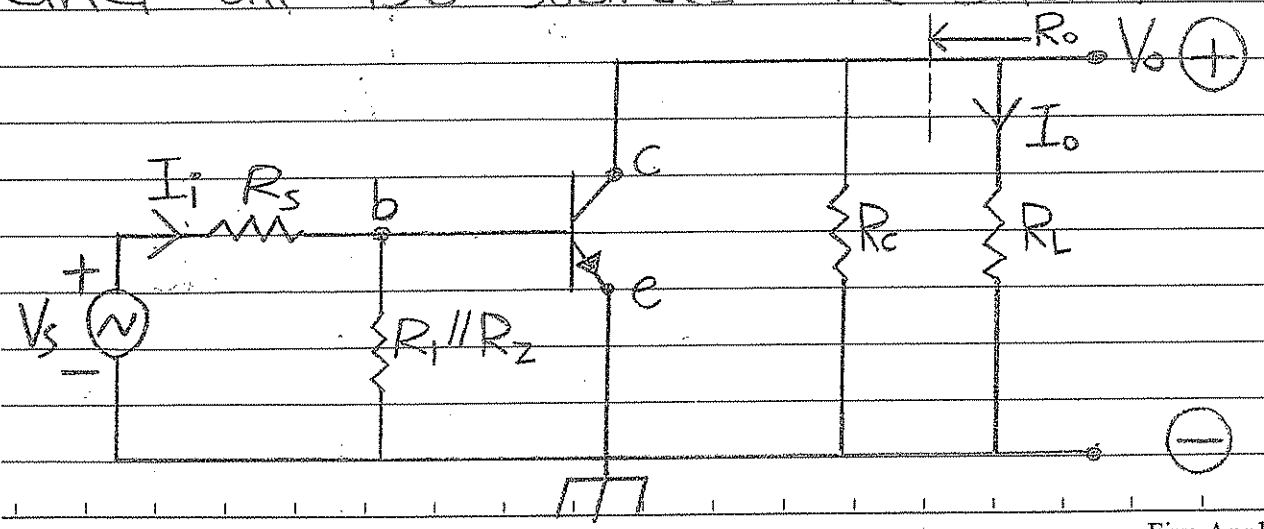② A.C Analysis : All Caps are short cct. and all DC Sources are short.



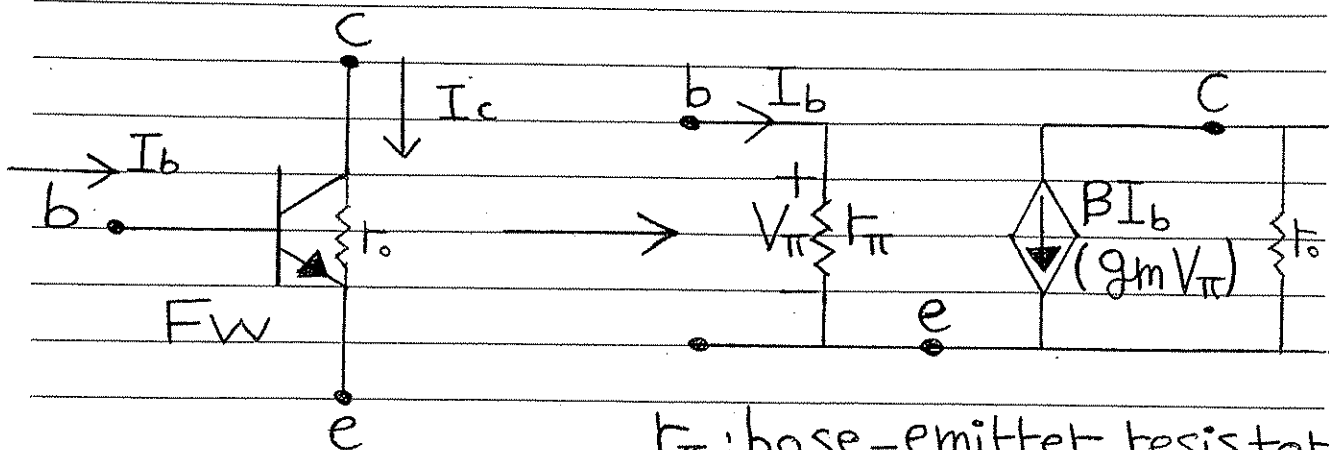To perform A.C Analysis, the (BJT) must be replaced by its model.



r_{π} : base-emitter resistor.

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{V_T}{\frac{I_{CQ}}{\beta}} = \frac{\beta V_T}{I_{CQ}}$$

Where: V_T : Thermal Voltage

$$V_T = 26 \text{ mV at R.T.}$$

g_m : Transconductance



$$g_m = \frac{I_{CQ}}{V_T}$$


r_o : Transistor O/P Resistance.

$$r_o = \frac{V_A}{I_{CQ}}$$

V_A : Early Voltage, (given) $[50V < V_A < 300V]$

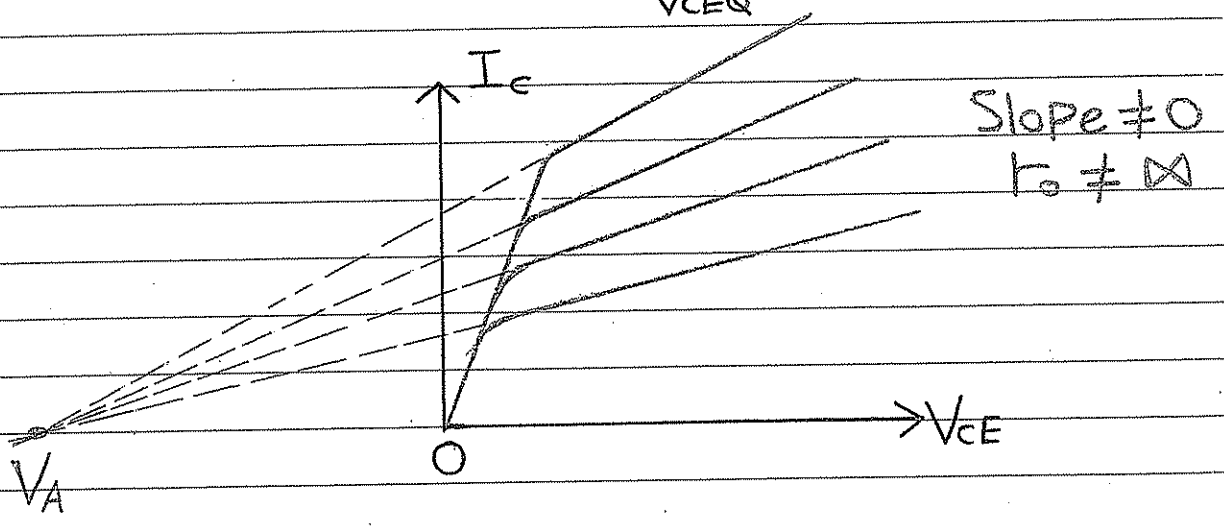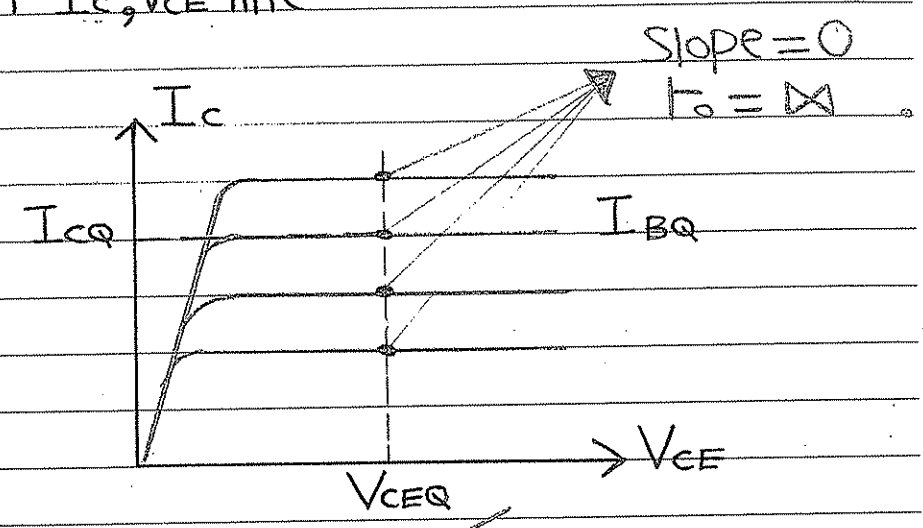$r_o = \frac{1}{\text{Slope of } I_c, V_{CE} \text{ line}}$



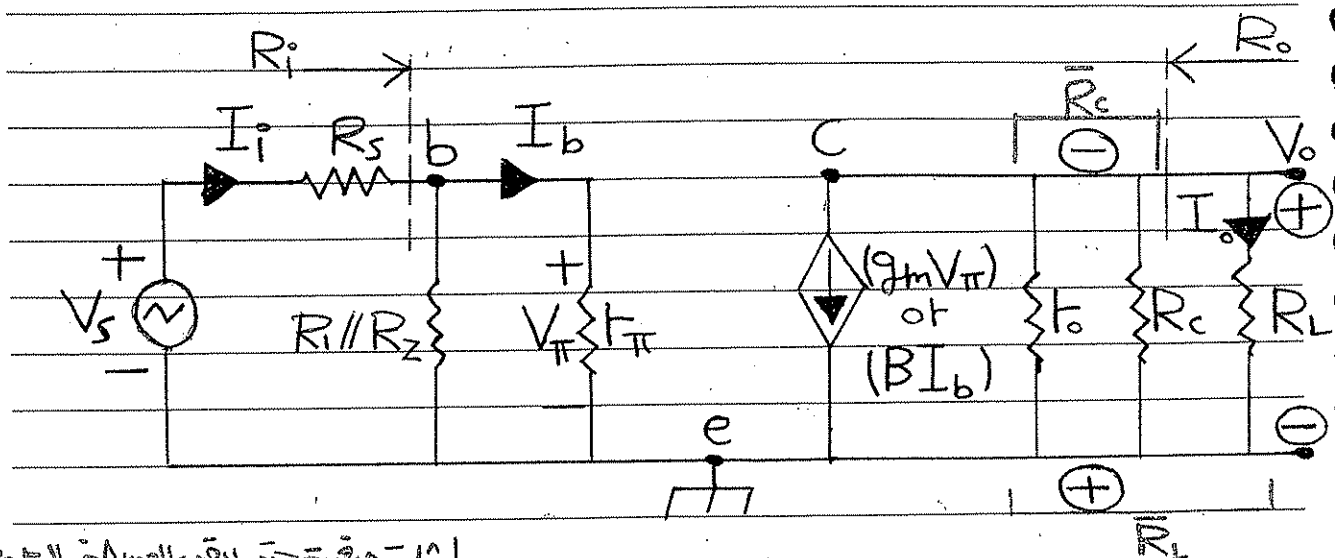


إشارة صغيرة حتى يبقى الـ Amplifier linear.

Small-Signal AC equivalent CCT. for the Amplifier.

$$1) A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{\pi}} * \frac{V_{\pi}}{V_s}$$

$$V_o = -g_m V_{\pi} R_L \rightarrow \frac{V_o}{V_{\pi}} = -g_m R_L$$

$$R_L = r_o // R_c // R_L$$

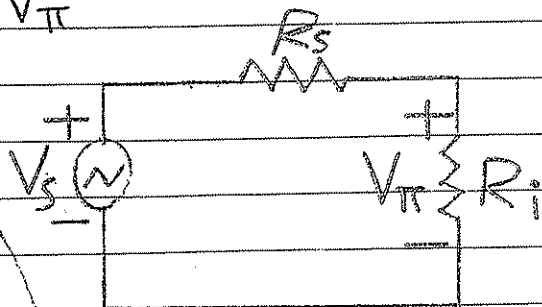

$$V_{\pi} = V_s \frac{R_i}{R_s + R_i}$$

$$V_o = -g_m V_s \cdot R_i \frac{R_L}{R_s + R_i}$$

$$\frac{V_o}{V_s} = A_v = -g_m R_L \frac{R_i}{R_i + R_s}$$

→ means 180° phase shift

between V_s and V_o .

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.67 \text{ mA}}{26 \text{ mV}} = 64 \text{ mA/V}$$

$$R_L = r_o \parallel R_c \parallel R_L$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{160 \text{ V}}{1.67 \text{ mA}} \approx 95 \text{ k}\Omega$$

$$R_L = 95 \parallel 3 \parallel 6 = 1.98 \text{ k}\Omega$$

$$R_i = r_{\pi} \parallel R_{Th}$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{50 \cdot 26}{1.67 \text{ mA}} = 780 \Omega$$

$$A_v = -64 * 1.98 * 0.78$$

$$= -126 * 0.78 = -98.3 = \frac{V_o}{V_s}$$

$$V_o = -98.3 V_s$$

! انحصار أن V_s تكبيره بـ 98.3 وانقلابه 180° .

$$2) A_I = \frac{I_o}{I_i} = \frac{I_o}{I_b} * \frac{I_b}{I_i}$$

$$I_o = -\beta I_b \frac{R_c}{R_c + R_L} \rightarrow \frac{I_o}{I_b} = -\frac{\beta R_c}{R_c + R_L}$$

$$\bar{R}_c = r_o \parallel R_c \rightarrow R_c = 2.9 \text{ k}\Omega$$

$$I_b = I_i * \frac{R_{Th}}{R_{Th} + r_{\pi}} \rightarrow \frac{I_b}{I_i} = \frac{R_{Th}}{R_{Th} + r_{\pi}}$$

$$\therefore A_I = \frac{-\beta R_c}{R_c + R_L} \cdot \frac{R_{Th}}{R_{Th} + r_{\pi}}$$

$$= \frac{-50 * 2.9}{2.9 + 6} \cdot \frac{9}{9 + 780}$$

$$= \frac{-1305}{13728.6} = -0.09 \text{ A}$$

(A_I) and (A_v) relation :

$$A_I = \frac{I_o}{I_i} = \frac{\frac{V_o}{R_L}}{\frac{V_s}{R_s + R_i}} = \frac{V_o}{V_s} * \frac{R_s + R_i}{R_L}$$


$A_I = A_v * \frac{R_s + R_i}{R_L}$	#
-------------------------------------	---

$$A_v = \frac{V_o}{V_i} = \frac{I_o * R_L}{I_i (R_s + R_i)}$$

$A_v = A_I * \frac{R_L}{R_s + R_i}$	#
-------------------------------------	---

ii C-E with R_E :

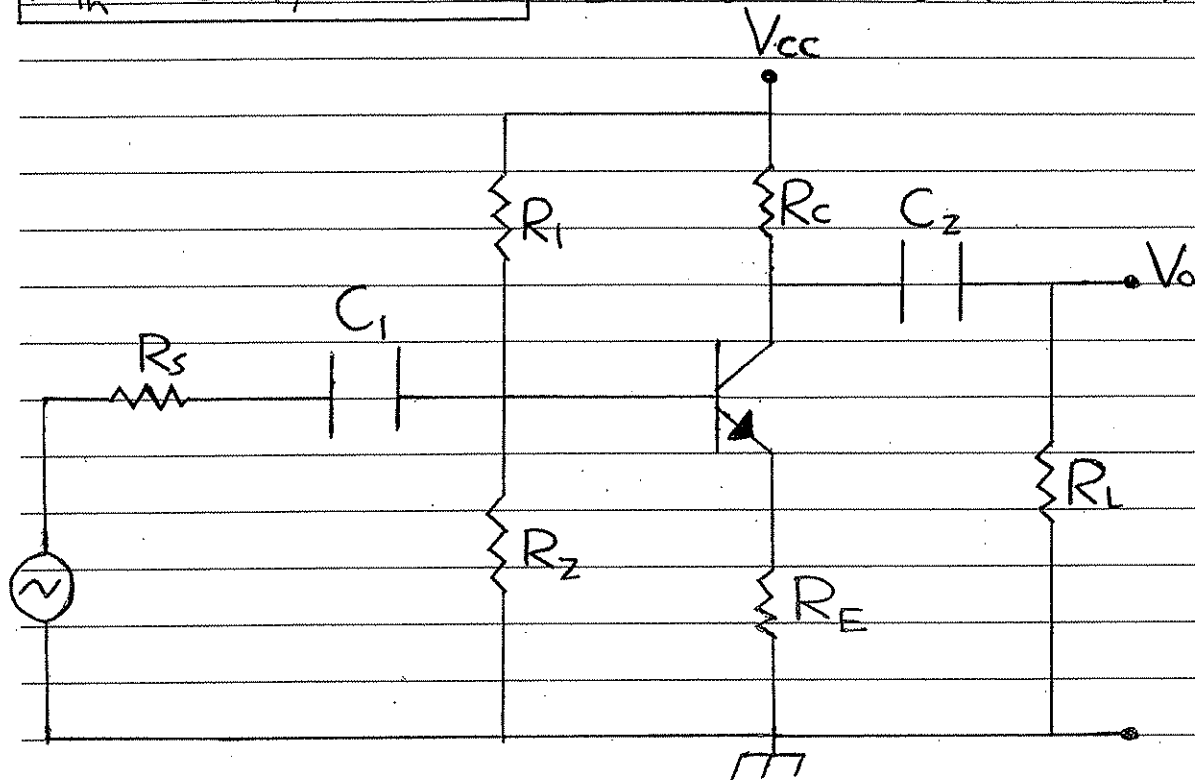$R_{Th} = 0.1(\beta + 1)R_E$ Bias Stable Condition.




DC Analysis :

The advantages of R_E is stabilize the Q-Point against β -Variation.

β etc ~~not~~ Q-pt

All Caps. are Open Circuit :

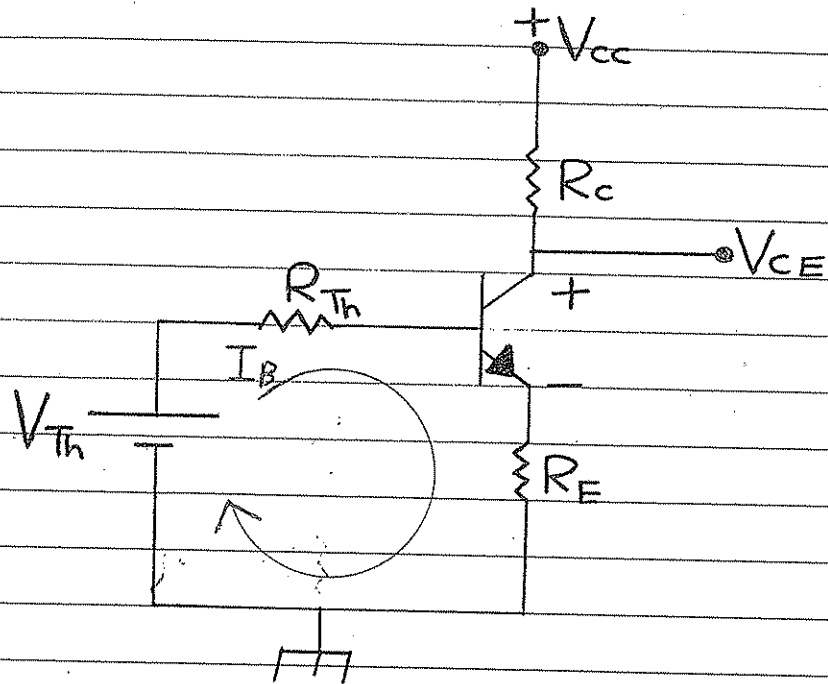

$$R_{Th} = R_1 // R_2 \quad ; \quad V_{Th} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

$$-V_{Th} + I_B R_{Th} + V_{BE} + I_B (\beta + 1) R_E = 0$$

$$\# I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}$$




$$\# I_C = \beta I_B$$

$$\# V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

#.

AC Analysis:

All Caps. and DC Sources are Short CCT.

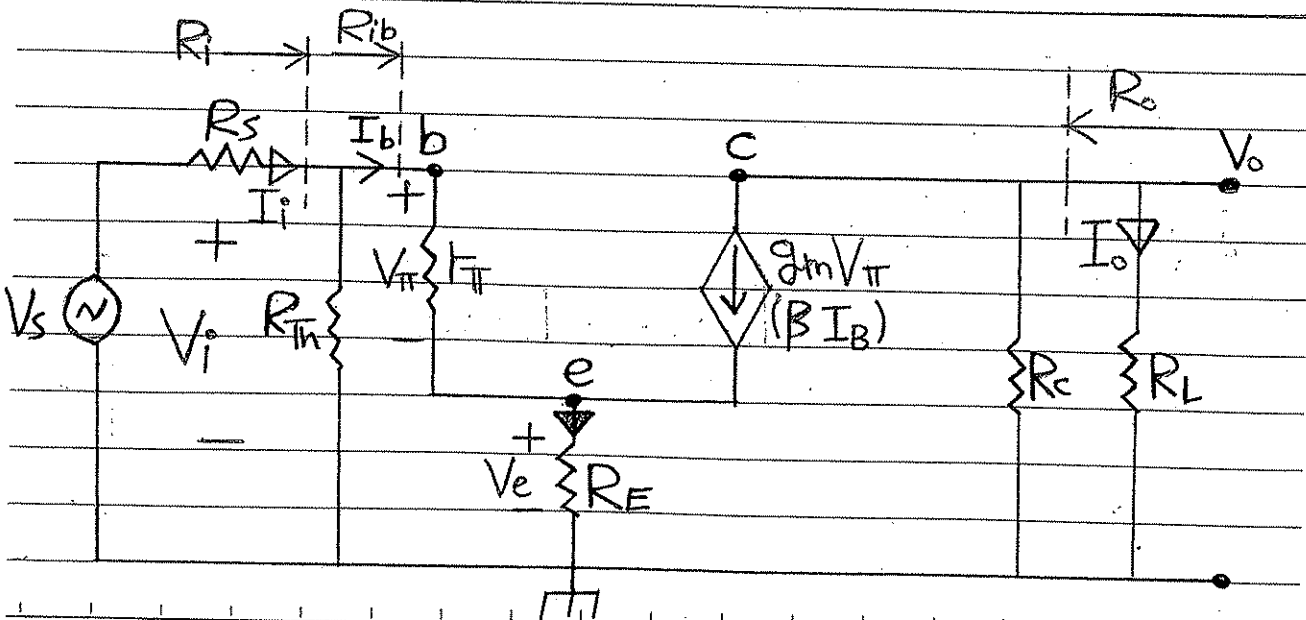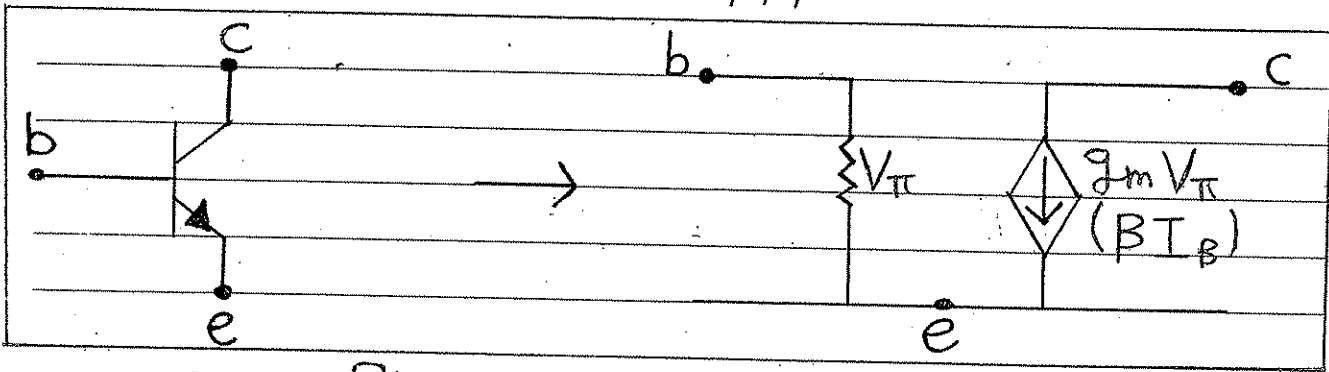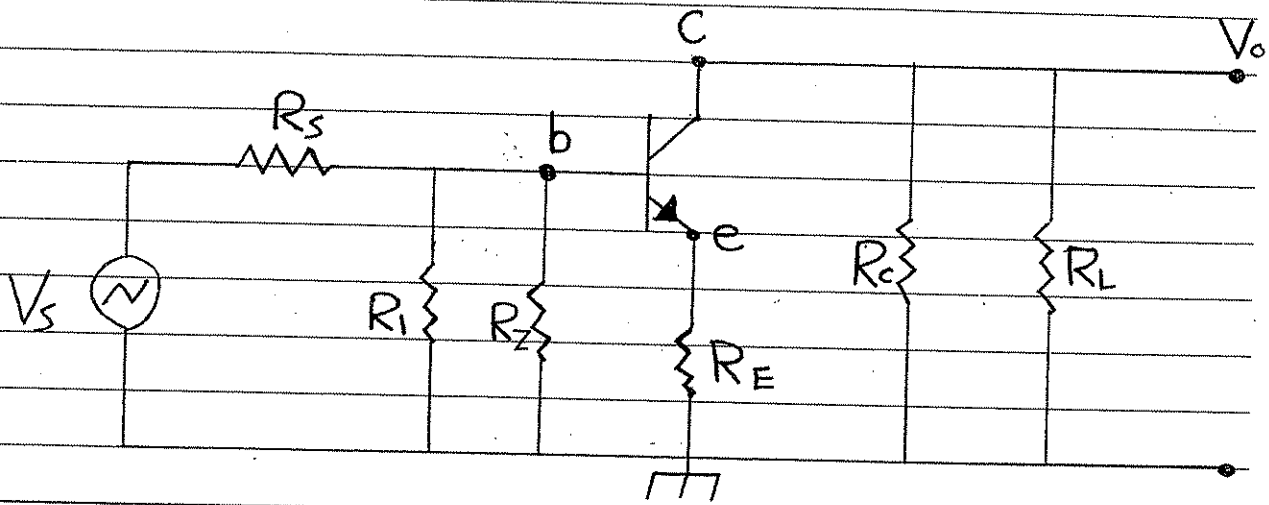

[S.S A.C. Fant. CCT.]

$$A_v = \frac{V_o}{V_s} = \frac{V_o}{V_i} * \frac{V_i}{V_s}$$

$$V_i = V_{\pi} + V_e = I_b \cdot r_{\pi} + I_e \cdot R_E$$

$$I_e = (\beta + 1) I_b$$


$$V_i = I_b (r_{\pi} + (\beta + 1) R_E)$$

$$V_o = -\beta I_b (R_c \parallel R_L)$$

$$\frac{V_o}{V_i} = \frac{-\beta I_b (R_c \parallel R_L)}{I_b (r_{\pi} + (\beta + 1) R_E)}$$

$$\frac{V_i}{V_s} = \frac{R_i}{R_i + R_s}$$
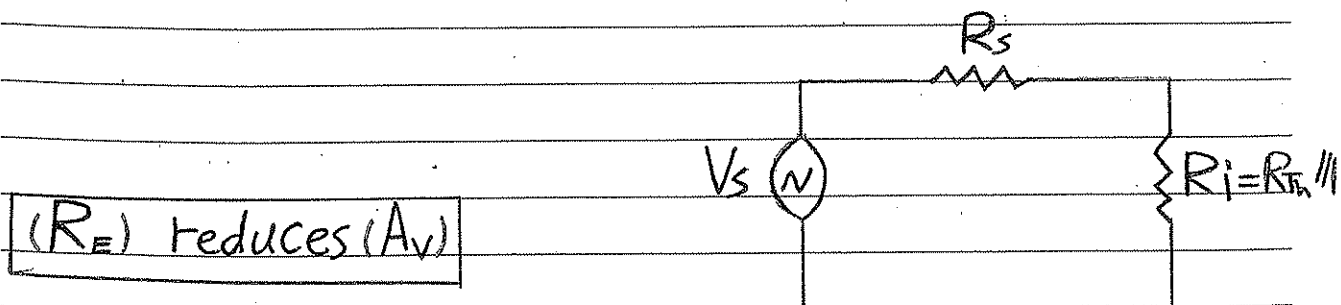
$$\frac{V_o}{V_s} = A_v = \frac{-\beta (R_c \parallel R_L)}{r_{\pi} + (\beta + 1) R_E} \cdot \frac{R_i}{R_i + R_s}$$



$$R_i = R_{Th} // R_{ib}$$

$$\# R_{ib} = \frac{V_i}{I_b} = \frac{I_b r_{\pi} + (\beta + 1) I_b \cdot R_E}{I_b}$$

$$\therefore R_{ib} = r_{\pi} + (\beta + 1) R_E$$

(R_E) increases (R_{ib})

$$A_I = \frac{I_o}{I_i} = \frac{\frac{V_o}{R_L}}{\frac{V_i}{R_i}} = \frac{V_o}{R_L} \cdot \frac{R_i}{V_i}$$

$$= \frac{V_o}{V_i} * \frac{R_i + R_s}{R_L}$$

$$= A_v \frac{R_i + R_s}{R_L}$$

(R_E) reduces (A_I)


Consider A_v expression :-

If $[(\beta+1)R_E \gg r_{\pi}]$ and $[\beta \gg 1]$

$$A_v \approx -\frac{(R_C \parallel R_L)}{R_E} \cdot \frac{R_i}{R_i + R_S}$$


i.e. (R_E) stabilize (A_v) against $(\beta\text{-Variation})$

iii] C-E with bypass Cap. (C_E) :-

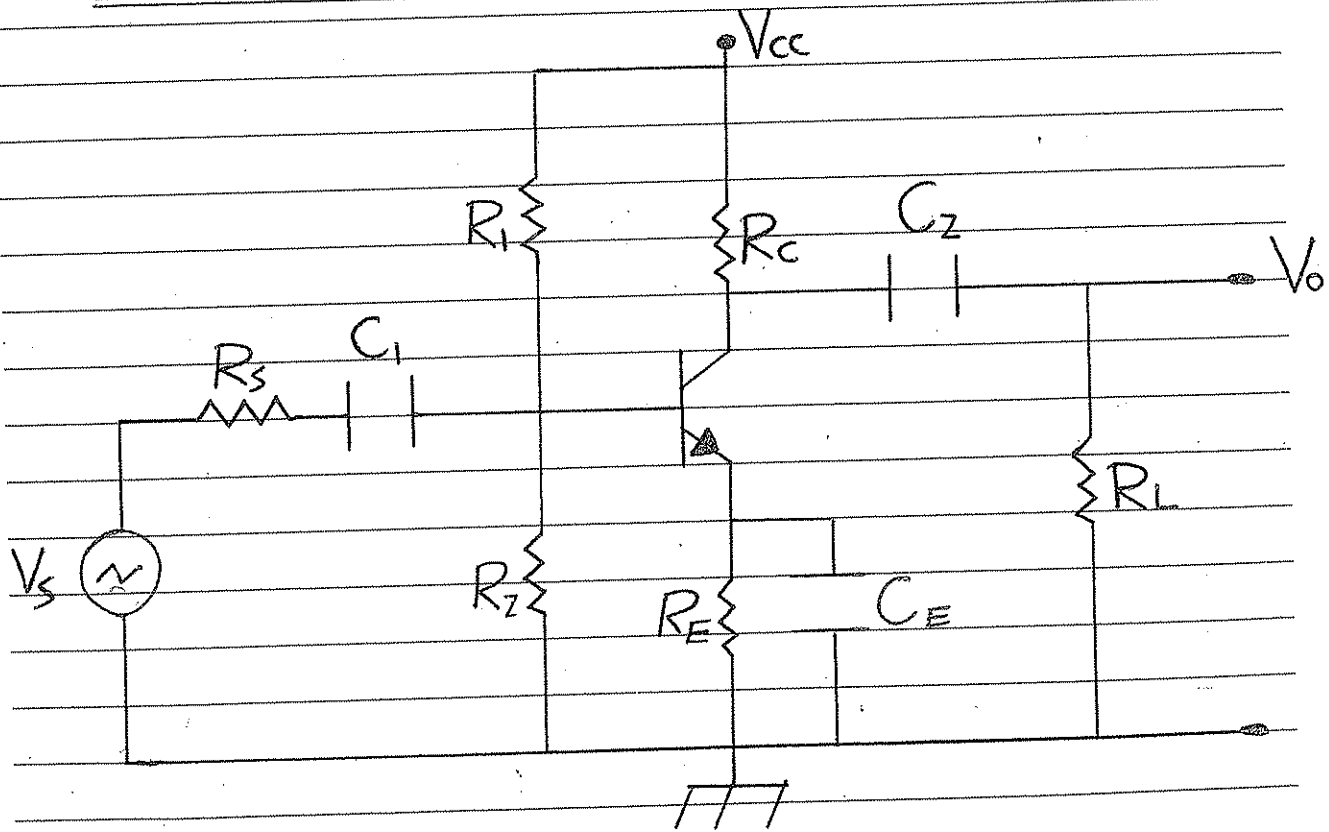

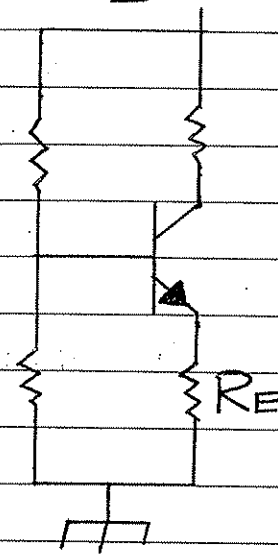
1) For DC Analysis :-

[C_E is Open CCT., and the CCT. is analysis as CE with R_E].



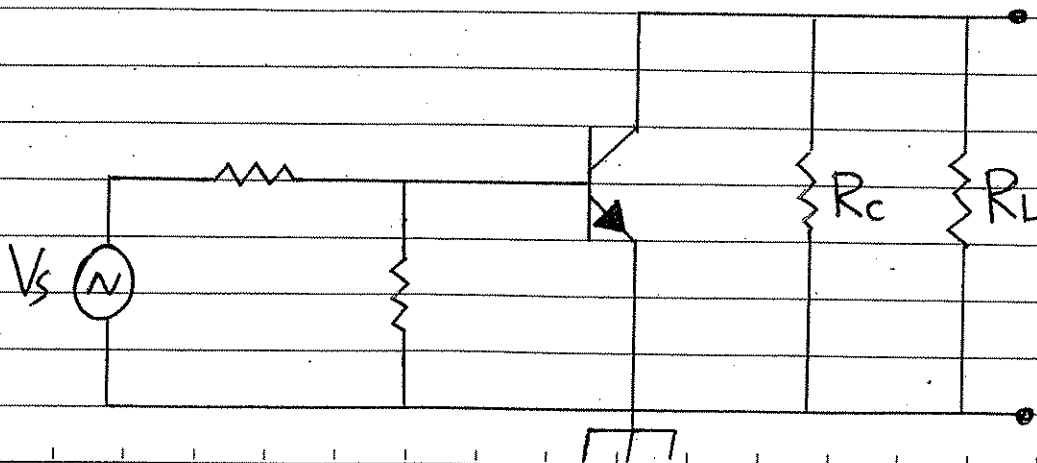
2) For AC Analysis :-

[C_E is Short CCT., and the CCT. work as Basic CE Amp.].



$$A_v = -\beta(R_c \parallel R_L) \cdot \frac{R_i}{V_{\pi} + (\beta+1)R_{E1}} \cdot \frac{R_i}{R_i + R_s}$$
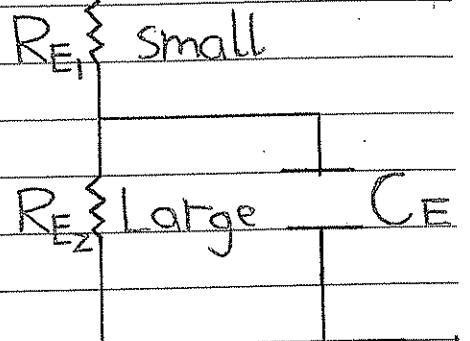
$$\approx -\frac{(R_c \parallel R_L) \cdot R_i}{R_{E1}} \cdot \frac{R_i}{R_i + R_s}$$



☘ To gain all advantages of R_E and minimize disadvantages; R_E is made of two parts, R_{E1} (Small), R_{E2} (Large), then bypass Large R_E with C_E . #

$$\text{AC Slope} = \frac{-1}{(R_c \parallel R_L) + R_{E1}}$$


$$\text{DC Slope} = \frac{-1}{R_c + R_{E1} + R_{E2}}$$

2] Common - Collector Amp. [Emitter-follower]


#C → Common terminal.

#Input to base.


#Output from Emitter.

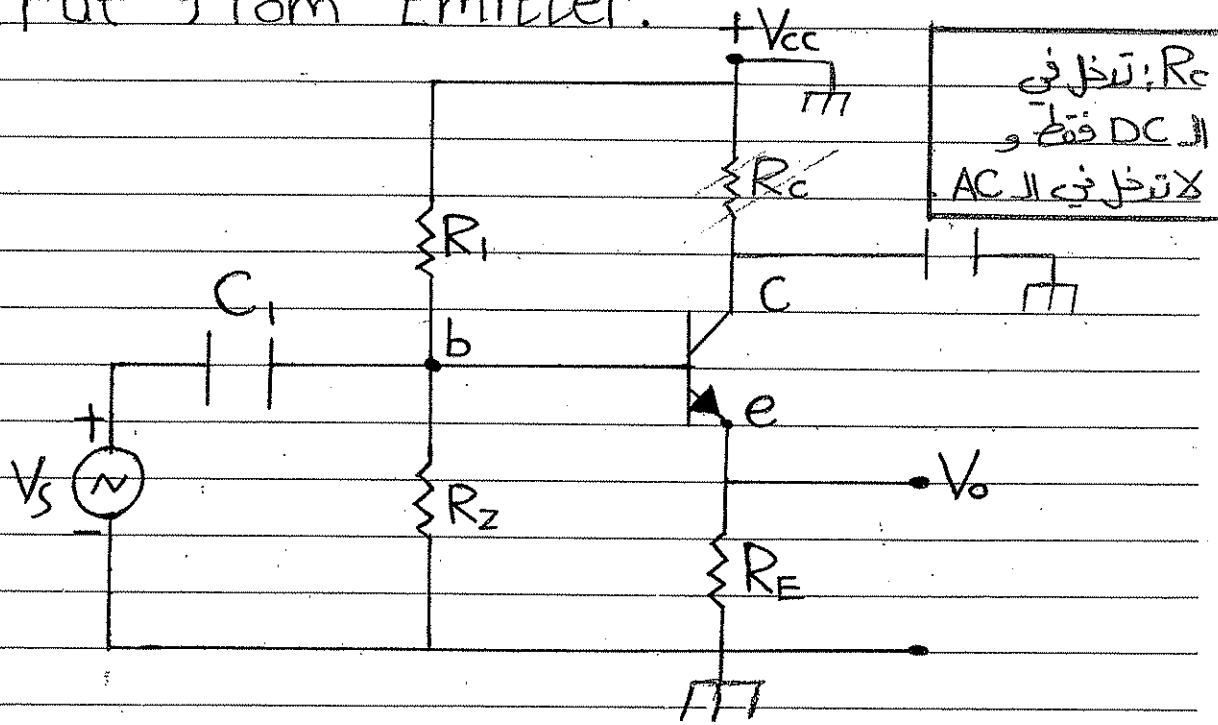

*For AC : [C is at ground].

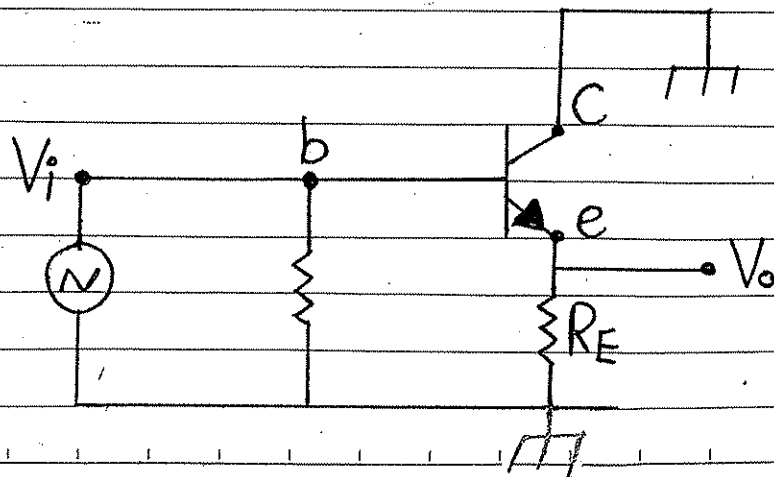

1) For D.C Analysis :-

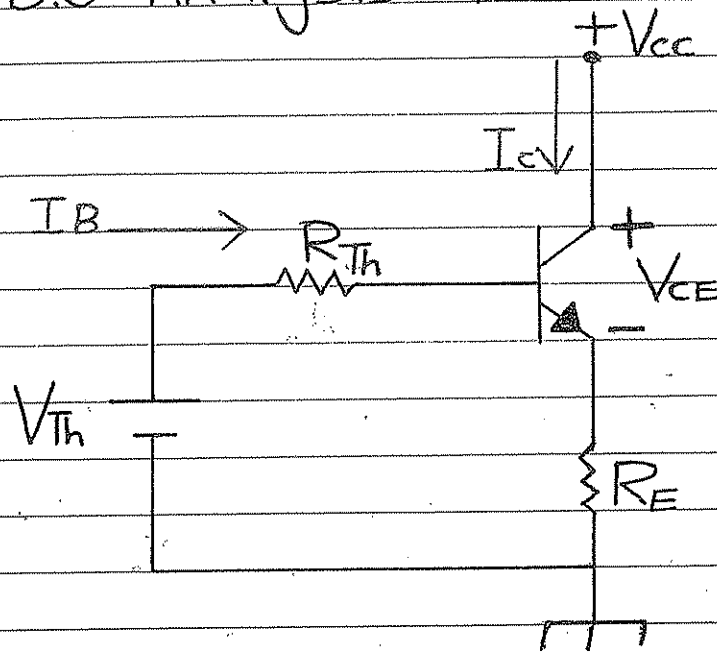



$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_E R_E$$




2) For A.C Analysis :-

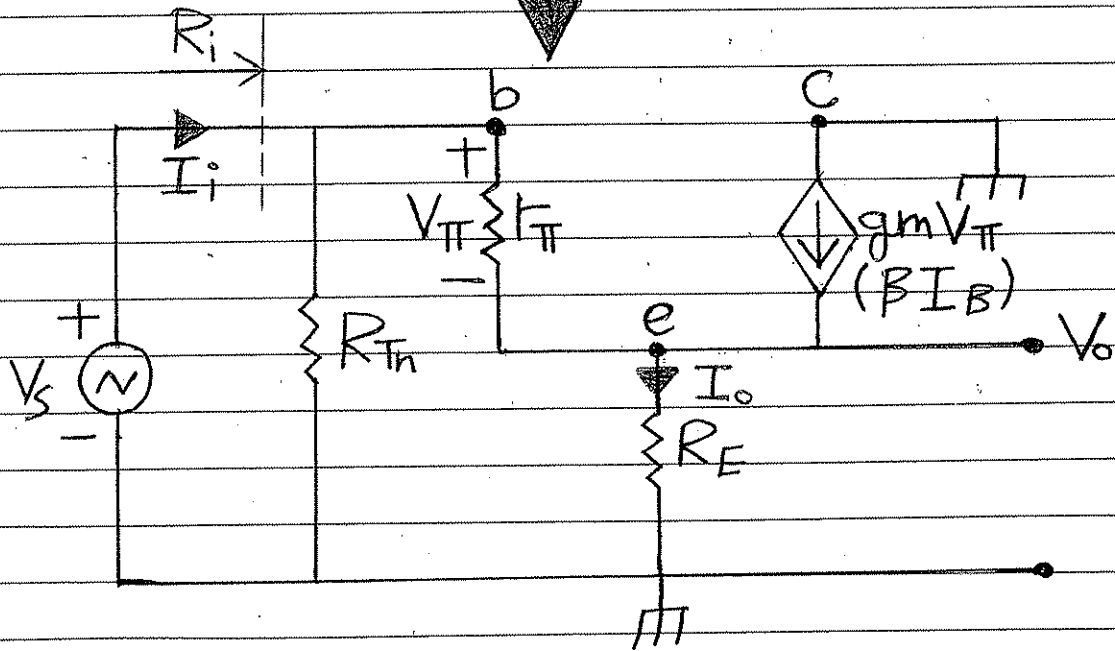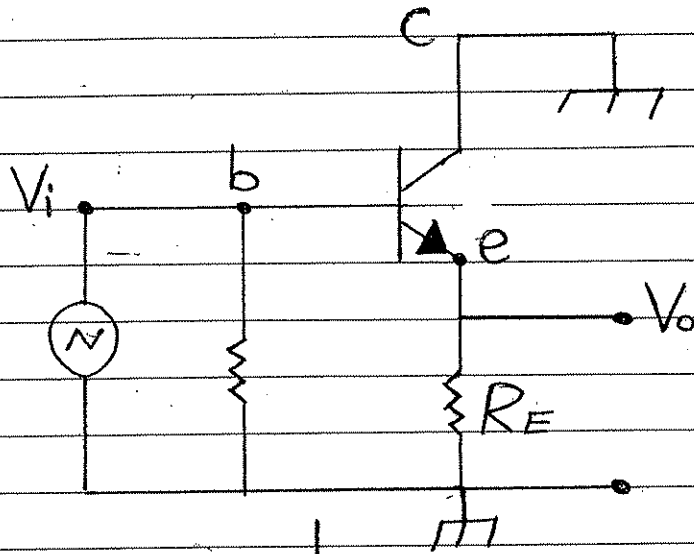

* [S.S A.C Eqnt. CCE]



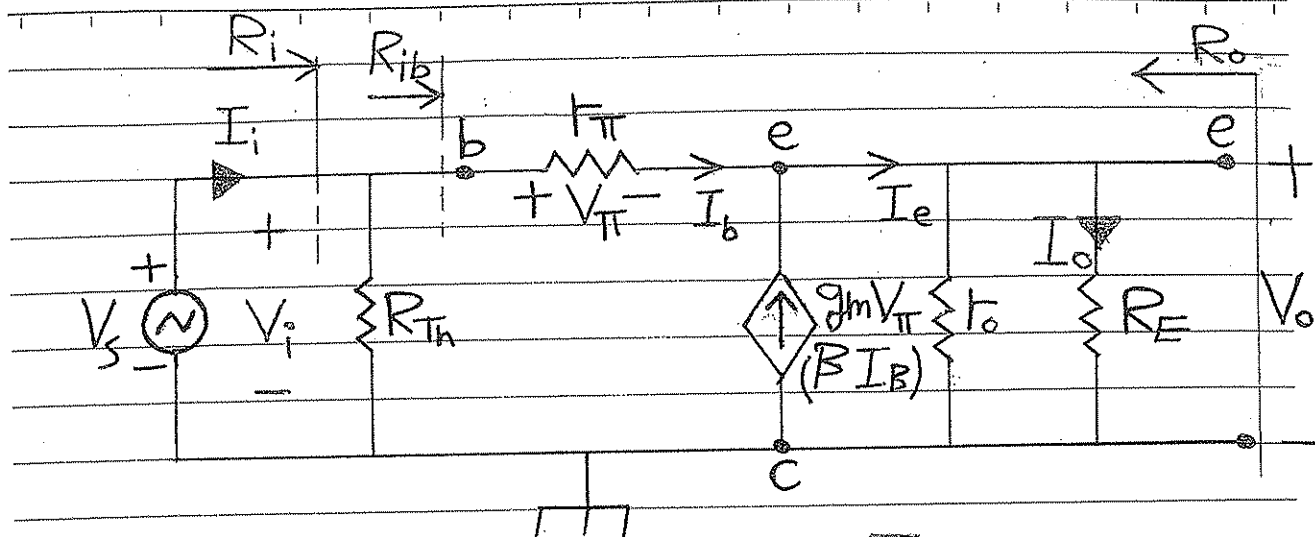

[S.S A.C Eqnt. CCT.]

$$A_v = \frac{V_o}{V_s}$$

$$V_o = I_e (r_o \parallel R_E)$$

$$= (\beta + 1) I_b (r_o \parallel R_E) \quad \#$$

$$-V_s + V_{\pi} + V_o = 0$$

$$V_s = I_b \cdot r_{\pi} + (\beta + 1) I_b (r_o \parallel R_E) \quad \#$$

$$A_v = \frac{(\beta + 1) I_b (r_o \parallel R_E)}{I_b r_{\pi} + (\beta + 1) I_b (r_o \parallel R_E)}$$

$$A_v = \frac{(\beta + 1)(r_o \parallel R_E)}{r_{\pi} + (\beta + 1)(r_o \parallel R_E)} \quad A_v < 1, V_o < V_s, \phi = 0$$

If $[(\beta+1)(r_o \parallel R_E) \gg r_{\pi}]$; then:

$$A_v = \frac{V_o}{V_s} \approx 1$$

$$V_o \approx V_s$$

* It's called Emitter-Followers because V_o follow $V_i(V_s)$ in magnitude and sign.

$$R_i = R_{Th} \parallel R_{ib}$$

$$\rightarrow R_{ib} = \frac{V_i}{I_b} = \frac{V_{\pi} + V_o}{I_b}$$

$$= \cancel{I_b} \cdot r_{\pi} + (\beta+1) \cancel{I_b} (r_o \parallel R_E)$$

$$R_{ib} = r_{\pi} + (\beta+1)(r_o \parallel R_E) \cancel{I_b}^{\cancel{I_b}}$$


$R_i \rightarrow$ high

$$A_I = \frac{I_o}{I_i} = \frac{I_o}{I_b} * \frac{I_b}{I_i}$$

$$I_o = \frac{(\beta+1) I_b r_o}{r_o + R_E}$$

$$\frac{I_o}{I_b} = \frac{(\beta+1) r_o}{r_o + R_E}$$

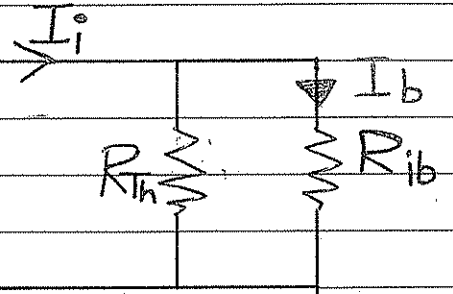
$$\frac{I_b}{I_i} = \frac{R_{Th}}{R_{Th} + R_i}$$



$$A_I = \frac{(\beta+1) r_o}{r_o + R_E} \cdot \frac{R_{Th}}{R_{Th} + R_{ib}} \quad A_I > 1$$

$$(A_I)_{max} \approx \beta + 1$$

$$R_o = \frac{V_x}{I_x} \quad | \quad V_s = 0$$

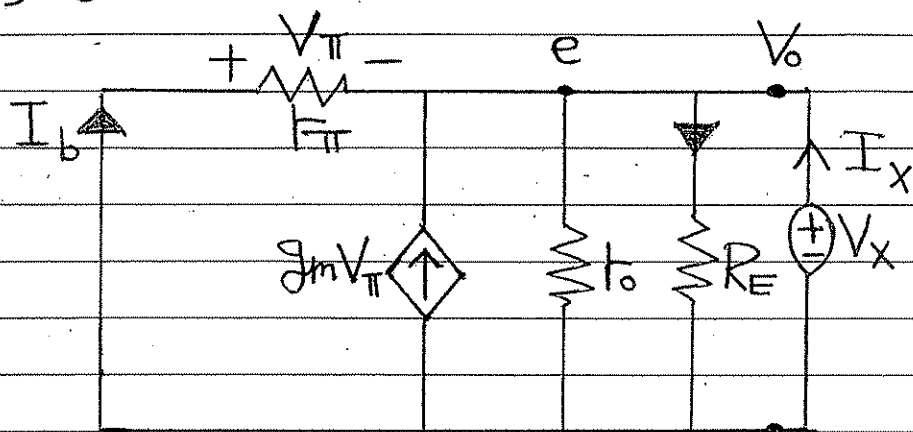

KCL at node (e) :

$$I_x + g_m V_{\pi} = \frac{V_x}{R_E} + \frac{V_x}{r_o} + \frac{V_x}{r_{\pi}}$$

But : $V_x = -V_{\pi} \rightarrow V_{\pi} = -V_x$

$$\therefore I_x = V_x \left(g_m + \frac{1}{r_{\pi}} + \frac{1}{r_o} + \frac{1}{R_E} \right)$$

$$\frac{I_x}{V_x} = \frac{1}{R_o} = g_m r_{\pi} + 1 + \frac{1}{r_o} + \frac{1}{R_E}$$

$$* g_m r_{\pi} = \frac{I_{CQ}}{V_T} \cdot \frac{\beta V_T}{I_{CQ}} = \beta$$

$$\frac{1}{R_o} = \frac{B+1}{r_{\pi}} + \frac{1}{r_o} + \frac{1}{R_E}$$

$$\Rightarrow R_o = \frac{r_{\pi} \parallel r_o \parallel R_E}{B+1}$$

$R_o \rightarrow \text{Low}$

$$A_v < 1$$

$$A_I > 1$$

R_i : high } for C.C Amp.

R_o : Low

$$\phi = 0^\circ$$

C.C is used to solve Loading Problem.



$$V_L = V_s \cdot \frac{R_L}{R_L + R_s}$$

$$= V_s \cdot \frac{10}{10 + 1000}$$

$$\approx 0.01 V_s$$


$$10 \sin \omega t \text{ (V)}$$
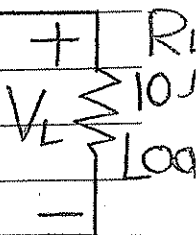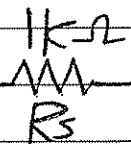
$$= \underline{\underline{0.1 \sin \omega t \text{ (V)}}}$$



[Sever Loading effect]

To Solve this problem :-

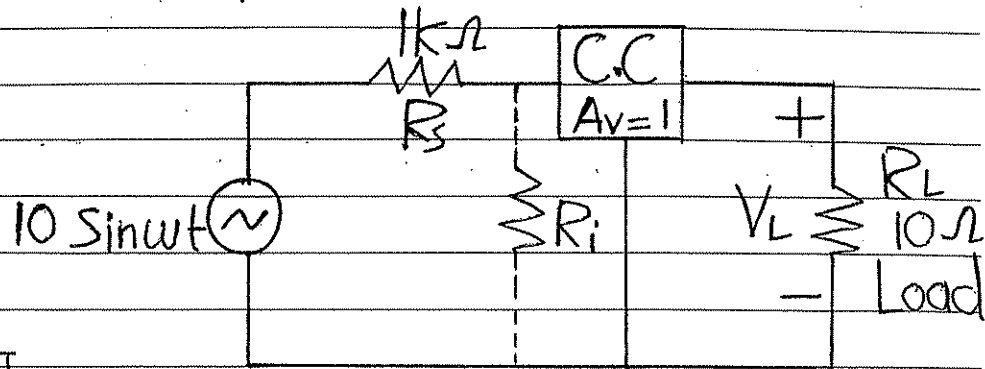


With C.C :-

$$V_x = V_s \frac{R_i}{R_i + R_s}$$

$$V_x \approx V_s ; V_L = V_x (A_v \approx 1)$$

$$\therefore V_L = V_s \text{ [NO Loading Effect]}$$

3] Common - Base Amp. :

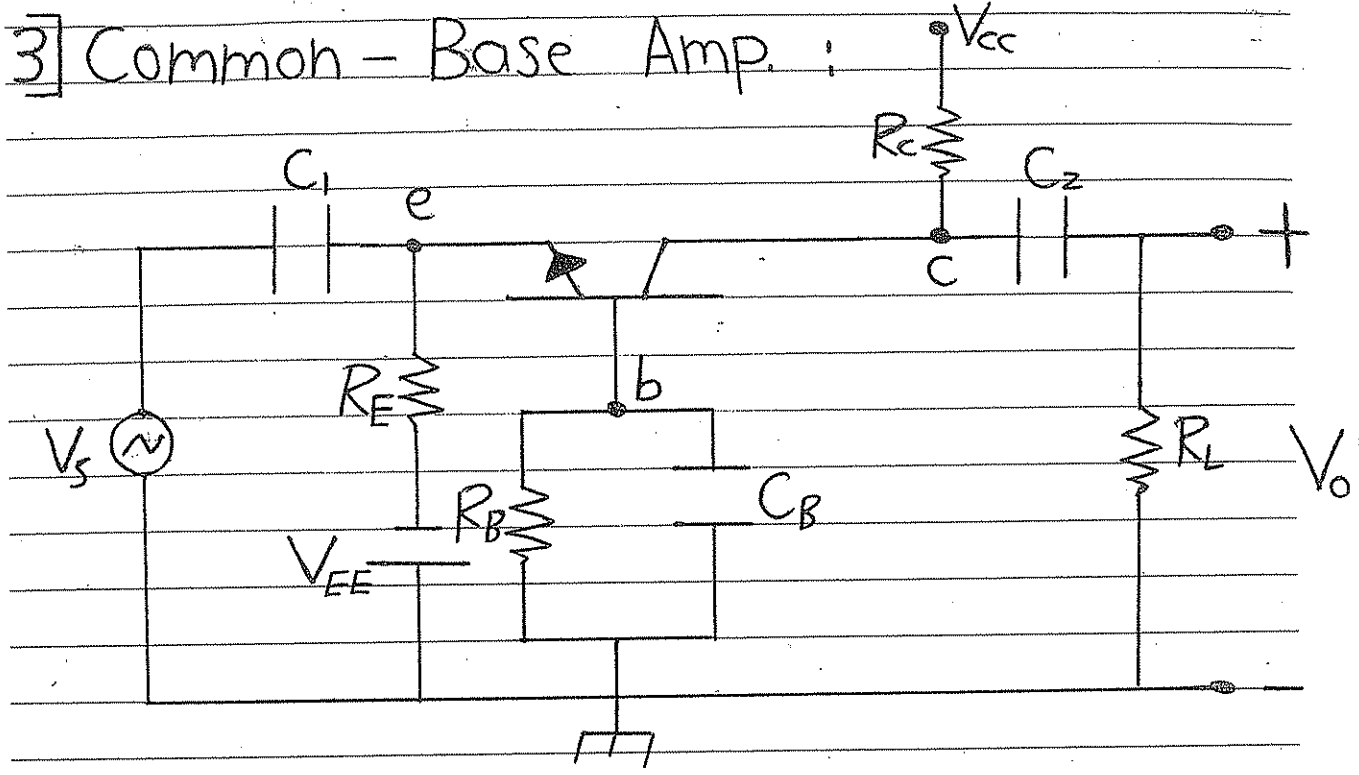


#Base → Common.


#Input to Emitter.

#Output from Collector.

For A.C : Base to ground.

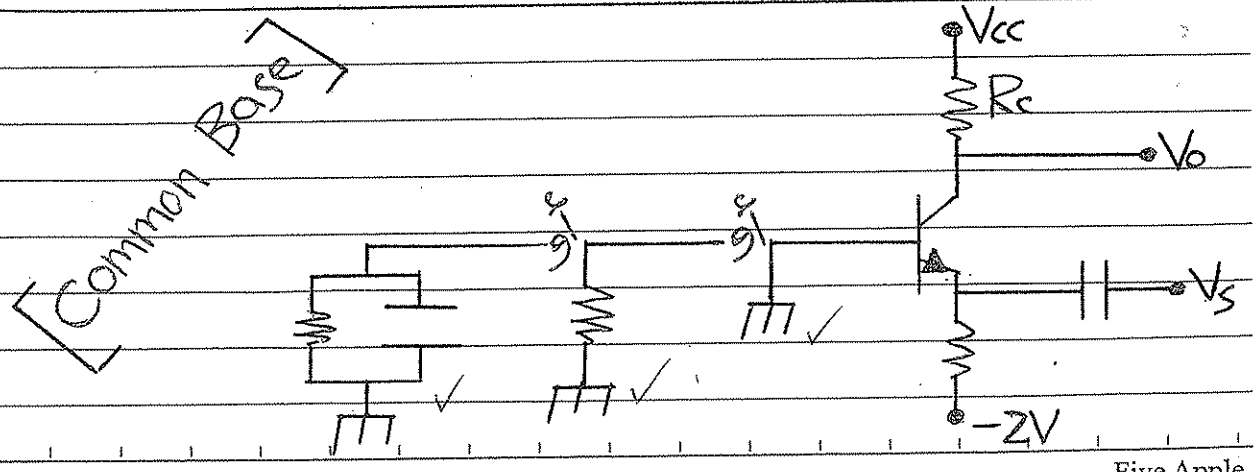

EXA.:-

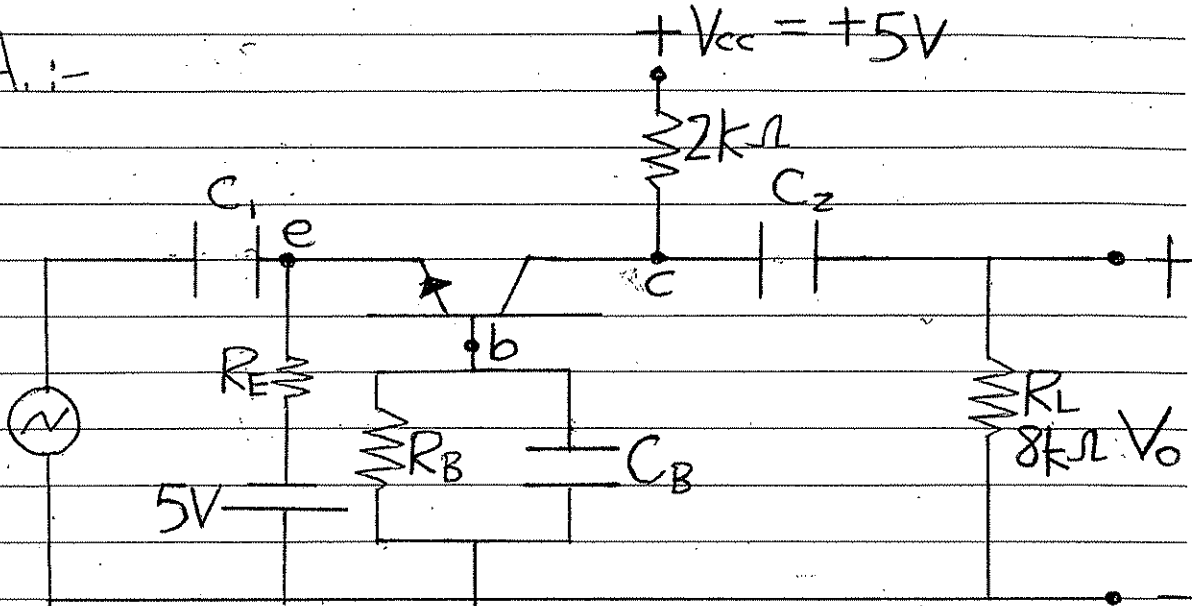


$\beta = 100$, $V_{BE} = 0.7$, $V_A = \infty$

1) Calculate R_B , R_E , Such that :

$I_{CQ} = 1\text{mA}$, $V_{CEQ} = 4\text{V}$

2) Draw S.S AC Eqnt. CCT. & find

A_v , A_I , R_i , R_o ?

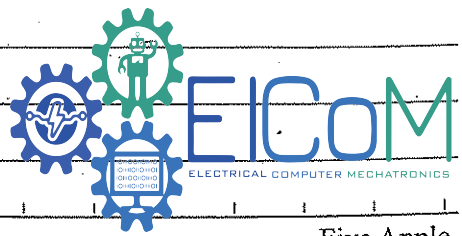



R_B :

$$I_B R_B + V_{BE} + I_E R_E - 5 = 0$$

$$R_B = \frac{5 - 0.7 - 1.01 \times 3.96}{1 \text{ mA} \times 100}$$

$$R_B = 30 \text{ k}\Omega$$

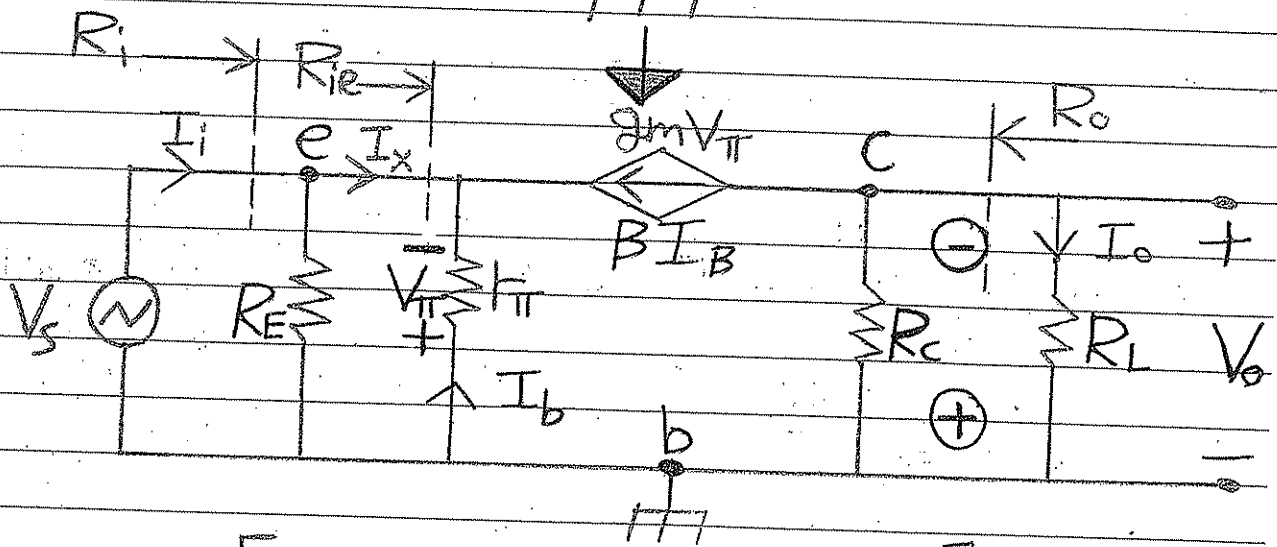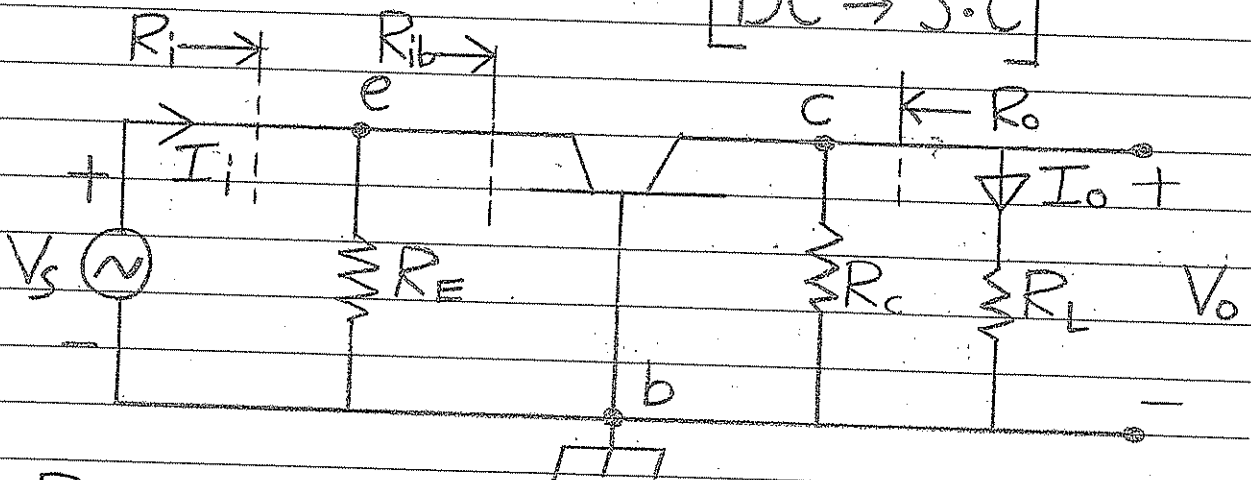2) For AC Analysis :- $[C \rightarrow S.C]$
 $[DC \rightarrow S.C]$



[S.S AC Eqnt. CCT.]

$$A_v = \frac{V_o}{V_s} = \frac{-g_m V_{\pi} (R_c \parallel R_L)}{-V_{\pi}}$$

$$A_v = g_m (R_c \parallel R_L) \quad A_v > 1, \quad \phi = 0^\circ$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} = 38.5 \text{ mA/V}$$

$$A_v = 38.5 (2 \parallel 8) \approx 61$$

$$R_o = \left. \frac{V_x}{I_x} \right|_{V_s=0}$$

When $V_s = 0 \rightarrow V_{\pi} = 0$

$g_m V_{\pi} = 0 \rightarrow$ Current source is Open.

$$R_o = R_c = 2 \text{ k}\Omega$$

$$R_i = R_E \parallel R_{ie}$$

$$R_{ie} = \frac{-V_{\pi}}{I_x} = \frac{-V_{\pi}}{-(\beta+1)I_b} = \frac{-I_b r_{\pi}}{-(\beta+1)I_b} = \frac{r_{\pi}}{\beta+1}$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{100 * 26 \text{ mV}}{1 \text{ mA}} = 2.6 \text{ k}\Omega$$

$$R_i = -3.96 \parallel \frac{2.6 \text{ k}}{101} \approx 25 \Omega$$

$$\begin{aligned}
 A_T &= \frac{I_o}{I_i} = \frac{\frac{V_o}{R_L}}{\frac{V_s}{R_i}} = V_o \cdot \frac{R_i}{V_s \cdot R_L} \\
 &= A_v \cdot \frac{R_i}{R_L} \\
 &= 61 \cdot \frac{25 \Omega}{8000} \\
 &= 0.19
 \end{aligned}$$

$$A_v > 1$$

$$A_T < 1$$

$$\phi = 0^\circ$$


R_i : Low.

R_o : moderate to high.

} for C.B. Amp.

Summary of - S.S. Amp :-

Amp.	A_v	A_I	R_i	R_o	phase
C.E (Basic)	> 1	> 1	moderate	moderate to high	180°
C.C	≤ 1	> 1	high	Low ($\sim \Omega$)	0°
C.B	> 1	≤ 1	Low ($\sim \Omega$)	moderate to high	0°

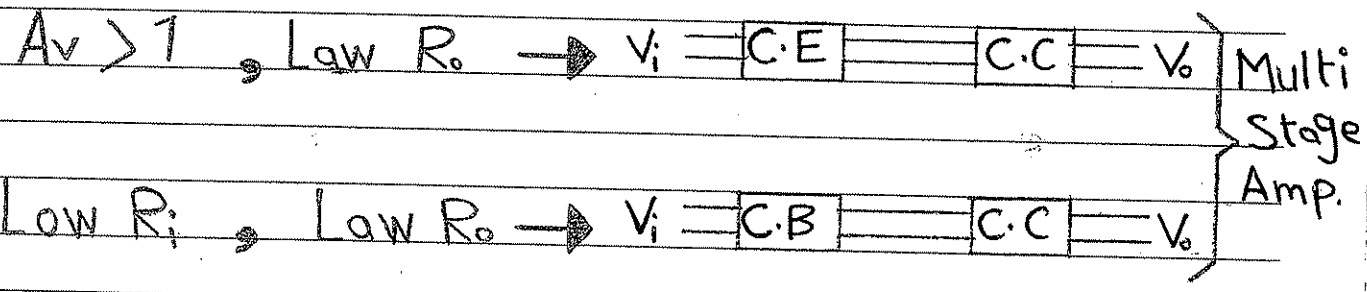


Multi Stage Amp.s :-


Amps contain more than single transistors (two at least), used to achieve certain specifications ($A_v > 1$, Low R_o) which can not be achieved used single-stage.

[M.S Amp.s]

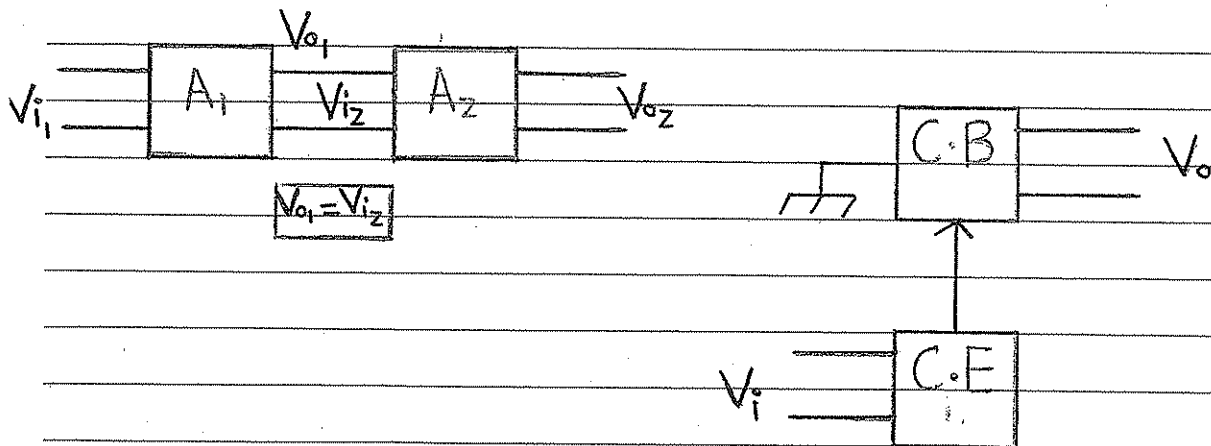
Cascade (Series connection):- # Cascode :-




Standard

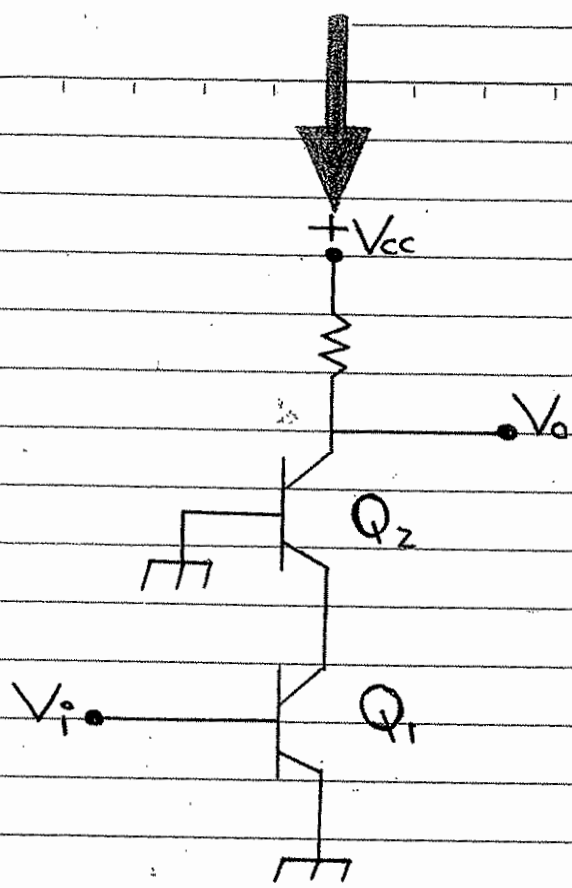

1] Cascade Amp.s :-

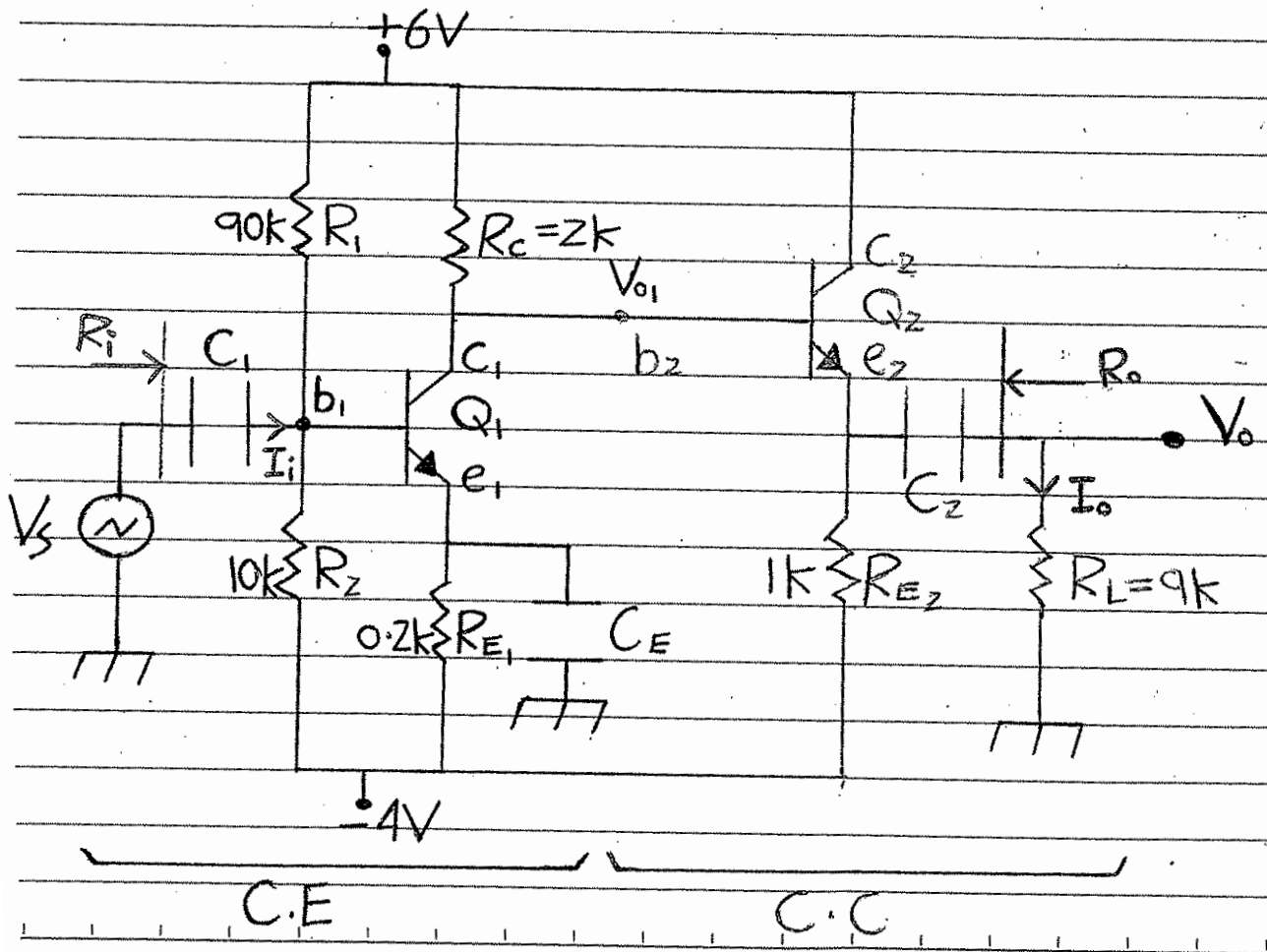

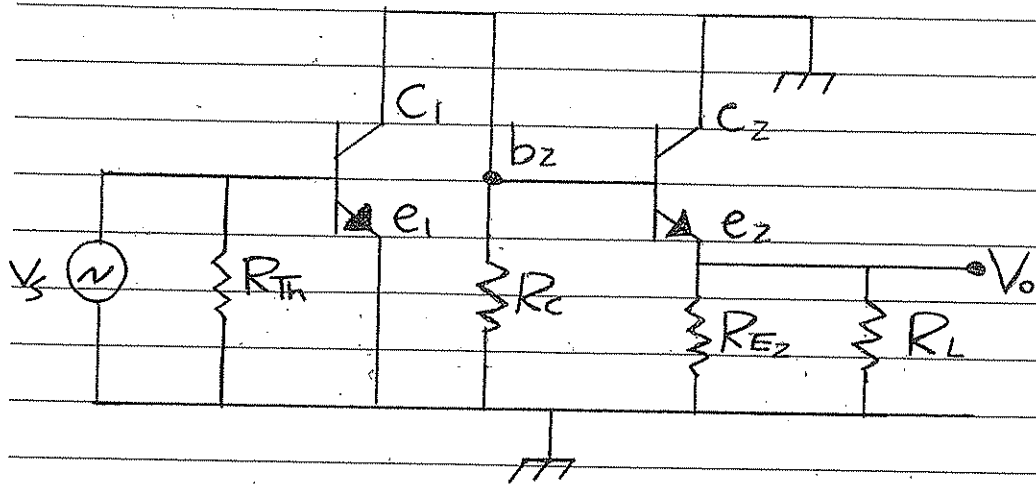

Q_1 and Q_2 are identical with $\beta_1 = \beta_2 = 150$

$$V_{BE1} = V_{BE2} = 0.7V, \quad V_{A1} = V_{A2} = \infty$$

1) Calculate $I_{CQ1}, V_{CEQ1}, I_{CQ2}, V_{CEQ2}$.


2) Draw S.S. A.C. Eqnt. CCT. and find:

R_i, R_o, A_v, A_I

R_i for Stage 1
 R_o for Stage 2

$A_{V1} = \frac{V_{o1}}{V_s}$
$A_{V2} = \frac{V_o}{V_{o1}}$

Sol:-

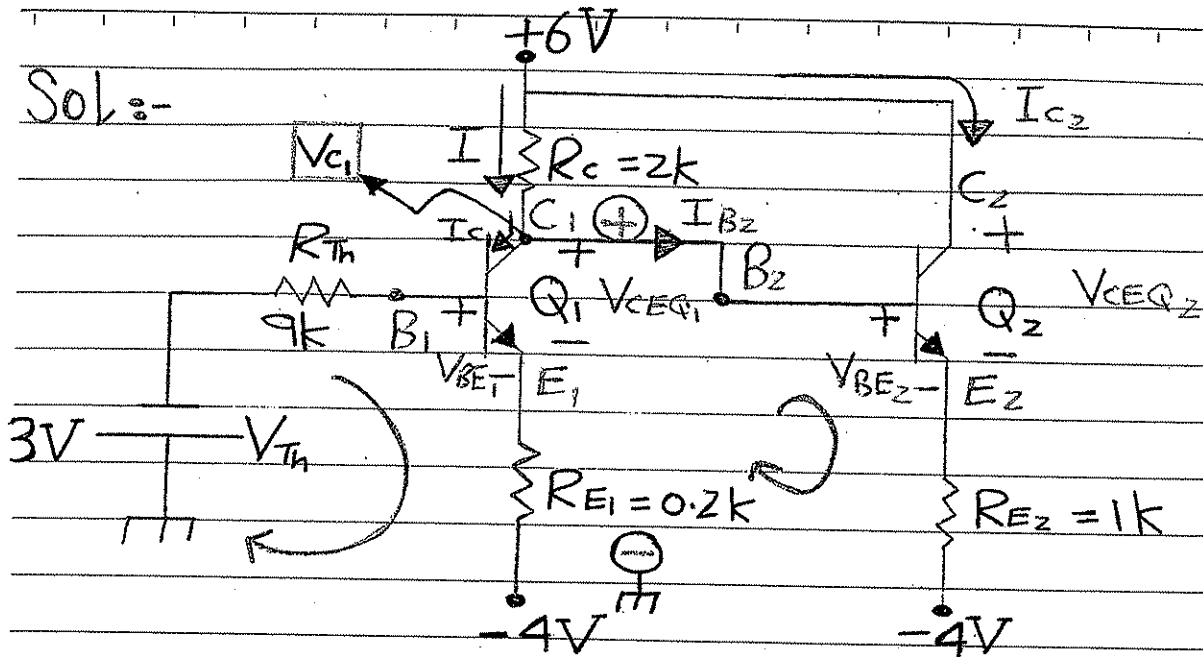

$$R_{Th} = 90 // 10 = 9k\Omega.$$

$$V_{Th} = \frac{6 \times 10}{100} + \frac{(-4) \times 90}{100} = -3V.$$

$$3 + R_{Th} I_{B1} + V_{BE1} + (B+1) I_{B1} R_{E1} - 4 = 0.$$

$$I_{B1} = \frac{(4-3-0.7)V}{R_{Th} + (B+1)R_{E1}} \checkmark \rightarrow I_{C1} = \beta I_{B1} \checkmark$$

$$\rightarrow I_{E1} = (B+1) I_{B1} \checkmark$$

$$-6 + I R_C + V_{CE1} + I_{E1} R_{E1} - 4 = 0$$

$$V_{CE1} = 10 - I_{E1} R_{E1} - I \cdot R_C$$

To find I : KCL at node C_1 :-

$$I = I_{C_1} + I_{B_2}$$

$$I = \frac{6 - V_{C_1}}{R_C}$$

$$I_{B_2} : -V_{C_1} + V_{BE_2} + (B+1)I_{B_2}R_{E_2} - 4 = 0$$

$$I_{B_2} = \frac{V_{C_1} + 4 - V_{BE_2}}{(B+1)R_{E_2}}$$

$$\Rightarrow \frac{6 - V_{C_1}}{2k} = I_{C_1} + \frac{V_{C_1} + 3.3}{151 * 1}$$

Solve for V_{C_1} ;

$$\Rightarrow I \checkmark, V_{CE_1} \checkmark$$



$$\Rightarrow I_{B_2} \rightarrow I_{C_2} \rightarrow I_{E_2} \rightarrow V_{CE_2} \checkmark$$

* Slope for stage 2:

$$DC \text{ II} \rightarrow -1$$

$$AC \text{ II} \rightarrow \frac{R_{E_2}}{R_{E_2} \parallel R_L} \cdot -1$$

For AC :-

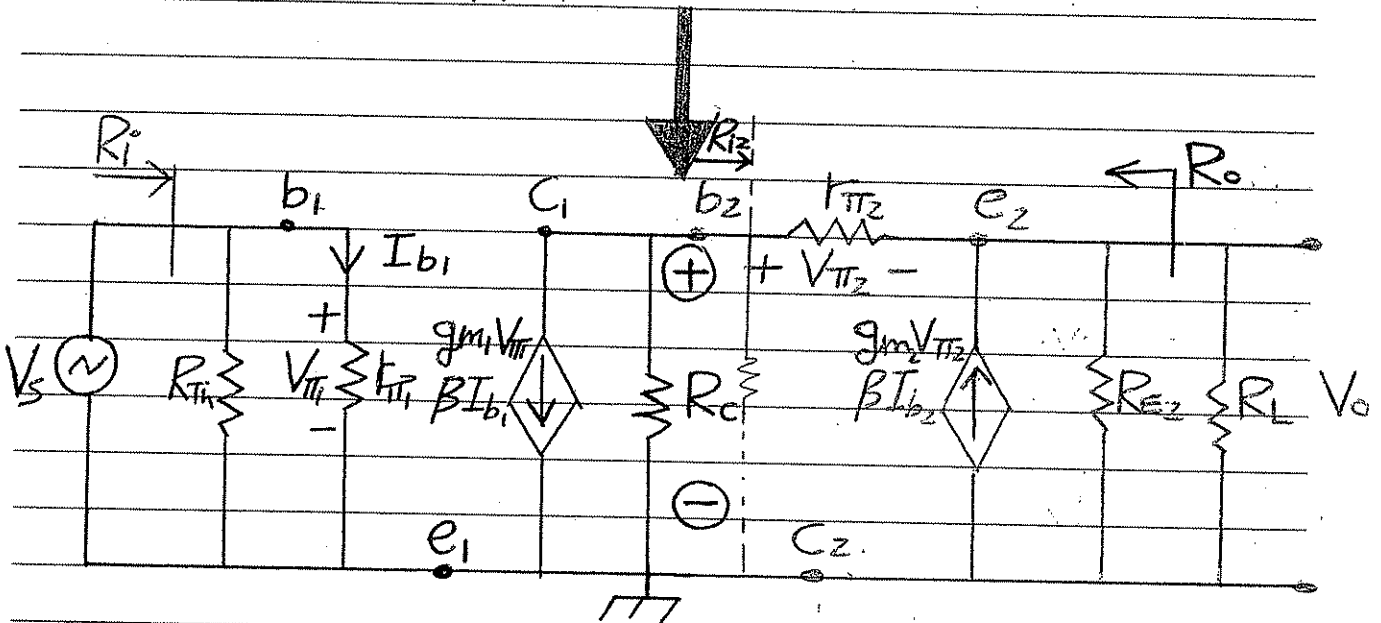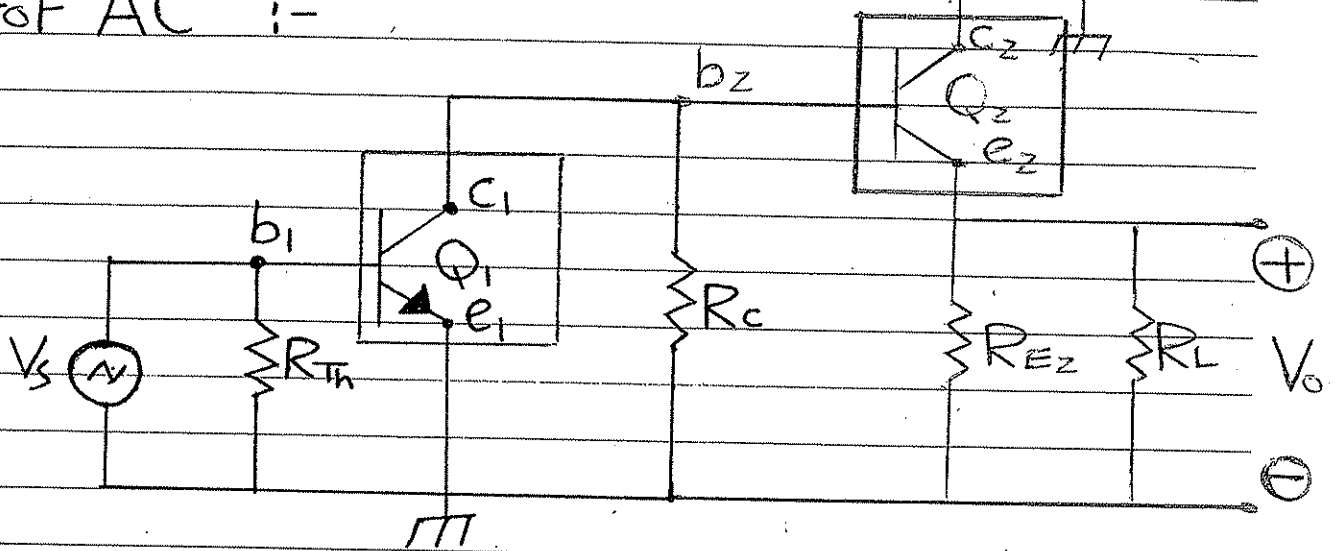

S.S.A.C Eqnt. Cct.

$$R_i = R_{i_1} = R_{Th} \parallel r_{\pi 1}$$

$$R_o = R_{o_2} = \frac{V_x}{I_x} \Big|_{V_s=0}$$

$$V_s = 0 \rightarrow V_{\pi_1} = 0 \rightarrow g_{m_1} V_{\pi_1} = 0 \text{ ; Open Ckt.}$$

$$R_o = \left(\frac{R_c + r_{\pi_2}}{\beta + 1} \right) \parallel R_{E_2}$$

* Stage 1
↑

$$R_{o_2} = \frac{r_{\pi_2}}{\beta + 1} \parallel R_{E_2}$$

$$\# A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{o_1}} * \frac{V_{o_1}}{V_s}$$

$$\frac{V_o}{V_{o_1}} = A_{v_2} = \frac{(B+1)(R_E \parallel R_L)}{r_{\pi_2} + (B+1)(R_E \parallel R_L)}$$

$$\frac{V_{o_1}}{V_s} = A_{v_1} = \frac{V_{o_1}}{V_{\pi_1}}$$

$$V_{o_1} = -g_{m_1} V_{\pi_1} (R_c \parallel R_{i_2})$$


$$\rightarrow \frac{V_{o_1}}{V_{\pi_1}} = -g_m (R_c \parallel R_{i_2})$$

$$R_{i_2} = R_{i_b} = r_{\pi_2} + (B+1)(R_E \parallel R_L)$$

$$\rightarrow A_v = \underbrace{-g_{m1}(R_c // R_{i2})}_{A_{v1}} \cdot \underbrace{\frac{(\beta+1)(R_{E2} // R_L)}{r_{\pi2} + (\beta+1)(R_{E2} // R_L)}}_{A_{v2}}$$


$$A_T = \frac{I_o}{I_i} = \frac{\frac{V_o}{R_L}}{\frac{V_s}{R_i}} = \frac{V_o}{V_s} * \frac{R_i}{R_L}$$


$$A_T = A_v \cdot \frac{R_i}{R_L}$$

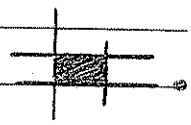

2/ Cascode Amp.s :-

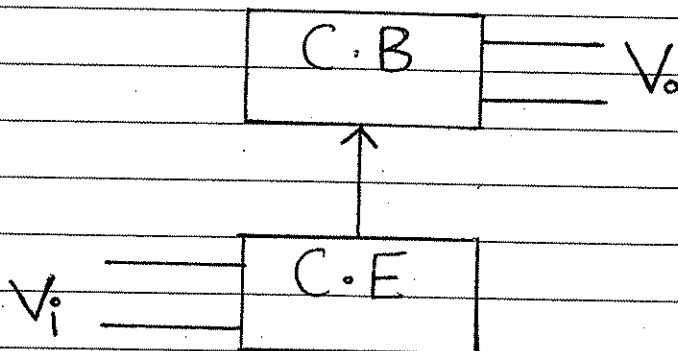Used For high-freq. Application (as a wideband Amp.).



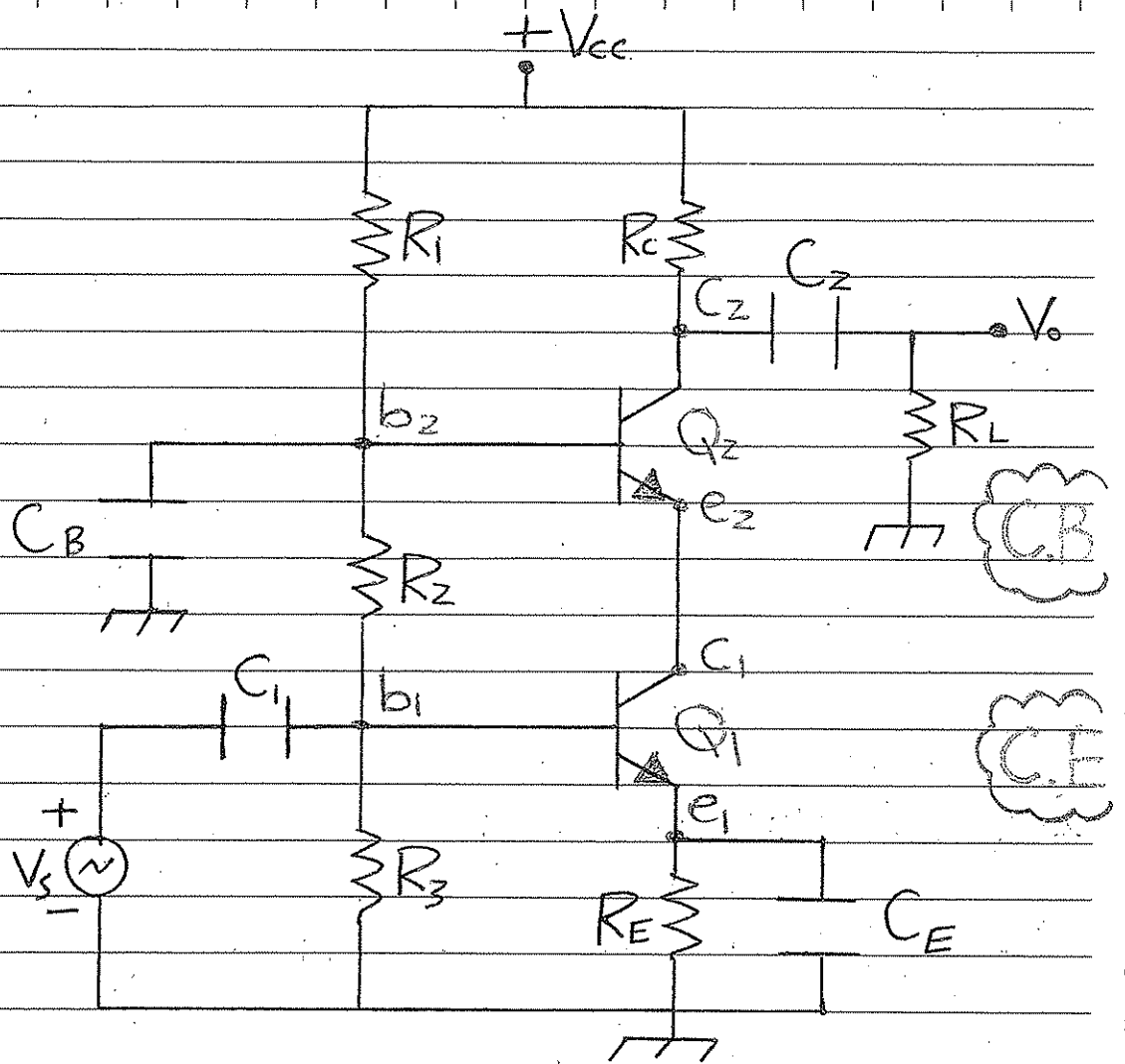


For DC Analysis :-

$I_{CQ1}, I_{CQ2} \checkmark$

$V_{CEQ1}, V_{CEQ2} \checkmark$

$\beta \checkmark$

$V_{BE} \checkmark$

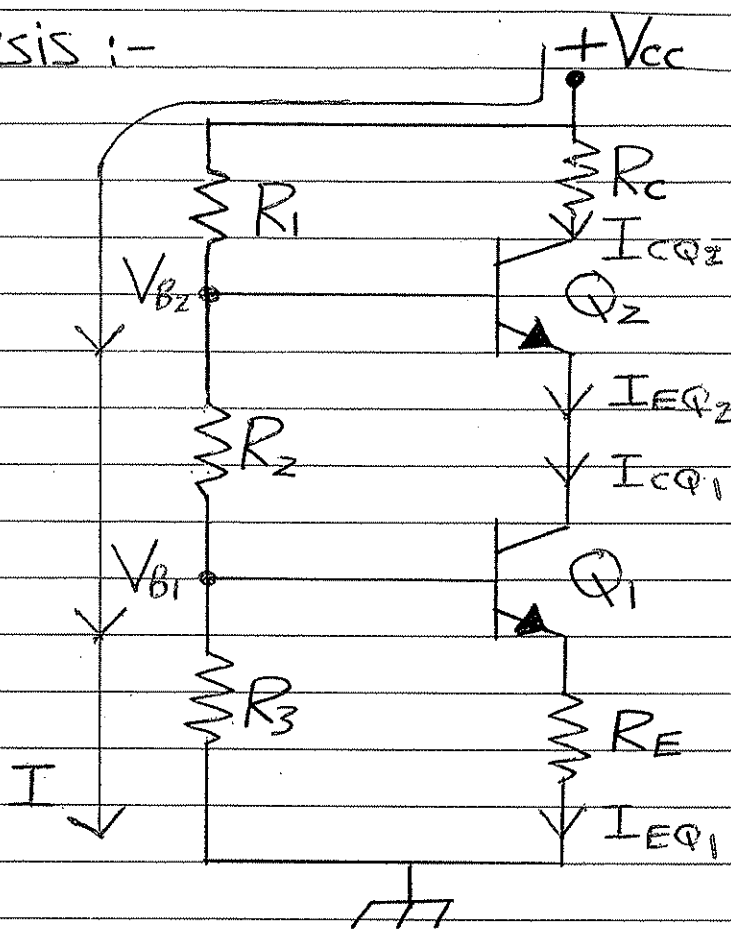

Assume :

$I_C = I_E$

$I_B = 0$

$V_{B1} = I \cdot R_3$

$V_{B1} = V_{CC} \cdot \frac{R_3}{R_1 + R_2 + R_3}$

$-V_{B1} + V_{BE1} + I_{E1} R_E = 0$

$I_{E1} = \frac{V_{B1} - V_{BE}}{R_E}$

$I_{E1} = I_{C1} = I_{E2} = I_{C2}$

$$-V_{B_2} + V_{BE_2} + V_{CE_1} + I_{E_1} R_E = 0$$


$$V_{CE_1} = V_{B_2} - V_{BE_2} - I_{E_1} R_E \quad \checkmark$$



$$V_{B_2} = I(R_2 + R_3)$$

$$-V_{CC} + I_{C_2} R_C + V_{CE_2} + V_{CE_1} + I_E R_E = 0$$

$$V_{CE_2} = V_{CC} - V_{CE_1} - I_E R_E - I_C R_C \quad \checkmark$$

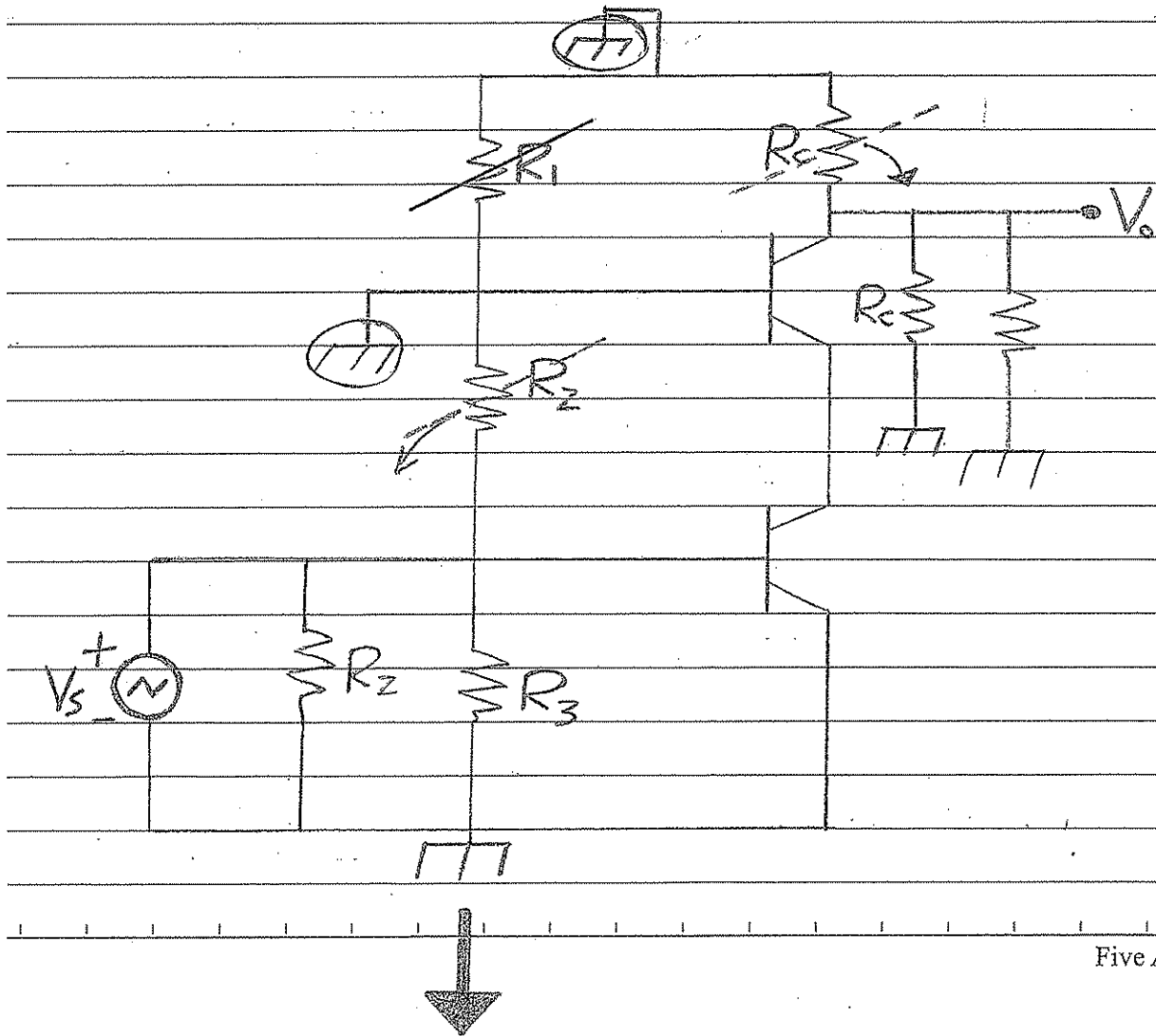For AC Analysis :- $[A_v, A_I, R_i, R_o]$



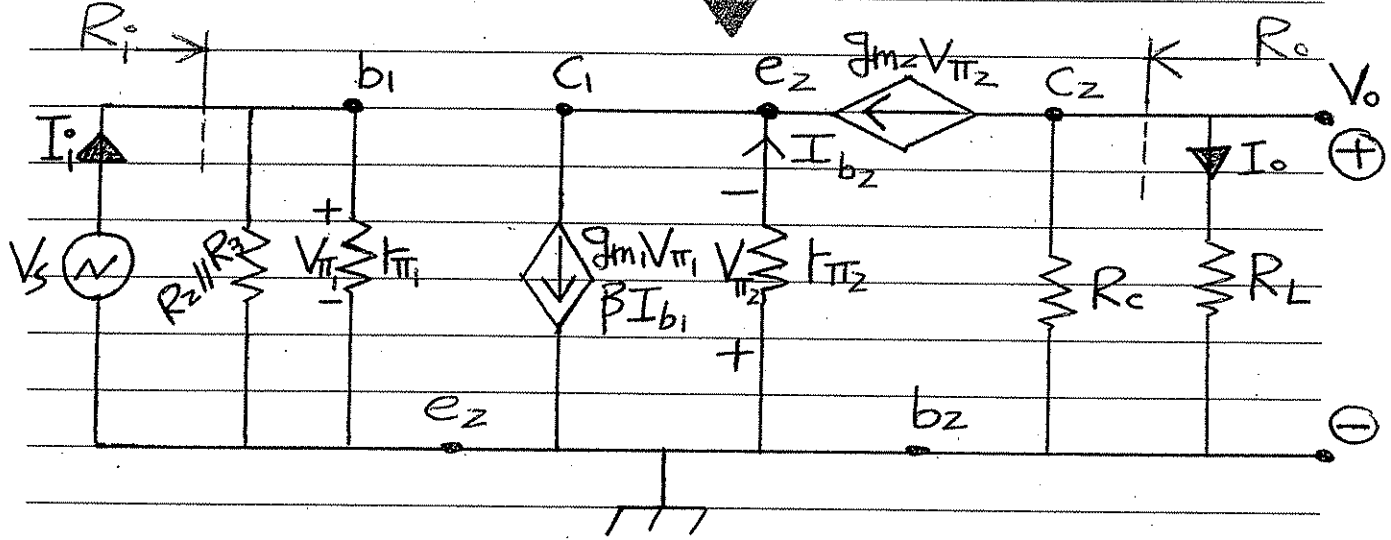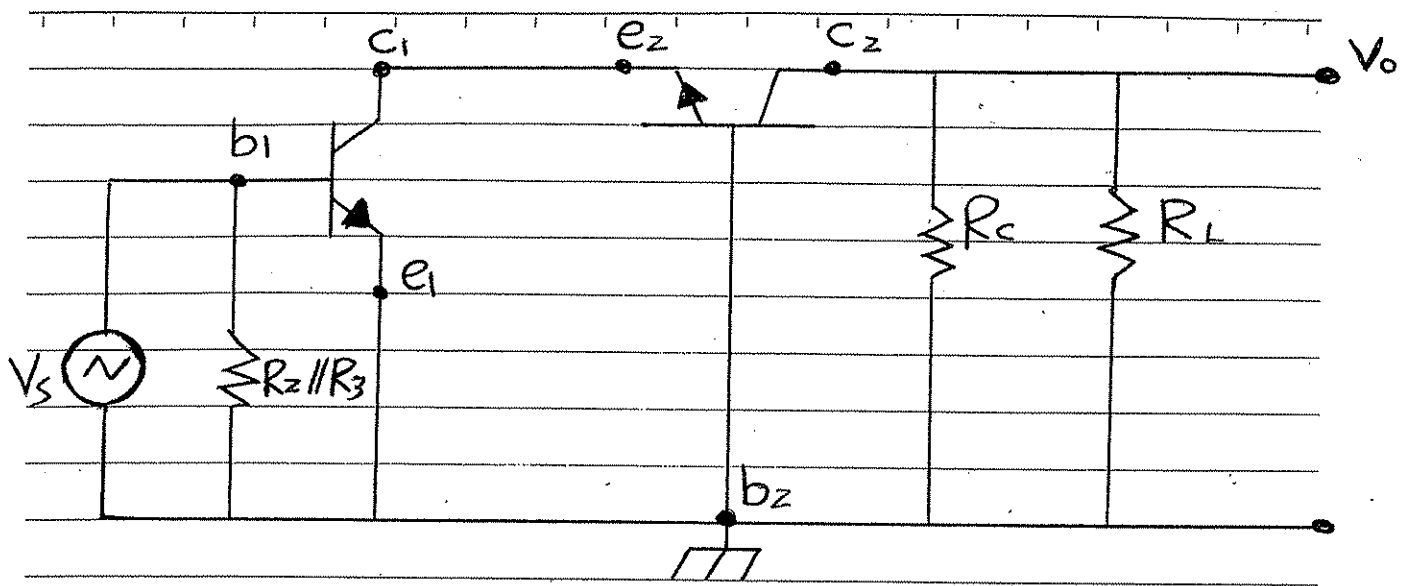

S.S A.C Eqnt. CCT.

$$A_v = \frac{V_o}{V_s}$$

$$V_o = -g_{m2} V_{\pi2} (R_c // R_L)$$

* KCL at node (e_2) :-

$$g_{m2} V_{\pi2} + I_{b2} = g_{m1} V_{\pi1}$$

$$g_{m2} V_{\pi2} + \frac{V_{\pi2}}{r_{\pi2}} = g_{m1} V_{\pi1}$$

$$V_{\pi2} \left(g_{m2} + \frac{1}{r_{\pi2}} \right) = g_{m1} V_{\pi1}$$

$$V_{\pi2} \left(\frac{g_{m2} r_{\pi2} + 1}{r_{\pi2}} \right) = g_{m1} V_{\pi1}$$

$$V_{\pi2} \left(\frac{\beta + 1}{r_{\pi2}} \right) = g_{m1} V_{\pi1}$$

$$V_{\pi2} = \frac{r_{\pi2}}{\beta + 1} g_{m1} V_{\pi1}$$

$$\blacktriangleright V_o = -g_{m2} \frac{r_{\pi2}}{\beta + 1} g_{m1} V_{\pi1} (R_c // R_L)$$

$$\blacktriangleright V_{\pi1} = V_s$$

$$\frac{V_o}{V_s} = \frac{-\beta_2 g_{m1} (R_c \parallel R_L)}{\beta_2 + 1}$$

$$A_v \approx -g_{m1} (R_c \parallel R_L)$$

for stage 1.

Stage 2, common base : $I_{C1} = I_{C2}$ ~~بجواب التيار~~

$$A_I = \frac{I_o}{I_i} = \frac{\frac{V_o}{R_L}}{\frac{V_s}{R_i}}$$

$$A_I = A_v \cdot \frac{R_i}{R_L}$$

$$R_i = R_2 \parallel R_3 \parallel r_{\pi 1}$$


$$R_o = \frac{V_x}{I_x} \Big|_{V_s = 0}$$

$$R_o = R_c$$

Darlington pair CCT. :-

[Multi Stage]

Used for Very high Current gain.

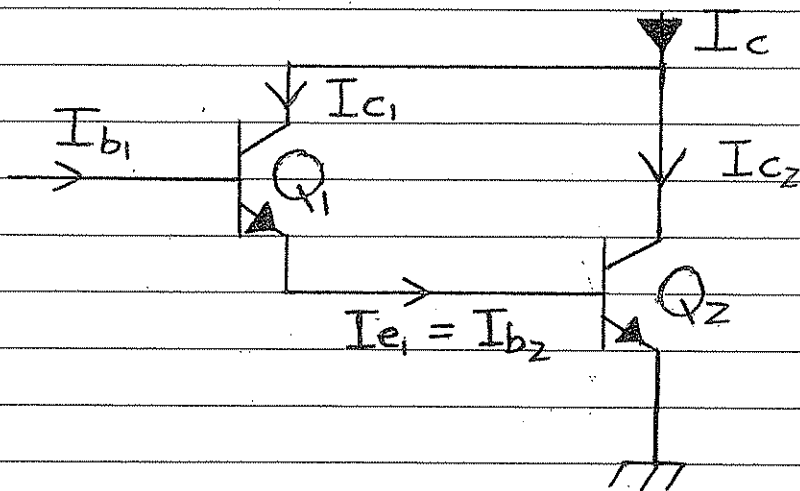

Darlington pair


$$I_c = I_{c1} + I_{c2}$$
$$= \beta I_{b1} + \beta I_{b2}$$

$$I_{b2} = I_{e1} = (\beta + 1) I_{b1}$$


$$I_c = \beta I_{b1} + \beta (\beta + 1) I_{b1}$$
$$= \beta I_{b1} + \beta I_{b1} + \beta^2 I_{b1}$$

$$I_c = I_{b1} (\beta^2 + 2\beta)$$
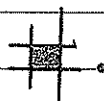
$$\frac{I_c}{I_{b1}} = \beta_{\text{composit}} \approx \beta^2$$



EXA. :-

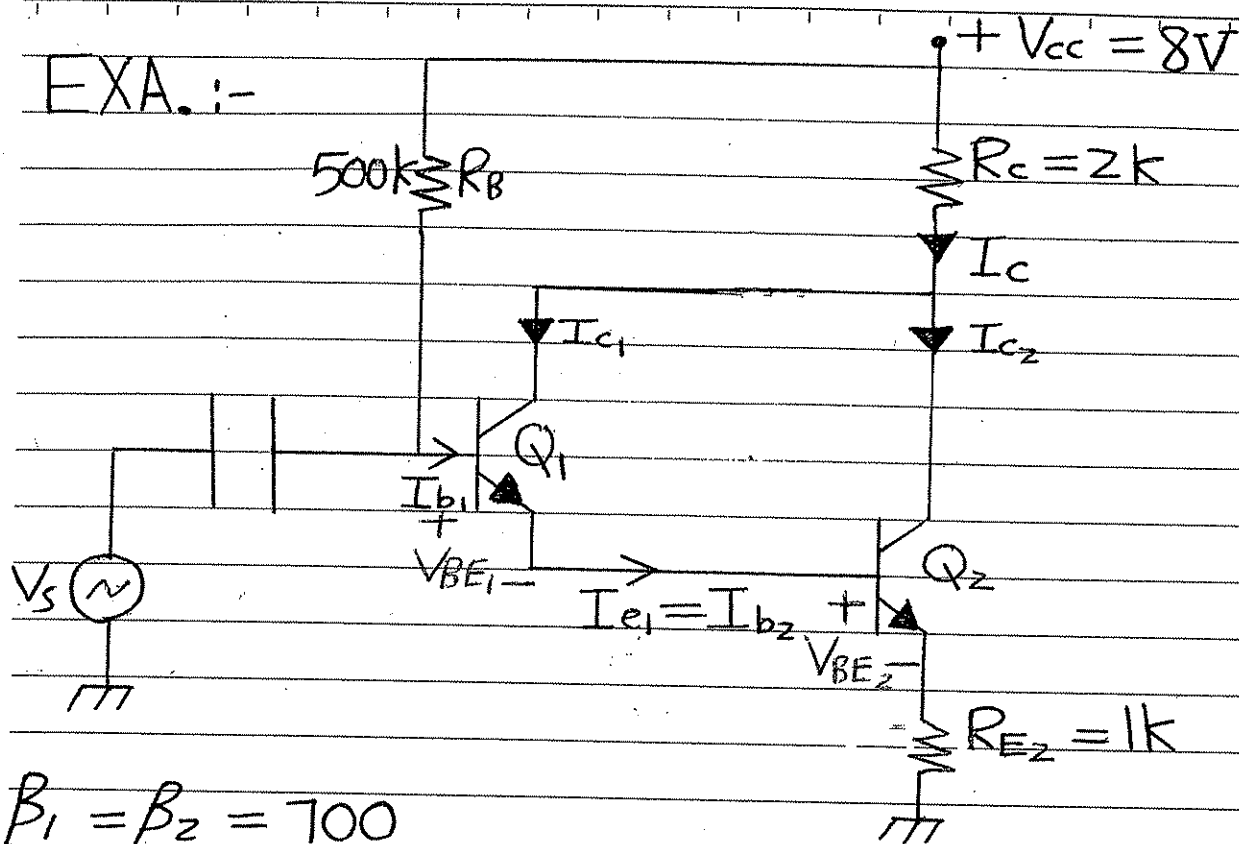

$$\beta_1 = \beta_2 = 700$$

$$V_{BE1} = V_{BE2} = 0.6V$$

Sol: - for DC analysis :-


$$-8 + I_{B1}R_B + V_{BE1} + V_{BE2} + I_{E2}R_{E2} = 0$$

$$I_{E2} = (\beta + 1)I_{B2} = (\beta + 1)(\beta + 1)I_{B1} = (\beta + 1)^2 I_{B1}$$


$$\rightarrow I_{B1} = \frac{8 - 0.6 - 0.6}{500k + (701)^2 * 1} = \dots$$

$$V_{CE1} = \dots ; V_{CE2} = \dots$$

For AC analysis :

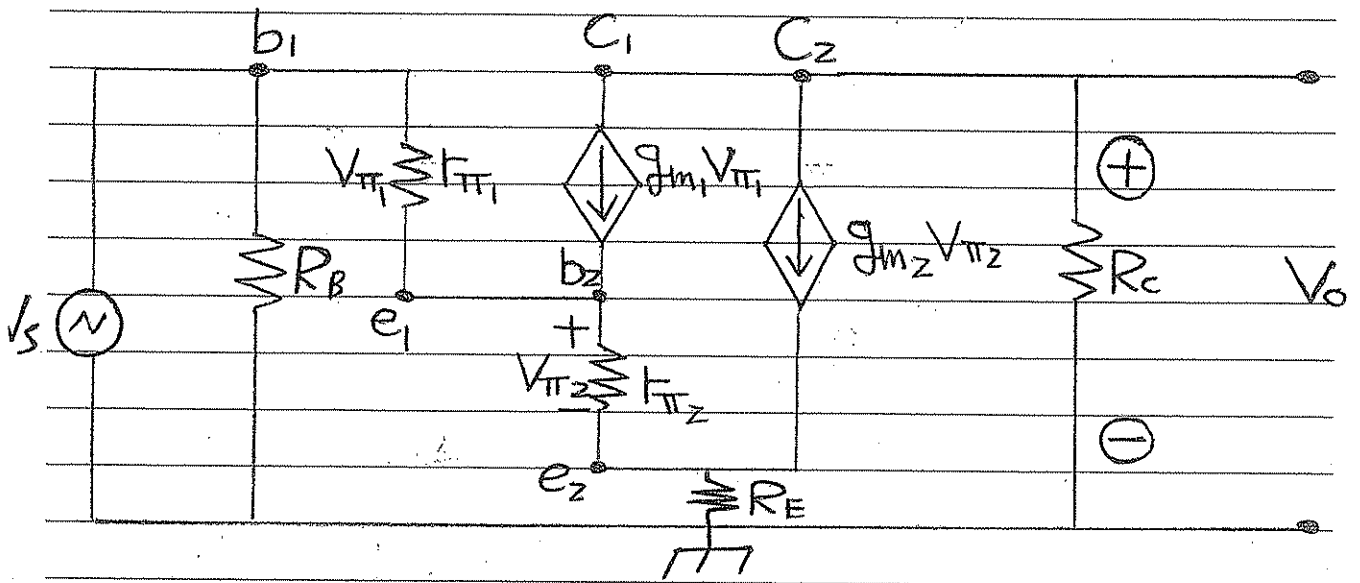

* Resistance-Reflection Rule [R.R.R] :-

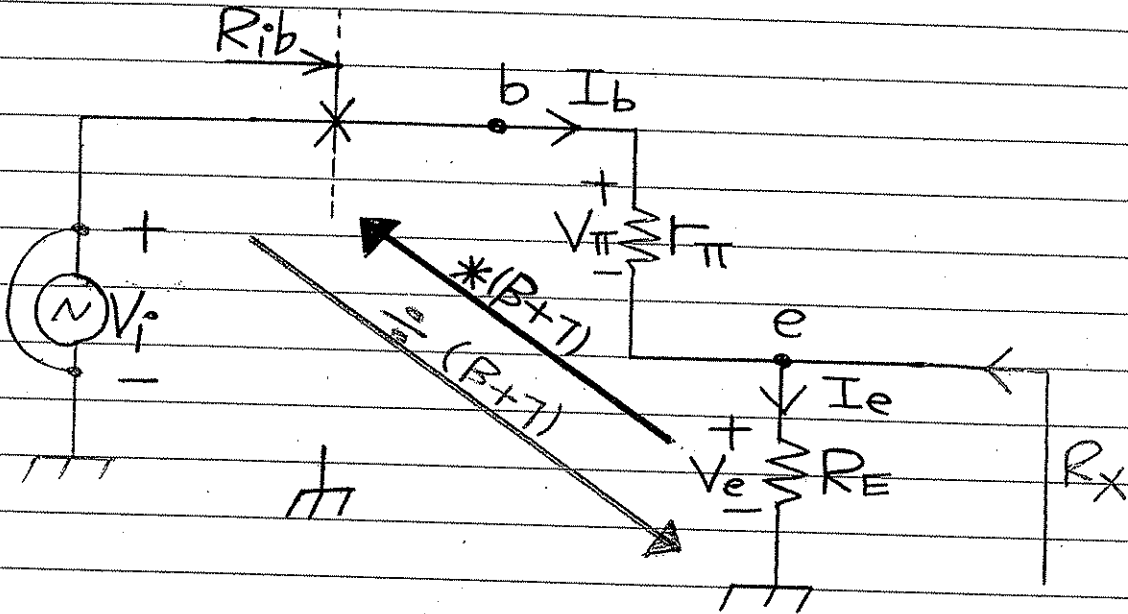

$$R_{ib} = r_{\pi} + (\beta+1)R_E$$


* Inverse R.R.R :-

$$R_x = \frac{r_{\pi} \parallel R_E}{(\beta+1)}$$

Chapter(4): Basic (FET) Amplifiers :- 60

The MOSFET must be biased in Saturation Regn. to be used as an Amplifier. This requires D.C Analysis of MOSFET CCT.

D.C Analysis of MOSFET CCT. :-

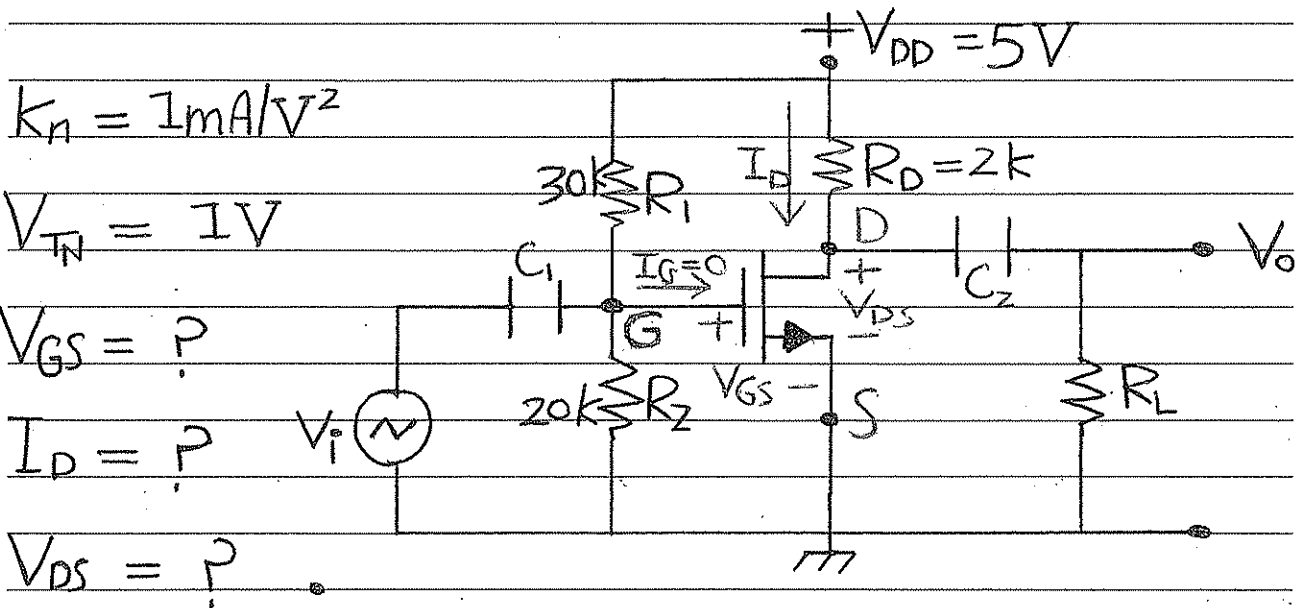


$$k_n = 1 \text{ mA/V}^2$$

$$V_{TN} = 1 \text{ V}$$

$$V_{GS} = ?$$

$$I_D = ?$$

$$V_{DS} = ?$$

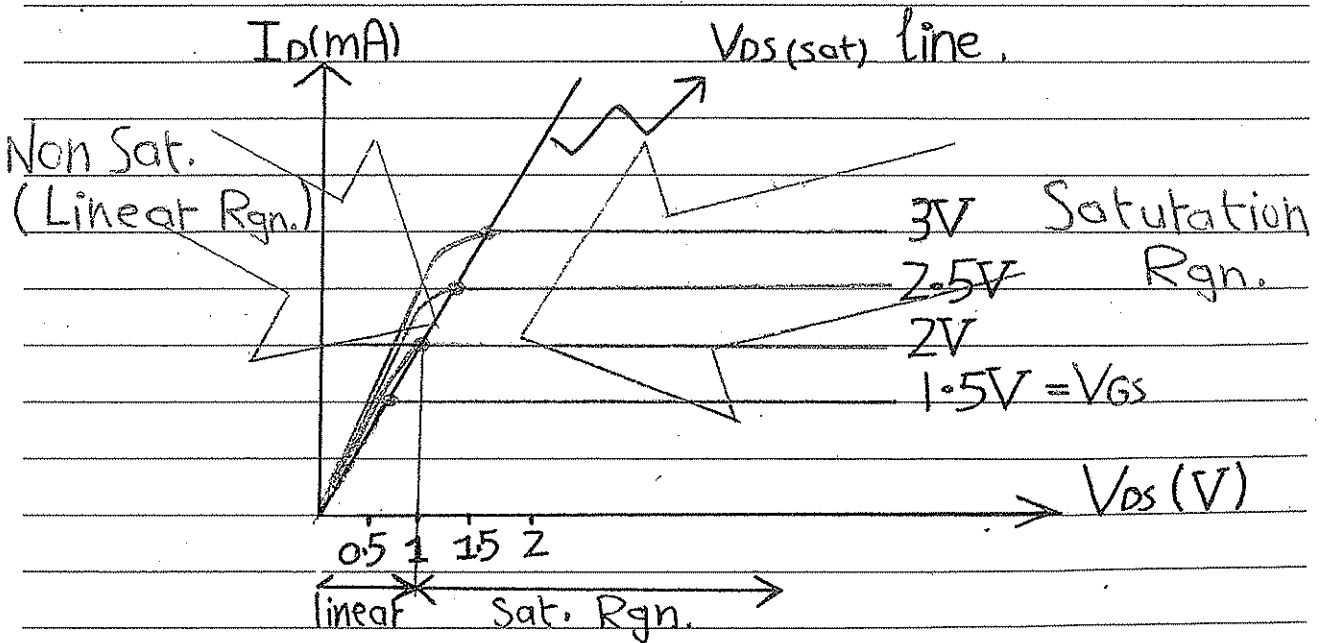

$$V_{DS(sat)} = V_{GS} - V_{TN}$$

$$V_{TN} = 1$$

* MOSFET Operations Regions :-

1) Saturation Regn. :-

In this Regn. ; $V_{DS} > V_{DS(sat)}$

Where $V_{DS(sat)} = V_{GS} - V_{TN}$
↳ from ckt. ↳ given.

then :-

$$I_D = k_n (V_{GS} - V_{TN})^2$$

∴ The MOSFET is used as an Amplifier.

2) NON Saturation Regn. :- [Linear Regn.] :-

When $V_{DS} < V_{DS(sat)}$

$$\text{then ; } I_D = k_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

and the MOSFET is used as Voltage - Controlled Resistor.

For this Example:-

→ For DC Analysis : Assume the MOSFET is in Sat. Regn. :-

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$V_{GS} = V_G - V_S$$

$$= \frac{5 \times 20}{50} - 0 = 2V$$


$$I_D = 1(2-1)^2 = 1mA$$

$$V_{DS} = V_{DD} - I_D R_D = 5 - 1 \times 2 = 3V$$

$$V_{DS_{sat.}} = V_{GS} - V_{TN} = 2 - 1 = 1V$$

Since $V_{DS} > V_{DS_{sat.}}$ MOSFET is in Sat. and can be used as Amp.

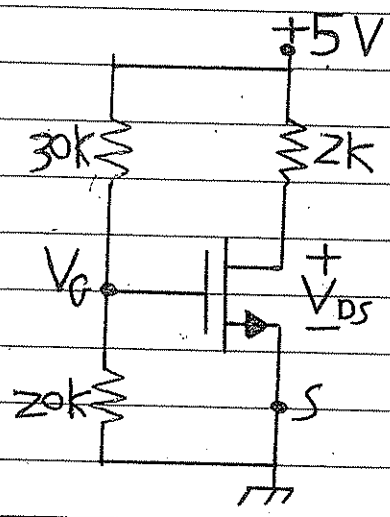
$$P_D = I_D \cdot V_{DS} = 1 \times 3 = 3mW$$



D.C.l.l :- KVL for D-S loop :-

$$V_{DD} + I_D R_D + V_{DS} = 0$$

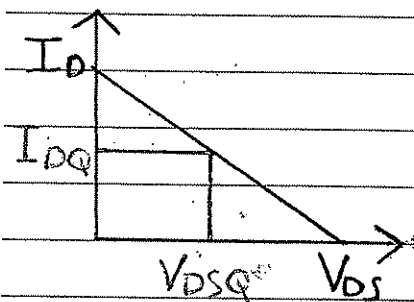
$$V_{DS} = V_{DD} - I_D R_D \quad \text{D.C.l.l Eqn.}$$



$$\text{Slope} = -\frac{1}{R_D}$$

1] For $I_D = 0$, $V_{DS} = V_{DD} = 5V \rightarrow P_1(5V, 0)$

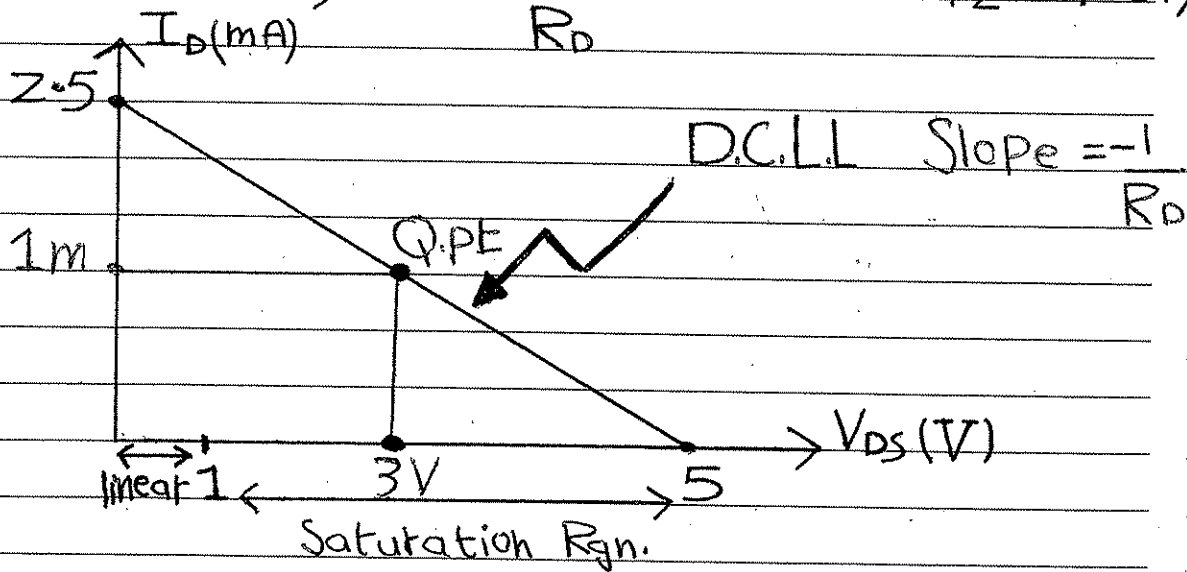2] For $V_{DS} = 0$, $I_D = \frac{V_{DD}}{R_D} = 2.5\text{mA} \rightarrow P_2(0, 2.5\text{mA})$




Q.Pt:

at the Center of Sat. Rgn. : $\frac{5+1}{2} = 3$


at the center of D.C.l.l : $\frac{5}{2} = 2.5$

MOSFET Amplifiers :-


1) Common Source Amp. :-

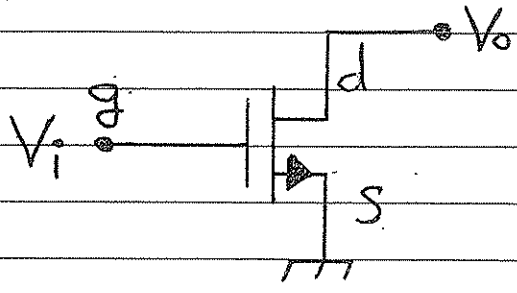

2) Common Drain Amp. :-

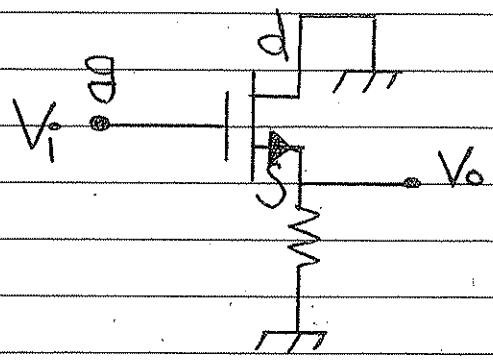


3) Common gate Amp. :-

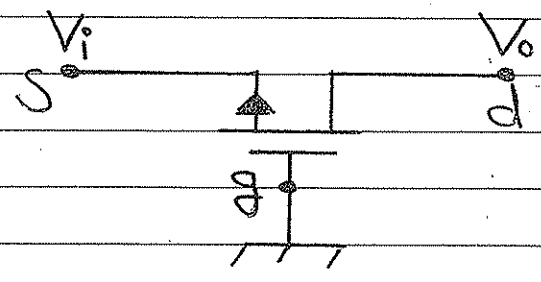


Common Source Amp. :

i) Basic Common Source Amp. :-

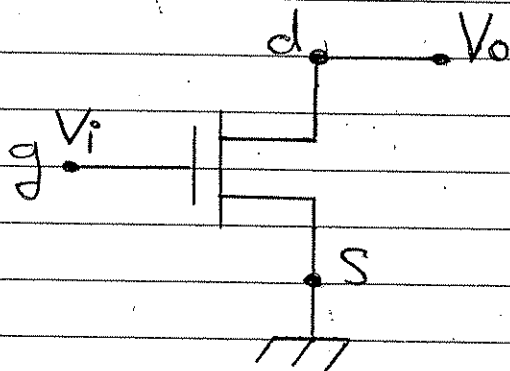

EXA. :-

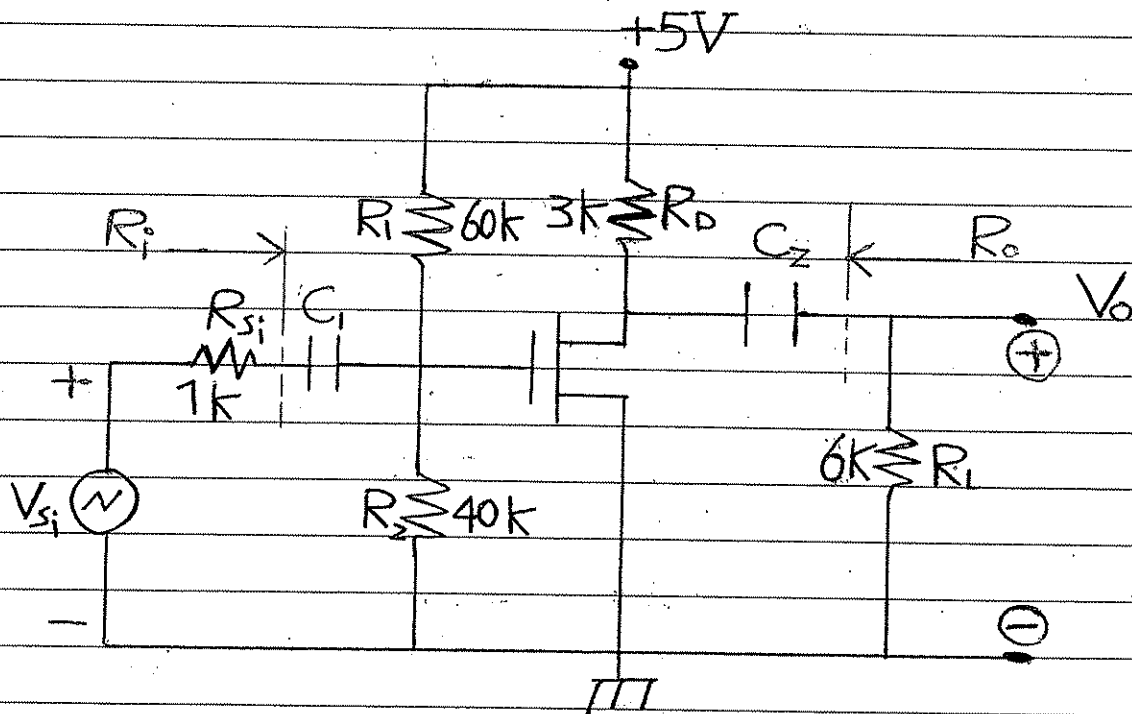

$$K_n = 1 \frac{\text{mA}}{\text{V}^2}, \quad V_{TN} = 1\text{V}, \quad \lambda = 0.01 \text{V}^{-1}$$

1) Calculate V_{GSQ} , I_{DQ} , V_{DSQ} .

2) Draw S.S.A.C Eqnt. CCT. and find

$$A_v = \frac{V_o}{V_{si}}, R_i, R_o.$$

Solution:

1) DC analysis :- [C : 0.C]

Assume the MOSFET

in Saturation Rgn. :-

$$I_D = k_n (V_{GS} - V_{TN})^2$$

$$\# V_{GS} = V_G - V_S$$


$$= \frac{V_{DD} \cdot R_2}{R_1 + R_2} - 0 = \frac{5 \cdot 40}{40 + 60} = 2V \quad \#$$

OR :-

$$-2 + I_G R_G + V_{GS} = 0$$

$$V_{GS} = 2V.$$

#

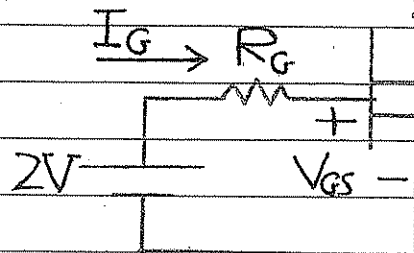

$$\ast I_D = 1(2-1)^2 = 1 \text{ mA}$$


$$-V_{DD} + I_D R_D + V_{DS} = 0$$

$$\ast V_{DS} = 5 - 1 \times 3 = 2 \text{ V}$$


$$V_{DS(sat)} = V_{GS} - V_{TN} = 2 - 1 = 1 \text{ V}$$

Since $V_{DS} > V_{DS(sat)}$ \therefore MOSFET in Sat. Rgn.

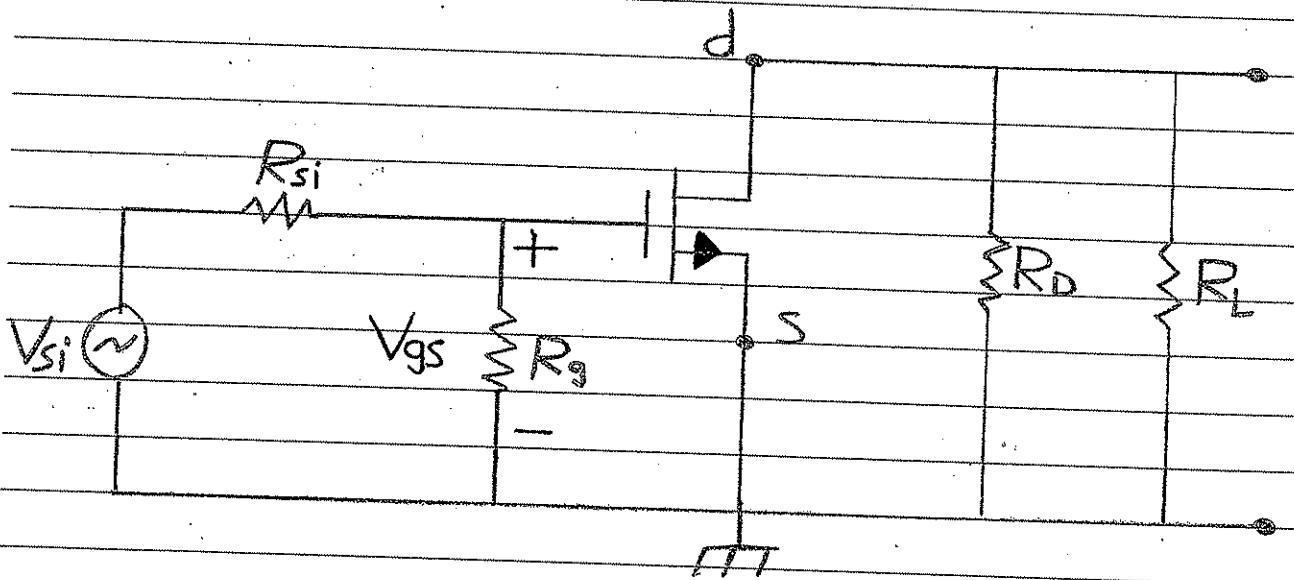2) AC analysis :- [C : S.C ; DC : S.C] \ast



MOSFET Model:-

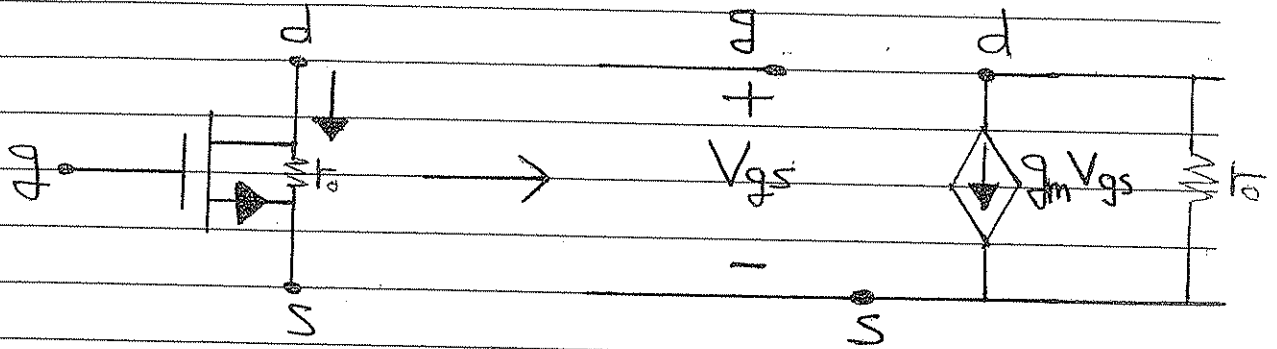

g_m : Transconductance $\left[\frac{\text{mA}}{\text{V}} \right]$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = 2k_n (V_{GS} - V_{TN})$$

or:


$$g_m = 2\sqrt{k_n I_D}$$

r_o : MOSFET o/p resistance.

$$r_o = \frac{1}{\lambda I_{DQ}}$$

λ : Channel length modulation parameter.


$$[\text{V}^{-1}]$$

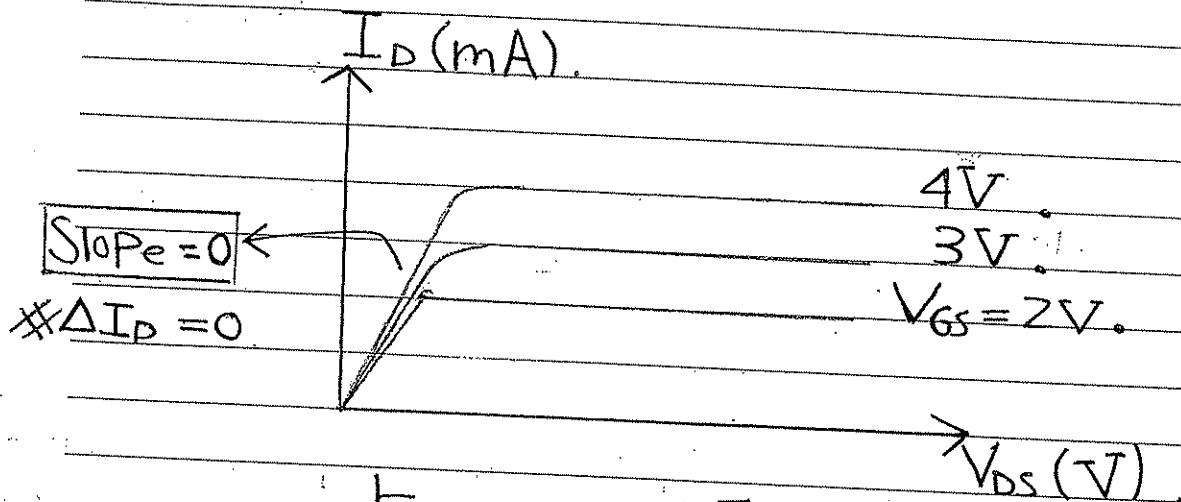


$$r_o = \frac{1}{0}$$

Slope of (I_D, V_{DS}) line

$$r_o = \frac{1}{0} = \infty$$

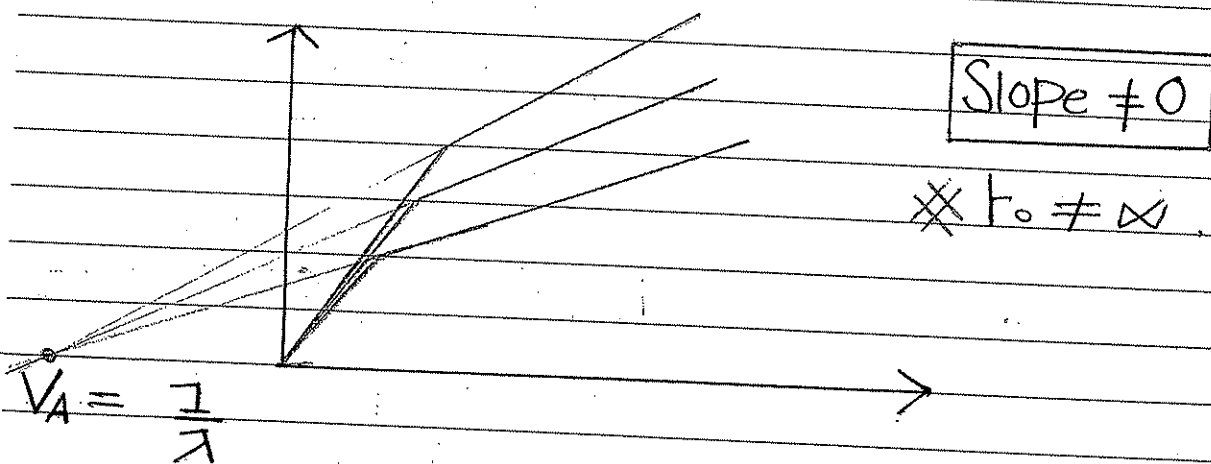

$$r_o = \frac{1}{\lambda I_{DQ}}$$

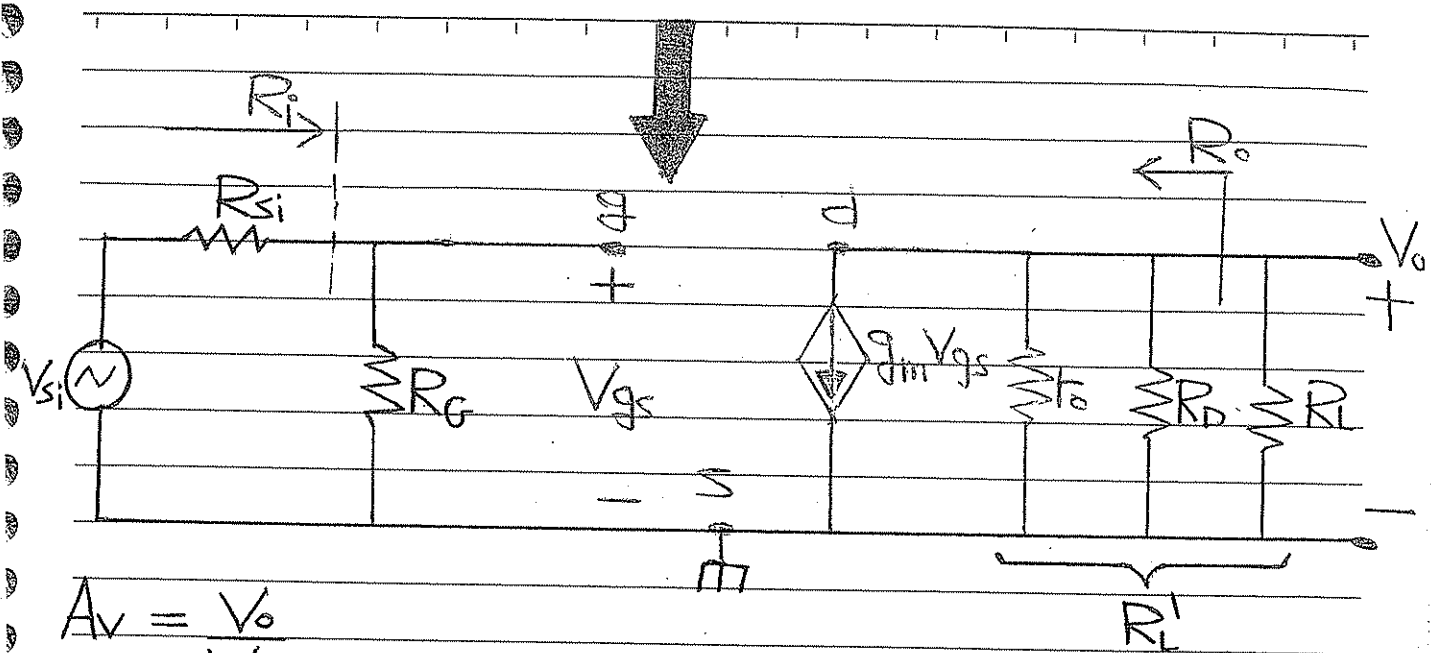

$$A_v = \frac{V_o}{V_{s_i}}$$

$$V_o = -g_m V_{gs} R'_L \quad ; \quad R'_L = r_o \parallel R_D \parallel R_L$$

$$V_{gs} = V_{s_i} \cdot \frac{R_g}{R_g + R_{s_i}}$$

$$\therefore V_o = -g_m R'_L \frac{V_{s_i} \cdot R_g}{R_g + R_{s_i}}$$

$$\frac{V_o}{V_{s_i}} = A_v = - \frac{g_m R'_L \cdot R_g}{R_g + R_{s_i}}$$

> means 180° phase-shift

between (Vsi) and (Vo) . #.

$$g_m = 2\sqrt{k_n I_D} = 2\sqrt{1 \times 1} = 2 \text{ mA/V}$$

$$R_L' = r_o \parallel R_D \parallel R_L$$

$$\# r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{0.01 \times 1 \times 10^{-3}} = 100 \text{ k}\Omega$$

$$\therefore R_L' = 100 \parallel 3 \parallel 6 = 1.95 \text{ k}\Omega$$



$$R_G = R_1 \parallel R_2 = 40 \parallel 60 = 24 \text{ k}\Omega$$

$$A_v = -2 \times 1.95 \times 24$$

$$= -3.9 \times 0.96 = -3.8 \quad \#$$

For $V_{si} = 2 \sin \omega t$ (V), then:
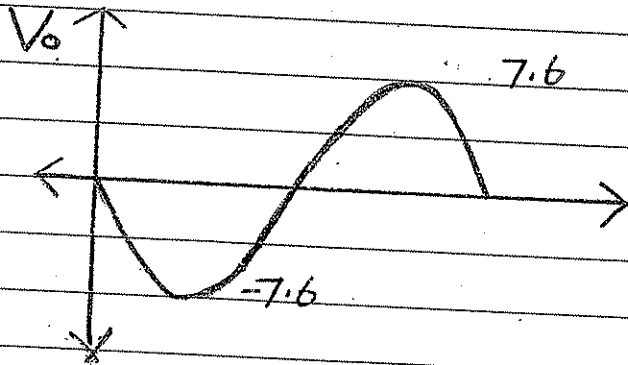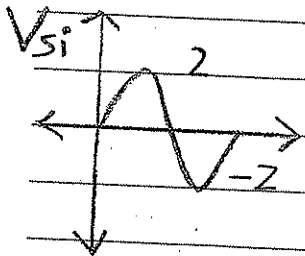
$$V_o = -3.8 \times 2 = -7.6 \sin \omega t \rightarrow \text{مقلوبه و مقلوبه}$$



$$R_i = R_G = 24 \text{ k}\Omega$$

$$R_o = \frac{V_x}{I_x} \Big|_{V_{si}=0}, \text{ When } V_{si} = 0 \text{ :-}$$

then. $V_{gs} = 0 \iff g_m V_{gs} = 0$; dependent
current source is
Open Circuit.


$$R_o = R_D \parallel r_o$$

$$= 3 \parallel 100 = 2.9 \text{ k}\Omega \quad \#$$

$$\# R_i \uparrow, R_o \uparrow, A_v \uparrow, R_o \text{ calc}$$

$$\# V_z \uparrow, V_g \uparrow, V_{gs} \uparrow, A_v \uparrow$$


D.C.L.L :-

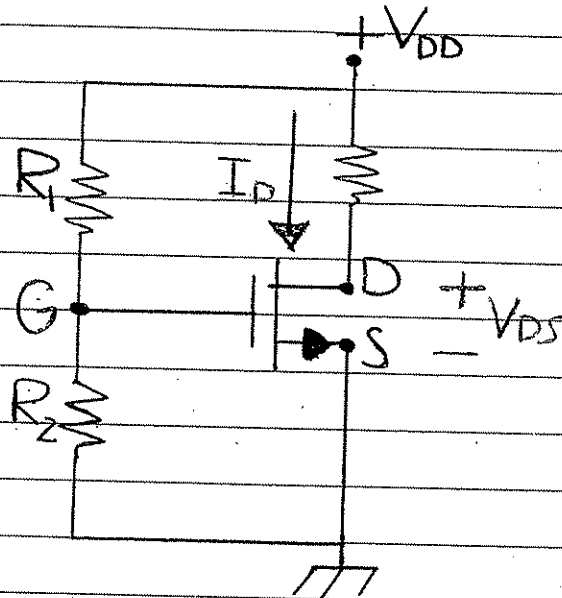


$$-V_{DD} + I_D R_D + V_{DS} = 0$$

$$I_D = \frac{V_{DD} - V_{DS}}{R_D} \rightarrow I_D = \frac{V_{DD} - V_{DS}}{R_D}$$

Slope = $-\frac{1}{R_D}$

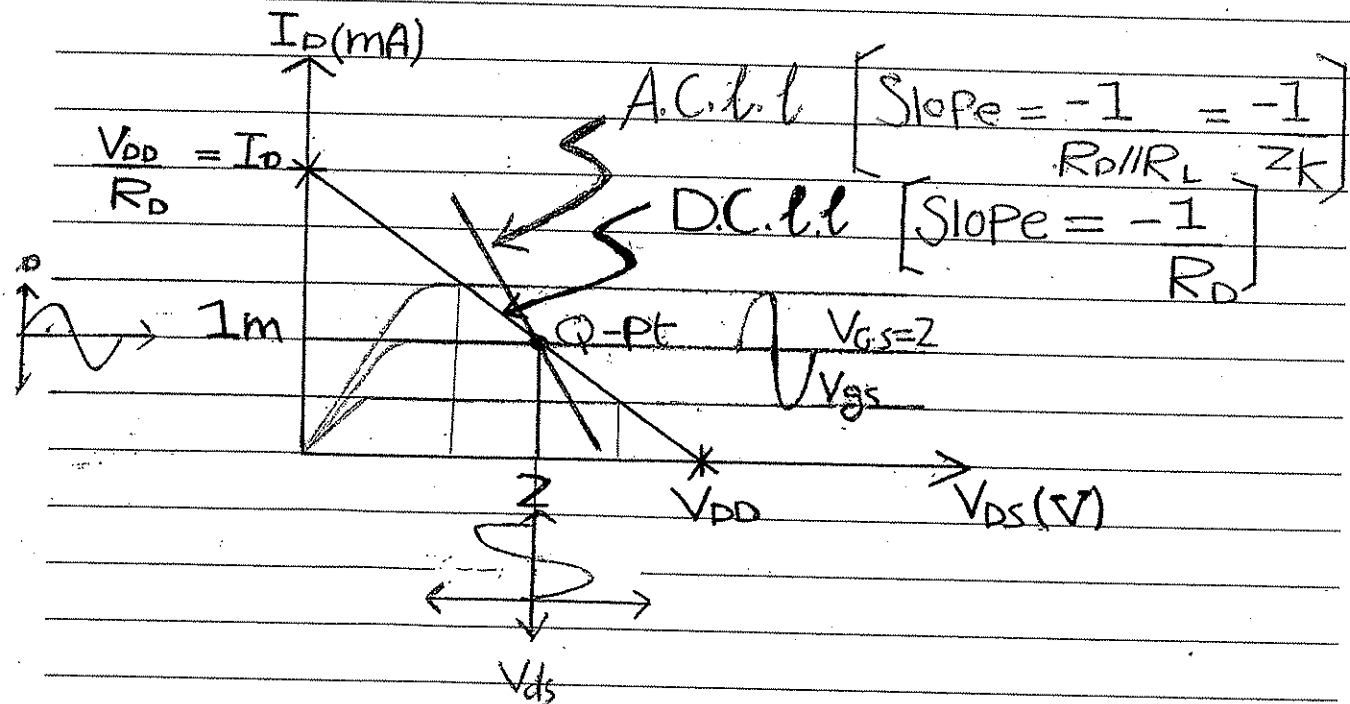

A.C.L.L :-

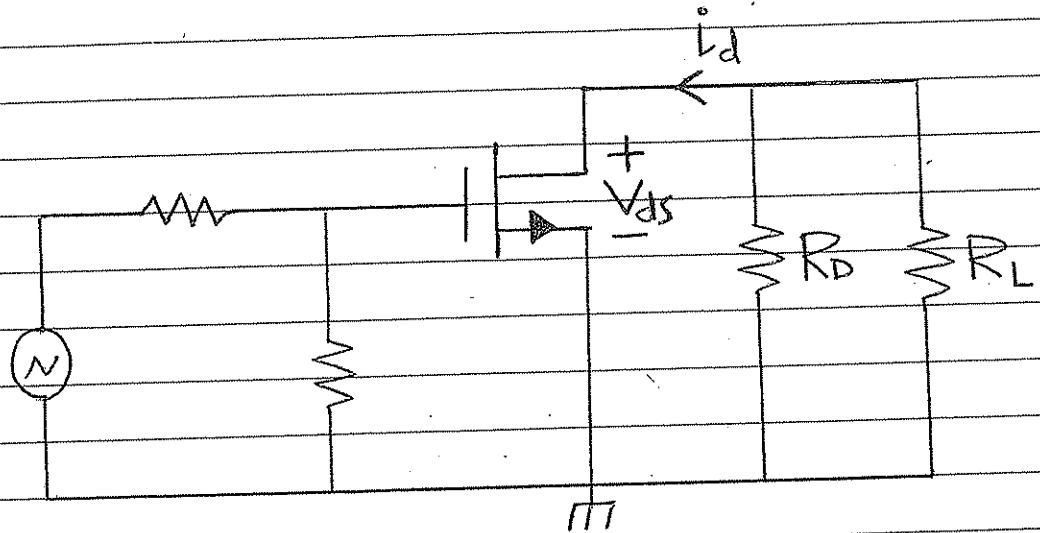

$$V_{ds} + i_D (R_D // R_L) = 0$$

$$V_{ds} = -i_D (R_D // R_L) \text{ --- A.C.L.L Eqn.}$$


$\text{Slope} = \frac{-1}{(R_D // R_L)}$
--

(-1) / (R_D // R_L)

ii) Common Source with R_S :-

R_S : Stabilize (Q-pt.) against (k_n) parameter variation.

EXA. :-

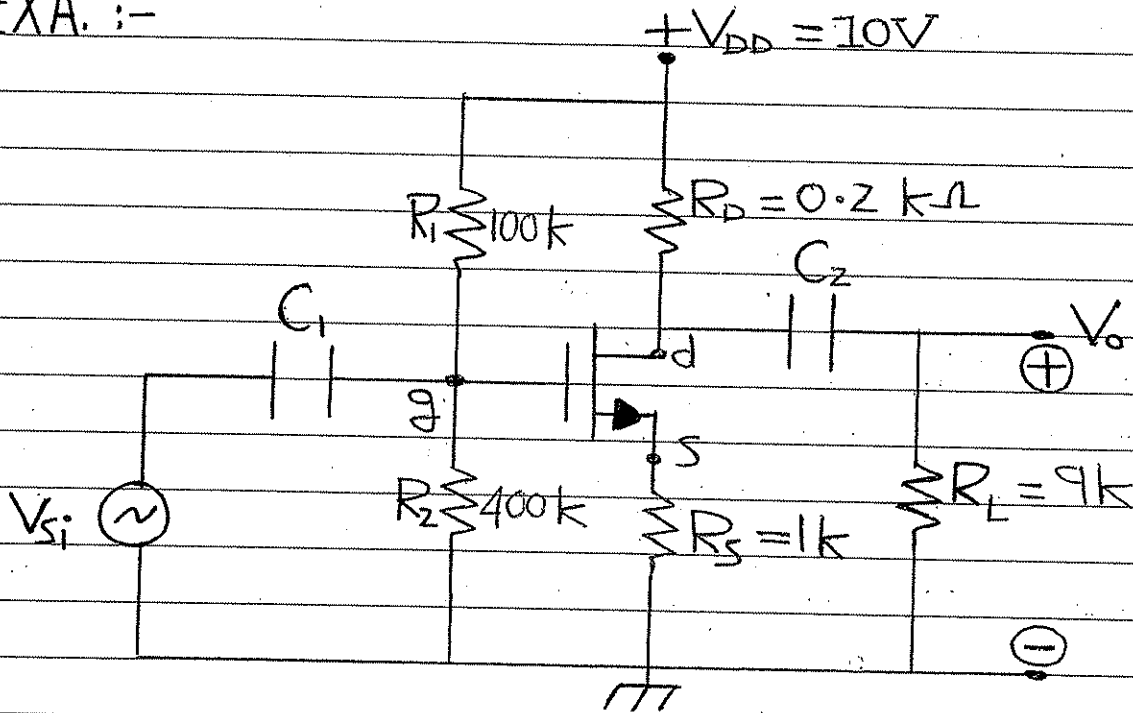

$k_n = \frac{4mA}{V^2}$, $V_{TN} = 1V$, $\lambda = 0$:-

1) Calculate V_{GSQ} , I_{DQ} , V_{DSQ} .

2) Draw S.S.A.C Eqnt. CCT. and find

A_v , R_i , R_o .

Sol:- For DC Analysis :-


Assume the MOSFET

in Sat. Rgn. :-

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$* V_{GS} = V_G - V_S$$
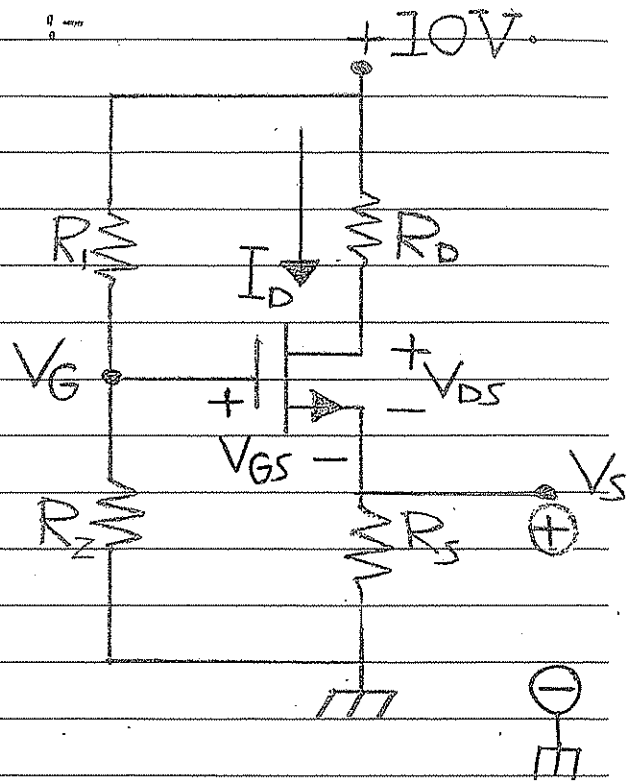
$$V_G = \frac{10 * R_2}{R_1 + R_2} \\ = \frac{10 * 400}{500} = 8V$$



$$V_S = I_D R_S = 1 * I_D = I_D$$

$$\therefore V_{GS} = 8 - I_D \rightarrow I_D = 8 - V_{GS}$$

$$\rightarrow 8 - V_{GS} = 4(V_{GS} - 1)^2$$

$$4(V_{GS}^2 - 2V_{GS} + 1) + V_{GS} - 8 = 0$$

$$4V_{GS}^2 - 7V_{GS} - 4 = 0$$

$$\{AX^2 + BX + C = 0\}$$

$$V_{GS} = \frac{7 \pm \sqrt{(49) + 4 * 4 * 4}}{8}$$

$$= \frac{7 \pm \sqrt{113}}{8} = \frac{7 \pm 10.6}{8} = 2.2V \text{ or } -0.45V$$

$$\sqrt{113} = 10.6$$

$$\therefore V_{GSQ} = 2.2V. \quad \#$$

$$I_D = 8 - 2.2 = 5.8 \text{ mA}. \quad \#$$

$$-10 + I_D R_D + V_{DS} + I_D R_S = 0$$

$$V_{DS} = 10 - 5.8(1 + 0.2) \approx 3V.$$

$$\therefore V_{DS(\text{sat.})} = 2.2 - 1 = 1.2V. \quad \#$$


V_D :

$$-10 + I_D R_D' + V_D = 0$$

$$V_D = 10 - (5.8 * 0.2) = 8.84V. \quad \#$$


$$\text{Slope} = \frac{-1}{R_D + R_S} \quad \#$$

*For AC Analysis :- [C.S.C ; D.C.S.C].

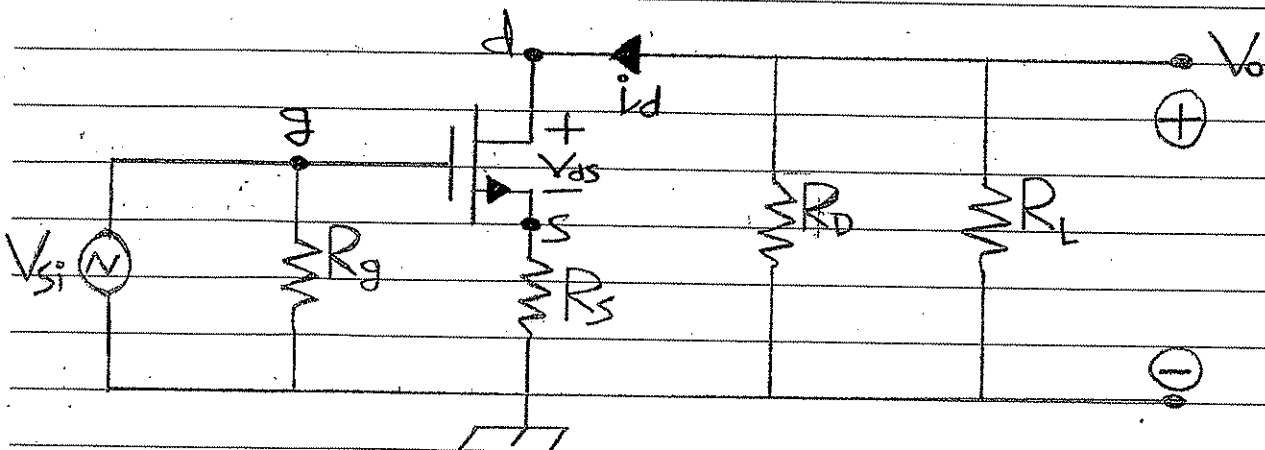

$$V_{ds} + i_d R_s + i_d (R_L // R_D) = 0$$
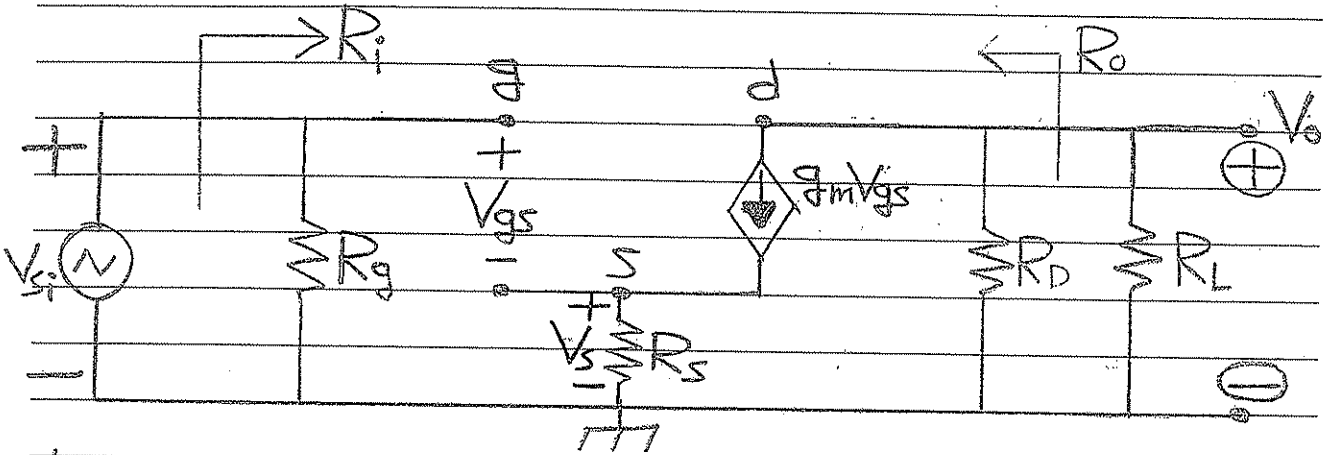
$$V_{ds} = -i_d (R_s + R_L // R_D) \rightarrow \text{AC.1.1 Eqn.}$$



$$A_v = \frac{V_o}{V_{si}} = \frac{-g_m V_{gs} (R_D // R_L)}{V_{si}}$$

$$-V_{si} + V_{gs} + V_s = 0$$

$$V_{gs} + g_m V_{gs} R_s = V_{si}$$

$$V_{gs} (1 + g_m R_s) = V_{si}$$

$$V_{gs} = \frac{V_{si}}{1 + g_m R_s}$$

$$A_v = \frac{-g_m V_{gs} (R_D // R_L)}{V_{gs} (1 + g_m R_s)} \rightarrow \boxed{A_v = \frac{-g_m (R_D // R_L)}{1 + g_m R_s}}$$

*** R_s reduces A_v**

$$g_m = 2\sqrt{k_n I_D} = 2\sqrt{4 \times 5.8} = 9.6 \text{ mA/V}$$


$$A_v = \frac{-9.6 (0.2 // 9)}{1 + (9.6 * 1)} = -0.17 \#$$


$$R_i = R_g = 100 // 400 \\ = 80 \text{ k}\Omega \#$$

$$R_o = \left. \frac{V_x}{I_x} \right|_{V_s=0}$$

$$= R_D = 0.2 \text{ k}\Omega \#$$

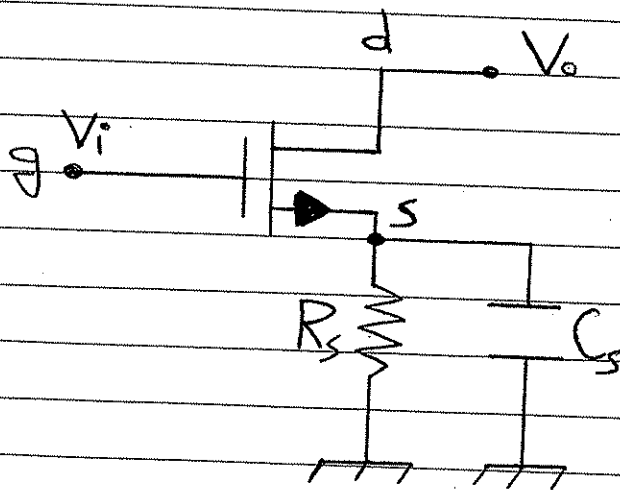iii) Common Source with bypass Capacitor C_s



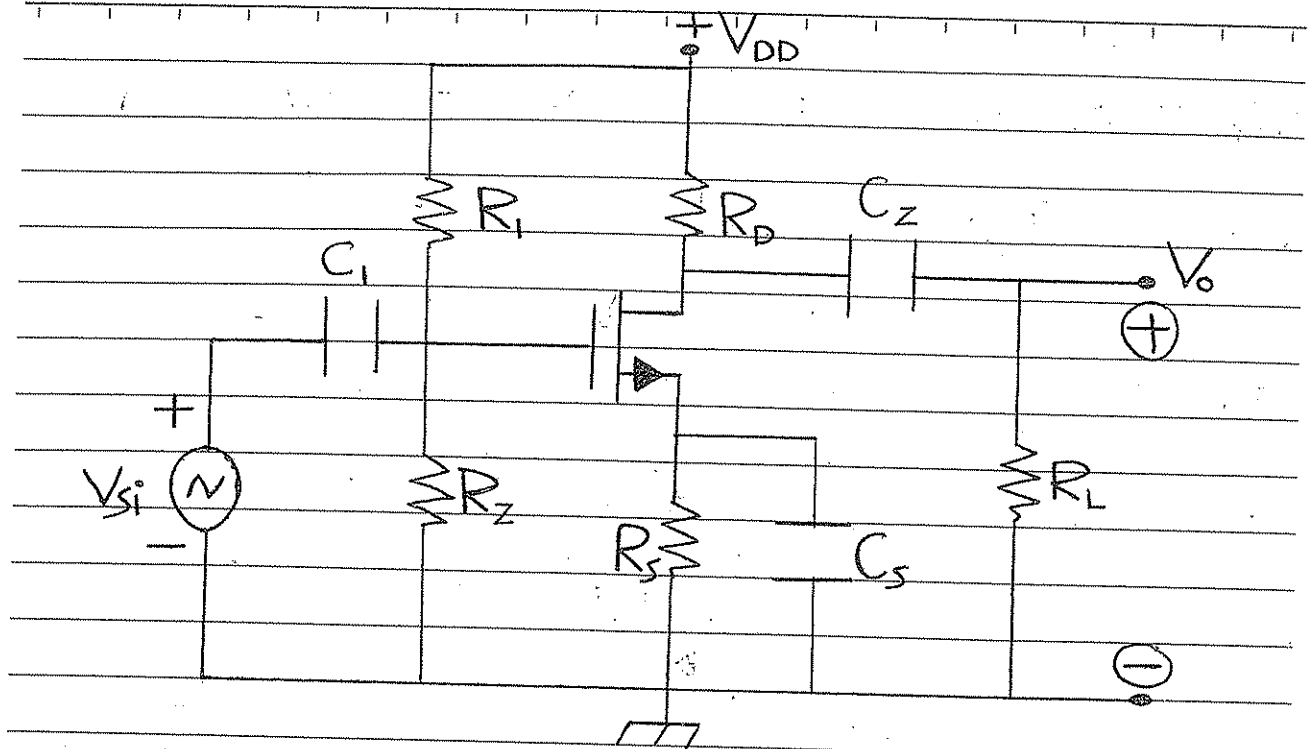

For DC analysis, (C_S) is open ckt. and the ckt. behaves as [C.S with R_S].

For AC analysis, (C_S) is short ckt. and the ckt. behaves as [Basic C.S Amp.].


EXA. :-

Design the Circuit Shown to have the following Specification :-


$$I_{DQ} = 1 \text{ mA} , V_{DSQ} = 10 \text{ V} , A_v = -14 ,$$

$$R_i = 200 \text{ k}\Omega ;$$

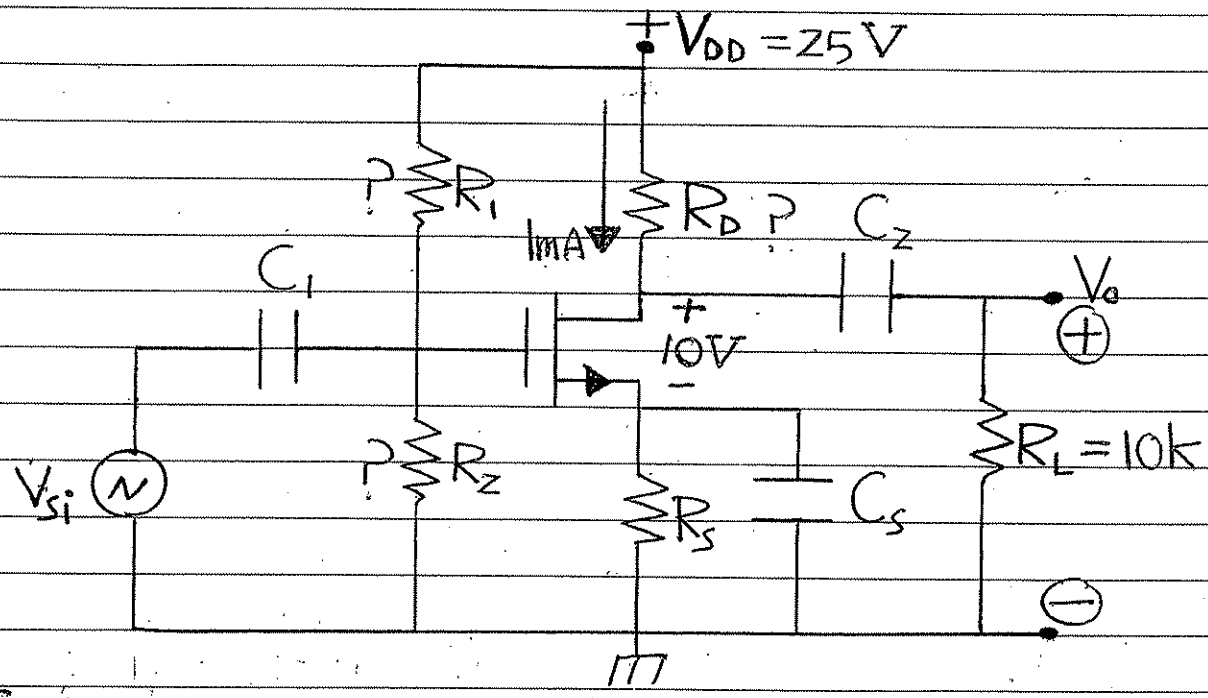Given :- $V_{TN} = 1V$, $k_n = 2 \frac{mA}{V^2}$, $\lambda = 0$
 $V_{DD} = 25V$, for $R_L = 10k\Omega$



Solution :-

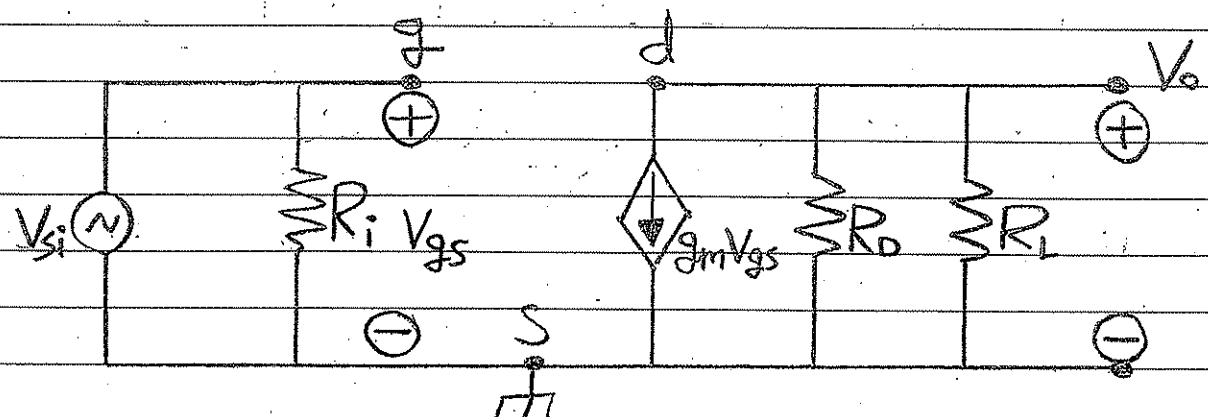

$$A_v = \frac{-V_o}{V_{si}} = -\frac{g_m V_{gs}}{V_{gs}} (R_D // R_L)$$

$$A_v = -g_m (R_D // R_L)$$

$$g_m = 2\sqrt{k_n I_D} = 2\sqrt{2 \times 1} = 2.8 \text{ mA/V}$$

$$-14 = -2.8(R_D // R_L)$$


$$\rightarrow R_D // R_L = 5 \text{ k}\Omega$$

$$5 = 10 // R_D \rightarrow \underline{R_D = 10 \text{ k}\Omega} \quad \#$$

$$-V_{DD} + I_D R_D + V_{DS} + I_D R_S = 0$$

$$R_D + R_S = 25 - 10 = 15 \text{ k}\Omega$$
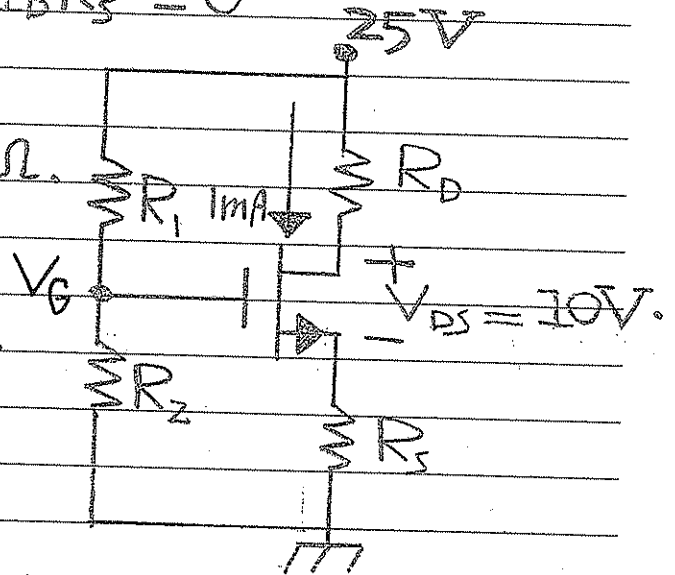
$$\therefore R_S = 15 - 10 = 5 \text{ k}\Omega$$



From DC analysis :-

$$V_G \cdot R_1 = V_{DD} R_2 \cdot R_1 \cdot R_1$$

بعضوب الكورني العادلة

$$R_1 = \frac{V_{DD} R_2}{V_G} \quad ; \quad R_i = R_1 // R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$V_{GS} = V_G - V_S$$

$$\boxed{V_G = V_{GS} + V_S}$$

$$\# V_S = I_D R_S = 1 * 5 = 5V.$$

$$\# I_D = k_n (V_{GS} - V_{TN})^2$$

$$\sqrt{\frac{I_D}{k_n}} = V_{GS} - V_{TN}$$

$$\rightarrow V_{GS} = V_{TN} \mp \sqrt{\frac{I_D}{k_n}}$$

$$= 2 \mp \sqrt{\frac{1}{2}} = 2 \mp 0.7$$

$$= \boxed{2.7} \text{ or } 1.3 \text{ V.}$$

$$V_G = 2.7 + 5 = 7.7 \text{ V. } \checkmark \quad \times$$

$$\rightarrow R_1 = \frac{25}{7.7} * 200k = 649 \text{ k}\Omega. \#.$$

$$\rightarrow R_2 :$$

$$R_i = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$200 = \frac{649 \cdot R_2}{649 + R_2}$$

$$\therefore R_2 = \frac{649 * 200}{649 - 200} = 289 \text{ k}\Omega. \#.$$

2] Common - Drain Amplifier :-


[Source Follower]

Note :-

C-D & C-C :- Voltage - Followers.
($V_o \approx V_i$)

C-B & C-G :- Current - Followers.
($I_o \approx I_i$)

EXA. :

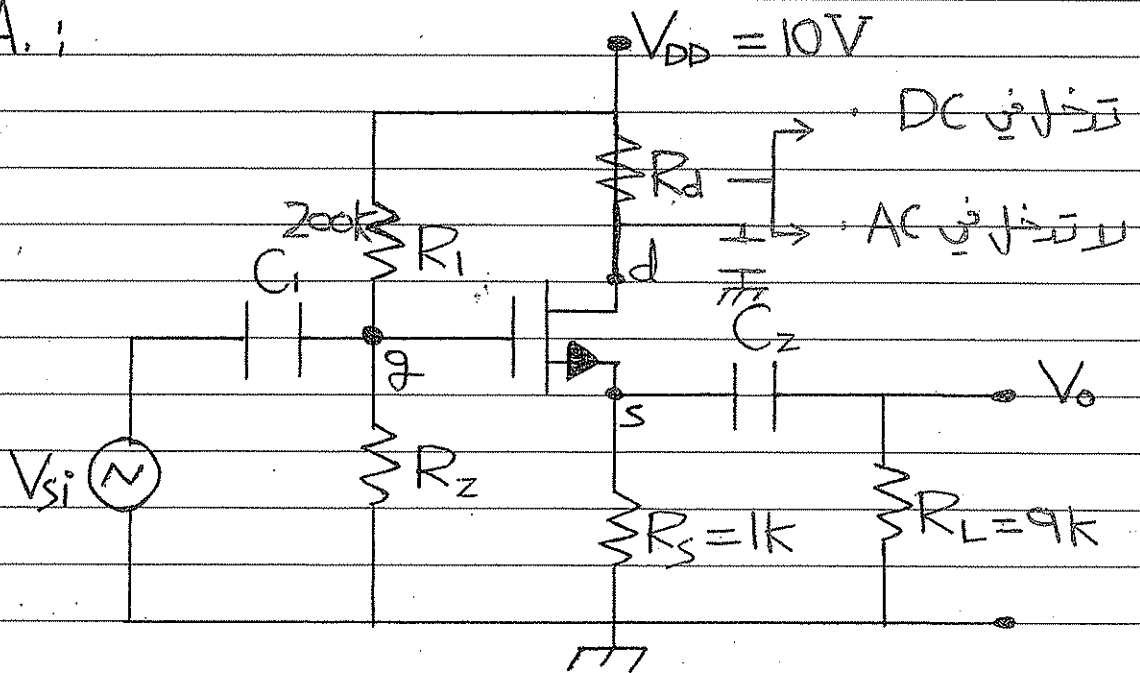

D → ground.

i/P : to gate. , O/P : from Source.

$$k_n = \frac{4 \text{ mA}}{\text{V}^2}, \quad V_{TN} = 1, \quad \lambda = 0.01 \text{ V}^{-1}$$


Given $V_S = 4 \text{ V}$:

1] Find V_{GSQ} , V_{DSQ} , R_2 ?

2] Draw A.C Eqnt. cct. & Find R_i, R_o, A_v .

Sol.

For DC analysis :- C : Open Cct.

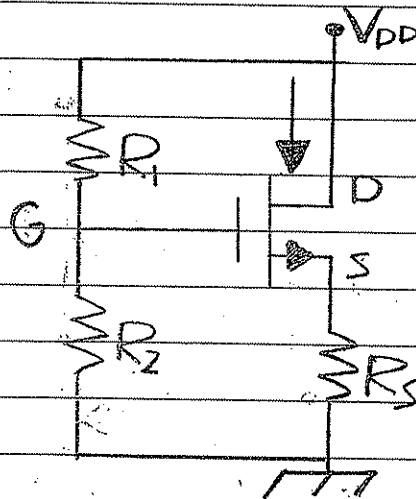

$$V_S = I_D R_S \rightarrow I_D = \frac{V_S}{R_S} = \frac{4}{1 \text{ k}} = 4 \text{ mA}$$

$$I_D = k_n (V_{GS} - V_{TN})^2$$

$$V_{GS} = V_{TN} \pm \sqrt{\frac{I_D}{k_n}} = 1 \pm \sqrt{\frac{4}{4}} = 2 \text{ V or } 0 \text{ V}$$

✓ X

$$V_{DS} = V_D - V_S = 10 - 4 = 6V. \quad ; \quad \boxed{V_{DD} = V_D}$$

$$V_{GS} = V_G - V_S \rightarrow V_G = V_{GS} + V_S$$

$$= 2 + 4 = 6V.$$


$$V_G = \frac{V_{DD} \cdot R_2}{R_1 + R_2}$$

$$R_2 = \frac{10 \cdot R_2}{200 + R_2} \rightarrow 10R_2 = 1200 + 6R_2$$

$$\therefore 4R_2 = 1200$$

$$R_2 = 300 \text{ k}\Omega.$$

For A.C analysis :-

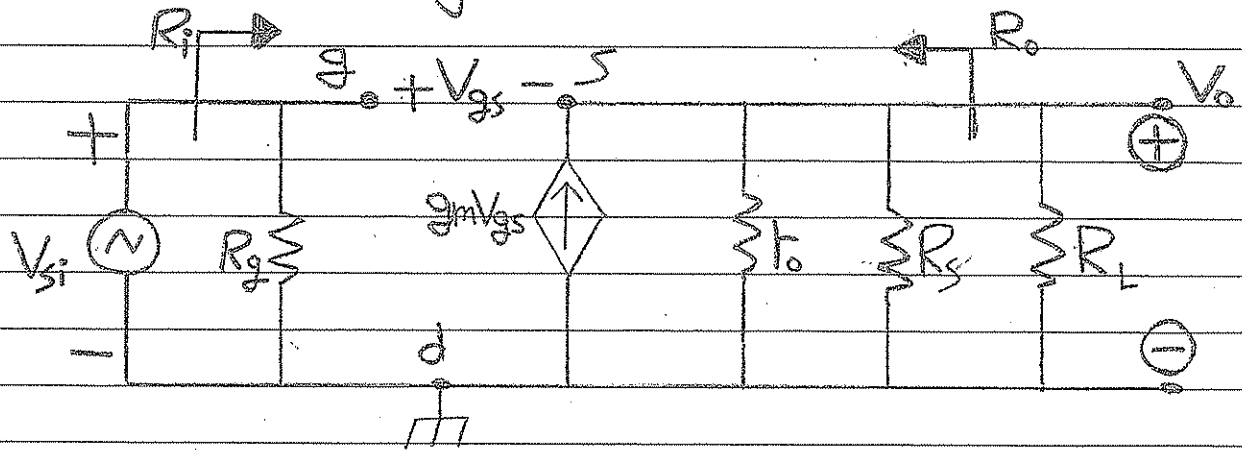

S.S.A.C Eqnt. CCT.

$$A_v = \frac{V_o}{V_{si}}$$

$$V_o = g_m V_{gs} R_L \quad ; \quad R_L = r_{o1} // R_S // R_L$$

$$-V_{si} + V_{gs} + V_o = 0$$

$$V_{si} = V_{gs} + V_o$$

$$\rightarrow V_{si} = V_{gs} + g_m V_{gs} R_L$$

$$\therefore A_v = \frac{V_o}{V_{si}} = \frac{g_m V_{gs} R_L}{V_{gs} (1 + g_m R_L)} = \frac{g_m R_L}{1 + g_m R_L} \quad \times$$

$$A_v = \frac{g_m R_L}{1 + g_m R_L} \quad ; \quad A_v < 1, \quad \phi = 0$$

$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{4 \times 4} = 8 \text{ mA/V}$$

$$R_L = r_o // R_S // R_L$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 4 \times 10^{-3}} = \frac{10^5}{4} = 25 \text{ k}\Omega$$

$$R_L = 25 \text{ k} // 1 \text{ k} // 9 \text{ k}$$


$$= 0.85 \text{ k}\Omega$$

$$A_v = \frac{8 * 0.85}{1 + (8 * 0.85)} = \frac{7}{8} \approx 0.88 \quad \#$$

$$R_i = R_g = R_1 // R_2$$

$$= 200 // 300 = 120 \text{ k}\Omega \quad \#$$

$$R_o = \frac{V_x}{I_x} \Big|_{V_{si}=0}$$

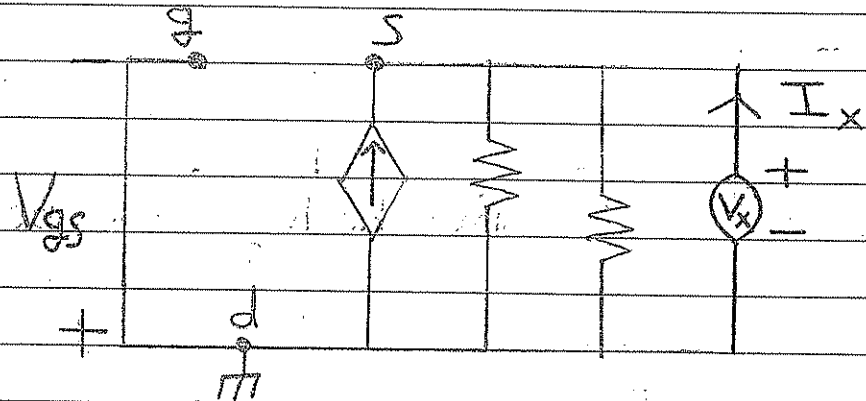

KCL at node (S) :-

$$I_x + g_m V_{gs} = \frac{V_x}{r_o} + \frac{V_x}{R_s}$$

but: When $V_{si} = 0 \rightarrow V_{gs} = -V_x$

$$I_x = V_x \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)$$

$$\frac{I_x}{V_x} = \frac{1}{R_o} = g_m + \frac{1}{r_o} + \frac{1}{R_s}$$

$$R_o = \frac{1}{g_m} // r_o // R_s$$

Law in general. ~~✘~~

$$R_o = \frac{1}{8 * 10^{-3}} // 25k // 1k$$

$$= 125 \Omega // 25k // 1k = 120 \Omega$$

$$A_v < 1$$

$$\phi = 0$$

$R_o \rightarrow$ Low.

$R_i = R_{Th} \rightarrow R_2, R_1$ (maybe high maybe low.)

$$* A_v = \frac{g_m R_L}{1 + g_m R_L}$$

if $g_m R_L \gg 1$ then $A_v \approx 1$

$$* V_o = V_{si}$$


So it's Source follower because V_i follow V_o in magnitude and ϕ .

* In General : MOSFET Ccts have

($A_v \rightarrow$ Low) if we compare it with BJT Ccts

3] Common-Gate Amplifier :

EXA. :

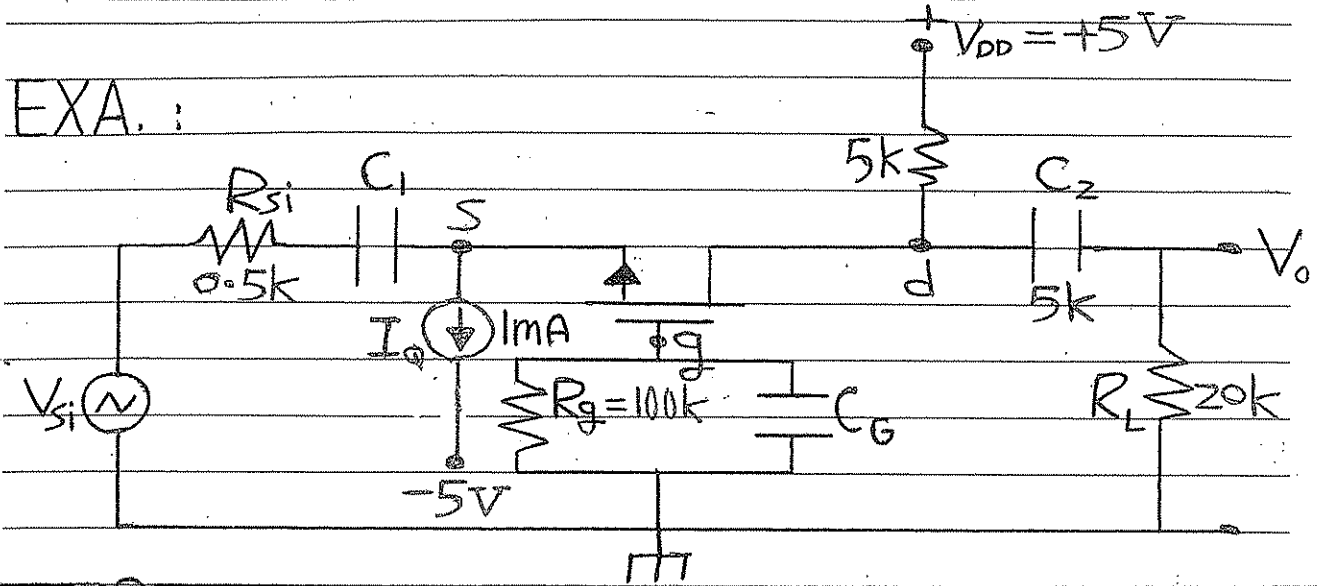

◆ R_g : To protect the gate from Static Charge.

$$V_g = I_g R_g = 0$$


بجانب أن تآون V_g (-) حثتآون
 V_{gs} (+) وتآون الأارة.

Bypass Cap. :- Because bypassing the AC signal to ground.

G → ground.

i/P to Source.

O/P from Drain.

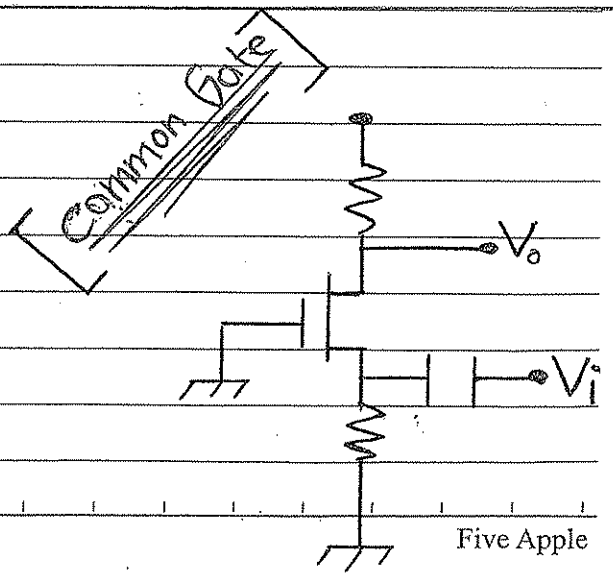

~~XX~~ D.C Analysis :-


Given :

$$K_n = 25 \mu\text{A}/\text{V}^2$$

$$V_{TN} = 1\text{V}$$

$$\frac{W}{L} = 80$$

$$\lambda = 0$$

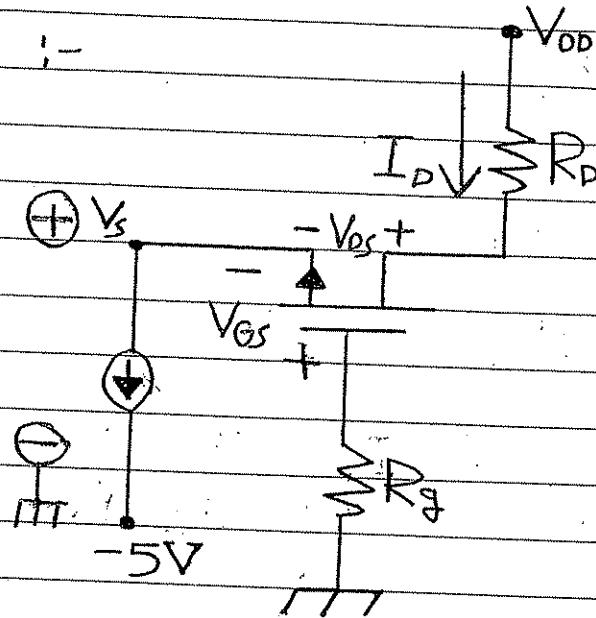

1) Find: V_{DS} , V_S , P_D

2) Draw AC Eqnt. CCT and find A_v , R_i , R_o , A_I .

Solution :-

For DC analysis :-

$$-V_{DD} + I_D R_D + V_{DS} + V_S = 0$$

$$V_{DS} = 5 - I_D R_D - V_S = 5 - (1 \times 5) - V_S$$

$$\rightarrow \boxed{V_{DS} = -V_S} = -V_S$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = -V_S \rightarrow \boxed{V_S = -V_{GS}}$$

$$V_{GS} = V_{TH} + \sqrt{\frac{I_D}{k_n}}$$

$$k_n = \frac{\mu_n \cdot C_{ox} \cdot W}{2L} = k_n \cdot \frac{W}{2L}$$

$$k_n = \mu_n \cdot C_{ox}$$

$$k_n = 25 \cdot \frac{80}{2} = 1000 \mu A/V^2$$

$$= 1 mA/V^2$$

$$V_{GS} = 1 \mp \sqrt{\frac{1m}{1m}} = 2V \text{ or } 0V$$

$$V_S = -V_{GS} = -2V \quad \#$$

$$V_{DS} = -(-2) = 2V \quad \#$$



$$\text{or: } V_{DS} = V_D - V_S$$

$$V_D = 5 - I_D R_D = 0$$

$$V_{DS} = -(-2) = 2V \quad \#$$

$$P_D = I_D * V_{DS} \quad \#$$

A.C analysis :-

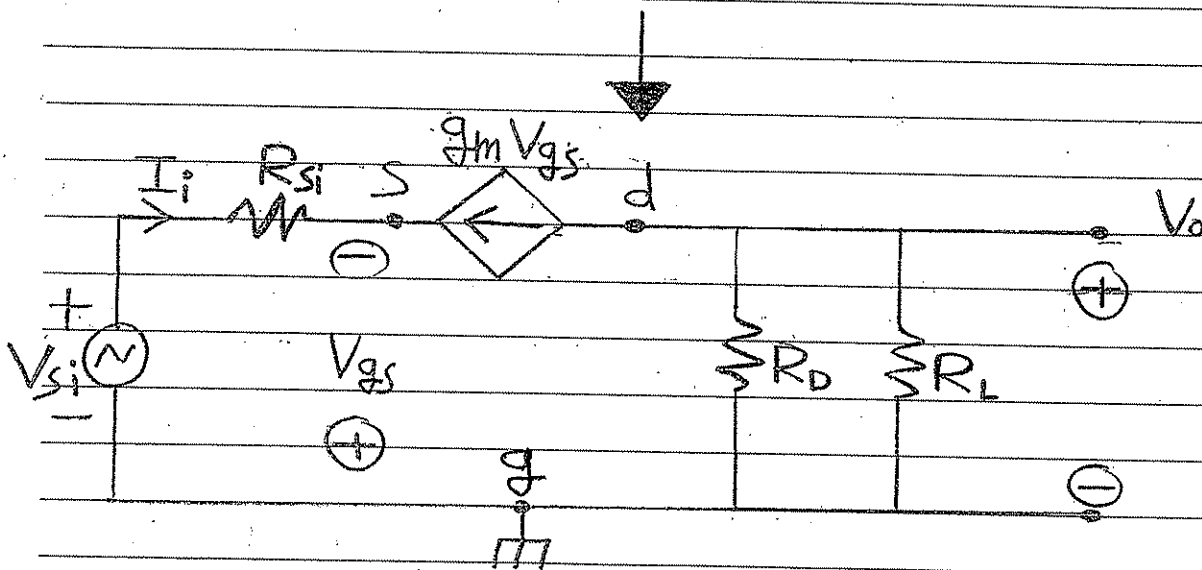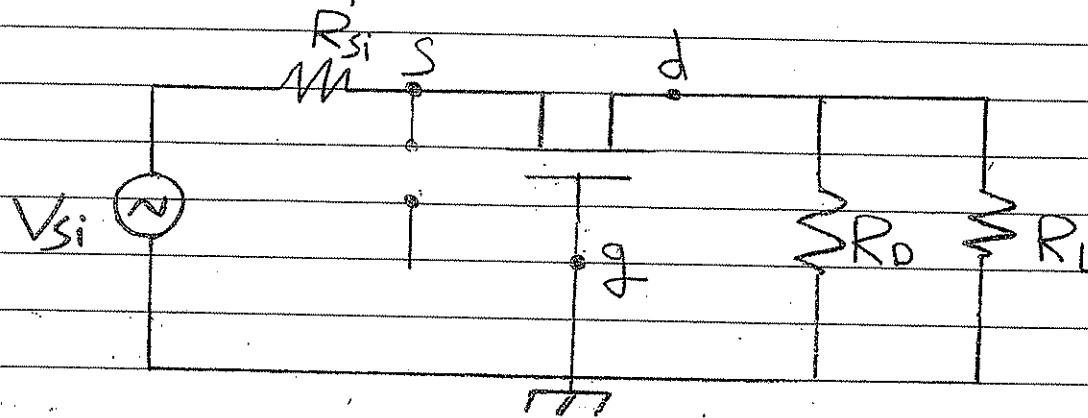

S.S.A.C Eqnt. Ckt.

$$A_v = \frac{V_o}{V_{s_i}}$$

$$V_o = -g_m (R_D // R_L) V_{g_s}$$

$$-V_{s_i} + I_i R_{s_i} - V_{g_s} = 0$$

$$I_i = -g_m V_{g_s}$$

$$-V_{si} - g_m V_{gs} R_{si} - V_{gs} = 0$$

$$V_{si} = -V_{gs} (1 + g_m R_{si})$$

$$\therefore A_v = \frac{V_o}{V_{si}} = \frac{-g_m (R_o // R_L) V_{gs}}{-V_{gs} (1 + g_m R_{si})}$$

$$A_v = \frac{g_m (R_o // R_L)}{1 + g_m R_{si}} \quad ; A_v > 1 \rightarrow \phi = 0^\circ \quad \#$$

$$g_m = 2\sqrt{k_n I_D} = 2\sqrt{1 \times 1} = 2 \text{ mA/V}$$

$$A_v = \frac{2 * (5 // 20)}{1 + 2(0.5)} = 4 \quad \#$$

$$R_o = \left. \frac{V_x}{I_x} \right|_{V_{si}=0}$$

$$R_o = R_D = 5 \text{ k}\Omega \quad \#$$

$$R_i = \frac{-V_{gs}}{I_i} = \frac{-V_{gs}}{-g_m V_{gs}} = \frac{1}{g_m} = \frac{1}{2 \text{ m}} = 0.5 \text{ k}\Omega = 500 \Omega \quad \#$$

* if there is (R_s) :

$$\therefore R_i = R_s // \frac{1}{g_m} \quad [\text{Law}]$$

* For NO R_L :

$$A_I = \frac{I_o}{I_i} \approx 1$$

$I_o \approx I_i$, C-G is Current follower.
(I_o follow I_i)

In Genetal:


$$A_I = \frac{g_m R_{Si}}{1 + g_m R_{Si}} \cdot \frac{R_D}{R_D + R_L}$$

Summary of Single Stage MOSFET Amp. :-

Amp.	A_V	A_I	ϕ	R_i	R_o
C.S (Basic)	> 1		180°	R_{TH}	moderate to high.
C.D	≤ 1		0°	R_{TH}	Low.
C.G	> 1	1	0°	Low	moderate to high.

Multi-Stage :-

1] Cascade Amp. :- [Series Connection]

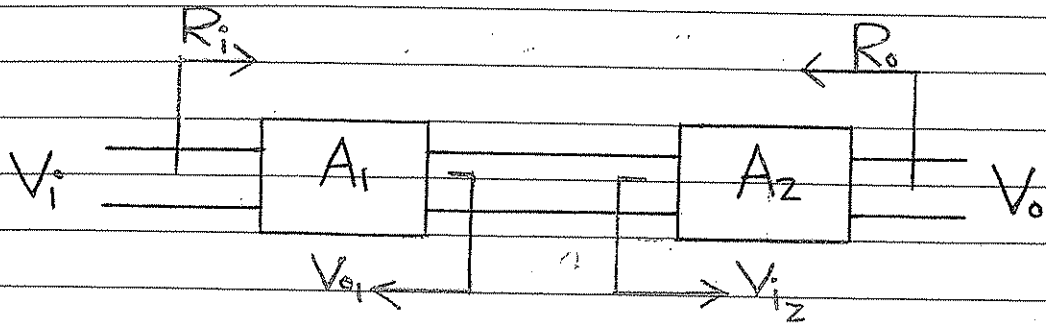

$$\# A_{v1} = \frac{V_{o1}}{V_i}$$

$$\# A_{v2} = \frac{V_o}{V_{i2}}$$



$$\# A_v = \frac{V_o}{V_i}$$

$$R_i = R_{i1}$$


$$R_o = R_{o2}$$

تمتد السماء ونظير النجوم في الفضاء

ففي كل بقعة كبريت ما هناك من يتمد في الفضاء

متساثلًا من احتمالية وجودك .

EXA.:

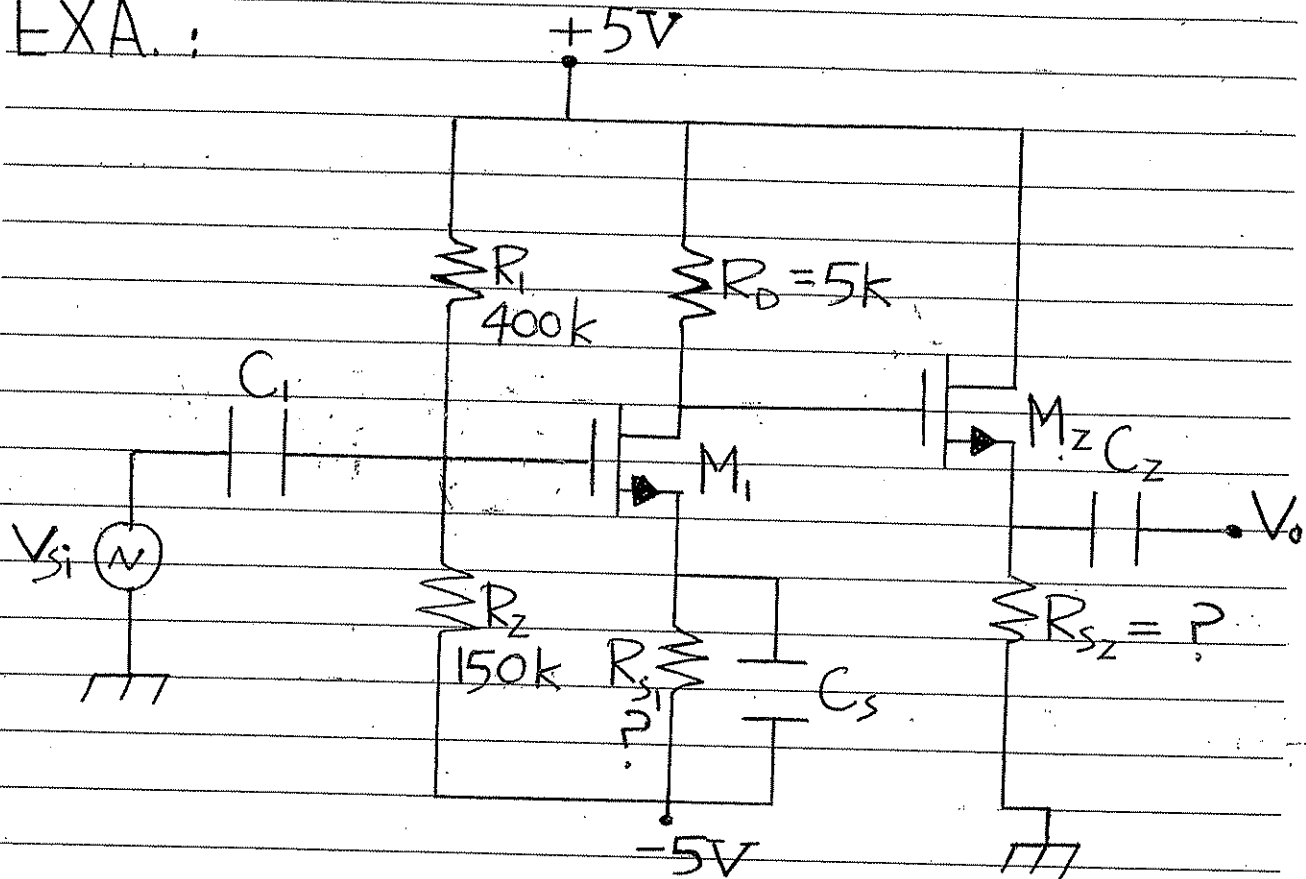

$$I_{D1} = 0.2 \text{ mA} \quad , \quad k_{n1} = 0.5 \text{ mA/V}^2$$

$$I_{D2} = 0.5 \text{ mA} \quad , \quad k_{n2} = 0.7 \text{ mA/V}^2$$

$$V_{TN} = 1V \quad , \quad \lambda_1 = \lambda_2 = 0$$

1) Find R_{S1} , R_{S2} .

2) Draw S.S.A.C Eqnt. CCT. and find A_v , R_i , R_o .

Sol i:-

1)
$$-V_{S1} + I_{D1} R_{S1} - 5 = 0$$


$$R_{S1} = \frac{5 + V_{S1}}{I_{D1}}$$

$$V_{GS1} = V_{G1} - V_{S1}$$

$$V_{S1} = V_{G1} - V_{GS1}$$

$$V_{G1} = \frac{5 \cdot 150}{550} + \frac{-5 \cdot 400}{550}$$
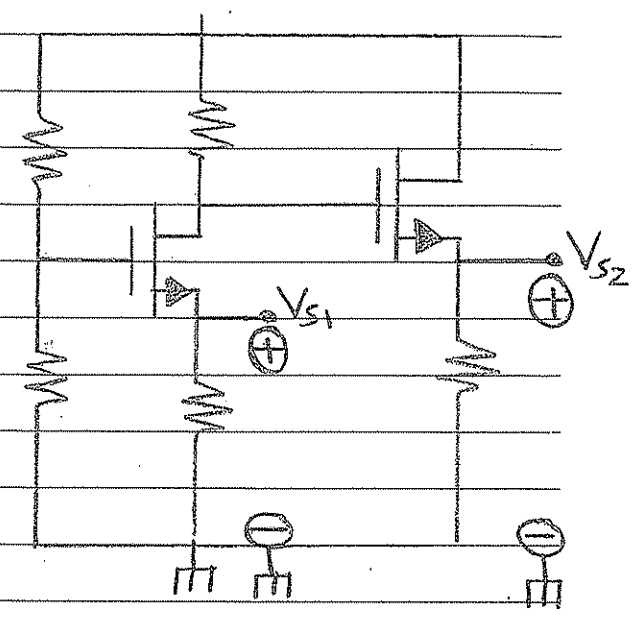
$$V_{GS1} = V_{TN} \pm \sqrt{\frac{I_{D1}}{K_{n1}}}$$




$$R_{S2} = \frac{V_{S2}}{I_{D2}}$$


$$V_{S2} = V_{G2} - V_{GS2}$$


$$V_{G2} = V_{D1} = 5 - (I_{D1} * R_D)$$
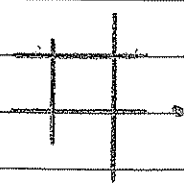
$$V_{GS2} = V_{TN} \pm \sqrt{\frac{I_{D2}}{K_{n2}}}$$



2) For AC analysis :-

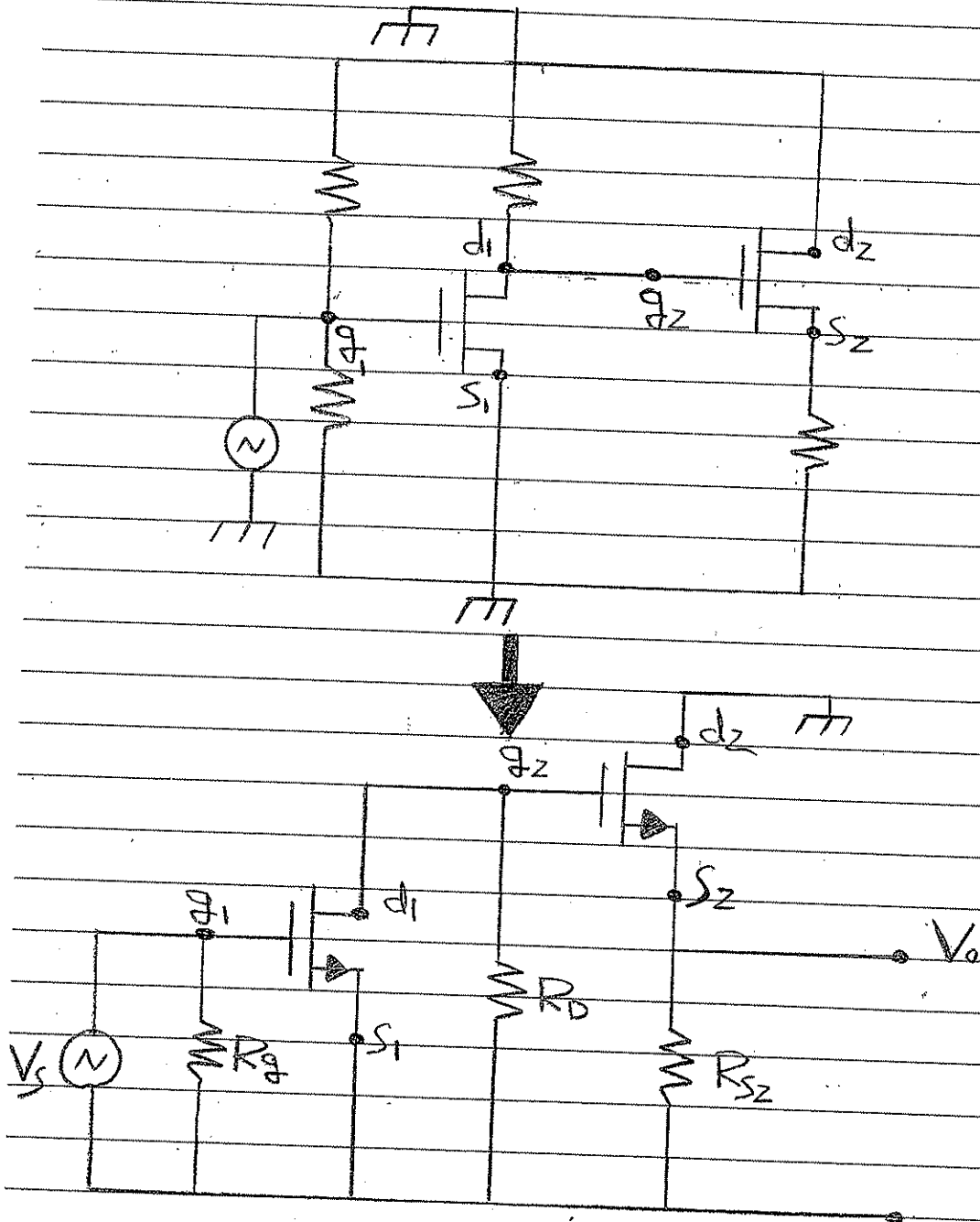

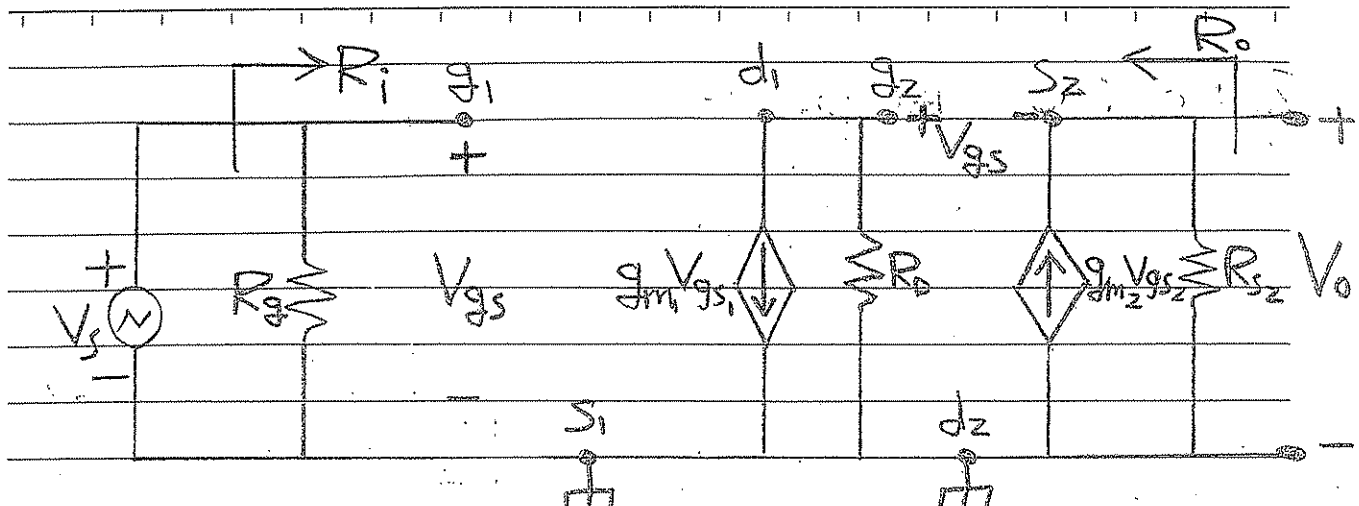

{ S.S.A.C Egnt. CCT. }

$$R_i = R_{i1} = R_g = R_1 // R_2$$

$$R_o = R_{o2} = \frac{1}{g_{m2}} // R_{S2}$$

$$A_v = \frac{V_o}{V_{s_i}} = \frac{V_o}{V_{o_1}} * \frac{V_{o_1}}{V_{s_i}} = A_{v_2} * A_{v_1}$$

$$\frac{V_o}{V_{o_1}} = \frac{g_{m2} R_{S2}}{1 + (g_{m2} R_{S2})} = A_{v_2}$$


$$\frac{V_{o_1}}{V_{s_i}} = \frac{-g_{m1} V_{gs1} R_D}{V_{gs1}} = -g_{m1} R_D = A_{v_1}$$

$$A_v = \frac{-g_{m1} R_D * g_{m2} R_{S2}}{1 + g_{m2} R_{S2}}$$

$$R_{i1} = R_g ; R_{i2} = \infty$$

2TCascode Amp. :-

EXA. :-

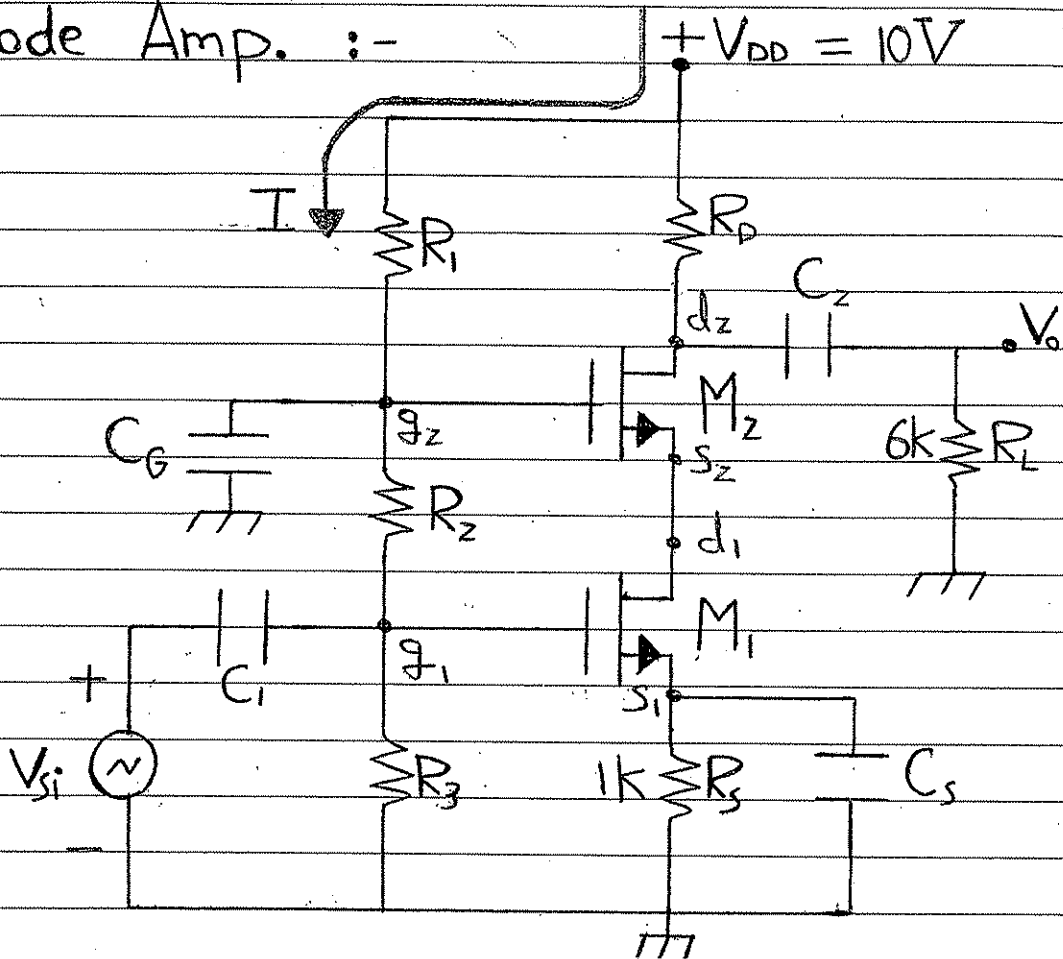

$$k_{n1} = k_{n2} = \frac{1 \text{ mA}}{V^2}$$

$$V_{TN1} = V_{TN2} = 1 \text{ V}$$

$$\lambda_1 = \lambda_2 = 0$$

1) Design the CCT. to have $I_D = 1 \text{ mA}$,

$V_{DS1} = V_{DS2} = 3 \text{ V}$ and $I = 2\% I_D$.


2) Draw S.S.A.C Eqnt. CCT. and find:

R_i, R_o, A_v .

Sol.:

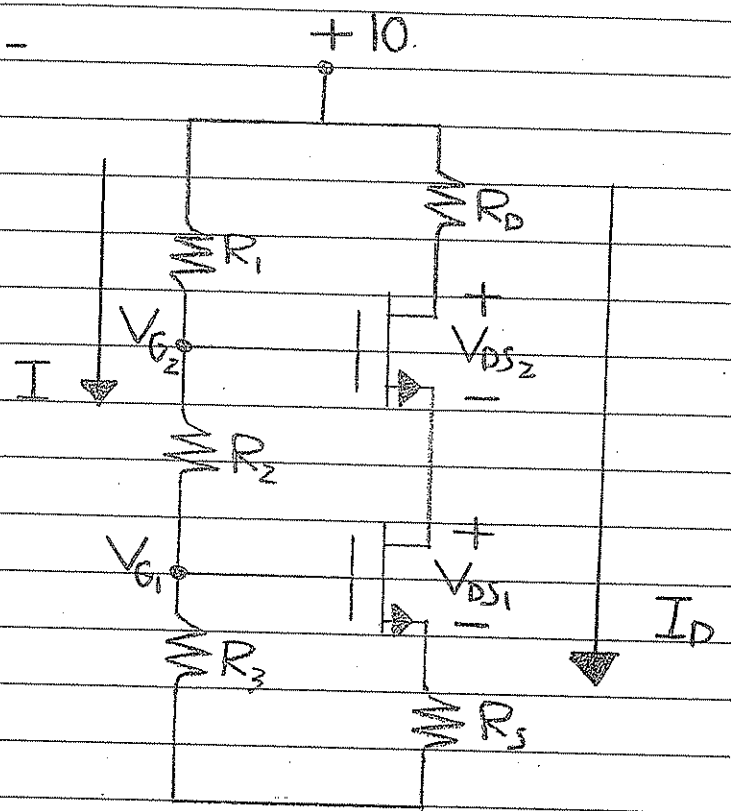1) For D.C analysis :-

$I = 2\% I_D$
$= 2 * 1 / 100$
$= 0.02 \text{ mA}$



$$R_D = \frac{10 - V_{DS1} - V_{DS2} - I_D R_S}{I_D}$$

$$= \frac{10 - 7}{1 \text{ m}}$$

$$= 3 \text{ k}\Omega$$

$$R_3 = \frac{V_{G1}}{I} \quad , \quad R_2 = \frac{V_{G2} - V_{G1}}{I} \quad , \quad R_1 = \frac{10 - V_{G2}}{I}$$

$$* V_{G1} = V_{GS1} + I_D R_S$$

$$= V_{GS1} + 1$$

$$V_{GS1} = V_{TN1} + \sqrt{\frac{I_D}{k_n}} = 1 \pm \sqrt{1} = 2V \text{ or } 0V$$

$$\rightarrow V_{GS1} = V_{GS2} = 2V. \quad \therefore V_{G1} = 2 + 1 = 3V.$$



$$R_3 = \frac{3}{0.02} = 150 \text{ k}\Omega.$$

$$V_{G2} = V_{GS2} + V_{DS1} + I_{D1} R_S$$

$$= 2 + 3 + 1 = 6V.$$

$$R_2 = \frac{6 - 3}{0.02} = 150 \text{ k}\Omega. \quad ; \quad R_1 = \frac{10 - 6}{0.02} = 200 \text{ k}\Omega.$$

2) For AC analysis:-

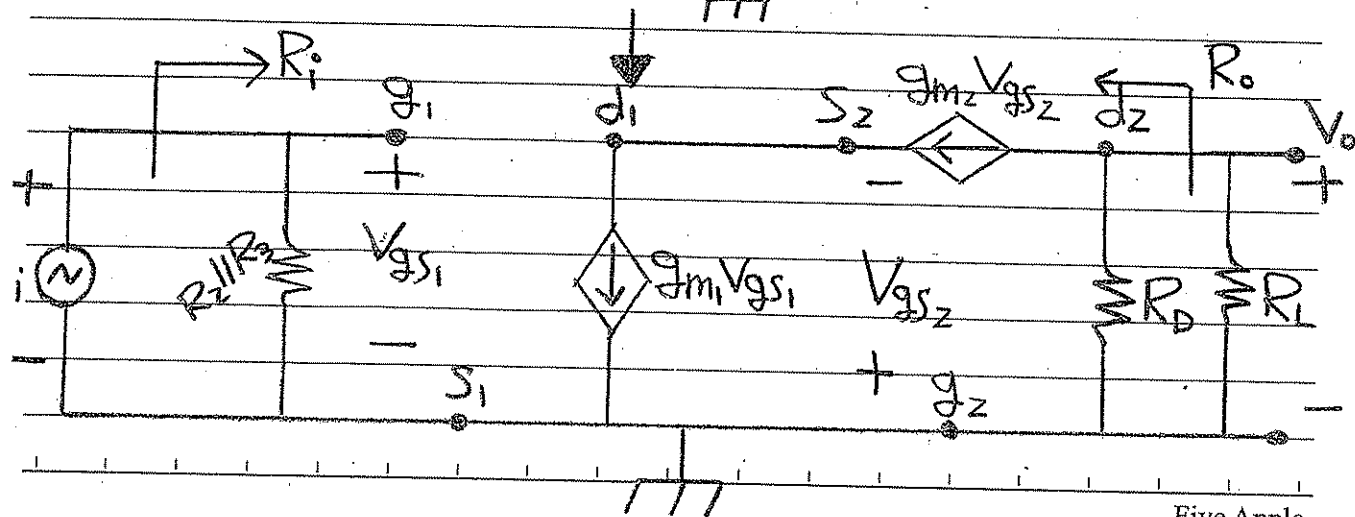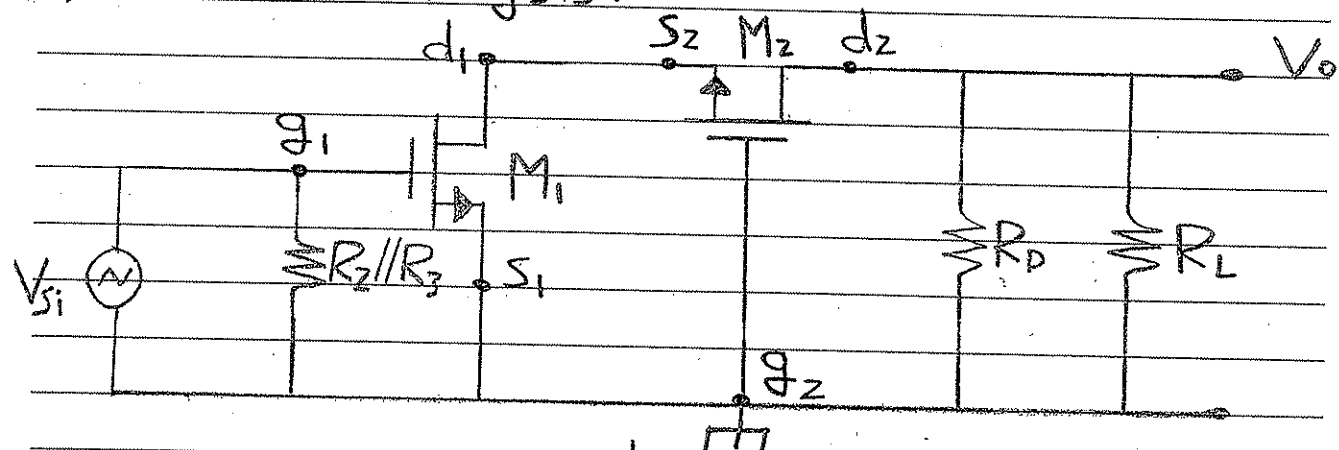

$$R_i = R_2 // R_3 = 75 \text{ k}\Omega$$

$$R_o = R_D = 3 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_{s_i}} = \frac{V_o}{V_{g_{s_1}}}$$

$$A_v = -g_{m_1} V_{g_{s_1}} (R_D // R_L)$$

$$A_v = -g_{m_1} (R_D // R_L)$$

$$\rightarrow A_v = -2 (3 // 6)$$

$$= -4$$



$$g_{m_1} = 2 \sqrt{1 \times 1} = 2 \text{ mA/V}$$

$$R_{o_1} = \infty$$

$$R_{i_2} = \frac{1}{g_{m_2}}$$


Handwritten text on lined paper, consisting of approximately 30 lines of illegible cursive script.

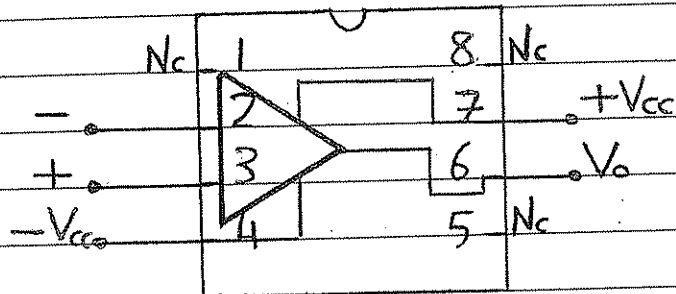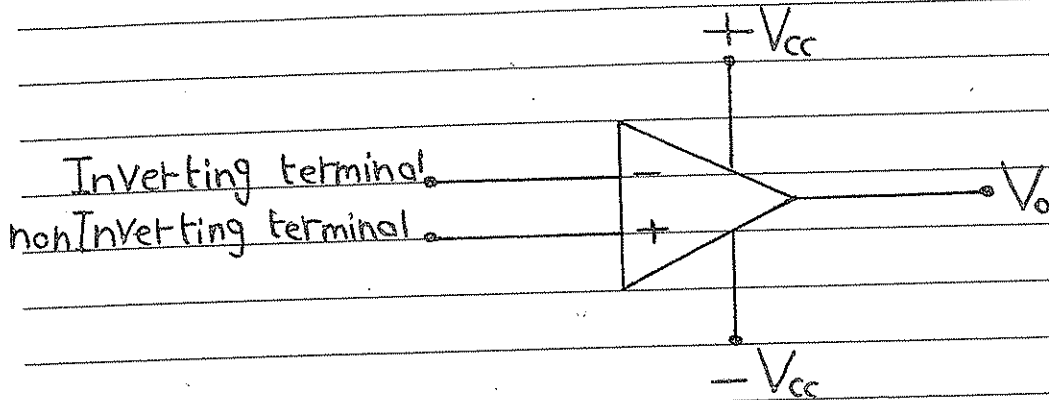Chapter (13) :- Operational Amplifier :- (OP-Amp.)




Nc: Not Connected

741

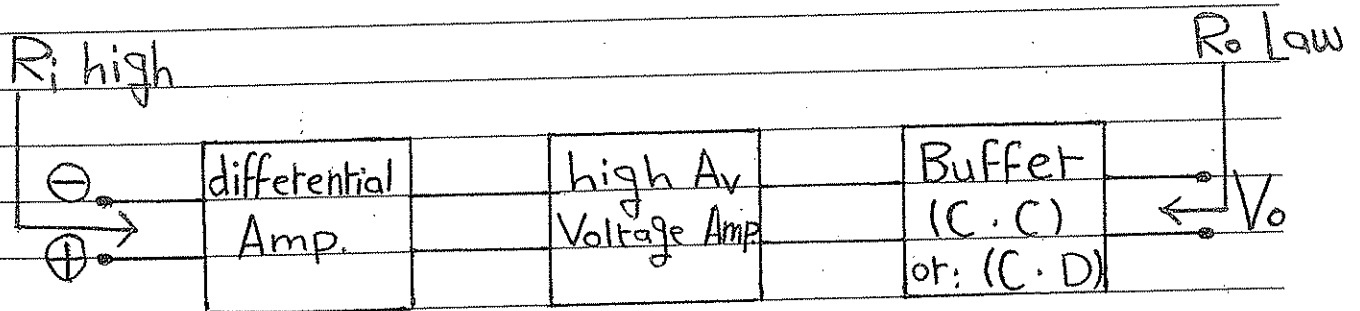

Block diagram for Simple OP - Amp.

1) $[R_i \text{ high}]$: Why ?

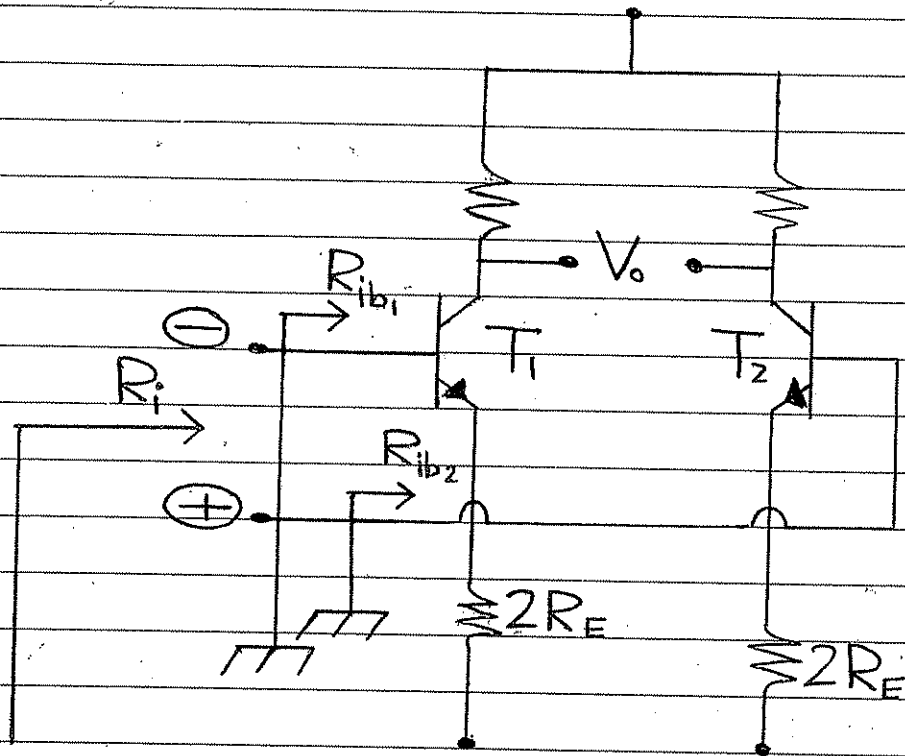

$$R_{ib1} = R_{ib2} = (\beta + 1) 2R_E + r_{\pi}$$

$$R_i = R_{ib1} + R_{ib2}$$


$$= 4(\beta + 1)R_E + 2r_{\pi}$$

$R_i \rightarrow \text{high}$

#


2) $[A_v \text{ high}]$. #

BJT :

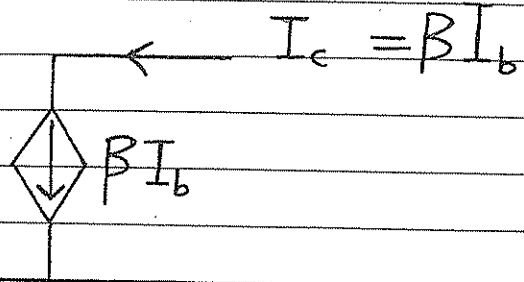


Current - Controlled Current Source.

FET :

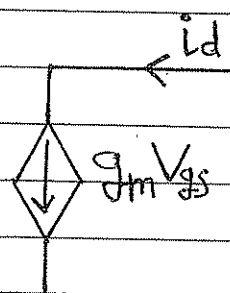

Voltage - Controlled Current Source.

OP-Amp. :

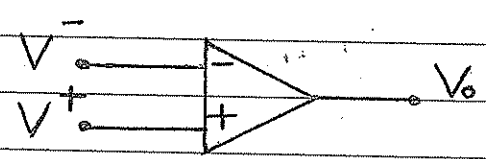

Voltage - Controlled Voltage Source.

$$V_o = A(V^+ - V^-) \longrightarrow V_o = AV_d$$

V_d : differential Voltage.

$$V_d = V^+ - V^-$$

OP-Amp. is very high gain multistage Voltage Amplifier.

✱ Ideal C/C :-


1) $A_o = \infty$

↳ Open-loop Voltage gain.
(device without connection)

2) $R_{in} = \infty$ (biasing Current $I^+ = I^- = 0$)

3) $R_o = 0$

4) Bandwidth (BW) = ∞

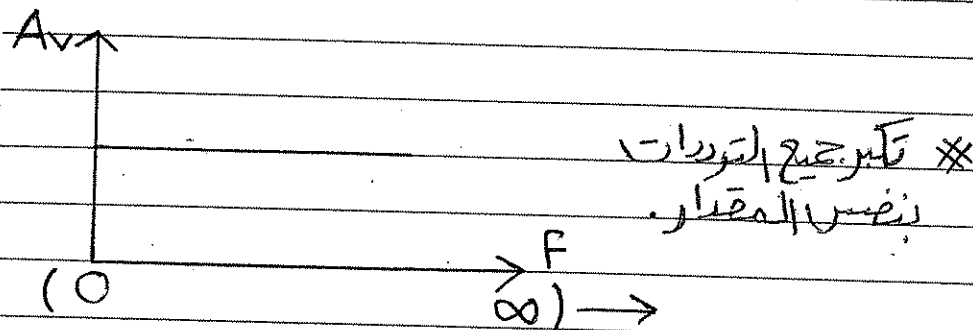

5) Perfect balance ;

$$V_o = 0 \text{ when } V^+ = V^-$$

$$V_o = A_o (V^+ - V^-)$$

~~NON~~ Ideal C/C :- [Real op-Amp.]

		741 (BiPolar op-Amp.)	CA3140
1)	A_o	2×10^5	10^4
2)	R_i	$2M\Omega$	$10^6 M\Omega$
3)	R_o	60Ω	
4)	Bw	$1MHz$	$5M$
5)	V_{off}	$10\mu V$	

↳ Voltage offset.

مقدار الفولتية الزائدة ونقصها
على أحد أطراف ال OP.AMP.
لتصبح $(V_o = 0)$.

ال OP.AMP. الحديث مستقر ذاتيا.


~~✖~~ Transfer C/C :-

$$V_o = A_o (V^+ - V^-) = A_o \cdot V_d$$

$$V_{o_{max}} = \pm V_{cc}$$

$$= A_o \cdot V_d$$
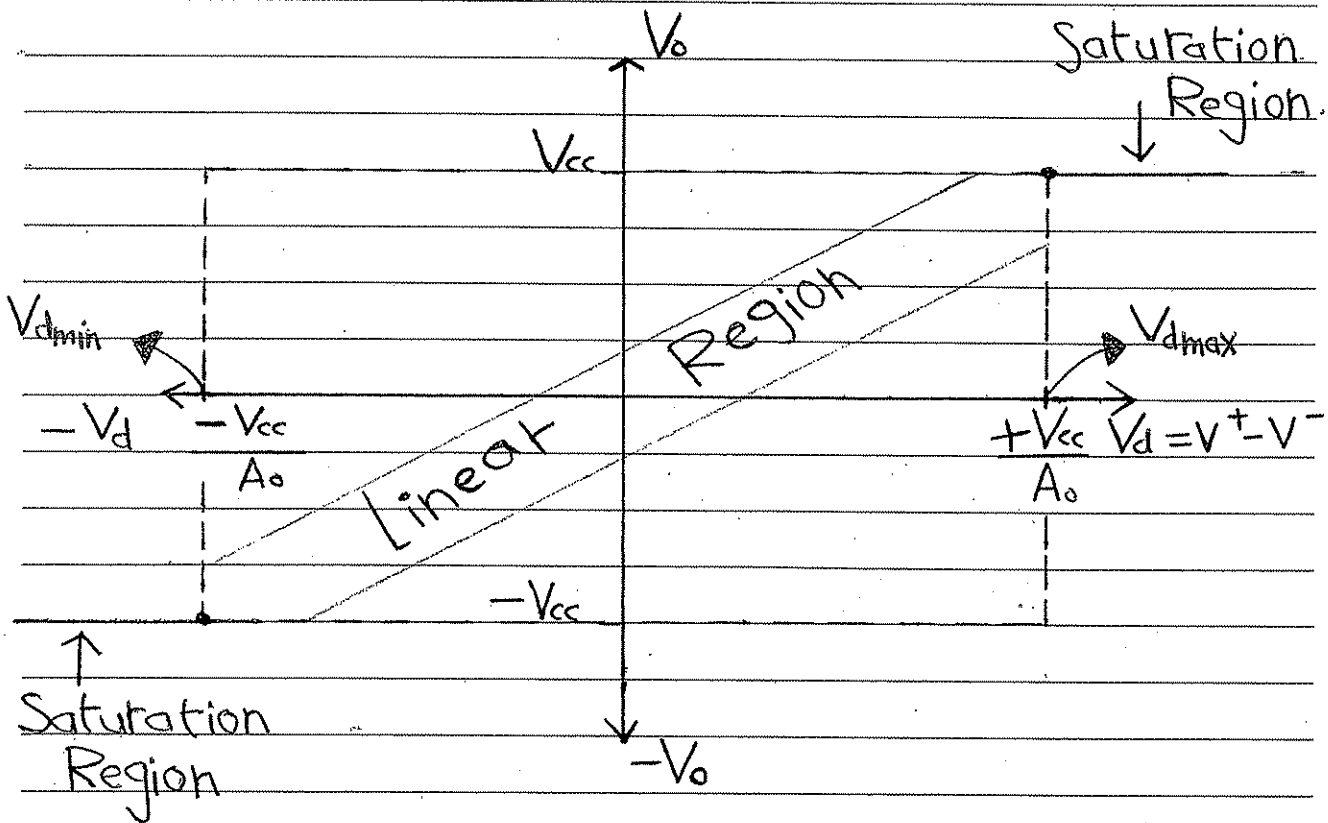
$$\therefore V_{d_{max}} = \frac{\pm V_{cc}}{A_o}$$



Operating Regions :-

1) Linear Region :-

$$V_o = A_o \cdot V_d$$

$$\frac{-V_{cc}}{A_o} < V_d < \frac{+V_{cc}}{A_o}$$

2) Saturation Region :-

$$V_o = +V_{cc}$$


i] If $V_d > \frac{+V_{cc}}{A_o}$ then :-

$$V_o = +V_{cc}$$

ii] If $V_d < \frac{-V_{cc}}{A_o}$ then :-


$$V_o = -V_{cc}$$

* Eqnt. CCT. of OP-Amp. :-

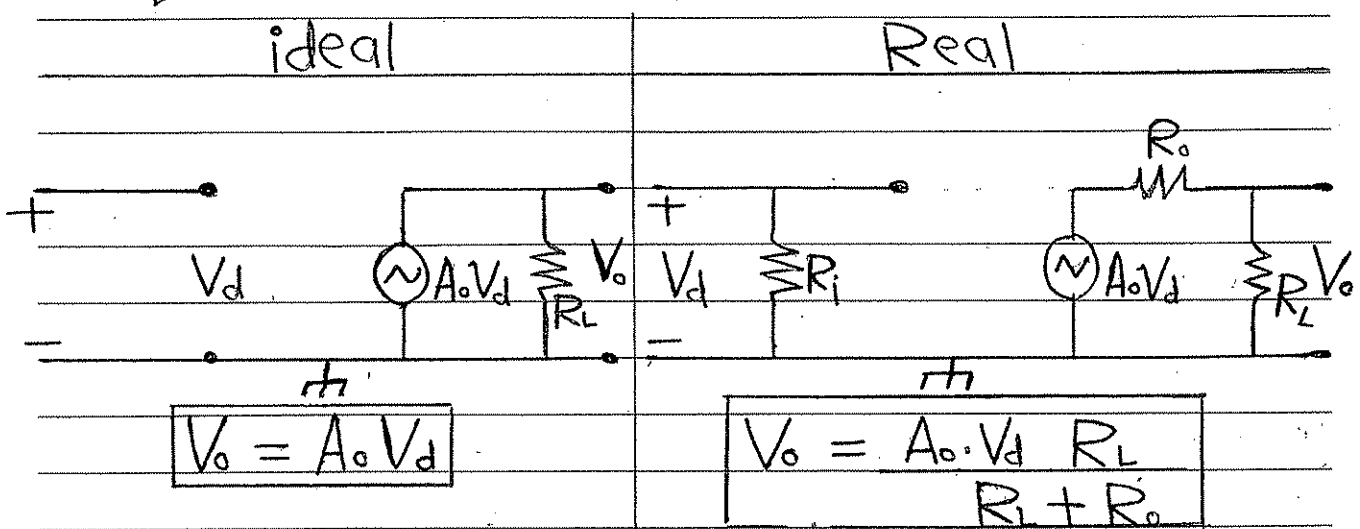


* V_0 independant on R_L * V_0 depends on R_L .

Voltage Amp. In general:

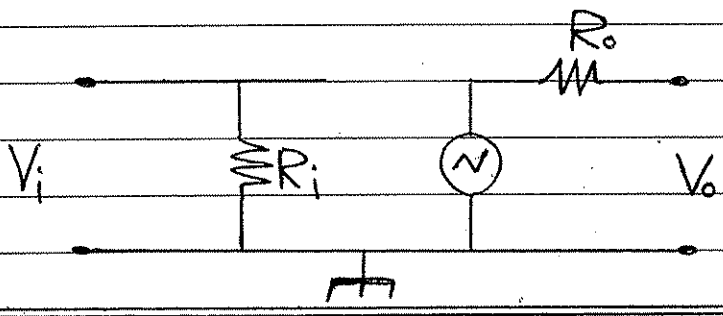

Applications of Op-Amp. :-

1) Inverting Amp. :-

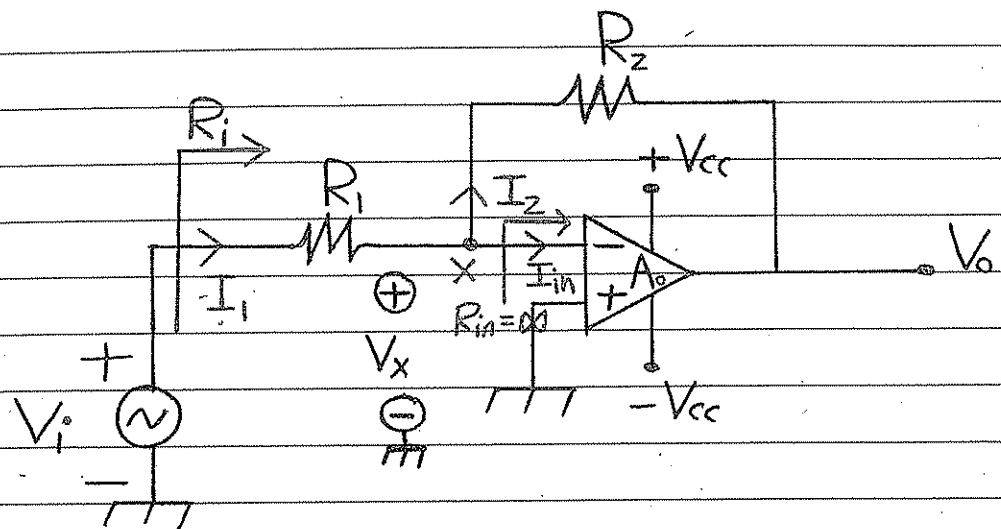

A_o : Open loop cct.

KCL at node X :-

$$I_1 = I_2 + I_{in}$$

$$\frac{V_i - V_x}{R_1} = \frac{V_x - V_o}{R_2} + I_{in}$$

Assume Ideal op-Amp. :

→ $I_{in} = 0$ ($R_{in} = \infty$)

→ $A_o = \infty$

$$V_o = A_o (V^+ - V^-) \Rightarrow V^+ - V^- = \frac{V_o}{A_o} = 0$$

$$V^+ = V^- = 0 \text{ (Virtual ground)}$$

$$V_x = V^- = V^+ = 0$$

$$\frac{V_i}{R_1} = -\frac{V_o}{R_2}$$

$$V_o = -\frac{R_2}{R_1} V_i$$

$$\frac{V_o}{V_i} = A_v = -\frac{R_2}{R_1}$$

→ Closed Loop gain of the cct.

$$R_i = \frac{V_i}{I_i} \quad ; R_i \text{ for the cct.}$$

$$\rightarrow -V_i + I_i R_1 + V_x = 0$$

$$V_i = I_i R_1$$

$$R_i = \frac{I_i R_1}{I_i} \rightarrow \boxed{R_i = R_1} \quad \#$$

EXA :-

1) Design an Inverting Amp. to have

$$A_v = -100 \quad \text{and} \quad R_i = 1 \text{ k}\Omega$$

2) Draw $V_o(t)$ when $V_{cc} = \pm 15V$ and V_i is :
 a) $0.1 \sin \omega t (V)$
 b) $0.2 \sin \omega t (V)$



Sol.:

1) $R_1 = R_2 = 1k\Omega$


$A_v = -\frac{R_2}{R_1} \Rightarrow -100 = -\frac{R_2}{1k} \Rightarrow R_2 = 100k\Omega$

2) a) $V_o = A_v \cdot V_i$ $A_v = \frac{V_o}{V_i}$
 $= -100 \cdot (0.1 \sin \omega t)$
 $= -10 \sin \omega t (V)$

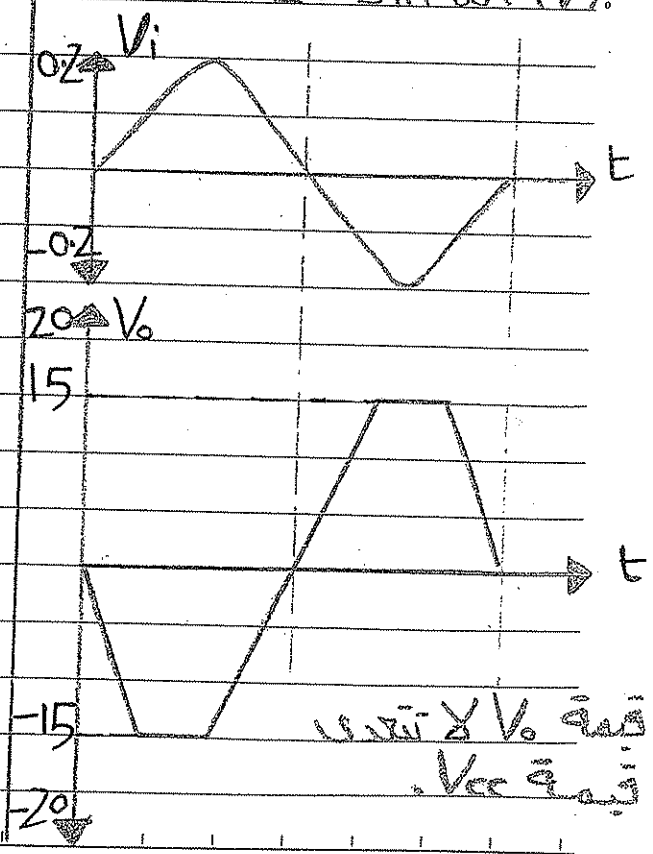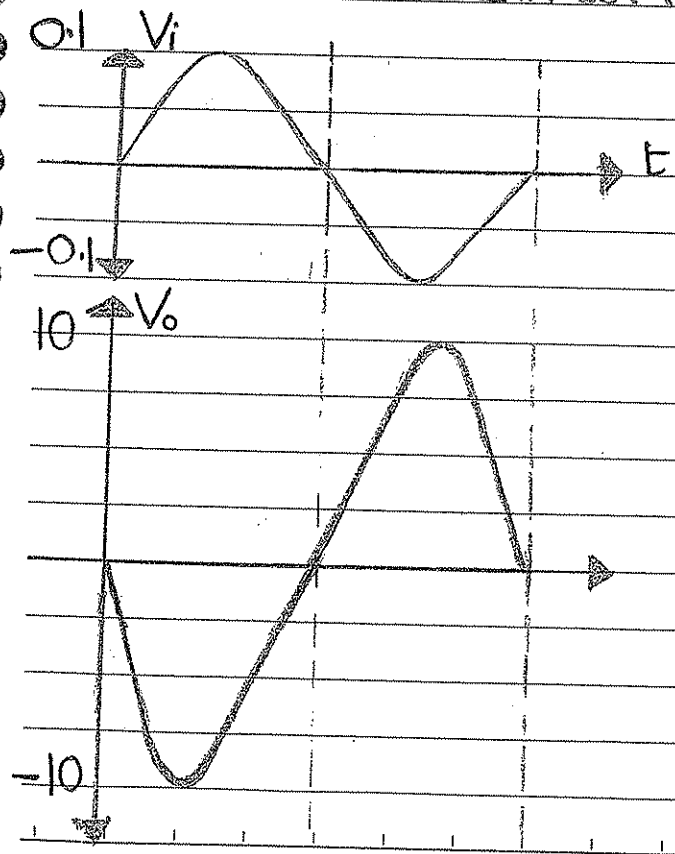b) $V_o = A_v \cdot V_i$
 $= -100 (0.2 \sin \omega t)$
 $= -20 \sin \omega t (V)$



EXA :-

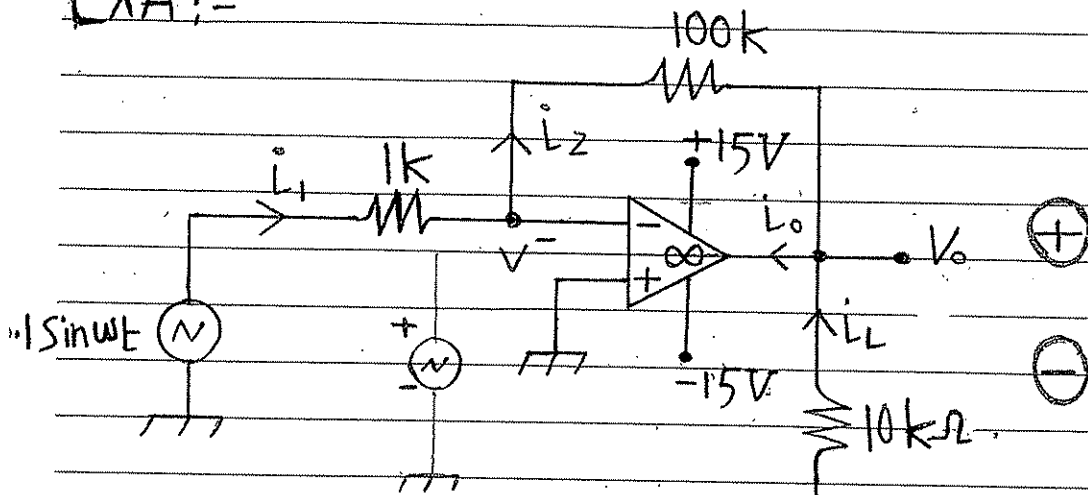

Calculate and Draw I_1 , I_2 , I_L .

Sol. :-

$$-V_i + I_1 R_1 + V^- = 0 \quad (V^- = V^+ = 0 \text{ V.G.})$$

$$I_1 = \frac{V_i}{R_1} = \frac{0.1 \sin wt (V)}{1k} = 0.1 \sin wt \text{ mA.} \quad \#$$

$$I_1 = I_2 + I_{in} \rightarrow 0$$

$$I_1 = I_2 = 0.1 \sin wt \text{ mA.} \quad \#$$

$$V_o = -\frac{R_2}{R_1} V_i$$

$$= -\frac{100}{1} (0.1 \sin wt)$$

$$= -10 \sin wt (V). \quad \#$$

$$i_L = \frac{0 - V_o}{R_L} = -\frac{(-10 \sin \omega t)}{10 \text{ k}} = 1 \sin \omega t \text{ (mA)} \quad \#.$$


$$i_o = i_2 + i_L = 1.1 \sin \omega t \text{ (mA)}. \quad \#.$$

∴ Op. Amp. is Sink Current.

↓
تسبب تيار

* $R_L \uparrow$, $i_L \downarrow$, i_1 , i_2 , V_o .
لنتاثير

2) Inverting Summing Amp :-

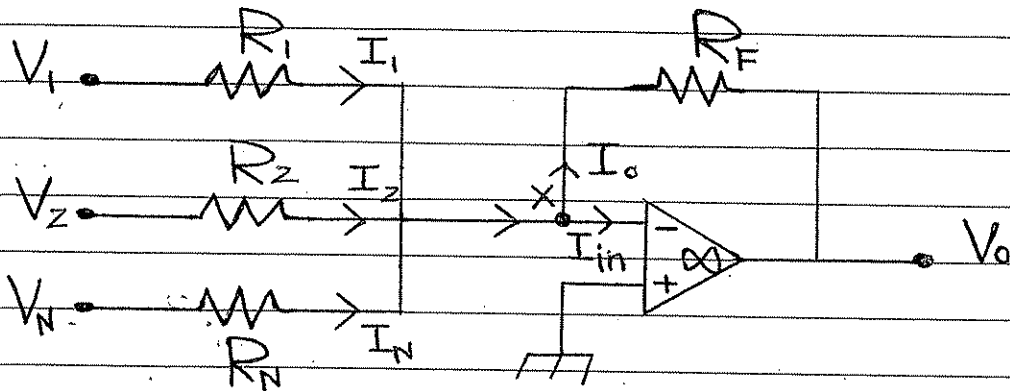

KCL at node X :-

$$I_1 + I_2 + \dots + I_N = I_o + I_{in}$$

$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} + \dots + \frac{V_N - V_x}{R_N} = \frac{V_x - V_o}{R_F} + I_{in}$$

But for ideal op_Amp. :

$$V_x = V = V' = 0 \text{ (Virtual ground)}$$

$$I_{in} = 0 \text{ (} R_i = \infty \text{)}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_N}{R_N} = \frac{V_o}{R_F}$$

$$\therefore V_o = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \dots + \frac{R_F}{R_N} V_N \right)$$

Special Case : When $[R_1 = R_2 = R_N = R]$:

$$V_o = \frac{R_F}{R} (V_1 + V_2 + \dots + V_N) \quad \#$$

$$\times \times V_o = -(5V_1 + 10V_2 + 15V_3)$$

$$\left[\begin{array}{ccc} R_F = 5 & , & R_F = 10 & , & R_F = 15 \\ R_1 & & R_2 & & R_3 \end{array} \right]$$

$$\times \times V_o = -10(V_1 + V_2 + V_3)$$

$$\left[\begin{array}{cccc} R_F = R_F = R_F = R_F = -10 \\ R_1 & R_2 & R_3 & R \end{array} \right]$$

Singhals can be D.C or A.C

دع ايتسامتك اول ملامحك (: فري لك حبة وفي الدين

حبة وفي القلب سعادة .

EXA.: For the CGT. Shown ;

$$R_1 = 1k, R_2 = 2k, R_3 = 3k ; R_F = 6k\Omega$$

$$V_1 = 1V \text{ d.c}$$

$$V_2 = -2V \text{ d.c}$$

$$V_3 = 2 \sin \omega t (V).$$


Calculate and Draw V_o ?

Sol.


$$V_o = - \left(\frac{R_F V_1}{R_1} + \frac{R_F V_2}{R_2} + \frac{R_F V_3}{R_3} \right)$$

$$= - \left[\frac{6}{1} (1) + \frac{6}{2} (-2) + \frac{6}{3} (2 \sin \omega t) \right]$$

$$= -6 + 6 - 4 \sin \omega t (V).$$

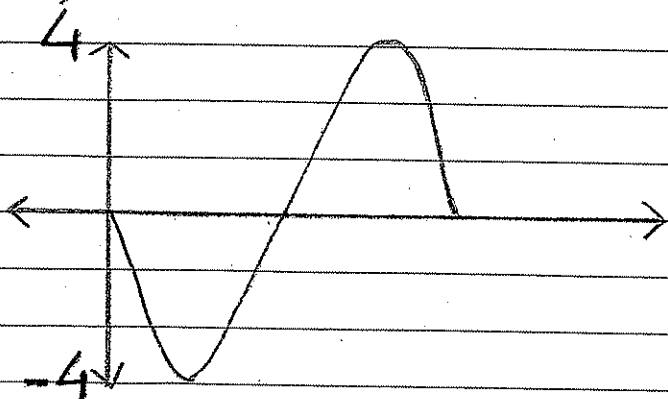

3) NON Inverting Amp. :-

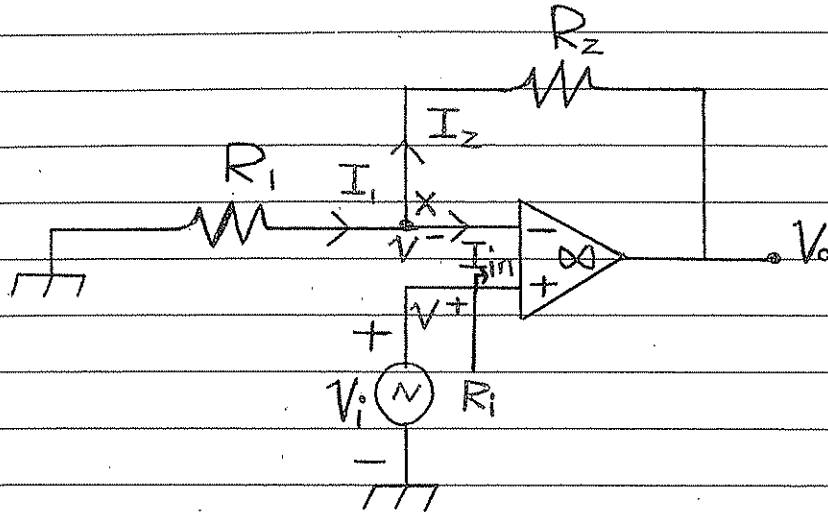

At node X :-

$$I_1 = I_2 + I_{in}$$

$$0 - \frac{V_x}{R_1} = \frac{V_x - V_o}{R_2} + I_{in}$$

But for Ideal OP-Amp. :-

$$I_{in} = 0 \quad (R_i = \infty)$$

$$V^+ = V^- = V_x = V_i \quad (\text{Virtual Short})$$

$$\frac{V_o}{R_2} = \frac{V_i}{R_1} + \frac{V_i}{R_2}$$


$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$

$$\frac{V_o}{V_i} = A_v = 1 + \frac{R_2}{R_1} \quad \#$$



Close loop Voltage gain.

$$R_i = \infty$$

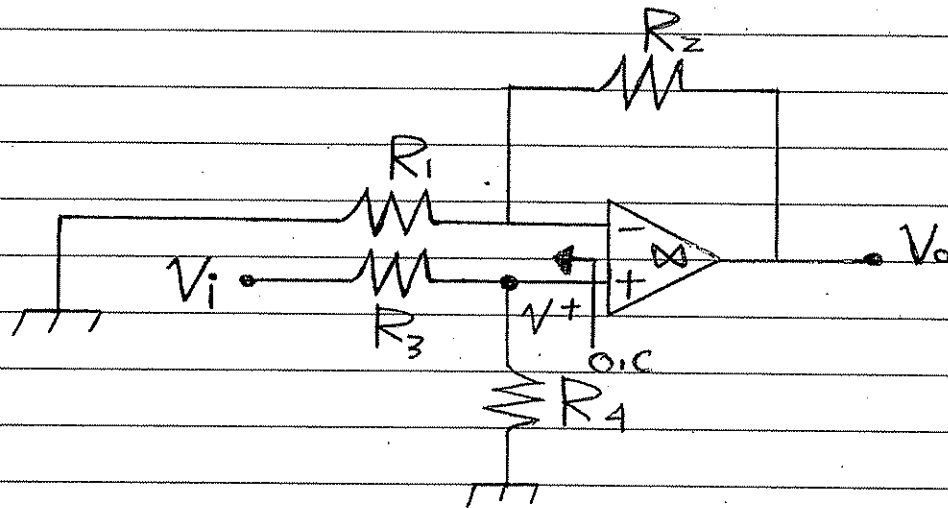


$$V_o = \left(1 + \frac{R_2}{R_1}\right) V^+$$

$$V^+ = V_i \frac{R_4}{R_4 + R_3}$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i \frac{R_4}{R_3 + R_4}$$

$$\frac{V_o}{V_i} = A_v = \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} \quad \#$$

EXA. :- Assume ideal Op-Amp. :-

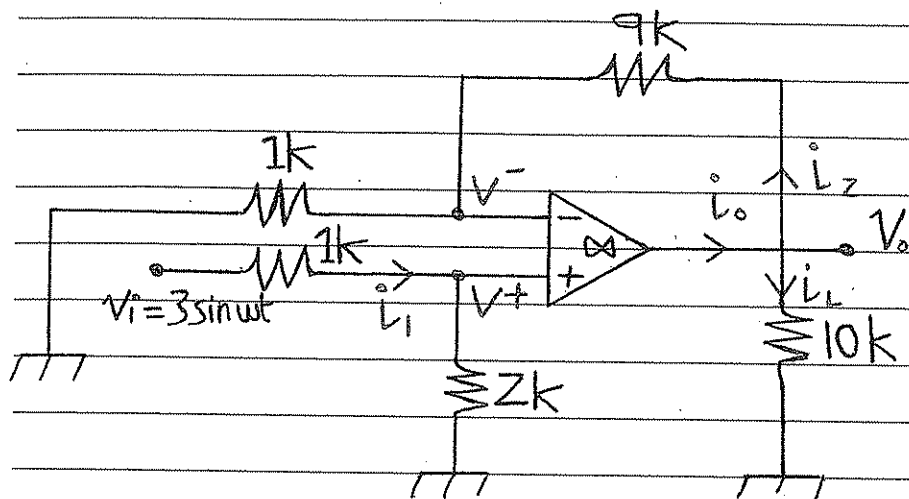

Calculate and Draw $V_0(t)$, $i_0(t)$, $i_L(t)$, $i_1(t)$, $i_2(t)$.

$$\text{Sol. :- } V_0 = (1 + \frac{9}{2}) V^+$$

$$V^+ = V_i \times \frac{2}{1+2} = \frac{2}{3} V_i$$

$$V^+ = \frac{2}{3} (3 \sin wt)$$

$$V^+ = 2 \sin wt \text{ (V)}$$

$$\therefore V_0 = 10 (2 \sin wt) = 20 \sin wt \text{ (V)}$$

$$i_L = \frac{V_0}{R_L} = 2 \sin wt \text{ (mA)}$$

$$i_2 = \frac{V_0}{9+1} = 2 \sin wt \text{ (mA)}$$

$$I_o = I_z + I_L$$

$$= 2 \sin(\omega t) + 2 \sin(\omega t) = 4 \sin \omega t \text{ (mA)}$$


$$I_i = \frac{V_i}{1+2} = \sin \omega t \text{ (mA)} \quad \#$$

OP-Amp \rightarrow Source Current.

4) Voltage-Follower

[Buffer] :-

* Special case of non-Inverting Amp. :

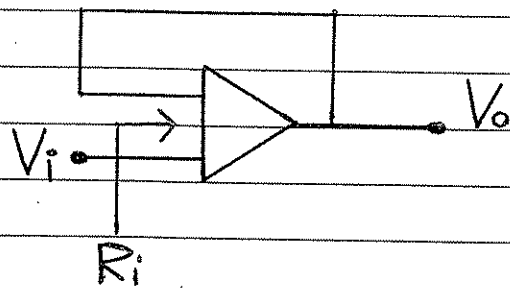


$$A_v = \frac{V_o}{V_i} = 1 + \frac{R_z}{R_i} = 1$$

$$V_o = V_i$$

$$A_v = 1, \quad \theta = 0^\circ, \quad R_i = \infty, \quad R_o = 0$$

#

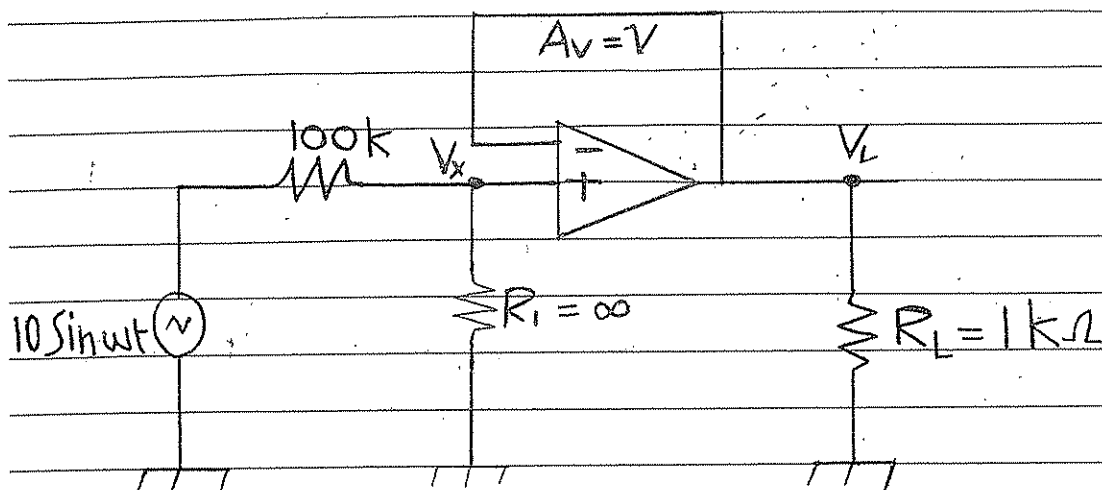

$$V_L = 10 \frac{1}{100+1} = 0.1 \sin \omega t \text{ (V)}$$

Sever loading effect.

To solve this problem ; we use Buffer :-


$$V_x = V_i \cdot \frac{R_{in}}{R_{in} + R_s} \approx V_i$$

$$V_x = V_L = V_i = 10 \sin \omega t \text{ (V)}. \quad \text{[No Loading]}$$

So, The main usage of Buffer to Cancel Loading Effect.

~~✘~~ Buffer better than Common Collector.


5) Difference Amp, :-

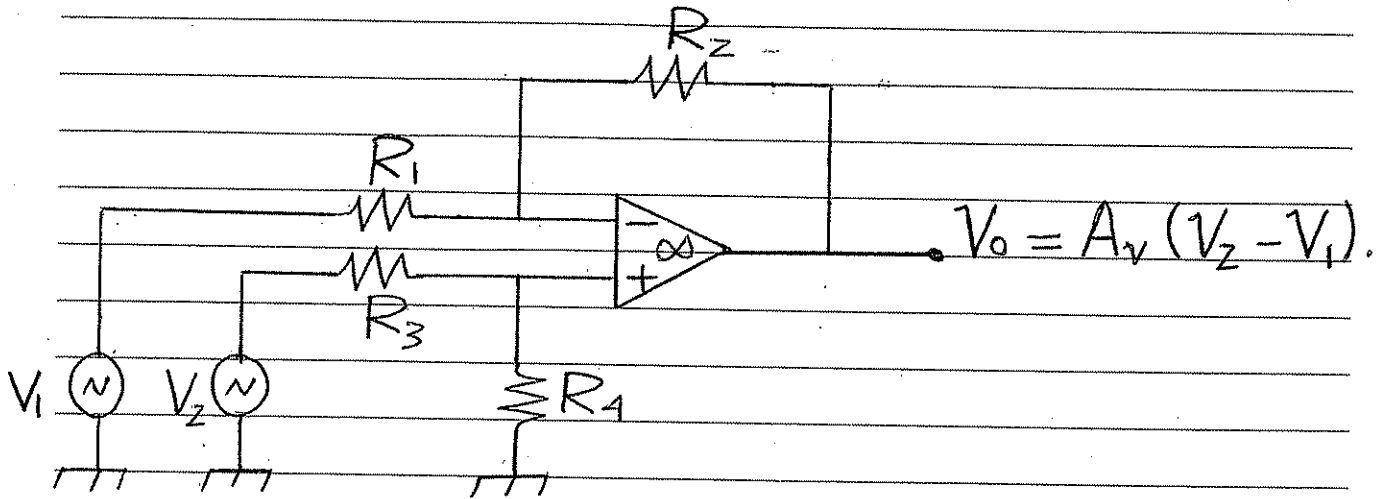

By using Superposition principle :-

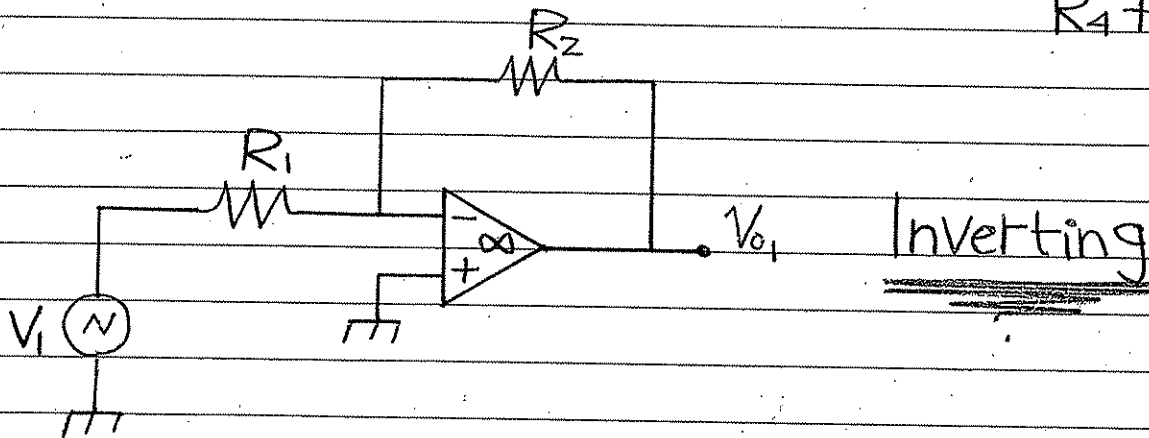
1) Effect of V_1 ($V_2 = 0$) :-

When $V_2 = 0$ (Short cct.), $V^+ = 0$. $R_4 = 0$



$V_{01} = -\frac{R_2}{R_1} V_1$

2) Effect of V_2 ($V_1=0$) :-

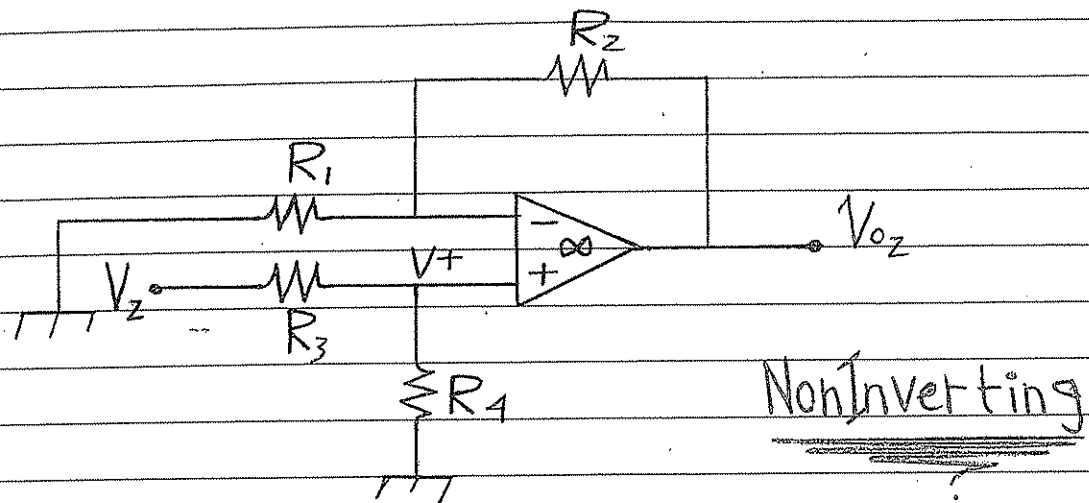

$$V_{02} = \left(1 + \frac{R_2}{R_1}\right) V^+ \quad ; \quad V^+ = V_2 \cdot \frac{R_4}{R_3 + R_4}$$

$$V_{02} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2 \quad \#$$

$$V_0 = V_{01} + V_{02}$$

$$= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2 - \frac{R_2}{R_1} V_1$$

$$= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{\frac{R_4}{R_3}}{1 + \frac{R_4}{R_3}}\right) V_2 - \frac{R_2}{R_1} V_1$$


Choose $\frac{R_4}{R_3} = \frac{R_2}{R_1}$, then :

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_2}{R_1}\right) V_2 - \frac{R_2}{R_1} V_1$$

$$= \frac{R_2}{R_1} V_2 - \frac{R_2}{R_1} V_1$$

$$= \frac{R_2}{R_1} (V_2 - V_1)$$
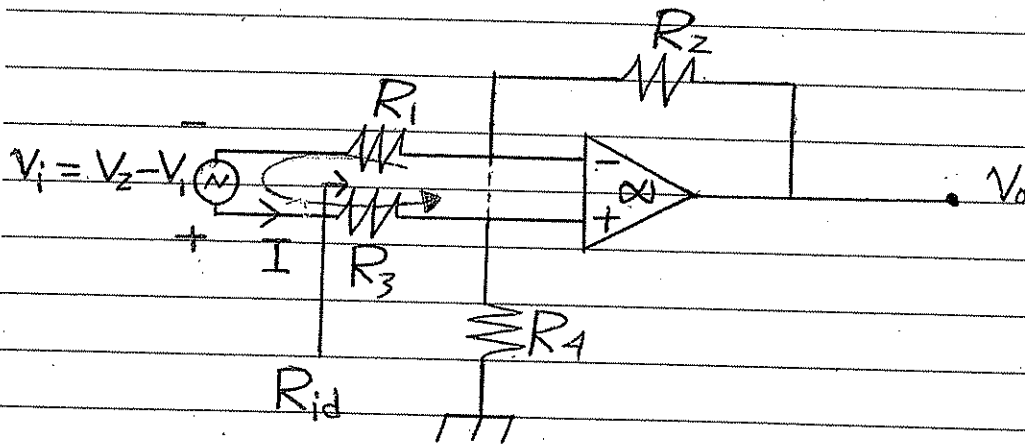
$$\therefore A_{vd} = \frac{V_o}{V_2 - V_1} = \frac{R_2}{R_1} \quad \#$$



$$R_{id} = \frac{V_i}{I}$$

$$-V_i + IR_3 + IR_1 = 0$$

$$V_i = I(R_3 + R_1)$$

$$\frac{V_i}{I} = R_3 + R_1 = R_{id} \quad \#$$

EXA.: Design a Difference Amp. to have

$$R_i = 20 \text{ k}\Omega, \quad A_{vd} = 50.$$

Sol.

$$A_{vd} = \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

$$R_{id} = R_1 + R_3$$

Choose $R_1 = R_3$, $R_2 = R_4$; Then:

$$R_{id} = 2R_1 = 2R_3$$

$$\therefore R_1 = R_3 = \frac{20}{2} = 10 \text{ k}\Omega$$

$$50 = \frac{R_2}{10} \longrightarrow R_2 = 500 \text{ k}\Omega$$

$$R_4 = R_2 = 500 \text{ k}\Omega \quad \#$$

إذا كانت قيمة

R_i عالية

أو A_{vd} عالية

أو كلاهما عالي


يجب أن تقبل بقيم عالية جداً لـ R_3 و R_4

وهذا غير مرغوب في عمارة Design

ال Design يتطلب استخدام مقاومات ذات الأبعاد جيدة ليس عالية ولا قليلة $[k \Omega$ مناسبة]

الحل مشكلة القيم العالية لـ R_3, R_4 :-

6) Instrumentation Amp. :-

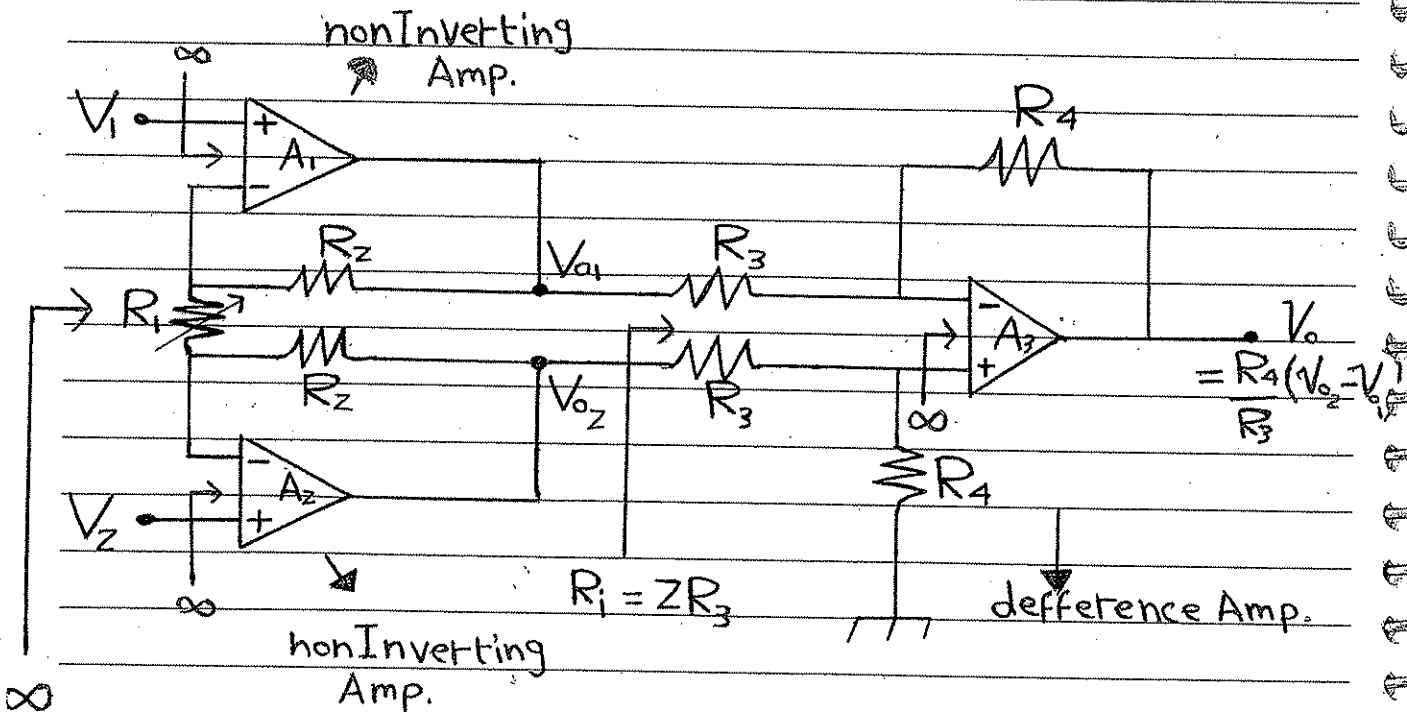

* Instrumentation Amp. used to achieve high Input Resistance ; high, adjustable Single element dependant gain using reasonable Values of Resistors.

A_3 : Difference Amp.

A_1 & A_2 : Non Inverting Amp.


$$V_o = \frac{R_4}{R_3} (V_{o_2} - V_{o_1})$$

V_{o_1} ?

Using Superposition :-

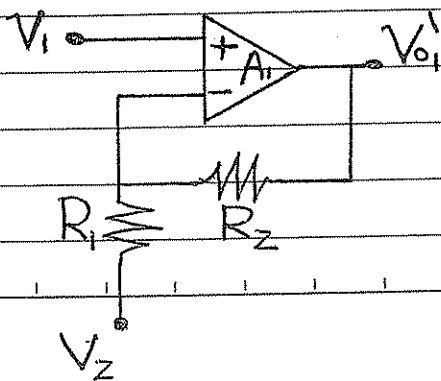
1) Effect of V_1 ($V_2 = 0$):

$$V_{o_1}' = \left(1 + \frac{R_2}{R_1}\right) V_1$$




2) Effect of V_2 ($V_1 = 0$):

$$V_{o_1}'' = -\frac{R_2}{R_1} V_2$$

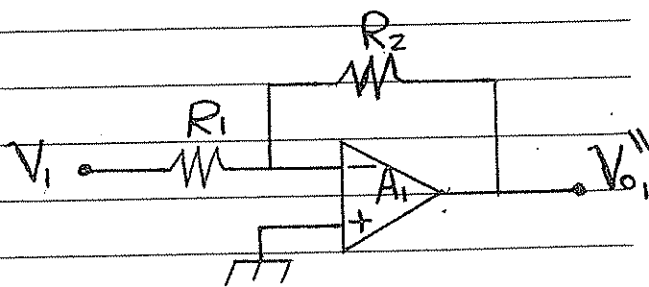

$$V_{o1} = V_{o1}' + V_{o1}''$$
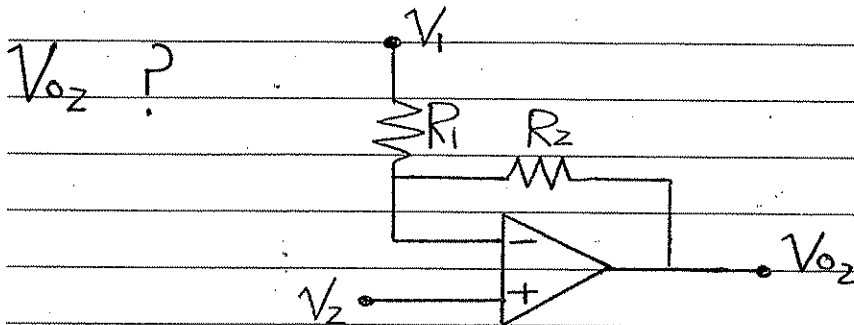
$$V_{o1} = \left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2$$



$$V_{o2} = \left(1 + \frac{R_2}{R_1}\right) V_2 - \frac{R_2}{R_1} V_1$$

$$V_o = \frac{R_4}{R_3} \left[\left(1 + \frac{R_2}{R_1}\right) V_2 - \frac{R_2}{R_1} V_1 - \left(\left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2 \right) \right]$$

$$V_o = \frac{R_4}{R_3} \left(1 + 2\frac{R_2}{R_1}\right) (V_2 - V_1)$$

$V_o = A_{dI} (V_2 - V_1)$; where :

$$A_{dI} = \frac{R_4}{R_3} \left(1 + 2\frac{R_2}{R_1}\right) \quad \#$$

$$R_{i3} = 2R_3 \quad \#$$


EXA. :- Design an Instrumentation Amp. to have a gain ranging from (5 \rightarrow 500), The max. available Resistance is 100 k Ω .

Sol.

$$A_{dI} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right)$$

Choose R_1 to be Variable Resistance.

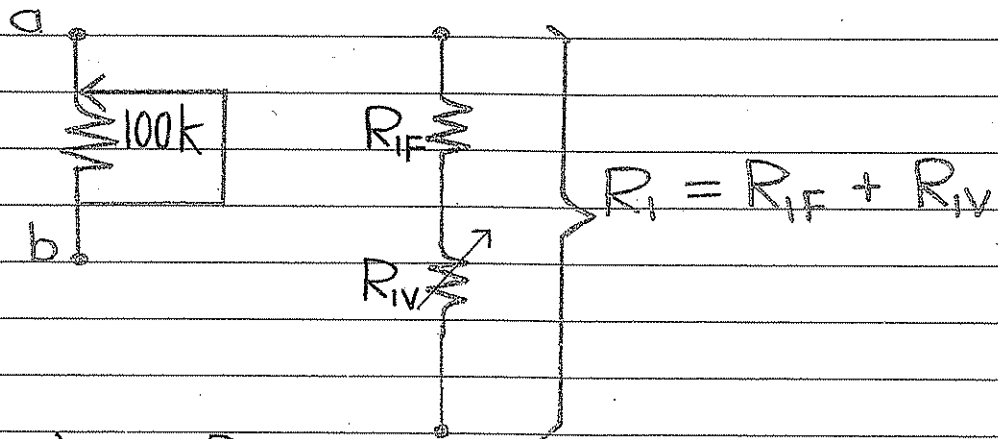If $R_1 = 0 \rightarrow A_{dI} \Rightarrow \infty \rightarrow$ OP-Amp. In Saturation.



$A_{dI}(\text{min}) \rightarrow R_1, \text{max}$

$A_{dI}(\text{max}) \rightarrow R_1, \text{min}$

Choose R_{IV} to be 100k Ω potentiometer.

$$R_{1, \text{min}} = R_{IF}$$

$$R_{1, \text{max}} = R_{IF} + 100$$

$$5 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) \quad \text{--- 1}$$

$$500 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) \quad \text{--- 2}$$

$$\text{let } \frac{R_4}{R_3} = 2$$

نختار رقم أقل من (5) ولا تكون عنده قيمة \rightarrow

From 1 : $1 + \frac{2R_2}{R_1}$ تساوي ديفر أو سالبة .

$$5 = 2 \left(1 + \frac{2R_2}{100 + R_{IF}} \right)$$

$$1.5 = \frac{2R_2}{100 + R_{IF}} \quad \rightarrow 2R_2 = 150 + 1.5R_{IF} \quad \text{--- 3}$$

From 2 :

$$500 = 2 \left(1 + \frac{2R_2}{R_{IF}} \right)$$

$$249 = \frac{2R_2}{R_{IF}} \quad \rightarrow 2R_2 = 249 R_{IF} \quad \text{--- 4}$$

Equate 3 & 4 :-


$$249 R_{IF} = 150 + 1.5 R_{IF}$$

$$247.5 R_{IF} = 150 \rightarrow R_{IF} = 0.61 \text{ k}\Omega$$

$$\text{from 4 : } R_2 = \frac{249 \times 0.61}{2} = 74.5 \text{ k}\Omega$$

$$\frac{R_4}{R_3} = 2 \rightarrow \text{Choose } R_3 = 1 \text{ k}\Omega, \text{ then } R_4 = 2 \text{ k}\Omega$$

7) Voltage-to-Current Converter :-

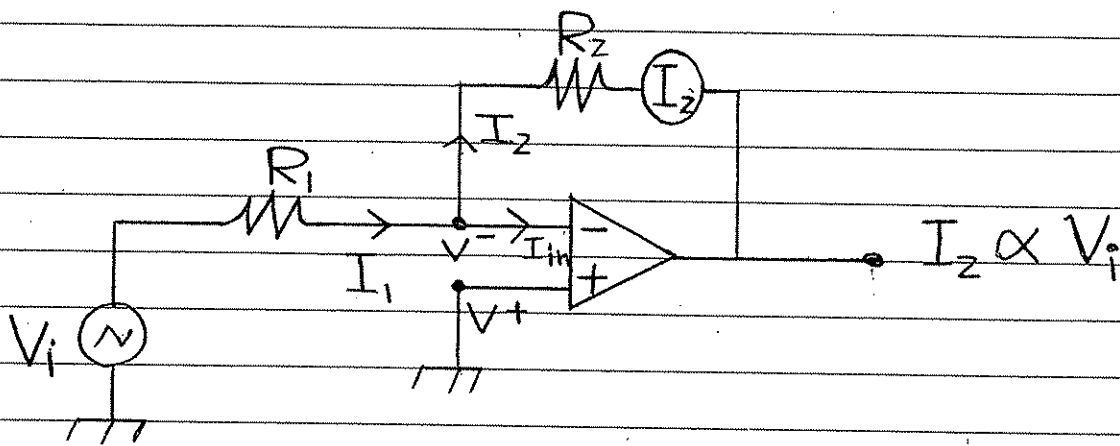

$$I_1 = I_{in} + I_2$$


$$\frac{V_i - V^-}{R_1} = I_{in} + I_2$$

$$\left. \begin{aligned} V^- = V^+ = 0 \text{ (Virtual ground)} \\ I_{in} = 0 \end{aligned} \right\} \text{Ideal op-Amp.}$$

$$\frac{V_i}{R_1} = I_2$$

i.e. I_2 is proportional to V_i and proportional constant is $\frac{1}{R_1}$.

8) Current-to-Voltage Converter :

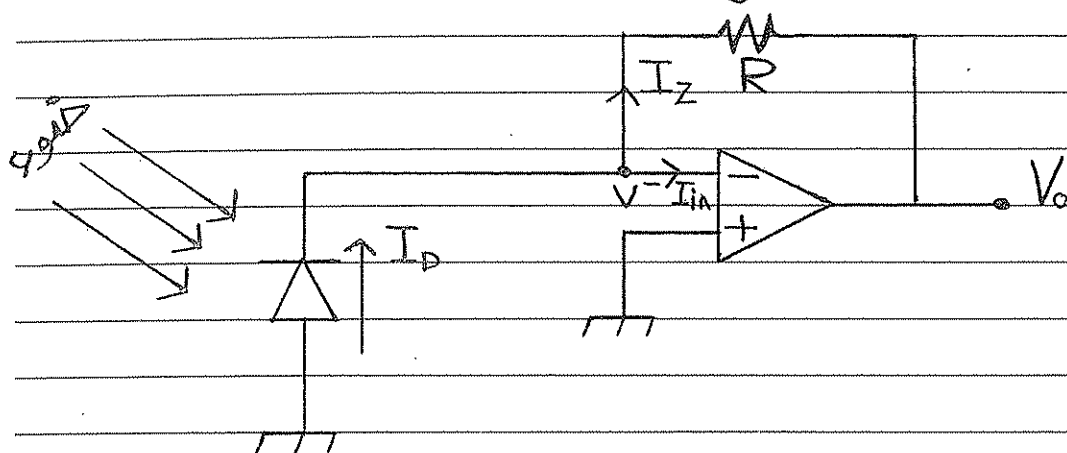

$$I_D = I_{in} + I_Z$$


$$= I_{in} + \frac{V - V_o}{R}$$

$$V_o = -I_D R$$

$$V_o \propto I_D$$

i.e. V_o is proportional to I_D and proportional constant is $-R$.

9) Integrator :-

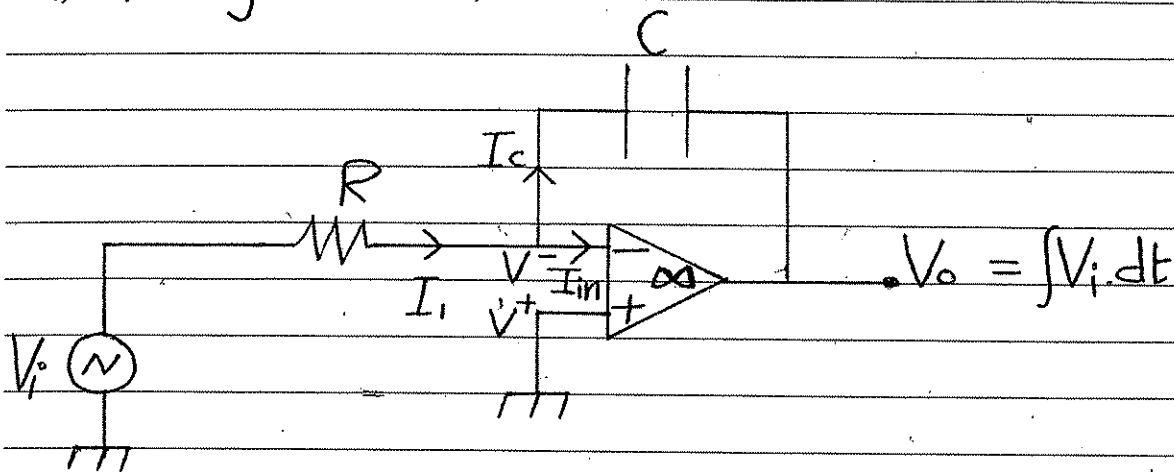

$$I_i = I_c + I_{in}$$

$$\frac{V_i - V^-}{R} = C \frac{dV_c}{dt} + I_{in}$$

$$\# V_c = V^- - V_o$$

$$V^- = V^+ = 0 \quad (\text{Virtual ground})$$


$$I_{in} = 0 \quad (R_i = \infty)$$

$$\rightarrow \frac{V_i}{R} = -C \frac{dV_o}{dt}$$

$$\int dV_o = \int -\frac{V_i}{RC} dt$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

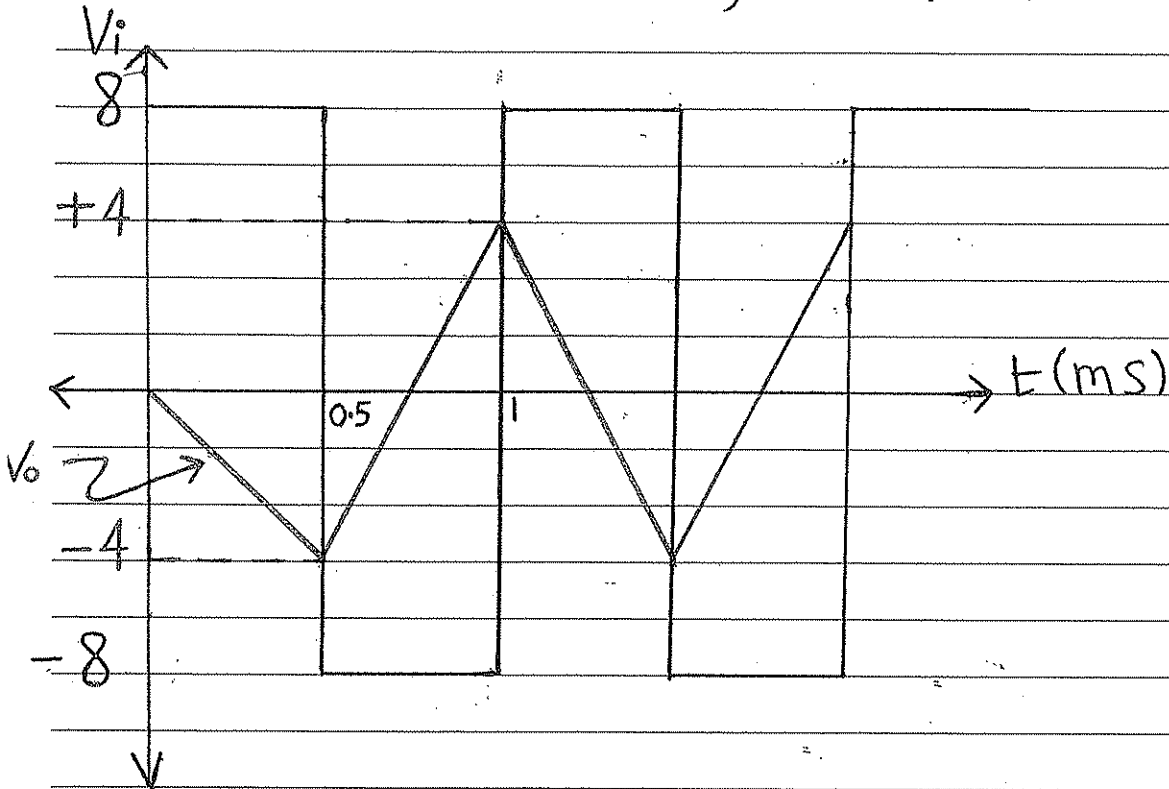EXA.: For $R = 1\text{ k}\Omega$, $C = 1\text{ }\mu\text{F}$



1) $t: (0 \rightarrow 0.5) \text{ ms}$, $V_i = 8\text{ V}$.

$$V_o = \frac{1}{10^3 \times 10^{-6}} \int_0^{0.5\text{ms}} 8 \, dt$$


$$= -10^3 (8 \times 0.5) \times 10^{-3} = -4\text{ V}$$

2) $t: (0.5 \rightarrow 1) \text{ ms}$, $V_i = -8\text{ V}$.

$$V_o = \frac{1}{10^3 \times 10^{-6}} \int_{0.5}^{1\text{ms}} -8 \, dt = -10^3 \cdot 8t \Big|_{0.5}^{1\text{ms}}$$

$$= +4\text{ V}$$

10) Differentiator :-

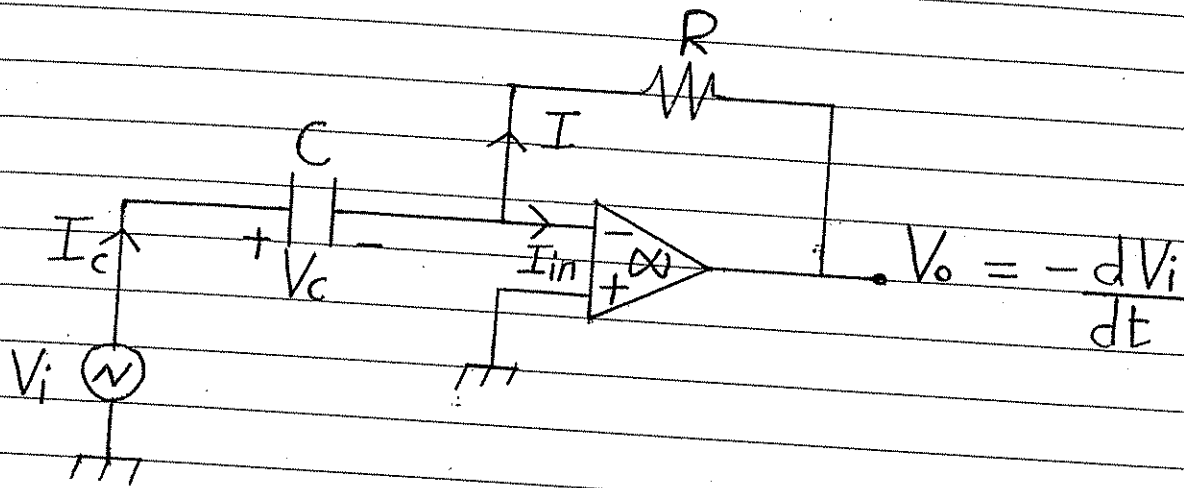

$$I_c = I + I_{in}$$

$$C \frac{dV_c}{dt} = \frac{V_i - V_o}{R} + I_{in}$$

$$V_c = V_i - V_o$$


$$V^- = V^+ = 0 \quad (\text{Virtual ground})$$

$$I_{in} = 0 \quad (R_i = \infty)$$

$$\rightarrow C \frac{dV_i}{dt} = -\frac{V_o}{R}$$

$$V_o = -RC \frac{dV_i}{dt}$$

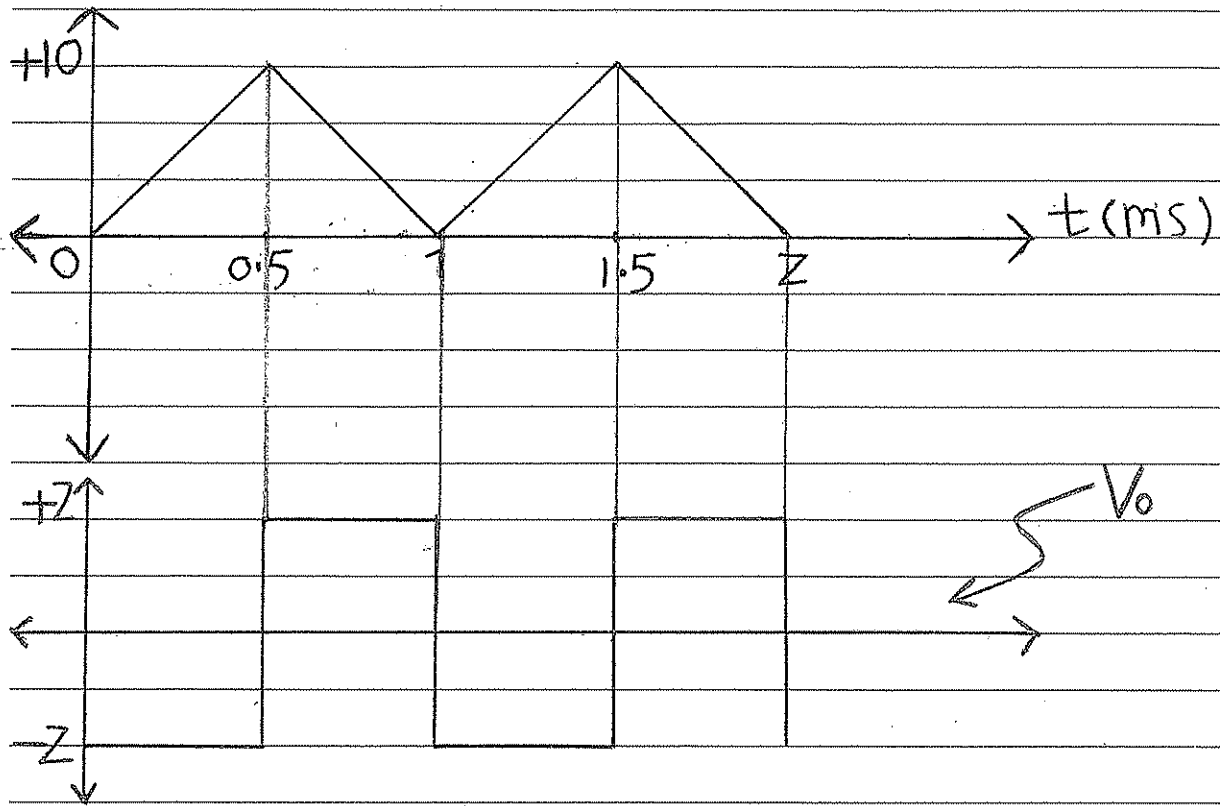EXA.: For $R = 1\text{K}\Omega$, $C = 0.1\mu\text{F}$.



1) $t: (0 \rightarrow 0.5) \text{ ms}$

$$V_o = -RC \frac{\Delta V_i}{\Delta t}$$

$$\frac{\Delta V_i}{\Delta t} = \frac{(10 - 0) \text{ V}}{(0.5 - 0) \text{ ms}} = 20 \times 10^3 = 2 \times 10^4 \text{ V/s}$$


$$V_o = -1 \times 10^3 \times 10^{-7} \times 2 \times 10^4 = -2 \text{ V}$$

2) $t: (0.5 \rightarrow 1) \text{ ms}$

$$\frac{\Delta V_i}{\Delta t} = \frac{(0 - 10) \text{ V}}{(1 - 0.5) \text{ ms}} = -2 \times 10^4 \text{ V/s}$$

$$V_o = -10^3 \times 10^{-7} \times (-2 \times 10^4) = +2 \text{ V}$$

Case:

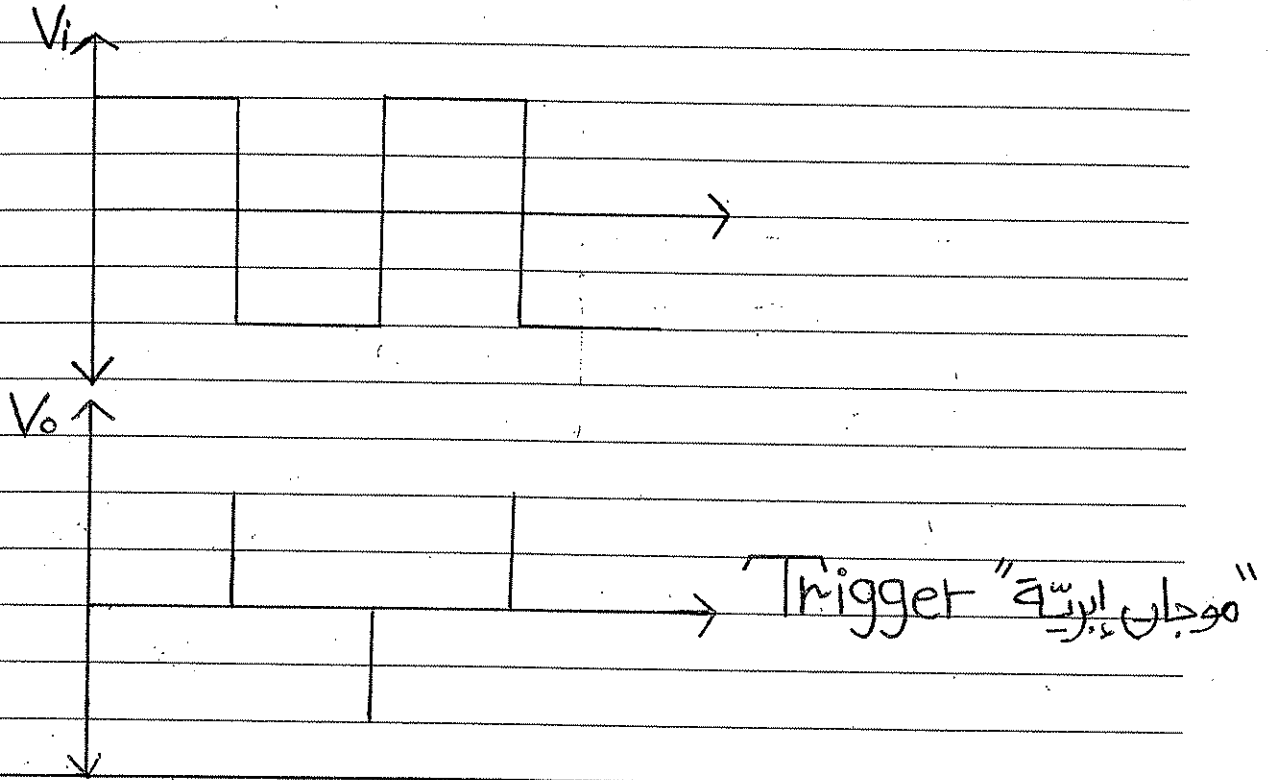

Integrator }
 Differentiator } # تأخير الموجات


* Differentiator :
 → high freq. → C : Short Cct. → OP-Amp. : Saturation.

← تغذي فيه المسألة نضع R_x مع C على التوالي

* Integrator :
 → Low freq. → C : OPen Cct. → OP-Amp. : Saturation.

← تغذي فيه المسألة نضع R_x مع C على التوالي

II) Voltage Comparator :-

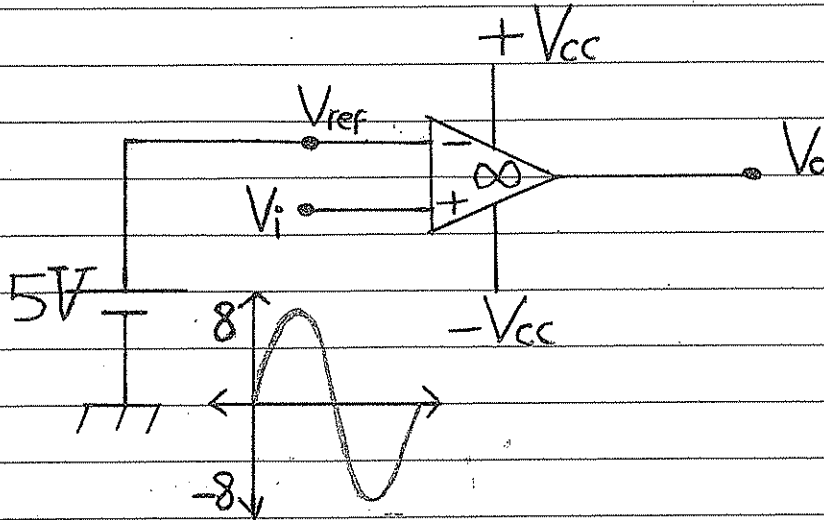

i) OP-Amp. works in open loop mode.

$$ii) V_o = \mp V_{cc}$$


$$V_o = A_o (V^+ - V^-)$$

\downarrow
 $\rightarrow \infty$

\uparrow if $V^+ > V^- \rightarrow V_o = +V_{cc}$.

\downarrow if $V^+ < V^- \rightarrow V_o = -V_{cc}$.

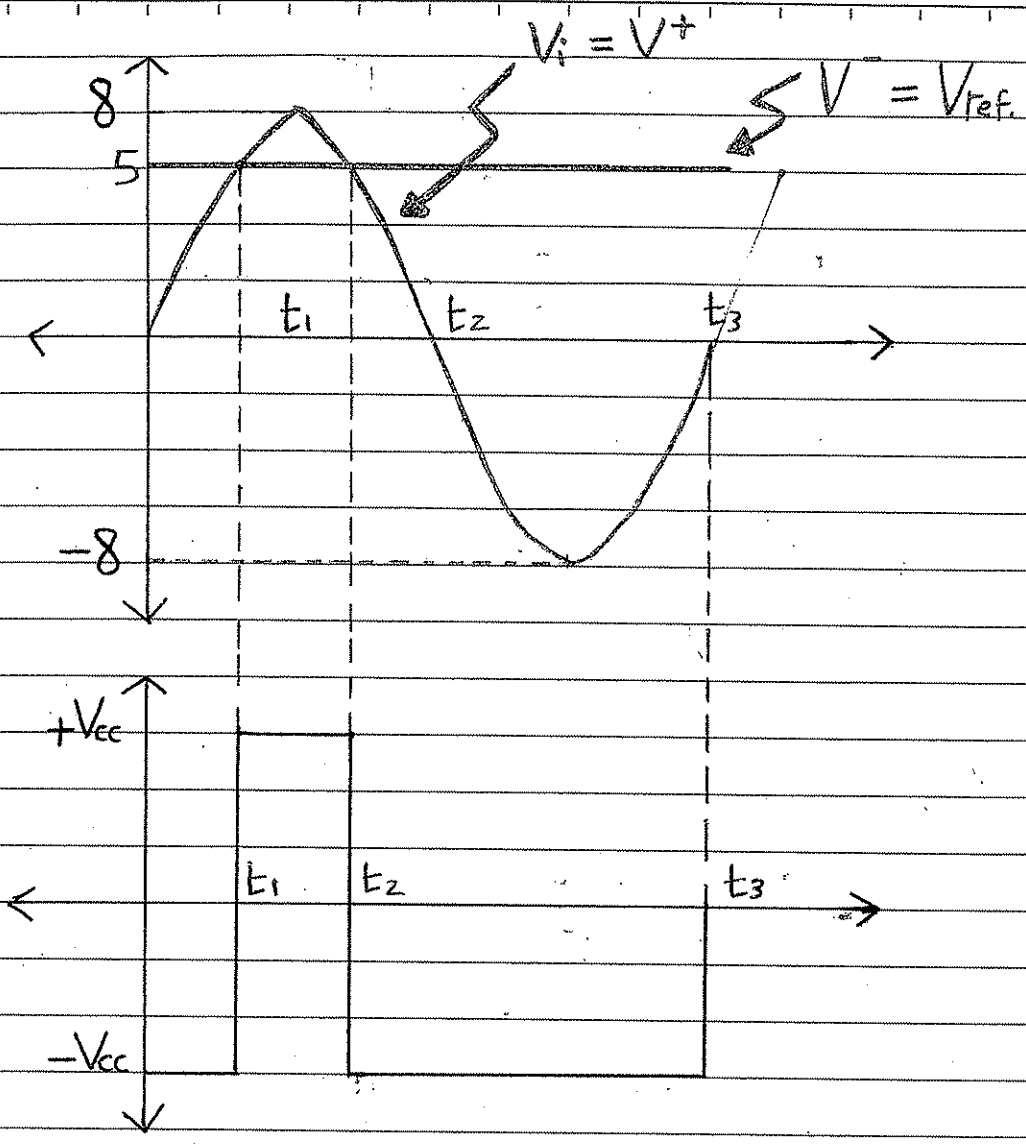نوسم $(V^+) V_i$ ← نوسم $(V^-) V_{ref}$ ← تقارن للحصول على V_o




From $0 \rightarrow t_1$; $V^+ < V^- \rightarrow V_o = -V_{cc}$

From $t_1 \rightarrow t_2$; $V^+ > V^- \rightarrow V_o = +V_{cc}$


From $t_2 \rightarrow t_3$; $V^+ < V^- \rightarrow V_o = -V_{cc}$

Case 1:

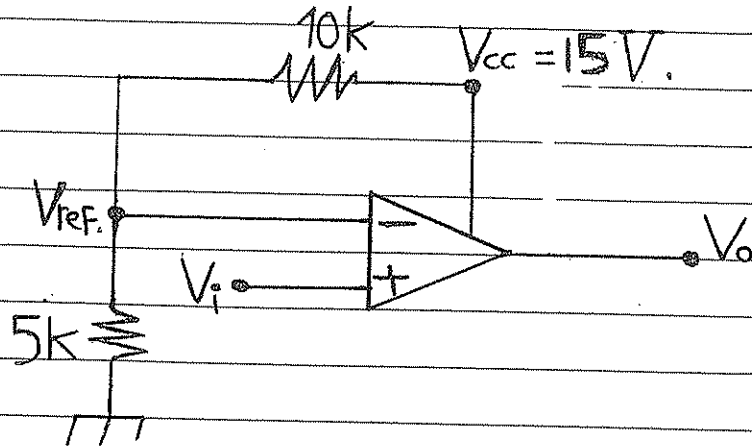

$$V_{ref} = \frac{15 \times 5}{15} = 5V \quad (\text{Voltage divider})$$

Case 2:

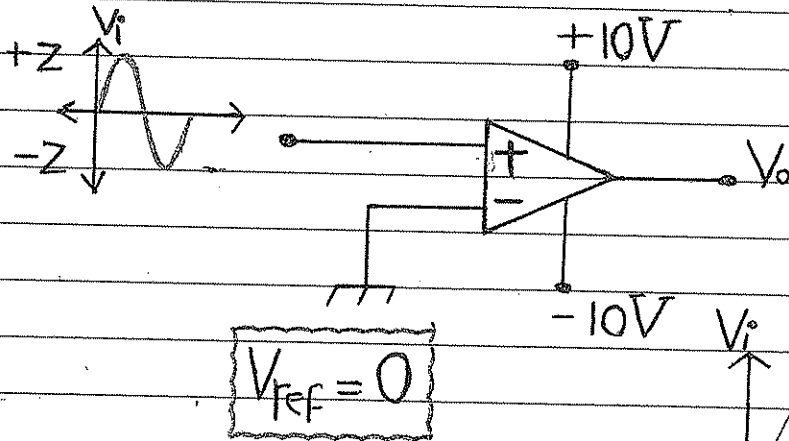

IF $V_{ref} = 0$, then the

circuit is called:


{Zero Crossing detector}

→ is a Voltage Comparator.


NON Linear Applications :

1] Precision Rectifier :-

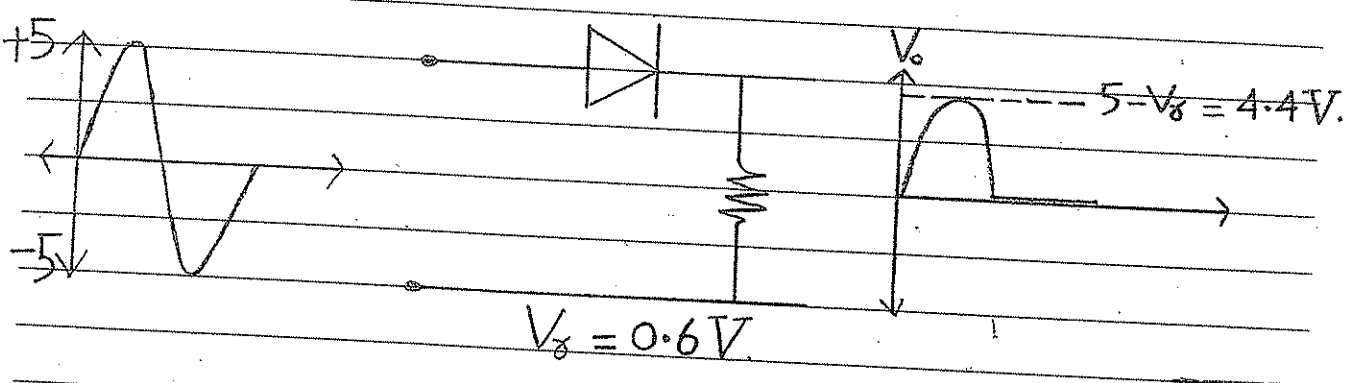precision rectifier Used to rectify signals with peak value $< V_s$.



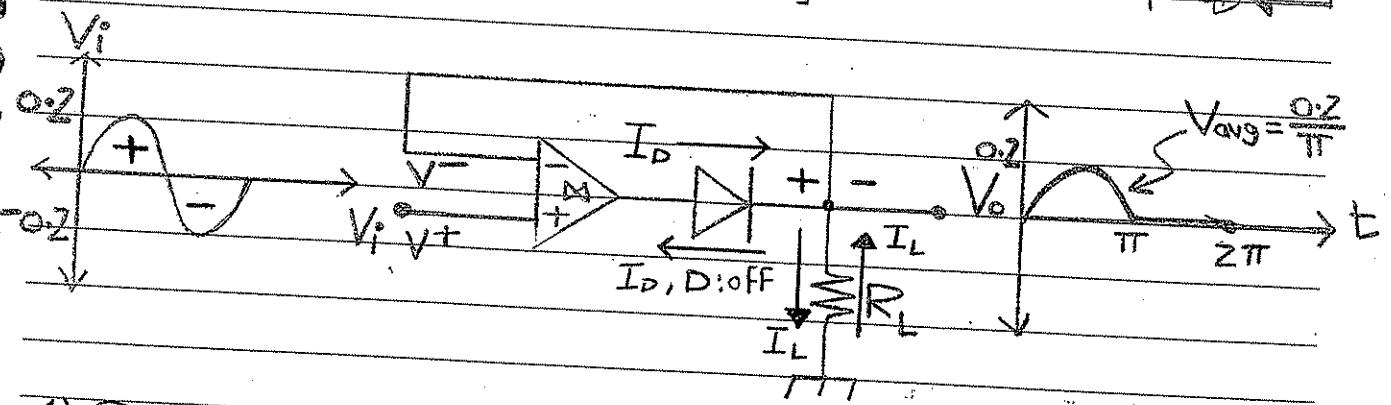∴ $[V_i < V_s]$ \rightarrow لا يمر التيار $[V_i > V_s]$ \rightarrow يمر التيار




1) During (+ve) H.C of V_i ; $V_o \rightarrow (+ve)$;

and I_L \downarrow , So Diode will be ON Closed-loop.

$$I_D = I_L \rightarrow \boxed{V_o = V_i} \#$$

2) During $(-Ve)$ H.C of V_i ; $V_o \rightarrow (-Ve)$; and $I_L \uparrow$, So Diode will be OFF, Open loop.
 $I_D = \ominus \rightarrow \boxed{V_o = 0} \neq$.

2] EXponential Amp. :

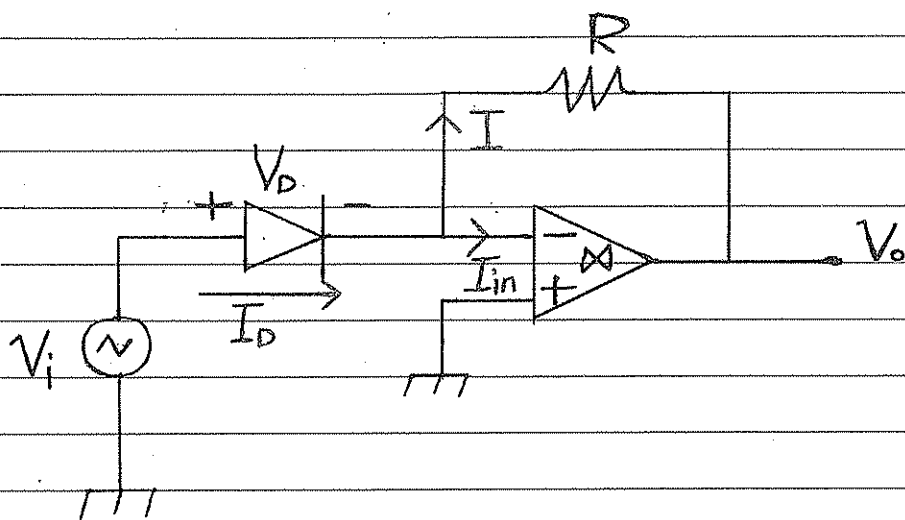

$$I_D = I + I_{in}$$

$$I_s e^{\frac{V_D}{nV_T}} = V^- - \frac{V_o}{R} + I_{in}$$

$$\# V_D = V_i - V^-$$

But: $V^- = V^+ = 0$ (Virtual ground)


$$I_{in} = 0$$

$$I_s e^{\frac{V_i}{nV_T}} = -V_o$$

$$V_o = -R I_s e^{\frac{V_i}{nV_T}}$$

$[V_o]$ exponentially linear with $[V_i]$.

3] Logarithmic Amp.:

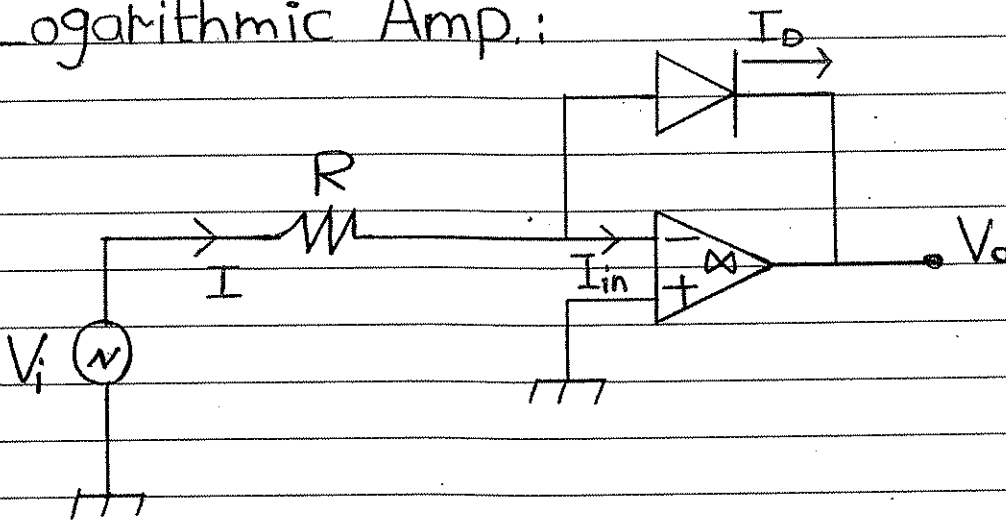

$$I = I_{in} + I_D$$

$$\frac{V_i - V^-}{R} = I_{in} + I_s e^{\frac{V_D}{nV_T}}$$

$$\# V_D = V^- - V_o$$

But: $V^- = V^+ = 0$ (Virtual ground)

$$I_{in} = 0$$

$$\frac{V_i}{R} = I_s e^{\frac{-V_o}{nV_T}}$$


$$\frac{V_i}{I_s R} = e^{\frac{-V_o}{nV_T}}$$

$$\frac{-V_o}{nV_T} = \ln \frac{V_i}{I_s R}$$


$$V_o = -nV_T \ln \frac{V_i}{I_s R}$$

Chapter (7) :- Frequency Response of Amp. :-

152

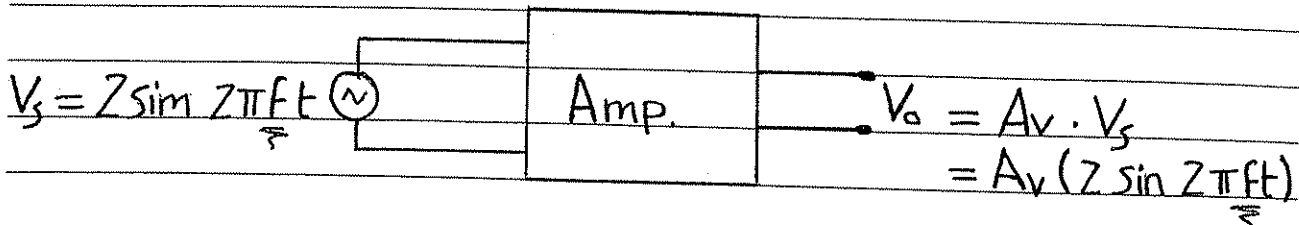

A_v, A_I

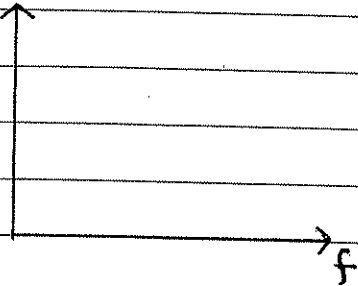

$$A_v = \frac{V_o}{V_s} = \frac{V_o}{Z \sin 2\pi f t}$$

• V_s (f) constant V_o constant

Frequency Response of Amp. Is a plot of Amp. gain (A_v or A_I) versus frequency.



The gain can be unitless [$A_v = \frac{V_o}{V_s}$, $A_I = \frac{I_o}{I_s}$]

or in dB where:

$$A_v (\text{dB}) = 20 \log \frac{V_o}{V_s}$$

$$A_I (\text{dB}) = 20 \log \frac{I_o}{I_s}$$

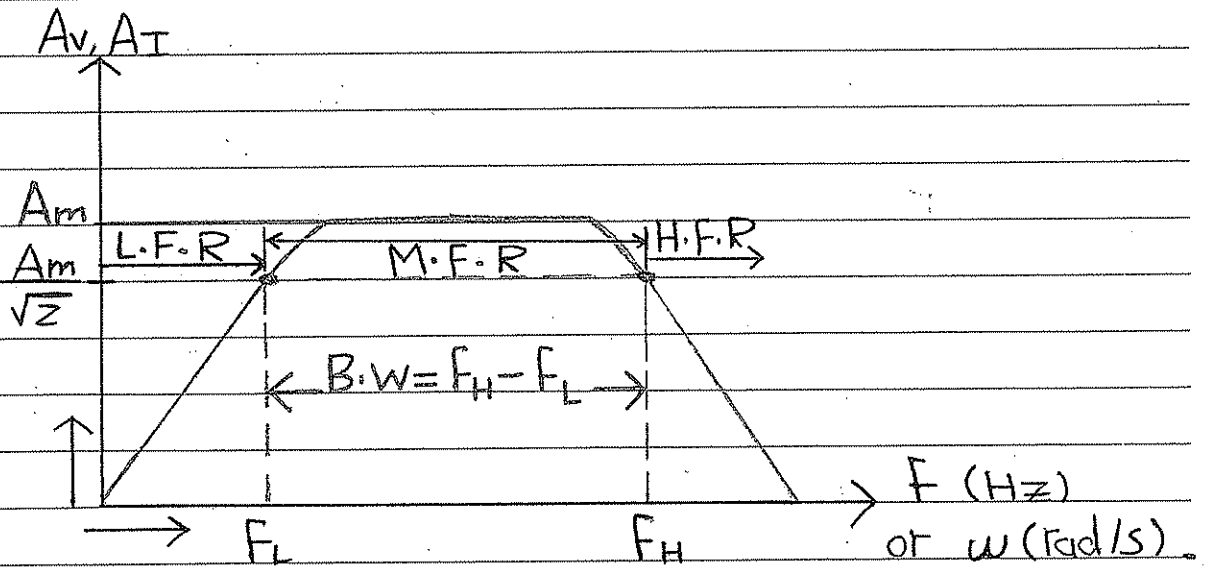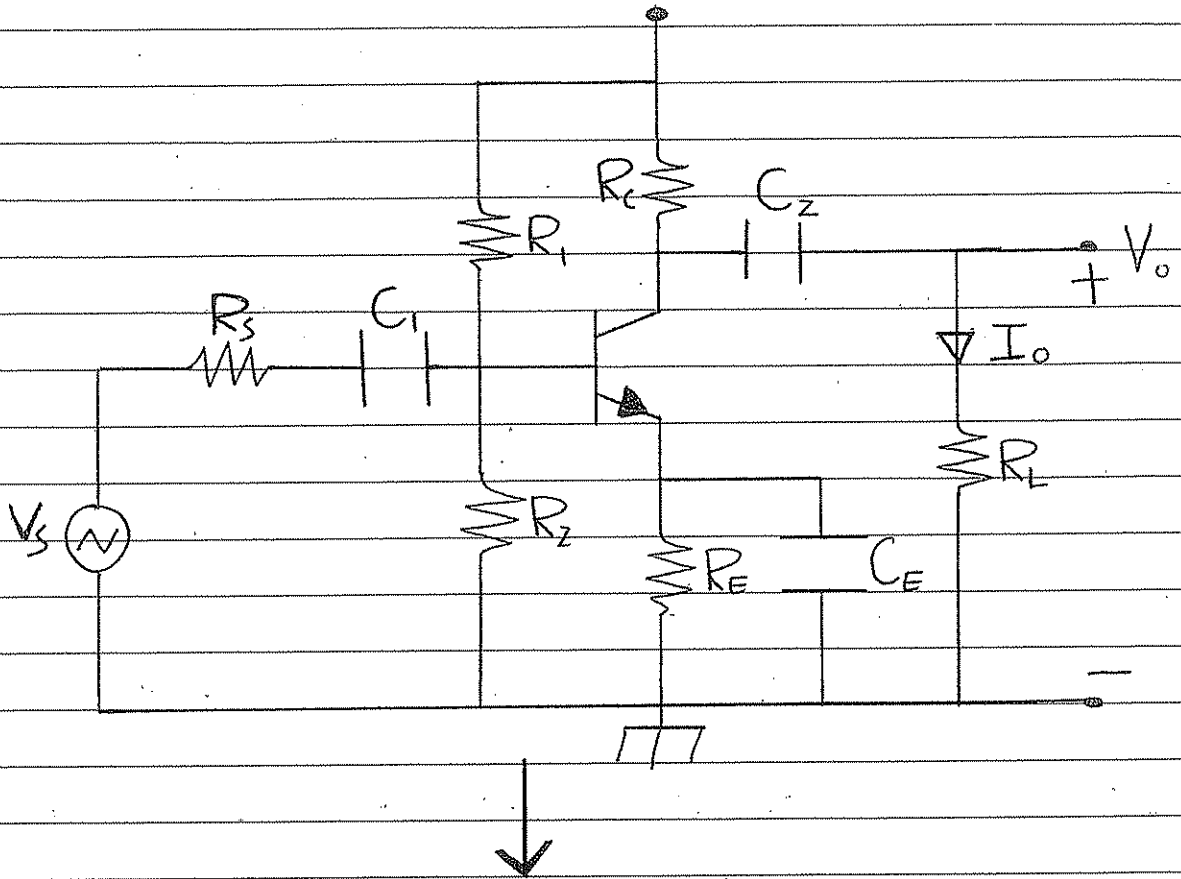The freq. can be in Hz or angular freq. ω (rad/s).



1] For any Amp. Contain at least one Coupling or bypass Cap.; the typical freq Response is Shown.


2] The typical freq. Resp. Contains three regions [L.F.R, M.F.R, H.F.R].

1) Low Frequency region (L.F.R) :-

The gain is freq. dependant such that as $f \uparrow$, $A_v \uparrow$ due to the effect of Coupling and bypass Cap.s where $f \uparrow$, $(X_{C_1}, X_{C_2}) \downarrow$ and

Since they are in the series path of signal

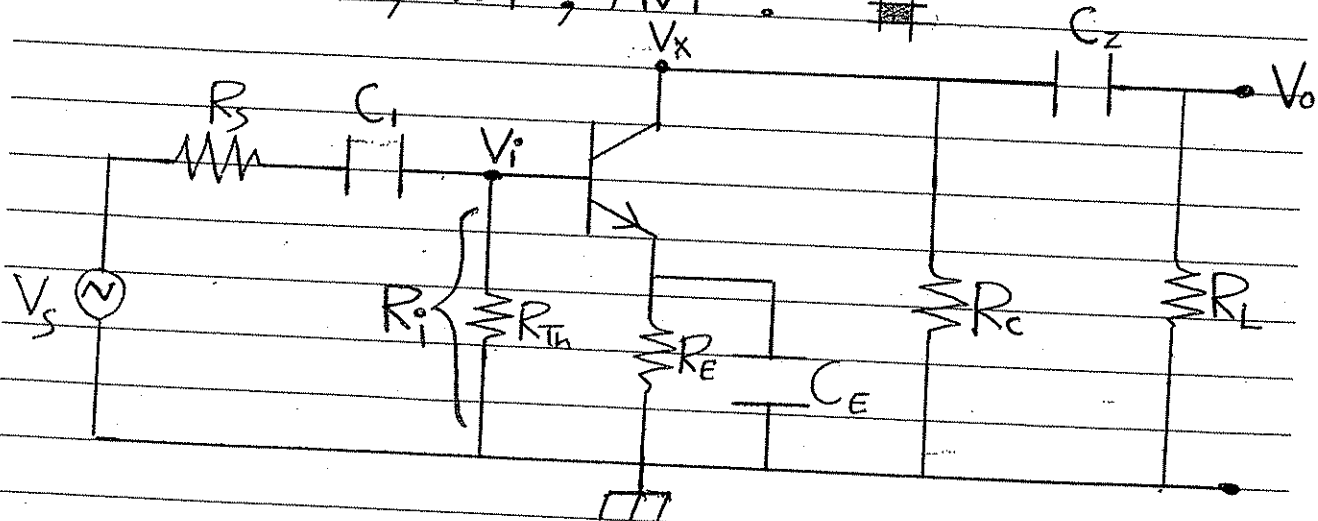So as $X_C \downarrow$, $V_o \uparrow$, $A_v \uparrow$.



$$X_c = \frac{1}{2\pi FC}$$

$$V_i = V_s \cdot \frac{R_i}{R_i + R_s + X_{c1}} \quad \text{V.D.R}$$


$$V_x = k \cdot V_i$$

$$V_o = V_x \cdot \frac{R_L}{R_L + X_{c2}} \quad \text{V.D.R}$$

IF $f \uparrow$, $(X_{c1} \& X_{c2}) \downarrow$, $V_i \uparrow$, $V_x \uparrow$, $V_o \uparrow$, $(A_v = \frac{V_o}{V_s}) \uparrow$.

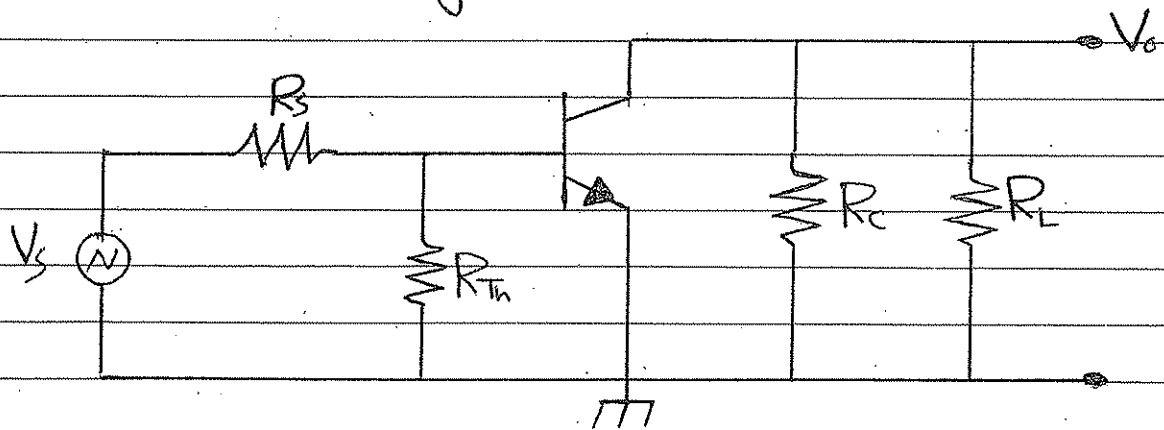ii) Medium Frequency Region (M.F.R) :-

All Cap.s are considered Short CCT. and the CCT. behaves as a pure Resistive Amp. with a certain gain (A_m).



$$A_v = -g_m (R_C \parallel R_L) \frac{R_i}{R_i + R_s} \quad \#$$

This Regn. extends from $f_L \rightarrow f_H$ over a Band Width (B.W) = $f_H - f_L$.



{ Useful range of
Amp. Operation }



iii) High Frequency Regn. :-

All Caps are short ckt. ; but New Aray Caps appear effectivily (No physical existance) Called : C_M ; Jn. Cap.

C_{π} ; diffusion Cap.

Their effect is in parallel with Input and output side.

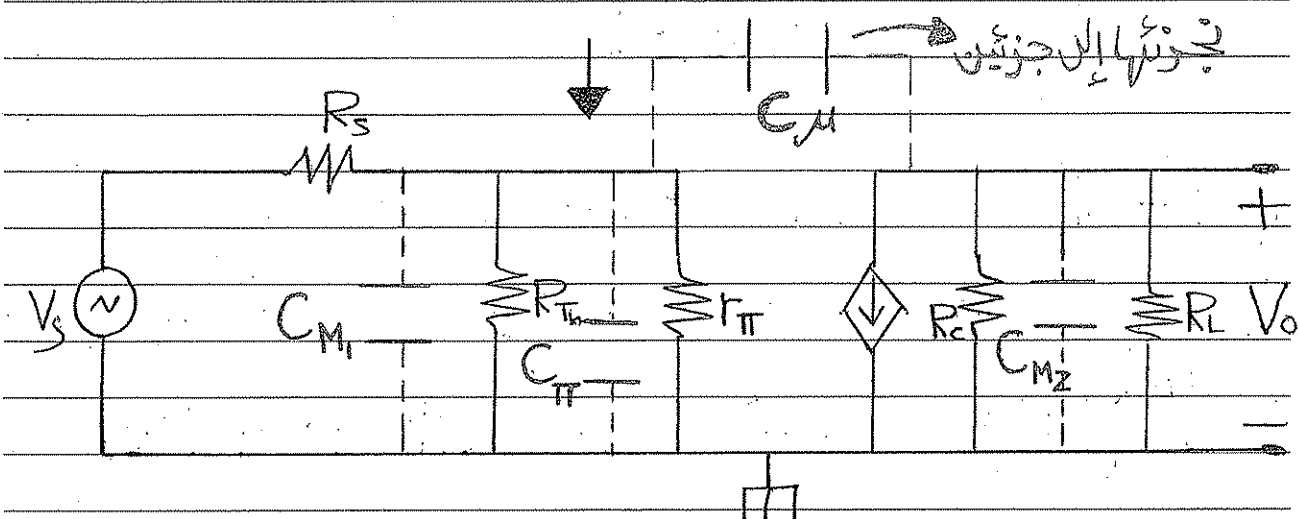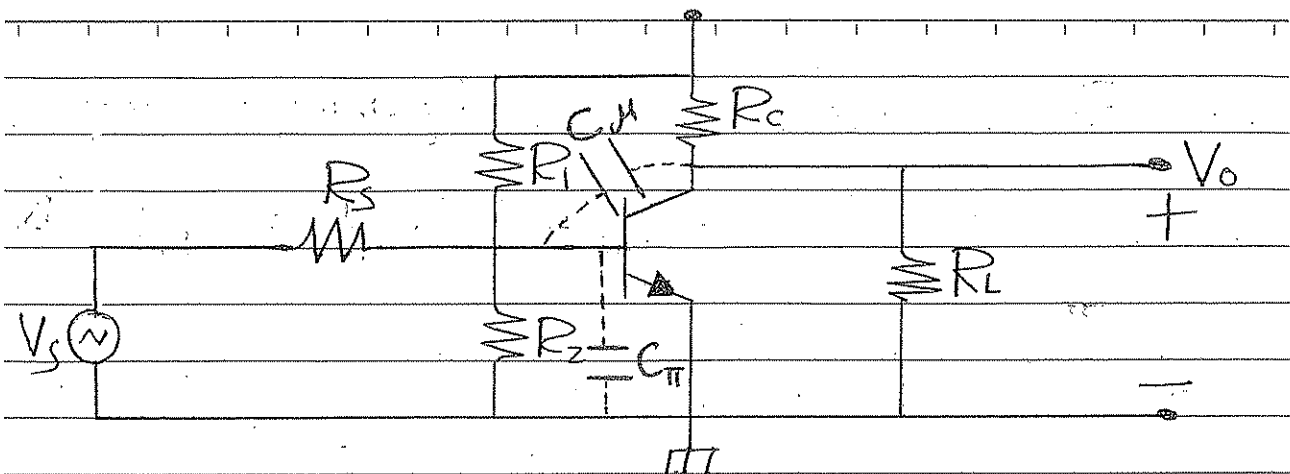
as $f \uparrow$ their reactances X_c decrease ; decreasing V_o and A_v .



$$V_o = -g_m V_{\pi} (R_C \parallel R_L \parallel X_{C_{M2}})$$

$$A_v = \frac{V_o}{V_s}$$

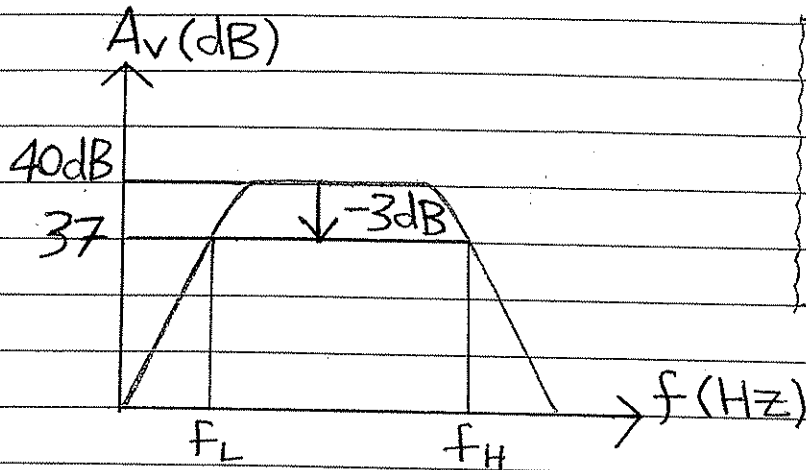as $f \uparrow$, $X_{C_{M2}} \downarrow$, $V_o \downarrow$, $A_v \downarrow$.



$$A_v = \frac{V_o}{V_i}$$

ثابت $V_i \rightarrow$

انما A_v على $\sqrt{2}$

من V_o انما على $\sqrt{2}$

The boundaries between L.F.R, M.F.R, & H.F.R are called :-


1) Cut off frequencies.

* $f_L \rightarrow$ Low - Cut off freq.

* $f_H \rightarrow$ high - Cut off freq.

2) -3dB frequencies.

3) Break frequencies.

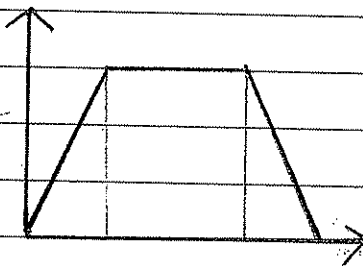

4) half-power frequencies :-

$$\cancel{P_{FL}} = P_{FH} = \frac{1}{2} P_{MF}$$

$$P = \frac{V_0^2}{R} \text{ (MF)}$$

at (f_L) and (f_H) :-

$$V_{ofL} = V_{ofH} = \frac{V_0}{\sqrt{2}}$$

$$\therefore P_{LF} = P_{HF} = \left(\frac{V_0}{\sqrt{2}} \right)^2 / R$$

$$= \frac{V_0^2}{2} / R \quad ; \quad \frac{V_0^2}{R} = P_{MF}$$

$$= \frac{1}{2} P_{MF} \quad \circ$$

Ele. 2


21/7

- 5/1/21
160

EXA:- Given : $\beta = 100$, $V_{BE} = 0.7V$, $V_A = \infty$

$C_{\mu} = 2PF$, $C_{\pi} = 10PF$

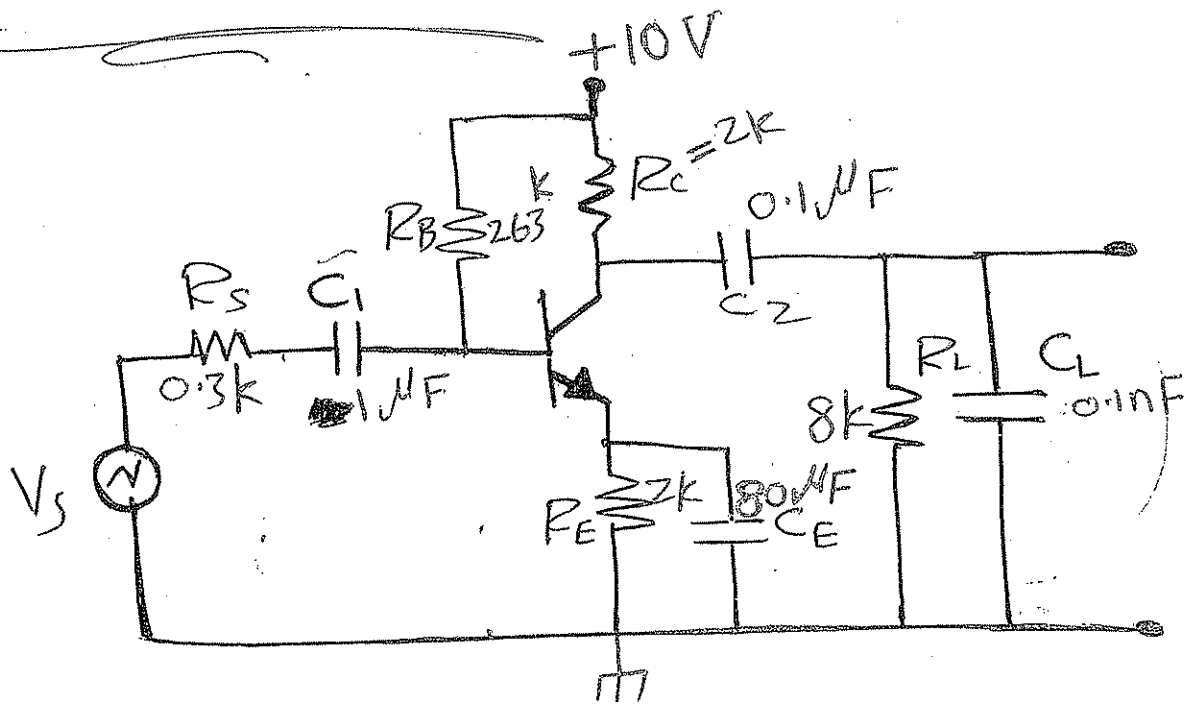- # 1) Draw M.F. Equivalent cct. and find A_{vm}
- 2) // L.F. Eqnt. cct and find f_L .
- 3) // H.F. // // // find f_H .
- 4) Sketch freq. Resp. ($A_v(dB)$ vs freq).







11

① In M.F.R :-

$C_1, C_2, C_E \rightarrow S-C$

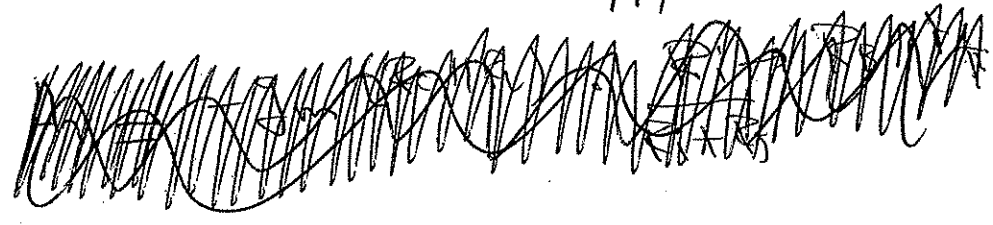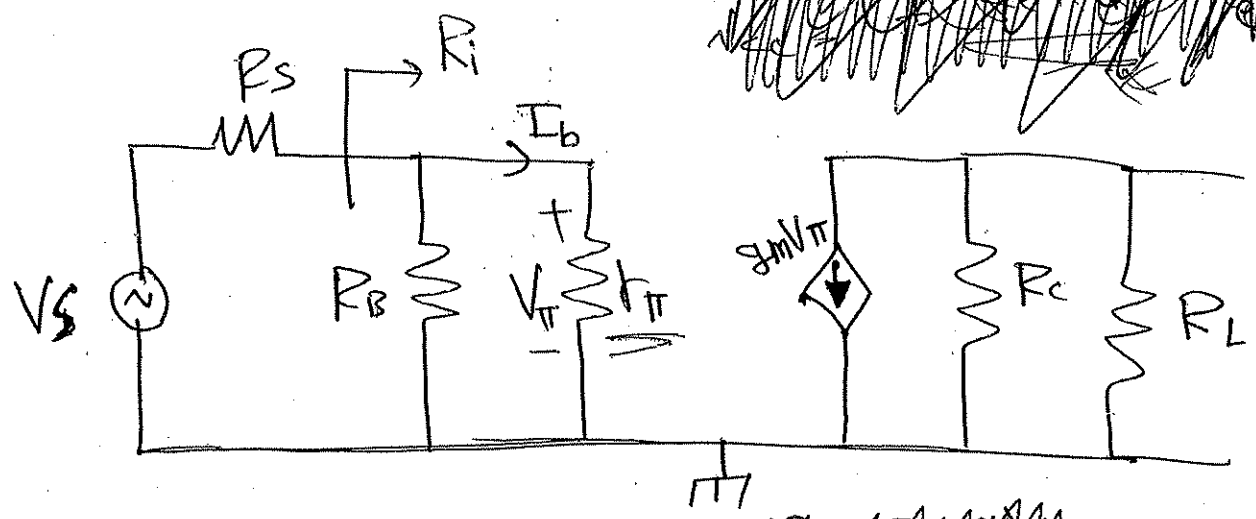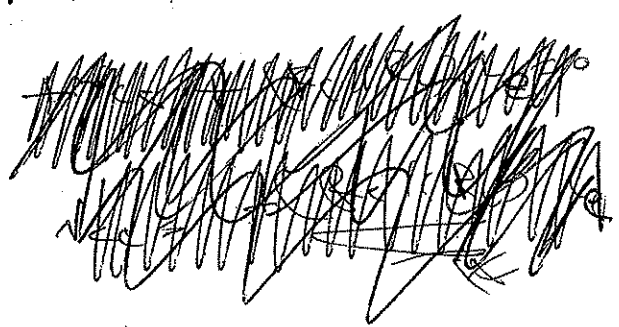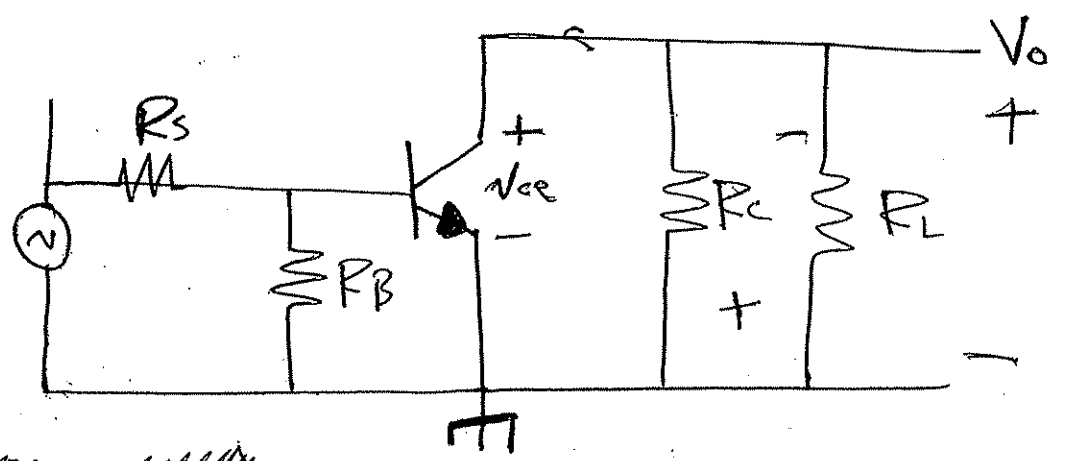$C_L, C_{\pi}, C_{\omega} \rightarrow O.C$




$$A_{vm} = \frac{v_o}{V_s} = \frac{v_o}{V_{\pi}} * \frac{V_{\pi}}{V_s}$$

$$V_o = -g_m V_{\pi} (R_c \parallel R_L)$$

$$\frac{V_o}{V_{\pi}} = -g_m (R_c \parallel R_L)$$
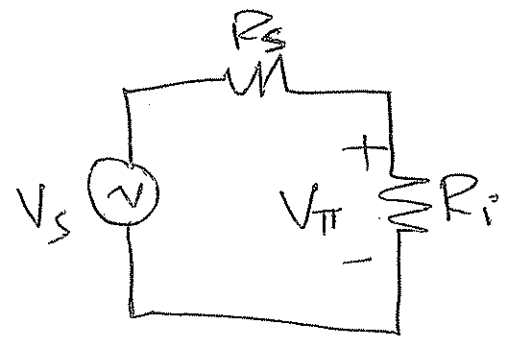
$$\frac{V_{\pi}}{V_s} = \frac{R_i}{R_i + R_s}$$



$$R_i = r_{\pi} \parallel R_B$$

$$A_{vm} = -g_m (R_c \parallel R_L) \frac{R_i}{R_i + R_s}$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}}$$


I_{CQ} D.C. analysis.

$$-10 + I_B 263 + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{(10 - 0.7)V}{263 + 101 * 2}$$

$$= \frac{9.3}{465} = 0.02 \text{ mA}$$
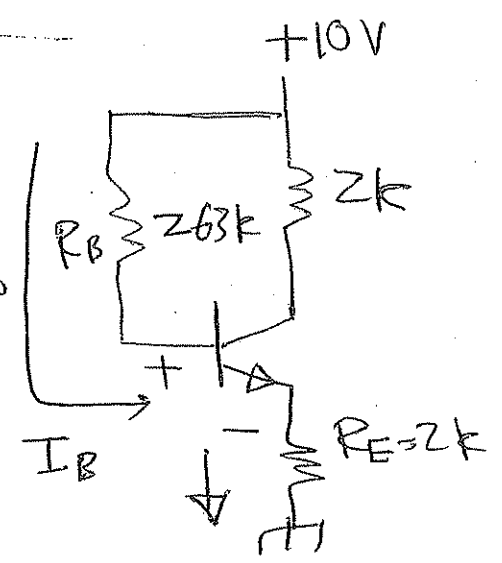
$$I_{CQ} = 100 * 0.02 = \underline{2 \text{ mA}}$$




$$f_{L2} = \frac{1}{2\pi C_2 R_{eq2}} \quad ; R_{eq2} = R_{Th} \text{ seen by } C_2.$$

$$R_{eq2} = R_C + R_L = 2 + 8 = 10 \text{ k}\Omega.$$

$$f_{L2} = \frac{1}{2\pi * 0.1 * 10^{-6} * 10^4} = \frac{10^3}{2\pi}$$

$$= 160 \text{ Hz}$$

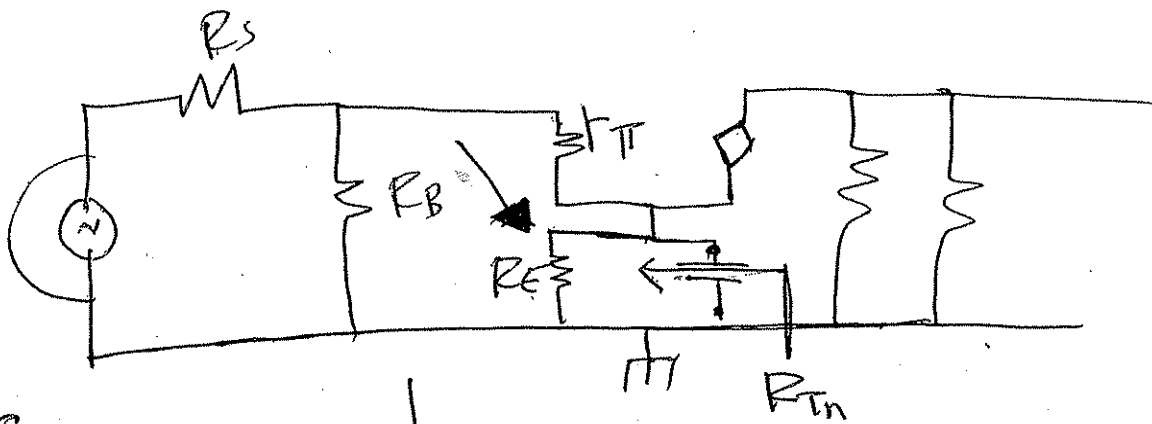iii) Effect of C_E ($C_1, C_2 \rightarrow \text{s.c}$) i-



$$f_{L3} = \frac{1}{2\pi C_E R_{eq3}}$$


$$R_{eq3} = R_{Th} \text{ seen by } C_E.$$

$$R_{eq3} = \left((R_S \parallel R_B) + r_{\pi} \right) \parallel R_E$$

$$= 0.3 \parallel 263 + 1.3 \parallel 2k = 15 \Omega$$


$$f_{L3} = \frac{1}{2\pi \times 80 \times 10^{-6} \times 15}$$
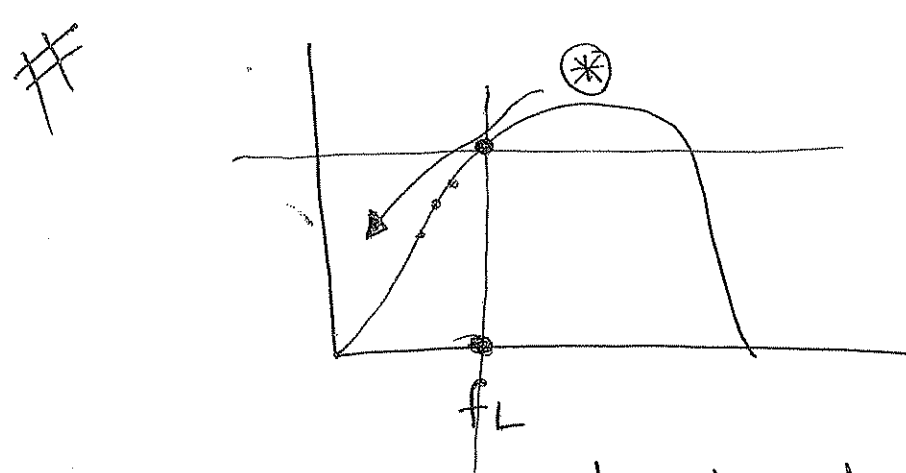
$$= \frac{10^6}{160 * 15 * \pi} = \underline{\underline{133 \text{ Hz.}}}$$




$f_{L(\text{eff})}$ = The highest value.
 $= 160 \text{ Hz.}$

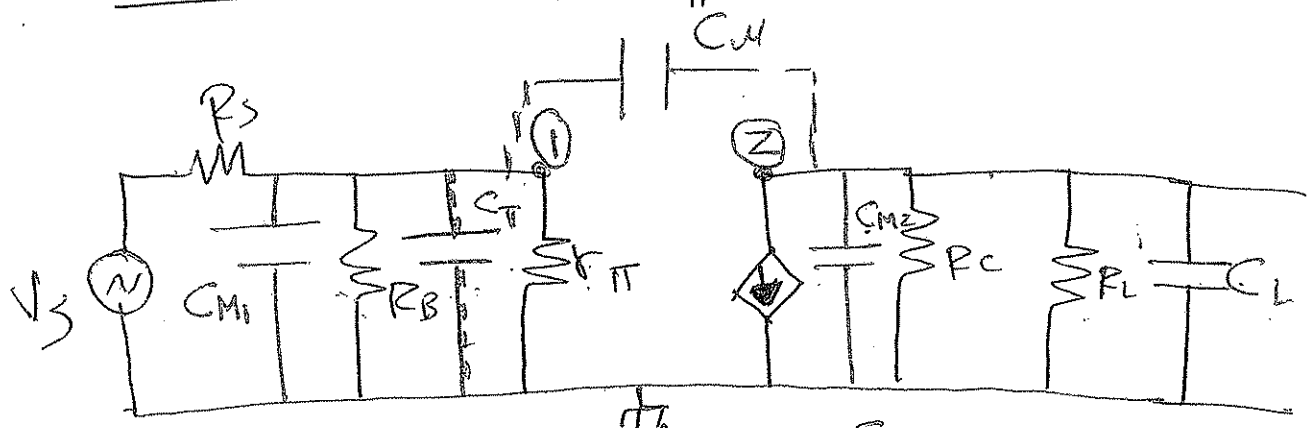③ H-F-R: $[C_{11}, C_{21}, C_E \rightarrow \text{S-C}$
 $C_M, C_{\pi}, C_L \rightarrow \text{exis.}]$



H-F-S-S-A-C Eqnt. ct. 7

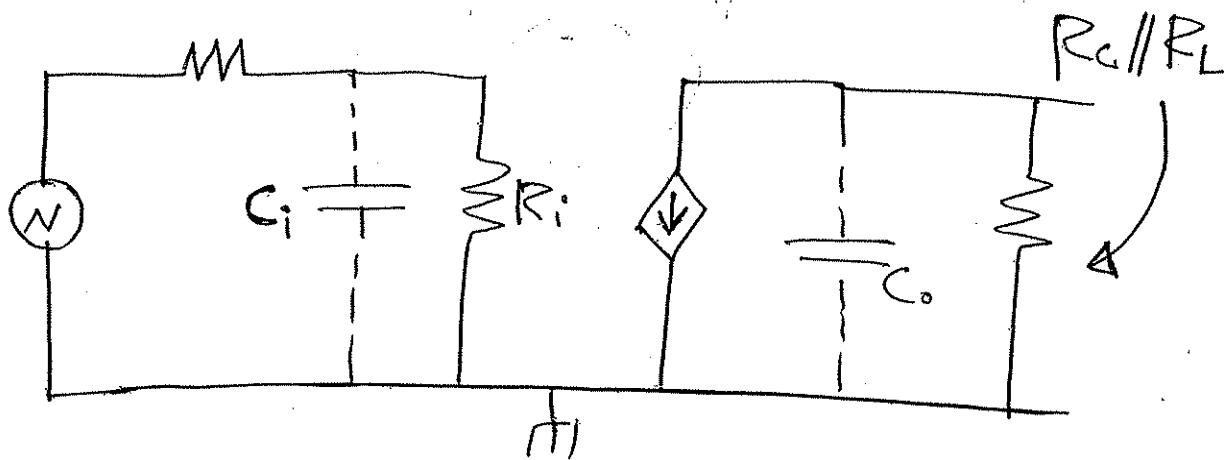

$$C_i = C_{\pi} + C_{M1}$$

$$C_o = C_L + C_{M2}$$

$$C_{M1} = C_{\mu} (1 - k)$$

$$C_{M2} = C_{\mu} \left(1 - \frac{1}{k}\right)$$

$$k = \frac{V_z}{V_i} = \frac{V_o}{V_i} = \frac{V_o}{V_{\pi}} = \frac{-g_m V_{\pi} (R_c || R_L)}{V_{\pi}}$$

$$k = -g_m (R_c || R_L)$$

$$= -78 (2 || 8) = -120$$

C.E, C.S. \rightarrow k_{av} $\alpha = \frac{v_i}{v_o}$

#

18

$$f_{Hi} = \frac{1}{2\pi C_i R_{eq_i}}$$

$R_{eq_i} = R_{in}$ seen by C_i

$$R_{eq_i} = (R_s \parallel R_i) = 0.3 \parallel 1.2 = 0.28 \text{ k}\Omega.$$

$$C_i = C_{M1} + C_{\pi}$$

$$C_{M1} = 2(1 - (-120)) = 242 \text{ p.F}$$

$$C_i = 242 + 10 = \underline{\underline{252 \text{ p.F}}}$$

$$f_{Hi} = \frac{1}{2\pi * 252 * 10^{-12} * 0.28 * 10^3}$$

$$= \frac{10^9}{150\pi} \approx \underline{\underline{2 \text{ MHz.}}}$$

$$f_{H_0} = \frac{1}{2\pi C_0 R_{eq2}}$$

$R_{eq2} = R_{Th}$ seen by C_0 .

$$R_{eq2} = R_c \parallel R_L = (2 \parallel 10) = 1.6 \text{ k}\Omega.$$

$$C_0 = C_{M2} + C_L$$

$$C_{M2} = C_M \left(1 - \frac{1}{k}\right)$$

BJT: $k \gg 1$

If $k \gg 1$ $\therefore C_{M2} \approx C_M = 2 \text{ pF.}$

$$C_0 = 2 \text{ pF} + 0.1 \text{ nF} = 102 \text{ pF.}$$


$$f_{H_0} = \frac{1}{2\pi * 102 * 10^{-12} * 1.6 * 10^3}$$

$$= \frac{10^7}{3.2\pi} = 1 \text{ MHz} \#.$$

f_{Heff} is the lowest value

\therefore — 1 MHz #.

10

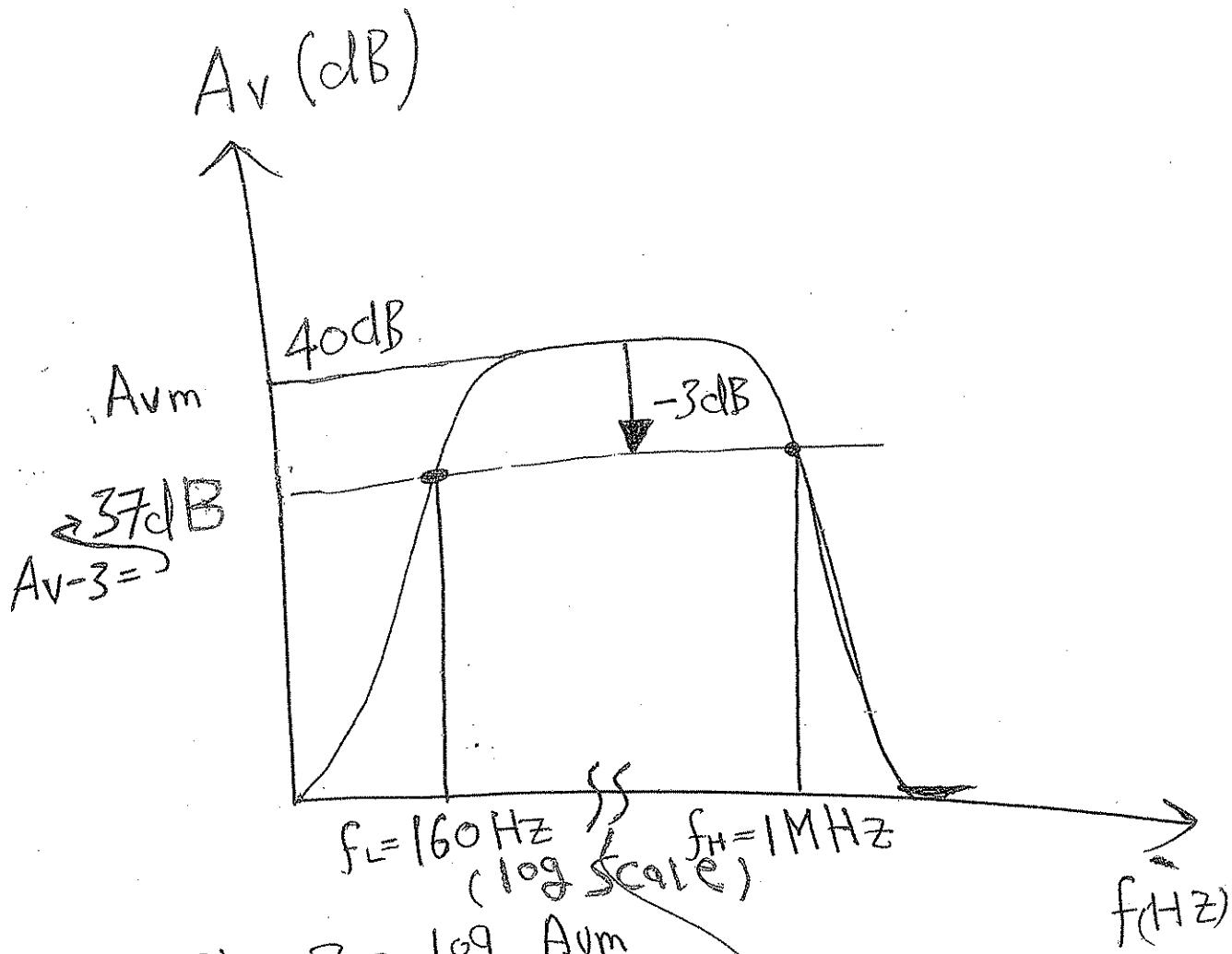


$$\begin{aligned}
 A_v(\text{dB}) &= 20 \log A_{vm} \\
 &= 20 \log 100 \\
 &= \underline{\underline{40\text{ dB}}}
 \end{aligned}$$

Very very long scale.

#



Freq. Resp. For C.S Amp. :-

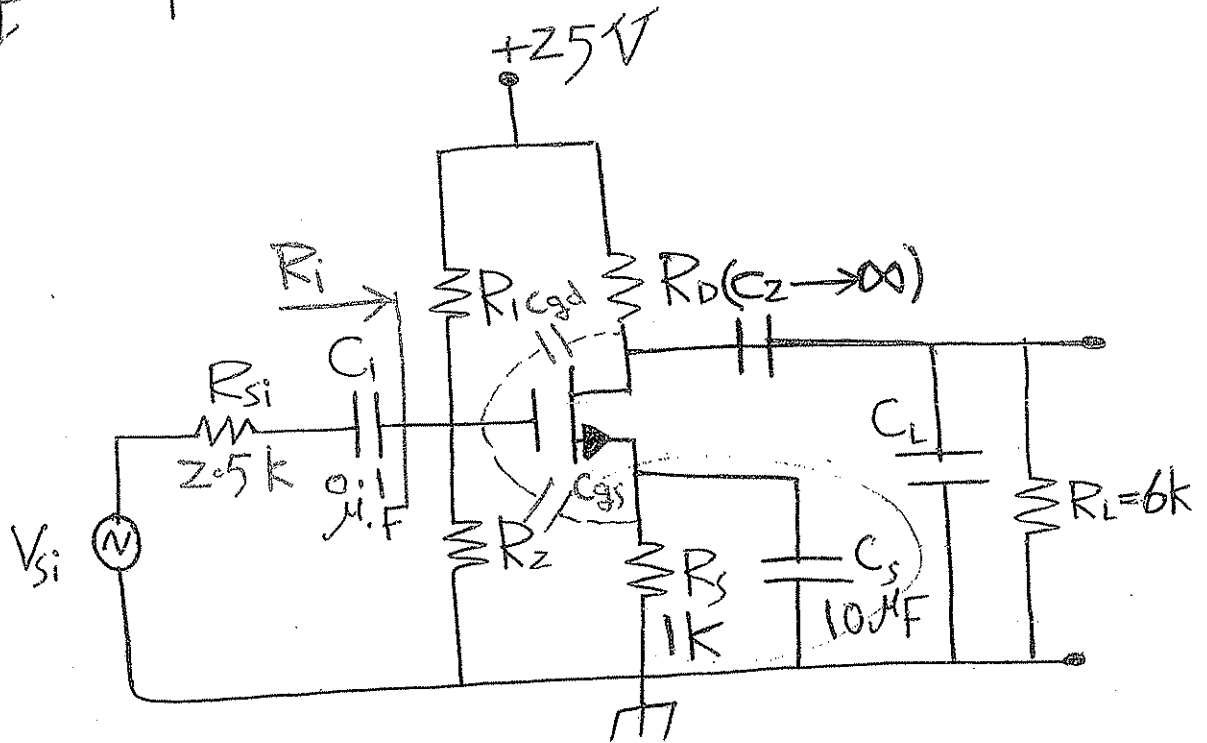

Given : $I_D = 5mA$.

$k_n = 1.25 mA/V^2$, $V_{TN} = 1V$, $\lambda = 0$

$C_{gs} = 20 pF$; $C_{gd} = 5 pF$.

1) Design the cct. to give $A_v = \frac{V_o}{V_{si}} = -8$
 (Find R_D, R_1, R_2) (let $R_i = 10k\Omega$).

2) Calculate f_L, f_H

3) Calculate C_L required to give $f_H = 30kHz$


4) Sketch freq. Resp.



Sol.

R_D ? M.F. Eqn. cct.

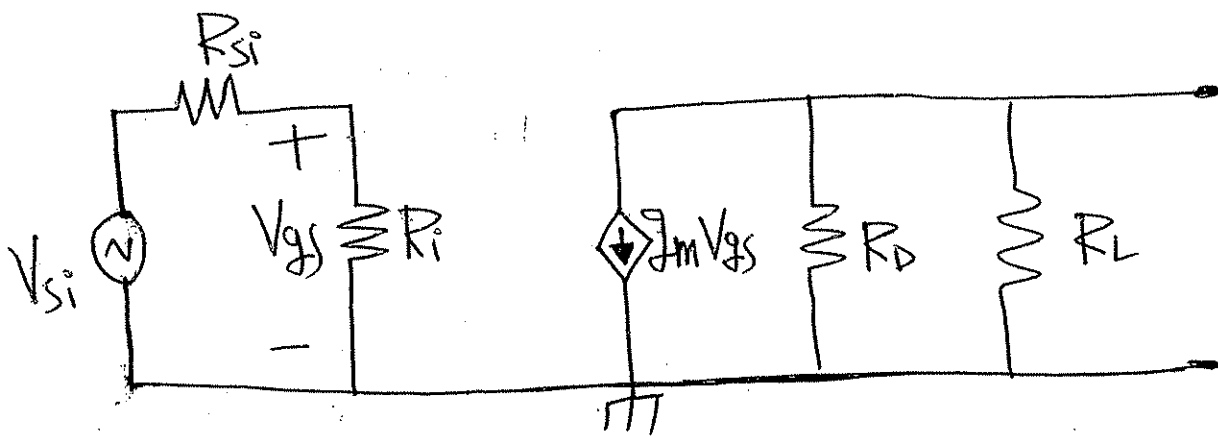$C_1, C_S \rightarrow S.C$, $C_{gd}, C_{gs}, C_L \rightarrow O.C.$



$$A_v = \frac{V_o}{V_{si}} = \frac{V_o}{V_{gs}} * \frac{V_{gs}}{V_{si}}$$

$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$\frac{V_o}{V_{gs}} = -g_m (R_D \parallel R_L)$$

V_{gs}

$$V_{gs} = \frac{V_{si} R_i}{R_i + R_{si}} \Rightarrow \frac{V_{gs}}{V_{si}} = \frac{R_i}{R_i + R_{si}}$$

$$A_v = -g_m \underbrace{(R_D \parallel R_L)}_{R_L'} \frac{R_i}{R_i + R_{si}'}$$

$$I_m = 2 \sqrt{k_n I_D} = 2 \sqrt{1.25 * 5}$$

$$= 5 \frac{\text{mA}}{\text{V}}$$

174

$$-8 = -5 \bar{R}_L \frac{10}{2.5 + 10}$$

$$-8 = -4 R_L' \rightarrow R_L' = 2 \text{ k}\Omega$$

$$= R_D \parallel 6 \text{ k}$$

$$\Rightarrow R_D = 3 \text{ k}\Omega \quad \#$$

R_1 & R_2 (from D.C.):

$$R_1 V_G = \frac{25 R_2 R_1}{R_2 + R_1} \rightarrow R_i$$

$$R_1 = \frac{25}{V_G} R_i$$

$$V_{GS} = V_G - V_S$$

$$V_G = V_{GS} + V_S$$

3

$$V_{GS} = V_{TN} + \sqrt{\frac{I_D}{k_n}}$$

$$= 1 + \sqrt{\frac{5}{1.25}} = 1 + \sqrt{4}$$

$$= 3V \text{ or } \textcircled{-1V}$$

X

$$V_S = I_D \cdot R_S = 5 * 1 = 5V.$$

$$V_G = 3 + 5 = 8V.$$

$$R_1 = \frac{25}{8} * 10 = \underline{31.25 \text{ k}\Omega}.$$


$$R_2 = \frac{R_1 * R_i}{R_1 - R_i} = \frac{31.25 * 10}{31.25 - 10}$$
$$= \frac{312.5}{21.25} = 14.75k.$$

$f_L \rightarrow (L.F. \text{ Eqnt. ckt.})$

176

$(C_1, C_s \rightarrow \text{exist})$, $(C_{gs}, C_{gd}, C_L) \rightarrow O.C$

$(C_2 \rightarrow S.C)$

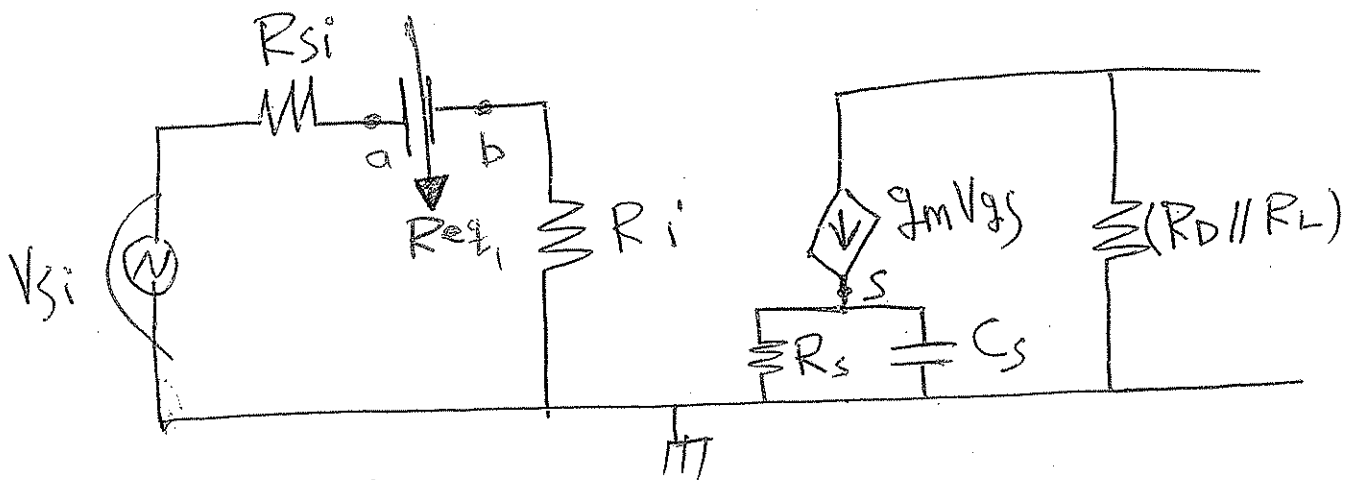

$$f_{L1} = \frac{1}{2\pi C_1 R_{eq1}}$$

$$R_{eq1} = R_{si} + R_i = 12.5 \text{ k}\Omega$$

$$f_{L1} = \frac{1}{2\pi * 1 * 10^{-7} * 12.5 * 10^3} = \frac{10^4}{25\pi} \text{ Hz} = 127 \text{ Hz}$$

$$f_{Ls} = \frac{1}{2\pi C_s \cdot R_{eq2}} = \frac{1}{2\pi C_s \cdot R_s}$$



$$= \frac{1}{2\pi * 10^{-5} * 1 * 10^3}$$

$$= \frac{100}{2\pi} = 16 \text{ Hz}$$

5

f_H ? \rightarrow (H.F. Eqnt. Ct.)

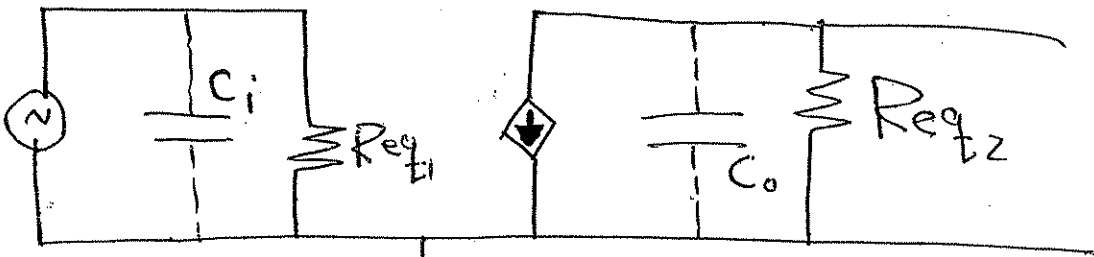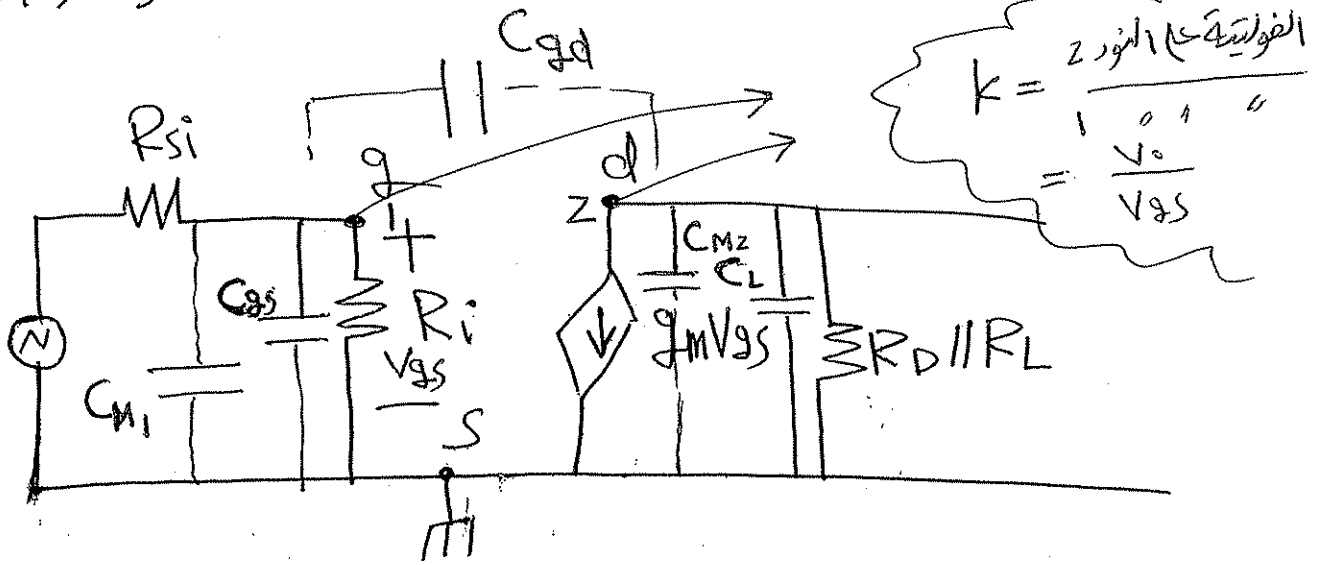$(C_1, C_5, C_2 \rightarrow s.c)$ و $(C_{gs}, C_{gd}, C_L \rightarrow \text{exist})$



$$f_{Hi} = \frac{1}{2\pi C_i R_{eq1}}$$

$$C_i = C_{M1} + C_{gs}$$

$$C_{M1} = C_{gd} (1 - k)$$

$$k = \frac{V_o}{V_{gs}} = \frac{-g_m V_{gs} (R_D \parallel R_L)}{V_{gs}}$$

$$k = -g_m (R_D \parallel R_L) = -5 * 2 = -10$$

□

$$C_{M1} = 5 (1 - (-10)) = 55 \text{ P.F.} \quad 178$$

$$C_i = 20 + 55 = 75 \text{ P.F.}$$

$$R_{eq1} = R_{s1} \parallel R_i = 2.5 \parallel 10 = 2 \text{ k}\Omega$$

$$f_{H1} = \frac{1}{2\pi * 10^3 * 75 * 10^{-12}} = \frac{10^9}{300\pi} = 1.1 \text{ MHz.}$$

$$f_{H0} = \frac{1}{2\pi R_{eq2} C_0}$$

$$\Rightarrow R_{eq2} = R_D \parallel R_L = 2 \text{ k}\Omega$$

$$\Rightarrow C_0 = C_{M2} + C_L \Rightarrow C_{M2} = C_{gd} \left(1 - \frac{1}{K}\right) = 5 \left(1 - \left(-\frac{1}{10}\right)\right) = 5.5 \text{ P.F.}$$


* Given $f_{H0} = 30 \text{ kHz}$ ∴ :-

$$C_0 = \frac{1}{2\pi R_{eq2} \cdot 30 * 10^3} = \frac{1}{2\pi * 3 * 10^4 * 2 * 10^3} = \frac{10^{-7} * 10^{12}}{12\pi} \text{ F} = \frac{10^5}{12\pi} \text{ P.F.} = 2600 \text{ PF} \quad \boxed{7}$$

$$C_L = 2600 - 5.5$$

$$= 2594.5 \text{ P-F.}$$

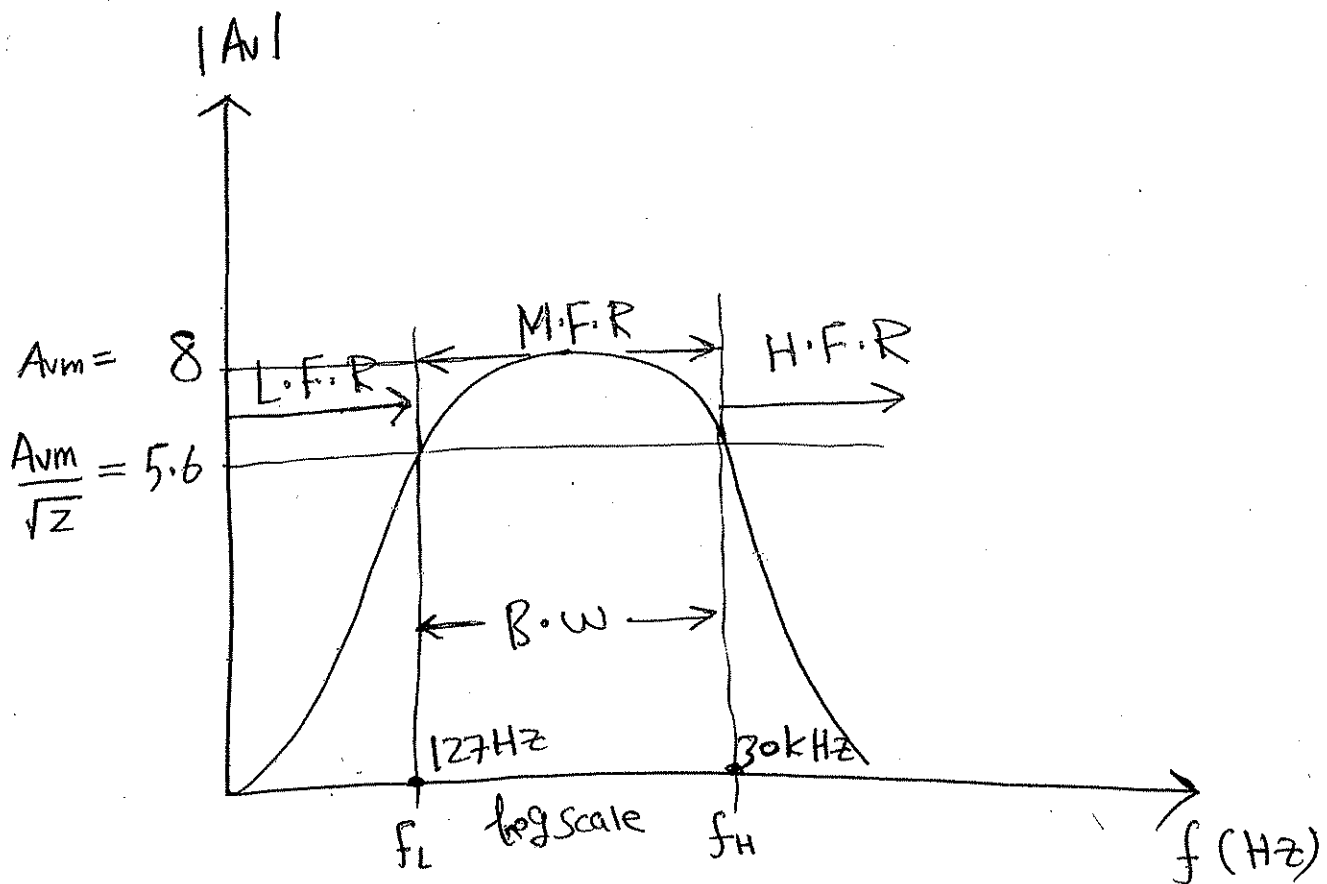$C \rightarrow 0 \rightarrow (X_C \rightarrow \infty) \rightarrow \text{Open ckt.}$
 $C \rightarrow \infty \rightarrow (X_C \rightarrow 0) \rightarrow \text{Short ckt.}$




فرضیات
 C_1 ، C_2 ، C_3

فرض موجودات

180

$|A_v|$ ↓

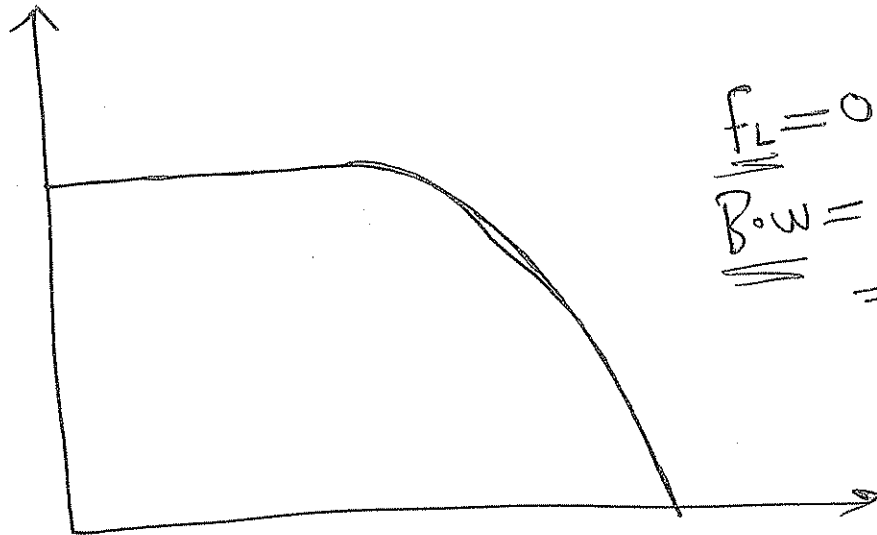

$$\underline{f_L = 0}$$
$$\underline{B.W = 30 - 0}$$
$$\underline{= 30 \text{ MHz}}$$

$f(\text{Hz})$




Q1: Design the MOSFET Amplifier

shown in Fig. to have
 midband voltage-gain
 of 10, and $f_L = 200\text{ Hz}$
 $f_H = 3\text{ kHz}$. The
 Amplifier input Resistance
 must not exceed $36\text{ k}\Omega$.

(Find R_1, R_2, C_1, C_L, R_D).

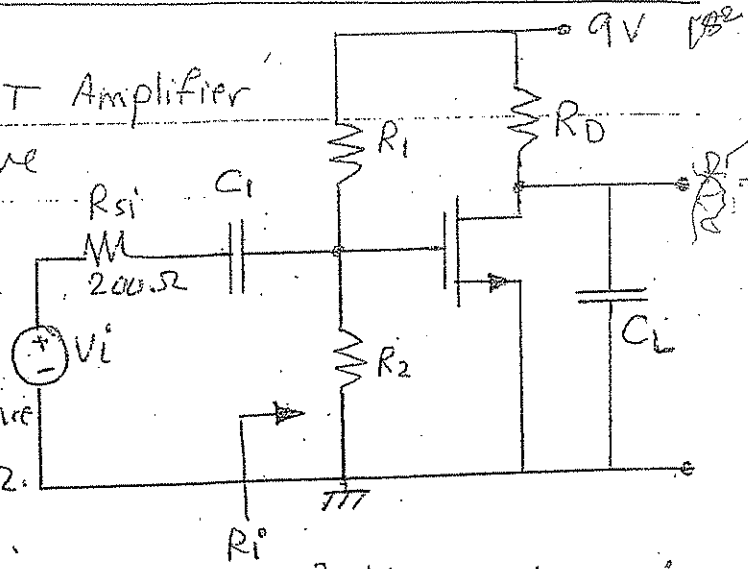* Use a MOSFET with $K_n = 0.3\text{ mA/V}^2$, $V_T = 1\text{ V}$ biased
 at $I_{DQ} = 0.2\text{ mA}$.



Q2: For the circuit shown in Fig.

The MOSFET parameters are:


$K_n = 1\text{ mA/V}^2$, $V_{TN} = 2\text{ V}$, $\lambda = 0$

$C_{gs} = 5\text{ pF}$, $C_{gd} = 1\text{ pF}$.

- 1) Draw the Small-Signal Equivalent cct. at low-, medium- and high-frequency.

- 2) Calculate f_L and f_H , B.W and the midband voltage-gain.

- 3) Sketch the frequency Response of the Amp. indicating $|A_{vm}|_{dB}$ versus frequency.

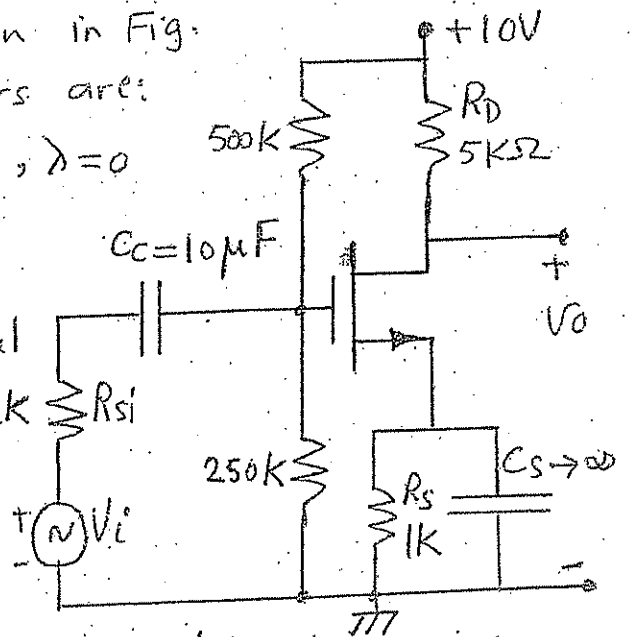


Q3: For the circuit shown in Fig.

the transistor parameters are:
 $\beta = 100$, $V_{BE} = 0.7V$, $V_A = \infty$,
 Neglect transistor internal
 capacitances,

1) Draw the low-, Midband.
 and high-Frequency Eqnt.
 circuits.

2) Calculate $|A_m|_{dB}$, f_L and f_H .

3) Sketch the frequency Resp.

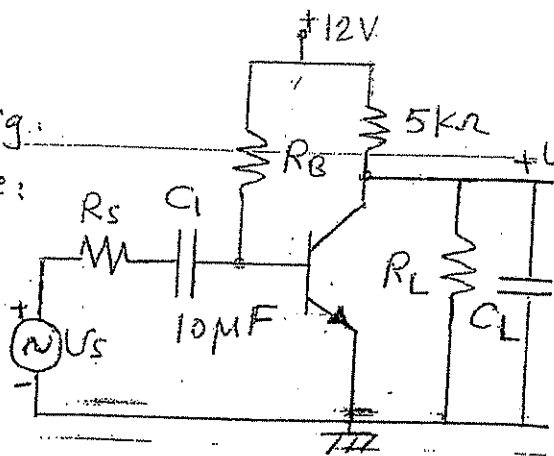

$$R_B = 1M\Omega$$

$$R_L = 500k\Omega$$

$$C_L = 10\mu F$$

$$R_s = 1k\Omega$$

Q4: For the Eqnt. circuit shown:

$$R_s = 4k\Omega, R_E = 400\Omega$$


$$R_c = 2k\Omega \text{ and the device}$$

$$\text{has } g_m = 70mA/V, V_{\pi} = 2k\Omega$$

$$\beta = 100, C_{\mu} = 5pF.$$

1) Calculate C_c required
 to give $f_L = 35Hz$.

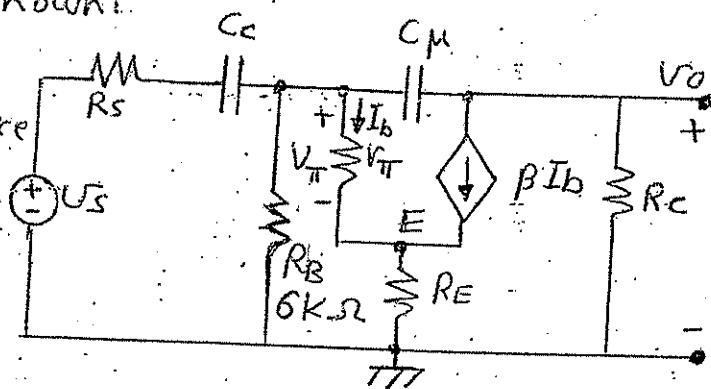2) Calculate A_m , f_H and sketch the frequency Resp.



Q5: For the circuit shown the device

is biased at $I_{CQ} = 0.32mA$ and

has $V_A = 200V$, $\beta = 120$, $C_{\mu} = 1pF$.

unity-gain freq. $f_T = 600MHz$.

$$(f_T = \frac{g_m}{2\pi(C_{\mu} + C_{\pi})})$$

1) Calculate f_L , f_H , $|A_m|_{dB}$.

2) Sketch the freq. Response.

