



تقدم لجنة EICoM الاكاديمية

دفتر لمادة:

الالكترونيات (2)

من شرح:

د.هادي العيثاوي

جزيل الشكر للطالب:

مؤمن القطامي



"Chapter 1"


(1) سطر 61

(*) Mosfet Amplifiers:

- The Mosfet must be biased in sat. Re to be used as an amplifier.

$K_n = 1$

$V_{TN} = 2V$

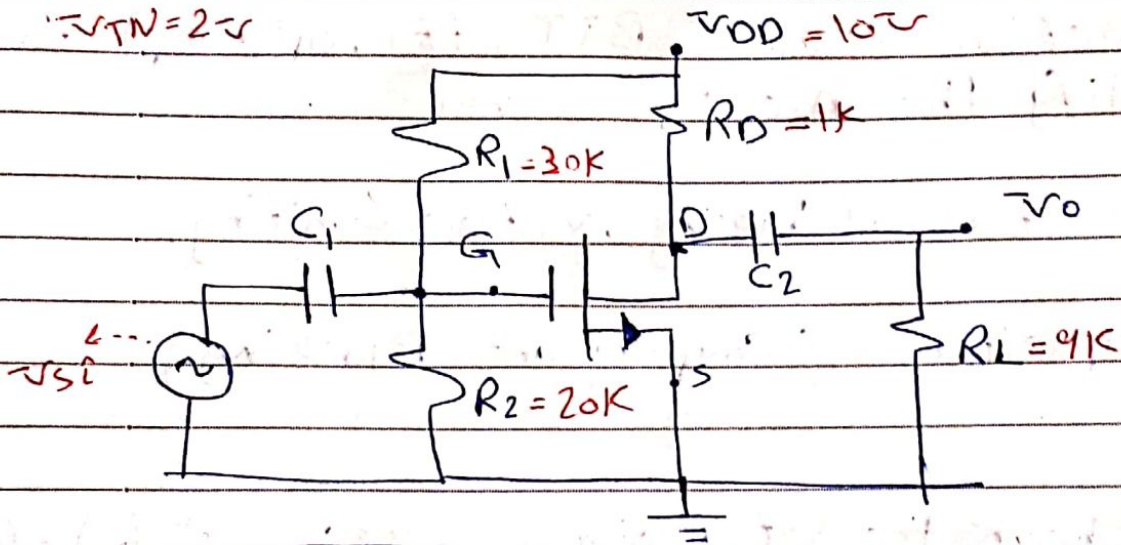

Source) V_{si} (AC source voltage) ← Signal voltage ← V_{si} (AC source voltage)

AC source voltage ← Signal voltage ← V_{si} (AC source voltage)

biasing. ← Voltage ← (R_2, R_1) divider (*)

voltage limiting ← R_D Resistor. (*)

Coupling and blocking : Capacitors (*) وظيفة

O.S for DC and S.C for AC.

نفسه، لا ينفصل بالتيار المستمر (D.C) ويمنع التيار المتردد (A.C) من المرور. (تسمى بـ "كابتور" في د.C) وفي س.ك ينفصل

D.C voltage → V_{DD} وظيفة لتوفير الجهد للـ Mosfet في Sat

2

Any Amplifier Contains:

① Dc sources to bias the device in proper mode (sat for Mosfet)
(F.A.M for BJT).

Diode


② Active device (BJT, FET, op-Amp) to Amplify the A.C. i/p signal.

③ Resistors : (biasing, voltage Limiting)

④ Capacitors: (Coupling and Blocking)
A.C S.C D.C O.C

- to check the sat. Region: $\omega \ll \omega_{L}, \omega_{C}, \omega_{P} \otimes$
Dc Analysis must be carried out:

① All Capacitors O.C:

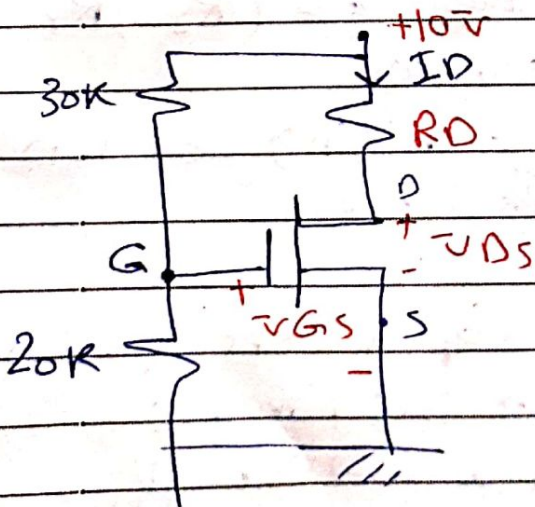

$$V_{GS} = V_G - V_S$$

$$V_G = \frac{10 \times 20}{50} = 4V$$

$$V_{GS} = V_G = 4V$$

- Assume the Mosfet in sat:

$I_D = k_n (V_{GS} - V_{TN})^2$ — (1)

$I_D = 4mA$

to find V_{DS} :

$-10 + I_D R_D + V_{DS} = 0$

$V_{DS} = 6V$

$V_{DS}(sat) = V_{GS} - V_{TN}$ — (2)

$V_{DS}(sat) = 2V$

since $V_{DS} > V_{DS}(sat)$, Mosfet in sat Region

$P_D = I_D V_{DS} = 24mWatt$

- D.C.L.L and Q-point

KVL for Drain source loop:

$-10 + I_D R_D + V_{DS} = 0$

$I_D = \frac{10 - V_{DS}}{R_D}$

$I_D = -\frac{1}{R_D} \cdot V_{DS} + 10$

slope


$y = mx + b$

m: slope.

- for equa (2):

for $I_D = 0$, $V_{DS} = 10V$ $P_1 (10V, 0)$

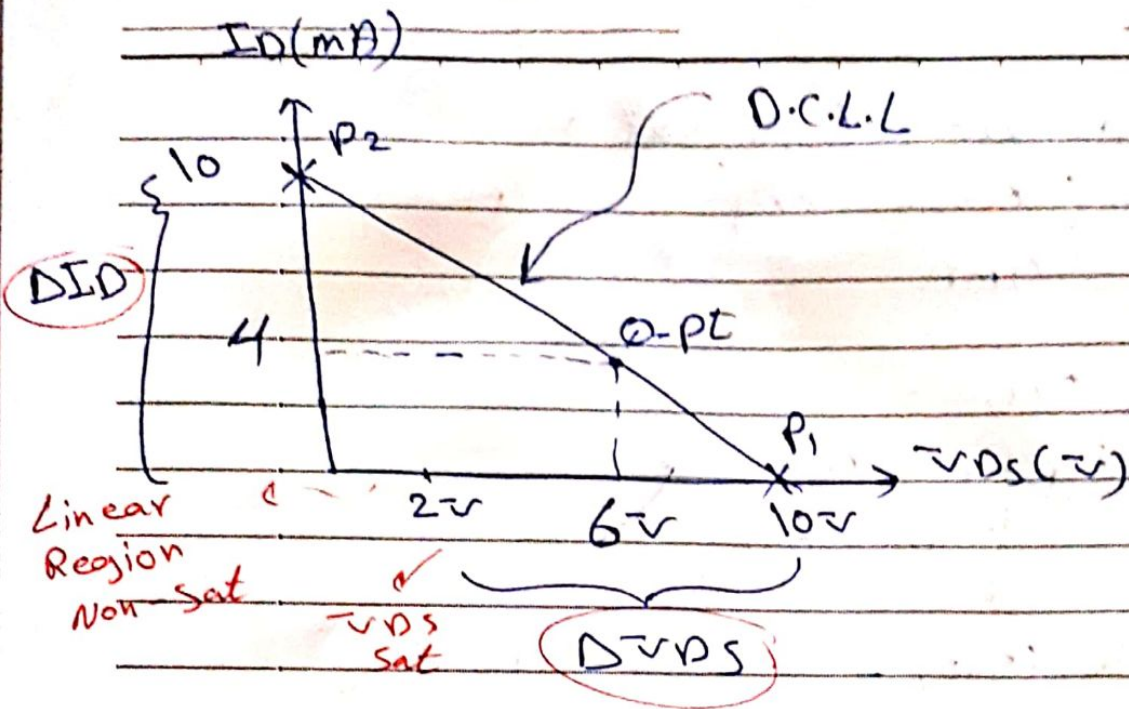for $V_{DS} = 0$, $I_D = 10mA$ $P_2 (0, 10mA)$



- slope = $-\frac{\Delta I_D}{\Delta V_{DS}} = -1 \text{ mA/V}$ or $-\frac{1}{R_D} = -1 \text{ mA/V}$

Q-P (V_{DSQ}, I_{DQ}), (6V, 4mA)

* Repeat D.C. Analysis
 (calculate I_D, V_{DS}), for $R_D = 2.5 \text{ k}\Omega$
 $- V_{GS} = 4 \text{ V}$ (المنطق)

$I_D = K_n (V_{GS} - V_{TN})^2 = 4 \text{ mA}$

$V_{DS} = 10 - I_D R_D = \text{zero}$

But $V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 2 \text{ V}$
 since $V_{DS}(\text{sat}) > V_{DS}$, so mosfet in
 Non-Sat Region.


$I_D = K_n (2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2)$ (3)

$\frac{10 - V_{DS}}{R_D} = (4V_{DS} - V_{DS}^2) \rightarrow$ Obtain 2 values
 for V_{DS} , the correct value for

$V_{DS}, V_{DS} < V_{DS}(\text{sat})$.


(5)

2021 5/10/2021

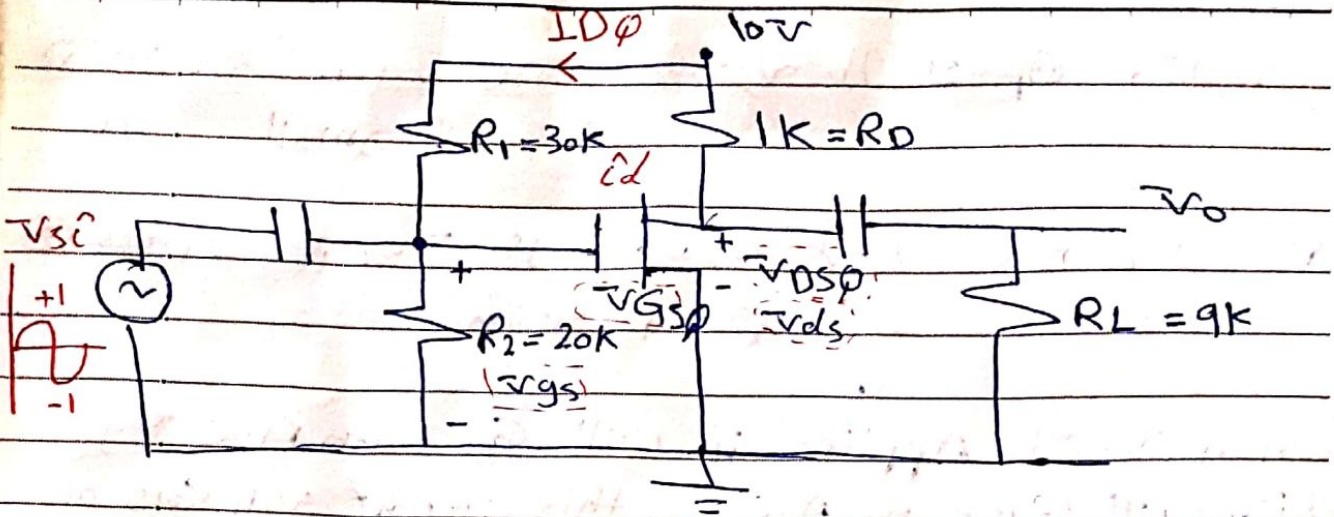

- From DC $\rightarrow V_{GSQ} = 4V, I_{DQ} = 4mA$
 $V_{DSQ} = 6V, V_{TN} = 2V, k_n = 1mA$

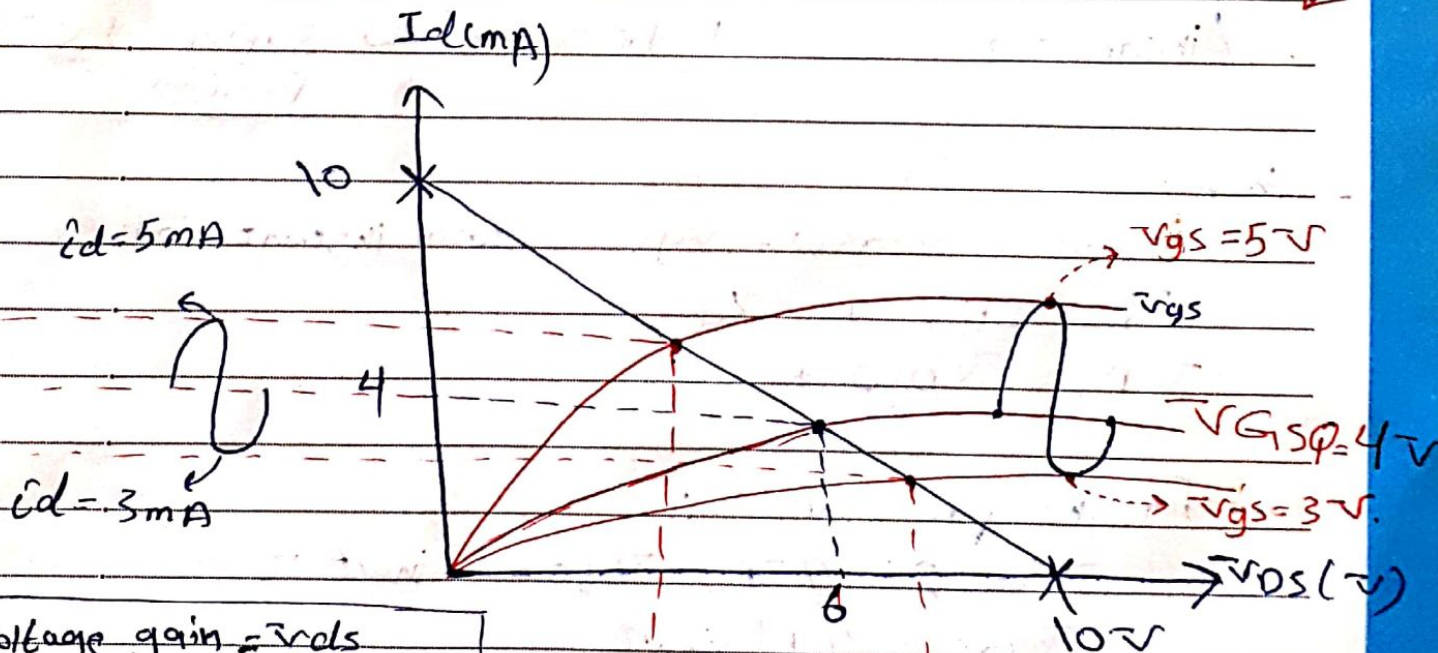
$$I_D = k_n (V_{GS} - V_{TN})^2, \quad I_{DT} = 4 + I_d$$



Voltage gain = $\frac{v_{ds}}{v_{sc}}$

AC $\frac{1}{1}$ DC $\frac{1}{1}$
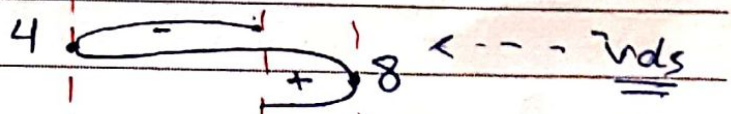
$$\frac{v_{ds}(p1)}{v_{sc}p} = \frac{5-1}{1-1} = -2$$



6

A.C \hat{v}_{gs} , Capital I_D \hat{v}_{gs} , D.C v_{GS} \hat{v}_{gs} \hat{v}_{ds} \hat{v}_{gs}
Small I_D

D.C I_D A.C \hat{v}_{gs} \hat{v}_{ds} Total I_D \hat{v}_{gs}
"super position"

- When \hat{v}_{gs} is Applied it will cause an A.C \hat{v}_{gs} which will cause an A.C \hat{i}_d , this current will cause an A.C \hat{v}_{ds} .

- But, the Amplifier contains A.C and D.C, the total response will be $A.C + D.C$, According to super position theorem, because Amplifier is linear cct.

Linear cct \hat{v}_{gs} \hat{v}_{ds} super position

- then: I_D $A.C$
 $v_{GS} = v_{GS0} + \hat{v}_{gs} \rightarrow$ total instantaneous
 $i_D = I_{D0} + \hat{i}_d$
 $v_{DS} = v_{DS0} + \hat{v}_{ds}$

- For the previous cct:

$$v_{GS0} = 4V, \hat{v}_{gs} = 1\sin\omega t V$$
$$v_{GS} = 4 + 1\sin\omega t$$

7

* Ac Analysis using Mosfet Model (equivalent cct)

- For Ac analysis all Capacitors and Dc → short cct.


1

$$X_c = \frac{1}{2\pi f c} \Rightarrow \text{For D.C} \rightarrow f=0 \Rightarrow X_c = \infty \Rightarrow \text{O.C}$$



$$\Rightarrow \text{For A.C} \rightarrow f = \uparrow \Rightarrow X_c = \text{zero} \Rightarrow \text{S.C}$$

→ (obtain Ac cct)

2] Replace Mosfet by it's model.

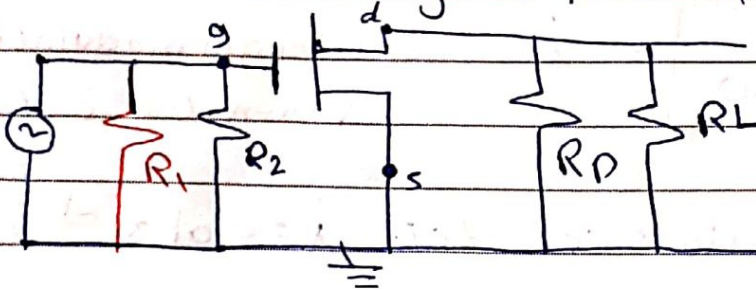

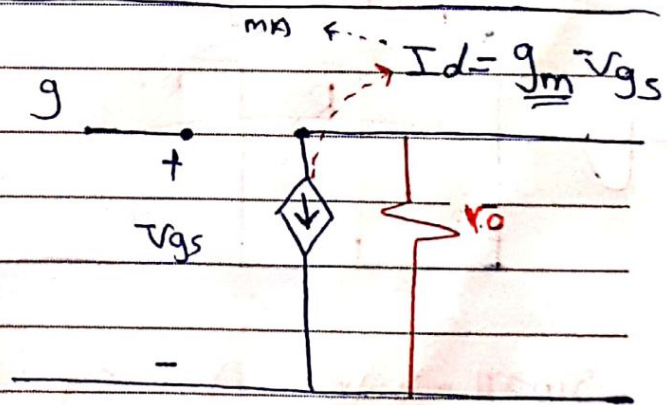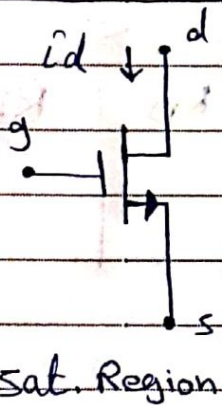في د.س. نغلق كل المكثفات و نفتح كل المكثفات في ا.س. نغلق كل المكثفات و نفتح كل المكثفات



gm: Trans conductance

$$\left(\frac{A}{V}, \frac{mA}{V}, \frac{\mu A}{V} \right) \dots$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\partial (k_n (V_{GS} - V_{TN})^2)}{\partial V_{GS}}$$

⇒

$$g_m = 2k_n (V_{GS} - V_{TN}) \text{ OR } g_m = 2\sqrt{k_n I_D}$$

9


⊗ لا فلكيف، انحر، gm ، تقدر الـ قيم، D.C ، لا بد من
D.C analysis

⊗ المقاومة r_o : هي المقاومة التي تكونها التوازي بين drain و source . تسمى "output resistance"

- If the Mosfet has an o/p resistance r_o , then it must be included in model.

$r_o = \frac{1}{\lambda I_{DQ}}$ ، λ : Channel length modulation parameter (v^{-1})

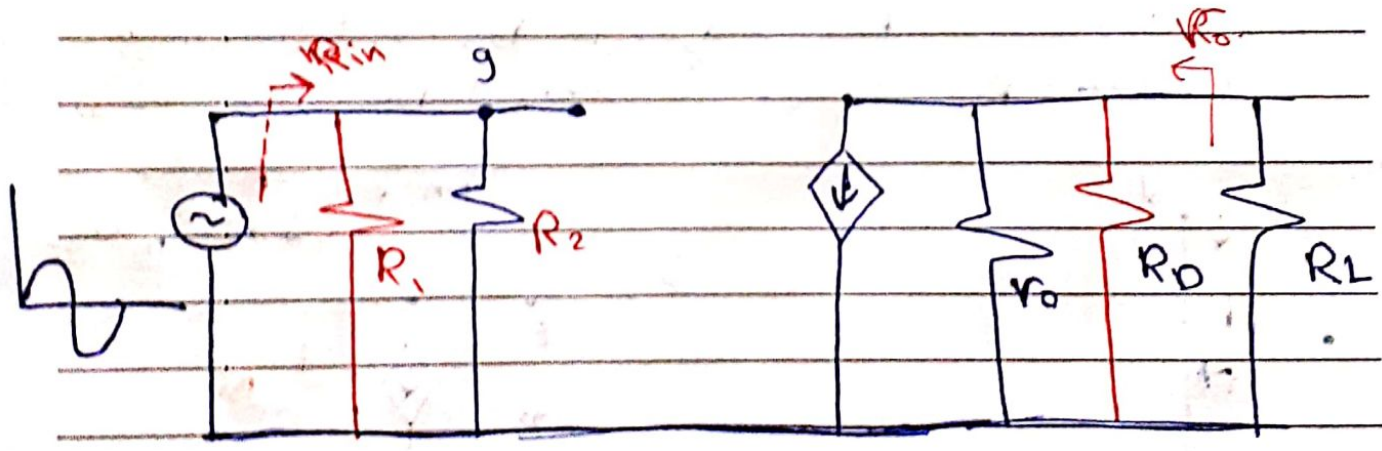- In the previous cct let $\lambda = 0.01 v^{-1}$



"Small-signal A.C equivalent cct"

ليس يتبعها هيك I_D لأنهم مبصر، فلكيف، (Transistor) ، منطق ، منطق
Sat region


هيك يتغير هالك، لاسم ، هيك فلكيف ، "Linear cct"

(9)

Input Resistance :

$$R_{in} = R_1 \parallel R_2 = 20 \parallel 30 = 12 \text{ k}\Omega$$

- output Resistance : $R_o = \frac{v_x}{I_x} \Big|_{v_{sc} = 0}$

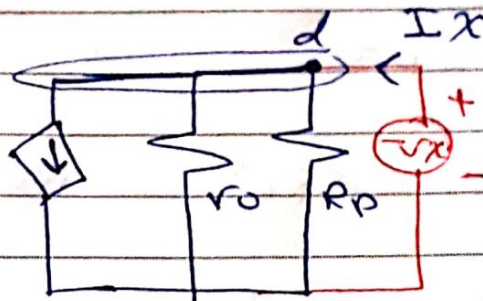


- KCL at Node (d):

$$I_x = \frac{v_x}{R_D} + \frac{v_x}{r_o} + g_m v_{gs}$$

- but when $v_{sc} = 0$, $v_{gs} = 0$
then $g_m v_{gs} = 0$

$$I_x = v_x \left(\frac{1}{r_o} + \frac{1}{R_D} \right)$$
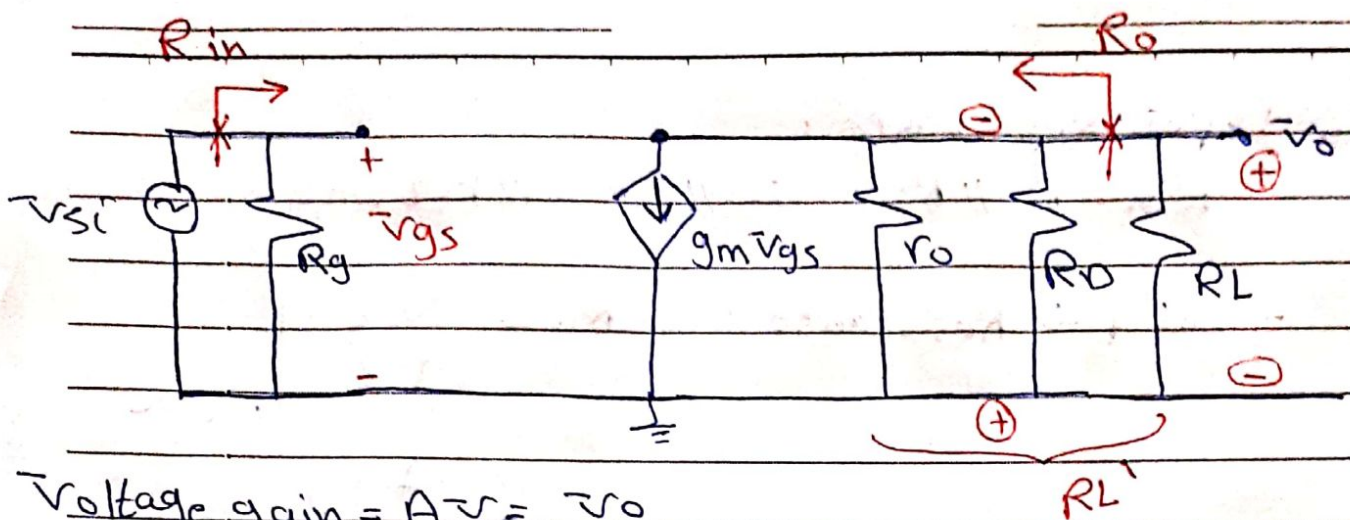
$$\frac{I_x}{v_x} = \frac{1}{R_o} = \frac{1}{r_o} + \frac{1}{R_D} \Rightarrow R_o = r_o \parallel R_D$$



Voltage gain = $A_v = \frac{v_o}{v_{s_i c}}$

$v_o = -g_m v_{gs} R_L'$; $R_L' = r_o \parallel R_D \parallel R_L$

$v_{gs} = v_{s_i c}$; $\therefore A_v = \frac{-v_o}{v_{s_i c}} = \frac{-g_m v_{gs} R_L'}{v_{s_i c}} =$

$A_v = -g_m R_L'$

↳ phase shift of 180° between v_o and v_sic

$g_m = 2 \sqrt{K_n I_D} \Rightarrow g_m = 4 \text{ mA/V}$

$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 4 \times 10^{-3}} = 25 \text{ k}\Omega$

$A_v = -4 (25 \parallel 1 \parallel 9) \approx -4 \times 0.85 = -3.4$

$A_v = \frac{v_o}{v_{s_i c}} \Rightarrow v_o = A_v \cdot v_{s_i c} = -3.4 v_{s_i c}$
 ↳ تضخم

تذكر : $R_o \leftarrow$ excluded R_L
 بحيث ان تغير R_L لا يؤثر في قيمة R_o


بما R_L لا تتغير مع A_v ، كما ان R_L قد تتغير
 تذكر r_o هي مقاومة داخل MOSFET (نصف) انما هو

(11)

A.C.L.L D.C.L.L

* A.C Load Line:

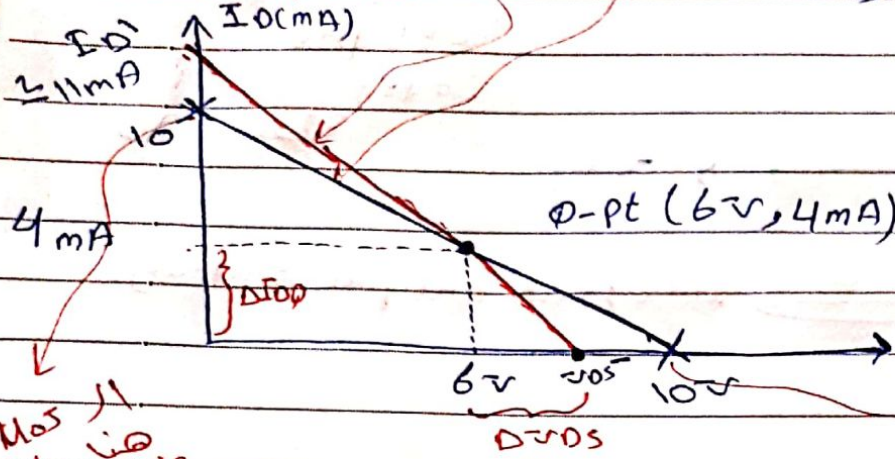
Slope = $-\frac{1}{1k\Omega} = -\frac{1}{R_D} = -\frac{1}{1k}$



Mos ...
Cut-off

$\Delta v_{DS} = v_{DS} - v_{DSQ}$

write KVL for A.C ckt.

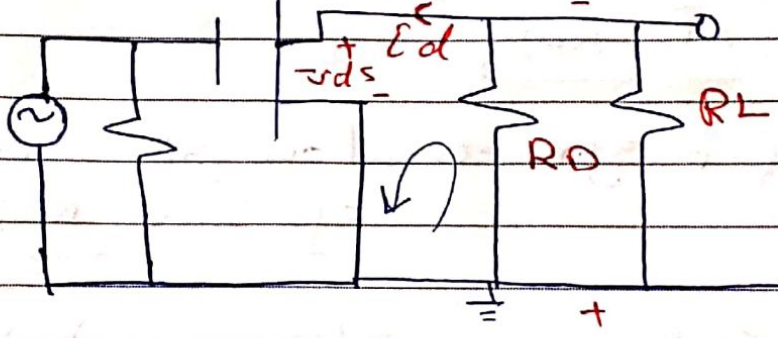

$v_{DS} + i_d(R_D // R_L) = 0 \Rightarrow v_{DS} = -i_d(R_D // R_L)$

∴ A.C.L.L equation

$i_d = -\frac{1}{R_D // R_L} * v_{DS} \Rightarrow \text{slope} = \frac{-1}{R_D // R_L} = \frac{-1}{1 // 9}$

$v_{DS} = v_{DSQ} + \Delta v_{DS}$

$i_D = I_{DQ} + \Delta i_D$

⇒


$v_{DS}' = v_{DSQ} + \Delta v_{DS}$

5.2x 1.2x 1.2

Slope $\Rightarrow \frac{\Delta I_D}{\Delta v_{DS}} \Rightarrow \Delta v_{DS} = \text{slope} * \Delta I_D = -R_L // R_D * \Delta I_D$

$|\Delta v_{DS}| = I_{DQ} (R_L // R_D) = 3.6 \text{ V}$

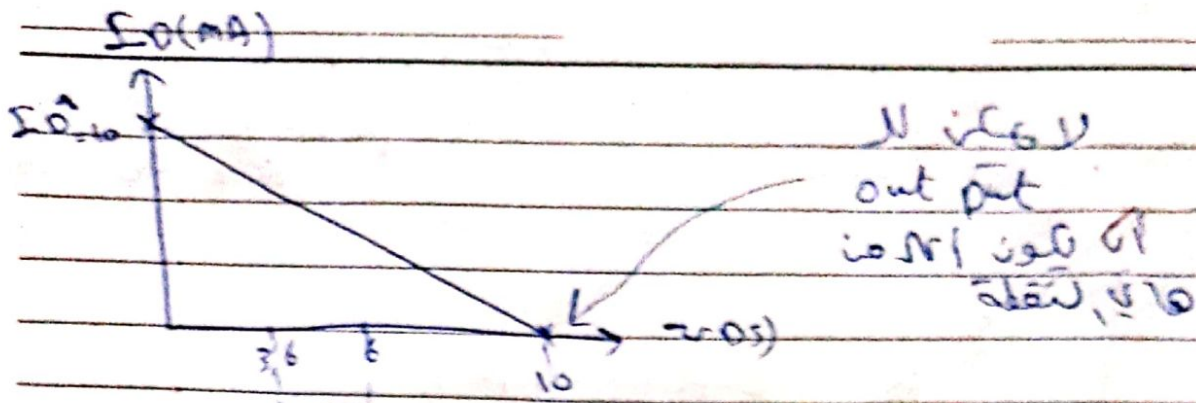$I_{DQ} = 4 \text{ mA}$
 $v_{DS}' = 9.6 \text{ V}$




Max P-P out put voltage \longleftrightarrow Max peak out put voltage

Max peak symmetrical out put voltage = ΔV_D
 $= I_{DQ} (R_D // R_L)$

Max P-P symmetrical out put voltage = $2 \times \Delta V_D$
 $= 2 I_{DQ} (R_L // R_D)$

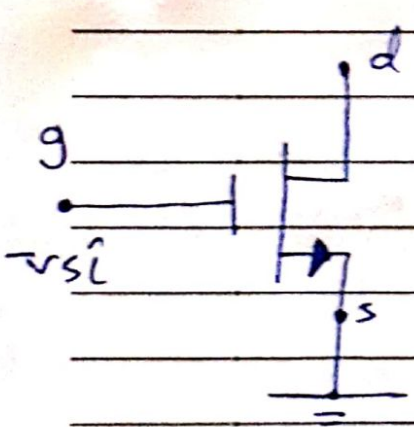Slope D.C $\angle =$ Slope A.C $\frac{1}{6} \rightarrow 200 \text{ V}$ \otimes



- Amp. configuration (Connection) C.S


Common source Amp

- S \rightarrow Common Terminal.
- Input to gate 1.
- output to drain 1.

① Basic Common source Amp.
 (S \rightarrow directly connected to ground).


Mosfet Amp Configuration:

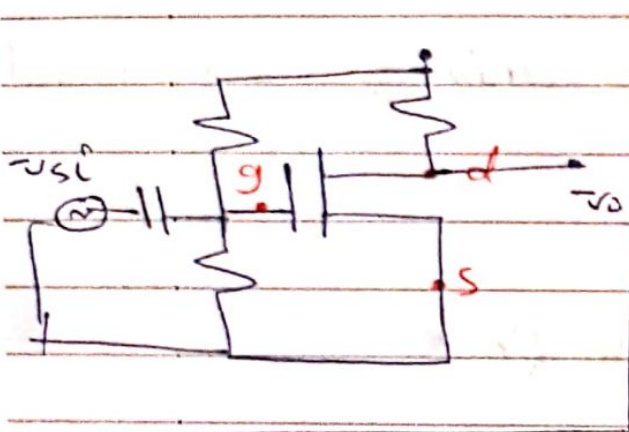① C.S Amp :- (input to gate), (out put from drain)
source → Common terminal




$\phi = 180^\circ$
out is In

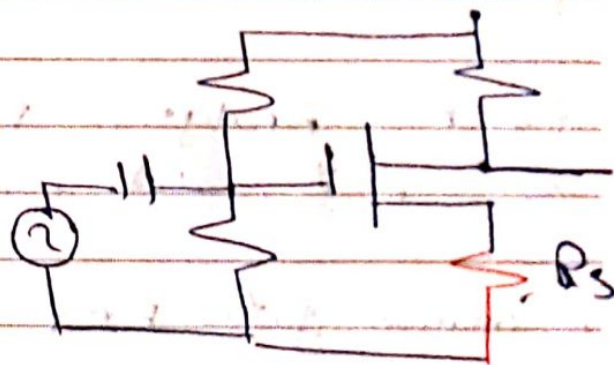② C.S with R_s
"source-follower"
 $A_v \approx 1$




③ C.S with by pass Capacitor

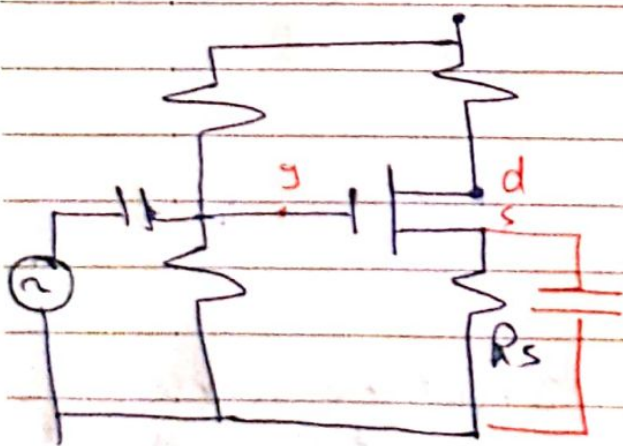

2] Common drain Amp:

"Input to gate out from source"

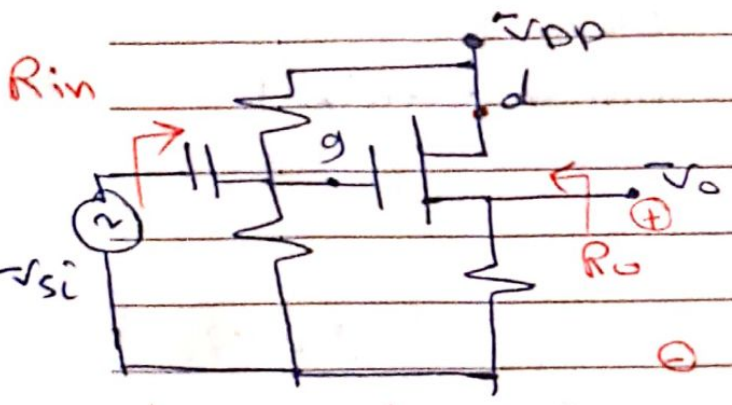


drain \rightarrow Common terminal

$\phi = 0 \Rightarrow v_o, v_{si} \Rightarrow$ in phase.

For A.C Analysis D.S.S.C \rightarrow v_p, v_{si} \rightarrow v_o
 $\phi = 0$ \rightarrow v_o, v_{si} in phase

3] Common gate Amp \Rightarrow G.G. Amp.

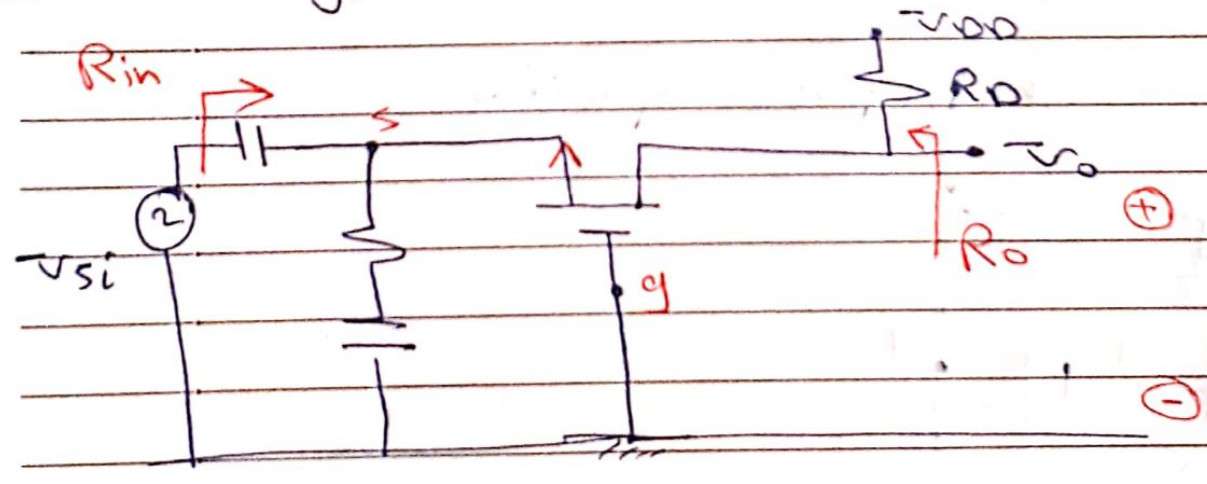


$\phi = 0$

"Input to source out put from drain"

Common terminal: gate

C.S. Amp: C.S with source resistance:

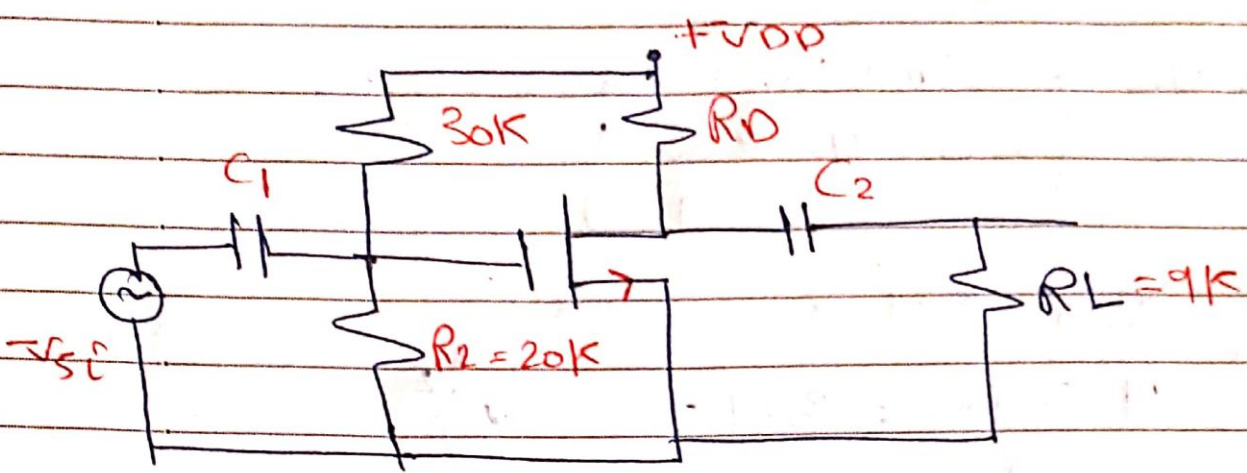


$K_n = 1 \text{ mA/V}^2$, $V_{TN} = 2 \text{ V}$, $\lambda = 0.01 \text{ V}^{-1}$

Sol: from D.C analysis \Rightarrow
 $V_{GS} = 4 \text{ V}$, $I_D = 4 \text{ mA}$, $V_{DS} = 6 \text{ V}$, $V_{DS(sat)} = 2 \text{ V}$.

$I_D = 1 \text{ mA} \leftarrow K_n = 2.5$ و كذا K_n ج
 $V_{DS} = 0 \leftarrow V_{D(sat)}$

لا نقدر ان نحصل على I_D من V_{GS} و V_{DS} في حال $V_{DS} < V_{DS(sat)}$
 و V_{GS} في حال $V_{GS} < V_{TN}$ و كذا V_{GS} في حال $V_{GS} < V_{TN}$
($0.1 \text{ K}\Omega$) \leftarrow source

For D.C Analysis \Rightarrow

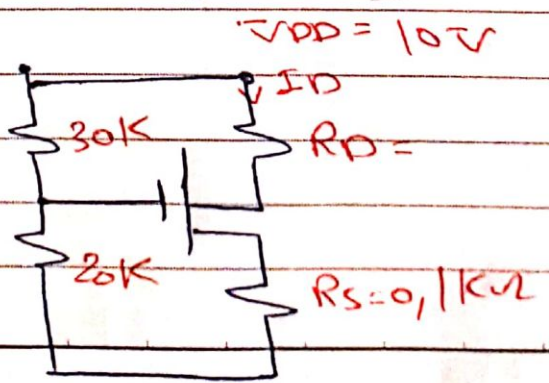

16

Assume the Mos in sat Region.

$$I = \frac{10}{50k} = 0,2 \text{ mA}$$

$$\Rightarrow \text{KVL: } -0,2 \text{ mA} \times 20k + V_{GS} + I_D \cdot R_S = 0$$

$$\boxed{I_D = \frac{4 - V_{GS}}{0,1}}$$

$$\Rightarrow I_D = K_n (V_{GS} - V_{TN})^2$$

$$\frac{4 - V_{GS}}{0,1} = 2,5 (V_{GS} - 4)^2$$

$$4 - V_{GS} = 2,5 \times 0,1 (V_{GS}^2 - 4V_{GS} + 4)$$

$$\frac{3}{0,25} = V_{GS}^2 \Rightarrow \boxed{V_{GS} = \sqrt{12} \text{ Volt}}$$


(mos) sat (constant)

V_D

17

"الطاقة رقم 5"

* C.s with R_s :

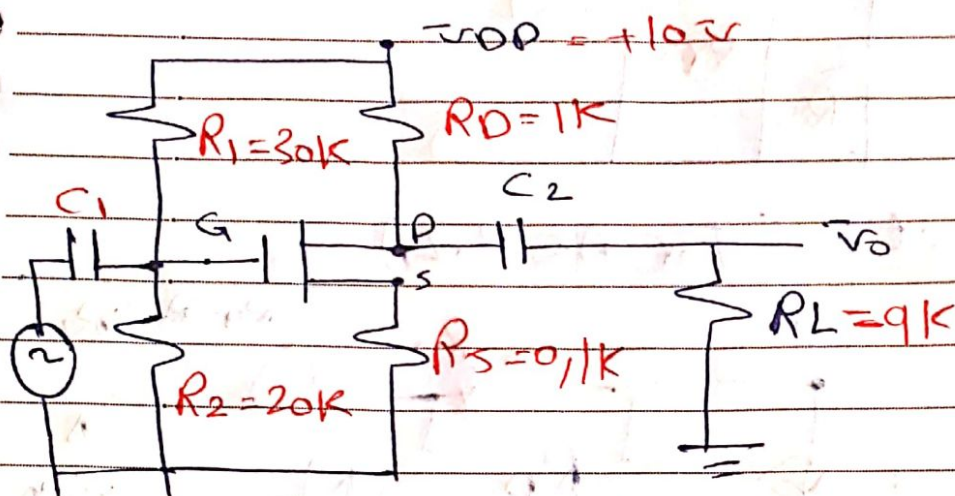

$K_n = 2,5 \text{ mA/V}^2$

$V_{TN} = 2 \text{ V}$

$\lambda = 0$

- * Calculate: ① V_{GSQ} , I_{DQ} , V_{DSQ} , V_s , V_D , P_D
- ② Draw S.S.A.C equivalent cct, Determine A_v , R_{in} , R_o .

③ Write D.C and A.C L.L and find their slope.

Sol: From D.C analysis:

$V_{GSQ} = 3,45 \text{ V}$, $I_D = 5,5 \text{ mA}$,


$V_{DS} = 3,95 \text{ V}$, $V_{D(sat)} = 1,45 \text{ V} \approx 1 \text{ V}$.

$V_s = I_D \cdot R_s = 0,55 \text{ V}$


$V_{DS} = V_D - V_s \Rightarrow V_D = 3,95 + 0,55 = 4,5 \text{ V}$

$P_D = \text{power dissipated in the Mos} = I_D V_{DS}$
 $= 5,5 \text{ mA} \times 3,95 = \dots \text{ mWatt.}$

18

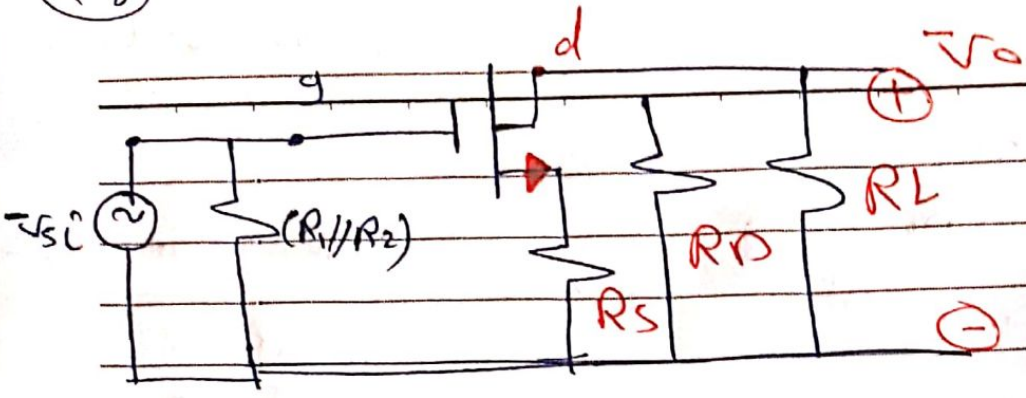

A.C cct. (for A.C L.L)

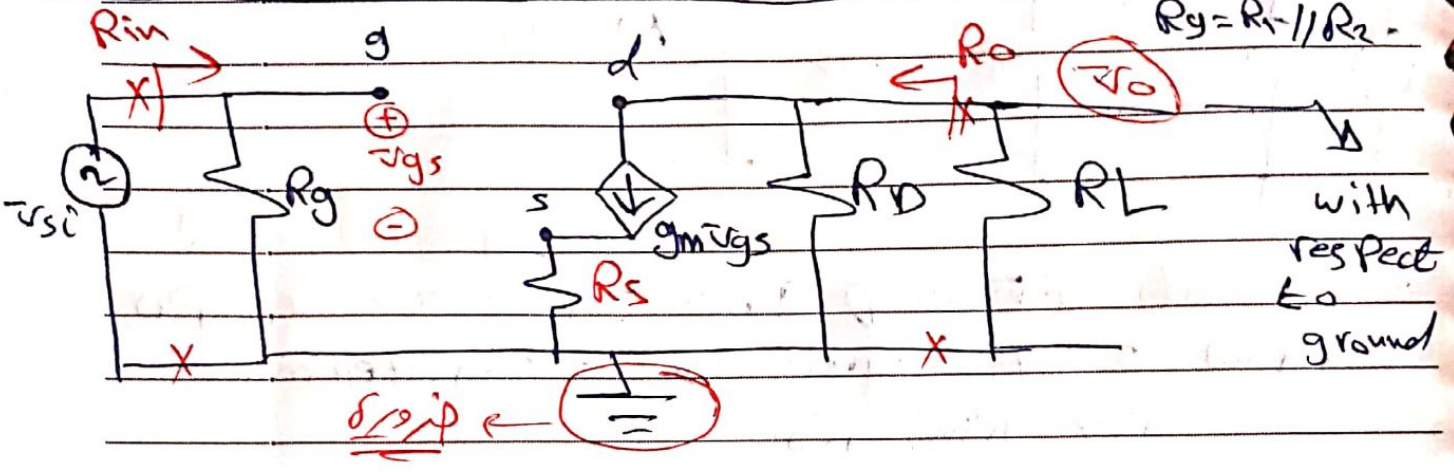

"Small signal equivalent circuit"

$$\frac{A_v}{A_v} = \frac{v_o}{v_{sc}} \Rightarrow v_o = -g_m v_{gs} (R_D || R_L)$$

$$-v_{sc} = v_{gs} + g_m v_{gs} R_s$$

$$\boxed{\frac{v_{sc}}{1 + g_m R_s} = v_{gs}}$$

$$v_o = -g_m \left(\frac{v_{sc}}{1 + g_m R_s} \right) (R_D || R_L)$$

$$\boxed{\frac{v_o}{v_{sc}} = A_v = \frac{-g_m (R_D || R_L)}{1 + g_m R_s}}$$

19

phase between v_{si} and v_o .

$A_V = \ominus 2,3 \Rightarrow \phi = 180^\circ, A_V > 1$

Note that R_S reduces A_V .

- R_S , stabilize ϕ pt against k_n parameter variation. (A_V), $v_{ds} < 0$,

$\Rightarrow R_{in} = R_g = R_1 // R_2 = 12k\Omega$

$\Rightarrow R_o = \frac{v_x}{I_x} \Big|_{v_{si}=0} \Rightarrow$ Dependent source is open ckt, $R_o = R_D = 1k\Omega$.

- D.C.L.L $\Rightarrow -v_{DD} + I_D R_D + v_{DS} + I_D R_S = 0$

$v_{DS} = v_{DD} - I_D (R_D + R_S)$

slope $\Rightarrow -\frac{1}{R_D + R_S}$

- A.C.L.L \Rightarrow


$v_{DS} + I_D R_S + I_D (R_D // R_L) = 0$

$v_{DS} = -I_D (R_S + R_D // R_L)$

slope = $-\frac{1}{(R_S + R_D // R_L)}$

* C.S with by-pass capacitor:

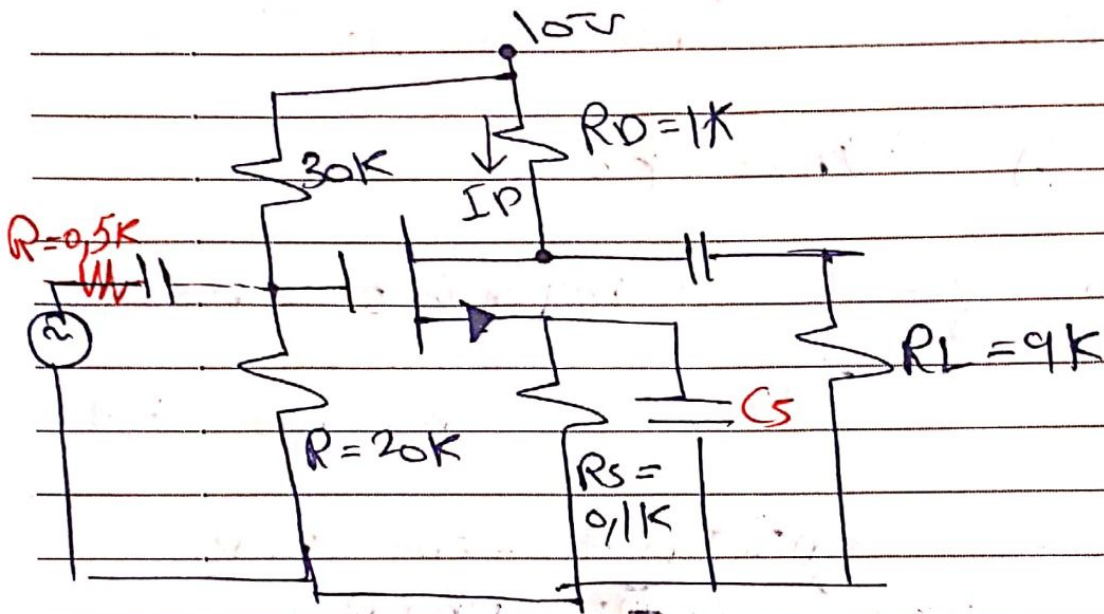عند V_{GSQ} و I_{DQ} و V_{DSQ} و V_D و V_S و A_v و P_{max} و R_{in} و R_o و $A.C$ و $S.C$ و $D.C$ و open circuit



- 1] Find V_{GSQ} , I_{DQ} , V_{DSQ} , V_D , V_S .
- 2] Draw S.S. A.C eq ckt and find A_v , R_{in} , R_o .
- 3] Write D.C, A.C. L.L equs and find their slopes
- 4] Calculate Max(P-P) Symmetrical o/p Voltage.

Sol: For D.C Analysis



- all caps \rightarrow a.c

The ckt is analysed as Common source with

~~R_S $V_{GSQ} = 3.45V$, $I_{DQ} = 5.5mA$, $V_{DSQ} = 3.95V$~~

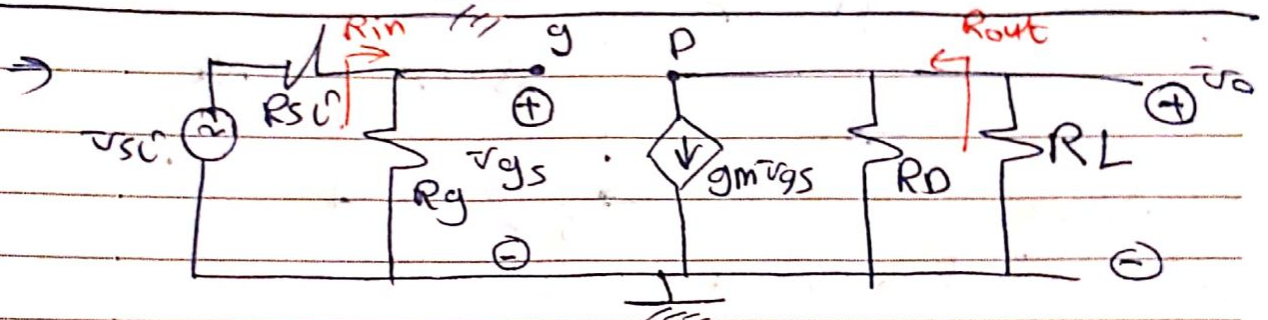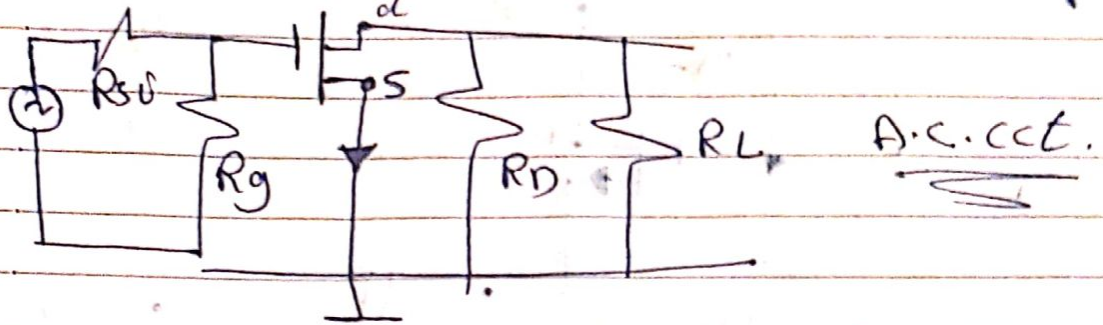(21)

- For A.C all caps and D.C sources are s.c and the cct behaves as basic C.S. Amp.



- $R_{in} = R_g$, $R_o \Rightarrow \frac{v_x}{I_x} \Big|_{v_{gs}=0} = R_D$

$A_v = \frac{v_o}{v_{sc}} \Rightarrow v_o = -g_m v_{gs} (R_D // R_L)$

$v_{gs} = \frac{v_{sc} \times R_g}{R_{sc} + R_g}$

$v_o = -g_m \left(\frac{v_{sc} \times R_g}{R_{sc} + R_g} \right) \times (R_D // R_L)$

A_v $\frac{v_o}{v_{sc}}$


$\frac{v_o}{v_{sc}} = A_v = -g_m \left(\frac{R_g}{R_{sc} + R_g} \right) \times (R_D // R_L) = -\frac{G}{2}$

- Max (p-p) \rightarrow Symmetrical out put voltage

$\therefore \text{Iromax (p-p)} = \boxed{2 \times 100 (R_L // R_D)} = \boxed{9, 9V}$

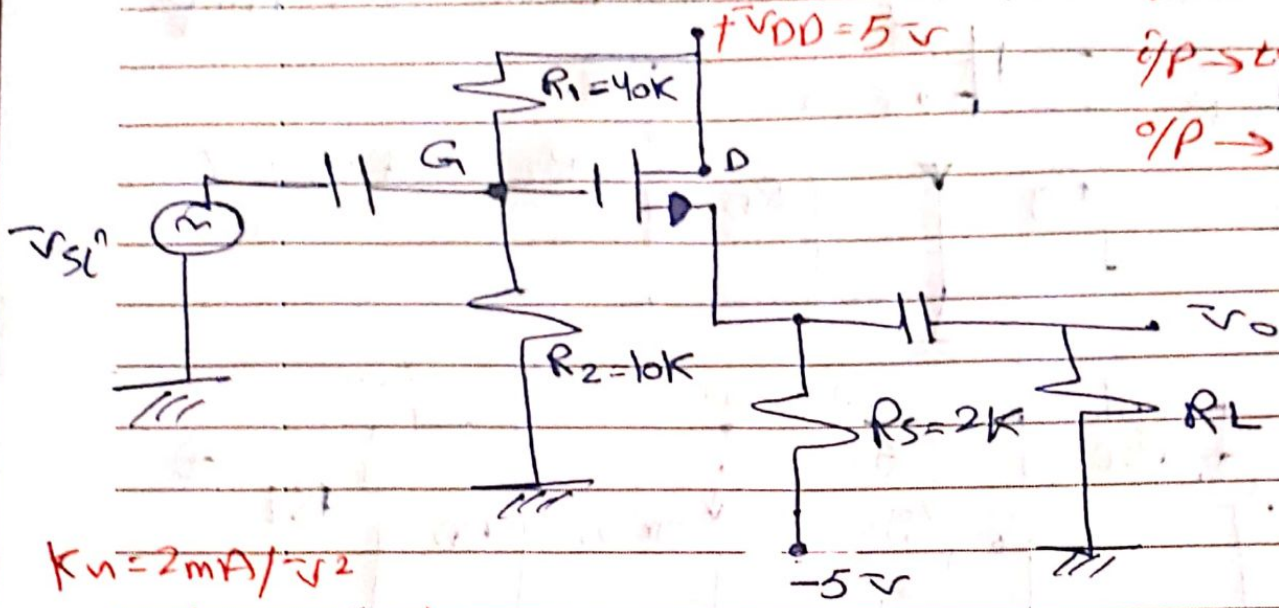2) Common Drain Amp.

For A.C:
Disat ground
i/p -> source
o/p -> from s



$K_n = 2 \text{ mA/V}^2$

$V_{TN} = 1 \text{ V}, \lambda = 0.02 \text{ V}^{-1}$

- 1) Calculate, V_{GSQ}, I_{DQ}, v_{DSQ}
- 2) Draw s.s. A.C equivalent circuit, find A_v, R_{in}, R_o .
- 3) write P.C and A.C.L.L and find slopes.

- For D.C, all capacitors \circ C:

$-V_{DD} + I(50k) = 0 \Rightarrow I = \frac{5}{50k} = 0.1 \text{ mA}$

\Rightarrow KVL: $-V_{R2} + V_{GS} + I_D R_S = 5 \Rightarrow I_D = \frac{6 - V_{GS}}{2}$

$I_D = K_n (V_{GS} - V_{TN})^2 \Rightarrow$

$\frac{6 - V_{GS}}{2} = 2 (V_{GS}^2 - 2V_{GS} + 1)$

$6 - V_{GS} = 4V_{GS}^2 - 8V_{GS} + 4 \Rightarrow 4V_{GS}^2 - 7V_{GS} - 2$

$V_{GS} = -0.25V$, $V_{GS} = 2V \rightarrow V_{TN}$ منه
 $I_{DQ} = 2mA$, $V_{DSQ} =$


$\rightarrow -V_{DD} + V_{DS} + I_D R_S = 0 \Rightarrow V_{DS} = 6V$

$V_{DS}(sat) = V_{GS} - V_{TN} = 2 - 1 = 1V$


$V_{GS} = -1V$, $V_D = 5V$

Amplifier 5 solution \leftarrow Sat منه

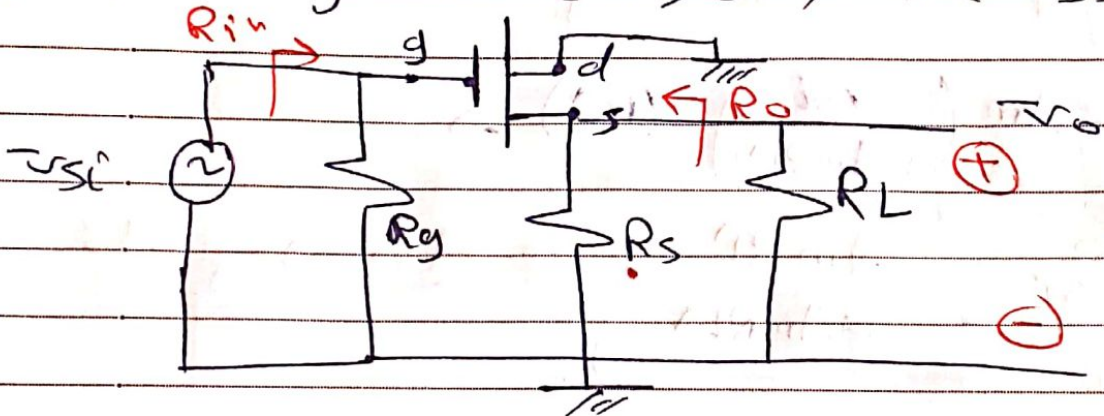* A.C analysis: C \rightarrow S, D.C \rightarrow S



A.C. cct s.s.

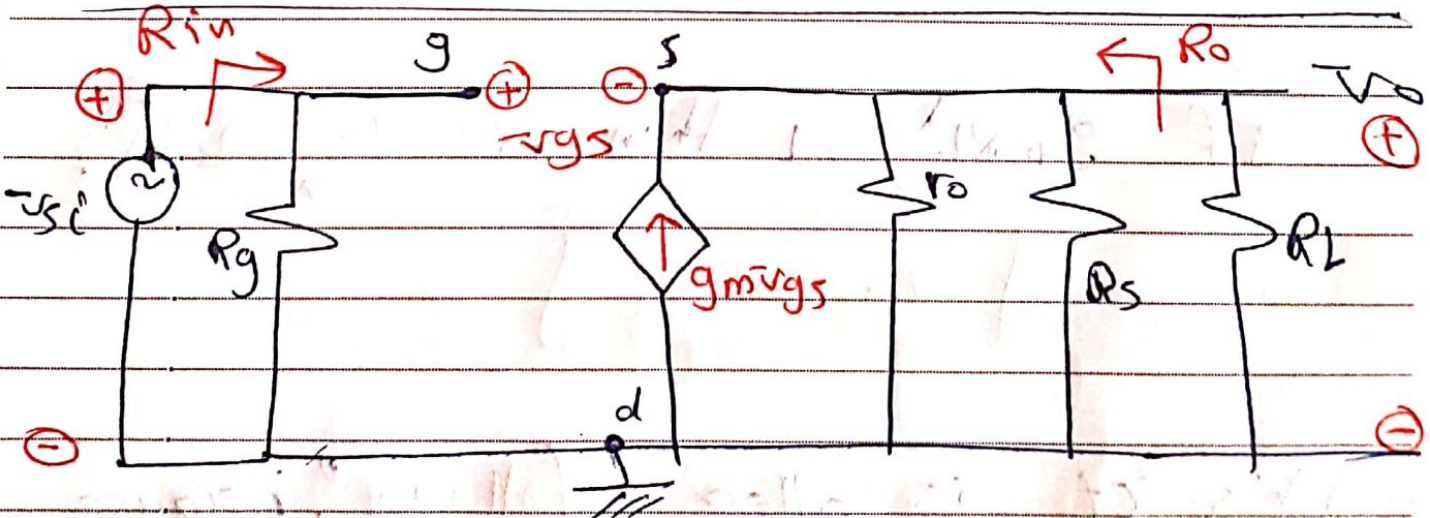

$R_{in} = R_g = R_1 // R_2 = 8K\Omega$

$$V_o = g_m v_{gs} (r_o \parallel R_S \parallel R_L)$$

⇒ Loop → (v_{gs} , v_o) ⇒

$$-v_{sc} + v_{gs} + v_o = 0 \Rightarrow$$

$$-v_{sc} + v_{gs} + g_m v_{gs} (R_L) = 0$$

$$v_{sc} = v_{gs} (1 + g_m R_L)$$

$$v_{gs} = \frac{v_{sc}}{1 + g_m R_L}$$

$$* v_o = g_m \left(\frac{v_{sc}}{1 + g_m R_L} \right) (R_L) \Rightarrow$$

$$A_v = \frac{v_o}{v_{sc}} = \frac{g_m R_L}{1 + g_m R_L}$$

① $v_o \approx v_{sc}$

$$A_v < 1, \Phi = \text{zero} \left(\frac{v_o}{v_{in}} \right)$$


If $g_m R_L \gg 1$ then $A_v = \frac{v_o}{v_{in}} = 1$ ①

$$v_o \approx v_{sc}$$

- This ckt is called "follower", because v_o is approximately follows v_{sc} in taken from source.

فوزر ckt، لا نستطيع أن نأخذها من المصدر ← Amp

25

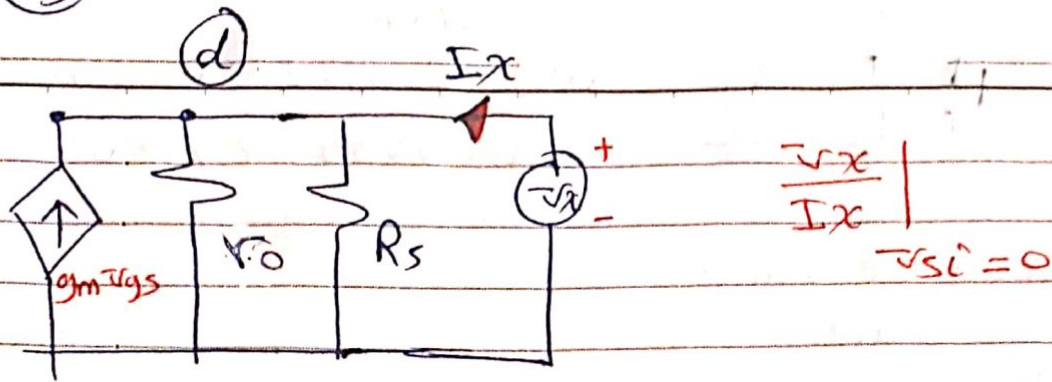

- KCL at Node (d):

$$\sum I_{in} = \sum I_{out} \Rightarrow g_m v_{gs} + I_x = v_x \left(\frac{1}{r_o} + \frac{1}{R_s} \right)$$

- Look, when $v_{sc} = 0 \Rightarrow$ then $v_{gs} = -v_x$

$$I_x = \frac{v_x}{r_o} + \frac{v_x}{R_s} + v_x g_m$$

$$\frac{I_x}{v_x} = \frac{1}{R_o} = \frac{1}{r_o} + \frac{1}{R_s} + g_m \quad \text{then}$$

$$R_o = (r_o \parallel R_s \parallel \frac{1}{g_m}) \Rightarrow \text{Note: Low } \underline{R_o}$$

$$R_o = \frac{1}{I_D} \parallel R_s \parallel \frac{1}{2\sqrt{k_n I_D}} \Rightarrow 250\Omega \parallel 25k \parallel 2k$$

$$\approx \boxed{220\Omega} \rightarrow \text{See def in def.}$$

$$\text{D.C.L.L} \Rightarrow -5 + v_{DS} + I_D R_s - 5 = 0$$

$$v_{DS} = 10 - I_D R_s$$

$$\text{Slope} \Rightarrow -\frac{1}{R_s} = -\frac{1}{2k}$$

(*) A.C.L.L \Rightarrow

$$v_{DS} + I_D (R_s \parallel R_L) = 0 \Rightarrow \text{Slope} \Rightarrow \frac{-1}{R_s \parallel R_L}$$

26




Common Drain
 DC I.D. is I_D
 A.C. I.D. is I_D

"7" \bar{v}_o , v_i v_o


* Common-gate Amp:

- i/p to source.
- o/p from drain.
- gate: Common terminal.

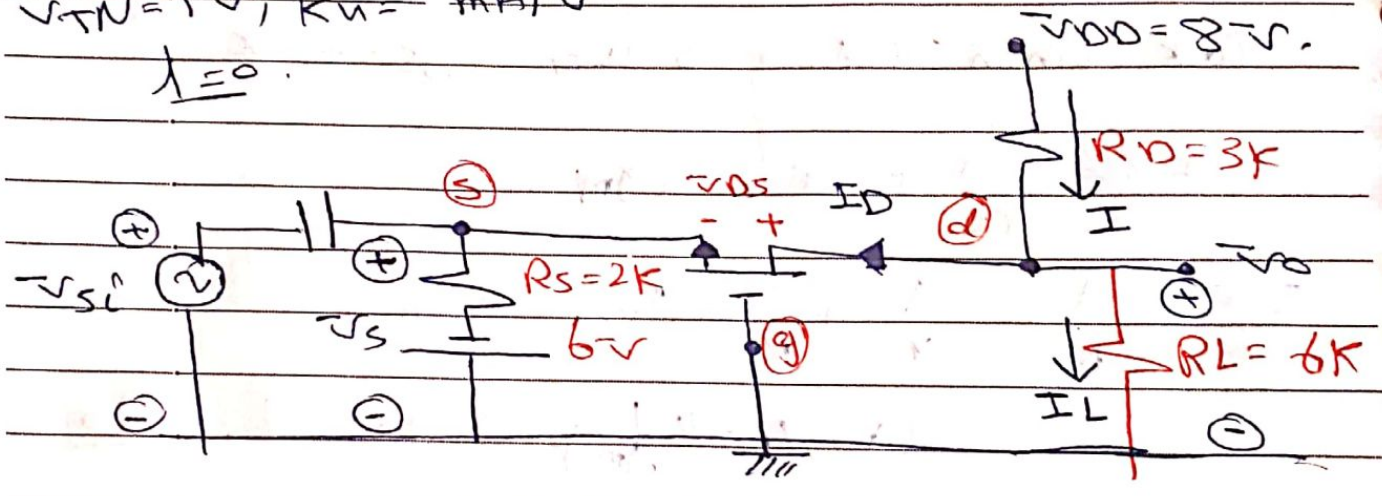$V_{TN} = 1V$, $K_n = mA/V^2$
 $\lambda = 0$



v_o , v_i , v_{DS}

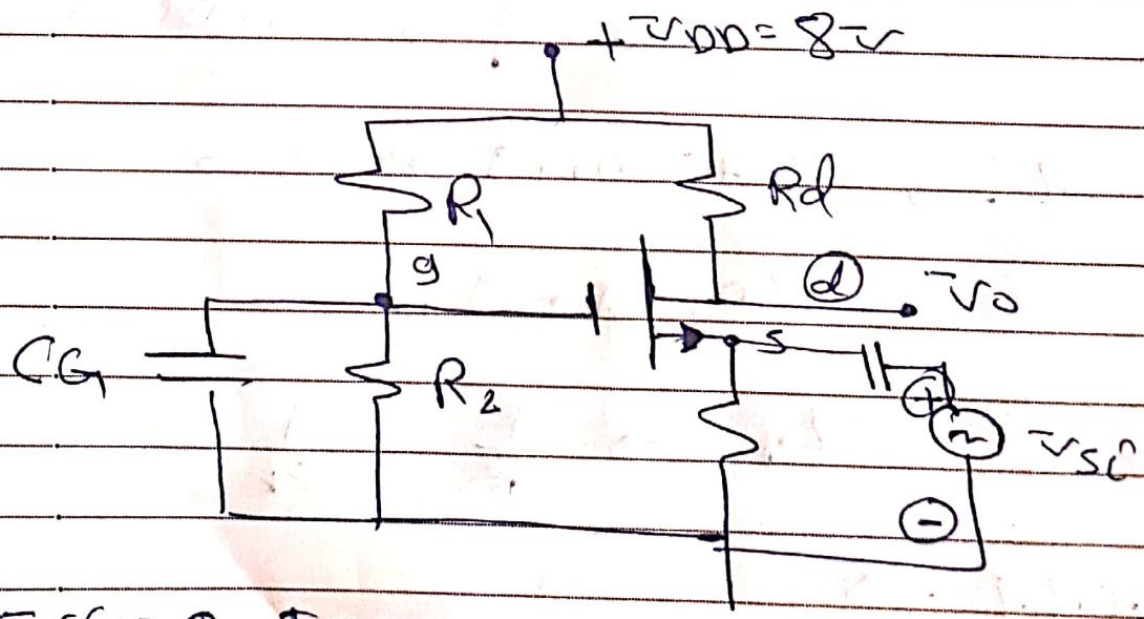

Find: ① v_{GSQ} , I_{DQ} , v_{DSQ}

② Draw s.s. eq ckt and find A_v , R_{in} , R_o .
 A.C

27

In P.C. Analysis

- Assume the MOS in sat region: \Rightarrow all C_p o.c.

$$I_D = k_n (v_{GS} - v_{TN})^2$$

$$v_{GS} = v_G - v_S \Rightarrow \boxed{v_G = 0}$$

$$-v_S + I_D R_S - 6 = 0$$

$$\boxed{v_S = -6 + I_D R_S}$$

$$v_{GS} = 0 - (-6 + I_D R_S) \Rightarrow I_D = \frac{-v_{GS} + 6}{R_S}$$

$$\frac{6 - v_{GS}}{R_S} \stackrel{1 \text{ mA}}{=} k_n (v_{GS} - 1)^2$$

$$6 - v_{GS} = 2 (v_{GS}^2 - 2v_{GS} - 1)$$

$$2v_{GS}^2 - 3v_{GS} - 4 = 0$$

$$\boxed{v_{GS} = 4 \text{ V}}$$

$$- I_{DQ} = \frac{6 - 4}{2k} = \boxed{1 \text{ mA}}$$

- to find v_{DS} : \Rightarrow

$$-v_{DD} + I_{RD} + v_{DS} + I_D R_S - 6 = 0$$

- KCL on Node (d): $\Sigma I_{in} = \Sigma I_{out}$

$$I = I_L + I_D \Rightarrow \frac{v_{dd} - v_d}{3k} = \frac{v_d}{6k} + 1 \text{ mA}$$

$$8 - v_d = 0.5 v_d + 3$$

$$5 = 1.5 v_d \Rightarrow \boxed{v_d = 3.33 \text{ V}}$$

$$\Rightarrow I = \frac{8 - 3.33}{3k} = \boxed{1.55 \text{ mA}}$$


25

$$V_{DS} = 14 - 1,55 \text{ mA} \times 5 \text{ k} - 1 \text{ mA} \times 2 \text{ k}$$

$$V_{DS} = 7 \text{ volt}$$


$$V_{DS(\text{sat})} = V_{GS} - V_{TN} = 4 - 1 = 3 \text{ volt}$$

A.C analysis:

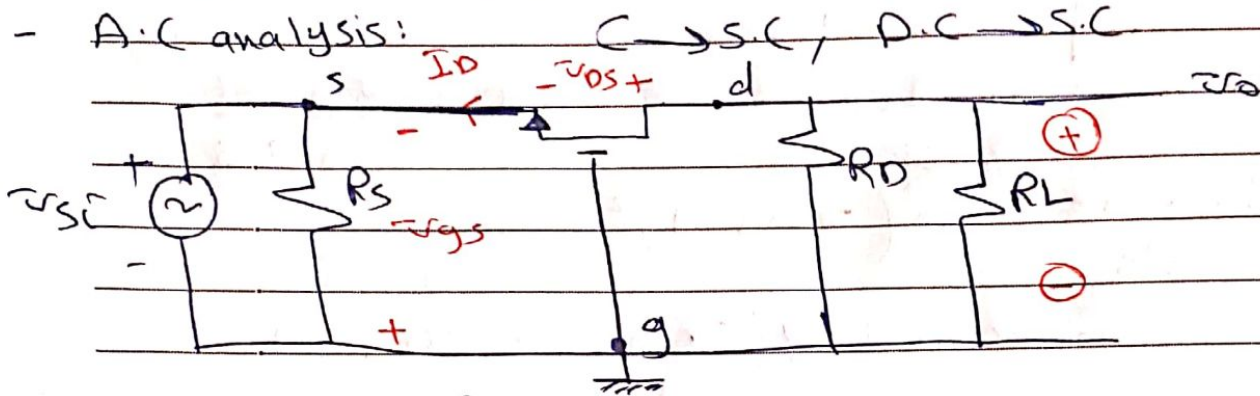

~~S.S A.C cct~~

كيف صدارة (A.C.L.L)

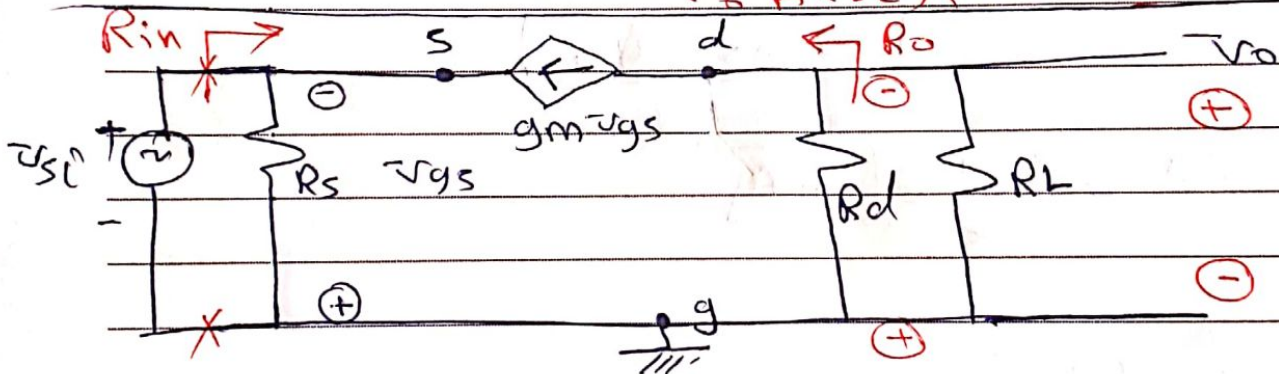

"S.S A.C equivalent"

$$A_v = \frac{v_o}{v_{gs}} \Rightarrow \frac{-g_m v_{gs} (R_D // R_L)}{-v_{gs}}$$

$$A_v = g_m (R_D // R_L)$$

$$(1) A_v > 1, \quad \phi = 0^\circ$$


Assume $k_n = 2 \text{ mA/V}^2$

$$g_m = 2 \sqrt{k_n I_D} = 2 \sqrt{1} = 2,828 \text{ mA/V} \Rightarrow A_v = 5,6$$

2a

- $R_o = \frac{v_x}{i_x} \Big|_{v_{sc}=0} \Rightarrow$ when $v_{sc}=0$, then $v_{gs}=0$
 i.e. $g_m v_{gs} = 0 \Rightarrow$ dep source o.c. \Rightarrow

$R_o = R_D = 3K\Omega$

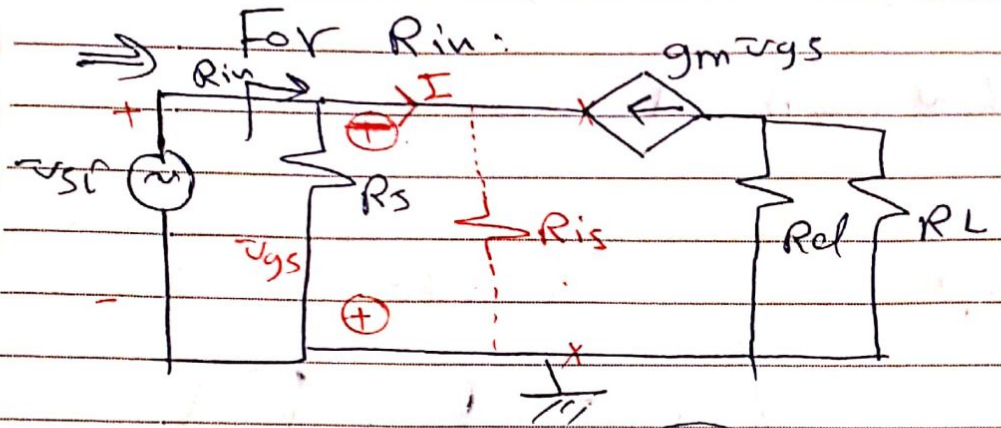

$R_{is} = \frac{-v_{gs}}{-g_m v_{gs}} = \frac{1}{g_m} \parallel R_s$

$R_{in} = 2K \parallel \frac{1000}{2.828} = 2K \parallel 350\Omega \Rightarrow 2320\Omega$

Comparison of single-stage:


Amp	A _v	∅	R _{in}	R _o
C.S	> 1	180°	Moderate	Moderate
C.D	< 1	0	Moderate	Low
C.G	> 1	0	low	Moderate

* Multi Stage Amps:

- Amps contain more than single-Mosfet (at least two Mos), used to achieve certain combined specifications which can't be achieved using single-stage such as:

- i) Low R_{in} , Low R_o , $A_v > 1$
- ii) high A_v

- Cascode Amp

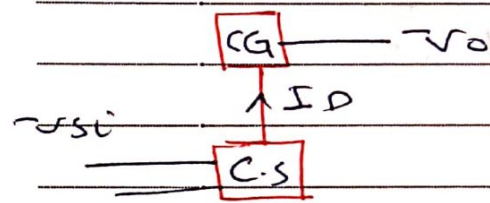


Cascade



31

"8" no, 5/15/19

Gas-Code Multistage:

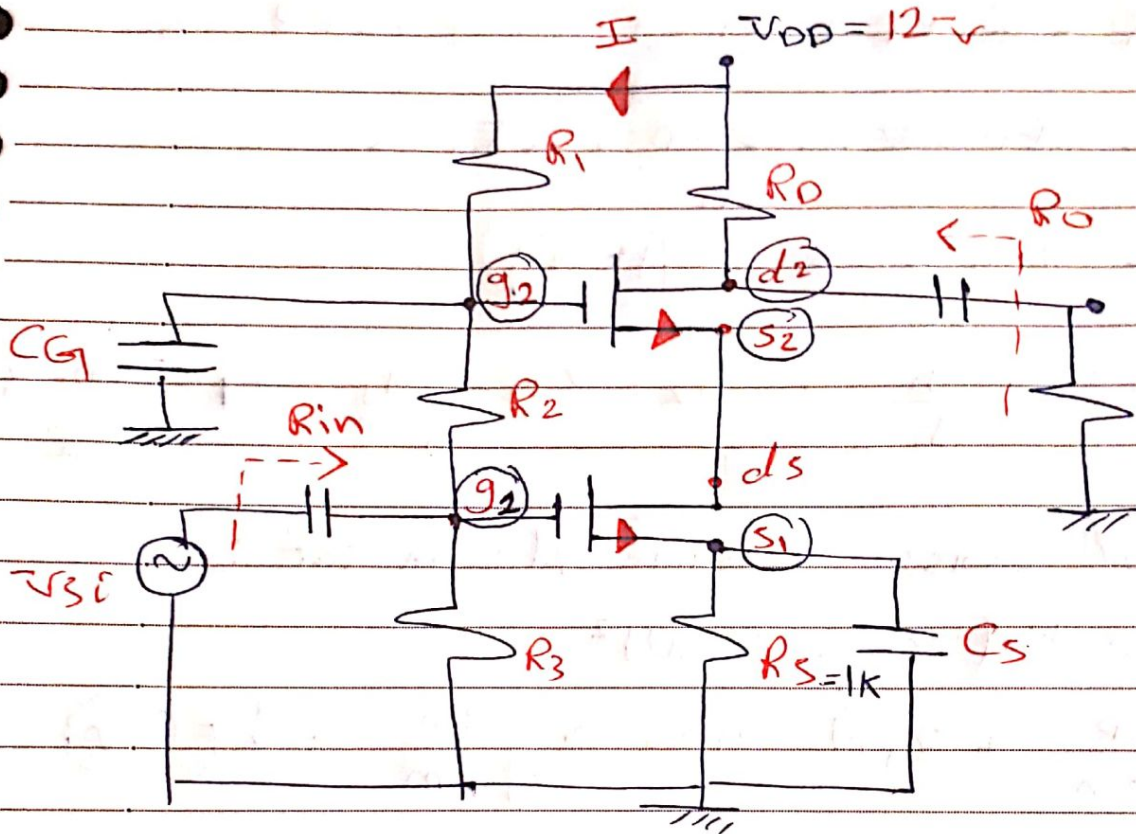

- Design the cct shown such that $I_{DD} = 2\text{mA}$, $V_{DS1} = V_{DS2} = 4\text{V}$

Given M_1 and M_2 are identical with

$$k_n = 2\text{mA/V}^2, V_{TN} = 1\text{V}, \lambda = 0$$

Use $I = 10\% I_D \Rightarrow I = 0.2\text{mA}$

① Find R_D, R_1, R_2, R_3 .

② Draw s.s.a.c. eqn cct and find A_v, R_{in}, R_o

32

⇒ D.C Analysis: all capacitors ∞ :

$$\textcircled{1} -V_{DD} + I_D R_D + V_{DS_2} + V_{DS_1} + I_D R_S = 0$$

$$R_D = \frac{V_{DD} - V_{DS_1} - V_{DS_2} - I_D R_S}{I_D}$$

$$R_D = \frac{12 - 8 - 2}{2\text{m}} = \boxed{1\text{k}\Omega}$$

$$\textcircled{2} R_3 = \frac{V_{G_1}}{I}, \quad R_2 = \frac{V_{G_2} - V_{G_1}}{I}, \quad R_1 = \frac{V_{DD} - V_{G_2}}{I}$$

⇒ Find V_{GS} : Assume MOS in sat:

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$\sqrt{\frac{I_D}{K_n}} + V_{TN} = V_{GS} \Rightarrow \sqrt{\frac{2\text{m}}{2\text{m}}} + 1 = \boxed{(2\text{V})}$$

$$\Rightarrow -V_{G_1} + V_{G_1} + I_D R_S = 0$$

$$V_{G_1} = 2 + 2\text{m} \times 1\text{k} = \boxed{4\text{V}}$$

$$R_3 = \frac{4}{0.12} = \boxed{20\text{k}\Omega}$$


$$\rightarrow -V_{G_2} + V_{G_2} + V_{DS} + I_D R_S = 0$$

$$V_{G_2} = 2 + 4 + 2\text{m} \times 1\text{k} = \boxed{8\text{V}}$$


$$R_2 = \frac{8 - 4}{0.12} = \boxed{20\text{k}\Omega}$$

33

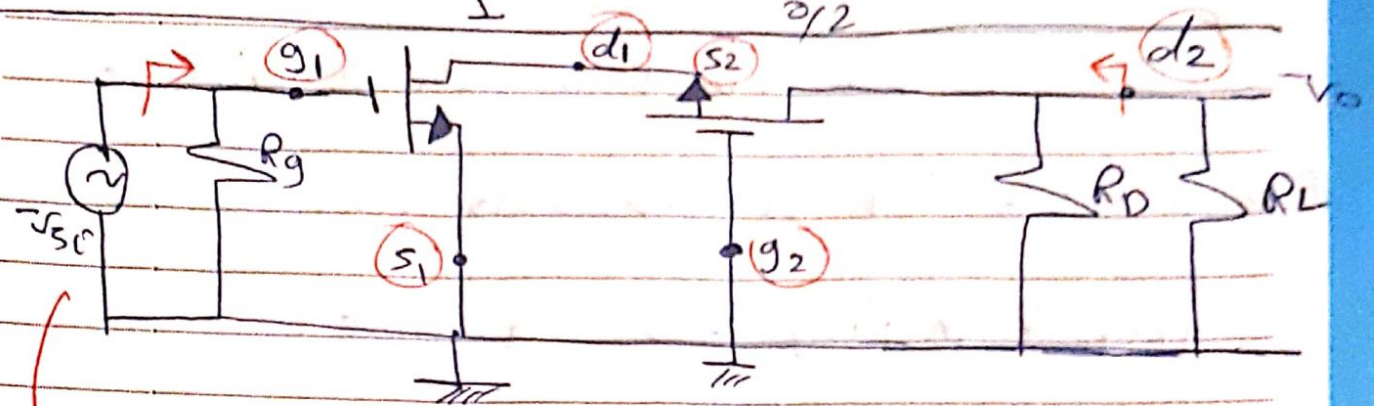$\Rightarrow R_1 = \frac{V_{DD} - V_{g2}}{I} = \frac{12 - 8}{0.2} = 20k\Omega$



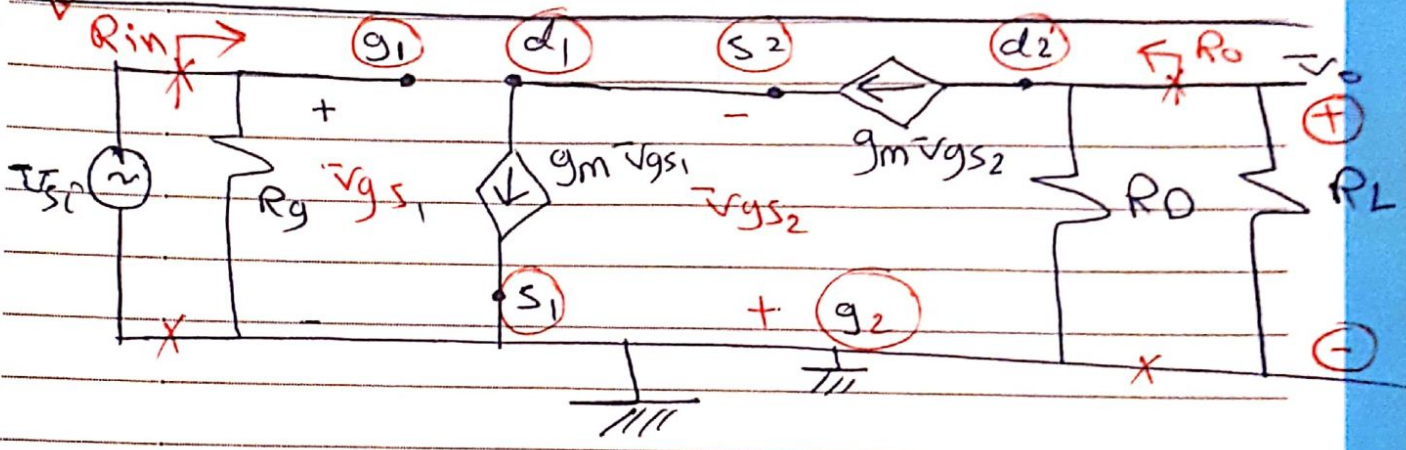A.C. cct $\Rightarrow R_g = R_1 \parallel R_2$



S.S. A.C. equ cct:

$R_{in} = R_2 \parallel R_3 \Rightarrow 20 \parallel 20 = 10k\Omega$

$A_v = \frac{v_o}{v_{sc}} = \frac{-g_m v_{gs1} \cdot (R_D \parallel R_L)}{v_{gs1}} = -g_m (R_D \parallel R_L)$

$g_m = 2\sqrt{I_D K_n} = 4mA/V \Rightarrow A_v = -2.5$

$R_o = \frac{v_x}{i_x} \Big|_{v_{sc}=0} \Rightarrow R_o = R_D = 2k\Omega$

34

⊗ لا کون داسے، Common gate لے کر لیتا ہاں

Cascode دے گا، gain سے نقصاں، C.S

لے کر دے گا، طاقت قبولیت C.G فائز ہوتا ہے

- For high freq \Rightarrow Cascode.


* لا بولڈ ان دائرے Common gate لم تکر لیکر بار

Cascode دایقلا، gain نفعہ کار، C.S.

لیکریں، ان، فافانے قولیے C.G. فانے تیا، ہو فافانے


For high freq \Rightarrow Cascode.
"دائیرے / تم د"

* Cascaded Multistage:

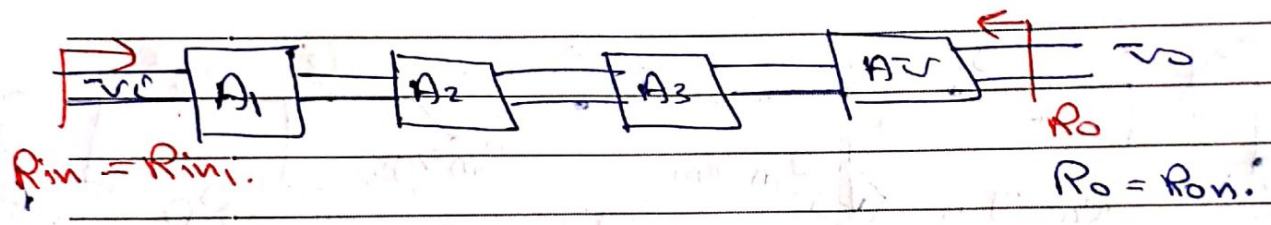

For M_1 :
 $K_{n1} = 0.5 \text{ mA/V}^2$
 $V_{TN1} = 2 \text{ V}$
 $\lambda = 0.01 \text{ V}^{-1}$

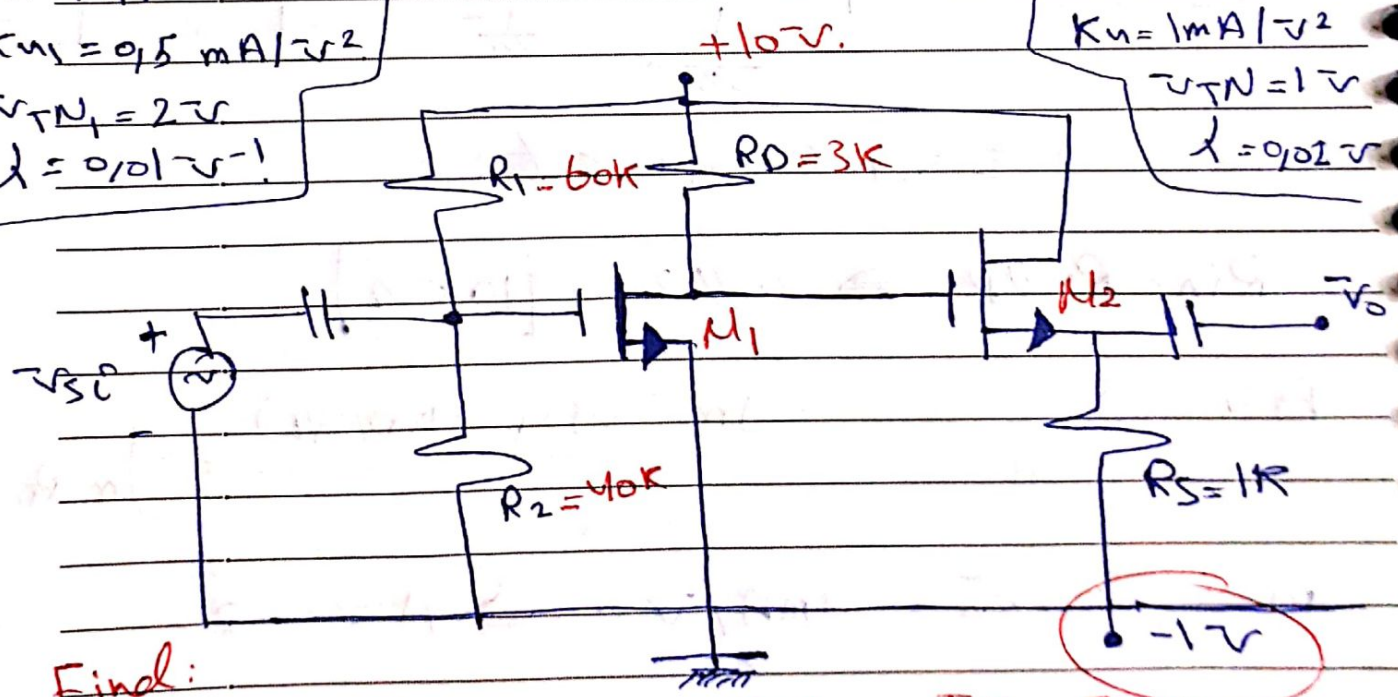For M_2 :
 $K_{n2} = 1 \text{ mA/V}^2$
 $V_{TN2} = 1 \text{ V}$
 $\lambda = 0.02 \text{ V}^{-1}$



Find:

- 1) $V_{GS1}, I_{D1}, V_{DS1}, V_{GS2}, I_{D2}, V_{DS2}$

2) Draw S.S.A.C eqy cct. anal find:

$A_v = \frac{v_o}{v_{sc}}$, $A_{v1} = \frac{v_{o1}}{v_{sc}}$, $A_{v2} = \frac{v_o}{v_{i2}}$

35

For D.C Analysis, all Capacitors o.c:

Assume M_1 and M_2 in saturation region:

$$I_1 = \frac{\sum V}{\sum R} = \frac{10}{R_2 + R_1} = \frac{10}{40k + 60k} = 0.1 \text{ mA}$$

$$\Rightarrow KVL: -0.1 \text{ mA} \times 40k + V_{GS1} = 0$$

$$\boxed{V_{GS1} = 4 \text{ V}}$$

$$I_{D1} = K_{n1} (V_{GS1} - V_{TN1})^2 \Rightarrow I_{D1} = 0.5 (3)^2 = 2 \text{ mA}$$

$$-10 + I_{D1} R_{D1} + V_{DS1} = 0 \Rightarrow V_{DS1} = 10 - 2 \text{ mA} \times 3k$$

$$\boxed{V_{DS1} = 4 \text{ V}}$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 4 - 2 = 2 \text{ V} \quad \text{sat}$$

For MOS 2 \Rightarrow Assume in sat Region:

$$-V_{DS1} + V_{GS2} + I_{D2} R_S - 1 = 0$$

$$I_{D2} = \frac{V_{DS1} + 1 - V_{GS2}}{R_S} = \boxed{5 - V_{GS2} = I_{D2}}$$

$$I_{D2} = K_{n2} (V_{GS2} - V_{TN2})^2$$

$$5 - V_{GS2} = (V_{GS2}^2 - 2V_{GS2} + 1)$$



$$0 = V_{GS2}^2 - V_{GS2} - 4$$

$$\boxed{V_{GS2} = 2.6 \text{ V}}$$

36

- $I_{D2} = 5 - 2,6 = 2,4 \text{ mA}$

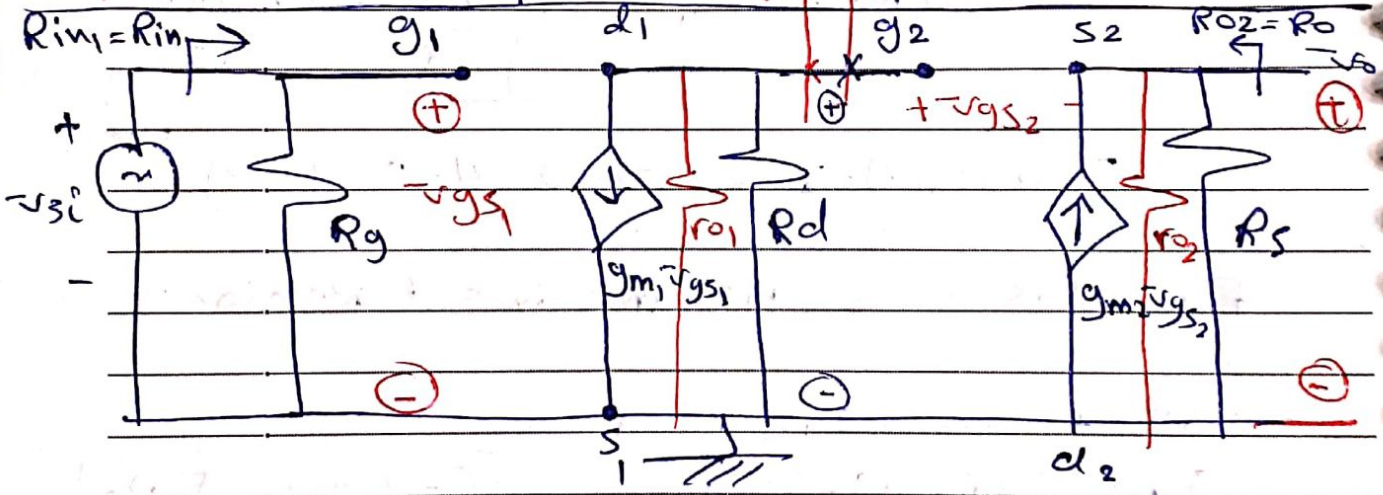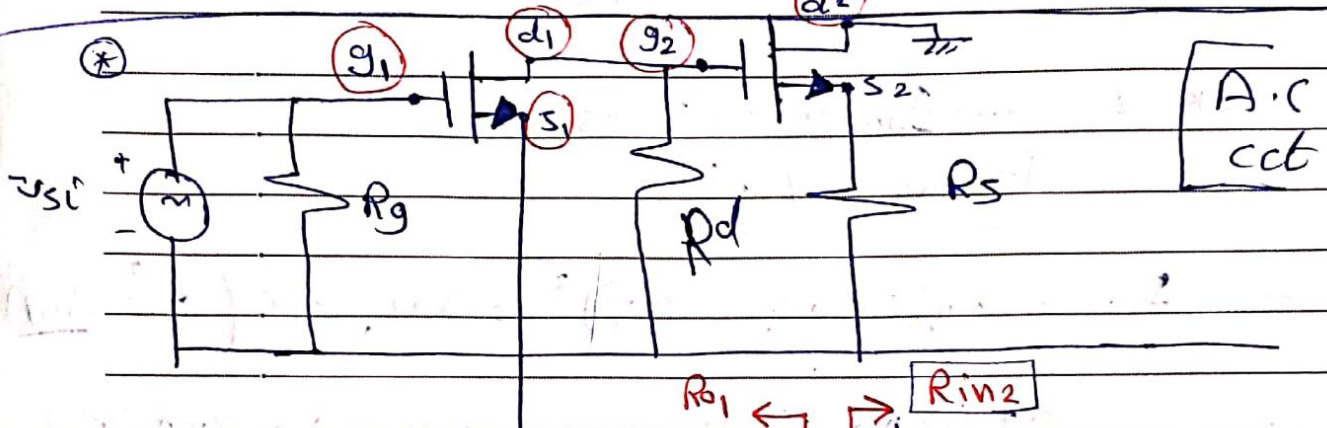- $-10 + V_{DS2} + I_{D2} R_S = 0$
 $V_{DS2} = 11 - 2,4 \times 1 = 8,6 \text{ V}$



$A_v = \frac{v_o}{v_{si}} = \frac{v_o}{v_{si2}} \times \frac{v_{si2}}{v_{si}}$
 $A_{v2} \quad A_{v1}$

$A_{v2} = \frac{v_o}{v_{si2}} = \left[v_o = g_{m2} v_{gs2} (r_{o2} || R_s) \right]$

37

* $-\bar{v}_{s2} + \bar{v}_{gs2} + \bar{v}_o = 0$

$-\bar{v}_{s2} = \bar{v}_{gs2} + g_{m2} \bar{v}_{gs2} (r_{o2} // R_s)$

$\bar{v}_{s2} = \bar{v}_{gs2} (1 + g_{m2} (r_{o2} // R_s))$

$A_{v2} = \frac{g_{m2} \bar{v}_{gs2} (r_{o2} // R_s)}{\bar{v}_{gs2} (1 + g_{m2} (r_{o2} // R_s))} = \frac{g_{m2} (r_{o2} // R_s)}{(1 + g_{m2} (r_{o2} // R_s))}$

$A_{v2} < 1$

$A_{v1} = \frac{\bar{v}_{o1}}{\bar{v}_{s1}} = \frac{-g_{m1} (r_{o1} // R_d) \cdot \bar{v}_{gs1}}{\bar{v}_{gs1}}$

$A_{v1} > 1 = -g_{m1} (r_{o1} // R_d)$

$A_v = A_{v1} * A_{v2} = \frac{-g_{m1} (r_{o1} // R_d) * g_{m2} (R_s // r_{o2})}{1 + g_{m2} (r_{o2} // R_s)}$

$R_{in} = R_{in1} = R_g = R_1 // R_2$


$R_o = R_{o2} = (r_{o2} // R_s // \frac{1}{g_m})$ "Low"

$R_{in2} = \infty$

$R_{o1} = r_{o1} // R_d$

* BJT Amplifiers:

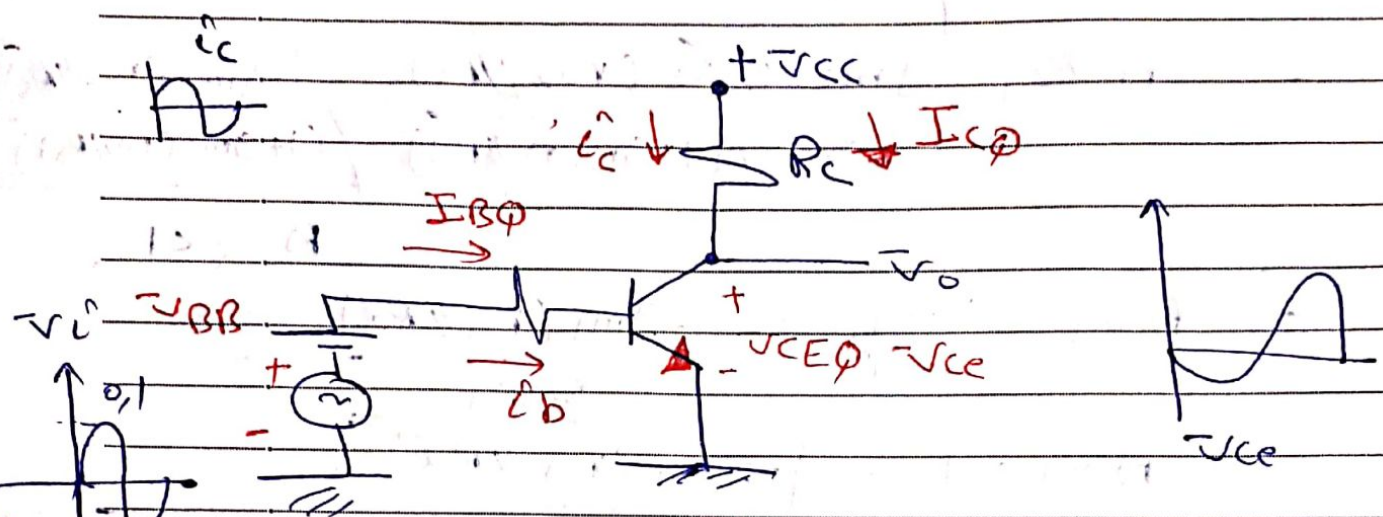
(BJT must be biased in F.A.N to be used as an Amp.)



$\beta = 100, V_{BE} = 0.7V$

① D.C Analysis (C → D.C), A.C → S.C

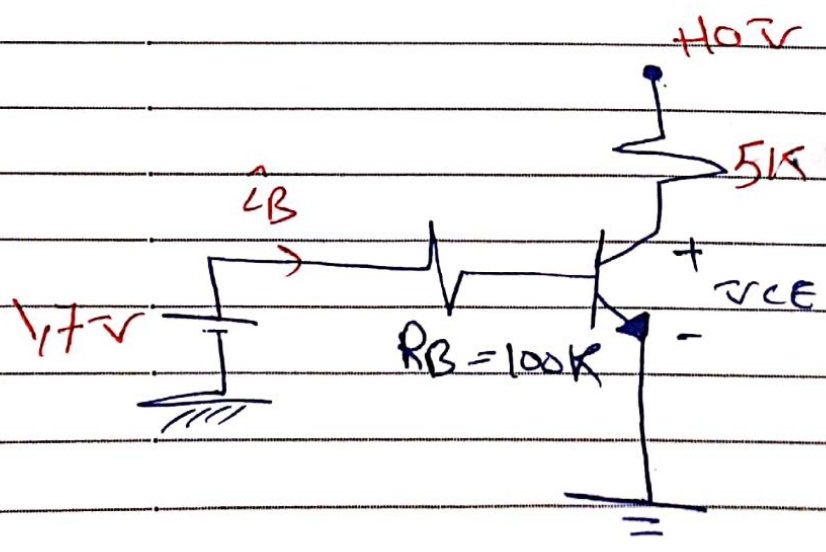- * Super position: ① D.C source → A.C → S.C
- ② A.C // 1 → D.C → S.C



39

KVL: $-1.7 + I_B R_B + V_{BE} = 0 \Rightarrow$

$$I_B = \frac{1.7 - V_{BE}}{R_B} = \frac{1.7 - 0.7}{100k} = \boxed{0.01mA}$$

$$I_C = \beta I_B \varnothing = \boxed{1mA}$$

KVL: $-10 + I_C \varnothing * 5K + V_{CE} = 0$

$$V_{CE} = 10 - 1mA * 5K = \boxed{5VOLT}$$

Since $I_B > 0$, then B-E Jun \rightarrow F.W
and $V_{CE} > V_{BE}$, B-C Jun \rightarrow ReTr

then BJT is in F.A.M.

* D.C.L.L and \varnothing -pt:

$$-10 + I_C R_C + V_{CE} = 0 \Rightarrow V_{CE} = 10 - I_C R_C$$

$$\boxed{\text{Slope} = -\frac{1}{R_C}}$$



i) for $I_C = 0 \Rightarrow V_{CE} = 10V \Rightarrow P_1 (10, 0)$

ii) for $V_{CE} = 0, I_C = 2mA, P_2 (0, 2mA)$

\varnothing -pt $\Rightarrow (V_{CE\varnothing}, I_C\varnothing)$

$(5V, 1mA)$

D.C.L.L

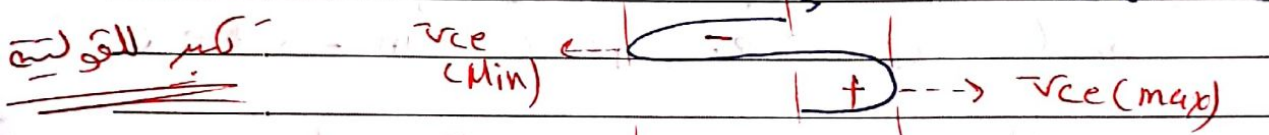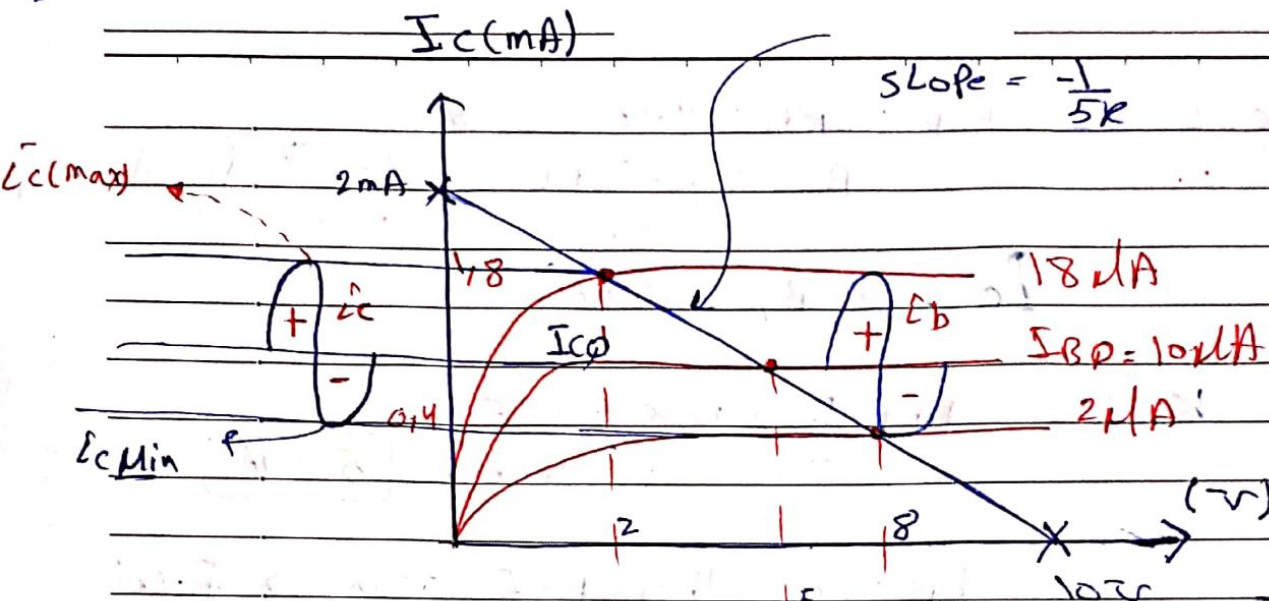

$$A_{Vc} = \left| \frac{V_{ce}}{V_{ce}} \right| = \frac{V_{ce p-p}}{V_{ce p-p}} = \frac{3}{0.1} = 30$$


تغير القوتية / BJT ، التغير في القوتية ، التغير في القوتية

Mosfet

BJT ، التغير في القوتية ، التغير في القوتية ، التغير في القوتية

"Current Controlled current source" ← BJT

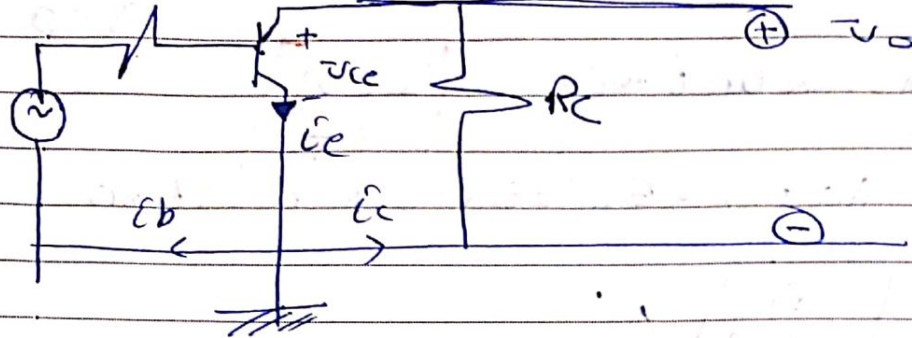* effect of A.C source: D.C. \rightarrow S.C




A.C.L.L $\Rightarrow v_{ce} + i_c R_C = 0 \Rightarrow v_{ce} = -i_c R_C$

$$\hat{i}_B = I_{BQ} + \hat{i}_b$$

$$\hat{i}_C = I_{CQ} + \hat{i}_c$$

$$v_{CE} = V_{CEQ} + v_{ce}$$

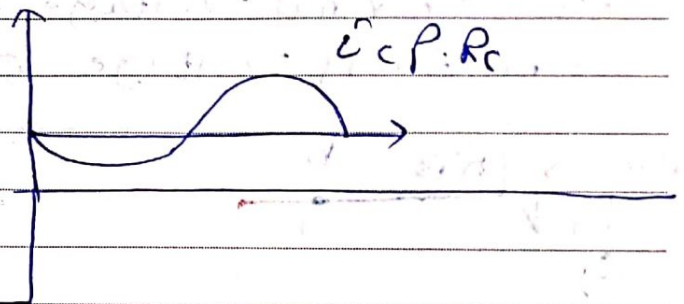


* Assume v_{in} drives a peak base current

$$i_B = 8 \mu A \Rightarrow \hat{i}_b = 8 \sin \omega t (\mu A) \Rightarrow$$

$$\hat{i}_B = (I_{BQ} + 8 \sin \omega t) \mu A.$$

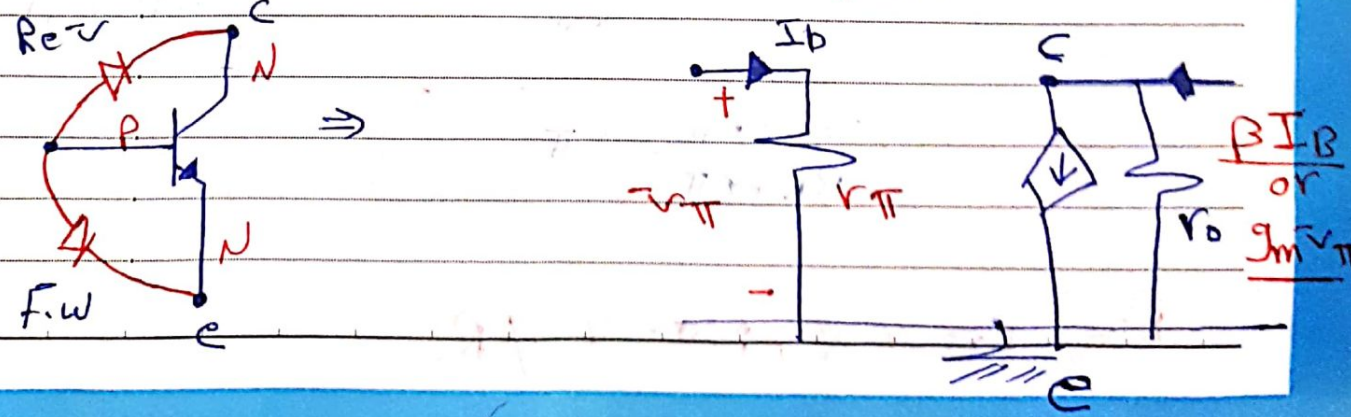* To perform A.C analysis the BJT in A.C ct is replaced by it's model (hybrid- π model)



r_{π} : F.W base-emitter resistance = $\frac{\beta V_T}{I_{CQ}}$


g_m : Transconductance = $\frac{I_{CQ}}{V_T}$

$r_o \Rightarrow$ Collector - Emitter o/p resistance

$r_o = \frac{V_A}{I_{CQ}}$

V_T : Thermal voltage = 26 mV .

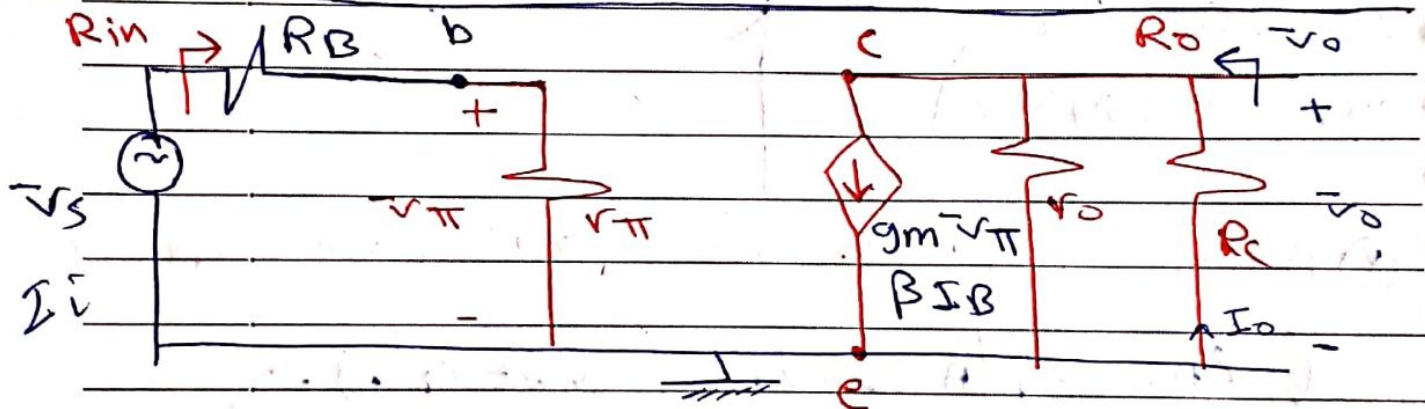V_A : Early voltage $50 < V_A < 30 \text{ V}$. (given)



S.S.A.C eq. ckt.

$$A_v = \frac{v_o}{v_s} = \frac{-g_m v_{\pi} (r_o \parallel R_c)}{v_{\pi} (R_B + r_{\pi})} = \frac{r_{\pi} * -g_m (r_o \parallel R_c)}{(R_B + r_{\pi})}$$

$\frac{v_s * r_{\pi}}{R_B + r_{\pi}} = v_{\pi}$

$R_{in} = R_B + r_{\pi}, R_o = r_o \parallel R_c$

ASI Current gain = $\frac{I_o}{I_i}$

$$I_o = \frac{-g_m V_{\pi} \times r_o \parallel R}{r_o + R_c} = \frac{\beta I_b \times r_o}{r_o + R_c}$$

$$[I_b = I_i] \Rightarrow [I_o = -\beta I_i \cdot r_o / (r_o + R_c)]$$


$$A_I = \frac{I_o}{I_i} = \frac{-\beta r_o}{r_o + R_c}$$

"10/5/16"

~~XXXXXXXXXXXXXXXXXXXXXXXXXXXX~~


*** Single stage BJT Amplifiers:**

Common Emitter Amp:

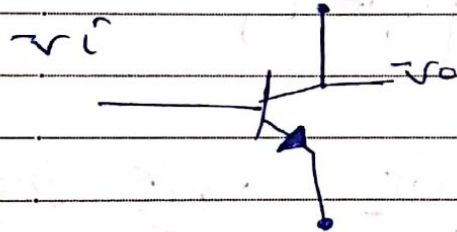

$v_i \rightarrow$ to base
 $v_o \rightarrow$ from collector
 $E \rightarrow$ Common-ter

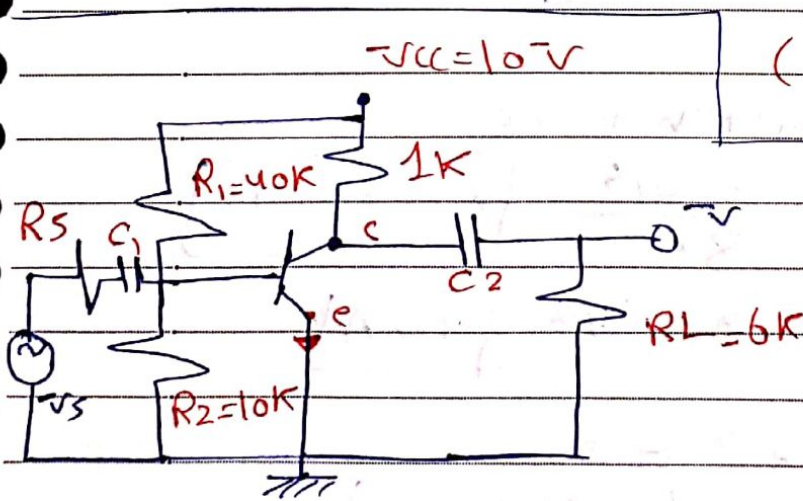
① Basic Common Emi
 (E \rightarrow directly connected to ground)



$\beta = 40$
 $v_{BE} = 0.6$
 $v_A = 100V$

- 1] find: I_B, I_C, V_{CE} .
- 2] Draw S.S.A.C eq ckt and determine A_v, A_i, R_{in}, R_o .
- 3] write DC and AC L.L equations and find their slopes

* D.C Analysis: All caps \rightarrow O.C

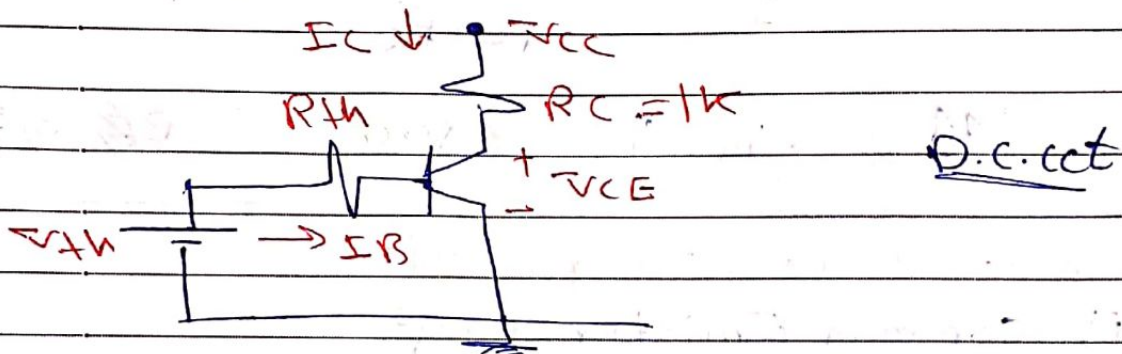

$$R_{Th} = R_1 // R_2 = \frac{400k \cdot 20k}{50k} = \boxed{8k\Omega}$$

$$V_{Th} = \frac{10 \cdot R_2}{R_1 + R_2} = \frac{10 \cdot 10k}{50k} = \frac{100k}{50k} = \boxed{2V}$$

KVL: $-V_{Th} + I_B R_{Th} + V_{BE} = 0$

$$I_B = \frac{2 - 0.6}{8k} = \boxed{0.175 \text{ mA}}$$

$$I_C = \beta I_B = 40 \cdot 0.175 = \boxed{7 \text{ mA}}$$



KVL: $-V_{CC} + I_C R_C + V_{CE} = 0$

$$V_{CE} = 10 - 7 \text{ mA} \cdot 1k = \boxed{3V}$$

$I_B > 0, V_{CE} > V_{BE}$ F.W.M.L

A.C. cct.

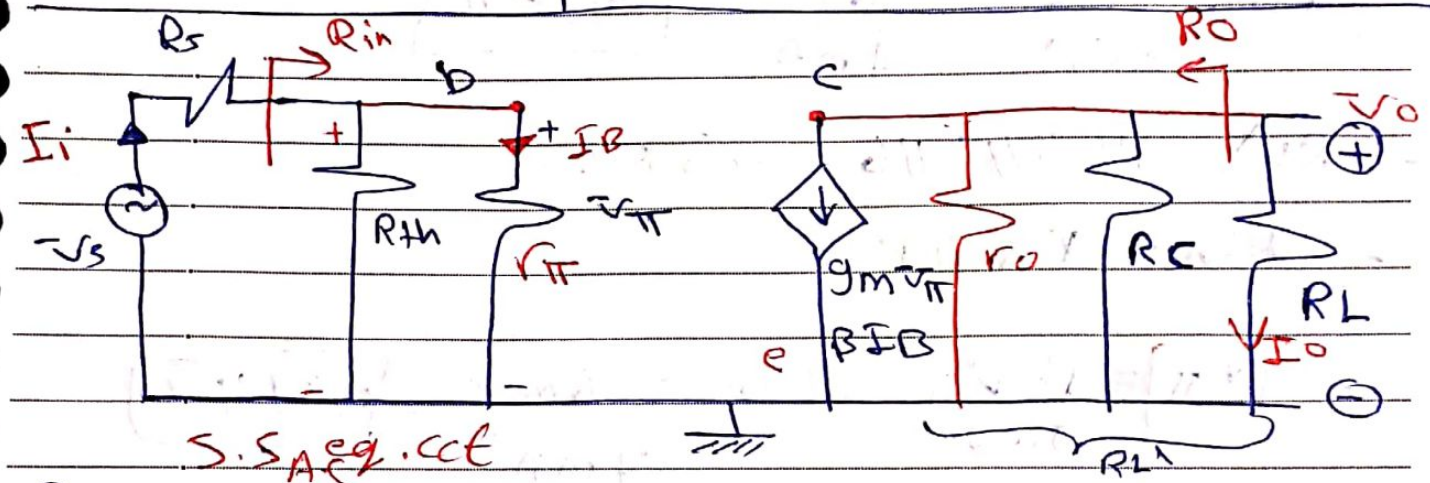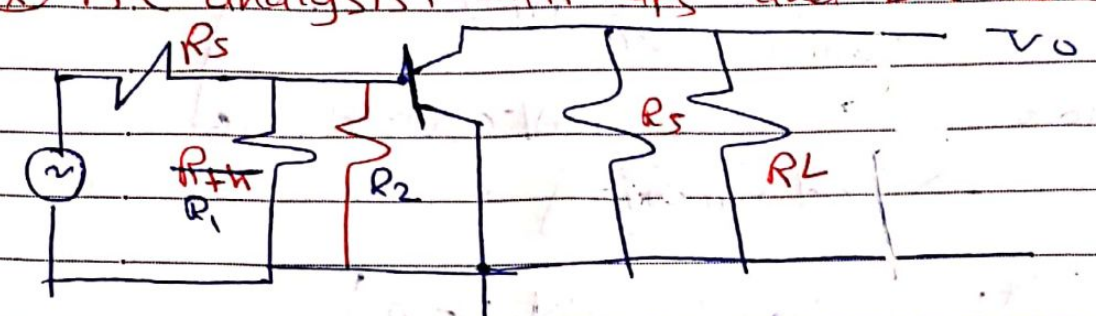* A.C analysis: all caps and D.C \rightarrow S.C.



S.S. eq. cct

RL is the load resistor $\leftarrow I_o$: \circledast $R_c \parallel R_L$

$$A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{\pi}} * \frac{V_{\pi}}{V_s}$$

$$\frac{V_o}{V_{\pi}} = \frac{-g_m V_{\pi} * R_L'}{V_{\pi}} = -g_m R_L' : R_L' = r_o \parallel R_c \parallel R_L$$

$$V_{\pi} = V_s * \frac{(R_{th} \parallel r_{\pi})}{(R_{th} \parallel r_{\pi}) + R_s} \Rightarrow \text{Voltage Divider}$$

Let $R_{in} = R_{th} \parallel r_{\pi}$

$$V_{\pi} = \frac{V_s * R_{in}}{R_{in} + R_s} \Rightarrow \frac{V_{\pi}}{V_s} = \frac{R_{in}}{R_{in} + R_s}$$

$$A_v = -g_m R_L' * \frac{V_s R_{in}}{R_{in} + R_s}$$

46

$$g_m = \frac{I_{CQ}}{V_T} = \frac{7 \text{ mA}}{26 \text{ mV}} = \frac{7}{26} \text{ A/V}$$

$$\frac{7 \times 1000}{26}$$

$$\Rightarrow 270 \text{ mA/V}$$

← mA/V) below is

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100 \text{ V}}{7 \text{ mA}} = 14,3 \text{ k}\Omega$$

$$- R_L' = 14,3 // 116 = 0,8 \text{ k}\Omega$$

$$- R_{in} = r_{\pi} // R_{Th} =$$

$$- r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26 \text{ mV}}{7 \text{ mA}} = 0,37 \text{ k}\Omega$$

$$- R_{in} = 0,37 // 8 = 0,35 \text{ k}\Omega$$

$$- A_V = \frac{-270 \times 0,8 \times 0,35}{0,35 + 0,15} = -151 = \frac{v_o}{v_s}$$

$$v_o = -151 v_s$$

* $A_I =$ Current gain: $\frac{I_o}{I_i} = \frac{I_o \times I_B}{I_B \times I_i}$

$$I_o = \frac{-\beta I_B \times (r_o // R_c)}{(r_o // R_c) + R_L} \Rightarrow \text{Let } R_c' = r_o // R_c$$

$$\frac{I_o}{I_B} = \frac{-\beta \cdot R_c'}{R_c' + R_L}$$

(17)

$$\frac{I_B}{I_i} = \frac{I_i \times R_{Th}}{R_{Th} + r_{\pi}} \Rightarrow \boxed{\frac{I_B}{I_i} = \frac{R_{Th}}{R_{Th} + r_{\pi}}}$$

$$A_I = \frac{I_o}{I_B} \times \frac{I_B}{I_i} = \frac{-\beta R_c'}{R_c' + R_L} \times \frac{R_{Th}}{R_{Th} + r_{\pi}} \approx -5$$

- $R_{in} = R_{Th} \parallel r_{\pi} = 0,35k\Omega$

- R_{in} (seen by signal generator) $\approx 0,35k + R_s = 0,7k\Omega$

- $R_{ib} = r_{\pi}$

$$\boxed{R_o \Rightarrow \frac{v_x}{i_x} = R_o \mid \Rightarrow r_o \parallel R_c = 0,9k\Omega}$$

$v_s = 0$

since $v_s = 0, v_{\pi} = 0$

(*) A_V and A_I Relations:

$$\textcircled{1} A_V = \frac{v_o}{v_s} = \frac{I_o \cdot R_L}{I_i (R_s + R_{in})} = \boxed{A_I \cdot \frac{R_L}{R_s + R_{in}}}$$

$$\textcircled{2} A_I = \frac{I_o}{I_i} = \frac{\frac{v_o}{R_L}}{\frac{v_s}{R_s + R_{in}}} = \boxed{A_V \cdot \frac{R_s + R_{in}}{R_L}}$$

↑ تنبأ R_s و R_L وضع و R_{in} و R_{out} بالعلامة \pm


$\beta = 60$
 (12.8)

② في البداية السابقة لدينا / ففقت قيمته $\beta = 60$

$I_B = 0,175 \text{ mA}$ و $I_C = 0$ و $V_{CE} = 0,5 \text{ V}$ و $I_C = 10,5 \text{ mA}$

Transistor في المنطقة (Sat Region)

(very sensitive to β variation)

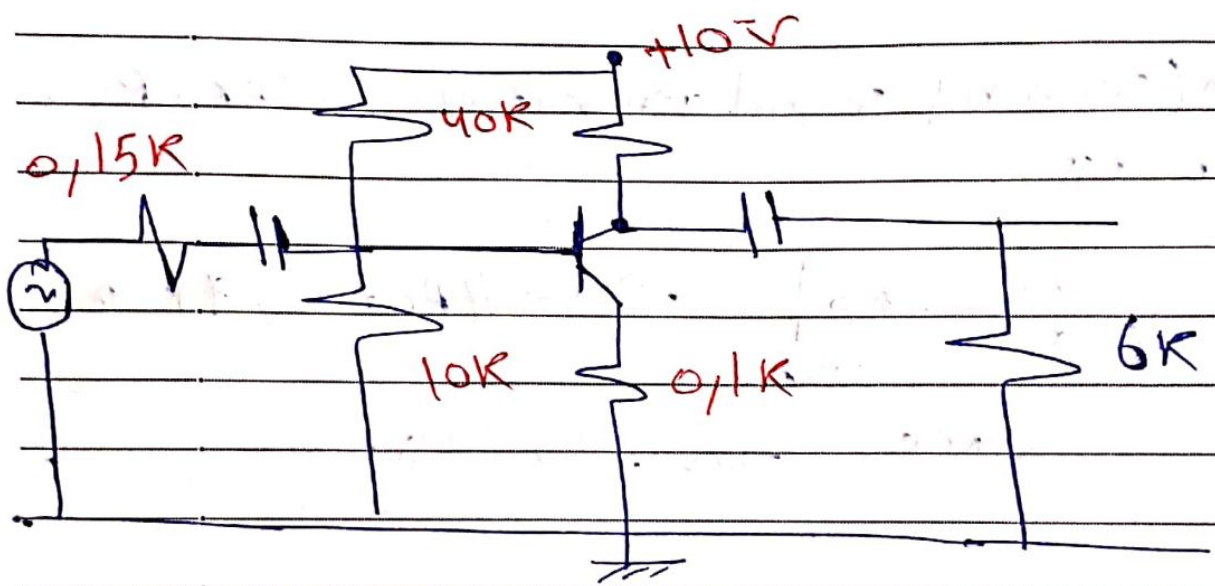


$\beta = 60, V_{BE} = 0,7 \text{ V}$

① Final I_B, I_C, V_{CE}

② Draw S.S.A.C. eqy. cct

③ Final $A_V, A_I, R_{in}, R_{inb}, R_o$

* D.C. Analysis :- All capacitors o.c :

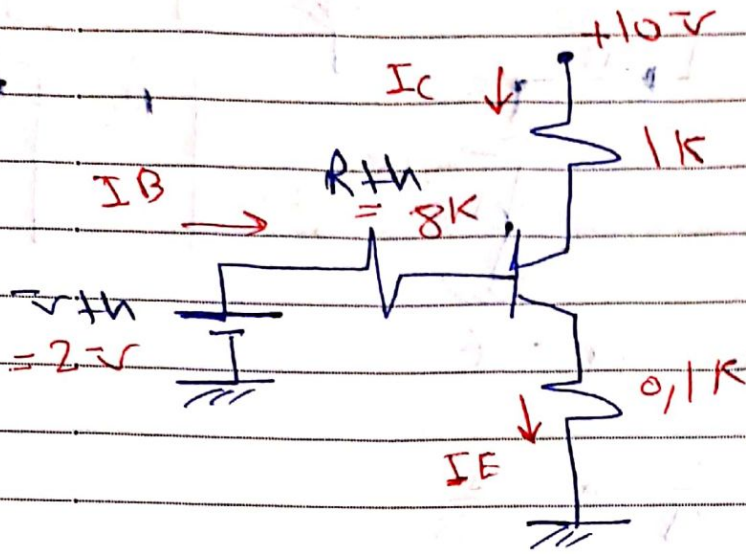

$$R_{th} = 8K\Omega \Rightarrow (R_1 || R_2)$$

$$V_{th} = \frac{10 \times 10K}{50K} = 2V$$

KVL: $-V_{th} + I_B R_{th} + V_{BE} + (\beta + 1) I_B \times 0.1K = 0$


$$I_B = 0.09mA$$

$$I_C = \beta I_B = 5.4mA$$


KVL: $-10 + I_C R_C + V_{CE} + (\beta + 1) I_B \times 0.1K = 0$

$$V_{CE} = 4V$$

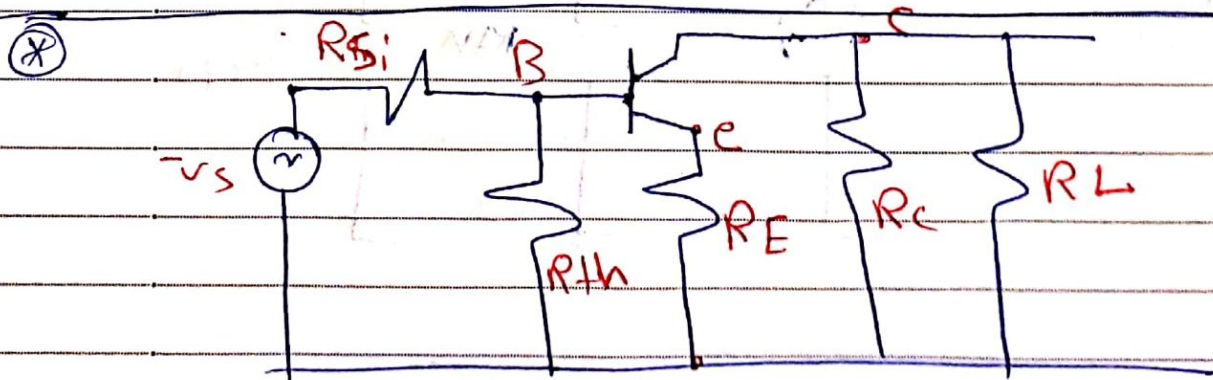(R_E is used to stabilize Q-pt, against β variation.) (Advantage)



A.c cct.

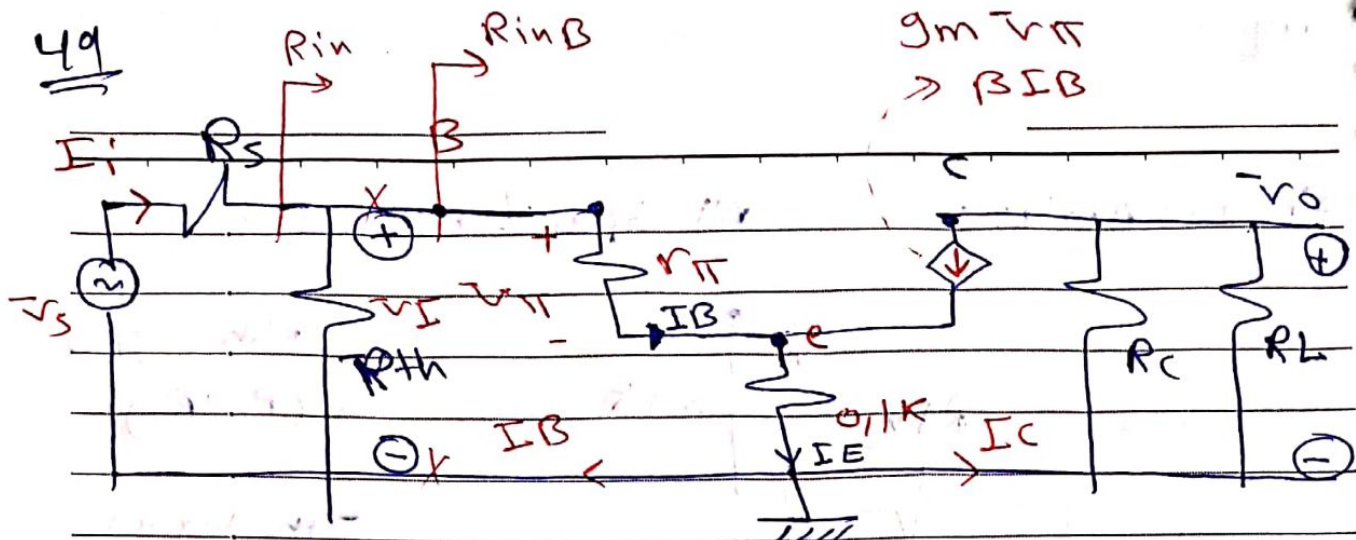


$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v_i} \times \frac{v_i}{v_s}$$

$$v_o = -\beta I_B (R_C \parallel R_L)$$

$$v_i = v_{\pi} + (\beta + 1) I_B R_E \Rightarrow v_i = I_B r_{\pi} + (\beta + 1) I_B R_E$$

$$v_i = I_B (r_{\pi} + (\beta + 1) R_E)$$
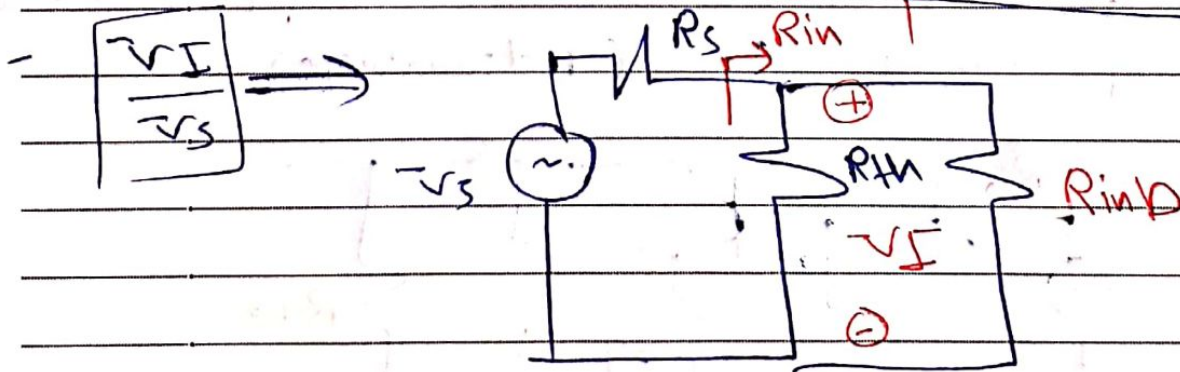
$$\frac{v_o}{v_i} = \frac{-\beta I_B (R_C \parallel R_L)}{I_B (r_{\pi} + (\beta + 1) R_E)} = \frac{-\beta (R_C \parallel R_L)}{r_{\pi} + (\beta + 1) R_E}$$



Note that $R_{in} = R_{\pi} \parallel R_{inB}$

$$\text{and } R_{inB} = \frac{v_i}{I_B}$$

$$\Rightarrow \text{voltage divider} \Rightarrow \frac{v_s \times (R_{\pi} \parallel R_{inB})}{R_s + (R_{\pi} \parallel R_{inB})} = v_i$$

50

2

(*) Then: $v_I = v_S * \frac{R_{in}}{R_S + R_{in}} \Rightarrow \boxed{\frac{v_I}{v_S} = \frac{R_{in}}{R_S + R_{in}}}$

Then $A_v = \frac{v_O}{v_I} * \frac{v_I}{v_S} =$

$$\boxed{\frac{-\beta (R_C // R_L)}{r_{\pi} + (\beta + 1) R_E} * \frac{R_{in}}{R_S + R_{in}}} = A_v$$

$R_{ib} = \frac{v_I}{I_B} = \frac{v_{\pi} + (\beta + 1) I_B R_E}{I_B} = \frac{I_B r_{\pi} + (\beta + 1) I_B R_E}{I_B}$

$R_{ib} = \frac{I_B (r_{\pi} + (\beta + 1) R_E)}{I_B} = \boxed{r_{\pi} + (\beta + 1) R_E}$

$r_{\pi} = \frac{\beta v_T}{I_C} = \frac{60 * 26 mV}{5.4 mA} = \boxed{290 \Omega}$

$R_{ib} = 290 + 61 * 1k = \boxed{6,129 k\Omega}$

$R_{in} = 6,129 // 8 = \dots k\Omega$

$A_v \approx -7,71$

" R_E reduces A_v but increases R_{in} "

↓
Advantage

51

$$R_o = \frac{v_x}{I_x} \quad | \quad v_s = 0, \quad v_{\pi} = 0, \quad g_m v_{\pi} = 0$$

D.C.S \Rightarrow O.C

$$R_o = R_c = 1k\Omega$$

$$A_I = \frac{I_o}{I_i} = \frac{\frac{v_o}{R_L}}{\frac{v_s}{R_s + R_{in}}} = A_V \cdot \frac{R_s + R_{in}}{R_L}$$

C.D.R

O.R

$$A_I = \frac{I_o}{I_b} \times \frac{I_b}{I_s}$$

$$\frac{I_o}{I_b} = \frac{-\beta I_b R_c}{(R_L + R_c)} \times \frac{I_b}{I_s} = \frac{-\beta R_c}{(R_L + R_c)}$$

Current division Rule.

$$\frac{I_b}{I_s} \Rightarrow$$

Current division.

$$I_s = I_i \rightarrow \text{source } v_i, I_i$$

$$I_b = I_i \times \frac{R_{th}}{R_{th} + R_{inb}} \Rightarrow \frac{I_b}{I_i} = \frac{R_{th}}{R_{th} + R_{inb}}$$

$$A_I = \frac{I_o}{I_i} = \frac{-\beta R_c}{R_L + R_c} \times \frac{R_{th}}{R_{th} + R_{inb}}$$

52

(*)

فيما يلي : $A_{v} \approx$

$$\text{For } \beta \gg 1, (\beta + 1)R_E \gg r_{\pi}$$

$$R_{in} \gg R_s$$


$$A_{v} \approx \frac{(R_C \parallel R_L)}{R_E}$$

R_E - stabilize A_{v} against β variation

- لا يؤثر β على A_{v} عند $R_E \gg \frac{r_{\pi}}{\beta}$
- لا يؤثر β على A_{v} عند $R_E \gg \frac{r_{\pi}}{\beta}$

iii) C.E with by pass capacitor.

(RE is bypassed)

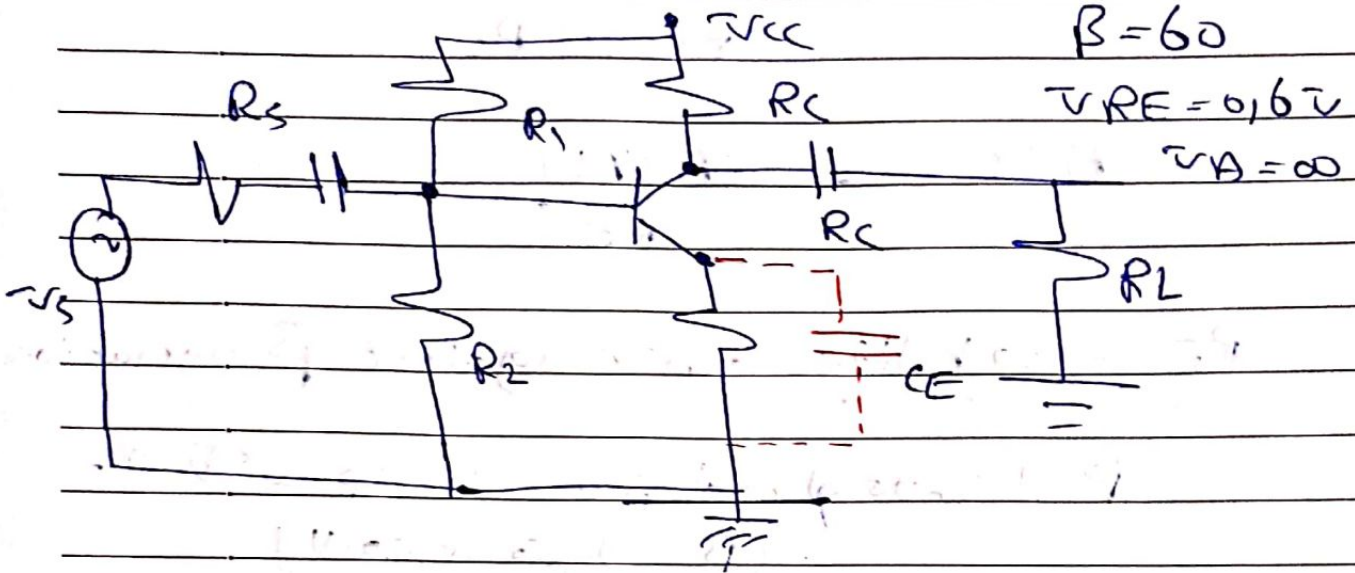


1) For D.C Analysis : CE → O.C

R_E is present and stabilize Q-pt.

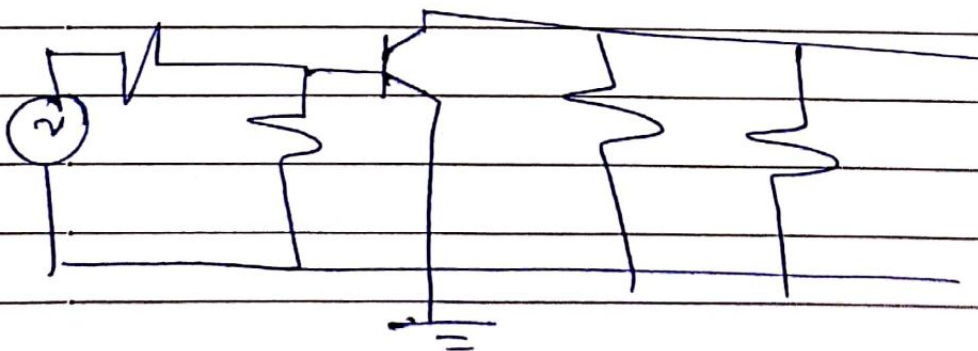2) For A.C analysis : CE → S.C → R_E → S.C

and the cct is analyzed as basic Common Emitter Amp.



$$A_v = -g_m R_C \parallel R_L \cdot \frac{R_{in}}{R_{in} + R_s}$$

⊗ دالة نقلية اقلها انا راننا اقم R_E لجزء كبير وجزء صغير في جزئيه اوله مع C_E كان اقله صغرته بجزء واحد



منه اقلها R_E ، A_v لقل كاله وعابره

R_{in} ، تنقص ، اختلاف كبير

بقاي
الصورة

R_{in}
قا
كثير

$A_v \rightarrow$ كاله

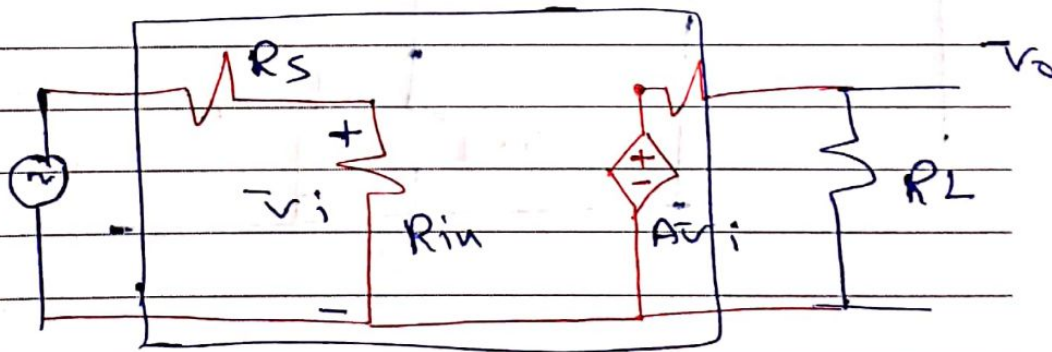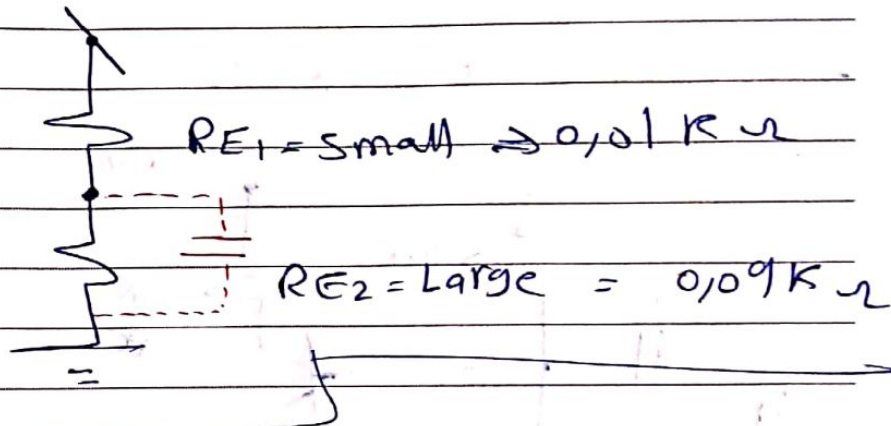

ideal voltage Amp $\Rightarrow R_{in} = \infty$, $R_o = zero$

دول او اقله ، ideal voltage Amp

$$V_i = \frac{V_s \cdot R_{in}}{R_{in} + R_s}$$


$$V_o = \frac{A_v V_i R_L}{R_o + R_L}$$

55 }

* to gain all advantages of R_E and minimize its disadvantages: R_E is usually made of 2 parts small value and large value.

- then connect CE across large value.

- For the cct shown:

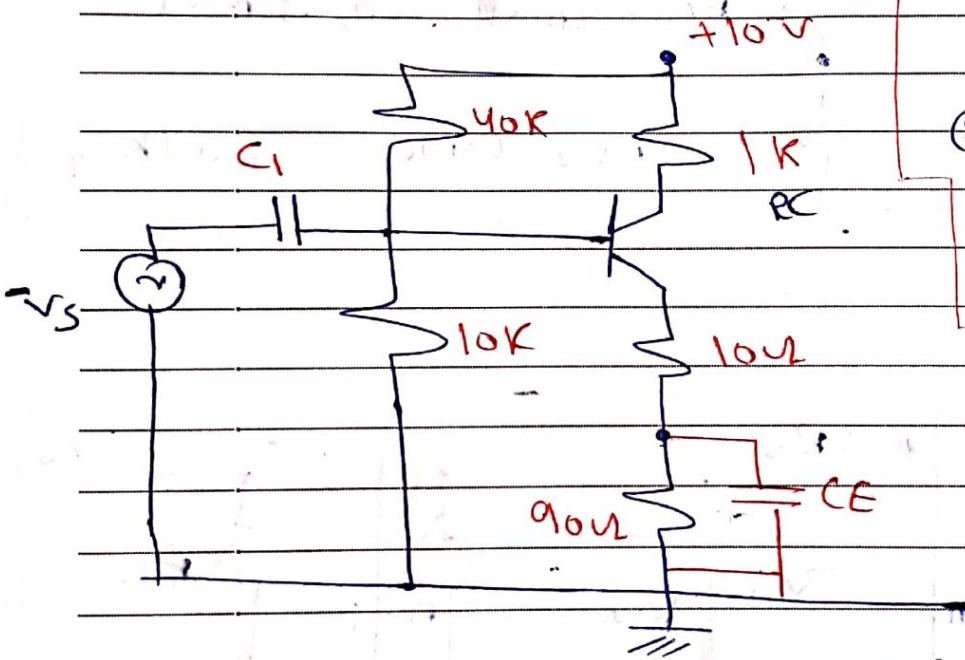

① Find:

I_{CQ}, V_{CEQ}

② Draw

s.s. Ac. eq. cct

③ Find

A_V, A_I, R_{in}, R_o

* write DC and AC equations and find their slopes.

$$R_{Th} = 0.1 (\beta + 1) R_E$$

For design Bias stable cct.

① For D.C. Analysis:



$I_{CQ} = 5.4 \text{ mA}$
 $V_{CEQ} = 4 \text{ V}$

D.C. Load


D.C.L.L

$$-V_{CC} + I_C R_C + V_{CE} + \frac{(\beta + 1) I_C R_E}{\beta} = 0$$

$$V_{CE} = V_{CC} - I_C \left(R_C + \frac{\beta + 1}{\beta} R_E \right)$$

→ slope for D.C.L

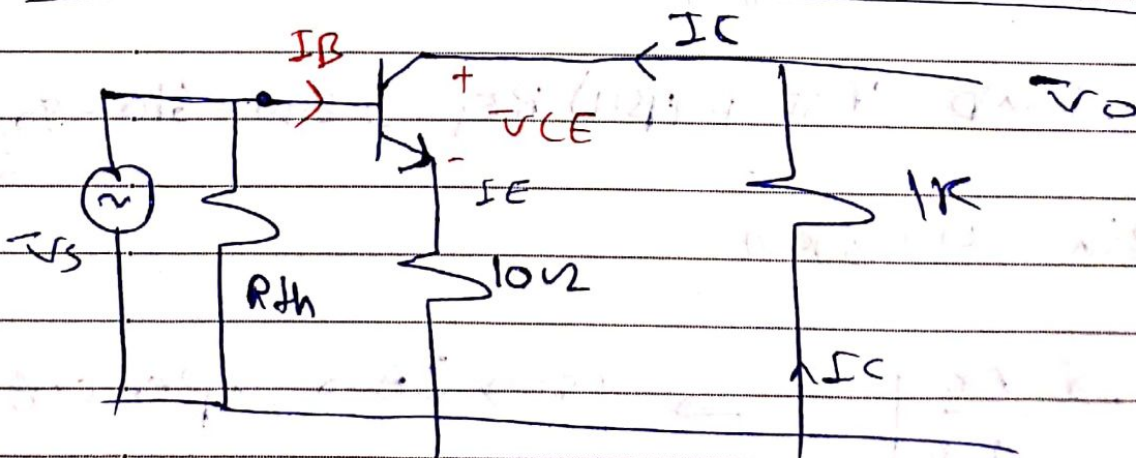D.C. analysis (D.C.L.L) is used to find the Q-point of the transistor. It involves analyzing the circuit with all capacitors open-circuited.




A.C.C.C.L

A.C.L.L ⇒ $V_{CE} + \frac{(\beta + 1) I_C R_E}{\beta} + I_C R_L = 0$

$$V_{CE} = -I_C \left(\frac{\beta + 1}{\beta} R_E + R_L \right)$$

57]

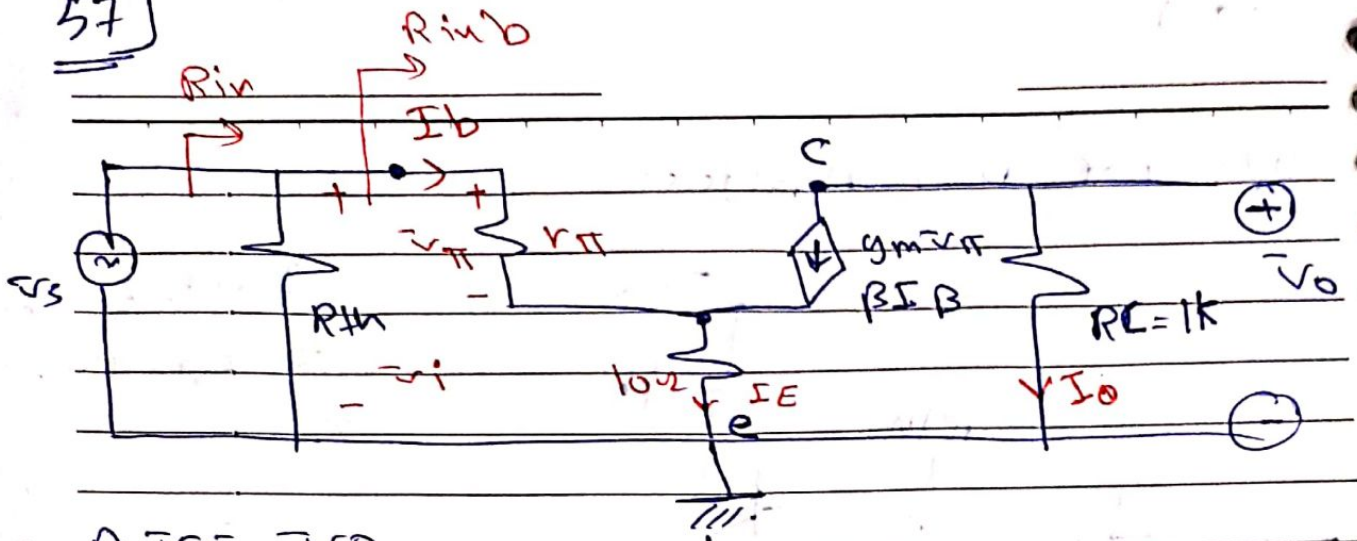

$$A_v = \frac{v_o}{v_i}$$

$$v_o = -\beta I_B R_C, \quad v_i = v_s = v_{\pi} + I_E R_E$$

$$v_i = I_B r_{\pi} + (\beta + 1) I_B R_E$$

$$v_i = I_B (r_{\pi} + (\beta + 1) R_E)$$

$$A_v = \frac{v_o}{v_i} = \frac{-\beta I_B R_C}{I_B (r_{\pi} + (\beta + 1) R_E)} = \frac{-\beta R_C}{r_{\pi} + (\beta + 1) R_E}$$

$$R_{in} = R_{TH} \parallel R_{inB}$$

$$R_{inB} = r_{\pi} + (\beta + 1) R_E = 290 + 6100 = 9000 \Omega$$

$$R_{in} = 0,8 k\Omega$$

$$R_o \rightarrow \frac{v_x}{I_x} \mid \Rightarrow v_s = 0, I_B = 0, \text{ open ckt}$$

$$R_o = R_C = 1 k\Omega$$

$$v_s = 0$$

$\frac{A_v}{A_v} \approx \frac{G}{R_E} \approx \frac{R_E}{R_E} \approx 1$

stabilize $\leftarrow R_E$) , ϕ -pt

180° phase shift, C.E) , ϕ -pt

$A_v > 1$, $A_i > 1$ C.E) , ϕ -pt

- (Voltage + Current Amp)

$R_o \approx R_C$ (Moderate r_{out})

$R_{in} = \text{Moderate}$

① C.E with R_E (reduce A_v , stabilize ϕ -pt)

$R_{in} \approx R_E$

② C.E with R_E Capacitor

$A_v \approx \frac{R_C}{r_e}$, $R_{in} \approx R_E$

First) , ϕ -pt

Qetami



Electricals 4 You
لجنة الهندسة الكهربائية

لجنة الهندسة الكهربائية | الجامعة الهاشمية

دفتر

Electronics 2

إعداد: مؤمن القطامي

من شرح: د. هادي العيثاوي





/Electricals.hu
/groups/Electricals4You



www.E4UHU.com

* Common-collector Amp [C.C [emitter-follower]]

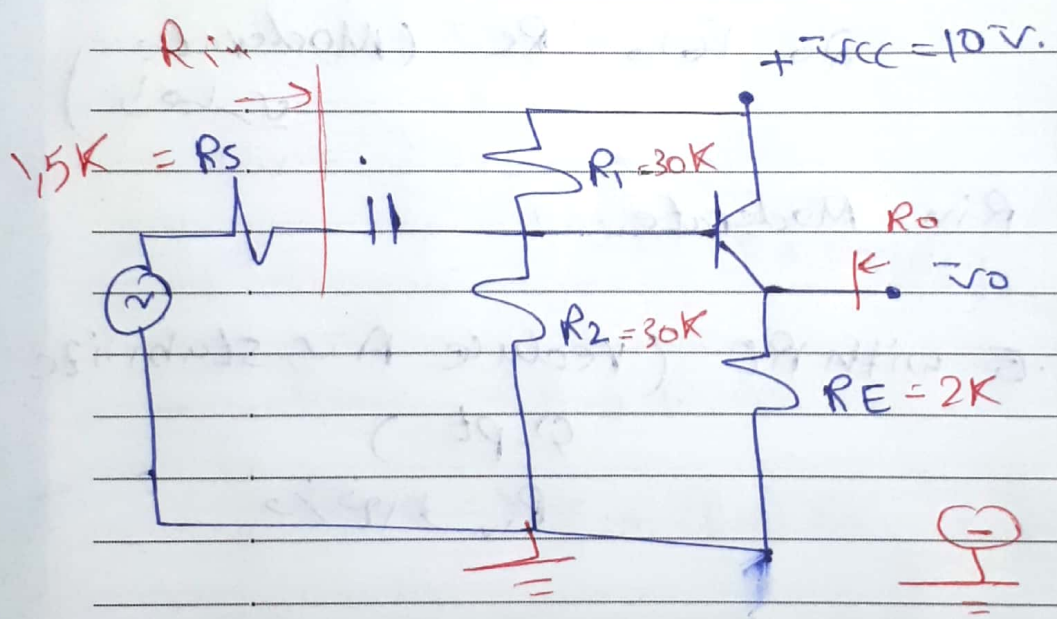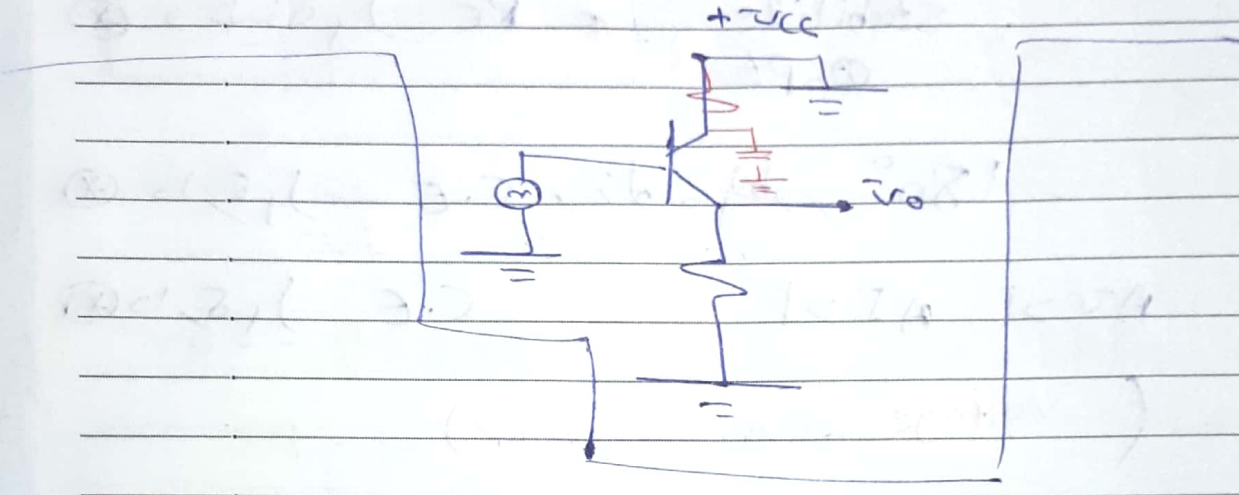$v_i \rightarrow$ base
 $v_o \rightarrow$ from \ominus C \rightarrow Common Terminal




$\beta = 100, V_{BE} = 0.7V$

$V_A = 200V$

1) Determine, I_{CQ} , V_{CEQ} .

2) Draw s.s.A.C equ ckt and find $A_v, A_i, R_{in}, R_b, R_o$.

60

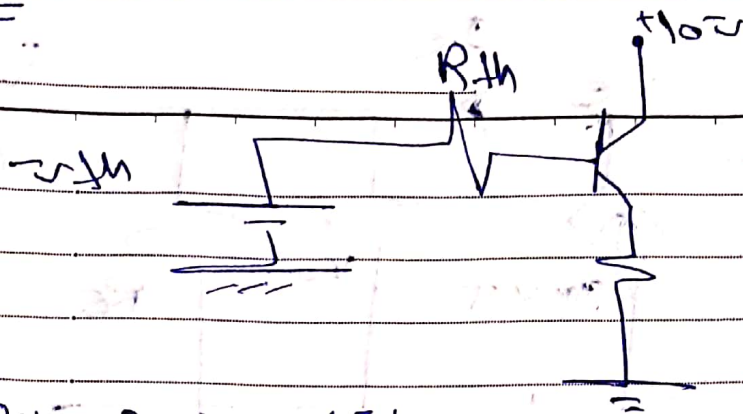

$$R_{th} = 30 // 30 = 15 k\Omega$$

$$V_{th} = 5V$$

KVL: $-V_{th} + I_B R_{th} + V_{BE} + (\beta + 1) I_B R_E = 0$

$$I_B = 0,02 mA$$

$$I_C = \beta I_B = 100 * 0,02 = \boxed{2 mA}$$

$$I_E = (\beta + 1) I_B = \boxed{2,02 mA}$$

KVL: $-V_{CC} + V_{CE} + I_E R_E = 0$

$$\boxed{V_{CE} = 5,96V}$$

D.C.L.L equation:


$$-10 + V_{CE} + I_E R_E = 0$$

$$V_{CE} = \frac{10 - 10I}{100} R_E I_C$$

$$\text{slope} \Rightarrow \frac{-\beta}{(\beta + 1) R_E}$$

Slope AC = slope D.C \Rightarrow in Common Collector.

61)

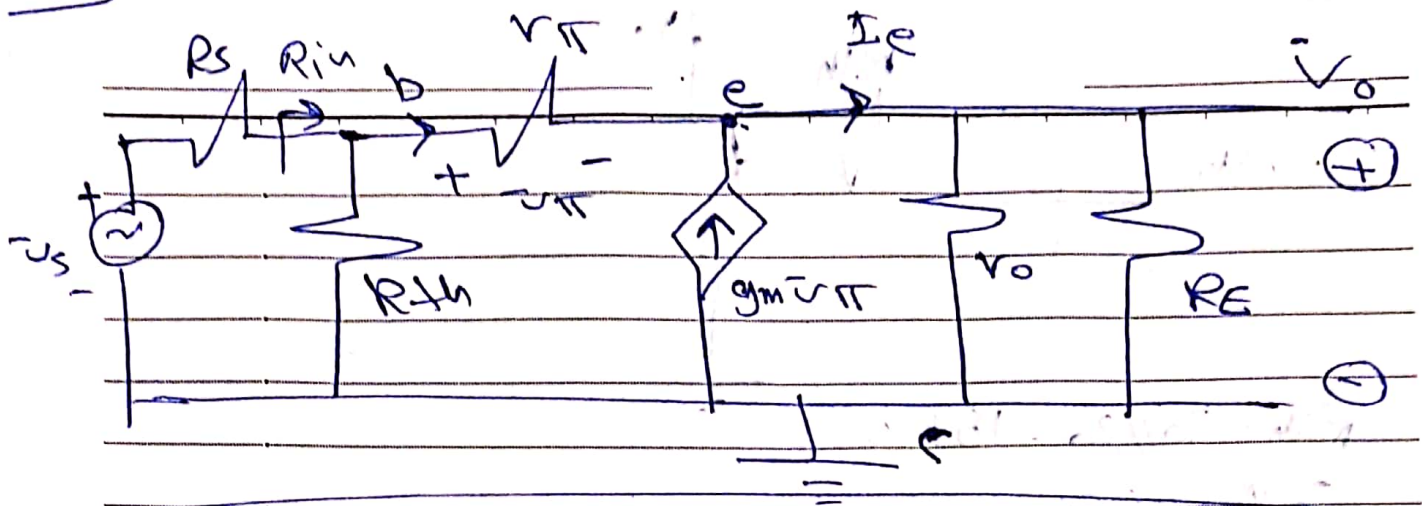

$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v_i} \times \frac{v_i}{v_s}$$

$$v_o = (\beta + 1) I_b \cdot (r_o \parallel R_E)$$

$$-v_s + v_{\pi} + v_o = 0$$

$$v_i = I_b r_{\pi} + (\beta + 1) I_b (r_o \parallel R_E)$$

$$\frac{v_o}{v_i} = \frac{(\beta + 1) I_b (r_o \parallel R_E)}{I_b (r_{\pi} + (\beta + 1) (r_o \parallel R_E))} = \frac{(\beta + 1) (r_o \parallel R_E)}{r_{\pi} + (\beta + 1) (r_o \parallel R_E)}$$

$$\frac{v_i}{v_s} = \frac{R_{in}}{R_{in} + R_s}$$

$$\Rightarrow R_{in} = R_{BH} \parallel R_{ib}$$

$$R_{ib} = \frac{v_i}{I_b} = r_{\pi} + (\beta + 1) (r_o \parallel R_E)$$

$$A_v = \frac{(\beta + 1) (r_o \parallel R_E) \cdot R_{in}}{r_{\pi} + (\beta + 1) (r_o \parallel R_E) \cdot R_{in} + R_s} = \frac{v_o}{v_s}$$

62)

$$A_V < 1, \phi = \text{zero}$$


$$\text{If } (\beta+1)(r_o \parallel R_E) \gg r_{\pi}$$

$$R_{in} \gg R_S, A_V \approx 1 \Rightarrow v_o \approx v_s$$

[emitter-follower] *منه الدارة تسمى الكولمب، الكولمب الكولمب، الكولمب الكولمب*

$$A_I = \frac{I_o}{I_{in}} = \frac{I_o}{I_b} \times \frac{I_b}{I_{in}}$$
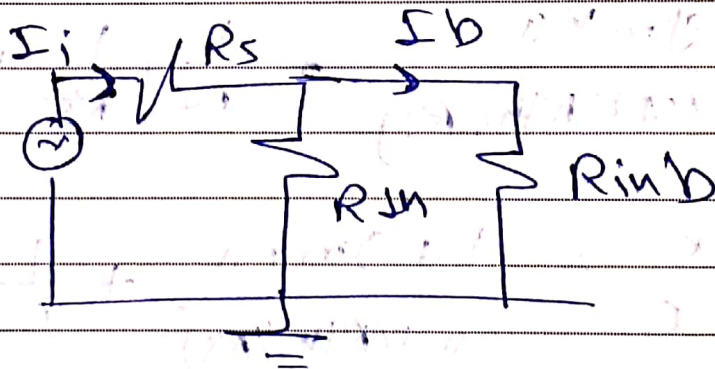
$$I_o = \frac{(\beta+1) \cdot I_b \cdot r_o}{r_o + R_E}$$



$$I_b = \frac{I_i \cdot R_{Th}}{R_{Th} + R_{in}} \Rightarrow \frac{I_b}{I_i} = \frac{R_{Th}}{R_{Th} + R_{in}}$$

$$A_I = \frac{(\beta+1) \cdot r_o}{r_o + R_E} \times \frac{R_{Th}}{R_{Th} + R_{in}}$$

- For $r_o \gg R_E$
 $R_{Th} \gg R_{in}$

$$A_I \approx (\beta+1) \Rightarrow \text{Max}$$

only we can use it as ~~voltage~~ current Amp but not voltage Amp.

b3

$R_{in} = R_{th} // R_{ib} \rightarrow$ high.

$R_o = \frac{v_x}{i_x} \Big|_{v_s = 0} \rightarrow$ KCL @ Node of v_{π}
 $\sum I_{in} = \sum I_{out}$

$$i_x + g_m v_{\pi} = \frac{v_x}{R_E} + \frac{v_x}{r_o} + \frac{v_x}{v_{\pi} + (R_{th} // R_S)}$$

$$v_{\pi} = - \frac{v_x \alpha}{v_{\pi} + (R_{th} // R_S)}$$

$$\frac{i_x}{v_x} = \frac{g_m v_{\pi}}{v_{\pi} + (R_{th} // R_S)} + \frac{1}{r_o} + \frac{1}{R_E} + \frac{1}{v_{\pi} + (R_S // R_{th})}$$

$$\frac{1}{R_o} = \frac{i_x}{v_x} = \frac{1 + g_m v_{\pi}}{v_{\pi} + (R_{th} // R_S)} + \frac{1}{r_o} + \frac{1}{R_E}$$

$$\frac{1}{R_o} = \frac{1 + \beta}{v_{\pi} + (R_{th} // R_S)} + \frac{1}{r_o} + \frac{1}{R_E}$$

$$R_o = \frac{v_{\pi} + (R_{th} // R_S)}{\beta + 1} // r_o // R_E$$



Resistor Reflection Rule \rightarrow Low

64)

[Emitter follower] ← C.C. 1, 0, 1, 0, 0, 0 ⊗

$A_v < 1$, $A_i > 1$, R_{in} : high, R_o : Low
 $\phi = \text{Zero}$

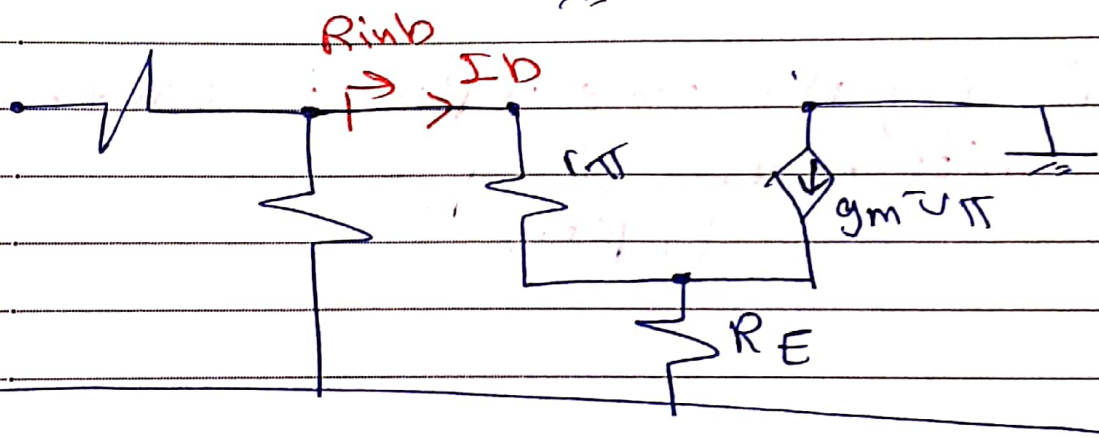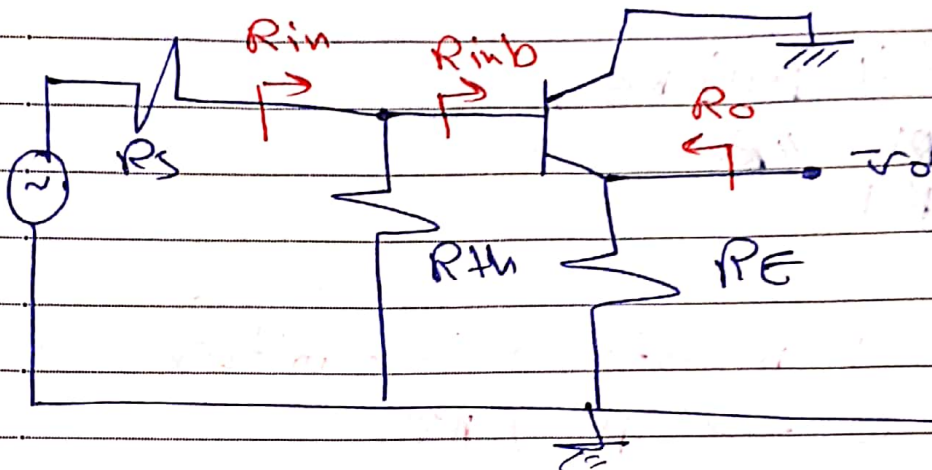
(15) 5, 1, 0, 0, 0
 ⊗ Resistance Reflection Rule (RRR):



Emitter \downarrow , is $\frac{v_o}{v_i}$ $\frac{i_o}{i_i}$ $I_e = (\beta + 1) I_B$
 $(\beta + 1) R_E \leftarrow$ Base \downarrow

$$R_{inb} = r_{\pi} + (\beta + 1) R_E$$

65

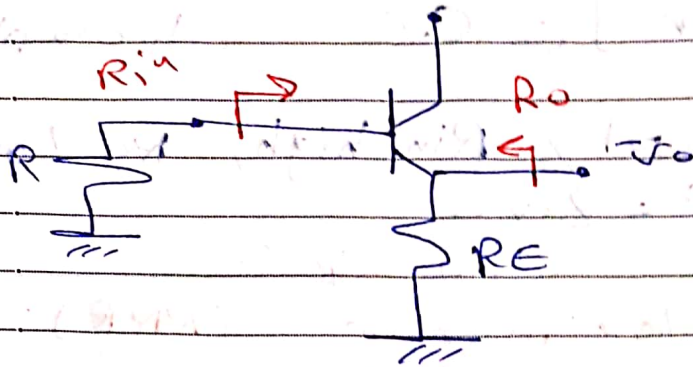

$$R_{in} = R \parallel (\beta + 1) R_E$$

$$R_o = \frac{R_L}{\beta + 1} \parallel R_E$$

RRR: Any Resistance in Emitter Seen from base $\Rightarrow (\beta + 1) R_E$


✓ IRR: Any Resistance in Base is Seen from inverse emitter as

$$\frac{R}{(\beta + 1)}$$

66

* Common-Base Amp (C.B) Amp.

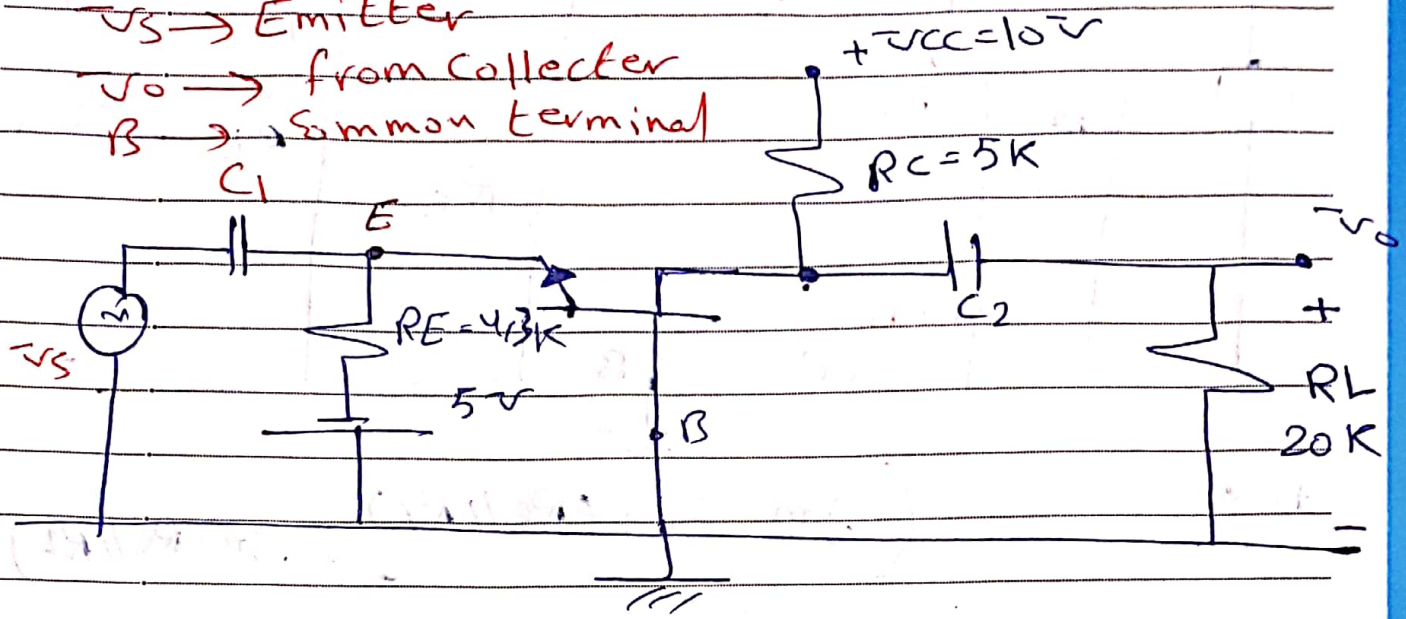$v_s \rightarrow$ Emitter
 $v_o \rightarrow$ from collector
 $B \rightarrow$ Common terminal



$\beta = 100, v_{BE} = 0.7V, v_A = \infty$

- Find \Rightarrow
- ① I_C, v_{CE}
 - ② Draw A.C ~~and~~ eq cct.
 - ③ A_v, R_{in}, R_o

KVL: $v_{BE} + I_E R_E - 5 = 0$

$$I_E = \frac{5 - v_{BE}}{R_E} = \frac{5 - 0.7}{4.3K} = 1mA$$

$I_C = \alpha I_E = 0.99mA$


KVL:

$$-10 + I_C R_C + v_{CE} + I_E R_E - 5 = 0$$

$$I_C = \frac{10 - I_E R_E + 5}{R_C} = \frac{10 - 1 \times 4.3 + 5}{5K}$$

$I_{C_E} = 5.75V$

67

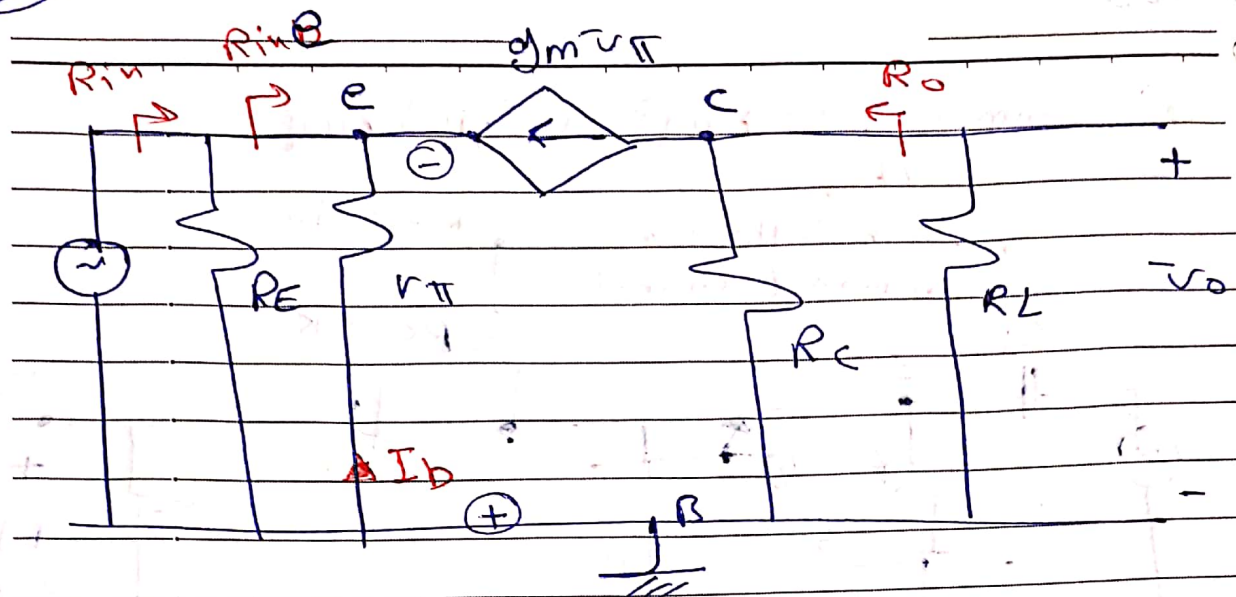

$$A_v = \frac{v_o}{v_s} = \frac{(g_m v_{\pi}) (R_C \parallel R_L)}{-v_{\pi}} = g_m (R_C \parallel R_L)$$

Note that $A_v > 1$, $\phi = \text{zero}$.

$$R_o = \frac{v_x}{i_x} \Rightarrow \text{when } v_s = 0, v_{\pi} = 0.$$

$$g_m = v_{\pi} = 0.$$

dep c.c is o.c.

$$R_o = R_C$$

$$R_o = R_C \parallel r_o \leftarrow v_o$$

68

68

$$R_{ie} = \frac{R_E}{\beta+1} \frac{v_{\pi}}{I} = \frac{-v_{\pi}}{-I_e} = \frac{v_{\pi}}{I_e}$$

$$\frac{v_{\pi}}{(\beta+1)I_D} = \frac{v_{\pi}}{(\beta+1) \times \frac{v_{\pi}}{r_{\pi}}} = \frac{v_{\pi}}{\beta+1}$$

() , r_{π} is the input resistance at the emitter.
 BASE is connected to emitter

$$\Rightarrow R_{in} = R_E // R_{ie} \Rightarrow R_E // \frac{r_{\pi}}{\beta+1} = R_{in}$$

R_{in} for Common Base is Low.
 Note that

$$-A_I = \frac{I_o}{I_i} = \frac{-g_m v_{\pi} \times R_c}{R_c + R_L} \quad \text{C.P.R}$$

$$v_{\pi} = -I_i \times R_{in} = -I_i \left(\frac{r_{\pi}}{\beta+1} // R_E \right)$$

But $\frac{r_{\pi}}{\beta+1} \ll R_E$

i.e $R_{in} \approx \frac{r_{\pi}}{\beta+1}$

$$v_{\pi} = -I_i \times \frac{r_{\pi}}{\beta+1}$$

$$I_o = \left(\frac{g_m r_{\pi}}{\beta+1} \times \frac{R_c}{R_c + R_L} \right) \times I_i$$

69

$$\frac{I_o}{I_i} = A_I = \frac{\beta}{\beta + 1} \times \frac{R_c}{R_c + R_L}$$

For No $R_L \Rightarrow A_I(\text{Max}) \approx \frac{\beta}{\beta + 1} \approx \alpha$

Note that:

$$|A_I| < 1, \quad |A_I| \approx 1 = \frac{I_o}{I_i}$$



"Current Follower"
"16 μ / 5.15 V"

* Summary for S.S BJT Amp:

Amp	A_V	A_I	ϕ	R_{in}	R_o
C.E	> 1	> 1	180°	moderate	moderate E_o high
C.C	< 1	> 1	0	high	low
C.B	> 1	< 1	0	Low	moderate E_o high

70

$AV > 1$, Low R_o , $\phi = 0^\circ$

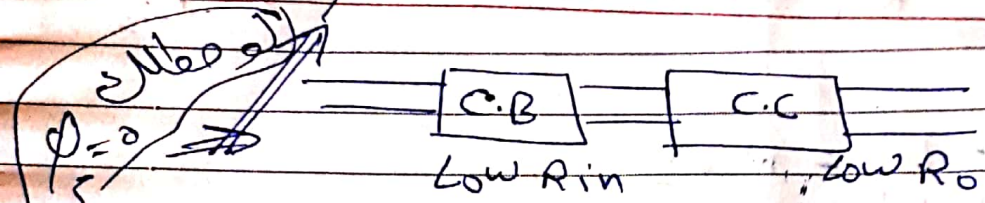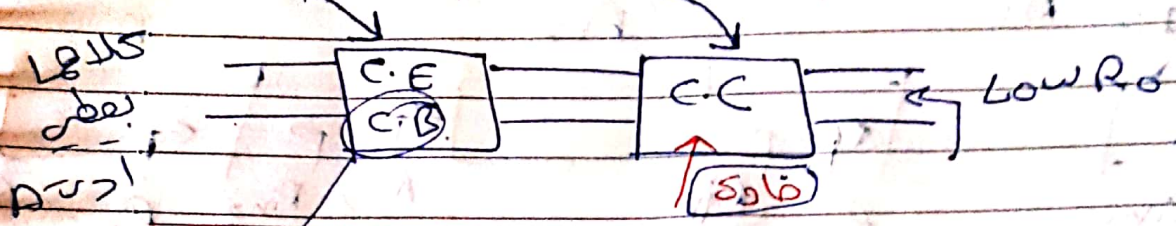


⊗ We must use Multistage if we want specific out put that can't get by single stage.

Multistage

Cascade

Cascode

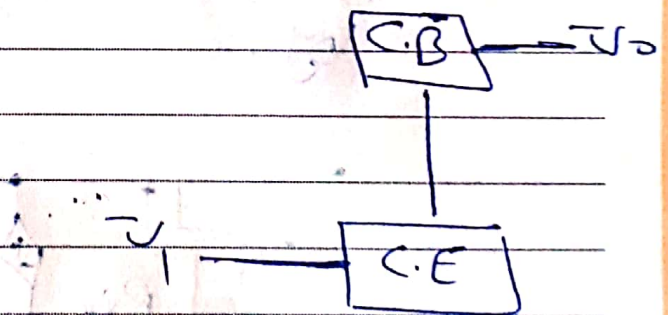


"or" "or"

wideband

low load Amp

(71)

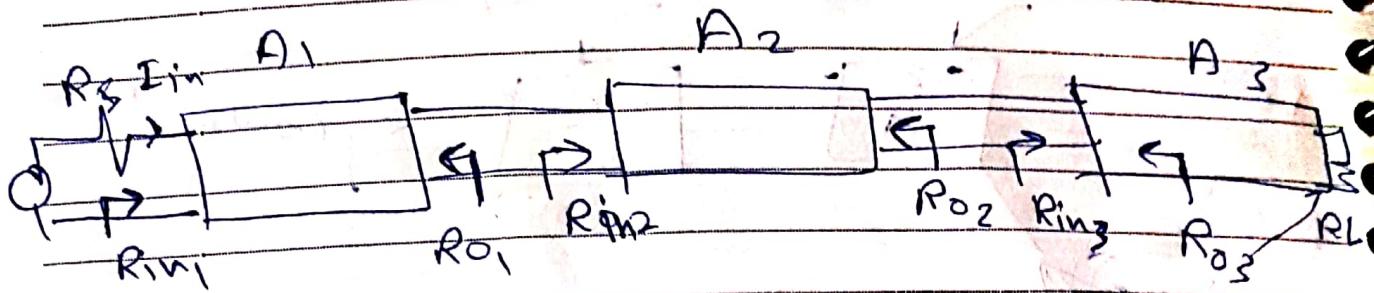

$$R_{in\ total} = R_{in1}$$

$$R_{o\ total} = R_{o3}$$


$$A_v = \frac{V_L}{V_S}$$

برك تاخر بعين لا يتاخر ال RL
 الة تفرقة كالدرا و بعينها

$$A_i = \frac{I_o}{I_{in}} = \frac{V_o}{\frac{R_L}{V_S}} = \left[A_v \cdot \frac{R_S + R_{in}}{R_L} \right]$$



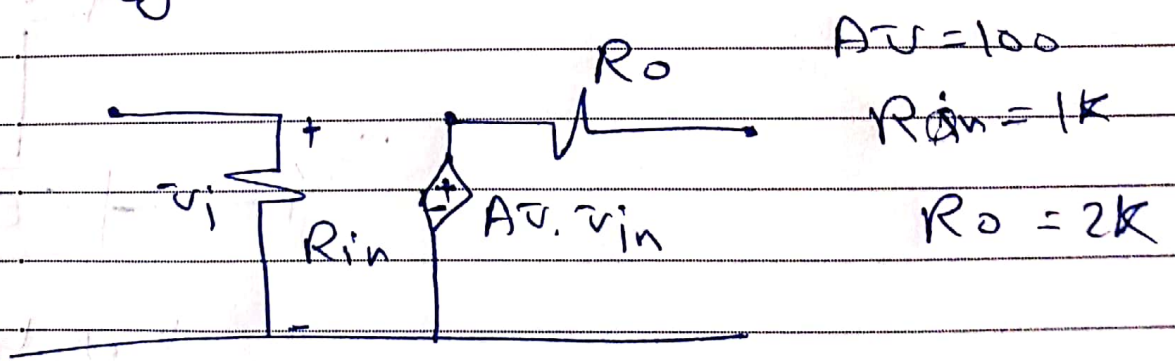
(*) any voltage Amp can be represented by:-



$$A_v = \frac{1}{2} * 100 * \frac{1}{2} * 100 * \frac{1}{2}$$


$$\frac{V_o * V_1}{V_1 * V_{o1}}$$

72

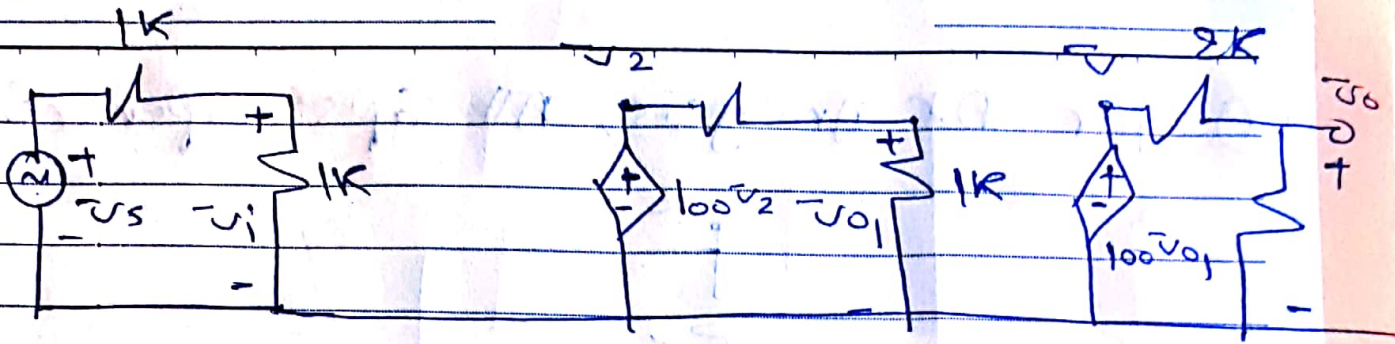

$$R_i = 1K \quad R_o = 2K$$

Ex:

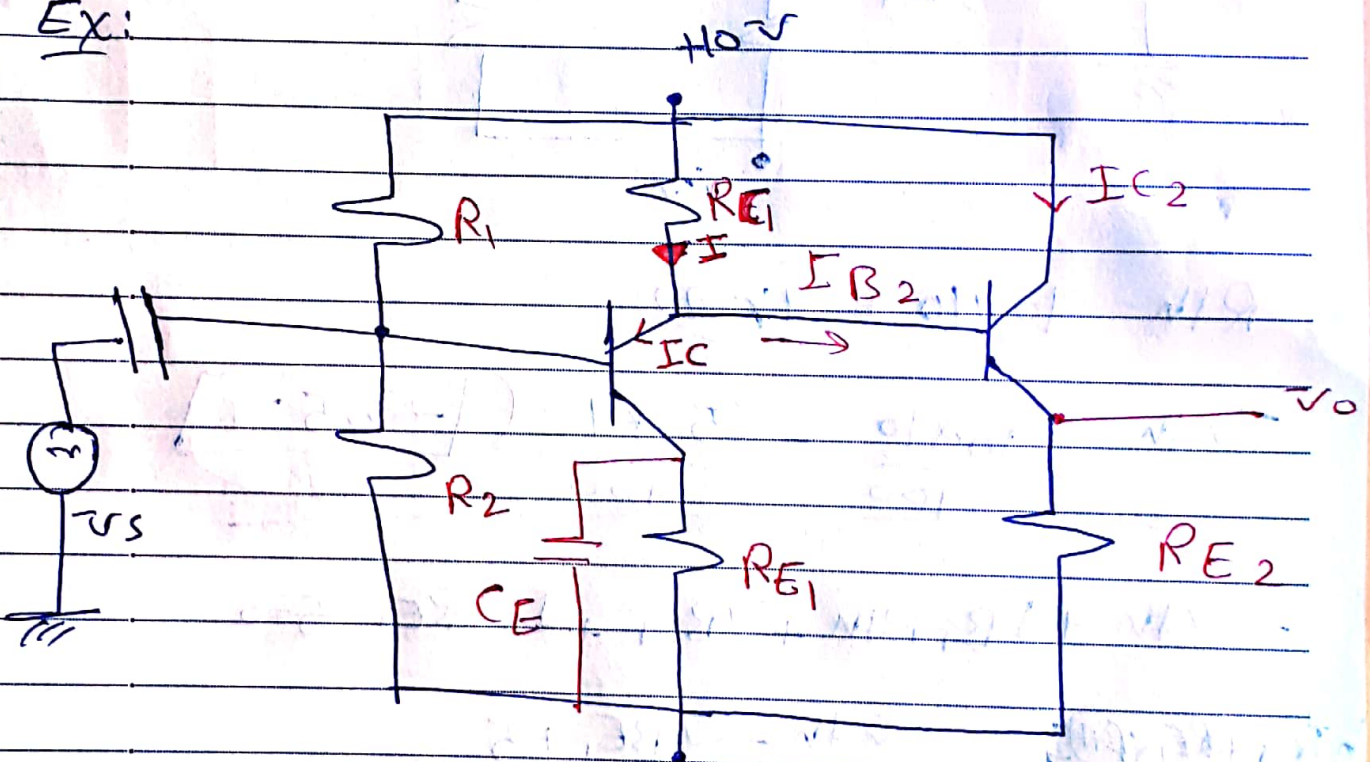

-5

① Q_1 and Q_2 are identical with $\beta = 100$, $V_{BE} = 0.7V$, $V_A = 100V$.


- $R_1 = 90K$
- $R_2 = 10K$
- $R_{C1} = 5K$
- $R_{E1} = 0.7K$
- $R_{E2} = 1K$
- $V_{BE} = 0.7V$

② find I_{B1} , I_{C1} , V_{CE1} , I_{B2} , I_{C2} , V_{CE2}

③ Draw s.s.a.c equivalent and find A_{V1} , A_{V2} , A_V , R_{in} , R_o , R_i , R_o , R_{i2}

73

* For D.C Analysis, All caps open ckt

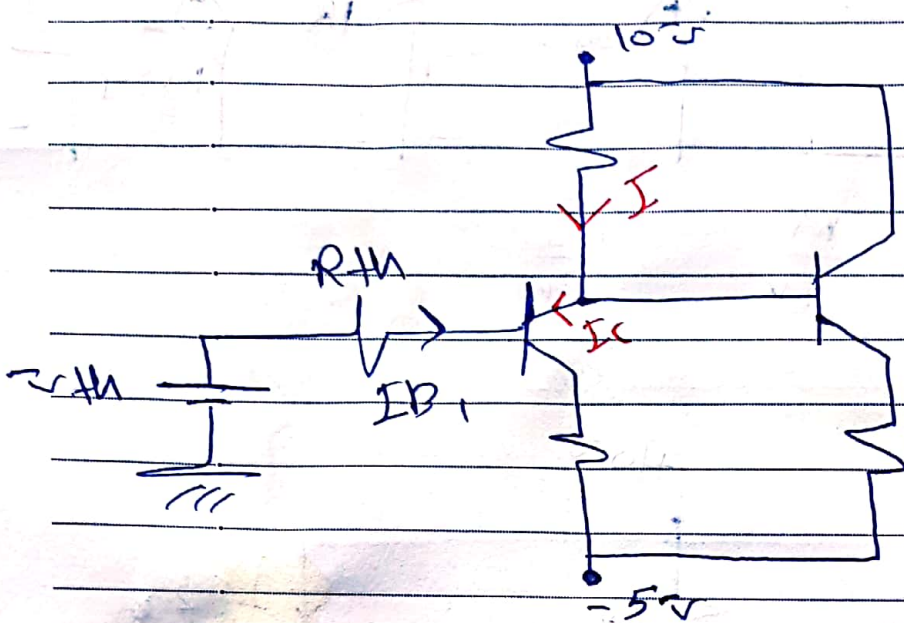

$$R_{Th} = 10 \parallel 10 = 9k\Omega$$

$$V_{Th} = \frac{10 \times 10}{100} - \frac{5 \times 90}{100} = -3,5V$$

$$-V_{Th} + I_{B1} R_{Th} + V_{BE1} + I_{E1} R_{E1} - 5 = 0$$

$$R_{Th} I_{B1} + R_{E1} (\beta + 1) I_{B1} = V_{Th} - V_{BE1} + 5$$

$$I_{B1} = \frac{-3,5 + 5 - 0,7}{9 + 10 \times 0,7} = \frac{0,8}{79,7} = 0,01 \text{ mA}$$

$$I_{C1} = \beta I_{B1} = 1 \text{ mA}$$

$$-10 + I_{C1} R_{C1} + V_{CE1} + I_{E1} R_{E1} - 5 = 0$$

$$V_{CE1} = 14,3 - I_{C1} R_{C1}$$

74

$I \Rightarrow$ KCL at node C_1 :

$$I = I_{C_1} + I_{B_2}$$

$$\frac{10 - V_{C_1}}{R_{C_1}} = 1\text{m} + I_{B_2}$$

$$\Rightarrow -V_{C_1} + V_{BE} + (\beta + 1) I_{B_2} R_{E_2} - 5 = 0$$

$$\frac{5 + V_{C_1} - V_{BE}}{(\beta + 1) R_{E_2}} = I_{B_2}$$

$$I_{B_2} = \frac{V_{C_1} + 4,3}{101 \times 1\text{k}}$$

$$\Rightarrow \frac{10 - V_{C_1}}{R_{C_1}} = 1\text{m} + \frac{V_{C_1}}{101} + \frac{4,3}{101}$$



$$\boxed{V_{C_1} = 4,5\text{V}}$$

$$I_{B_2} = \frac{4,5 + 4,3}{101\text{k}} = \boxed{0,08\text{mA}}$$

$$I = \frac{10 - 4,5}{5\text{k}} = 1,1\text{mA}$$

$$\underline{V_{CE_1} \checkmark, V_{CE_2} \checkmark}$$

75

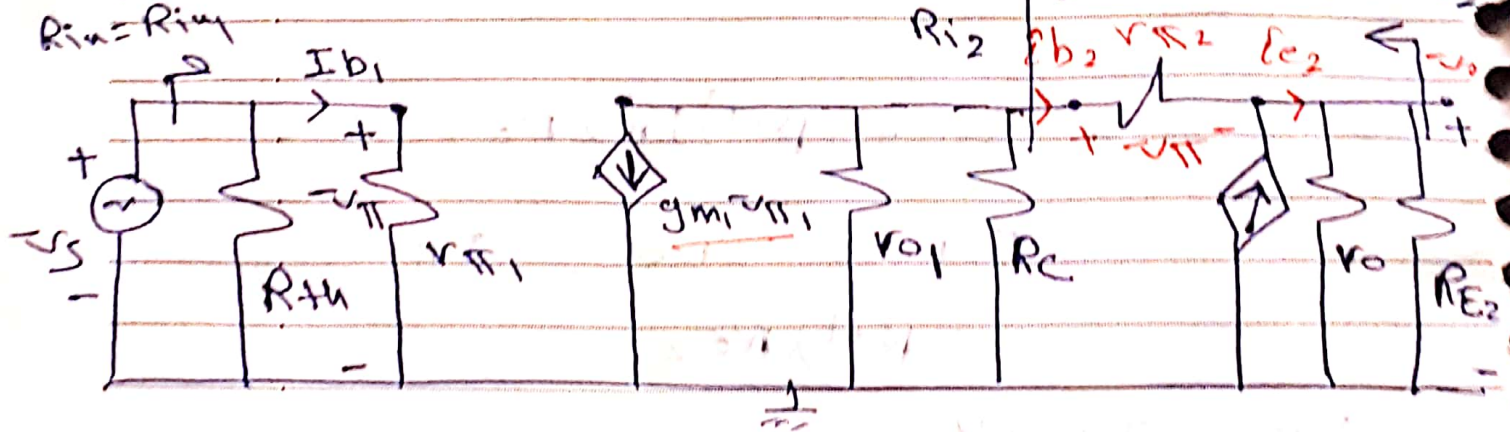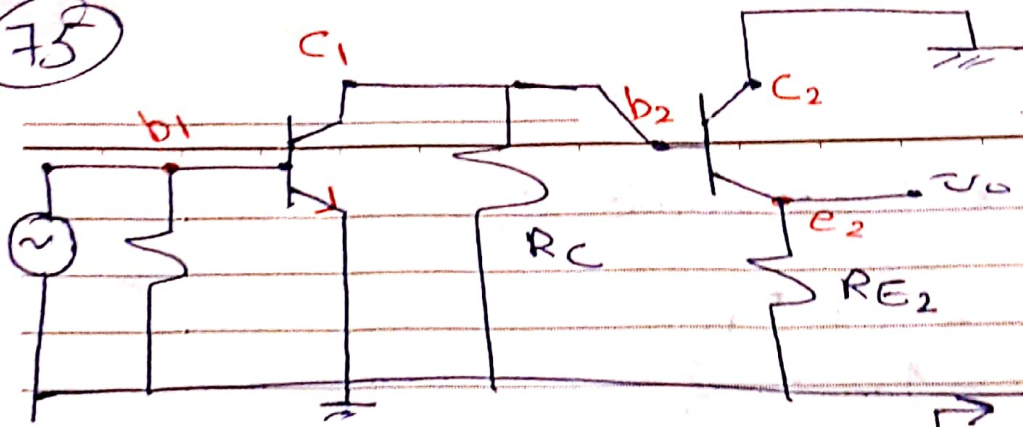

$$A_{V1} = \frac{v_{O1}}{v_S}, \quad A_{V2} = \frac{v_O}{v_{i2}}$$

$$A_{VT} = \frac{v_O}{v_{i2}} \times \frac{v_{O1}}{v_S} = A_{V2} \times A_{V1}$$

$$v_O = (\beta + 1) I_{b2} (v_{O2} \parallel R_{E2})$$

$$-v_{i2} + v_{\pi 2} + v_O = 0$$

$$-v_{i2} = I_{b2} r_{\pi 2} + (\beta + 1) I_{b2} (v_{O2} \parallel R_{E2})$$

$$A_{V2} = \frac{v_O}{v_{i2}} = \frac{(\beta + 1) I_{b2} (v_{O2} \parallel R_{E2})}{I_{b2} (r_{\pi 2} + (\beta + 1) (v_{O2} \parallel R_{E2}))}$$

$$A_{V2} = \frac{(\beta + 1) (v_{O2} \parallel R_{E2})}{(r_{\pi 2} + (\beta + 1) (v_{O2} \parallel R_{E2}))}$$

76

$$v_{o1} = -g_{m1} v_{\pi 1} (r_{o1} \parallel R_C \parallel R_{in2})$$

$$R_{in2} = R_{inb2} = \frac{v_x}{i_x} = r_{\pi 2} + (\beta + 1)(r_{o2} \parallel R_{E2})$$

"by Resistance Reflection Rule"

$$v_s = v_{\pi 1}$$

$$\Rightarrow A v_i = \frac{-g_{m1} v_{\pi 1} (r_{o1} \parallel R_C \parallel R_{in2})}{v_{\pi 1}}$$

$$A v_i = -g_{m1} (r_{o1} \parallel R_C \parallel R_{in2})$$

$$A v_T = \frac{-g_m (R_C \parallel r_{o1} \parallel R_{E2}) * (\beta + 1)(r_{o2} \parallel R_{E2})}{r_{\pi 2} + (\beta + 1)(r_{o2} \parallel R_{E2})}$$

$$A I = \frac{I_o}{I_i} = \frac{\frac{v_o}{R_{E2}}}{\frac{v_s}{R_{in}}} = A v * \frac{R_{in}}{R_E}$$

$$R_{in} = R_{th} \parallel r_{\pi 1}$$

$$R_{o1} = R_C \parallel r_{o1}$$

$$R_{in2} = R_{inb2} = (r_{\pi 2} + (\beta + 1)(r_{o2} \parallel R_{E2}))$$


$$R_o = R_{o2} = \frac{v_x}{i_x} \Big|_{v_s = 0}$$

when $v_s = 0, v_{\pi 1} = 0, g_{m1} v_{\pi 1} = 0 \Rightarrow$ IRRR $\Rightarrow R_o = R_{o2} = (r_{o1} \parallel R_C) + r_{\pi 2} \parallel (r_{o2} \parallel R_{E2})$
 $(\beta + 1)$

77


" 17 سہ لہجہ "

2) Cascode Multistage:

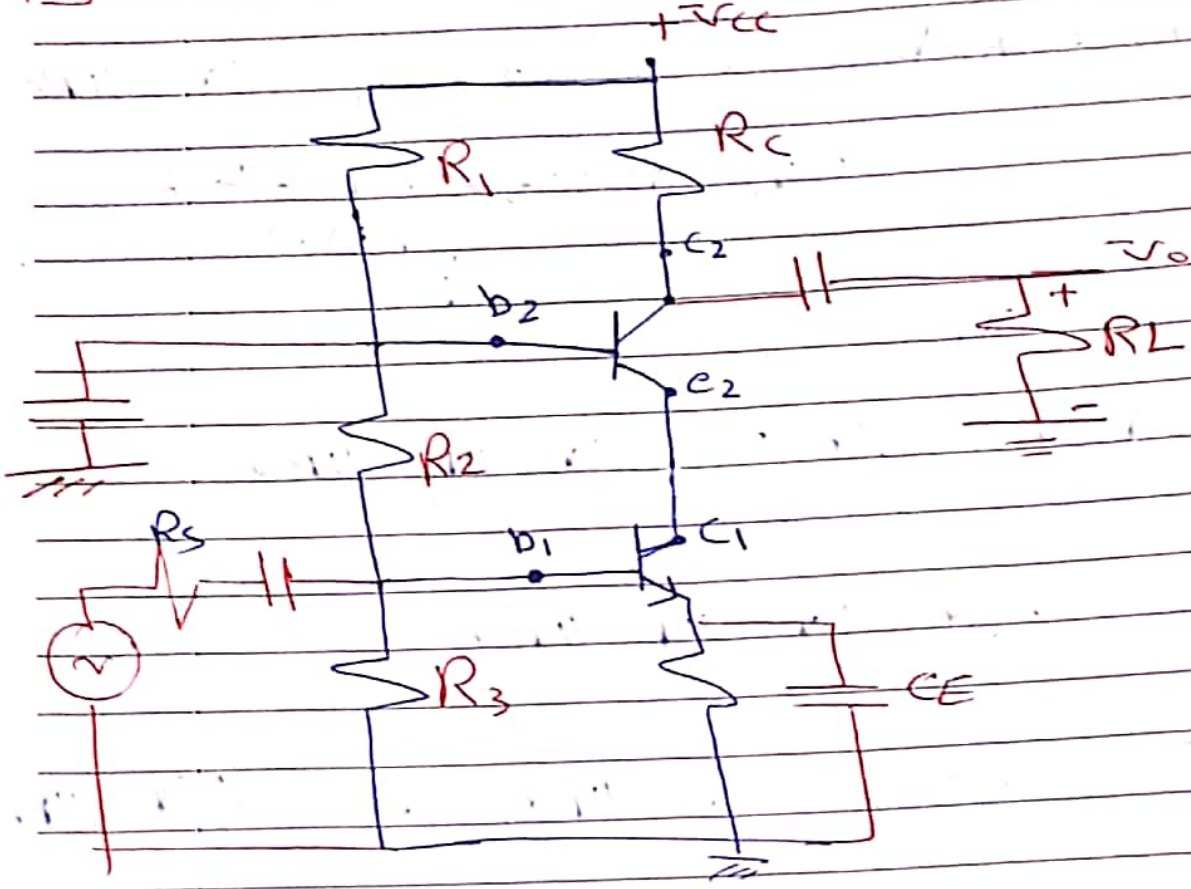

⊗ لا انتہی، ان کے ساتھ، (cascode) کے ساتھ

" C.E ⊕ C.B "

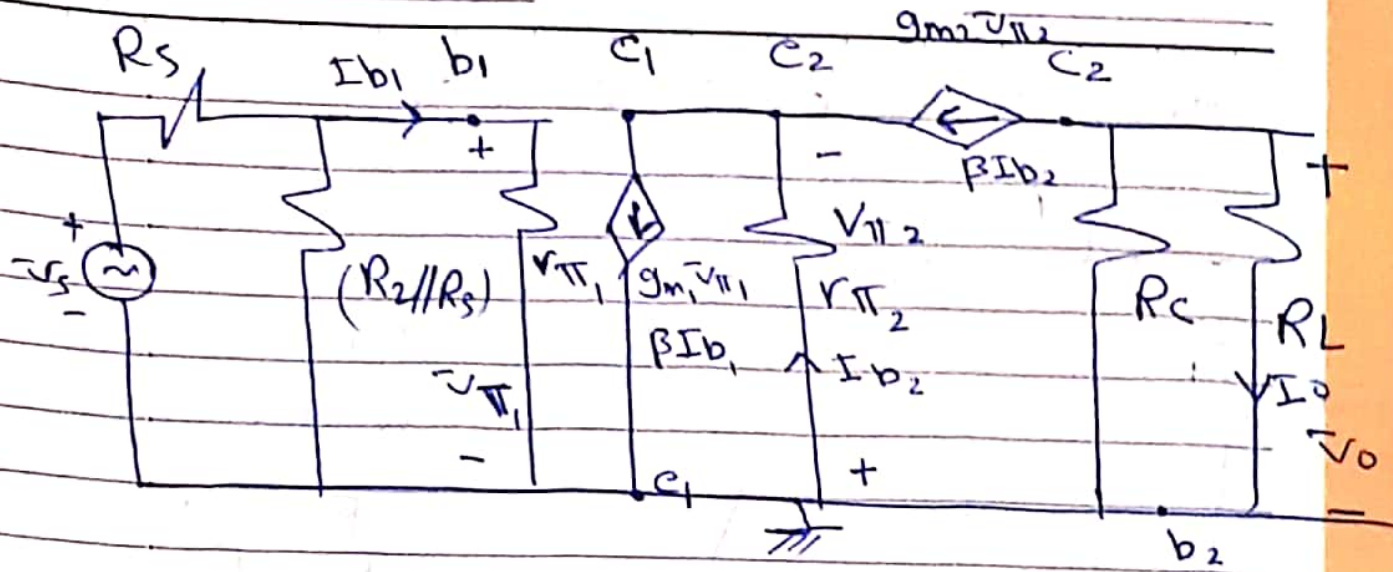

$$\Rightarrow \frac{v_o}{v_s} = AV = \frac{v_o}{v_{\pi 2}} \cdot \frac{v_{\pi 2}}{v_{\pi 1}} \cdot \frac{v_{\pi 1}}{v_s}$$

$$\frac{v_o}{v_{\pi 2}} = -g_{m2} (R_c // R_L) \leftarrow$$

KCL at Node c

$$I_{c2} + I_{b2} = I_{e2}$$


$$g_{m2} v_{\pi 2} + \frac{v_{\pi 2}}{r_{\pi 2}} = g_{m1} v_{\pi 1}$$

$$v_{\pi 2} \left(\frac{g_{m2} r_{\pi 2} + 1}{r_{\pi 2}} \right) = g_{m1} v_{\pi 1}$$

$$\frac{v_{\pi 2}}{v_{\pi 1}} = \frac{v_{\pi 2} g_{m1}}{\beta + 1} \Rightarrow \text{remember } \underline{g_m v_{\pi} = \beta}$$

79

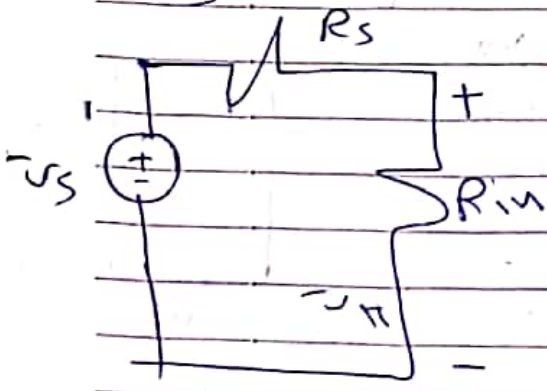$\frac{V_{\pi}}{V_S} \Rightarrow$ voltage divider:



$$V_{\pi} = V_S \times \frac{R_{in}}{R_{in} + R_S}$$

$$\frac{V_{\pi}}{V_S} = \frac{R_{in}}{R_{in} + R_S}$$

$$A_V = -g_{m2}(R_C // R_L) \times \frac{V_{\pi 2} g_{m1}}{(\beta + 1)} \times \frac{R_{in}}{R_{in} + R_S}$$

$$A_V = - \left(\frac{\beta}{\beta + 1} \right) g_{m1} (R_C // R_L) \times \frac{R_{in}}{R_{in} + R_S}$$

≈ 1

$$A_V = \frac{-g_{m1} (R_C // R_L) \times R_{in}}{R_{in} + R_S}$$

$$R_{in} = (R_2 // R_3) // R_{in b}$$

$$R_{in} = (R_2 // R_3) // V_{\pi 1}$$

$$R_o = R_C \Rightarrow \text{Common Base}$$

$$R_C // r_o \leftarrow r_o \approx 0.5 \text{ } \Omega$$

80 (x) لا تفسر، انظر: $r_{\pi 1}$ بين $+$ Base و $-$ Emitter

(x) // // // r_o بين $+$ C و $-$ E

$R_{o1} = \infty$

$R_{in2} = \frac{r_{\pi 2}}{\beta + 1}$

(x) Cascode \Leftarrow A و B

\Leftarrow C.B + C.E
 تفسر $r_{\pi 1}$ C.E

لا تفسر C.B دخل على $r_{\pi 1}$ ونسبة قولتة وهي
 ما يتغير $A < 1$

Analysis of Design \Leftarrow D.C Hint " $\bar{a} = 1$ "


$I_C = I_E$ \Leftarrow $\bar{a} = 1$

for high frequency. \Leftarrow Cascode \Leftarrow $\bar{a} = 1$

81

"Highest Current gain"

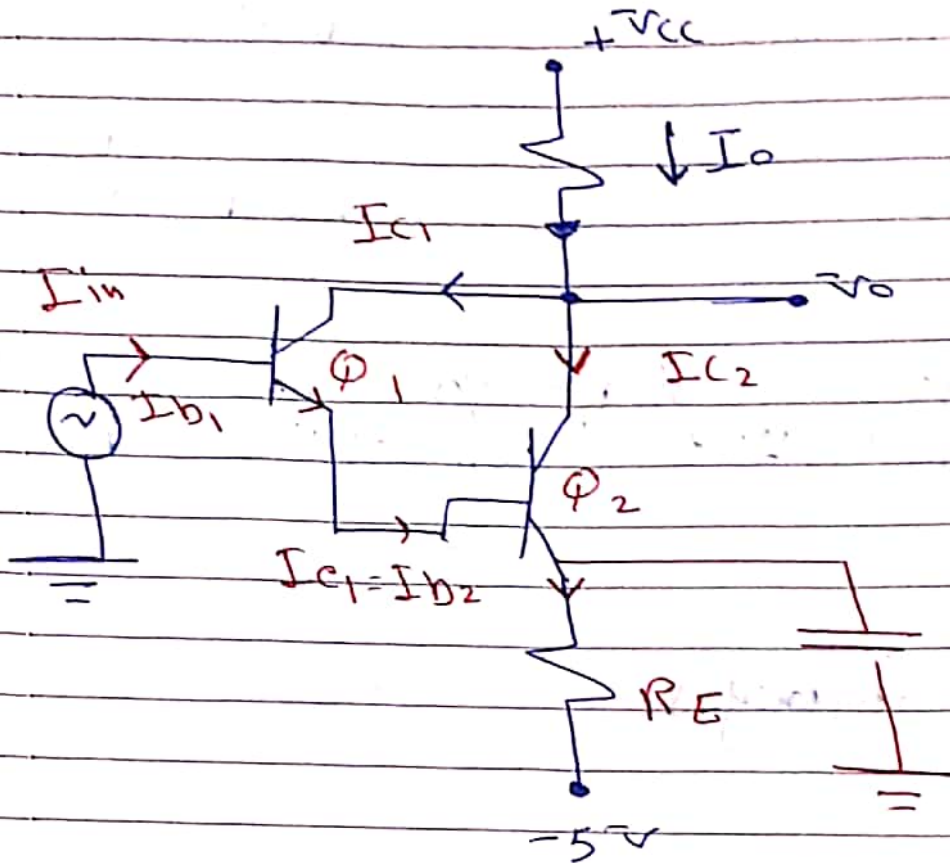3] Darlington Pair Configuration:
"Very high AI".



$$I_o = I_{C1} + I_{C2}$$
$$= \beta I_{b1} + \beta I_{b2}$$

$$\text{but } I_{b2} = I_{c1} - (\beta + 1) I_{b1}$$

$$I_{b1} = I_{in}$$


$$I_o = \beta I_{b1} + \beta(\beta + 1) I_{b1}$$

$$I_o = \beta I_{in} + \beta^2 I_{in} + \beta I_{in}$$

$$\frac{I_o}{I_{in}} = AI = \beta^2 + 2\beta \quad \underline{\underline{AI = \beta^2}}$$

82
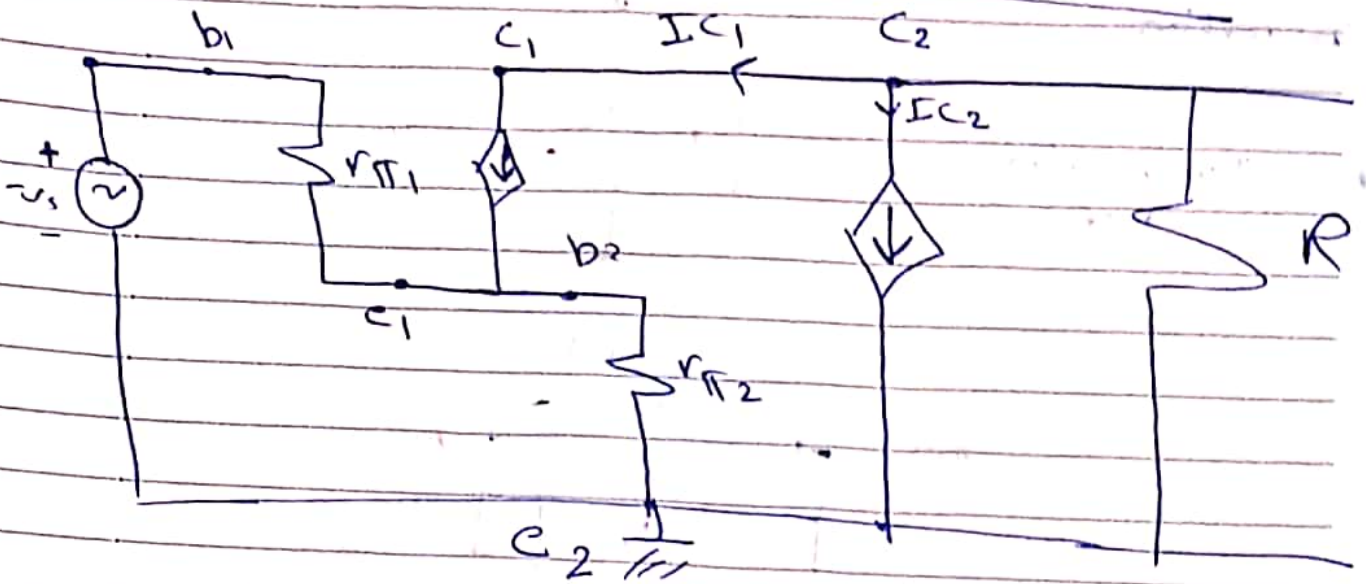
$$A_v = \frac{V_o}{V_s} = \frac{I_o R_c}{I_{in} R_{in}} = \beta I_b \times \frac{R_c}{R_{in}}$$



S.S.A.C equi cct.



Q3

"18 syllab"

* Operational Amplifier : (op. Amp)

Inverting

Non-Inverting
Ter.

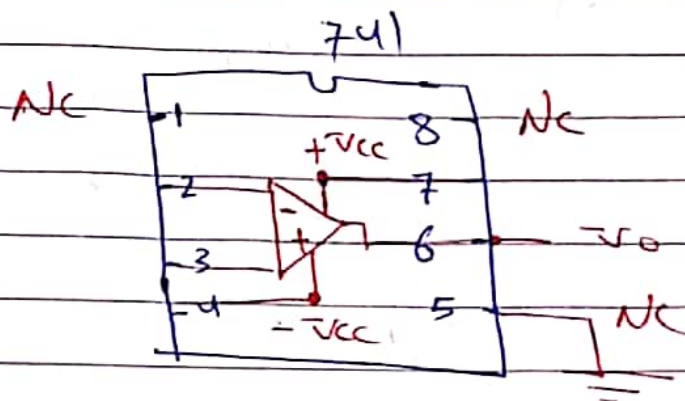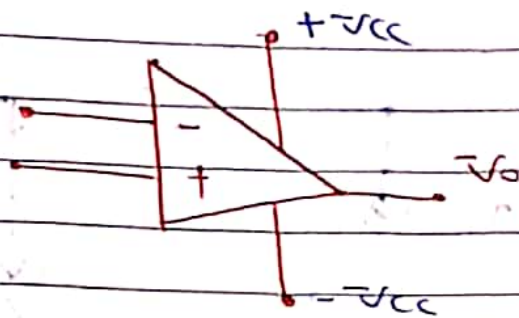

PIN - Diagram.

* op. Amp : very high gain voltage Amp contain multistage directly connected to BJT and FET compared.

it is a voltage controlled voltage source

$$"V_C V_S" \rightarrow V_O \propto V_i$$




$$V_o = A_o \cdot V_i, \quad A_o: \text{open loop gain}$$

84


⊗ BJT →

C.C.C.S

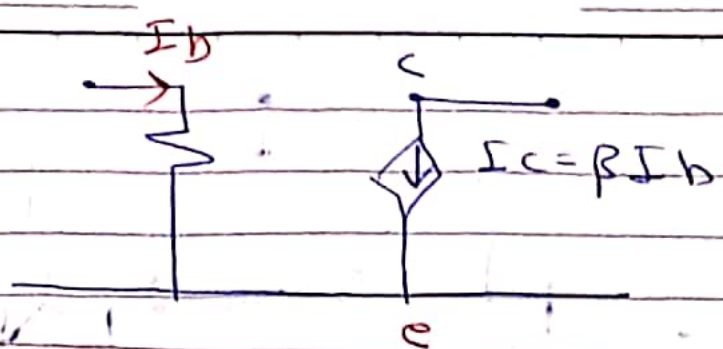



⊗ FET →

V.C.C.S

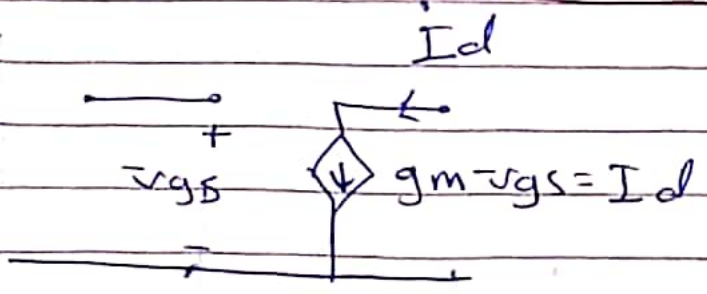

- the simple op-Amp contains:

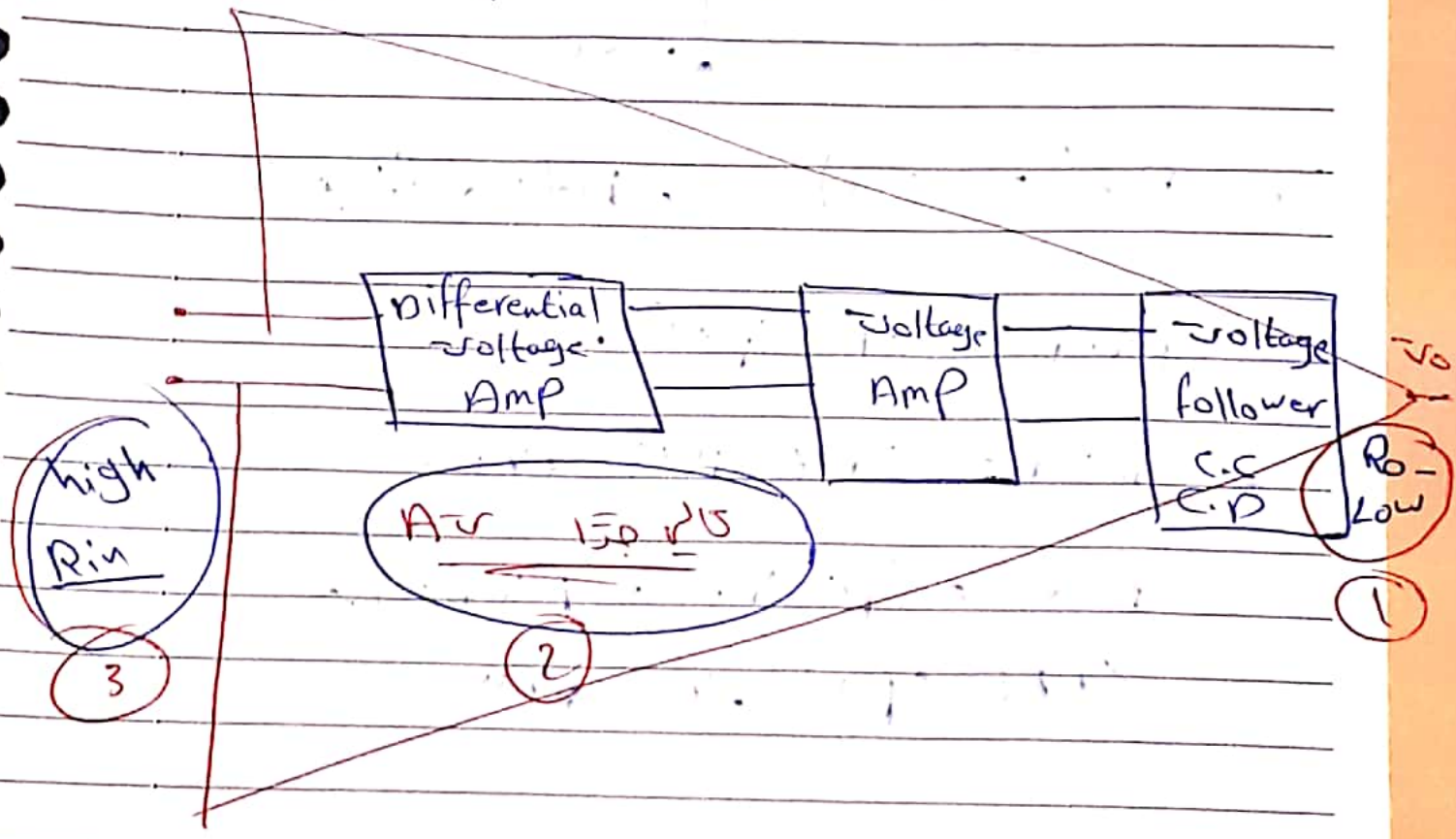

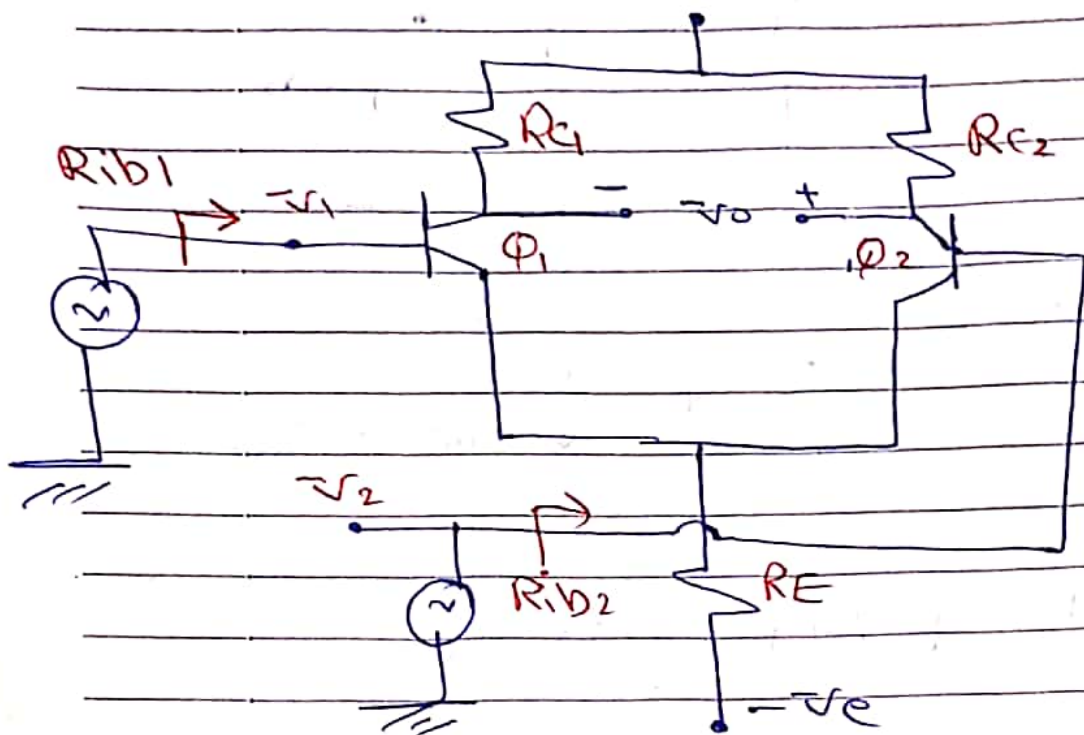


$v_o = A_d (v_2 - v_1)$, A_d : diff gain.

$R_{inb1} = 2RE(\beta + 1) + r_{\pi 1}$

$R_{inb2} = 2RE(\beta + 1) + r_{\pi 2}$


$R_{id} = (R_{inb1}) + (R_{inb2}) = 4RE(\beta + 1) + r_{\pi 1} + r_{\pi 2}$

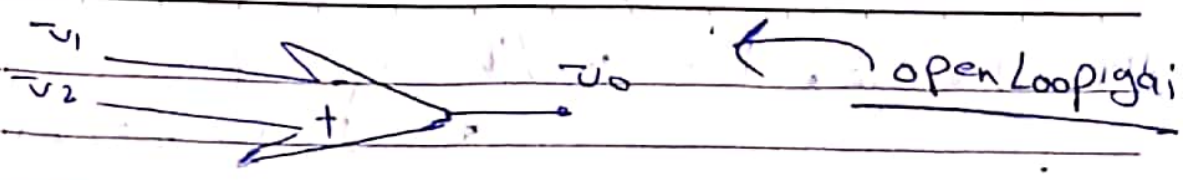R_{in} is very high. \leftarrow op-amp \rightarrow



$$\frac{v_o}{v_2 - v_1} = A_o \rightarrow \text{very high}$$

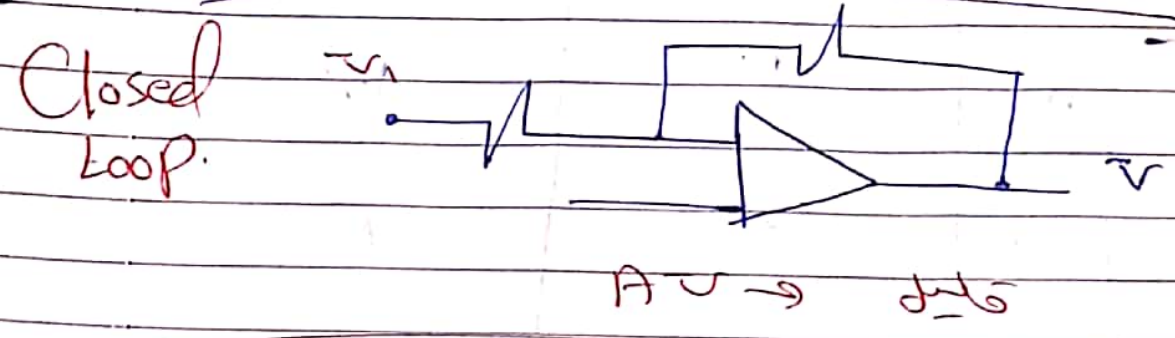A_o : تقوية قوة (تقوية) Amp
 A_v : تقوية CCT



*) تقوية قوة \leq op-Amp (تقوية) \leftarrow تقوية قوة
 (D.C) و (A.C) تقوية قوة

Directly connected \leftarrow system
 to each other

*) تقوية قوة Capacitors تقوية قوة

*) تقوية قوة op-Amp (تقوية) A_v, A_o

تقوية قوة \leftarrow system تقوية قوة
 تقوية قوة \leftarrow تقوية قوة تقوية قوة

87

opamp, V_{s} , Bandwidth, A_o , V_i \otimes
gain, no. of



\otimes op-Amp characteristics.

		ideal	Real (741 Bipolar op-Amp)
open loop gain	A_o	∞	10^5
Input Resistance	R_{in}	∞	$2M\Omega$
output Resistance	R_o	0	70Ω
Band width	B.W	∞	$1MHz$
Input Current	bias	Zero	$10nA$

88

"1st siglec"

(*) Transfer characteristics of op-Amp.

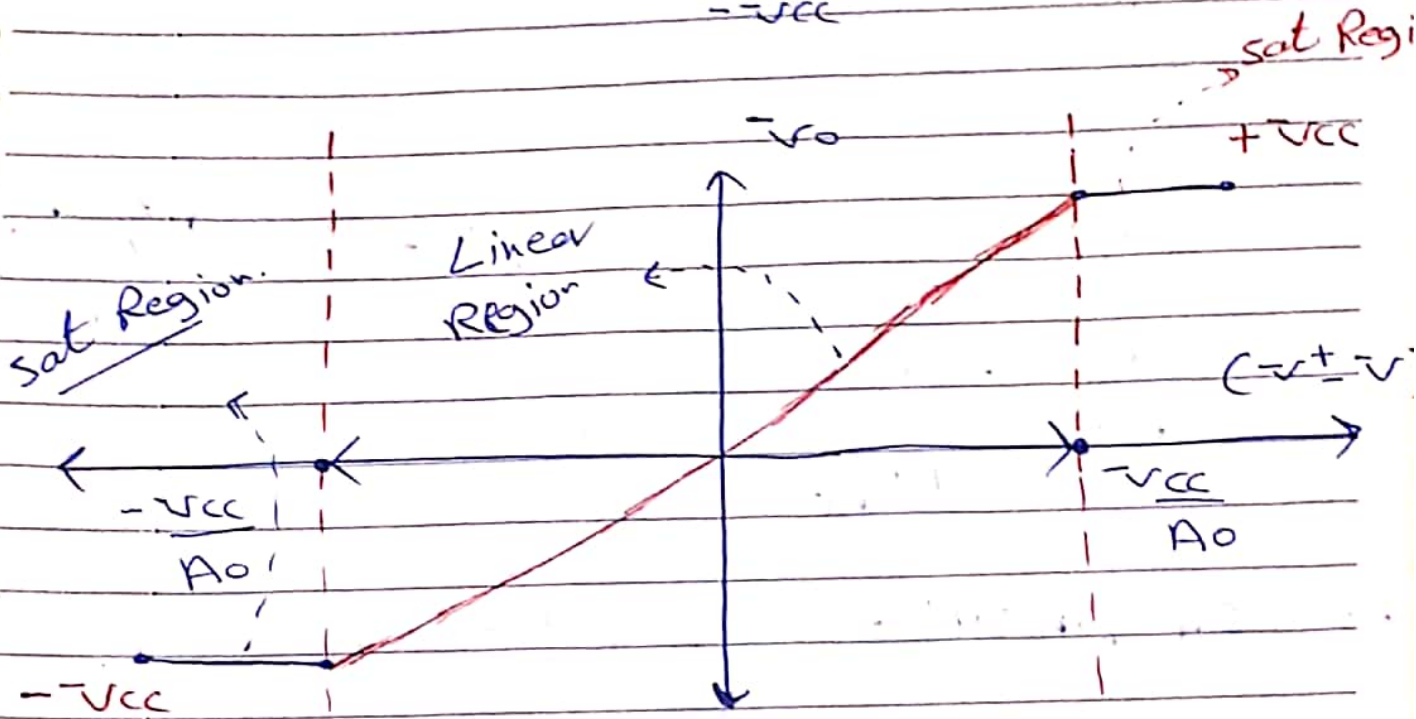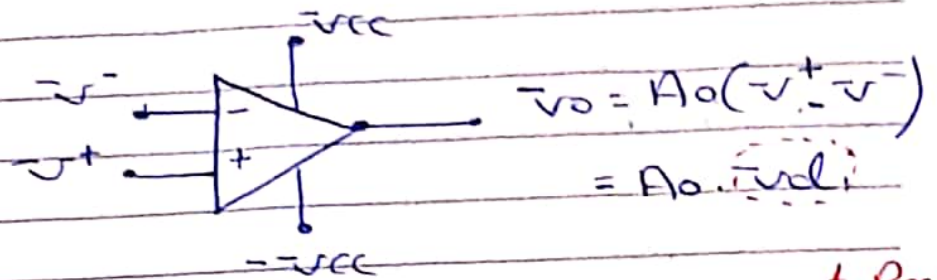

$$v_0(\text{max}) = +V_{CC} = A_0(v^+ - v^-)$$

ideally $A_0 = \infty$

(i) for $v^+ > v^- \Rightarrow v_0 = +V_{CC}$

(ii) for $v^+ < v^- \Rightarrow v_0 = -V_{CC}$

$$(v^+ - v^-)_{\text{max}} = \frac{V_{CC}}{A_0}$$

$$(v^+ - v^-) = -\frac{V_{CC}}{A_0}$$

89

① if $\Rightarrow \frac{-V_{CC}}{A_0} < v^+ - v^- < \frac{V_{CC}}{A_0}$

$v_o = A_0(v^+ - v^-)$

↳ Linear Region

$v_o \propto v^+ - v^-$

$v_d = v^+ - v^-$

② Saturation Region: $v_o \neq v_d$ (out put \neq in)

$\frac{-V_{CC}}{A_0} > v^+ - v^- > \frac{V_{CC}}{A_0}$

↳ $v_o = \pm V_{CC}$

Ex: for $\mu A 741: V_{CC} = \pm 15V, A_0 = 10^5$

① Linear Region:

$-\frac{V_{CC}}{A_0} < v_d < \frac{V_{CC}}{A_0} \Rightarrow \frac{15}{10^5} < v_d < \frac{15}{10^5}$

$-150\mu V < v_d < 150\mu V$

$v_o = A_0 \cdot v_d = A_0(v^+ - v^-)$


② Saturation Region: $150\mu V > v_d > 150\mu V$

$v_o = \pm V_{CC}$

(*) op-Amp Applications:

(A) Linear Applications:

(I) inverting Amplifier:

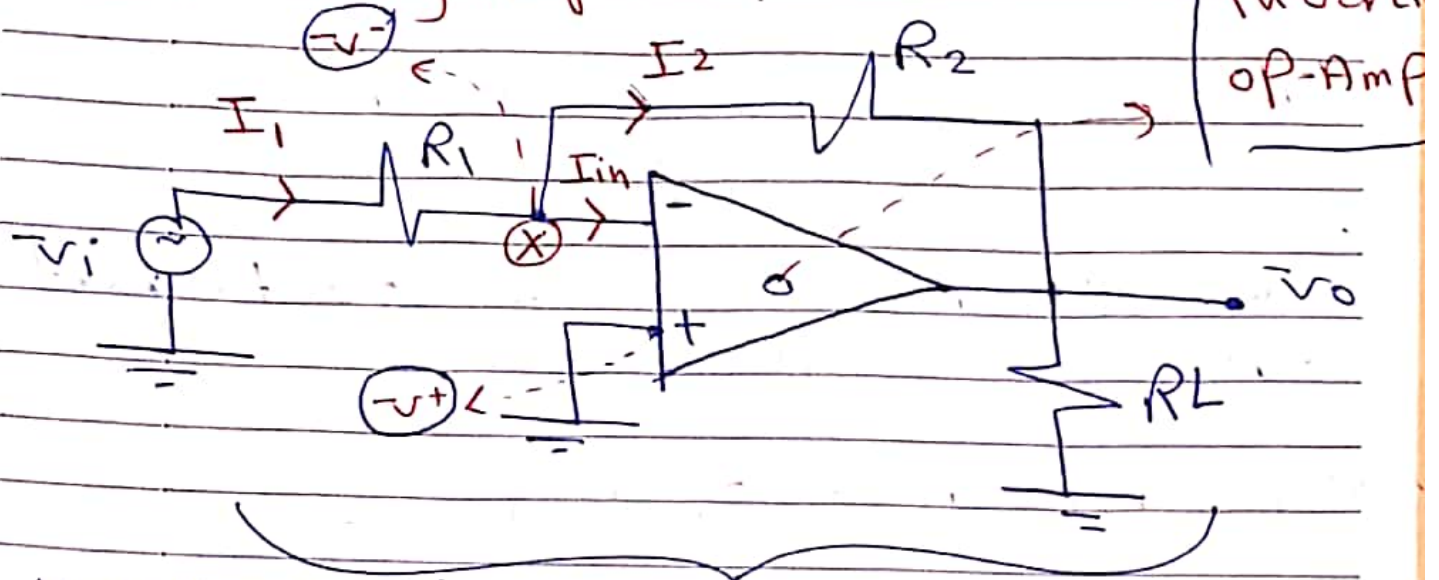

inverting Amplifier. v_o is v_i of v_o

KCL @ Node (x): $\sum I_{in} = \sum I_{out}$

$$I_1 = I_2 + I_{in}$$

$$\frac{v_i - v_x}{R_1} = \frac{v_x - v_o}{R_2} + I_{in}$$

Note: I_{in} is zero because $R_{in} = \infty$
 $I_{in} = \frac{v_i}{R_{in}} = \frac{v_i}{\infty} = \text{zero}$

(*) $v^+ = v^- \Rightarrow$ (virtual short)

قولنا $v^+ = v^-$ لان $v^+ = 0$ و $v^- = 0$ لان $v^+ = v^-$

(*) $v^+ = v^- = \text{zero}$ (virtual ground)
 لان $v^+ = 0$ و $v^- = 0$ لان $v^+ = v^-$

91

توضیح

$$v_o = A_o (v^+ - v^-)$$

$$v^+ - v^- = \frac{v_o}{A_o} \Rightarrow \text{For ideal op-Amp}$$

$$A_o = \infty$$



$$v^+ - v^- = \frac{v_o}{\infty} = \text{zero} \Rightarrow v^+ = v^-$$

virtual short \leftarrow short

- then if v^+ or v^- is connected to ground
 $v^+ = v^- = 0$ virtual ground.

⊗ Assuming ideal op-Amp then:

$$I_{in} = 0, \quad v^+ = v^- = \text{zero (v.g.)}$$

$$v_x = v^- - v^+ = \text{zero}$$

$$\frac{v_i - v_x}{R_1} = \frac{v_x - v_o}{R_2} + I_{in}$$

$$\frac{v_i}{R_1} = -\frac{v_o}{R_2} \Rightarrow v_o = -\frac{R_2}{R_1} v_i$$

$$\text{then } A_v = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

A_v : Closed Loop gain.

92

$$R_{in} = \frac{v_i}{I_1} \quad \left[\begin{array}{l} -v_i + I_1 R_1 + (-v_i - v_o) = 0 \\ \frac{v_i}{I_1} = R_1 \end{array} \right] \quad \text{zero}$$

$$R_{in} = R_1$$

بصورتی که R_1 و R_2 هر دو $10 \mu A$ و $10 \mu A$ (X)

* Let $R_2 = 10K$, $R_1 = 2K$, find A_v , R_{in} :

$$A_v = -\frac{R_2}{R_1} = -5 \quad / \quad R_{in} = R_1 = 2K\Omega$$

because $I_i = 0$ ideally.

$$I_1 = I_2 = \frac{v_i - v_x}{R_1} = \frac{v_i}{R_1} = \frac{4 \sin \omega t}{2K} = \boxed{2 \sin \omega t \text{ mA}}$$

Let $v_i = 4 \sin \omega t$

$$v_o = -\frac{R_2}{R_1} v_i \Rightarrow -\frac{10}{2} (4 \sin \omega t)$$

$$= -20 \sin \omega t \text{ Volt}$$

$I_L \Rightarrow v_o$) این است، این است، این است

این است، این است، این است، این است

$R_L = 20K$) این است، این است

$$I_L = 0 - \frac{v_o}{R_L} = \frac{20 \sin \omega t}{20K} = \boxed{1 \sin \omega t \text{ mA}}$$


Q3

(*) $R_o = R_o(\text{op-Amp.}) = \text{Zero (ideally)}$

- Note that :

$$I_o = I_2 + I_L$$
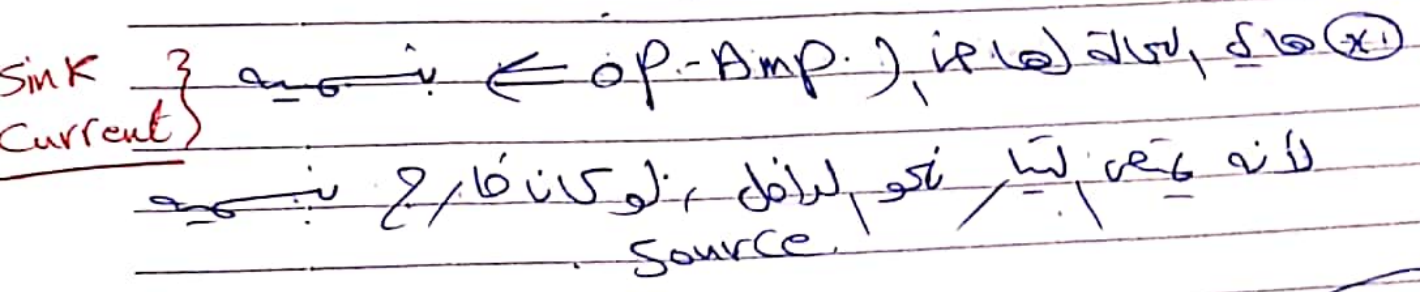
$$I_o = 2\sin\omega t + 1\sin\omega t = 3\sin\omega t \text{ mA}$$





qu

"20 8, 8, 100"

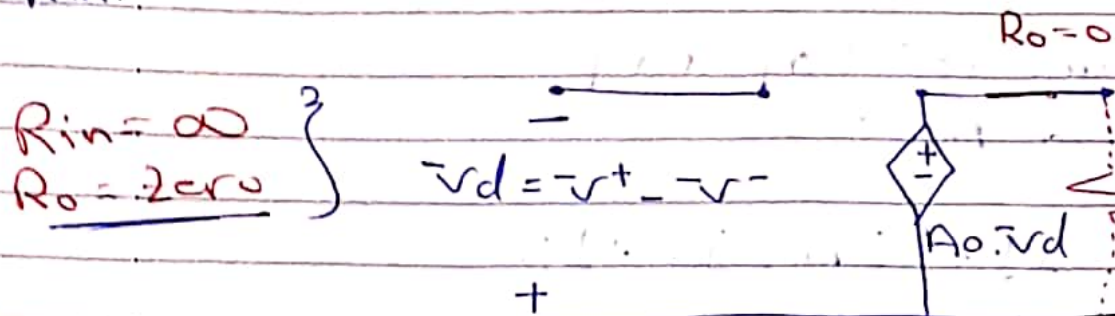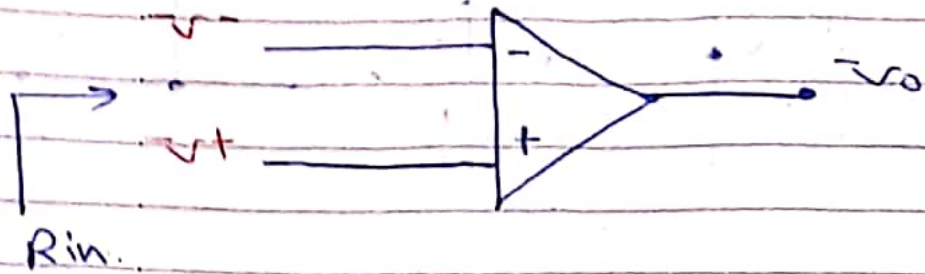(X) For ideal op-Amp:


$R_i = \infty, R_o = \text{zero}, A_o = \infty, B.W = \infty$



$v_o = A_o \cdot v_d \Rightarrow$ Note: v_o is indep on R_L .

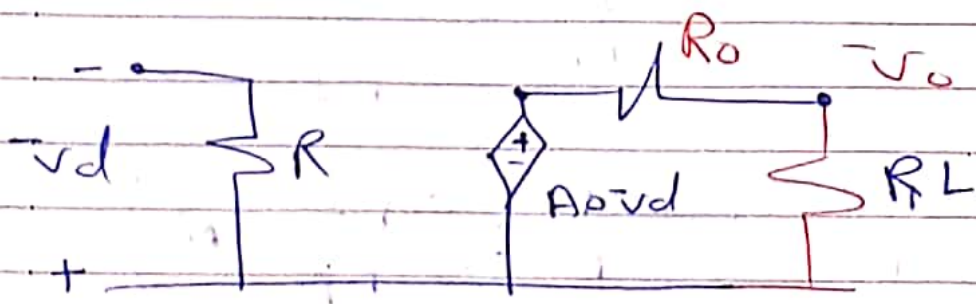(X) For Non-ideal op-Amp:

$R_i \neq \infty, R_o \neq \text{zero}, A_o \neq \infty, B.W \neq \infty$




$R_L \propto v_o, v_o$ depends on R_L

$v_o = A_o v_d \frac{R_L}{R_L + R_o}$, $v_d = v^+ - v^-$

95

نقطة تقاطع، I_{in} (A-v) , I_{out} (A-v) / R_L
 R_L, I_L

② Inverting summing Amp: R_f

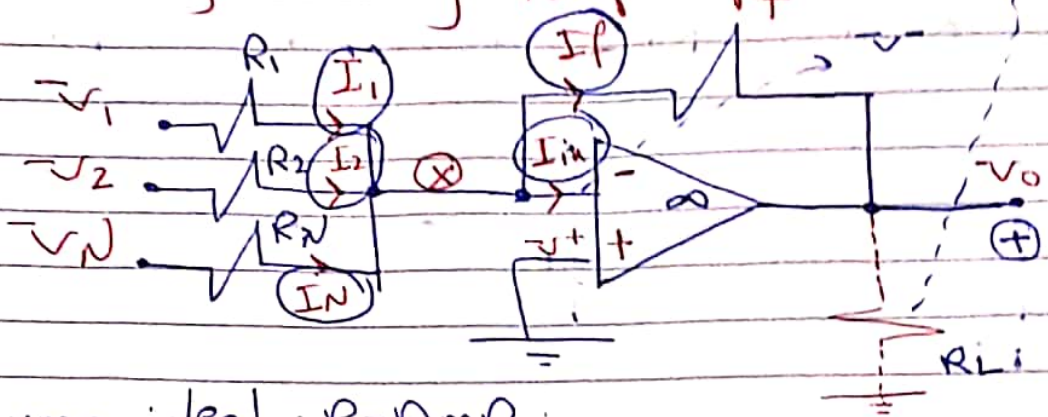

* Assume ideal op-Amp:
 KCL @ Node x:

$$I_1 + I_2 + I_N = I_f + I_{in}$$

$$\frac{v_1 - v_x}{R_1} + \frac{v_2 - v_x}{R_2} + \dots + \frac{v_N - v_x}{R_N} = \frac{v_x - v_o}{R_f} + I_{in}$$

ideal AMP virtual
 $I_{in} = 0, v_x = v^+ = v^- = 0$

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \dots + \frac{v_N}{R_N} = -\frac{v_o}{R_f}$$

$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_N} v_N \right)$$

For the same amplification factor for each signal choose $R_1 = R_2 = \dots = R_N = R$

then: $v_o = -\frac{R_f}{R} (v_1 + v_2 + \dots + v_N)$

(96)

* Note: $v_1, v_2, v_n \rightarrow$ can be AC or DC.

Ex: ^① Design a cct to procedure $v_o = -(5v_1 + 10v_2)$

$$v_o = -15(v_1 + v_2)$$

② draw volt for each case: if $v_1 = 2\sin\omega t, v_2 = -2$

[Sol:]

$$-(5v_1 + 10v_2) = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2\right)$$

$$\frac{R_f}{R_1} = 5, \quad \frac{R_f}{R_2} = 10 \Rightarrow$$

$$R_f = 5R_1, \quad R_f = 10R_2$$


Let $R_f = 10k\Omega$

هذا يعني ان R1 = 2k و R2 = 1k
و اننا نكون قد حصلنا على الحل.


then $R_1 = 2k\Omega, R_2 = 1k\Omega$.

$$v_o = -(5 \times 2\sin\omega t + 10 \times -2)$$

$$v_o = 20 - 10\sin\omega t$$

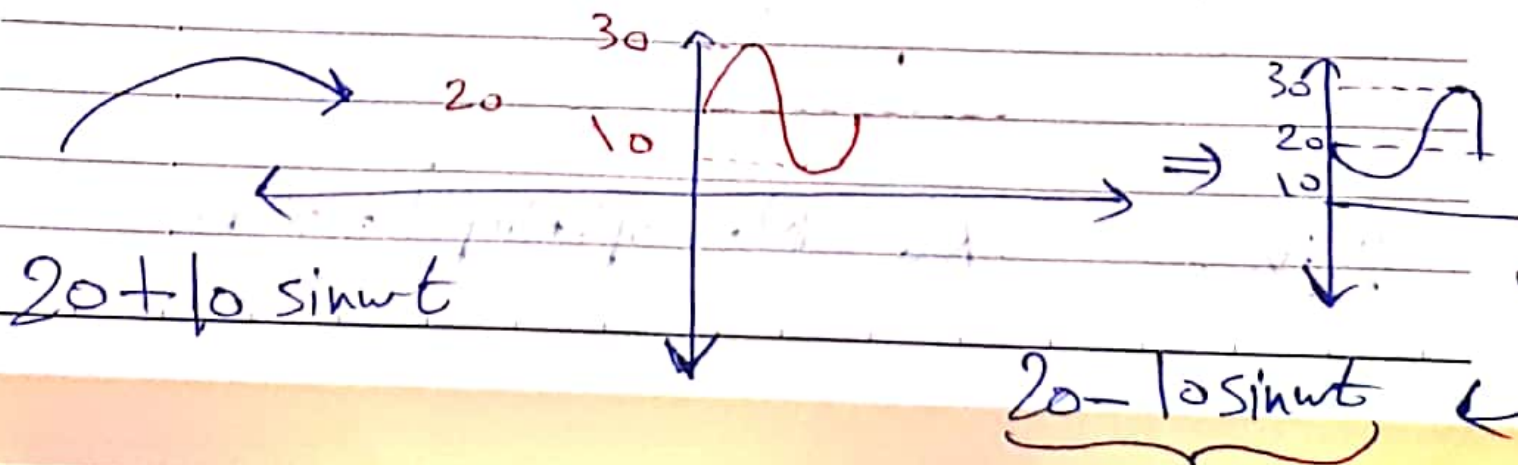

(97) 3 Non-Inverting Amp.

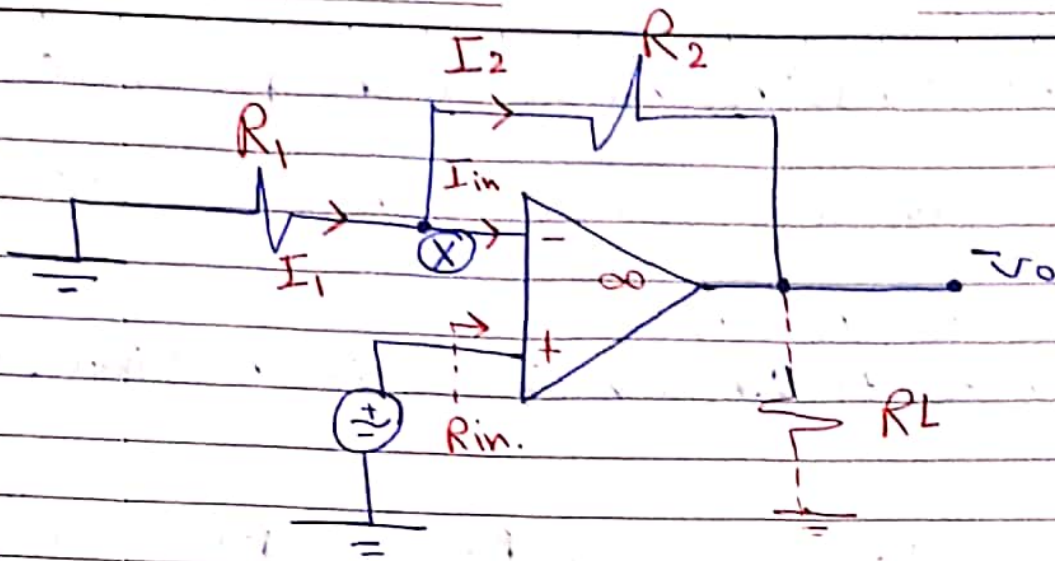

$$I_1 = I_{in} + I_2$$

$$\frac{-v_x}{R_1} = \frac{-v_o - v_x}{R_2} + I_{in} \Rightarrow I_{in} = \text{zero}$$

$v_x = v^+ = v^- = v_i$

$$\frac{-v_x}{R_1} = \frac{-v_o}{R_2} - \frac{v_x}{R_2}$$

(virtual short) ←


$$-\frac{v_i}{R_1} = \frac{-v_o}{R_2} - \frac{v_i}{R_2}$$

$$\frac{-v_o}{R_2} = -v_i \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{v_o}{v_i} = A_v = 1 + \frac{R_2}{R_1}$$

$$R_{in} = \infty, R_o = R_o (\text{op-amp}) = \text{zero}$$

0/8

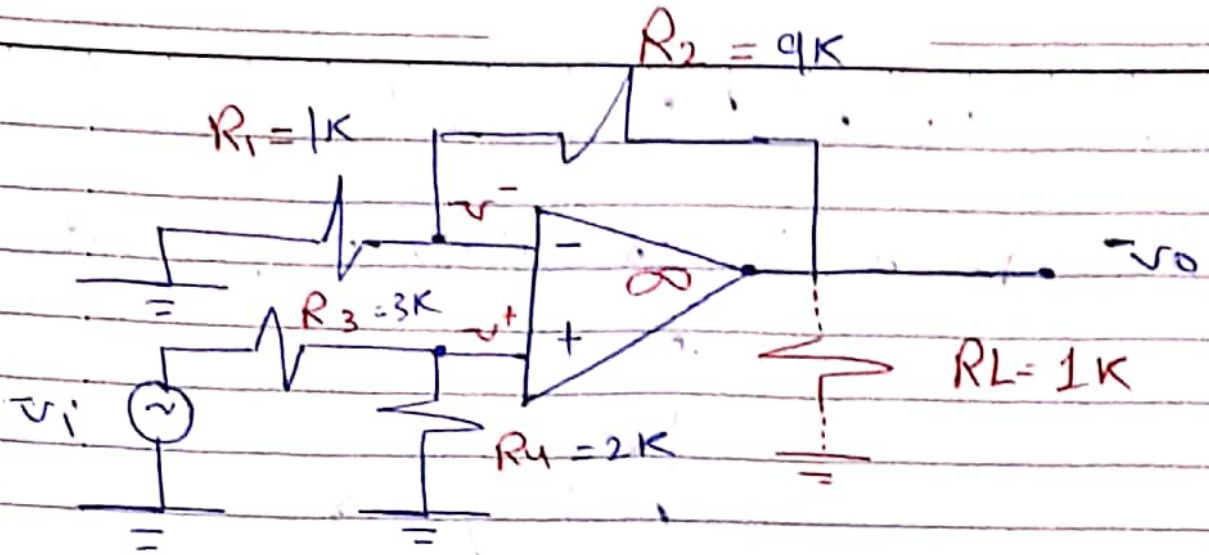

$$v_o = v_i = v^+ \quad \text{at } v_i \text{ is}$$

$$v_o = \left(1 + \frac{R_2}{R_1} \right) \cdot v^+$$

$$v^+ = \frac{v_i \times R_4}{R_3 + R_4}$$

$$v_o = \left(1 + \frac{R_2}{R_1} \right) \times v_i \times \frac{R_4}{R_3 + R_4}$$


$$\frac{v_o}{v_i} = A_v = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right)$$

- if $v_i = 0,5 \sin(\omega t)$, Calculate and draw $v_o(t)$, A_v .

9a

$$A_v = (1 + 9) \left(\frac{2}{5} \right) = 4$$
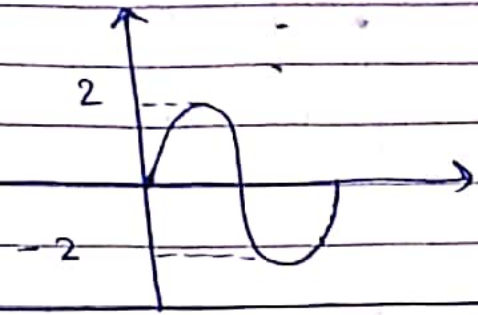
$$v_o = A_v \times v_i = 4 \times 0.5 \sin \omega t = \boxed{2 \sin \omega t \text{ V}}$$




$$v^+ = v^- = v_i \times \frac{R_4}{R_3 + R_4} \quad \text{no load } (\otimes)$$

$$= \frac{0.5 \sin \omega t \times 2k}{5k} = \boxed{0.2 \sin \omega t \text{ V}}$$

$v_o > v^+ \Rightarrow I_2$
 $v^+ < v_o \Rightarrow$
 (Arrows and handwritten notes indicating current flow directions)

Handwritten notes in Arabic script explaining the relationship between the output voltage and the non-inverting input voltage, and the resulting current flow.

Source
 Currents
 of -Amp

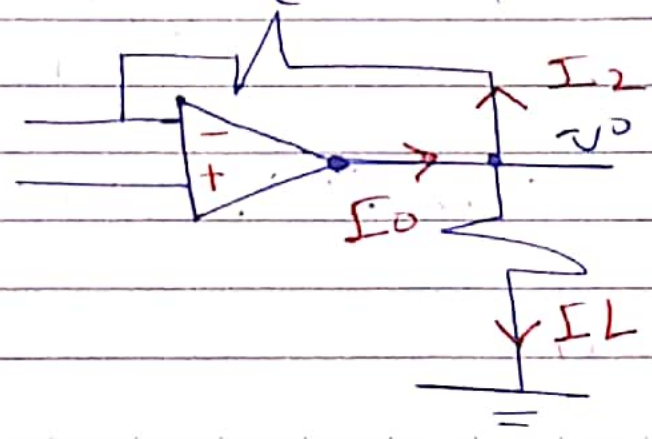

100

$$I_L = \frac{V_o}{R_L} = \frac{2 \sin \omega t}{1 \text{ k}} = 2 \sin \omega t \text{ mA}$$

$$I_2 = \frac{V_o - \text{zero}}{R_1 + R_2} \text{ OR } \frac{V_o - v^-}{R_2}$$

$$I_2 = \frac{\sin \omega t (2 - 0,2)}{9 \text{ k}} = \boxed{0,2 \sin \omega t \text{ mA}}$$

$$I_o = I_L + I_2 = \boxed{2,2 \sin \omega t \text{ mA}}$$


OP-Amp (source current).

101

" 21 6/5/20"

4] Voltage follower (Buffer):

-> special case of non-inverting Amp.

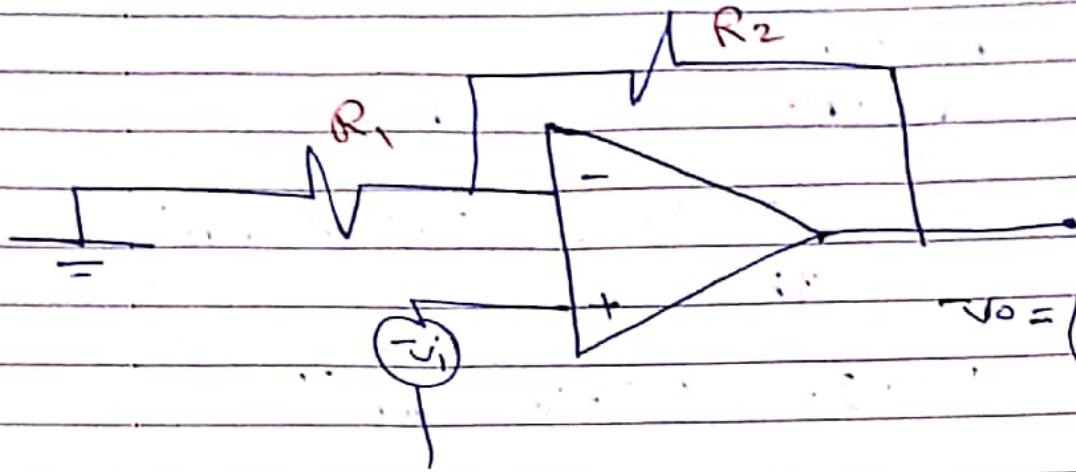


$$v_o = \left(1 + \frac{R_2}{R_1}\right) v_i$$

OR if $R_1 = \infty$

$$v_o = v_i$$

OR if R_2 is short

$$v_o = v_i$$

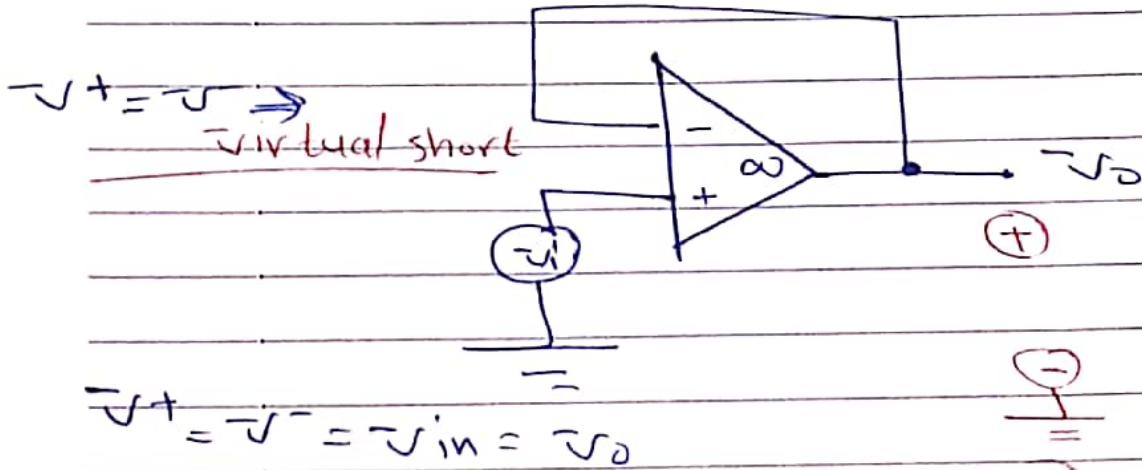


$$v^+ = v^- = v_{in} = v_o$$

$$A_v = 1 \quad R_{in} = \infty, \quad R_o = \text{zero}$$

$\phi = \text{zero}$, Ideal voltage follower.

(*) S (Voltage follower) $v_i = v_o$ $i_i \approx 0$

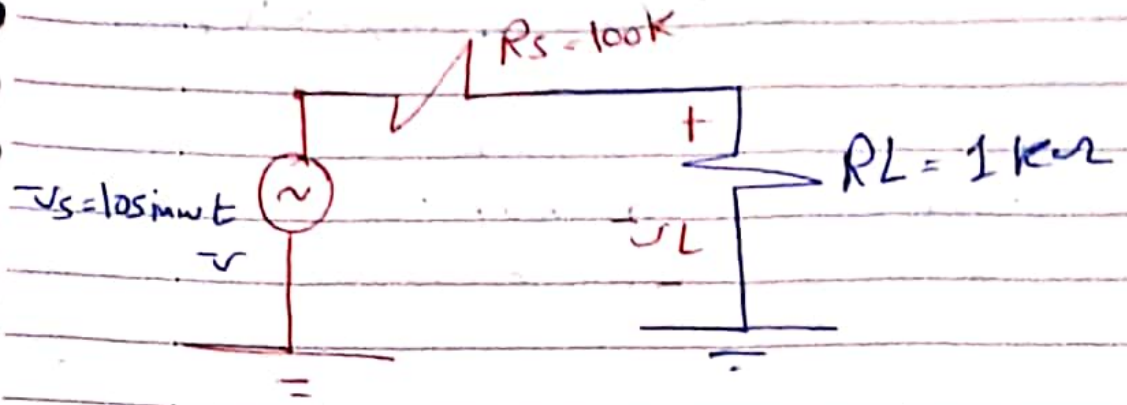It is used to minimize loading effect without Buffer.




(1) Without Buffer:

$$v_L = \frac{v_s \times R_L}{R_s + R_L} = 0.1 \sin \omega t$$

sever loading effect

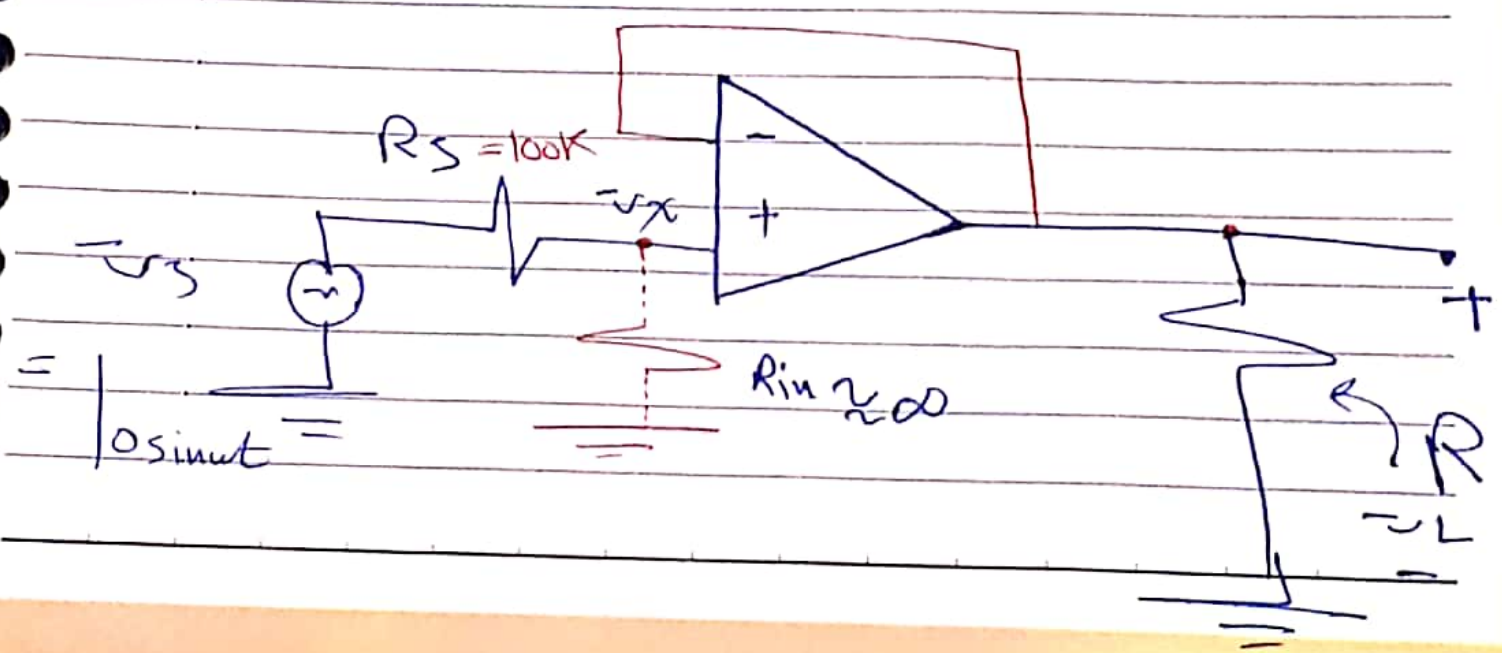- to minimize loading effect a buffer can be used:



103

$$\bar{v}_x = \bar{v}_s \frac{R_{in}}{R_s + R_{in}} \Rightarrow \bar{v}_x = \frac{\bar{v}_s}{1 + \frac{R_s}{R_{in}}}$$

$R_{in} \rightarrow \infty$

$\bar{v}_x = \bar{v}_s \Rightarrow$ فان هذا هو الهدف لنا انه
نقل التاثير من \bar{v}_i الى \bar{v}_o

$$\bar{v}_s = \bar{v}_x = \bar{v}_+ = \bar{v}_- = \bar{v}_L$$

$$\bar{v}_L = \bar{v}_s = 10 \sin \omega t \text{ V}$$

No Loading effect.


voltage follower

الاولى فقط، اتفينا على ما بيننا \bar{v}_o

الاولى هبة، انه $R_{in} = \infty$ لثانية هبة، انه

$$\bar{v}_i = \bar{v}_o = \boxed{} \quad A\bar{v} = 1$$


5) Difference Amp:

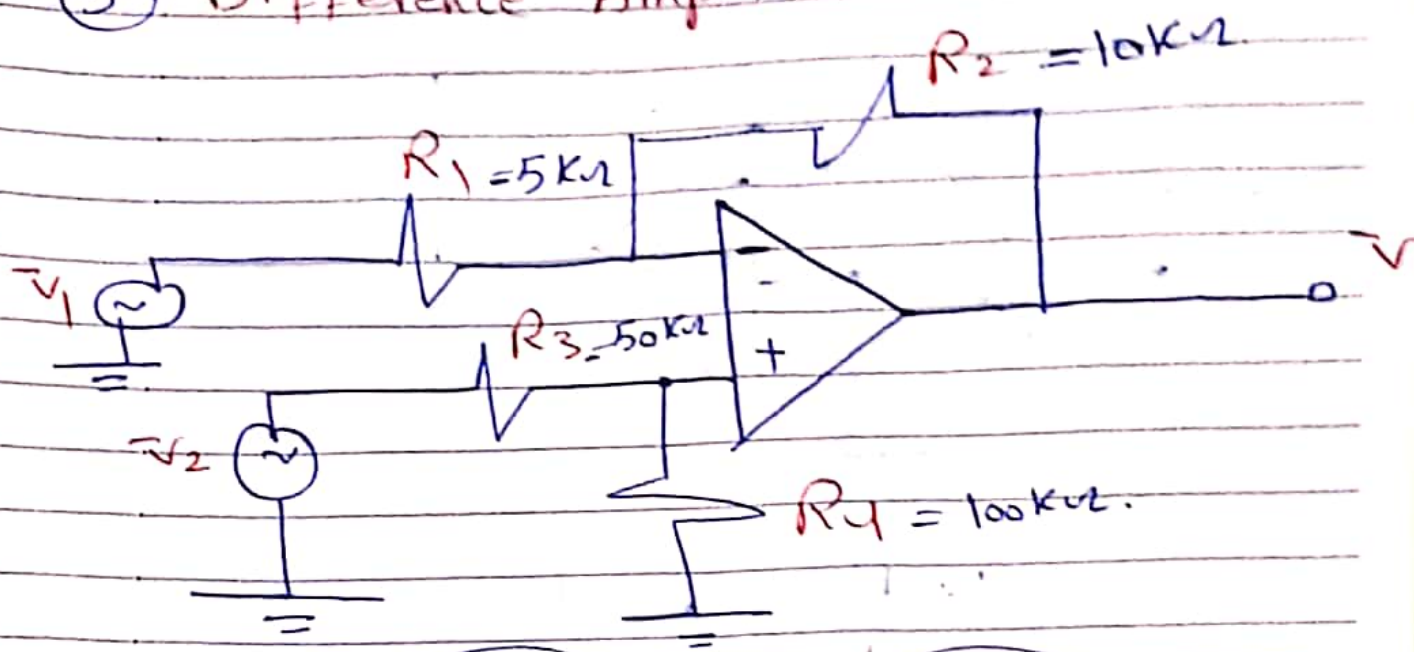

$$v_o = A_d (v_2 - v_1)$$
 where A_d is the differential gain.

* Use Superposition:

1) effect of v_1 : ($v_2 = \text{Zero}$)

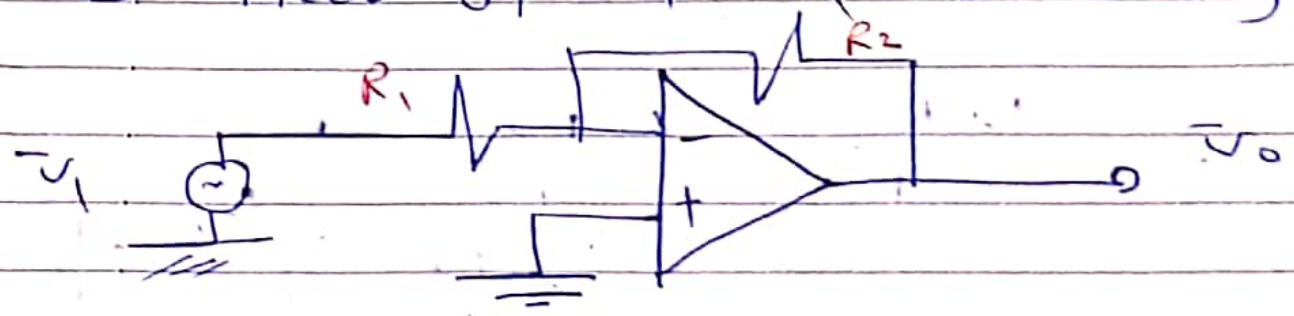


"Inverting Amp" v_1 \rightarrow v_o

$$v_o = -\frac{R_2}{R_1} v_1$$

105

Effect of v_2 : ($v_1 = 0$)

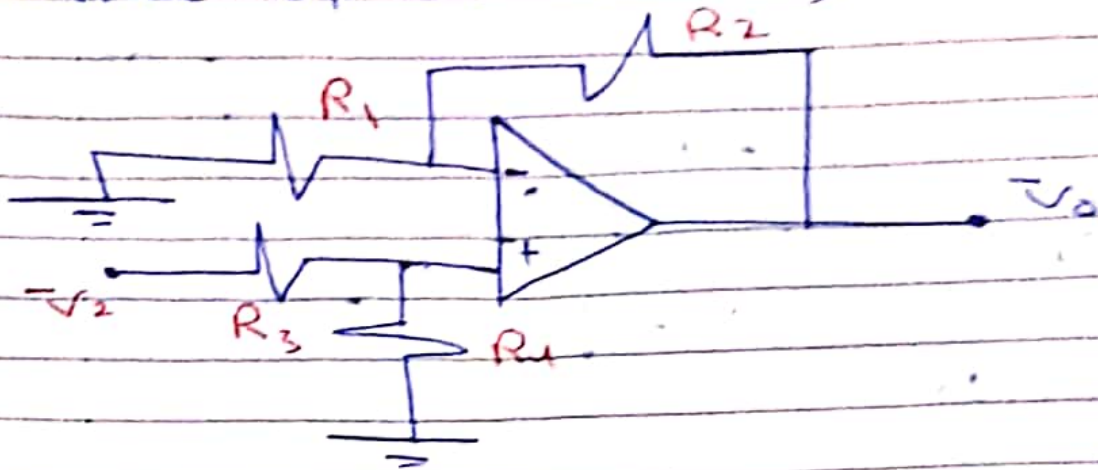

$$v_{o2} = \left(1 + \frac{R_2}{R_1}\right) v_t$$

$$v_t = \frac{v_2 \cdot R_4}{R_3 + R_4}$$

$$v_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{v_2 \cdot R_4}{R_3 + R_4}\right)$$

$$v_o = v_{o1} + v_{o2}$$

$$= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{\frac{R_4}{R_3}}{1 + \frac{R_4}{R_3}}\right) (v_2) = \frac{R_2}{R_1} v_1 +$$

Choose $\frac{R_2}{R_1} = \frac{R_4}{R_3}$

$$\text{Choose } \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

(106)

$$\text{then } v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{\frac{R_2}{R_1}}{1 + \frac{R_2}{R_1}}\right) v_2 - \frac{R_2}{R_1} v_1$$

$$v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

$$v_o = \boxed{Ad (v_2 - v_1)}$$

Ad: Differential voltage gain

$$Ad = \frac{v_o}{v_2 - v_1} = \frac{R_2}{R_1}$$

المكسب التفاضلي $\left(\frac{R_4}{R_3} - \frac{R_2}{R_1}\right)$ $\frac{v_2 - v_1}{v_2 - v_1}$

Let $v_1 = 1.5v$, $v_2 = 2v$

$$\text{then } \Rightarrow v_o = \left(\frac{R_2}{R_1} (v_2 - v_1)\right) = \frac{10}{5} (2 - 1.5) = \boxed{1v}$$


Let $R_2 = 8k\Omega$, $R_1 = 4k\Omega$

$R_4 = 3k\Omega$, $R_3 = 1k\Omega$

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{\frac{R_4}{R_3}}{1 + \frac{R_4}{R_3}}\right) v_2 - \frac{R_2}{R_1} v_1$$

$$v_o = \boxed{1.5v}$$

107

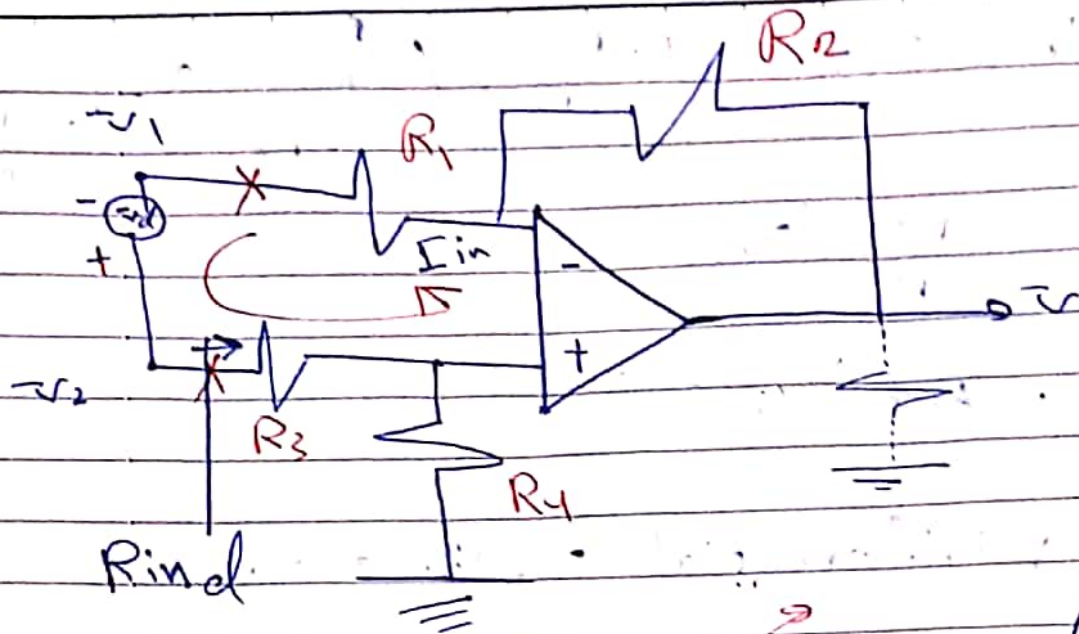

R-IL: $-v_d + (v^+ - v^-) + I_{in}(R_1 + R_3) = 0$

$\frac{v_d}{I_i} = R_3 + R_1 = R_{in}$

Q) Design an diff Amp to have $A_d = 50$ and $R_{in} = 20 \text{ k}\Omega$.

Sol: $R_{in} = R_1 + R_3$

Let $\frac{R_2}{R_1} = \frac{R_4}{R_3} \Rightarrow$ and

$\Rightarrow 20 \text{ k} = 2R_1 = 2R_3$ $R_2 = R_4$
 $R_1 = R_3$

$R_1 = R_3 = 10 \text{ k}\Omega$

108]


$$A_d = \frac{R_2}{R_1} \Rightarrow 50 = \frac{R_2}{10K} \rightarrow$$

$$R_2 = R_4 = 500K\Omega$$

② For $v_2 = 2 \sin \omega t$, $v_1 = 3 \sin \omega t$
Calculate and draw $v_o(t)$.

Sol: $v_o(t) = A_d (v_2 - v_1)$
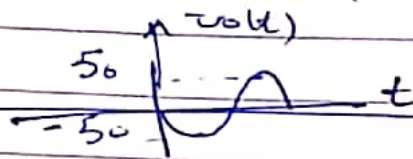
$$v_o(t) = 50 (-\sin \omega t) = \boxed{-50 \sin \omega t}$$



Se(oune) | $v_o(t)$

Putami


109

① فائز / 5 ip 50

* Instrumentation Amplifier:

- 1] A_1 and A_2 (Non-Inverting Amplifier)
- 2] $A_3 \Rightarrow$ Differential Amplifier,

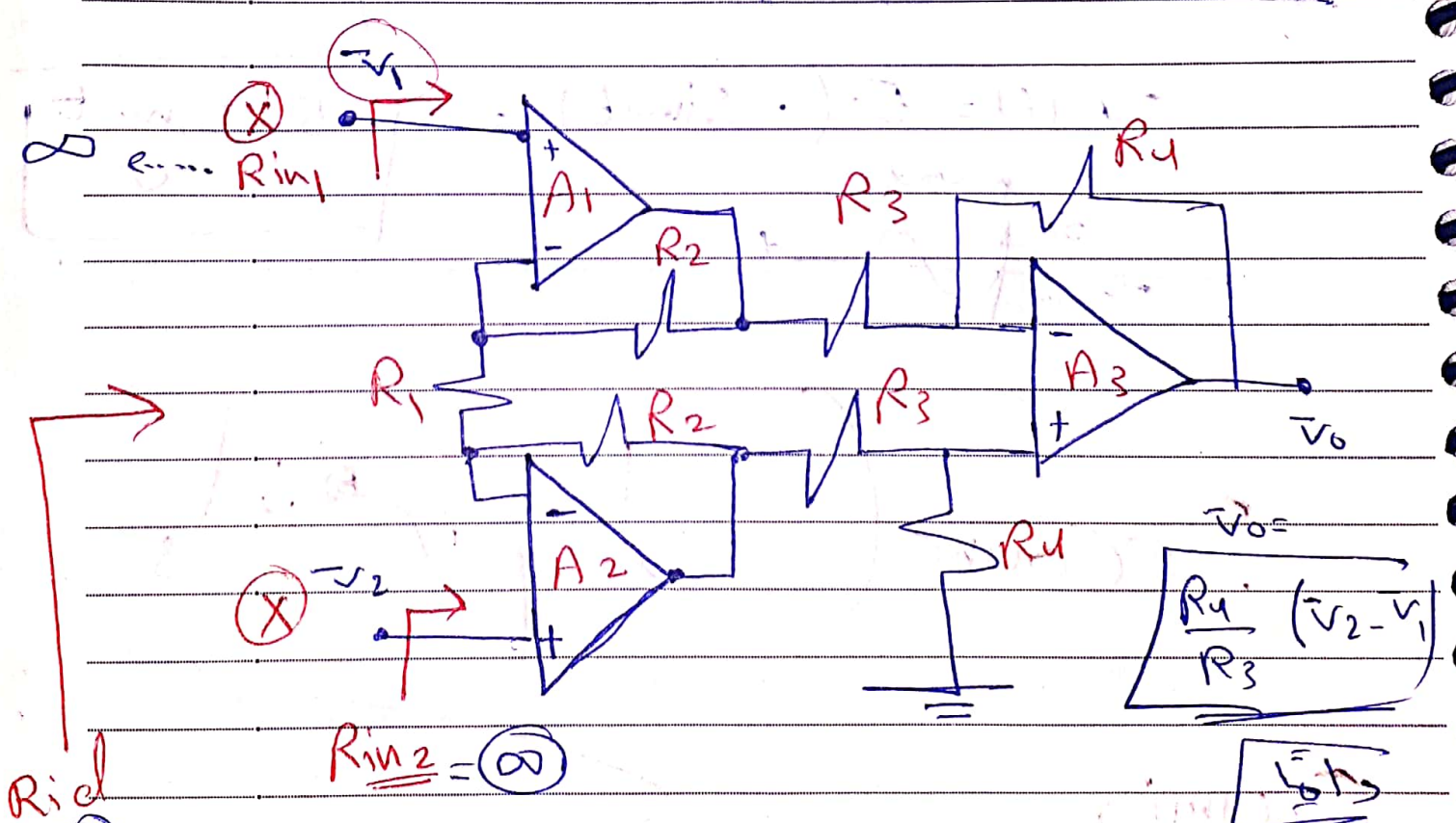* إذا كان لدينا قوتان V_1 و V_2 ولدينا R_{in} و R_1 و R_2 و R_3 و R_4 و A_1 و A_2 و A_3 فإننا نحصل على V_0 وهو $V_0 = \frac{R_4}{R_3} (V_2 - V_1)$ وهذا هو V_{diff} و R_{in} هو $R_{in} = \infty$ و R_{id} هو $R_{id} = \infty$ و A_{diff} هو $A_{diff} = \frac{V_0}{V_2 - V_1}$ و V_0 هو $V_0 = \frac{R_4}{R_3} (V_2 - V_1)$



$$A_{diff} = \frac{V_0}{V_2 - V_1}$$

* Properties of Instrument Amplifier:

* It is used to achieve:


1] very high R_{in} .

2] High gain (Adjustable and single element dependent gain). (Advantage)

Using reasonable Resistance values (k Ω).

* Using super position:

- For A_1 ; v_{o1} ?

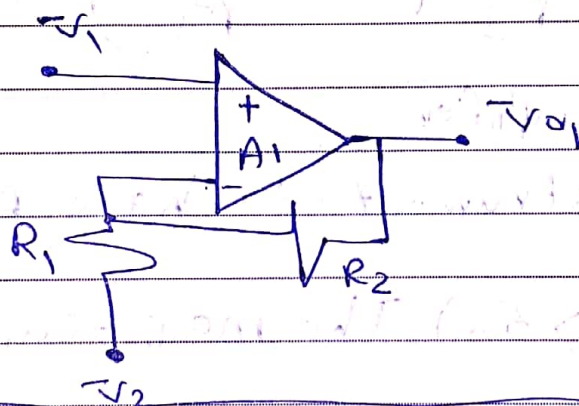


(i) effect of v_1 ($v_2=0$)

(Non-Inverting)

$$v_{o1}' = \left(1 + \frac{R_2}{R_1}\right) v_1$$

(ii) effect of v_2 ($v_1=0$):

$$v_{o1}'' = -\frac{R_2}{R_1} v_2$$

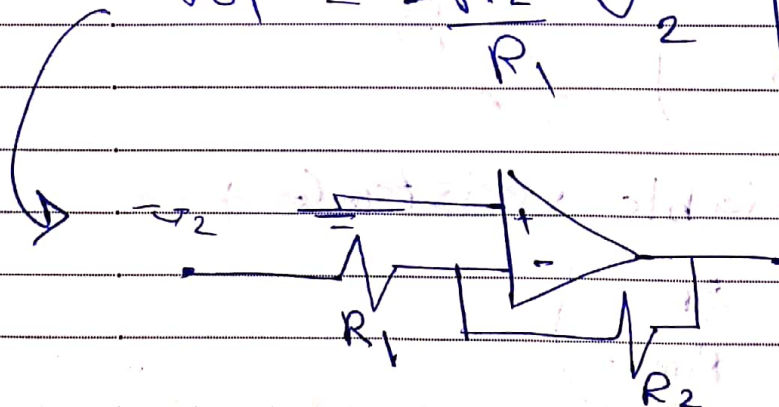

$$v_{o1} = \left(1 + \frac{R_2}{R_1}\right) v_1 - \frac{R_2}{R_1} v_2$$

III

(x) \rightarrow $\frac{R_2}{R_1} v_1$ \leftarrow $\frac{R_2}{R_1} v_2$

$$v_{o2} = \left(1 + \frac{R_2}{R_1}\right) v_2 - \frac{R_2}{R_1} v_1$$

$$v_o = \frac{R_4}{R_3} \left[\left(1 + \frac{R_2}{R_1}\right) v_2 - \frac{R_2}{R_1} v_1 - \left[\left(1 + \frac{R_2}{R_1}\right) v_1 - \frac{R_2}{R_1} v_2 \right] \right]$$

\Leftarrow $\frac{v_o}{v_2 - v_1}$ \rightarrow A_d

$$\frac{v_o}{v_2 - v_1} = A_d I = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right) \text{ متغيرة}$$

Amplifier

Ex: Design an Instrument to have A_d ranging from (5 \rightarrow 500), The max available resistance 100k Ω .

$$\left. \begin{aligned} A_d(\min) &= 5 \\ A_d(\max) &= 500 \end{aligned} \right\} A_d$$


Let R_1 variable resistance :

$$A_{d \min} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_{1 \max}}\right)$$

$$A_{d \max} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_{1 \min}}\right)$$

112

(0 → 100) ...

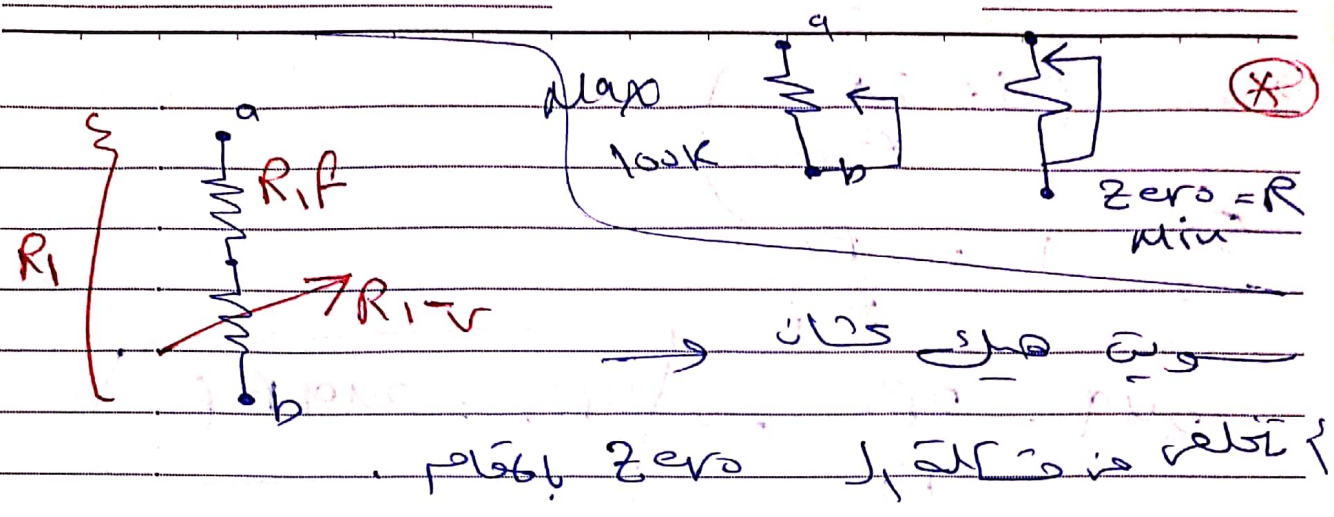

$$R_1 = R_{1f} + R_{1v}$$

* Choose a potentiometer of 100k

Let the gain of $A_3 = 2 = \frac{R_4}{R_3}$

$$5 = 2 \left(1 + \frac{2R_2}{R_{1max}} \right)$$

$$2R_2 = 1,5 R_{1max} \Rightarrow 2R_2 = 1,5 (100 + R_{1f})$$

$$2R_2 = 150 + 1,5 R_{1f}$$

$$R_{1max} = 100k + R_{1f}$$

$$R_{1min} = R_{1f}$$

113

$$500 = 2 \left(1 + \frac{2R_2}{R_{\text{in}}} \right)$$

$$\frac{500}{2} - 1 = \frac{2R_2}{R_f}$$

$$249 = \frac{2R_2}{R_f} \Rightarrow \boxed{2R_2 = 249 R_f}$$

$$150 + 1,5 R_f = 249 R_f$$

$$\boxed{0,6 \text{ k}\Omega = R_f}$$


$$\boxed{R_2 = 75 \text{ k}\Omega}$$

$$\frac{R_4}{R_3} = 2 \Rightarrow \text{Let } R_3 = 1 \text{ k}\Omega$$
$$R_4 = 2 \text{ k}\Omega$$

114

سيفه (2) سيطه

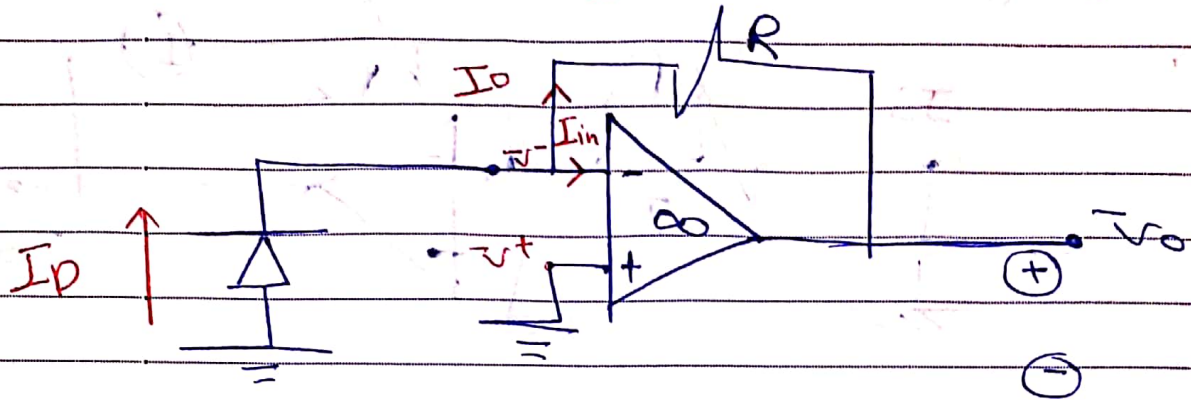[7] Current-to-voltage Converter: (I-to-v)



$$I_D = I_0 + I_{in}$$

$$I_D = \frac{v^- - v_0}{R} + I_{in}$$

but $I_{in} = 0$
 $v^- = v^+ = 0$ } ideal op-amp }

$$I_D = \frac{-v_0}{R} \Rightarrow \boxed{v_0 = -I_D \cdot R}$$

I_D الجهد الصافي $\leftarrow v_0$ و I_D


For $R = 5k\Omega \Rightarrow$

I_D (mA)	v_0 (v)
1	-5
3	-15

115

(V-to-I)

8] Voltage-to-Current Converter:

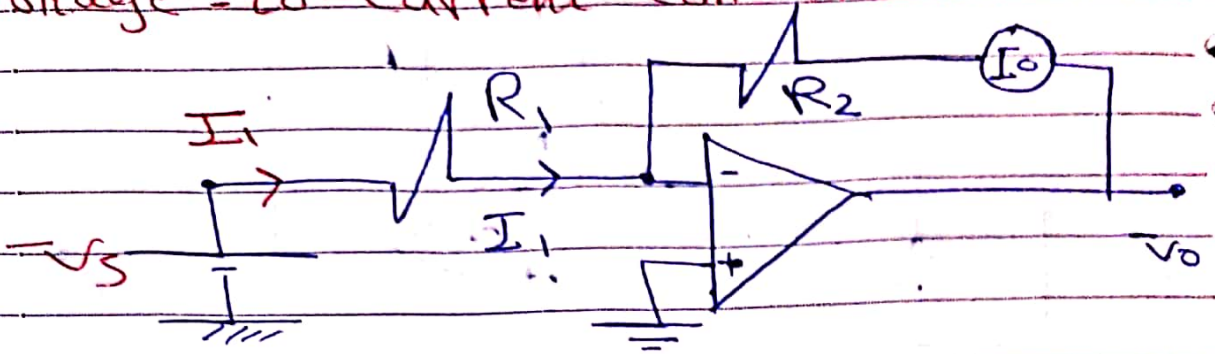

$$I_1 = I_{in} + I_o \Rightarrow$$

$$\frac{V_s - v^-}{R_1} = I_o \Rightarrow I_o = I_1$$


$$\boxed{\frac{V_s}{R_1} = I_o} \Rightarrow I_o \propto V_s$$

Let $R_1 = 2k\Omega$

V_s	I_o (mA)
2	1
8	4
10	5

116

9] Integrator:

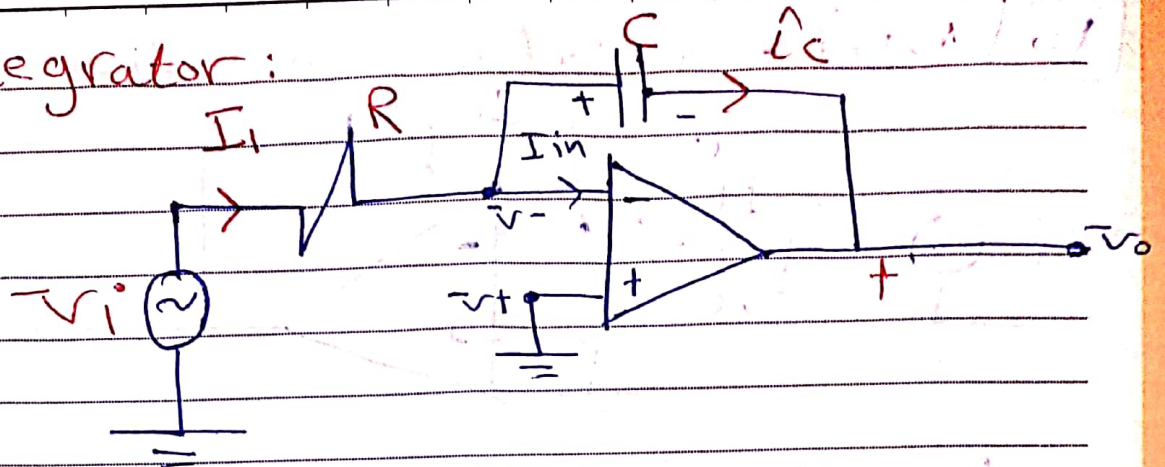

$$I_i = I_c + I_{in} \quad \rightarrow \quad I_{in} = \text{zero}$$

$$\frac{v_i}{R} = C \cdot \frac{dv_c}{dt}$$

$$v_c = -v_o$$


$$\frac{v_i}{R} = -C \cdot \frac{dv_o}{dt}$$

$$-\frac{v_i}{RC} = \frac{dv_o}{dt} \Rightarrow v_o = -\frac{1}{RC} \int v_i dt$$

Note: $I_{in} = 0$, $v^- = v^+ = 0 \rightarrow$ ideal op-Amp.

117

10] Differentiator Amplifier;

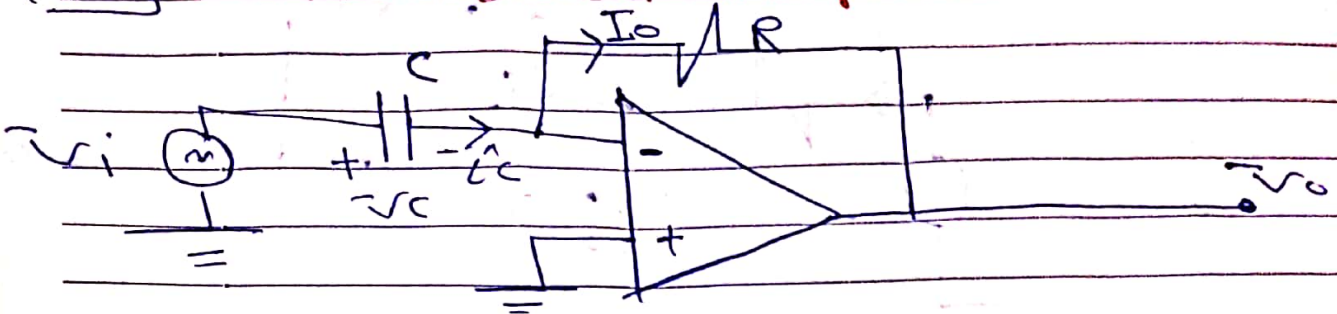

$i_c = I_o$ ----> Since $V_{in} = 0$

$$C \cdot \frac{dv_c}{dt} = -\frac{v_o}{R} \Rightarrow C \cdot \frac{dv_i}{dt} = -\frac{v_o}{R}$$


$$-\frac{v_o}{RC} = \frac{dv_i}{dt} \Rightarrow v_o = -RC \frac{dv_i}{dt}$$

Ex: Draw v_o(t) for v_i shown:

$f = 1 \text{ kHz}$

$R = 1 \text{ k}\Omega$

$C = 1 \mu\text{F}$

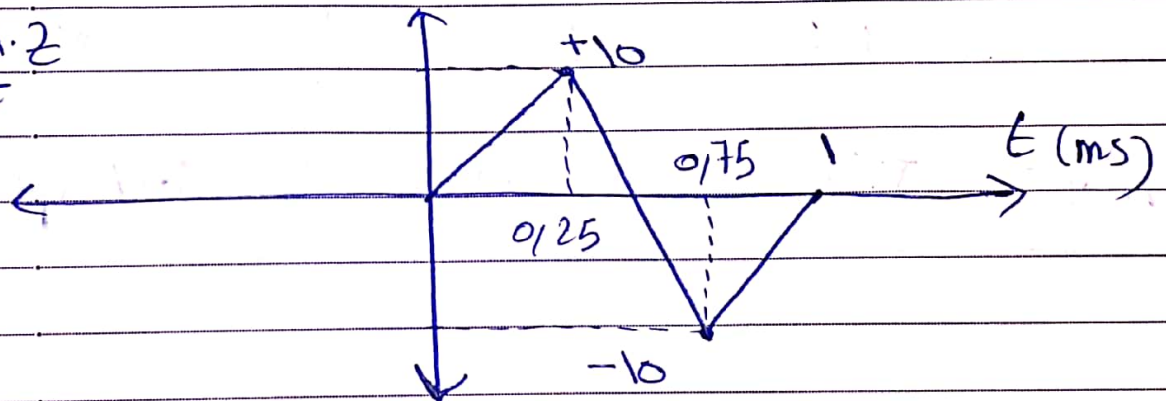

square wave \Rightarrow ramp \Rightarrow \otimes

① for $0 < t < 0,25$


$$v_o = -RC \frac{dv_i}{dt} = -10^3 \times 10^{-6} \times \frac{10}{0,25 \times 10^{-3}} = -40V$$

for $0,25 < t < 0,75$

$$v_o = -RC \cdot \frac{dv_i}{dt} = -10^3 \times 10^{-6} \times \frac{20}{-0,5 \times 10^{-3}} = +40V$$

for $0,75 < t < 1$
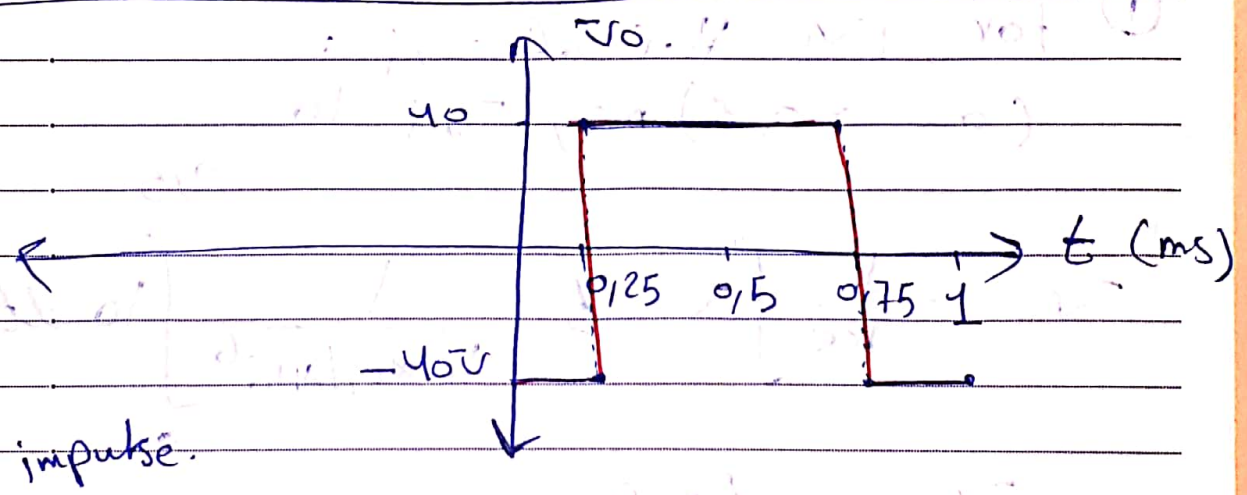
$$v_o = -RC \frac{dv_i}{dt} = -10^3 \times 10^{-6} \times \frac{10}{0,25 \times 10^{-3}} = -40V$$



output ↑ square is Input ↓ ⊗

119


for integration Amp.

Draw $v_o(t)$ for i/p shown in figure:

Let $\rightarrow R = 1k\Omega$

$C = 0.1\mu F$

$f = 1kHz$

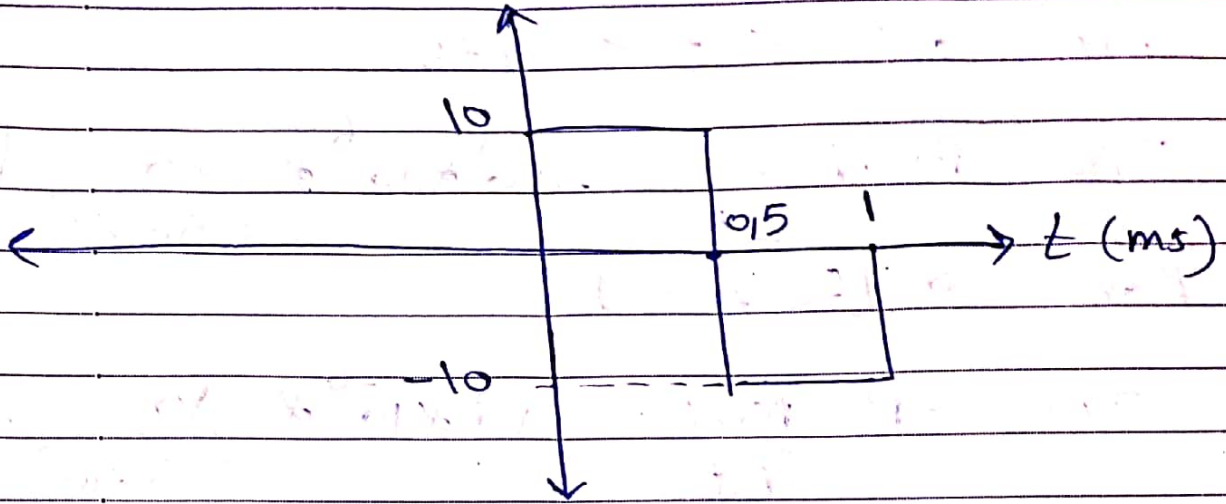

① for +ve H.C of v_i :
(0 \rightarrow 0.5) ms, $v_i = 10$

$$v_o = -\frac{1}{RC} \int v_i dt = \frac{-1}{1k \times 0.1 \times 10^{-6}} \int_0^{0.5} 10 dt$$


$v_o = -50V$

Ramp \iff Square wave 1 volt \rightarrow 1V (*)
wave

120


② for -ve H.C of v_i ($0.15 < t < 1$) ms:
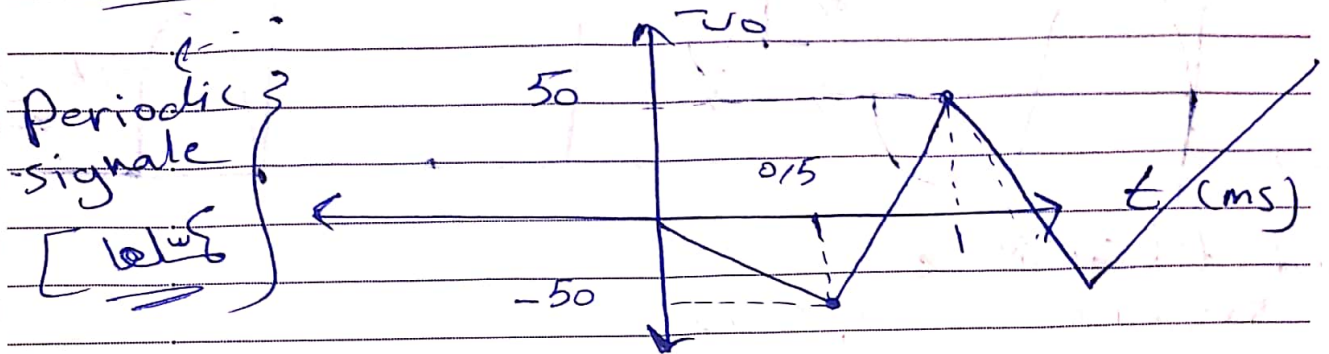
$$v_o = -\frac{1}{10^3 \times 10^{-7}} \int -10 \cdot dt = \boxed{v_o = +50V}$$



⊗ Non-Linear Applications:

□ precision Rectifier:

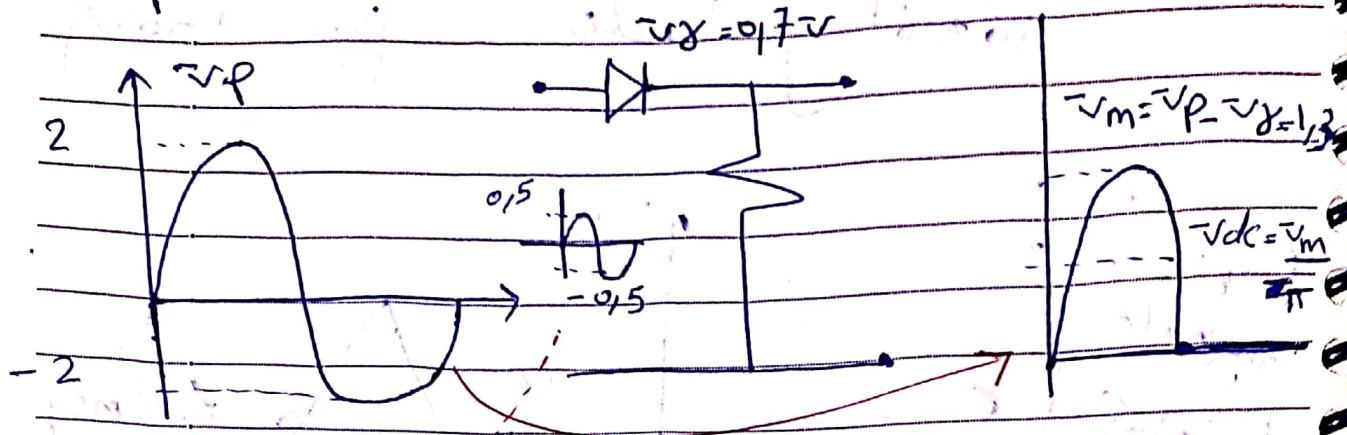

No rectification because $\Rightarrow V_p < V_\gamma$

فانقصر / سو rectification سو لاین $V_p < V_\gamma$



cts, used to rectify signal with $V_p < V_\gamma$.

⊗ فائیل 5، 6 بقودنا لایستناج فائیل 5، 6

الهدف / مقصد (H.W precision Rect) انتر آف

Rectification signal الی سون فائیل V_p V_γ فائیل 5، 6


* H.W precision Rect:

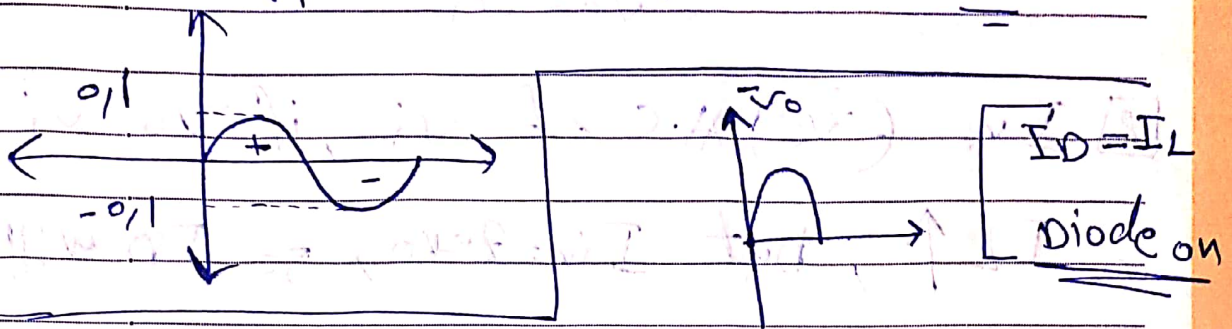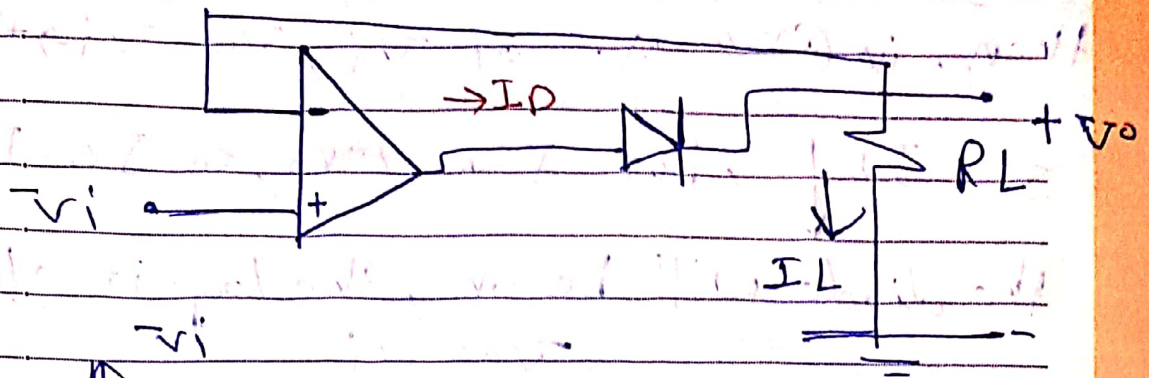

Diode, $I_D = I_L$, $v_o = 0$ for $v_i < 0$

$I_L = I_D = \text{zero}$ \leftarrow Diode Reverse off

$v_o = \text{zero}$ for $v_i < 0$

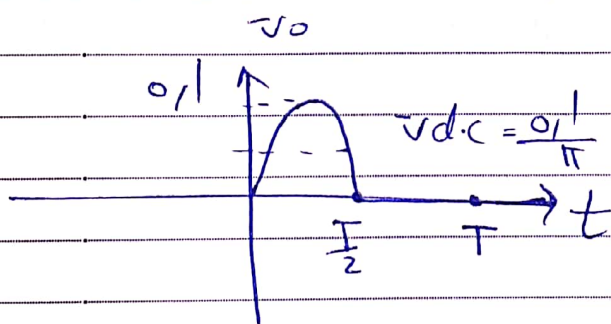

$v_o = v_i \Rightarrow (+ve)$ H.C

123

① Since the ckt is voltage follower ($v_o = v_i$) then, in \oplus ve H.C of v_i , $v_o = v_i \rightarrow +ve$ H.C

- So $I_L \downarrow$, but $I_{in} = \text{zero}$, so $I_D = I_L$

the diode will be on, the loop is closed
 $v_o = v_i$

② In \ominus ve H.C of v_i , if $v_o = v_i$

, $I_L \uparrow$, but $I_{in} = \text{zero}$, so I_D will


be negative, i.e. the diode is off

then the loop is open $v_o = \text{zero}$

1/24

[2] Voltage Comparator:

□ op. Amp is used in open-loop.

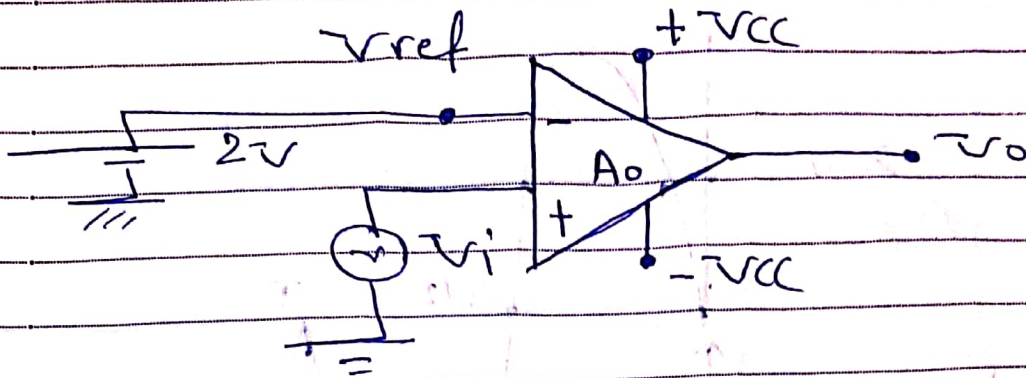

[2] $V_o = \pm V_{CC}$

⊗ In general $V_o = A_o (V^+ - V^-) \Rightarrow A_o \times V_d$

□ when $V^+ > V^- \Rightarrow V_d$ is positive.


But $A_o = \infty$ (ideal op-amp).

$$V_o = +V_{CC}$$

[2] if $V^+ < V^-$, V_d is $(-ve)$

$$V_o = A_o (-V_d) = -V_{CC}$$

① for this figure:

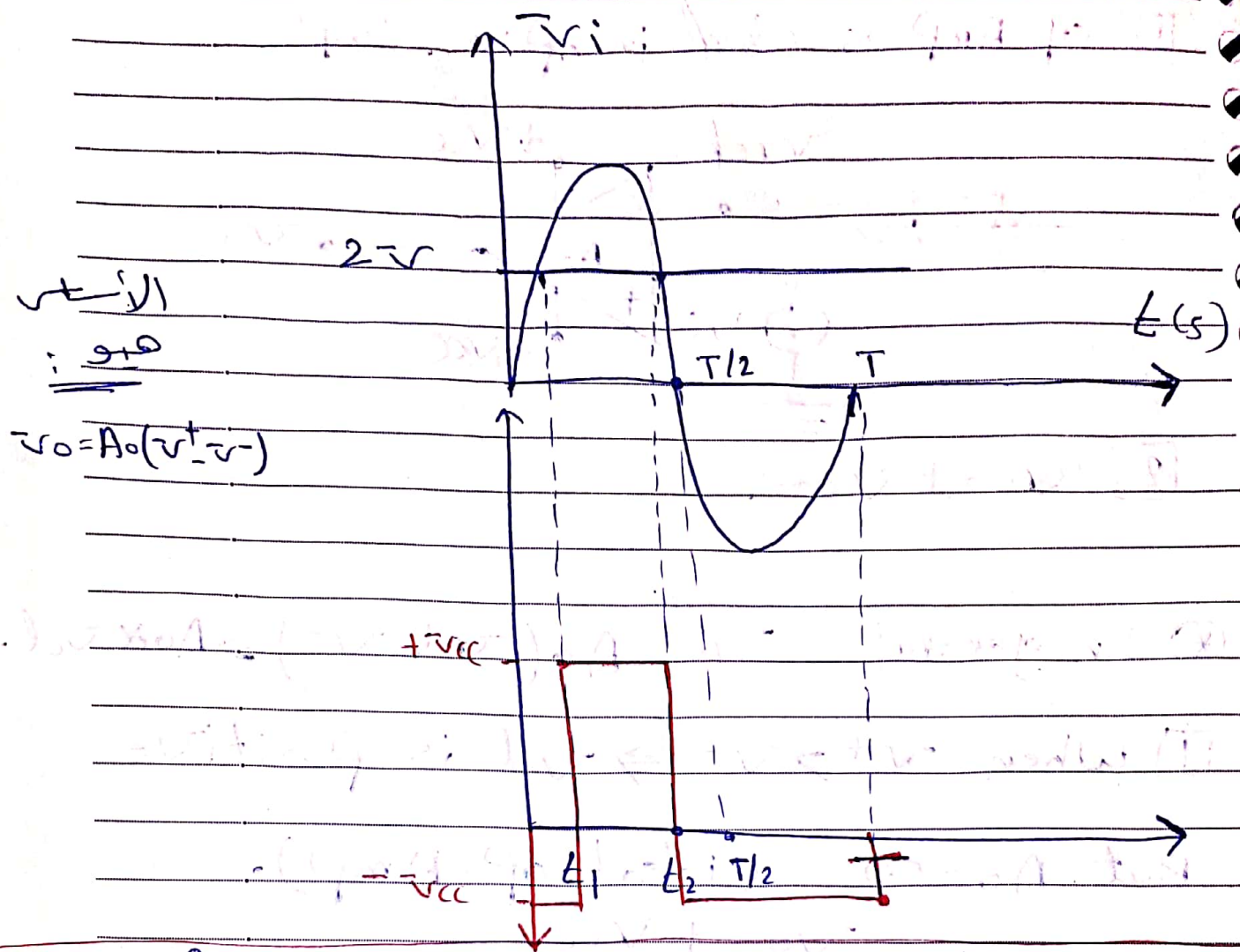

① for $0 < t < t_1 \Rightarrow v^+ > v^-$ then

v_d is $(-ve)$, $\Rightarrow v_o = -V_{cc}$

② for $t_1 < t < t_2 \Rightarrow v^+ > v^-$

v_d is $(+ve)$, $v_o = +V_{cc}$



③ for $t_2 < t < T \Rightarrow v^+ < v^-$, v_d is $(-ve)$

$v_o = -V_{cc}$

if $V_{ref} = \text{zero}$ (V_{dc}) (*)

Symmetrical square wave \Leftarrow applied to is V_{ref} wave.

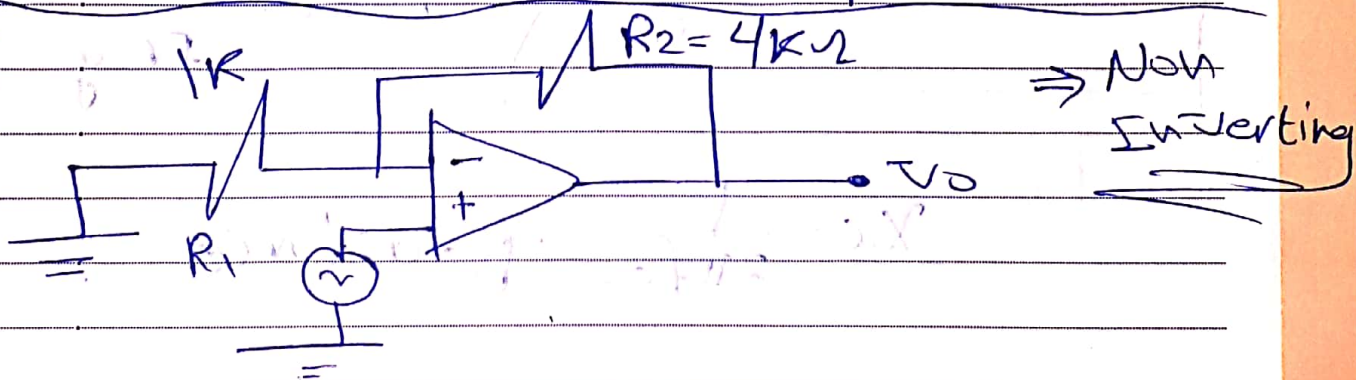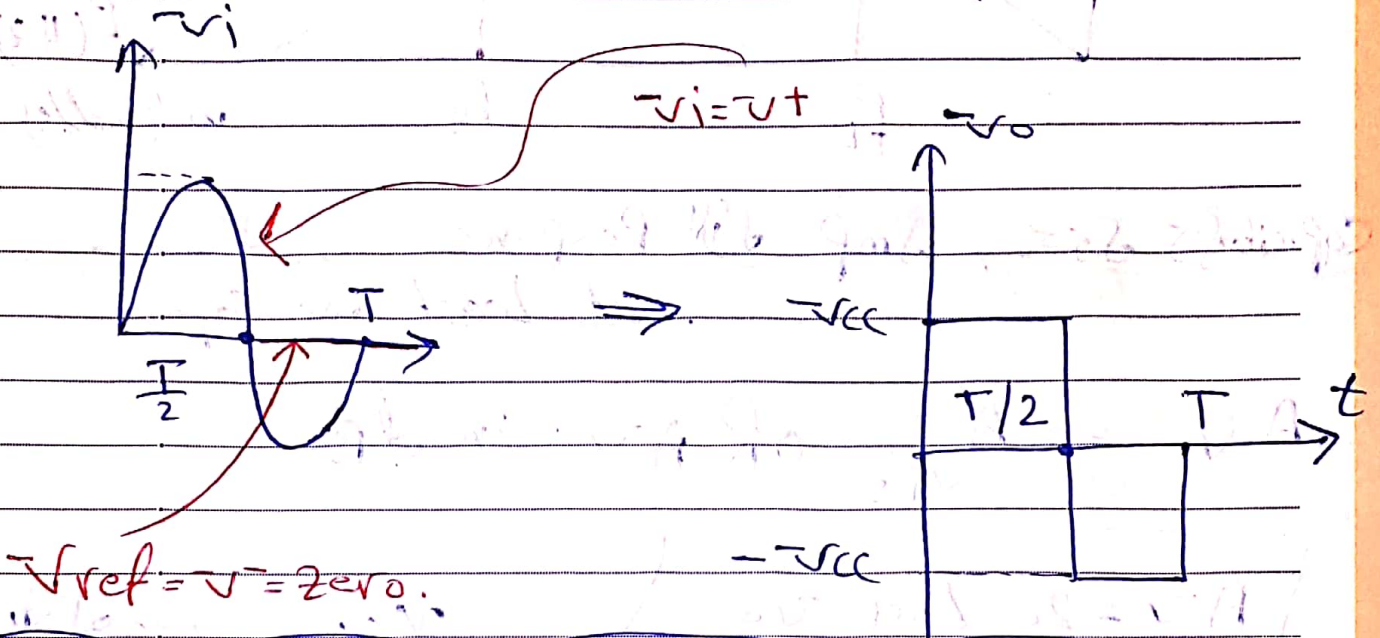When $V_{ref} = \text{zero}$ \Rightarrow the ckt is called "Zero Crossing detector"
 "تحت صفر، تقاطع، موجة مربعة"




$R_2 \rightarrow$ short \Rightarrow voltage follower

$R_2 \rightarrow$ open \Rightarrow voltage Comparator

$V_{ref} = \text{zero}$ (Zero Crossing detector)

* Amplifier frequency Response:

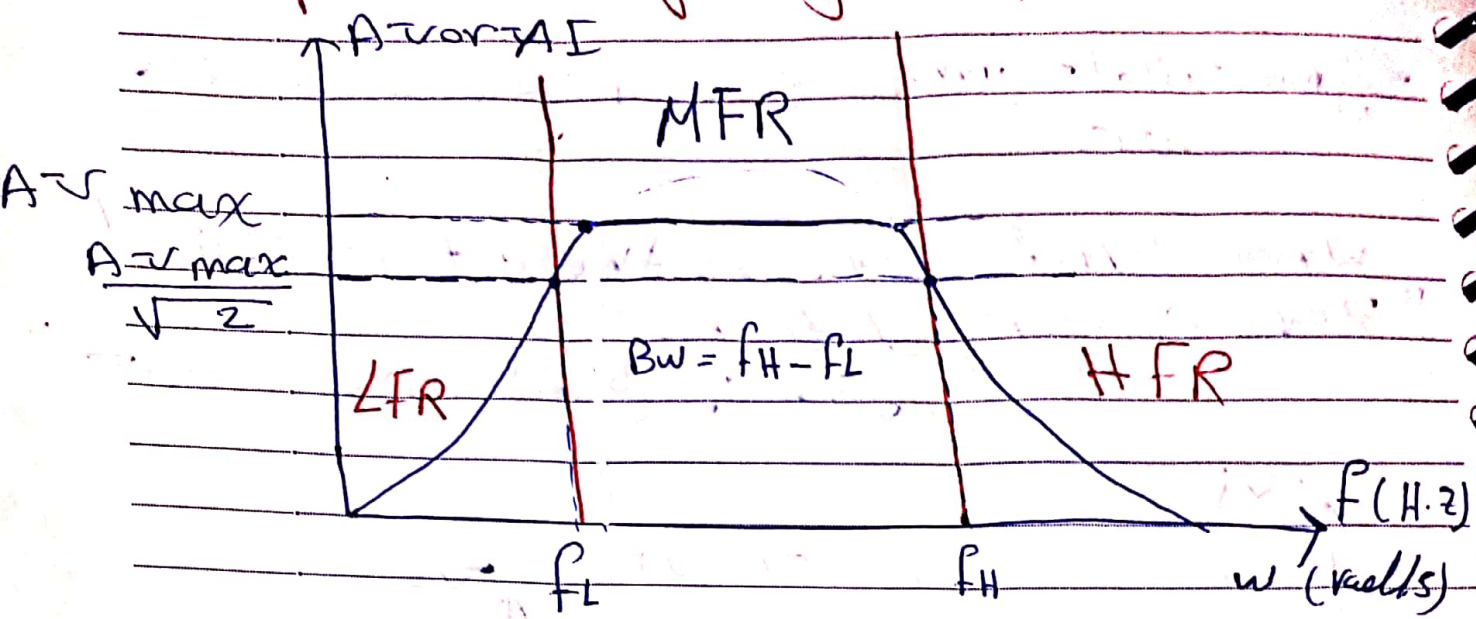

Capacitors سے Amp کی Response, ω \geq at least one caps.


$AV_v \rightarrow \frac{AV}{\sqrt{1+s}} \text{ OR } AV: \text{ in dB}$

$$AV = 20 \log \frac{V_o}{V_s}$$

X_C : ω کی فreq

$X_C = \frac{1}{2\pi f c}$ Reactance

128]

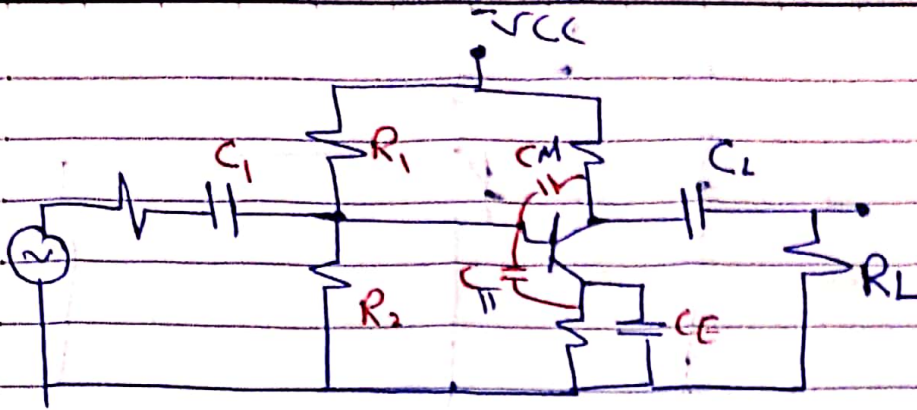

C_1, C_2 : Coupling , C_E : By pass (c).


Let $C = 1 \mu F$

$$X_C = \frac{1}{2\pi f C}$$

f	X_C
10 Hz	$1.7 \text{ K}\Omega$
1 kHz	17Ω
10 kHz	1.7Ω
100 kHz	0.17Ω
1 MHz	0.017Ω


فردی و باقیات
Reactance

لا حظ کیف و کذا
Capacitor
frequency

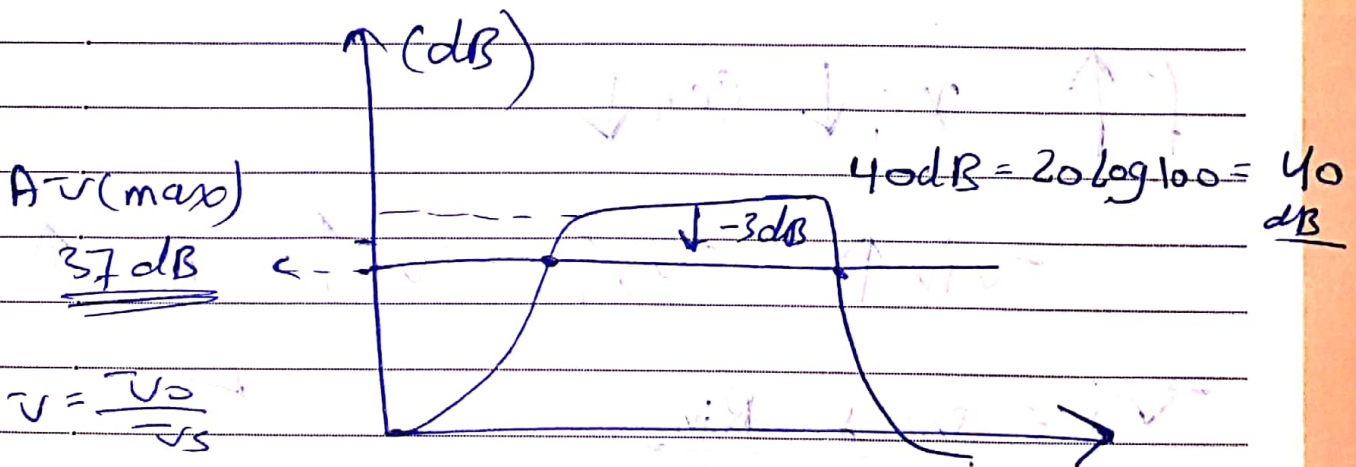

MFR \Rightarrow Region of Max (بجای)


129

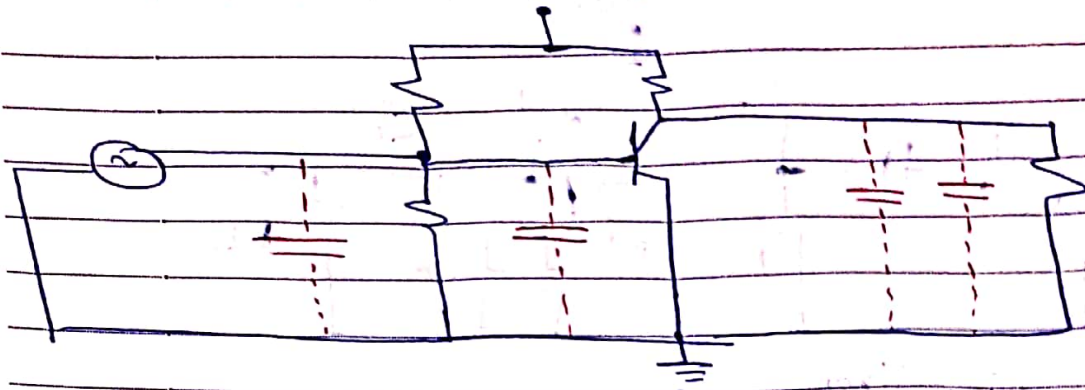

$$A_{v} = -g_m R_L'$$

$$A_{v} = -g_m Z_L$$

$$Z_L = r_c // R_L'$$

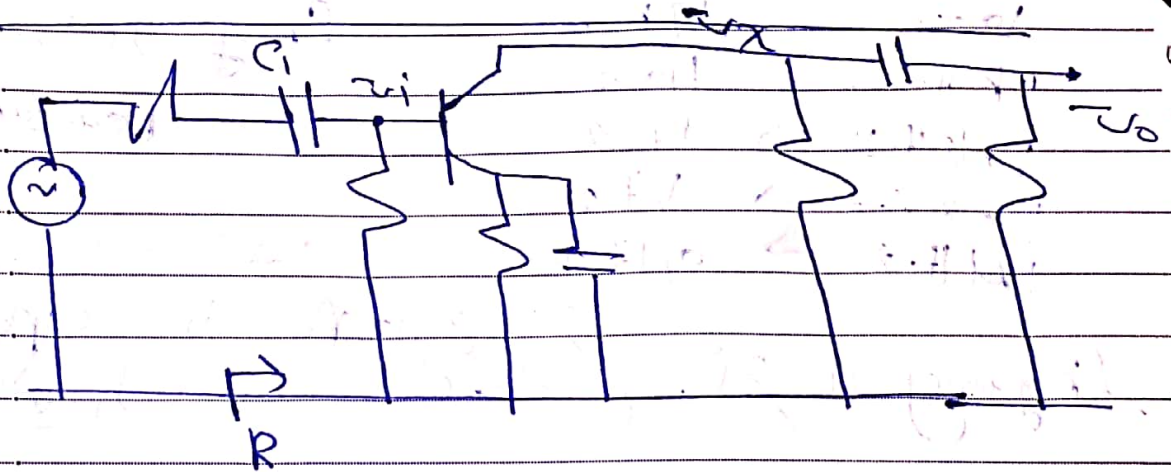

$f \uparrow$ $x_{C1} \downarrow$ $C_{C2} \downarrow$

$v_{in} \uparrow$ $v_x \uparrow$ $v_o \uparrow$ $A_v \uparrow$

$$v_i = v_s \times \frac{R_{in}}{R_{in} + R_s + x_{C1}}$$

$$v_x = k v_i$$


$$v_o = v_x \times \frac{R_e}{R_e + x_{C2}}$$

$$A_v = \frac{v_o}{v_i}$$


130

[دوائر (5) بسيطة]

Miller Rule

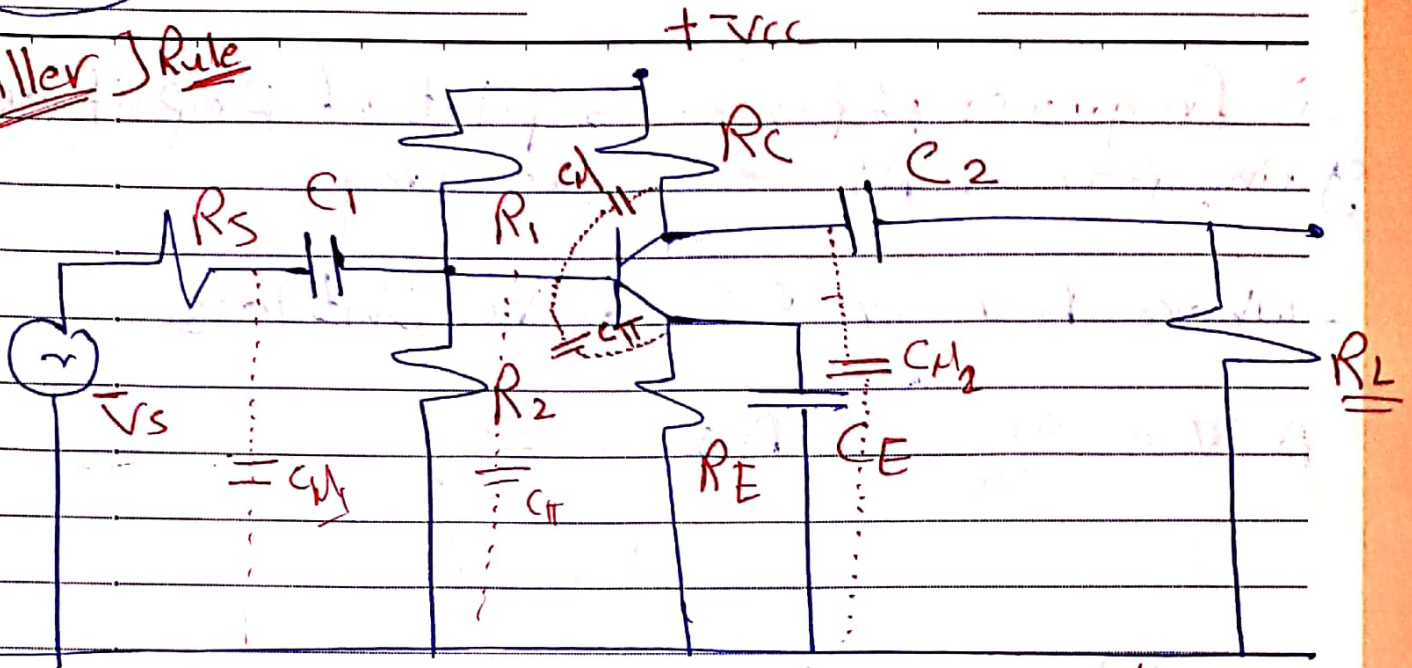

A_v or A_I Unitless or in dB.
(dB)

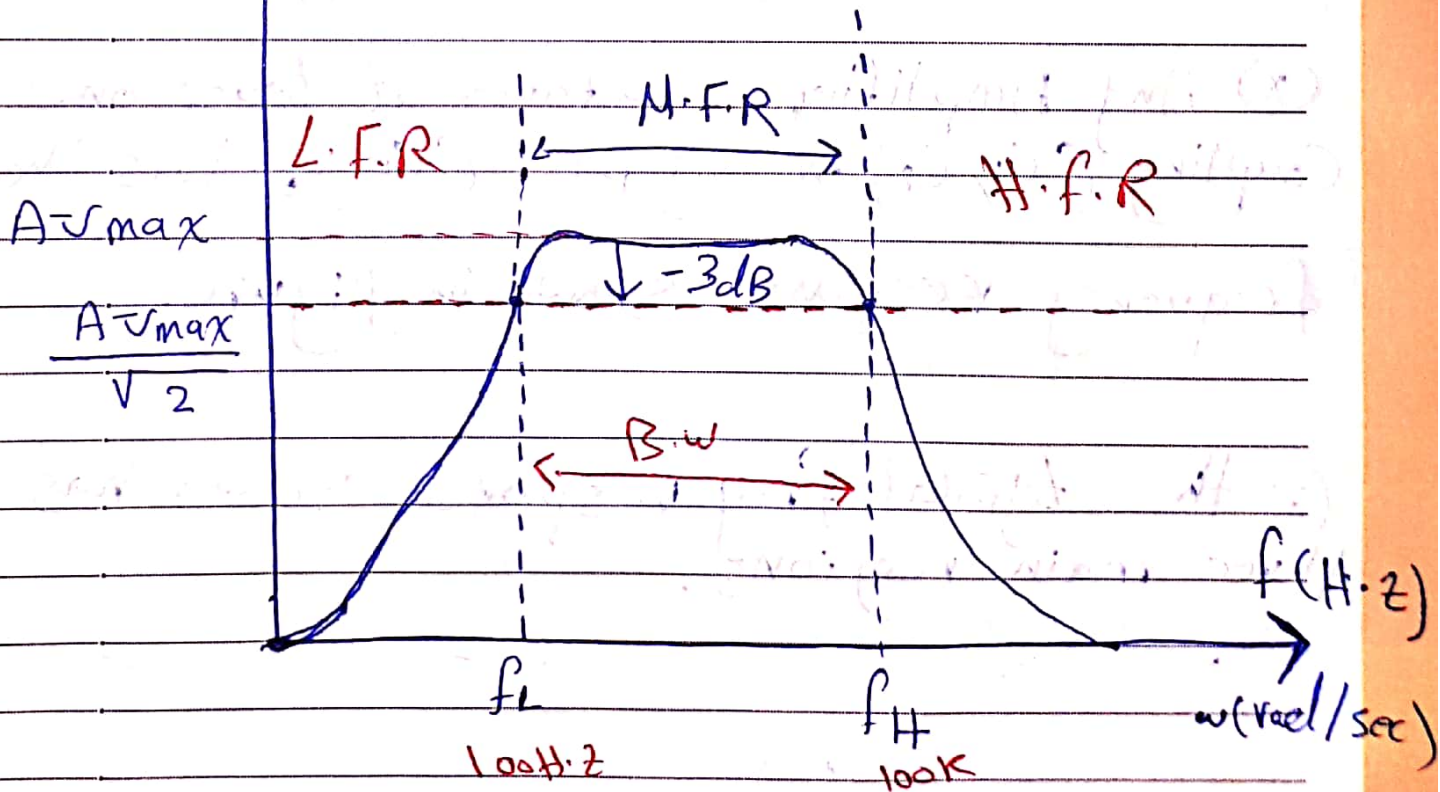

① Frequency Response: a plot of Amplifier gain A_V or A_I versus freq.

- where A_V or A_I can be Unitless.

$$A_V = \frac{V_o}{V_s} / \quad A_I = \frac{I_o}{I_s} /$$

OR in dB.

$$A_V(\text{dB}) = 20 \log \frac{V_o}{V_s} / \quad A_I = 20 \log \frac{I_o}{I_s}$$

* Any Amplifier contains at least one Coupling (C_1, C_2) or by pass (CE), has the frequency response shown in figure.

* the typical freq response shown has three main regions.

[1] Low - freq Region: (LFR):

* The gain is freq dependent, such that as $f \uparrow$, $A_v \uparrow$, ($A_v \propto f$),

freq dependent: Due to the effect of coupling and by pass capacitor.

where these capacitors are in series path of signal, and have considerable reactances X_c , as $f \uparrow$, $X_c \downarrow$, more signal reach o/p i.e. $v_o \uparrow$, and since $A_v = \frac{v_o}{v_s}$, and v_s is fixed, so $A_v \uparrow$.

[2] Medium freq Region: (All caps s.c.)

the cct behaves as a pure resistive cct, with a certain gain A_{vm} and a certain phase.

- It extends from $f_L \rightarrow f_H$, over a Band width (B.W), $f_H - f_L$, and this is the useful range of Amplifier response.

(frequency f_L to f_H)
All caps s.c. (s.c. = short circuit)

3] High freq Region:

- extends $f_H \rightarrow \infty$
 - the gain is freq dependent.
- such that $A_V \propto \frac{1}{f}$

as $f \uparrow$, $A_V \downarrow$

- all coupling by pass caps \Rightarrow S.C

- New stray capacitors appear effectively due physical structure of transistor, mainly

junction capacitor C_{j1} (between C-B) and

diffusion capacitor C_{π} (B-E).

($f, \omega R$ bi, HFR) is bes abt ut + ab, do so

$$A_V = g_m \cdot Z_L'$$

$$Z_L' = R_C \parallel R_L \parallel X_{C_{\mu 2}}$$

$$X_C = \frac{1}{2\pi f C_{\mu 2}}$$

$f \uparrow$, $X_{C_{\mu 2}} \downarrow$, $Z_L \downarrow$

$A_V \downarrow$

134

* Since they appear in shunt connection so
as $f \uparrow$, $X_C \downarrow$, $Z_L \downarrow$, $A \downarrow$

* The boundaries among these regions
are called Cut off frequencies (f_L, f_H): ①

② (-3dB frequencies) (f_L, f_H)

③ (Half-power frequencies) (f_L, f_H).

$$P_o(f_L) = P_o(f_H) = \frac{1}{2} P_o \Rightarrow \text{Medium freq region}$$

$$P = \frac{V^2}{R} \Rightarrow P_{mf} = \frac{V_{o \max}^2}{R}$$


$$P_{Lf} = P_{Hf} = \frac{\left(\frac{V_{o \max}}{\sqrt{2}} \right)^2}{R} = \frac{V_{o \max}^2}{R} \times \frac{1}{2}$$

$$P_{Lf} = P_{Hf} = \frac{1}{2} P_{mf}$$

135

$C_M = 2PF, C_{\pi} = 20PF$


6 s/p 150
Sh 10

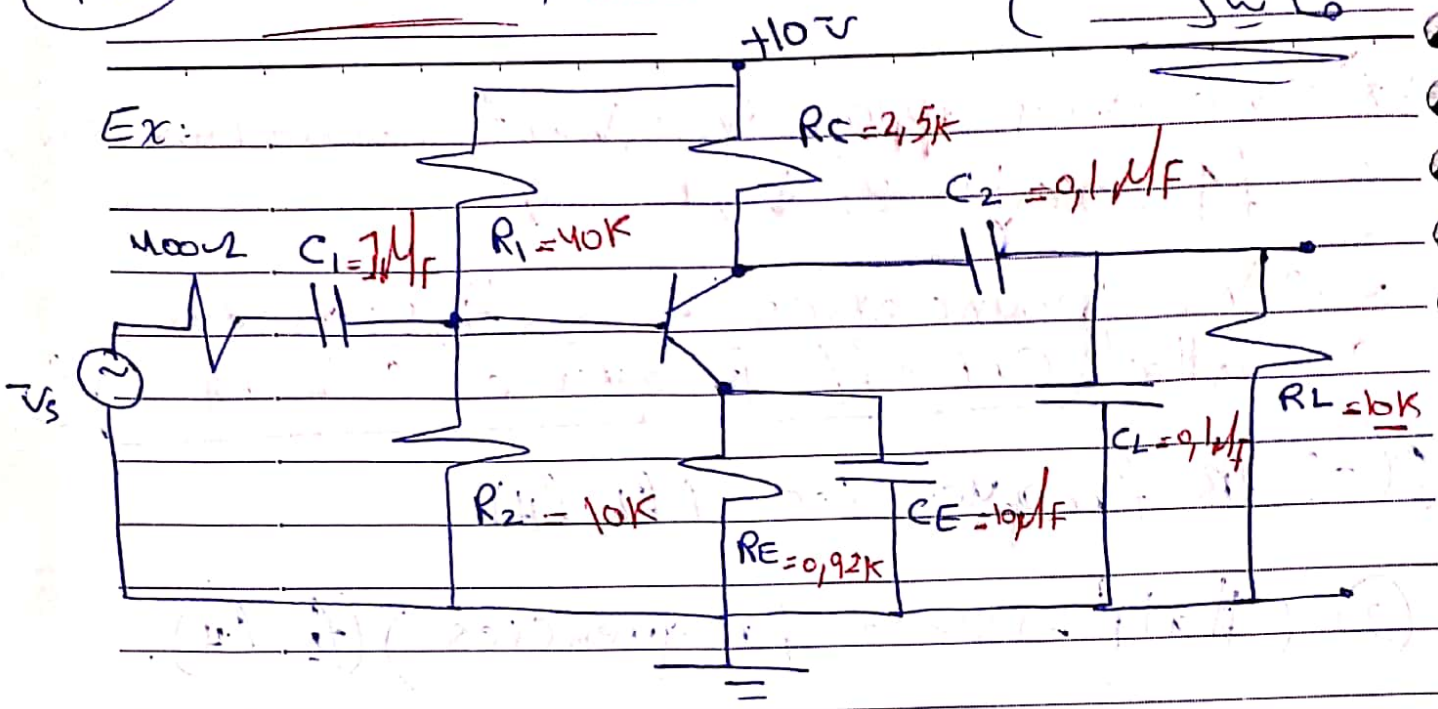

$\beta = 100, V_{BE} = 0.7V, V_A = \infty$

- ① Draw M.F equ cct.
- ② Draw H.F equ cct and FH.
- ③ Draw L.f equ cct, and find f_L .
- ④ sketch freq Response. (Bode plot).

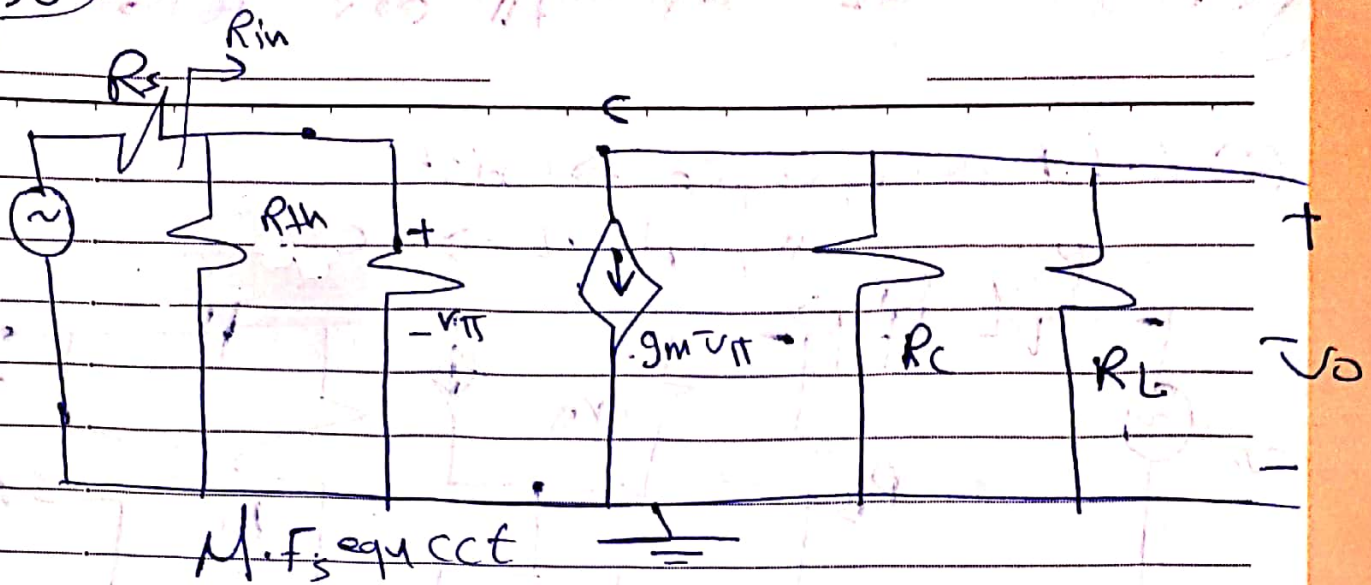① In M.F.R $\Rightarrow (C_1, C_E, C_2) \Rightarrow S.C$
 $\Rightarrow C_M, C_{\pi}, C_L \Rightarrow O.C$



$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v_{\pi}} \times \frac{v_{\pi}}{v_s}$$

$$A_v = \frac{-g_m v_{\pi} (R_C \parallel R_L) \times \frac{R_{in}}{R_{in} + R_s}}{v_{\pi}} = \frac{-g_m (R_C \parallel R_L) \cdot R_{in}}{R_{in} + R_s}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.3 \text{ mA}}{0.026} = \boxed{50 \text{ mA/V}}$$

D.C. Analysis $\Rightarrow v_{th} = 2 \text{ V}, R_{th} = 8 \text{ k}\Omega$

$$I_B = 0.013 \text{ mA}, I_C = \beta I_B = 1.3 \text{ mA}$$

$$r_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{100 \times 0.026}{1.3 \text{ m}} = \frac{2.6}{1.3} = 2 \text{ k}\Omega = \boxed{2 \text{ k}\Omega}$$

$$R_{in} = R_{th} \parallel r_{\pi} = 2 \text{ k}\Omega \parallel 8 \text{ k}\Omega = \boxed{1.6 \text{ k}\Omega}$$


$$A_v = \frac{-50 \times 2 \times 1.6}{1.6 + 400} = \boxed{-80}$$

137

PL No, FA des $\frac{1}{s}$

② L.f.R $\Rightarrow C_1, C_2, C_E \Rightarrow$ exist

$C_{\pi}, C_M, C_L \Rightarrow$ a.c

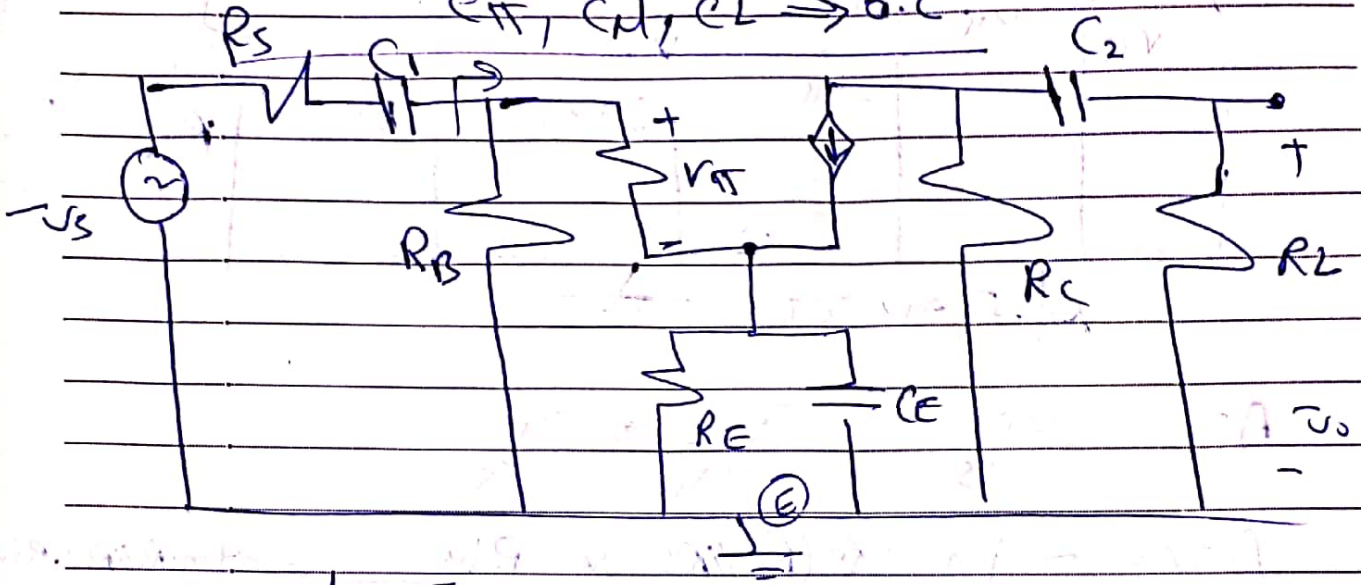

L.F.S.S A.C equ cct

① effect of $C_1 : (C_2, C_E \rightarrow \infty)$ s.c

$$f_{L1} = \frac{1}{2\pi C_1 \times R_{eq1}}, \quad R_{eq1} = R_{in} \text{ seen by } C_1$$

$$R_{eq1} = R_s + R_{in}, \quad R_{in} = R_B \parallel R_E$$

$$f_{L1} = \frac{1}{2\pi (0.4 + 1.6) \times 10^{-6}} = \frac{10^3}{4\pi} = 80 \text{ Hz}$$

138

C_1, C_2 S.C

$$f_{L2} = \frac{1}{2\pi C_2 \cdot R_{eq2}} \quad ; \quad R_{eq2} = R_L + R_C$$

$$f_{L2} = \frac{1}{2\pi \times 0,1 \times 10^{-6} \times 12,5K} \approx 127 \text{ H} \cdot \text{z}$$

⊗ effect of $C_E \Rightarrow (C_1, C_2) \Rightarrow$ S.C

$$f_{L3} = \frac{1}{2\pi C_E \cdot R_{eq3}} \Rightarrow R_{eq3} = \frac{(R_S // R_B) + r_{\pi}}{\beta + 1} // R_E$$

$$f_{L3} = \frac{1}{2\pi \times 10 \times 10^{-6} \times 20} = \frac{10^4}{4\pi} = \boxed{800 \frac{\text{H} \cdot \text{z}}{\text{K}}}$$


- the effective of f_L is the highest value

$$\boxed{f_L = 8000 \text{ H} \cdot \text{z}} = 8 \text{ K} \cdot \text{H} \cdot \text{z}$$

130

* High freq Region: $(C_1, C_2, C_e) \rightarrow s.c.$

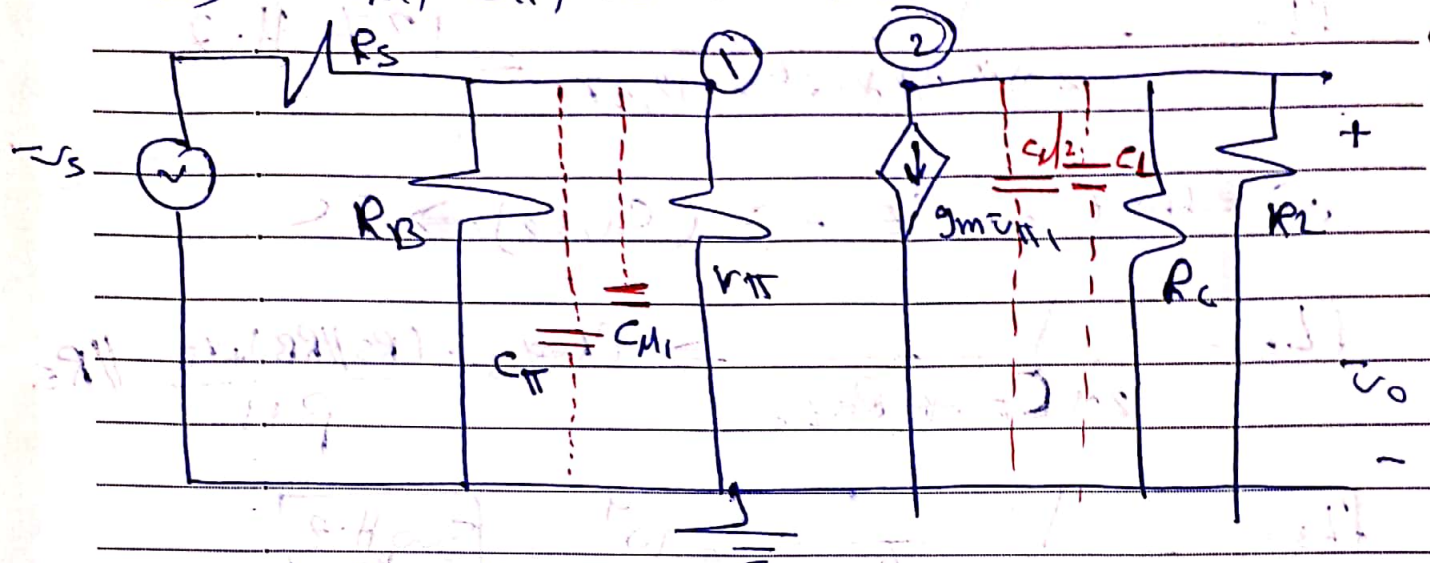$\Rightarrow C_M, C_{\pi}, C_L \Rightarrow$ exist



$$C_{M1} = (1 - K) \times C_M$$

$$K = \frac{v_2}{v_1}$$

$$C_{M2} = \left(1 + \frac{1}{K}\right) \times C_M$$

$$K = \frac{-g_m v_{\pi} (R_C || R_L)}{v_{\pi}} = -50 \times 2 = -100$$


$$C_{M1} = 2 \times 101 = 202 \text{ PF}$$

$$C_{M2} = 2 \times \left(1 + \frac{1}{100}\right) \approx 2 \text{ PF}$$

For $K \gg 1 \Rightarrow C_{M2} = C_M$

140

$C_L = 10 \mu F$

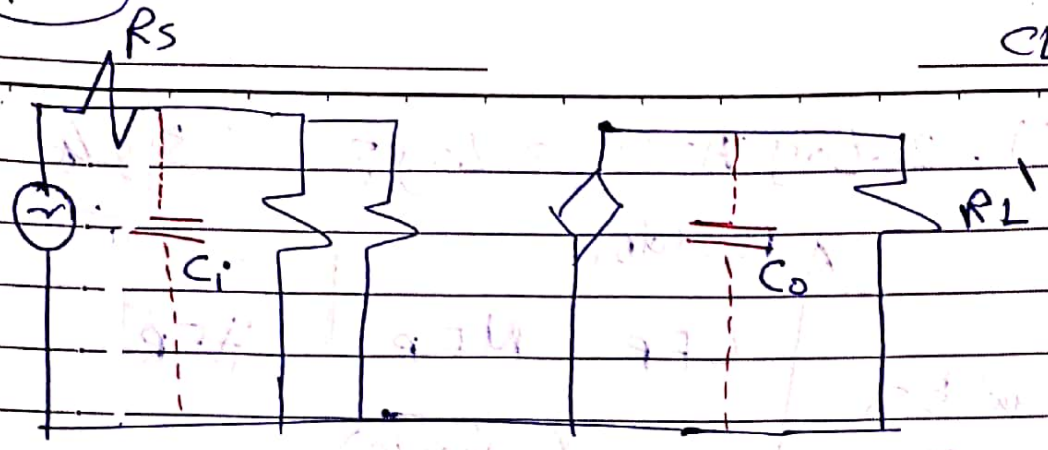

$$C_i = C_{\pi} + C_{M1} = 222 \text{ pF}$$

$$C_o = C_L + C_{M2} = 10000 \text{ pF} + 2 = 2 \text{ } \mu\text{F}$$

$$f_{Hi} = \frac{1}{2\pi R_{eq1} C_i} \quad , \quad R_{eq1} = R_{th} \text{ seen by } C_i$$

$$R_{eq1} = R_s // R_{in} \Rightarrow 0,4 // 1,6 = 0,32 \text{ k}$$

$$f_{Hi} = \frac{1}{2\pi \times 0,32 \text{ k} \times 10^3 \times 222 \times 10^{-12}} = 2,2 \text{ MHz}$$


$$f_{Ho} = \frac{1}{2\pi C_o R_{eq2}} \Rightarrow R_{eq2} = R_C // R_L = 2 \text{ k}$$

$$f_{Ho} = \frac{1}{2\pi \times 10 \times 10^{-9} \times 2 \text{ k}} = 8 \text{ kHz}$$


the effective f_H is 8 kHz

141
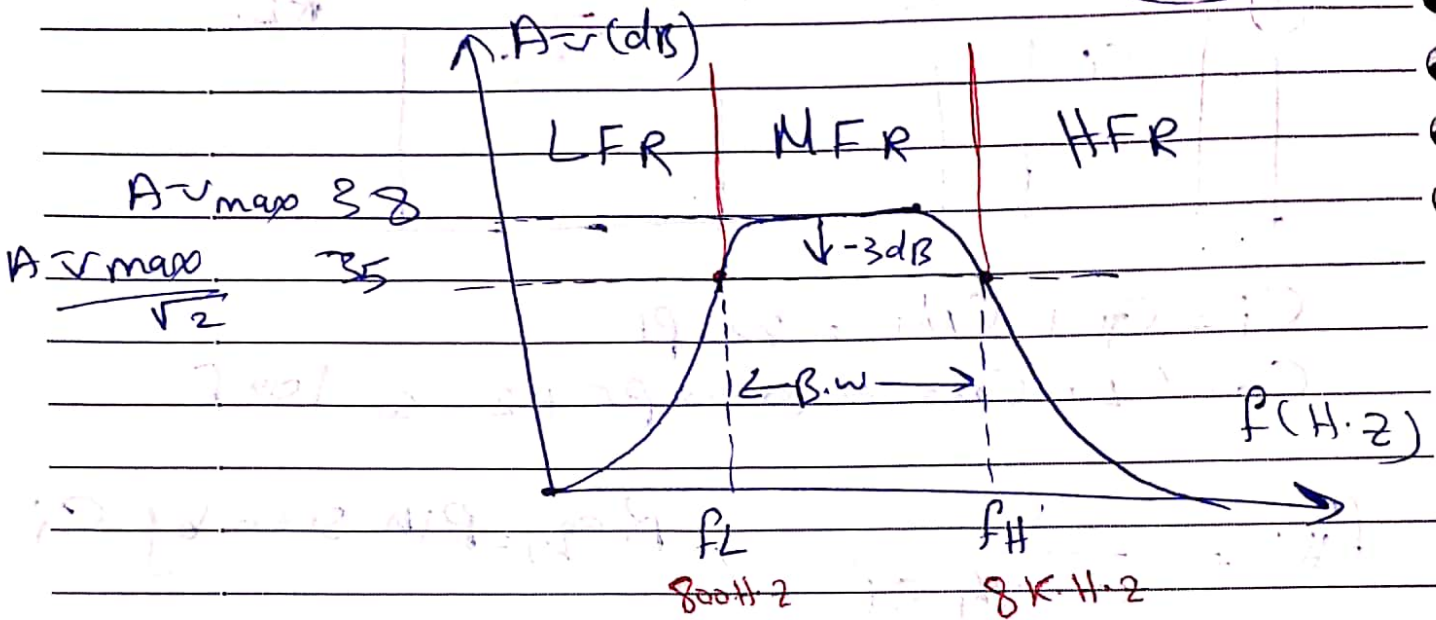
$$A_v \text{ (dB)} = 20 \log A_v = 20 \log 80 = 38 \text{ dB}$$




Freq Response of FET Amplifier.

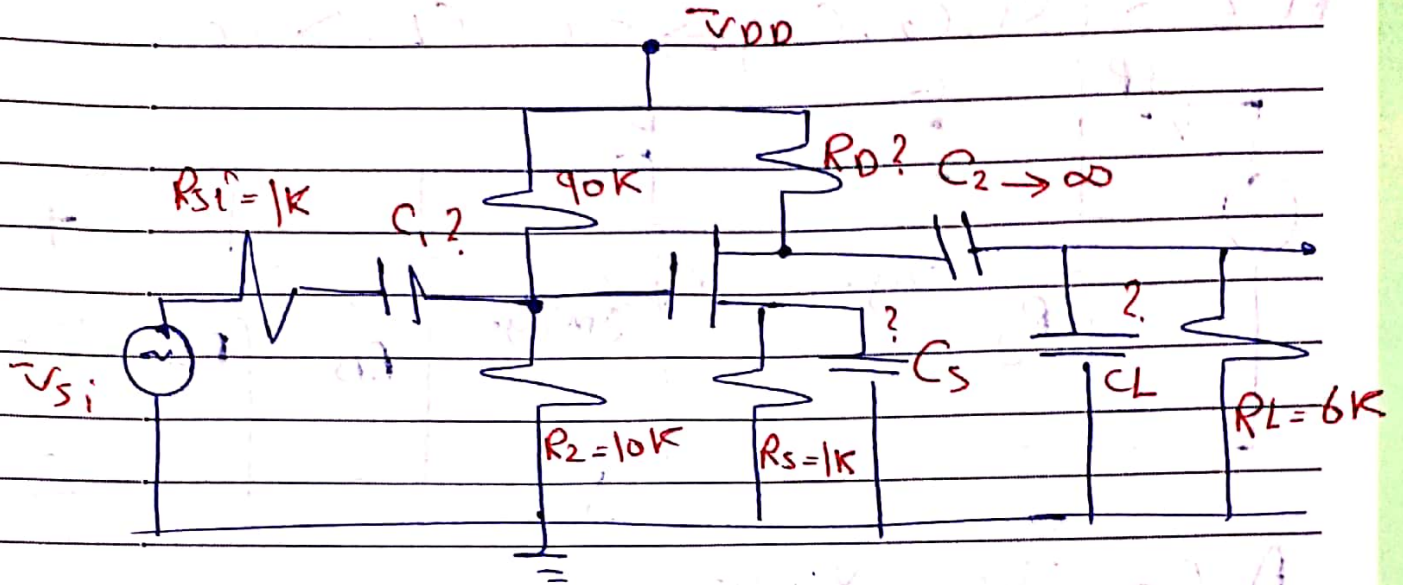

The cct is biased such that $g_m = 5 \text{ mA/V}$.


① Design the cct such that, $A_v = -11$ and $f_L = 500 \text{ Hz}$, $f_H = 200 \text{ kHz}$.

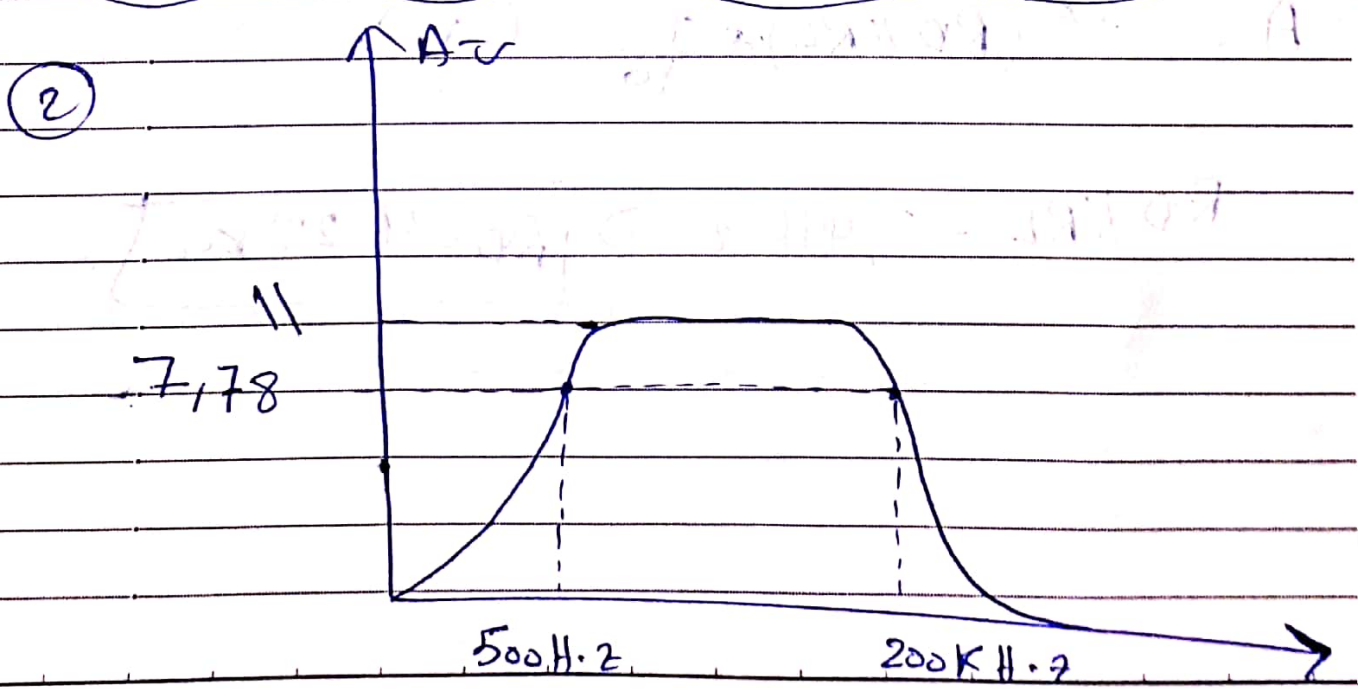② sketch the freq response of the Amplifier.



143
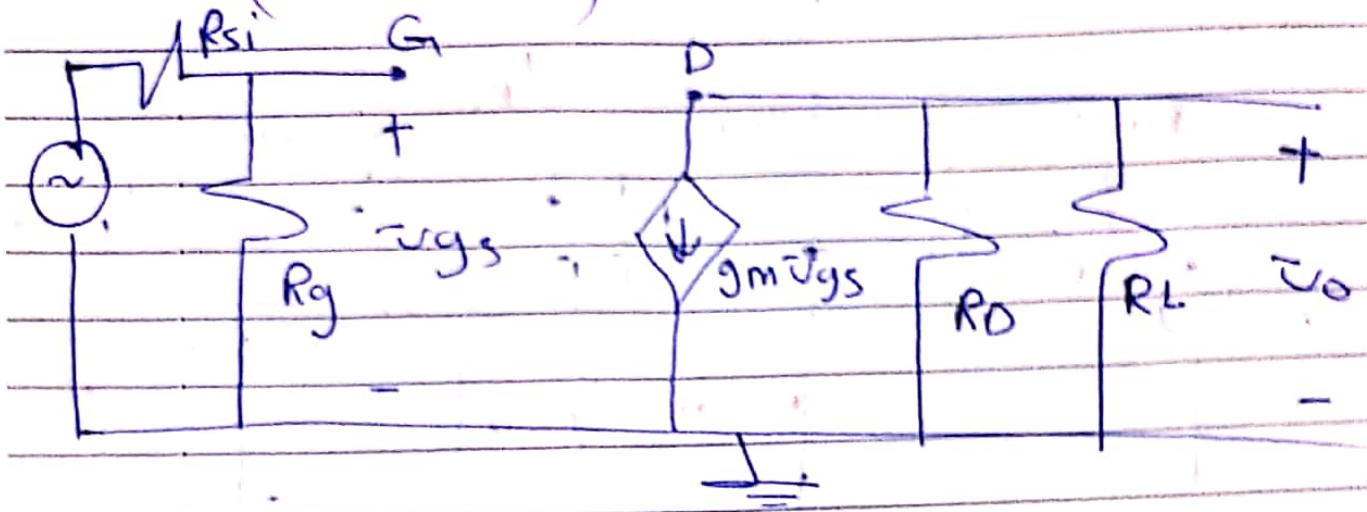
$$RD \Rightarrow (C_1, C_2, C_5) \Rightarrow sC, CL \Rightarrow 0C$$



$$A_v = \frac{v_o}{v_{gs}} \times \frac{v_{gs}}{v_{si}}$$

$$\Rightarrow \frac{-g_m(-v_{gs})(R_D \parallel R_L)}{v_{gs}} = -g_m v_{gs} (R_D \parallel R_L)$$

$$\frac{v_{gs}}{v_{si}} = \frac{R_g}{R_g + R_{si}}$$


$$A_v = -5(R_D \parallel R_L) \times \frac{9}{10} = -11$$

$$R_D \parallel R_L = 2,44 k\Omega \Rightarrow R_D = 4,28 k\Omega$$

144

C_1, C_2 exist, ~~C_2, C_1, C_1, C_2~~

* For LFR \Rightarrow

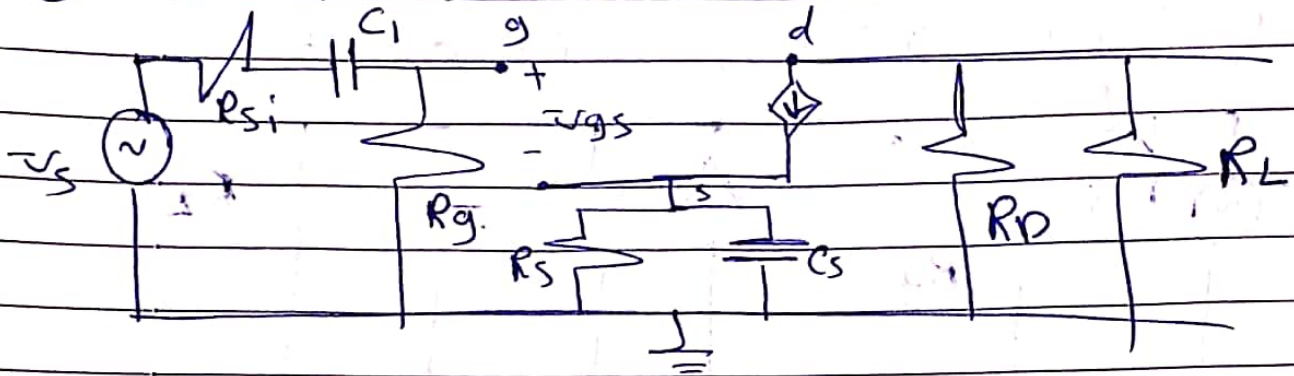

$$f_{L1} = \frac{1}{2\pi C_1 R_{eq1}} \Rightarrow C_1 = \frac{1}{2\pi f_L \times R_{eq1}}$$

$$R_{eq1} = R_{si} + R_g = 10 \text{ k}\Omega \Rightarrow C_1 = \frac{1}{2\pi \times 500 \times 10 \times 10^3}$$

$$C_1 = 32 \text{ nF}$$

$$\Rightarrow f_{L2} = \frac{1}{2\pi C_2 \times R_{eq2}} \Rightarrow C_2 = \frac{1}{2\pi \times 500 \times 1 \times 10^3} =$$

$$\text{then } \Rightarrow C_2 = 0,32 \text{ }\mu\text{F}$$

- Keep $C_2 = 0,32 \text{ }\mu\text{F}$, and multiply C_1 by 1

to make f_L depends on single caps


$$C_1 = 320 \text{ nF}$$

تحتفظ بوقت العبور و A_{vL} و A_{vH}
 بوقت العبور، A_{vL} و A_{vH} ، A_{vL} و A_{vH}

كان A_{vL} و A_{vH} A_{vL} و A_{vH} من واحد، A_{vL} و A_{vH} و A_{vL} و A_{vH}
 A_{vL} و A_{vH} gain، A_{vL} و A_{vH}

CL, High freq Region Analysis:

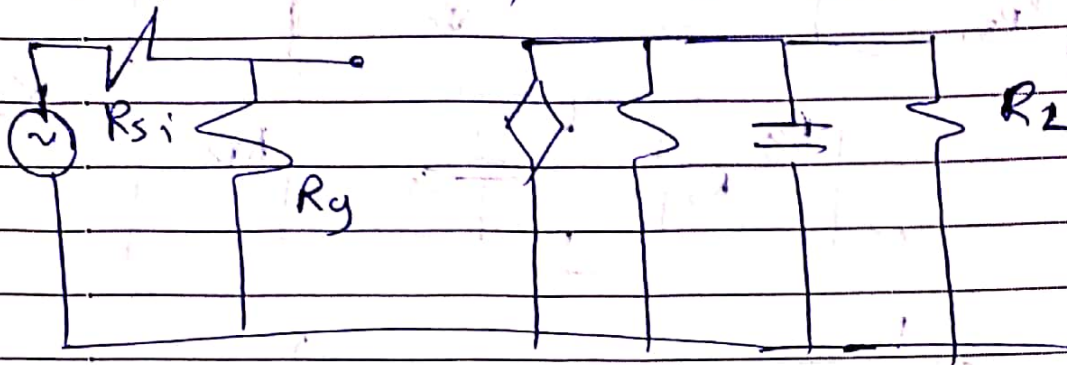
$C_1, C_2, C_s \Rightarrow S.C$, C_L exist



$$f_H = \frac{1}{2\pi C_L \cdot R_{eq}}, \quad R_{eq} = R_L \parallel R_D = 2,44 \text{ k}\Omega$$

$$C_L = \frac{1}{2\pi \cdot 2 \times 10^5 \cdot 2,44 \times 10^3} = 0,32 \text{ nF}$$

Ex:

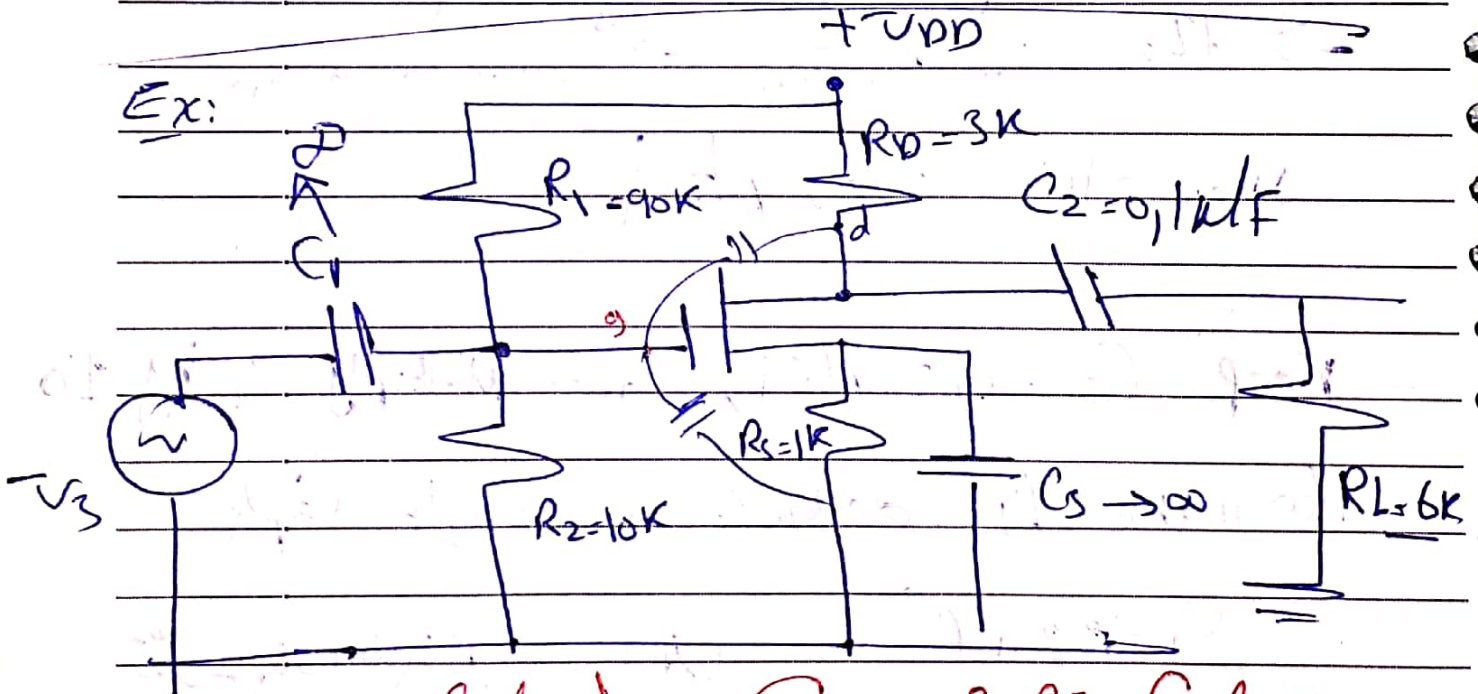

the Mosfet has $C_{gs} = 20 \text{ pF}$, $C_{gd} = 5 \text{ pF}$


$g_m = 5 \text{ mA/V}$

① Calculate A_{vm} , f_L , f_H

② sketch freq Response

① ACM ? from MFR Analysis:

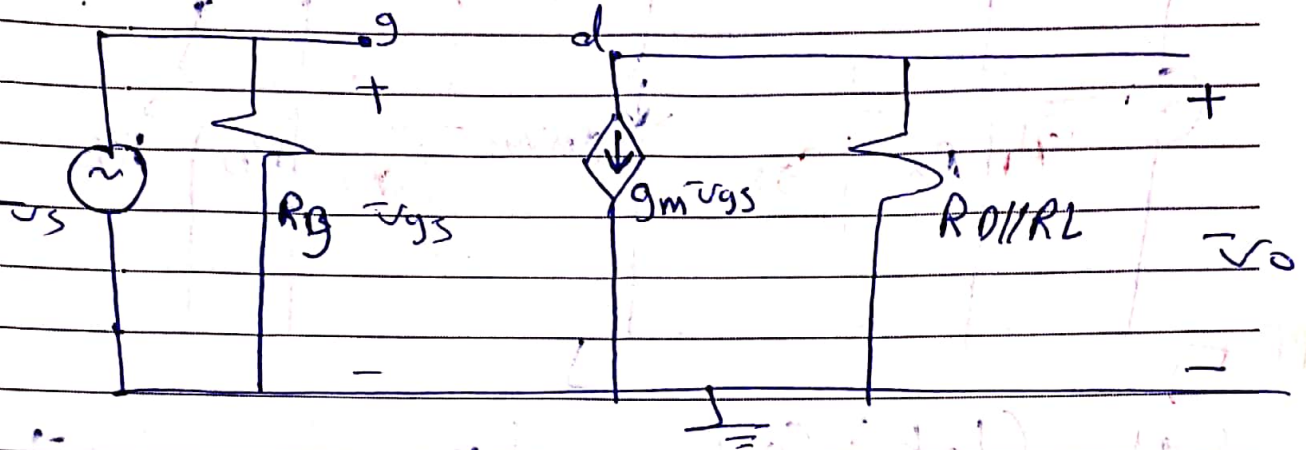
$\Rightarrow (C_1, C_s, C_2) \Rightarrow$ s.c , $C_{gs}, C_{gd} \rightarrow$ o.c



$$A_v = \frac{v_o}{v_s} = \frac{-g_m v_{gs} (R_D || R_L)}{v_{gs}} = -g_m (R_D || R_L) \quad (-10)$$

② LFR Analysis : (C_1, C_2) exist

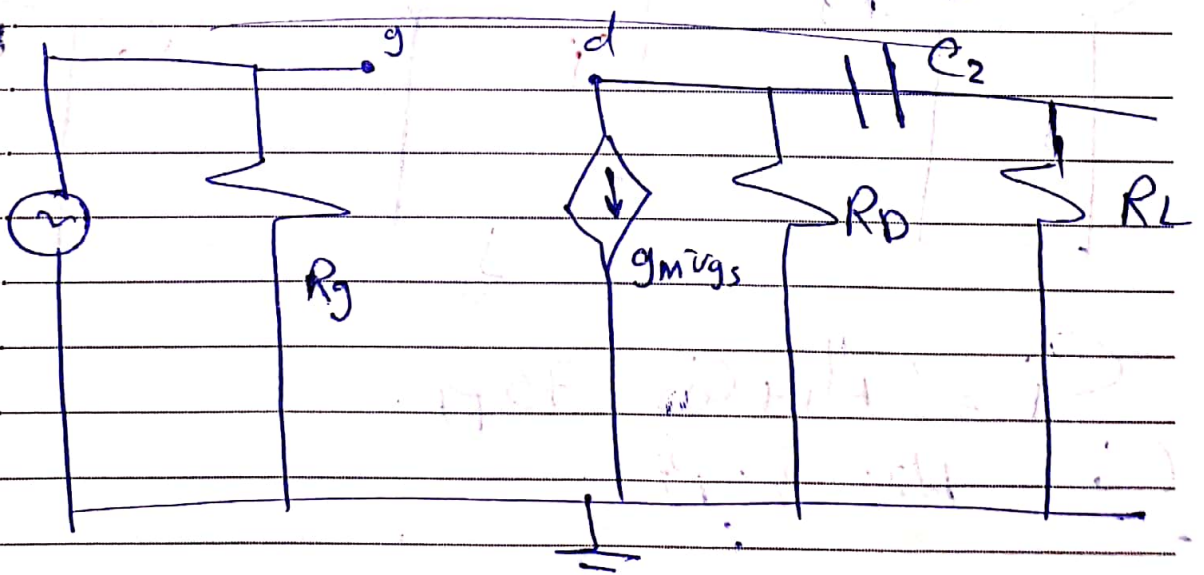
$\Rightarrow C_1, C_s \Rightarrow$ s.c , $C_{gs}, C_{gd} \rightarrow$ o.c



$$f_L = \frac{1}{2\pi C_2 * R_{eq2}} \quad ; \quad R_{eq2} = R_L + R_D = 9k\Omega$$

$$f_L = \frac{1}{2\pi * 0.1 * 10^{-6} * 9 * 10^3} = 177.11 \text{ Hz}$$

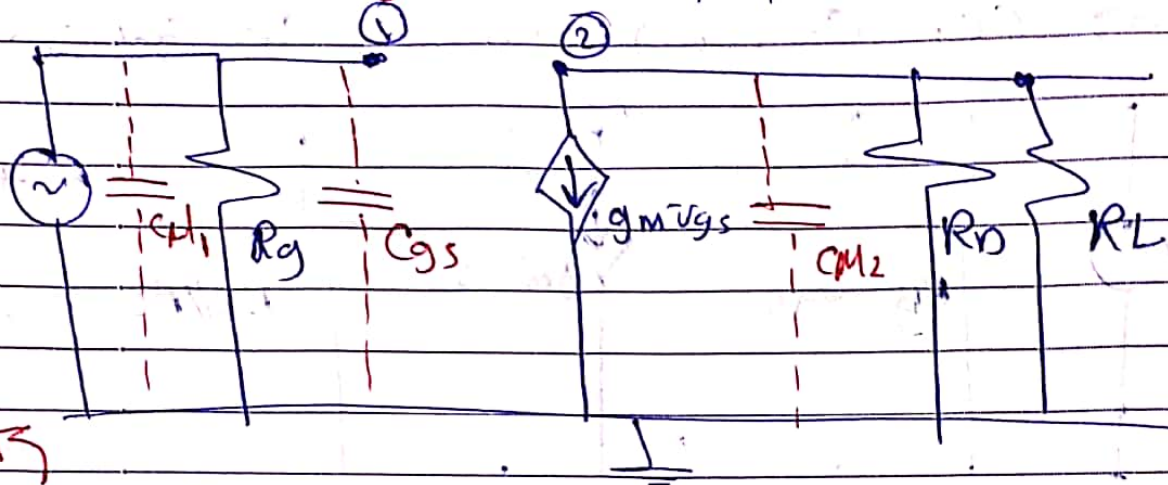* HFR Analysis $\Rightarrow C_2, C_1, C_3 \Rightarrow S.C$



55 PF


$$C_{M1} = (1 - K) C_{gd}$$

5.5 PF

$$C_{M2} = C_{gd} \left(1 - \frac{1}{K}\right)$$

$$K = -g_m v_{gs} (R_D // R_L)$$

$$K = -10$$

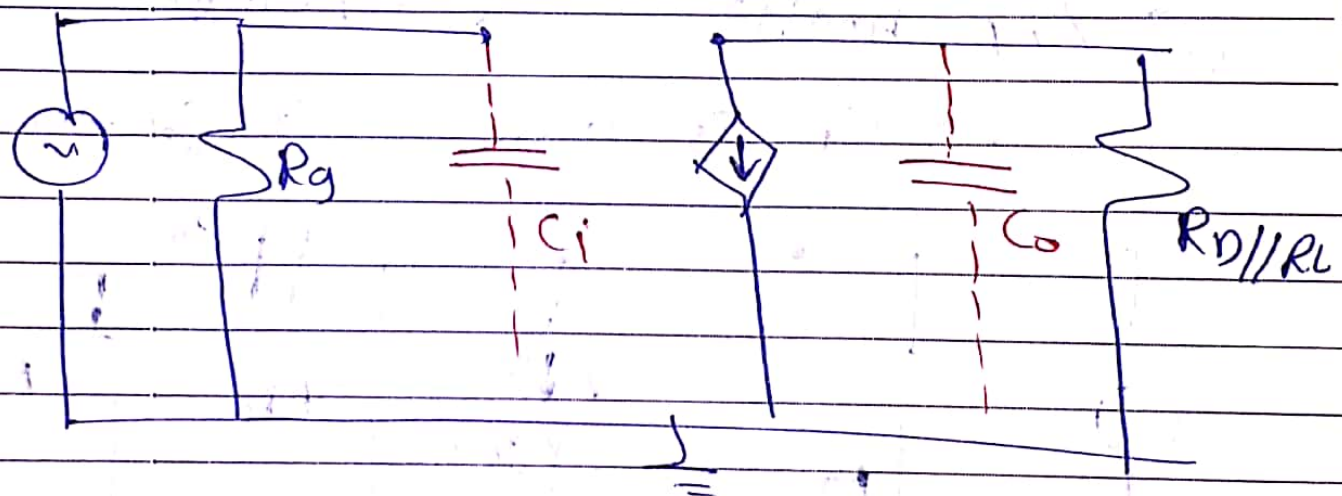

$$C_i = C_{M1} + C_{gs} = 75 \text{ pF}$$

$$C_o = C_{M2} = 5.5 \text{ pF}$$


$$f_{Hi} = \frac{1}{2\pi C_i R_{eq1}} \rightarrow R_{eq1} = \text{Zero}$$

$$f_{Hi} = \infty$$

148

$$f_{H0} = \frac{1}{2\pi C_0 \times R_{eq}} \rightarrow R_{eq} = R_D \parallel R_L = 2k\Omega$$
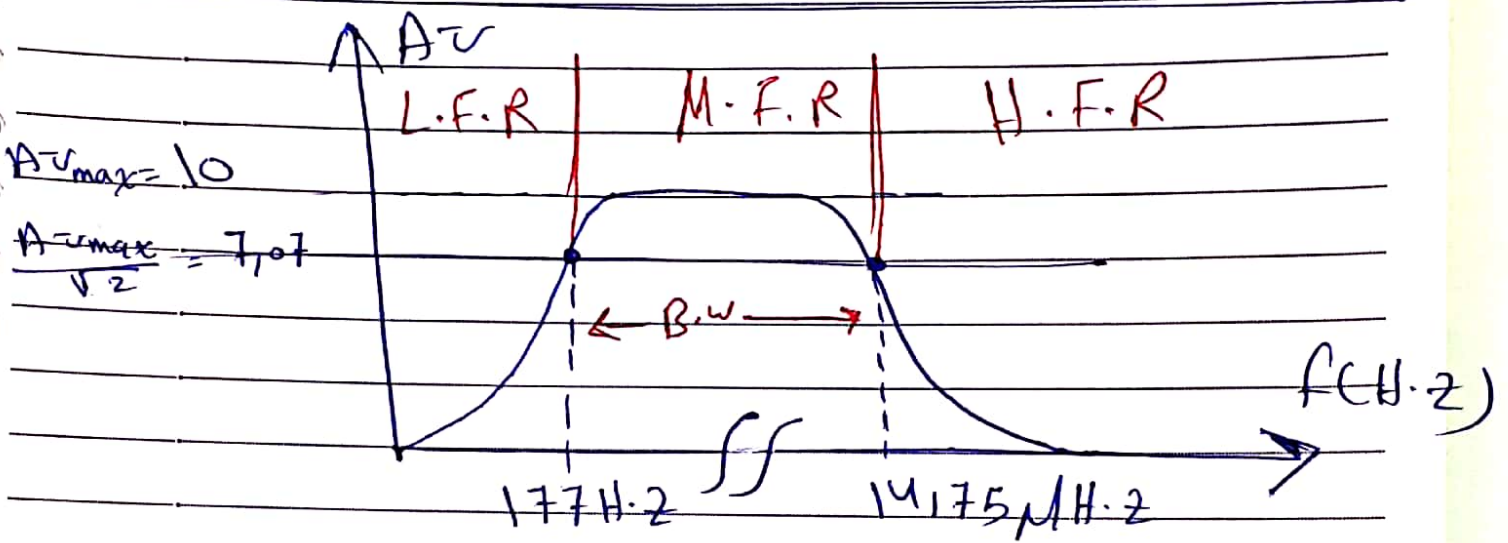
$$f_{H0} = \frac{1}{2\pi \times 5.5 \times 10^{-12} \times 2 \times 10^3} = 14.75 \text{ MHz}$$



سوال کے جواب کے ساتھ ساتھ اس کا جواب بھی

Putami