



تقدم لجنة EICoM الاكاديمية

دفتر لمادة:

**الالكترونيات (2)**


من شرح:

**د.هادي العيثاوي**

جزيل الشكر للطالب:  
**نمر عودة**



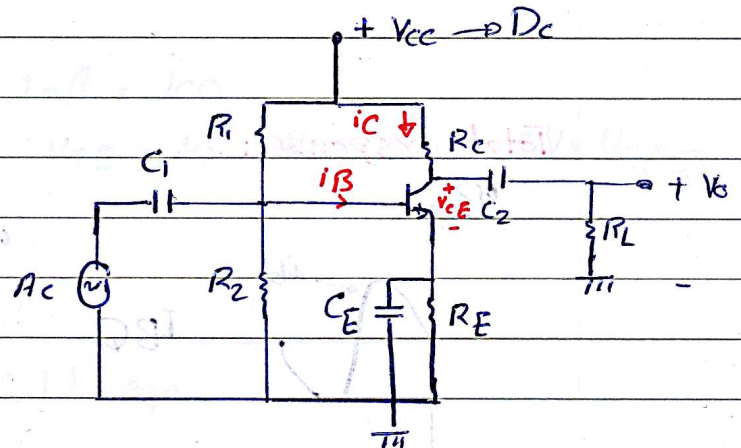- 1) The BJT must be biased in F.A.M to be used as an Amp.
- 2) Any Amp must have:
  - Dc source  $\rightarrow$  To biase BJT in F.A.M
  - Ac source  $\rightarrow$  To supply Ac signal.
  - Resistor or voltage & current limiting  $\rightarrow$  biasing.
  - Capacitors  $\rightarrow$   $C_1, C_2$  : Coupling Cap (Coupling for Ac & Blocking Dc)
  - $C_E$  : bypass Cap.




3) Amp is Linear circuit (so superposition is applied)

Total response

$$\begin{cases} i_B = I_{BQ} + i_b \\ i_C = I_{CQ} + i_c \\ V_{CE} = \underbrace{V_{CEQ}}_{D.C} + \underbrace{v_{ce}}_{A.C} \end{cases}$$

For No A.C :-

$$i_B = I_{BQ}, \quad i_C = I_{CQ}, \quad v_{CE} = V_{CEQ}$$

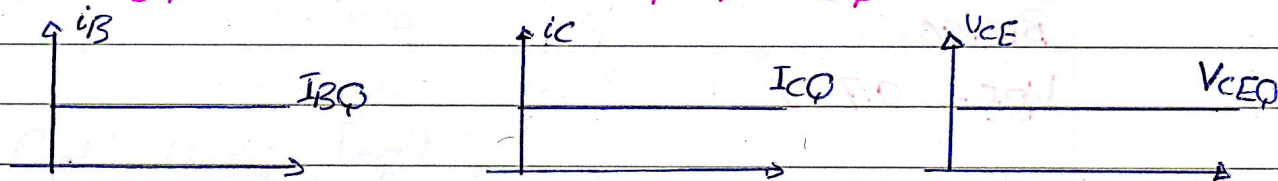





CH6

Monday 18.7.2016


when AC is applied:

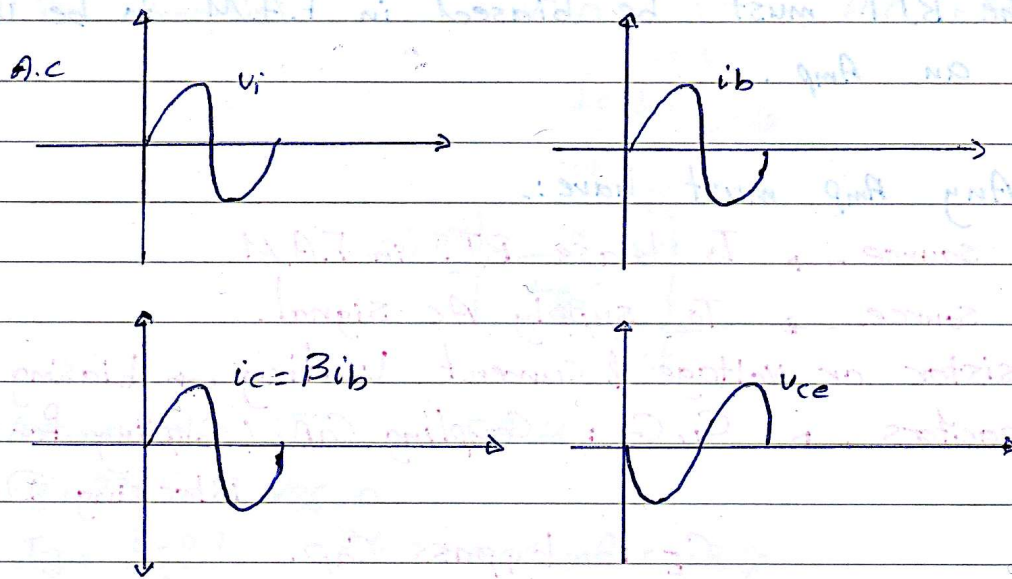

Total response:

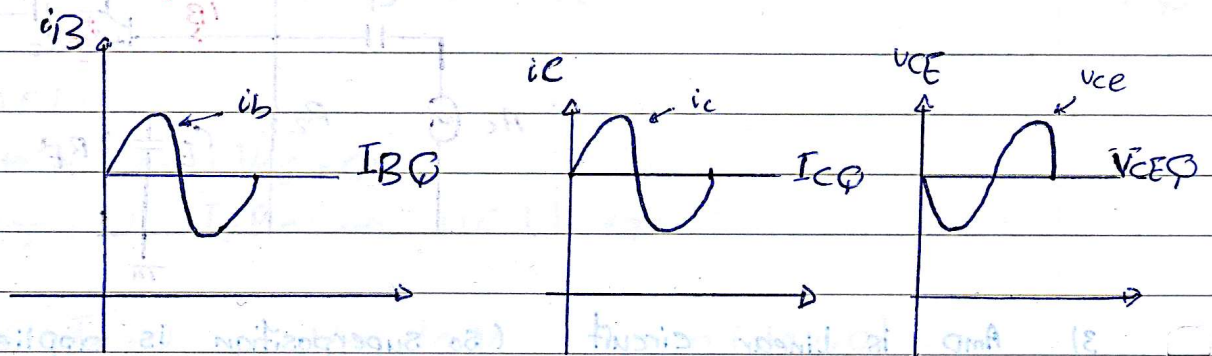

Basic Amp. Operation:

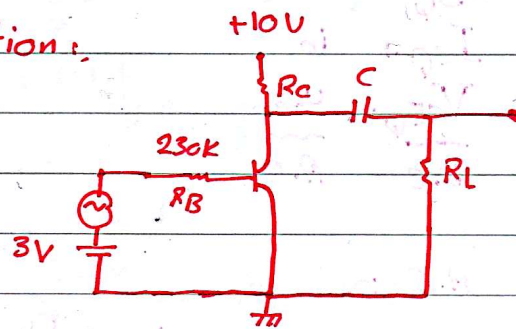


$$\beta = 100$$

$$V_{BE} = 0.7 \text{ V}$$

Using superposition:

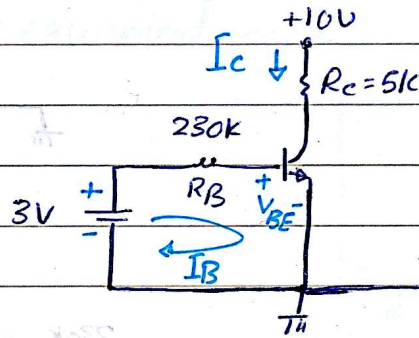1) Dc Analysis : Cap  $\rightarrow$  O.C , A.C  $\rightarrow$  Short cct.



Assume the BJT in F.A.M.:

$$-3 + 230 I_B + V_{BE} = 0$$

$$I_B = \frac{3 - 0.7}{230k} = \frac{2.3}{230k} = 0.01 \text{ mA} = I_{BQ}$$

$$I_C = \beta I_B = 100 \times 0.01 = 1 \text{ mA} = I_{CQ}$$

$$-10 + I_C R_C + V_{CE} = 0 \rightarrow V_{CE} = 10 - I_C R_C = 10 - 5 = 5 \text{ V} = V_{CEQ}$$


D.C.L.L

$$-10 + I_C R_C + V_{CE} = 0$$

$$V_{CE} = 10 - I_C R_C \Rightarrow \text{D.C.L.L eqn.}$$

For  $I_C = 0$  ,  $V_{CE} = 10 \text{ V}$  ,  $P_1 (10 \text{ V}, 0)$

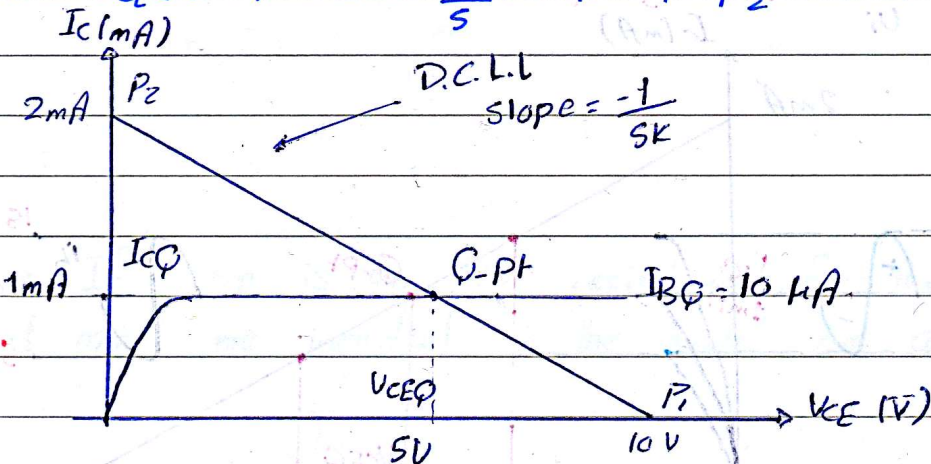For  $V_{CE} = 0$  ,  $I_C = \frac{10}{5} = 2 \text{ mA}$  ,  $P_2 (0, 2 \text{ mA})$




Qpt  $(V_{CEQ}, I_{CQ})$   
 $(5 \text{ V}, 1 \text{ mA})$



For A.C Analysis

C → S.C D.C Source → S.C

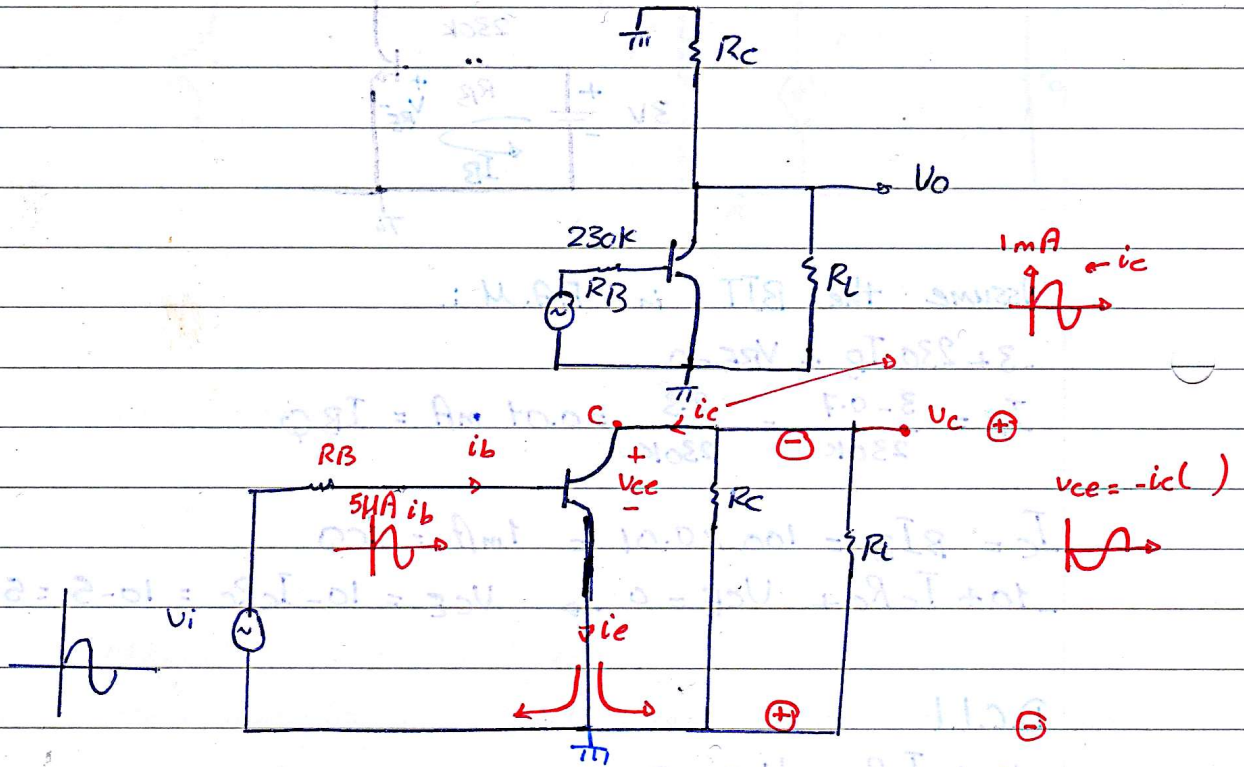


$$V_{ce} + i_c (R_C || R_L) = 0$$

$$V_{ce} = -i_c (R_C || R_L)$$

$$V_o = V_{ce}$$

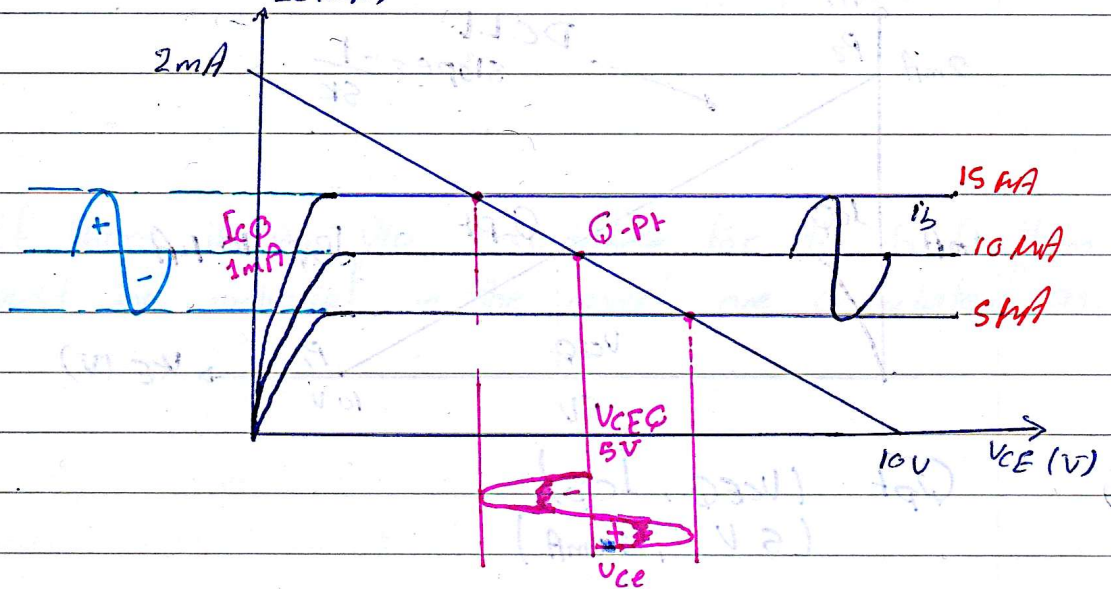
$$A_v = \frac{V_o}{V_i} \rightarrow \text{Voltage gain}$$





BJT Amp.

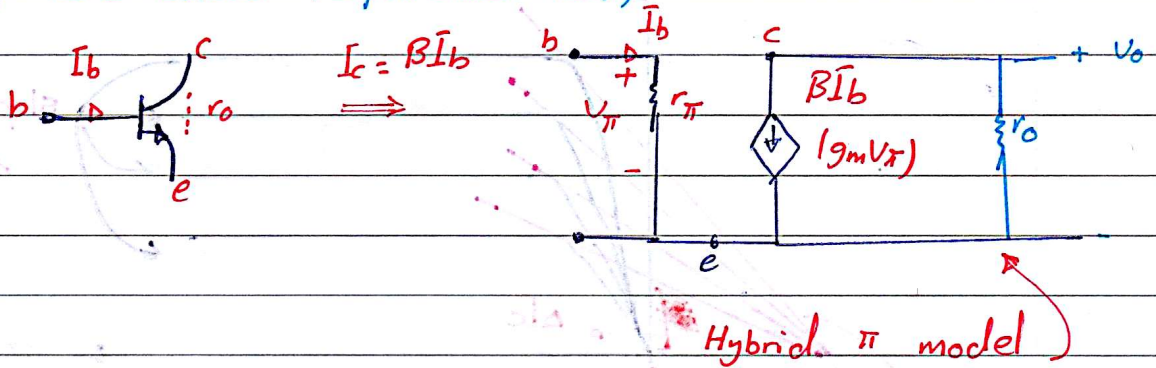To perform A.c Analysis, the BJT is replaced by it's model (equivalent cct)



$r_{\pi}$ : B.E resistance

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}}$$

$V_T$ : Thermal voltage (26 mV)

$g_m$ : Transconductance (A/V, mA/V, uA/V)

$$g_m = \frac{I_{CQ}}{V_T}$$

$$g_m V_T = \beta I_b$$

$$\frac{I_{CQ}}{V_T} (I_b r_{\pi}) = \frac{\beta V_T}{r_{\pi}}$$

$$\# V_T = I_b r_{\pi}$$

$$g_m r_{\pi} = \beta$$


⇒ If there is an Olp resistance for the BJT then it must be included in the model are calculated as:

$$r_o = \frac{V_A}{I_{CQ}}$$

$V_A$ : Early voltage

$V_A$ : gain (50 <  $V_A$  < 300) V

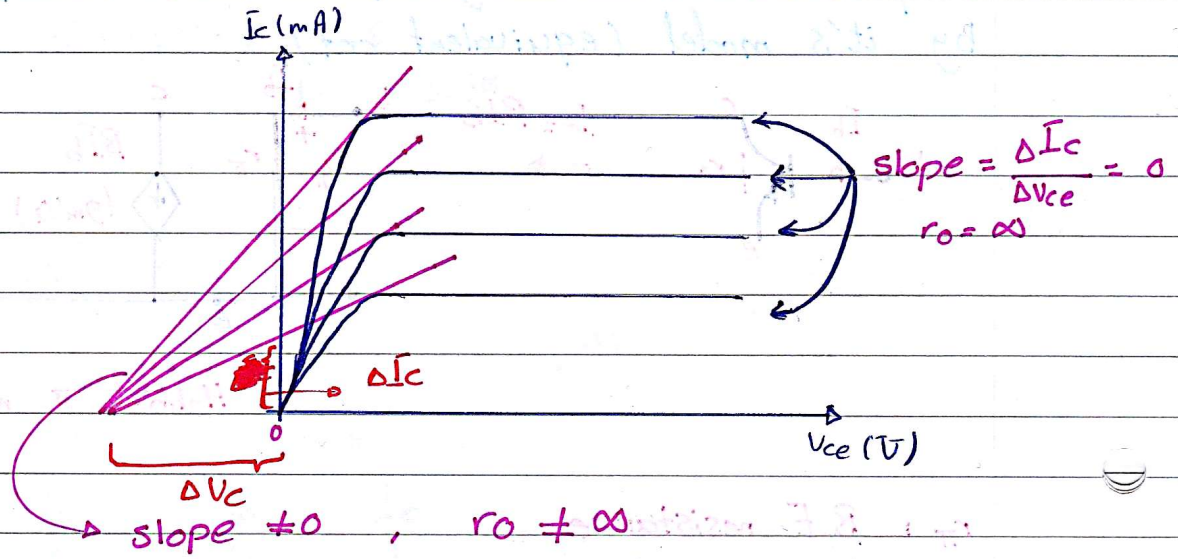
$r_o = \frac{1}{\text{slope of } (I_c, V_{ce}) \text{ Line}}$



$\text{Slope} = \frac{\Delta I_c}{\Delta V_{ce}} = \frac{I_{cQ}}{V_A}$

$\frac{1}{\text{slope}} = r_o = \frac{V_A}{I_{cQ}}$

Ac equivalent ckt for the Amp:-

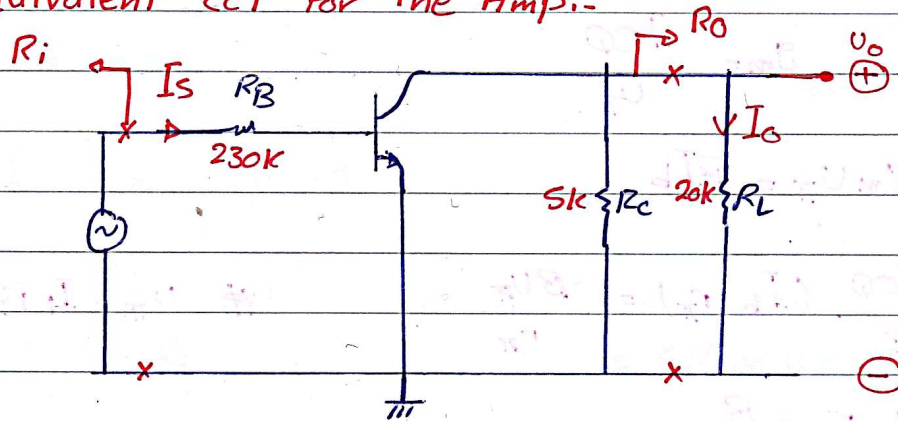

Back to the basic example:-

From D.C Analysis

$I_{cQ} = 1mA$

Find voltage gain :-  $A_v = \frac{V_o}{V_s}$

Current gain :-  $A_i = \frac{I_o}{I_s}$

input resistance  $R_i$


Output resistance  $R_o$




CHG

Tuesday 19. 7. 2016

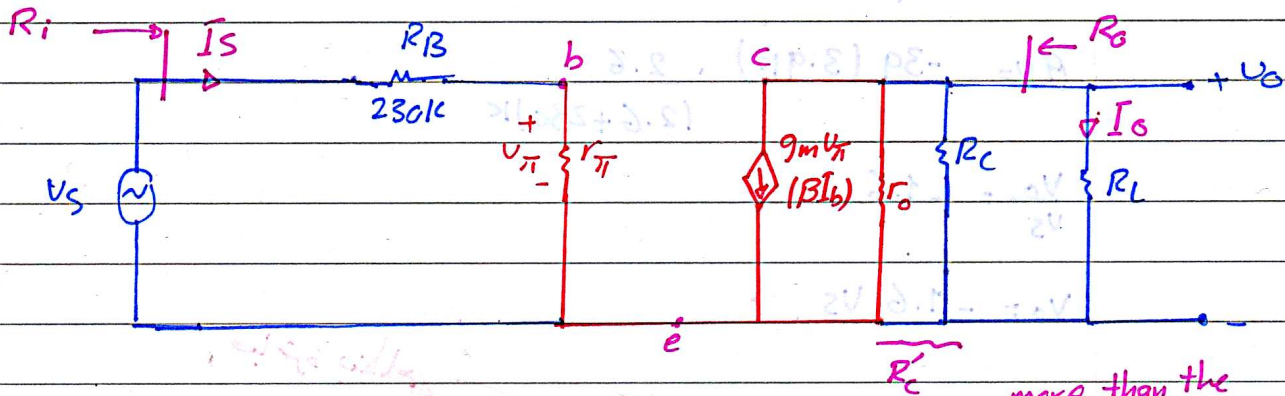Given:  $\beta=100$ ,  $V_T=26\text{ mV}$ ,  $V_A=100\text{ V}$



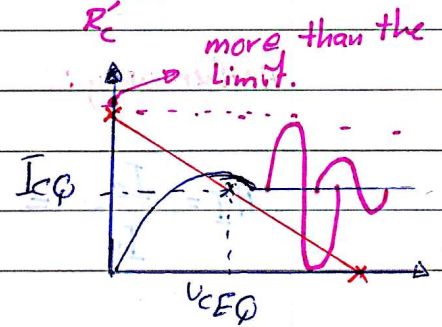Small signal A.C equivalent ckt  
For the Amp.



1) Voltage gain :  $A_v = \frac{V_o}{V_s}$

$V_o = -g_m V_{\pi} R'_L$ , where  $R'_L = r_o \parallel R_C \parallel R_L$

$V_{\pi} = V_s \frac{r_{\pi}}{r_{\pi} + R_B}$

$\therefore V_o = -g_m V_s \frac{r_{\pi}}{r_{\pi} + R_B} R'_L$

$\frac{V_o}{V_s} = A_v = \frac{-g_m r_{\pi} R'_L}{r_{\pi} + R_B}$

$\ominus$  means  $180^\circ$  phase shift between  $V_s$  &  $V_o$

$g_m = \frac{I_{CQ}}{V_T} = \frac{1\text{ mA}}{26\text{ mV}} = 39\text{ mA/V}$

$r_o = \frac{V_A}{I_{CQ}} = \frac{100\text{ V}}{1\text{ mA}} = 100\text{ k}\Omega$

$R'_L = 100 \parallel 5 \parallel 20\text{ k}$   
 $= 100 \parallel 4\text{ k} = 3.9\text{ k}\Omega$



• CH6

Tuesday

19.7.2016

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26 \text{ mV}}{1 \text{ mA}} = 2.6 \text{ k}\Omega$$

$$A_V = \frac{-39 (3.9 \text{ k}) \cdot 2.6}{(2.6 + 230) \text{ k}}$$

$$\frac{V_o}{V_s} = -1.6$$

$$V_o = -1.6 V_s$$

Another way :-  $\frac{V_o}{V_s} = \frac{V_o}{V_{\pi}} \times \frac{V_{\pi}}{V_s}$  صانعة بنظر

$$A_I = \frac{I_o}{I_s} = \frac{I_o}{I_b} \times \frac{I_b}{I_s}$$

$$I_o = -\beta I_b \frac{R_c'}{R_c' + R_L}$$

$$\frac{I_o}{I_b} = \frac{-\beta R_c'}{R_c' + R_L}$$

$$I_b = I_s \Rightarrow \frac{I_b}{I_s} = 1$$

$$\therefore A_I = \frac{-\beta R_c'}{R_c' + R_L} \cdot 1, \text{ where } R_c' = R_c \parallel r_o = 5 \parallel 100 \text{ k} = 4.8 \text{ k}\Omega$$

$$A_I = \frac{-100 (4.8)}{4.8 + 20} = -20$$

$$\frac{I_o}{I_s} = -20$$

$$I_o = -20 I_s$$

CH6

Tuesday

19.7.2016


$$R_i = \frac{V_s}{I_s}$$

$$-V_s + I_s R_B + I_s r_{\pi} = 0$$

$$V_s = I_s (R_B + r_{\pi})$$

$$R_i = \frac{V_s}{I_s} = R_B + r_{\pi} = 232.6 \text{ k}\Omega.$$

$$R_o = \frac{V_x}{I_x} \Big|_{V_s=0}$$

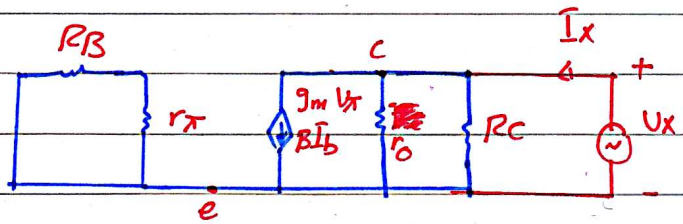

Kcl at C node:


$$I_x = \cancel{g_m V_{\pi}} + \frac{V_x}{R_c} + \frac{V_x}{r_o}$$

When  $V_s=0 \Rightarrow V_{\pi}=0$ 

$$I_x = V_x \left( \frac{1}{R_c} + \frac{1}{r_o} \right)$$

$$\frac{I_x}{V_x} = \frac{1}{R_c} + \frac{1}{r_o} = \frac{1}{R_o}$$

$$R_o = r_o \parallel R_c$$

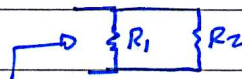

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_{eq} = R_1 \parallel R_2$$

$$R_o = 5 \parallel 100 \text{ k} = 4.8 \text{ k}\Omega.$$




Single stage BJT Amp.  
BJT Configuration. (Connection)


1) Common-Emitter Amp.

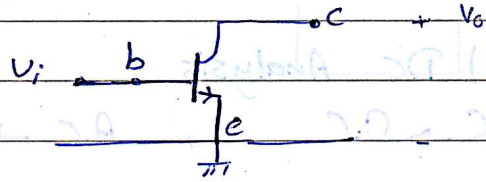

2) Common-Collector Amp.

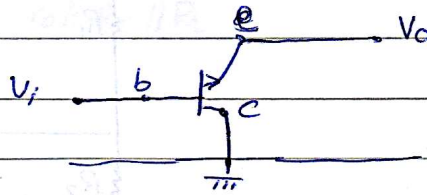

3) Common-Base Amp.

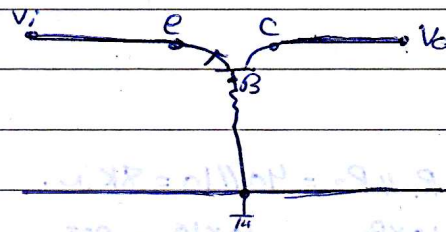


① C.E. Amplifier.

E - Common Terminal.

Vi to base

Vo from C

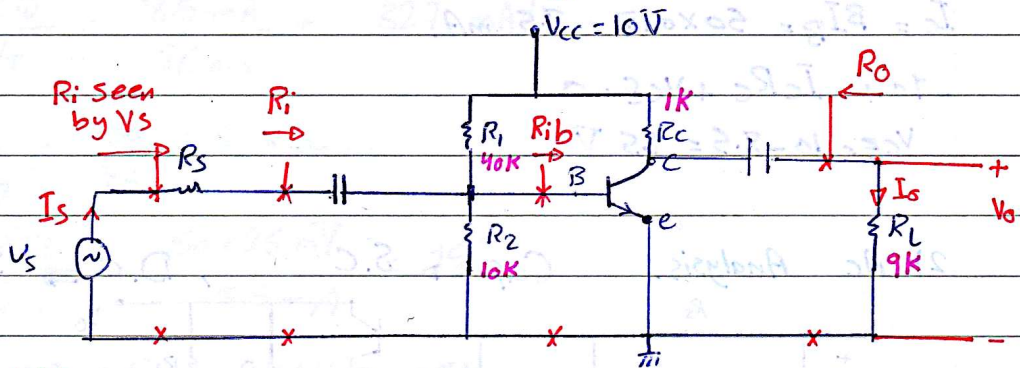① Basic C.E. Amp. (E is directly connected to the ground).



$V_{BE} = 0.6 \text{ V}$

$\beta = 50$


$V_A = 50 \text{ V}$



- 1) Calculate  $I_{CQ}$ ,  $V_{CEQ}$ .
- 2) Draw S.S.A.C equivalent cct & find  $A_v, A_i, R_o, R_i, R_{ib}$ ,  $R_i$  seen by  $V_s$ .

1) DC Analysis

C → O.C, A.C → S.C

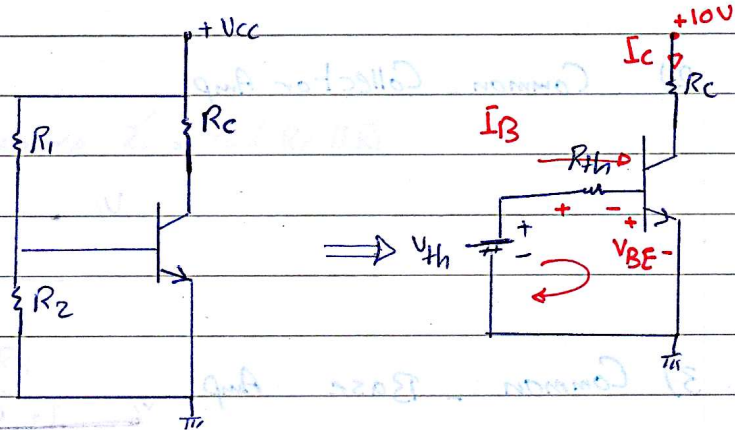

$$R_{th} = R_1 \parallel R_2 = 40 \parallel 10 = 8 \text{ k}\Omega$$

$$V_{th} = \frac{10 \times R_2}{R_1 + R_2} = \frac{10 \times 10}{50} = 2 \text{ V}$$

Assume the BJT in F.A.M.:

$$-V_{th} + I_B R_{th} + V_{BE} = 0$$


$$I_B = \frac{2 - 0.6}{8 \text{ k}} = 0.17 \text{ mA}$$

$$I_C = \beta I_B = 50 \times 0.17 = 8.5 \text{ mA}$$

$$-10 + I_C R_C + V_{CE} = 0$$


$$V_{CE} = 10 - 8.5 = 1.5 \text{ V}$$

2) AC Analysis. Cap → S.C, D.C → S.C

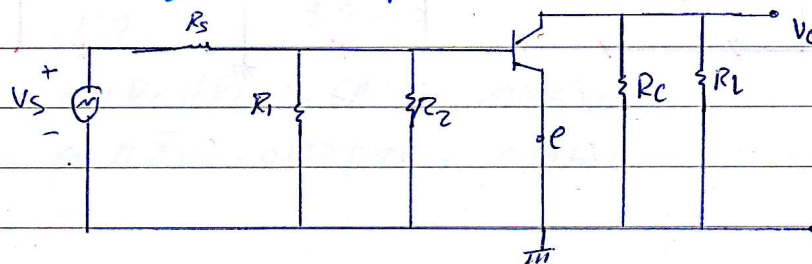

CH6


Wednesday 20.7.2016

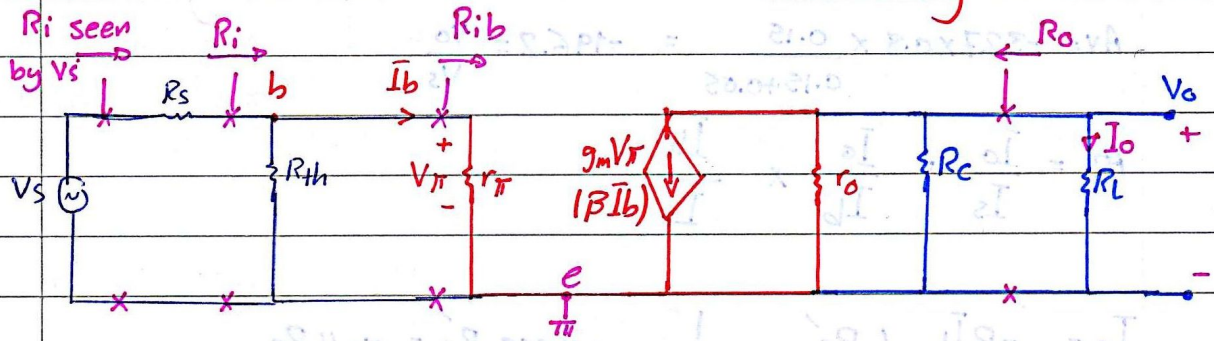

$$A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{\pi}} \times \frac{V_{\pi}}{V_s}$$

$$V_o = -g_m V_{\pi} R'_L, \text{ where } R'_L = r_o \parallel R_c \parallel R_L$$

$$\frac{V_o}{V_{\pi}} = -g_m R'_L$$

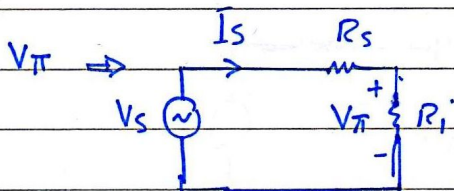

$$V_{\pi} = \frac{V_s R_i}{R_i + R_s} \quad (\text{VDR})$$

$$\frac{V_{\pi}}{V_s} = \frac{R_i}{R_i + R_s}$$

$$A_v = -g_m R'_L \frac{R_i}{R_i + R_s}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{8.5 \text{ mA}}{26 \text{ mV}} = 327 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{50}{8.5} = 6 \text{ k}\Omega$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{50 \times 26 \text{ mV}}{8.5 \text{ mA}} = 153 \mu\Omega$$

$$R'_L = r_o \parallel R_c \parallel R_L = 6 \parallel 1 \parallel 9 = 0.8 \text{ k}\Omega$$

$$R_i = r_{\pi} \parallel R_{Th} = 0.153 \parallel 8 \text{ k} = 0.15 \text{ k}\Omega$$



$$A_v = \frac{-327 \times 0.8 \times 0.15}{0.15 + 0.05} = -196.2 = \frac{V_o}{V_s}$$

$$A_I = \frac{I_o}{I_s} = \frac{I_o}{I_b} \times \frac{I_b}{I_s}$$

$$I_o = -\beta I_b \left( \frac{R_c'}{R_c' + R_L} \right), \text{ where } R_c' = r_o \parallel R_c$$

→ CDR

$$\frac{I_o}{I_b} = \frac{-\beta R_c'}{R_c' + R_L}$$

$$I_b = \frac{I_s R_{th}}{R_{th} + r_{\pi}}$$

$$\frac{I_b}{I_s} = \frac{R_{th}}{R_{th} + r_{\pi}}$$

$$A_I = \frac{-\beta R_c'}{R_c' + R_L} \cdot \frac{R_{th}}{R_{th} + r_{\pi}}$$

$$R_c' = r_o \parallel R_c = 6 \parallel 1 = 0.857 \text{ k}\Omega$$

$$A_I = \frac{-50 \times 0.85}{0.85 + 9} \times \frac{8}{8 + 0.153} = -4.2$$

$$R_{ib} = r_{\pi} = 0.153 \text{ k}\Omega$$


$$R_i = R_{th} \parallel R_{ib} = 8 \parallel 0.153 = 0.15 \text{ k}\Omega$$

$$R_i \text{ seen by } V_s = R_s + R_i = 0.05 + 0.15 = 0.2 \text{ k}\Omega$$

$$R_o = \frac{V_x}{I_x} \Big|_{V_s=0}$$

when  $V_s = 0 \Rightarrow V_{\pi} = 0$   
 $\therefore g_m V_{\pi} = 0 \Rightarrow$  The dep. C.S is Open
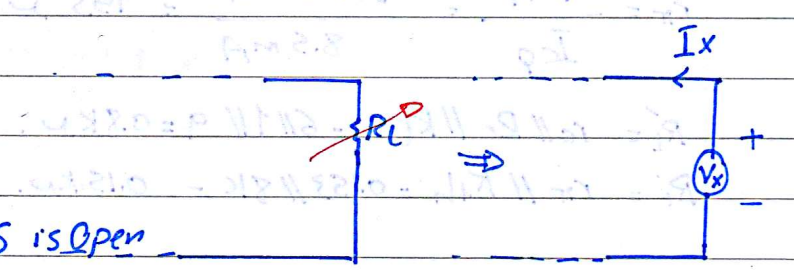
$$\text{So } R_o = r_o \parallel R_c = 0.857 \text{ k}\Omega$$






AI in terms of  $A_V$ :-

$$A_I = \frac{I_o}{I_s} = \frac{V_o / R_L}{V_s / (R_s + R_i)} = \frac{V_o}{V_s} \left( \frac{R_s + R_i}{R_L} \right) = A_V \frac{R_s + R_i}{R_L}$$


$A_V$  in terms of  $A_I$ :-

$$A_V = \frac{V_o}{V_s} = \frac{I_o \times R_L}{I_s (R_s + R_i)} = A_I \frac{R_L}{R_s + R_i}$$

A.c Load Line.

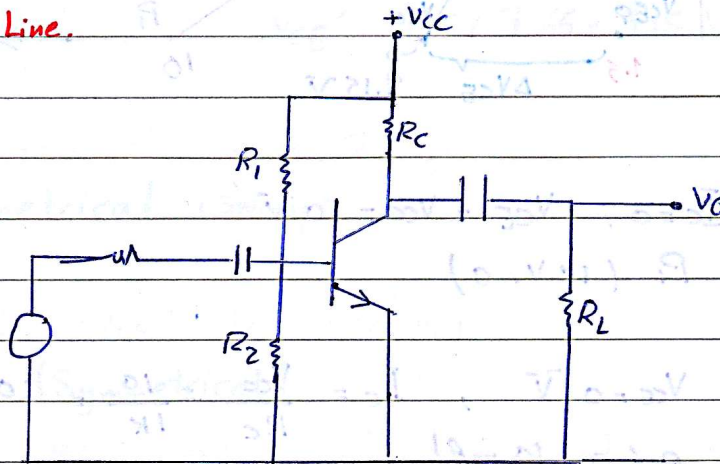

D.C.L.L

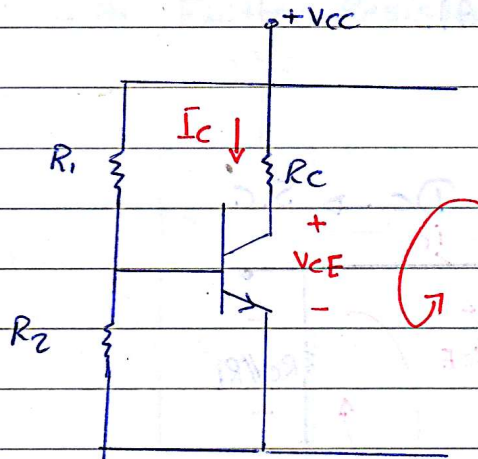


$$-V_{CC} + I_C R_C + V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C \Rightarrow \textcircled{1} \text{ D.C.L.L eq.}$$

or

$$I_C = \frac{V_{CC}}{R_C} - \frac{V_{CE}}{R_C} \Rightarrow \textcircled{2}$$

$$y = b + mx$$

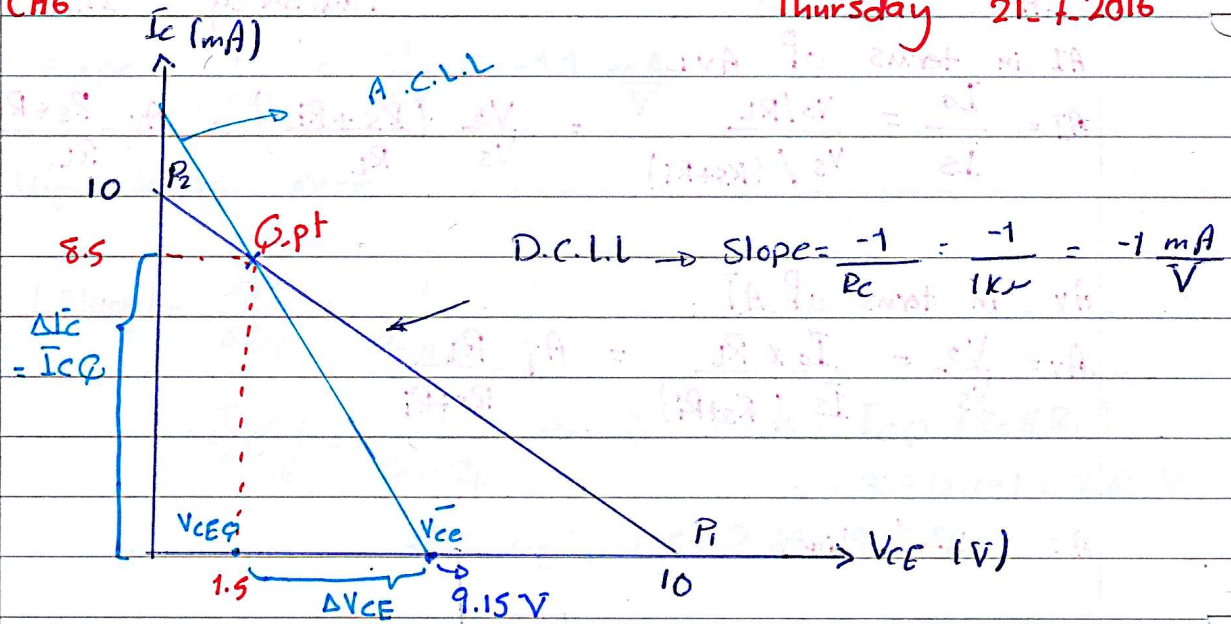


(i) For  $I_c = 0$ ,  $V_{ce} = V_{cc} = 10 \text{ V}$   
 $P_1 (10 \text{ V}, 0)$

(ii) For  $V_{ce} = 0 \text{ V}$ ,  $I_c = \frac{V_{cc}}{R_c} = \frac{10}{1k} = 10 \text{ mA}$   
 $P_2 (0, 10 \text{ mA})$

Q-pt (1.5 V, 8.5 mA)

A.C.L.L. →

For Ac, C → S.C, DC → S.C

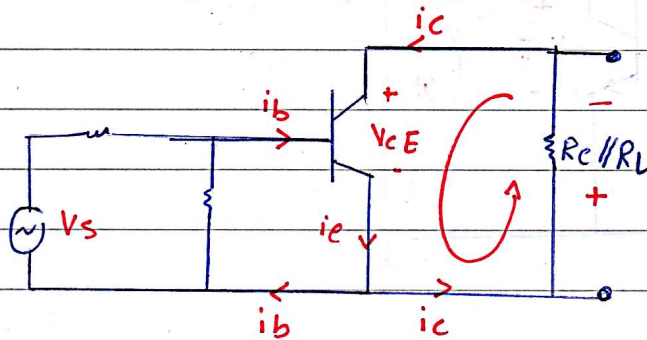

$$V_{ce} = -i_c (R_c \parallel R_L)$$

$$\text{Slope} = \frac{-1}{(R_c \parallel R_L)}$$

A.C.L.L & D.C.L.L intersects at Q-pt.



CH6

Thursday 21.7.2016

$$\text{slope} = \frac{-1}{(1119)} = \frac{-1}{0.9} = -1.1 \frac{\text{mA}}{\text{V}}$$

1st exam

$$V_{CE}' = V_{CEQ} + \Delta V_{CE}$$

118

Monday

$$|\text{slope}| = \frac{\Delta I_C}{\Delta V_{CE}} = \frac{1}{R_C \parallel R_L}$$

$$\frac{I_{CQ}}{\Delta V_{CE}} = \frac{1}{R_C \parallel R_L} \Rightarrow \Delta V_{CE} = I_{CQ} (R_C \parallel R_L) = 8.5(1119) = 7.65 \text{ V}$$

$$V_{CE}' = 1.5 + 7.65 = 9.15 \text{ V}$$


peak\_Symmetrical Output Voltage.  
peak\_Symmetrical (Swing)

$$V_{cep} (\text{max}) = \Delta V_{CE} = I_{CQ} (R_C \parallel R_L)$$

peak\_peak (Symmetrical)

$$\text{Output Voltage} = 2 \Delta V_{CE} = 2 I_{CQ} (R_C \parallel R_L)$$

(ii) C.E with Emitter Resistor  $R_E$ .

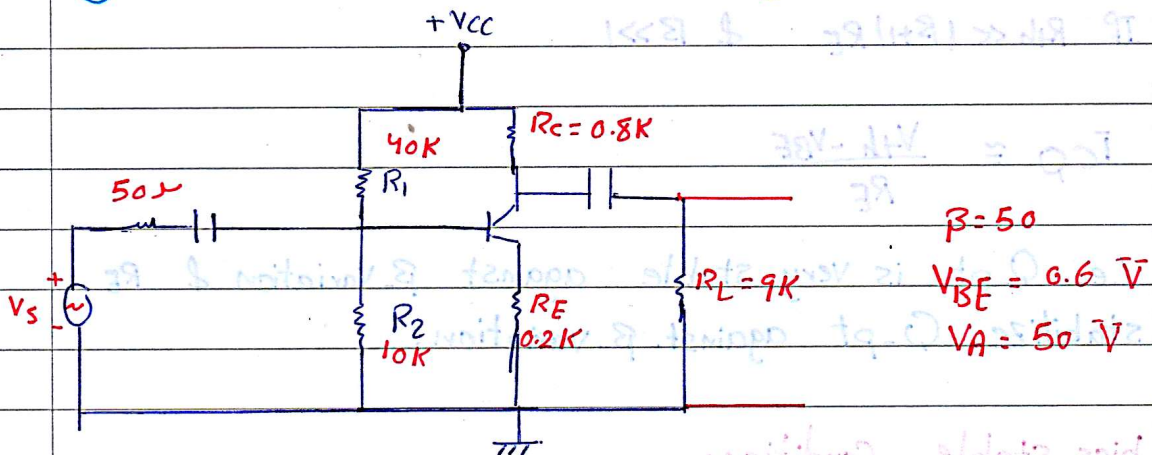


1) Find  $I_{CQ}$ ,  $V_{CEQ}$ .

2) Draw A.C eqnt cct & find  $A_v$ ,  $A_i$ ,  $R_{ib}$ ,  $R_i$

1) D.C Analysis : c  $\rightarrow$  O.C , A.C  $\rightarrow$  S.C

$$V_{th} = \frac{10 \times 10}{50} = 2V$$

$$R_{th} = 10 \parallel 40 = 8K\Omega$$

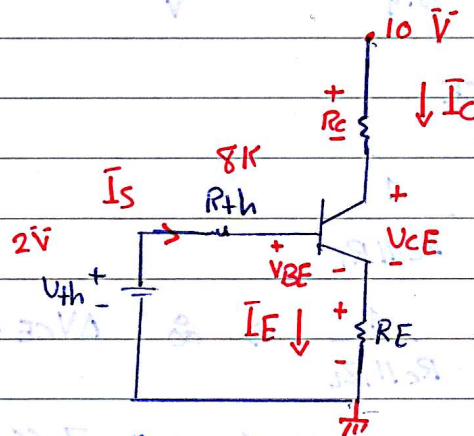

$$-V_{th} + R_{th} I_B + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E} = I_{BQ}$$

$$I_C = \beta I_B = \frac{\beta (V_{th} - V_{BE})}{R_{th} + (\beta + 1) R_E}$$

$$\text{If } R_{th} \ll (\beta + 1) R_E \text{ \& } \beta \gg 1$$

$$I_{CQ} \approx \frac{V_{th} - V_{BE}}{R_E}$$

i.e. Q pt is very stable against  $\beta$  variation &  $R_E$  stabilize Q pt against  $\beta$  variation.

bias stable condition:

$$R_{th} = 0.1 (\beta + 1) R_E$$

To check:

$$R_{th} \leq 0.1 (\beta + 1) R_E$$




$$I_B = \frac{(2 - 0.6)}{8 + 51 \times 0.2} = \frac{1.4 \text{ V}}{9 \text{ K}} = 0.077 \text{ mA} = I_{BQ}$$

$$I_{CQ} = \beta I_B = 3.85 \text{ mA}$$

$$I_{EQ} = (\beta + 1) I_B = 3.93 \text{ mA}$$

$$-10 + I_C R_C + V_{CE} + I_E R_E = 0$$
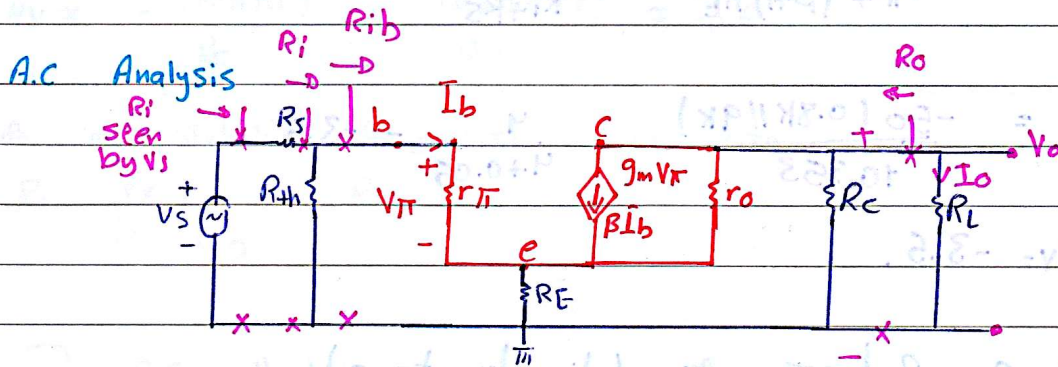
$$V_{CE} = 10 - 3.85 \times 0.8 - 3.93 \times 0.2 = 6.1 \text{ V}$$




$$A_v = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s}$$

Neglecting the effect of  $r_o$

$$V_o = -\beta I_b (R_L \parallel R_C)$$

$$V_i = V_{\pi} + V_e = I_b r_{\pi} + (\beta + 1) I_b R_E = I_b (r_{\pi} + (\beta + 1) R_E)$$
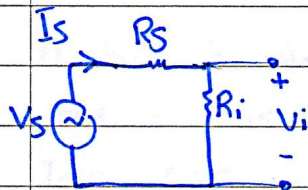
$$\frac{V_o}{V_i} = \frac{-\beta (R_L \parallel R_C)}{r_{\pi} + (\beta + 1) R_E}$$



$$\frac{V_i}{V_s} = \frac{R_i}{R_i + R_s}, \text{ where } R_i = R_{th} \parallel R_{ib}$$

$$R_{ib} = \frac{V_i}{I_b} = \frac{-\beta (r_{\pi} + (\beta + 1) R_E)}{-\beta} = r_{\pi} + (\beta + 1) R_E$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{50 \times 26 \text{ mV}}{3.85 \text{ mA}} = 338 \Omega$$

$$R_{ib} = 0.338 + 51 \times 0.2 = 10.353 \text{ k}\Omega$$

$$R_i = 8 \parallel 10.353 = 4 \text{ k}\Omega$$


$$A_v = \frac{-\beta (R_c \parallel R_L)}{r_{\pi} + (\beta + 1) R_E} \frac{R_i}{R_i + R_s}$$

$$= \frac{-50 (0.8 \text{ k}\Omega \parallel 9 \text{ k}\Omega)}{10.353} \frac{4}{4 + 0.05} = -3.5$$

$$A_v = -3.5$$

∞  $R_E$  Reduces  $A_v$  (disadvantage)

∞  $R_E$  increases  $R_i$  (advantage)

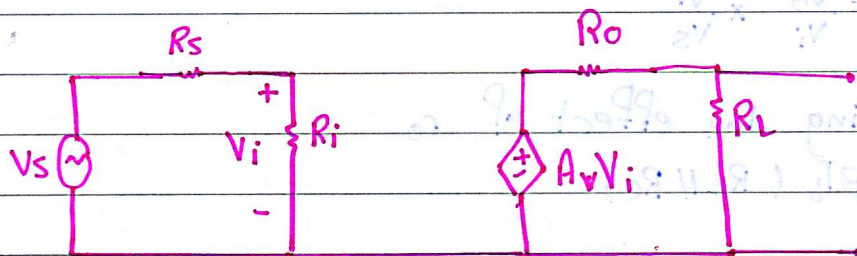

$$V_i = \frac{V_s R_i}{R_i + R_s}, \quad V_o = \frac{A_v V_i R_L}{R_L + R_o}$$

As  $R_i \uparrow$  and  $R_o \downarrow$  the Amp becomes close to ideal voltage.

$R_i = \infty$   
 $R_o = 0$  } ideal voltage Amp.

$$A_I = \frac{I_o}{I_s} = \frac{V_o}{R_L} \Big/ \frac{V_s}{R_s + R_i}$$

$$A_I = A_v \frac{R_s + R_i}{R_L}$$



CHG

Sunday 24.7.2016

so  $R_E$  increase  $A_I$  (Advantage).

$$= -4 \left( \frac{0.05 + 10.3}{9} \right) = -4.5$$

$$A_v = \frac{-\beta(R_C \parallel R_L)}{(\beta+1)R_E} \cdot \frac{R_i}{R_i + R_S} = -3.5$$


For  $R_i \gg R_S$  &  $(\beta+1)R_E \gg r_{\pi}$ ,  $\beta+1 \gg 1$

$$A_v \approx \frac{-(R_C \parallel R_L)}{R_E} \approx \frac{(0.8K \parallel 9K)}{0.2} \approx -3.6$$

so  $R_E$  stabilize  $A_v$  against  $\beta$  variation.

$$R_o = \left. \frac{V_x}{I_x} \right|_{V_s=0} = R_C$$

(iii) C.E with bypass Cap. CE

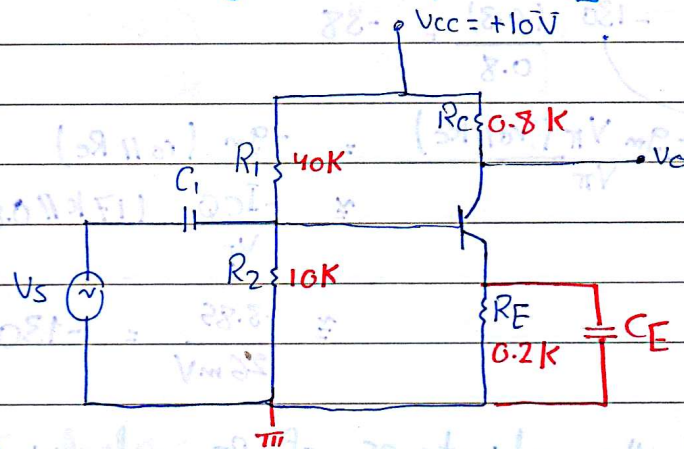

$$\beta = 50$$

$$V_{BE} = 0.6V$$

$$V_A = 50V$$


1) Find  $I_{CQ}$ ,  $V_{CEQ}$ .

2) Draw S.S.A.C cct & find  $A_v$ ,  $A_I$ ,  $R_i$ ,  $R_o$ .

1) For DC Analysis, C  $\rightarrow$  O.C, A.C  $\rightarrow$  S.C  
the cct is analyzed as C.E with  $R_E$ .

$$I_{CQ} = 3.85 \text{ mA}$$



$$V_{CEQ} = 6.1V$$

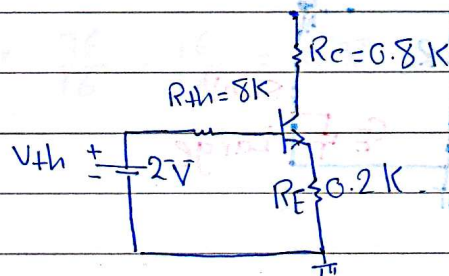

2) For A.C Analysis :-

C, CE → S.C

Dc → S.C

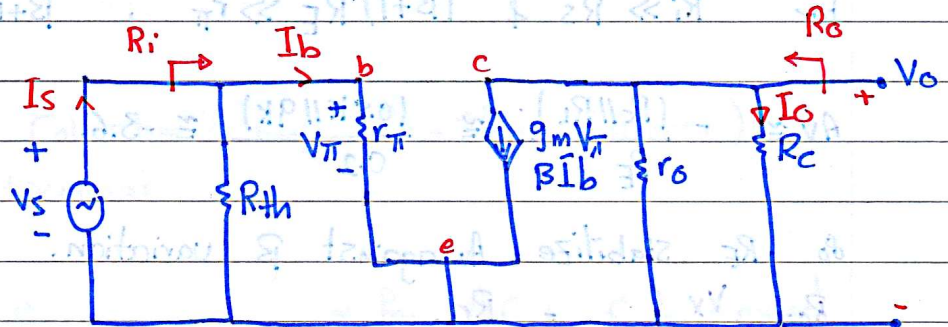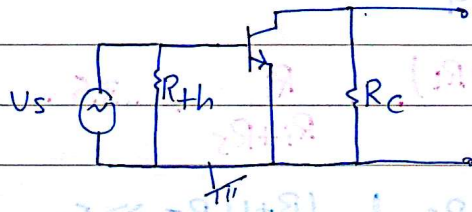

$$R_i = r_{\pi} \parallel R_{Th} = 338 \parallel 8k = 325 \Omega$$

$$R_o = R_c \parallel r_o \approx 0.8 k\Omega$$


$$A_I = A_V \frac{R_i}{R_c} = \frac{-130 (0.3)}{0.8} = -38$$

$$A_V = \frac{V_o}{V_s} = \frac{-g_m V_{\pi} (r_o \parallel R_c)}{V_{\pi}} = -g_m (r_o \parallel R_c)$$

$$\approx \frac{-I_{CQ}}{V_T} (17k \parallel 0.8)$$

$$\approx \frac{-3.85}{26 mV} = -130$$

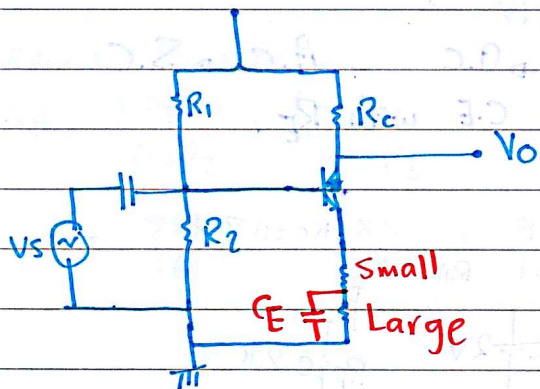\* To gain all the advantages of RE and minimize disadvantages, RE is made of two parts (Small RE & Large RE) then short out large RE with bypass cap (CE).



gain back depends on Dc



Basic C.E →

- 1)  $A_v > 1$
- 2)  $A_i > 1$
- 3)  $R_o$  moderate to high
- 4)  $R_i$  moderate to high.
- 5) phase shift =  $180^\circ = \phi$


2) Common Collector Amp (Emitter Follower)

C → Common terminal.

$V_i$  → Base

$V_o$  → From e

\* For A.C: c → ground.

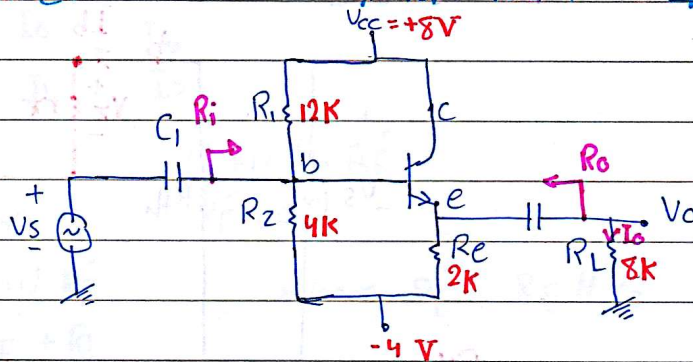


$\beta = 49, V_A = 50V, V_{BE} = 0.7V$

- 1) Find  $I_{CQ}, V_{CEQ}$ .
- 2) Draw s.s.A.C eqnt cct & find  $A_v, A_i, R_i, R_o$

1) D.C Analysis

c → D.C, A.C → S.C

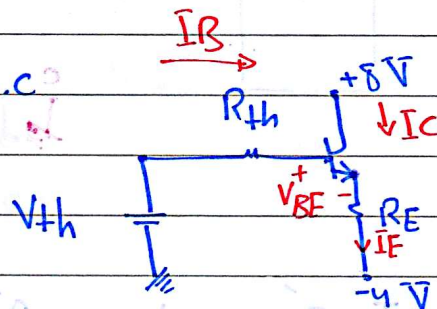

$R_{th} = R_1 || R_2 = 3k\Omega$

$V_{th} = \frac{8R_2}{R_1 + R_2} + \frac{(-4)R_1}{R_1 + R_2}$

$= \frac{8 \times 12}{16} - \frac{4 \times 4}{16} = \frac{96}{16} - \frac{16}{16} = 5V$

$$-V_{th} + I_B R_{th} + V_{BE} + (\beta + 1) I_B R_E - 4 = 0$$

$$I_B = \frac{5 + 4 - 0.7 \text{ V}}{R_{th} + 50 \times 2} = \frac{8.3}{103 \text{ k}} = 0.08 \text{ mA}$$


$$I_{CQ} = \beta I_B = 0.08 \times 49 \approx 4 \text{ mA}$$

$$-8 + V_{CE} + I_E R_E - 4 = 0$$

$$V_{CE} = 12 - (50 \times 0.08) \times 2 = 4 \text{ V}$$

2) A.C Analysis.

c → S.C      D.C → S.C

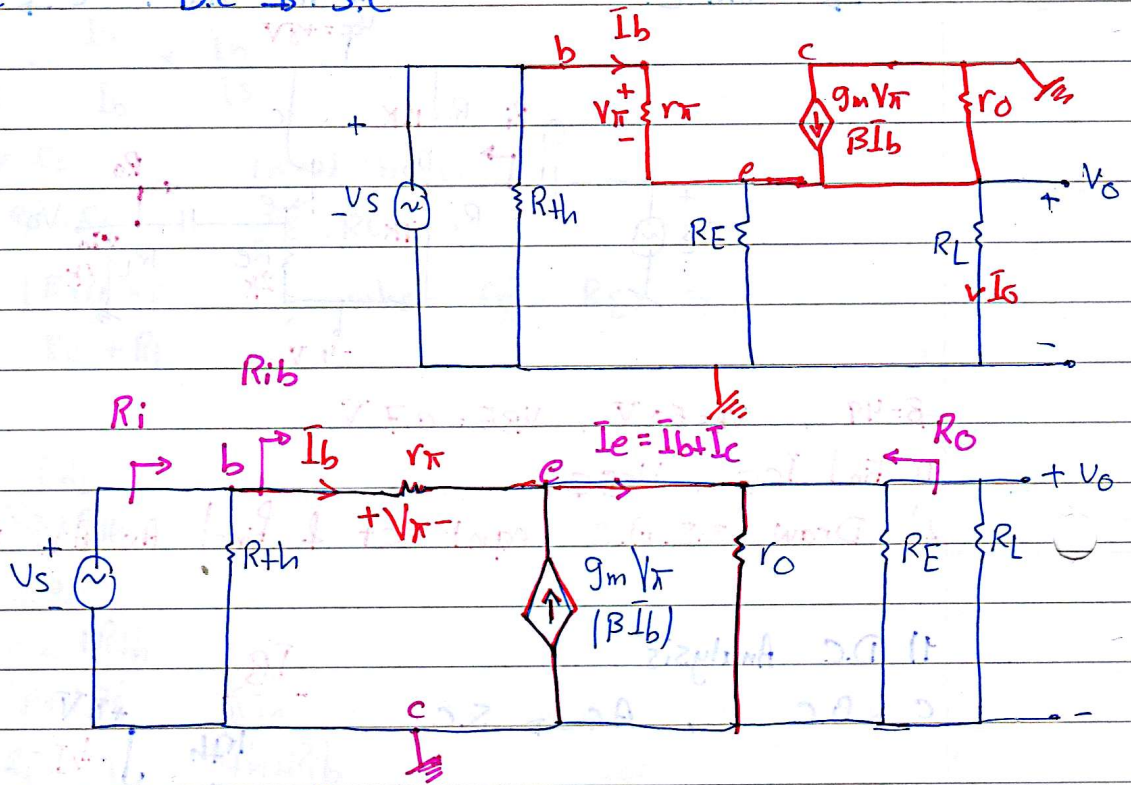

$$A_V = \frac{V_o}{V_s}$$

$$V_o = (\beta + 1) I_b R_L', \text{ where } R_L' = r_o \parallel R_E \parallel R_L$$

$$-V_s + V_{\pi} + V_o = 0$$

$$V_s = I_b r_{\pi} + (\beta + 1) I_b R_L'$$

$$A_V = \frac{(\beta + 1) R_L'}{r_{\pi} + (\beta + 1) R_L'} < 1 \quad \text{because: } -V_s + V_{be} + V_o = 0$$

$$V_o = V_s - V_{be}$$

1)  $A_V < 1$     2)  $\phi = 0$

$V_o$  always less than  $V_s$



For  $(\beta+1)R_i' \gg r_\pi$  &  $\beta \gg 1$   
 $A_v \approx 1 = \frac{V_o}{V_s} \rightarrow V_s = V_o$

i.e.  $V_o$  follows  $V_s$  in magnitude and sign, and since  $V_o$  is taken from Emitter so it is called (Emitter Follower).

$R_i = R_{th} \parallel R_{ib}$

$R_{ib} = \frac{V_i}{I_b} = \frac{V_\pi + V_o}{I_b} = \frac{I_b r_\pi + (\beta+1)I_b R_i'}{I_b}$

$R_{ib} = r_\pi + (\beta+1)R_i'$

$A_I = \frac{I_o}{I_s} = \frac{I_o}{I_b} \times \frac{I_b}{I_s}$

$I_o = \frac{I_e R_E}{R_E + R_L} = \frac{(\beta+1)I_b R_E}{R_E + R_L}$

$\frac{I_o}{I_b} = \frac{(\beta+1)R_E}{R_E + R_L}$ , where  $R_E = R_E \parallel r_o$

$I_b = I_s \frac{R_{th}}{R_{ib} + R_{th}}$


$\frac{I_b}{I_s} = \frac{R_{th}}{R_{ib} + R_{th}}$

$\therefore A_I = \frac{(\beta+1)R_E}{R_E + R_L} \frac{R_{th}}{R_{th} + R_{ib}}$

IF  $R_E \gg R_L$  &  $R_{th} \gg R_{ib}$

$A_I(\max) \approx (\beta+1)$

$R_o = \frac{V_x}{I_x} \Big|_{V_s=0}$

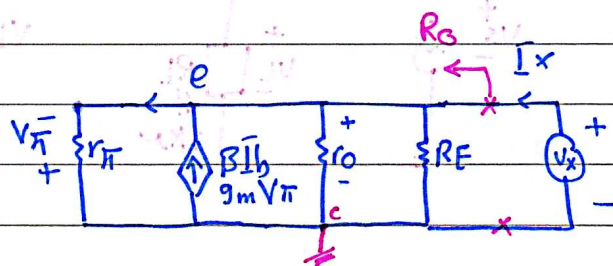

KCL at node e

$$I_x + g_m V_{\pi} = \frac{V_x}{r_{\pi}} + \frac{V_x}{R_E} + \frac{V_x}{r_o}$$

but when  $V_S = 0$ 

$$V_{\pi} = -V_x$$

$$\bar{I}_x = g_m V_x + \frac{V_x}{r_{\pi}} + \frac{V_x}{R_E} + \frac{V_x}{r_o}$$

$$\frac{\bar{I}_x}{V_x} = g_m + \frac{1}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{r_o} \rightarrow g_m r_{\pi} = \frac{I_{CQ} \beta V_T}{V_T I_{CQ}} = \beta$$


$$\frac{\bar{I}_x}{V_x} = \frac{\beta + 1}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{r_o}$$

$$\text{so } \frac{1}{R_o} = \frac{\beta + 1}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{r_o}$$

$$R_o = \frac{r_{\pi}}{\beta + 1} \parallel R_E \parallel r_o$$

1)  $A_v < 1$ 2)  $\phi = 0^\circ$ 3)  $A\bar{I} = 1$ 4)  $R_o \rightarrow$  Low5)  $R_i \rightarrow$  High.

Emitter Follower is used to minimize a loading effect (solve the problem of loading effect).

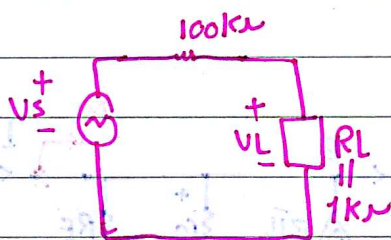Let  $V_S = 10$  Simult

$$V_L = \frac{V_S R_L}{R_S + R_L} = \frac{V_S}{100 + 1} \approx 0.01 V_S$$


sever loading effect.



CH6

Monday 25.7.2016

but when we use Emitter Follower

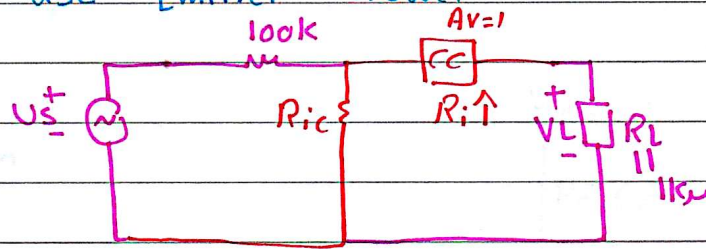

$$V_i = \frac{V_s R_{ic}}{R_{ic} + R_s}$$

but  $R_{ic} \gg R_s$

$$V_i \approx V_s$$

$$V_L = V_i \quad (A_v = 1 = \frac{V_L}{V_i})$$

$$\& \quad V_L = V_i = V_s = 10 \sin \omega t$$


(No loading effect).

3) Common Base Amp. (C.B)

B → Common

$V_i$  → Emitter

$V_o$  → From C

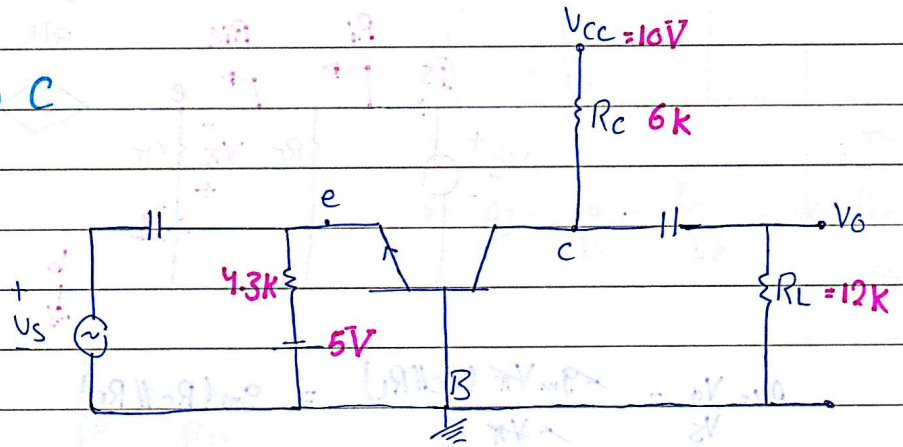


$\beta = 100$  ,  $V_{BE} = 0.7V$  ,  $V_A = \infty$

1) Find  $I_{CQ}$  ,  $V_{CEQ}$

2) Draw S.S.A.C eqnt cct & Find  $A_v$ ,  $A_i$ ,  $R_i$ ,  $R_o$

1) D.C Analysis

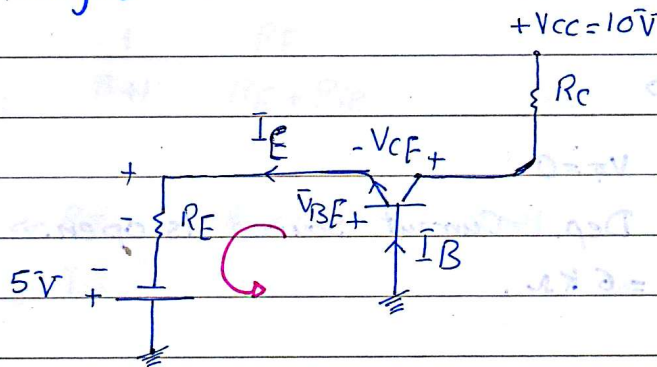

$$V_{BE} + I_E R_E - 5 = 0 \rightarrow I_E = \frac{5 - 0.7}{4.3k} = 1 \text{ mA}$$

$$I_C = \alpha I_E = \frac{100}{101} \times 1 = 0.99 \text{ mA}$$

$$-10 + I_C R_C + V_{CE} + I_E R_E - 5 = 0$$


$$V_{CE} = 15 - I_C R_C - I_E R_E = 15 - 0.99 \times 6 - 1 \times 4.3 = 4.76 \text{ V}$$

$$V_{CE} = 4.76 \text{ V}$$



2) Ac Analysis :-

C → S.C , D.C → S.C

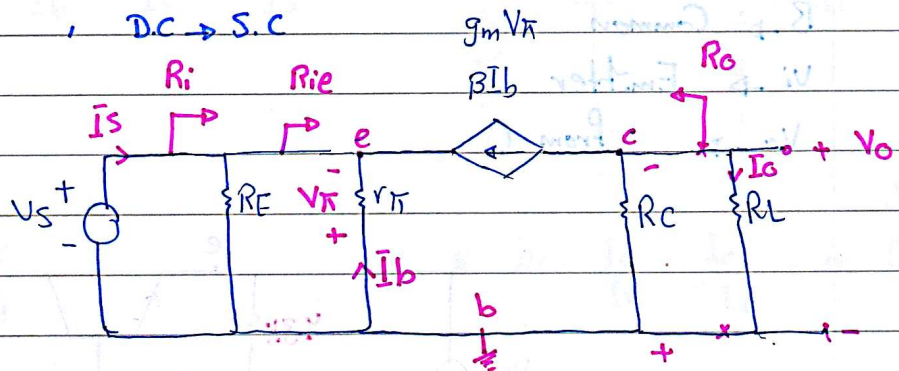

$$A_V = \frac{V_o}{V_s} = \frac{-g_m V_\pi (R_C \parallel R_L)}{-V_\pi} = g_m (R_C \parallel R_L)$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.99 \text{ mA}}{2.6 \text{ mV}} = 40 \text{ mA/V}$$

$$A_V = 40 \times (6 \parallel 10)$$

1)  $A_V > 1$  , 2)  $\phi = 0^\circ$

$$R_o = \frac{V_x}{I_x} \Big|_{V_s=0}$$

When  $V_s = 0$  ,  $V_\pi = 0$

$g_m V_\pi = 0 \rightarrow$  Dep. Current source is open.

$$R_o = R_C = 6 \text{ k}\Omega$$

$$R_i = R_E \parallel R_{ie}$$

$$R_{ie} = \frac{-V_\pi}{I} = \frac{-V_\pi}{-I_e} = \frac{V_\pi}{I_e} = \frac{I_b r_\pi}{(\beta+1)I_b} = \frac{r_\pi}{\beta+1}$$

$$R_{ie} = \frac{r_\pi}{\beta+1} \Rightarrow r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26}{0.99 \text{ mA}} = 2.65 \text{ k}\Omega$$


$$R_{ie} = \frac{2.65 \text{ k}}{101} = 26 \Omega$$

$$R_i = 4.3 \text{ k} \parallel 26 \Omega \approx 25 \Omega \quad \infty \quad 3) R_i \rightarrow \text{Low}$$

CH6

Tuesday 26.7.2016
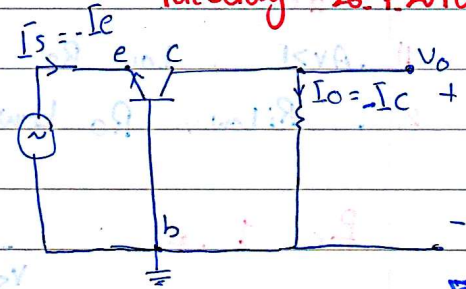
$$A_I = \frac{I_o}{I_s} = \frac{I_o}{I_b} \cdot \frac{I_b}{I_e} \cdot \frac{I_e}{I_s}$$




$$I_o = \frac{-\beta I_b R_C}{R_C + R_L}$$

$$\frac{I_o}{I_b} = \frac{-\beta R_C}{R_C + R_L}$$

$$* A_I = \frac{I_o}{I_s} = \frac{-I_c}{-I_e} = \alpha \text{ , for this cct}$$
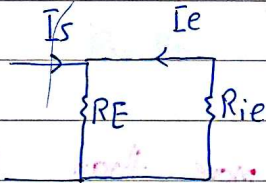
$$I_e = (\beta + 1) I_b \rightarrow \frac{I_b}{I_e} = \frac{1}{\beta + 1}$$



$$I_e = \frac{-I_s R_E}{R_E + R_{ie}}$$

$$\frac{I_e}{I_s} = \frac{-R_E}{R_E + R_{ie}}$$

$$A_I = \frac{\beta R_C}{R_C + R_L} \cdot \frac{1}{\beta + 1} \cdot \frac{R_E}{R_E + R_{ie}}$$

For  $R_{ie} \ll R_E$  ,  $R_L \ll R_C$  ;  $\beta \gg 1$

$$A_I \approx 1 \rightarrow I_o = I_s$$

4)  $A_I < 1$  .  $R_o$  moderate to high.


Comparison of s.s. BJT Amp.

Amp	$A_v$	$A_I$	$\phi$	$R_i$	$R_o$
C.E	$> 1$	$> 1$	$180^\circ$	moderate	moderate to high
C.C	$< 1$	$> 1$	$0^\circ$	high	Low
C.B	$> 1$	$< 1$	$0^\circ$	Low	moderate to high




- 1)  $AV > 1$ , Low  $R_o$  } we will use multi stage.  
 2)  $R_i$  Low,  $R_o$  Low

For 1  $\rightarrow$

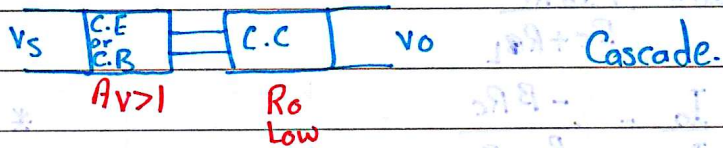

For 2  $\rightarrow$

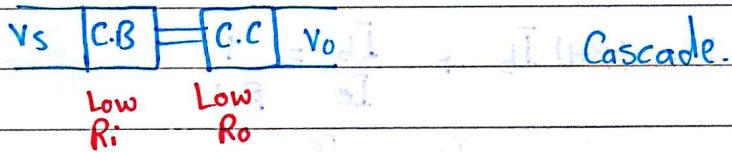

Multi-Stage BJT Amp:


They are ccts contain more than single stage (at least two stages) used to achieve certain specifications which can't be obtained from single stage.

Such as:

- 1)  $AV > 1$ , Low  $R_o$
- 2) Low  $R_i$ , Low  $R_o$
- 3) very high  $AV$  or  $AI$


There are two types

- 1) Cascade
- 2) Cascode

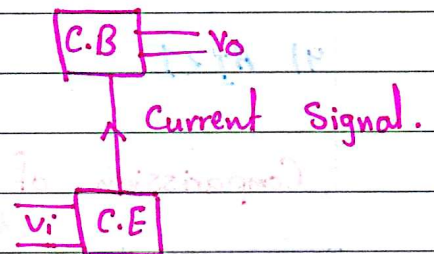

Multistage Amps


1) Cascade Multi-S

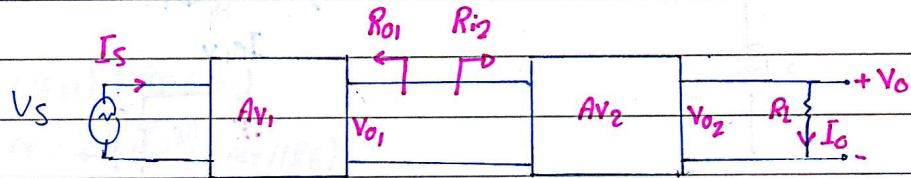

$$A_{VT} = \frac{V_o}{V_s}, \quad A_{IT} = \frac{I_o}{I_s}$$

$$R_i = R_{i1}, \quad R_o = R_{o2}$$

Ex

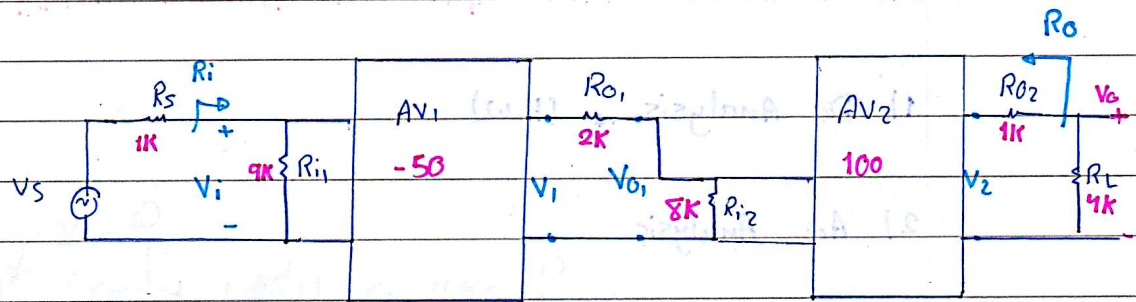

Calculate overall  $A_V, A_I, R_i, R_o$


$$R_i = R_{i1} = 9K, \quad R_o = R_{o2} = 1K$$

$$\begin{aligned} A_V &= \frac{V_o}{V_s} = \frac{V_o}{V_2} \cdot \frac{V_2}{V_{01}} \cdot \frac{V_{01}}{V_1} \cdot \frac{V_1}{V_i} \cdot \frac{V_i}{V_s} \\ &= \frac{R_L}{R_L + R_{o2}} \cdot A_{V2} \cdot \frac{R_{i2}}{R_{o1} + R_{i2}} \cdot A_{V1} \cdot \frac{R_{i1}}{R_{i1} + R_s} \\ &= \frac{4}{4+1} \cdot 100 \cdot \frac{8}{8+2} \cdot (-50) \cdot \frac{9}{9+1} = -2880 \end{aligned}$$

$$A_I = \frac{I_o}{I_s} = \frac{V_o / R_L}{V_s / (R_s + R_{i1})} = \frac{A_V \cdot R_s + R_{i1}}{R_L} = -2880 \left( \frac{1+9}{4} \right) = -2880 \times 2.5 = -7200$$



Exa.

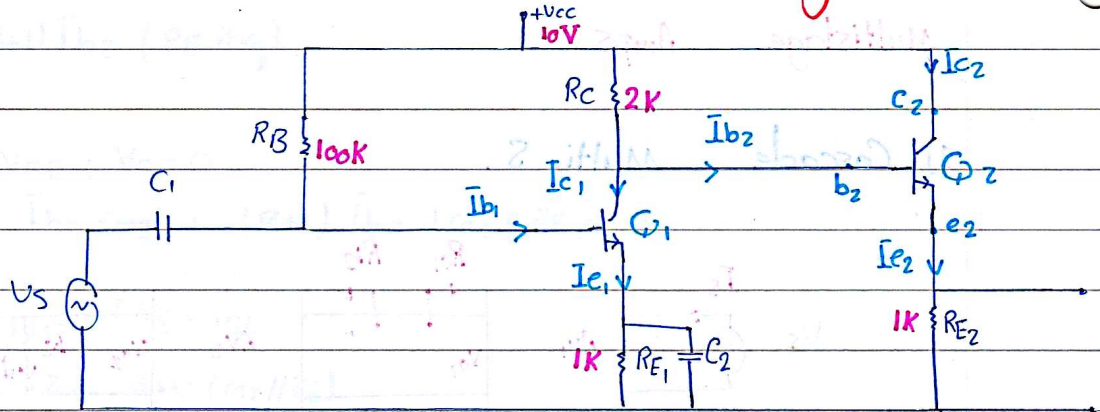


$\beta_1 = \beta_2 = 100$

$V_{A1} = V_{A2} = 100V$

- 1) Find  $I_{CQ1}, I_{CQ2}, V_{CEQ1}, V_{CEQ2}$
- 2) Draw S.S.A.C eqnt cct & Find  $A_v, A_i, R_i, R_o$

1) Dc Analysis → (H.W)

2) Ac Analysis

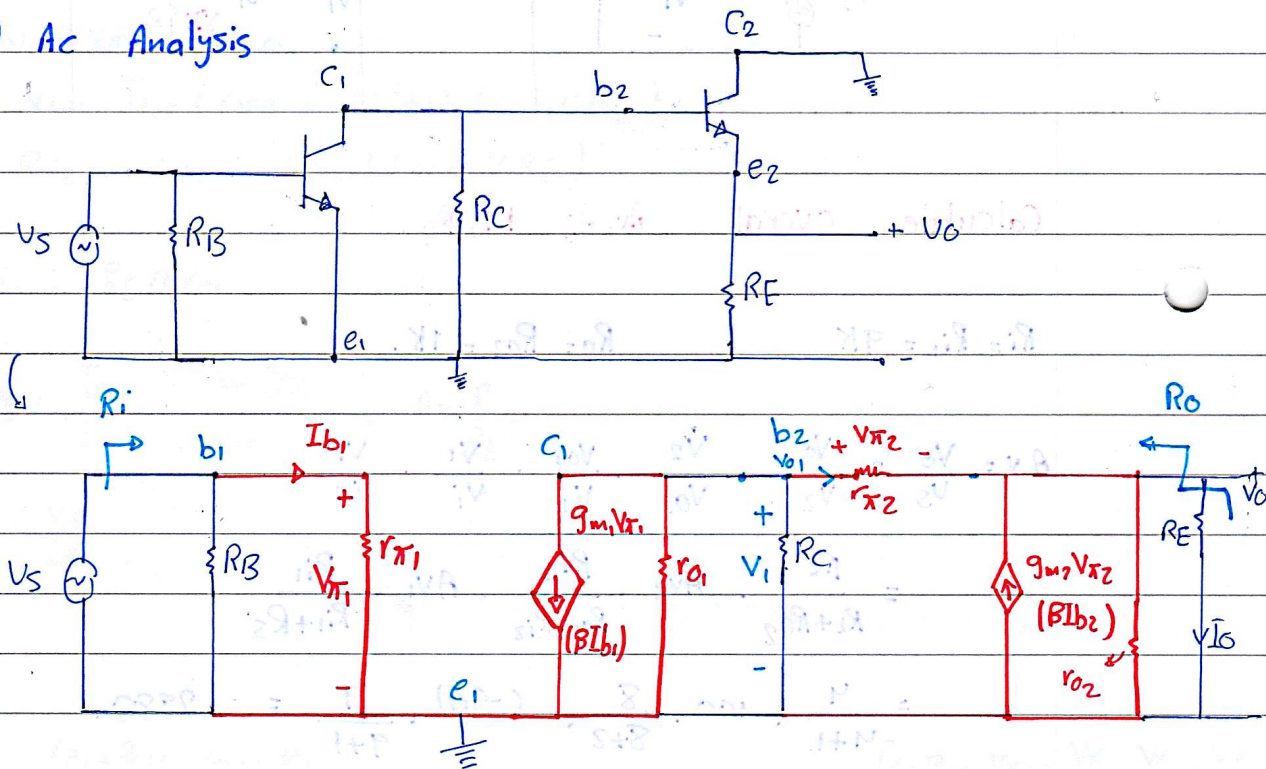

S.S.A.C eqnt cct:

$R_i(\text{input}) = (R_B \parallel r_{\pi 1})$

$A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{o1}} \cdot \frac{V_{o1}}{V_s}$

• Base Floating → Does not make The BJT in F.A.M.

CH6

wednesday 27.7.2016

$$V_o = (\beta + 1) \bar{I}_{b2} (R_E \parallel r_{o2})$$

$$-V_{o1} + V_{\pi 2} + V_o = 0$$

$$V_{o1} = \bar{I}_{b2} r_{\pi 2} + (\beta + 1) \bar{I}_{b2} (r_{o2} \parallel R_E)$$

$$\frac{V_o}{V_{o1}} = \frac{(\beta + 1) (R_E \parallel r_{o2})}{r_{\pi 2} + (\beta + 1) (r_{o2} \parallel R_E)}$$

$$V_{o1} = -g_{m1} V_{\pi 1} (r_{o1} \parallel R_c \parallel R_{i2})$$

$$A_v = -g_{m1} (r_{o1} \parallel R_c \parallel R_{i2}) \frac{(\beta + 1) (R_E \parallel r_{o2})}{r_{\pi 2} + (\beta + 1) (r_{o2} \parallel R_E)}$$

$$R_{i2} = \frac{V_1}{\bar{I}_{b2}}$$

$$-V_1 + V_{\pi 2} + V_o = 0$$


$$V_1 = \bar{I}_{b2} (r_{\pi 2} + (\beta + 1) (r_{o2} \parallel R_E))$$

$$R_{i2} = r_{\pi 2} + (\beta + 1) (r_{o2} \parallel R_E)$$

$$R_{o1} = R_E \parallel r_{o1}$$

$$A_I = \frac{I_o}{I_S} = \frac{V_o / R_E}{V_S / R_i} = \frac{A_v R_i}{R_E}$$

$$R_o = \frac{V_x}{I_x} \Big|_{V_S=0}$$

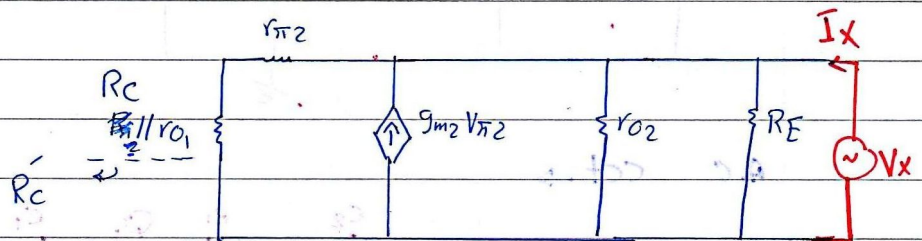


$$R_o = \frac{r_{\pi 2} + R_c \parallel r_{o1}}{\beta + 1} \parallel r_{o2} \parallel R_E$$

$$I_x + g_{m2} V_{\pi 2} = \frac{V_x}{R_E} + \frac{V_x}{r_{o2}} + \frac{V_x}{r_{\pi 2}}$$



Resistance Reflection Rule.

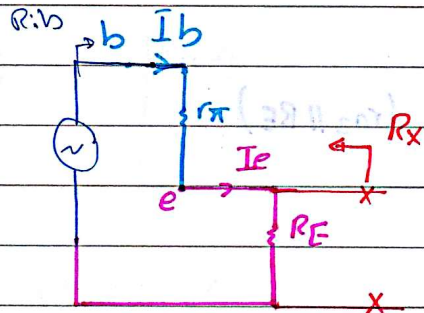


E  $\rightarrow$  B Multiply by  $(\beta+1)$   
 B  $\rightarrow$  E Divide by  $(\beta+1)$

$$R_{ib} = (\beta+1)R_E + r_{\pi}$$


$$R_x = \frac{r_{\pi}}{\beta+1} + R_E$$

Cascode Amp.

Exa.

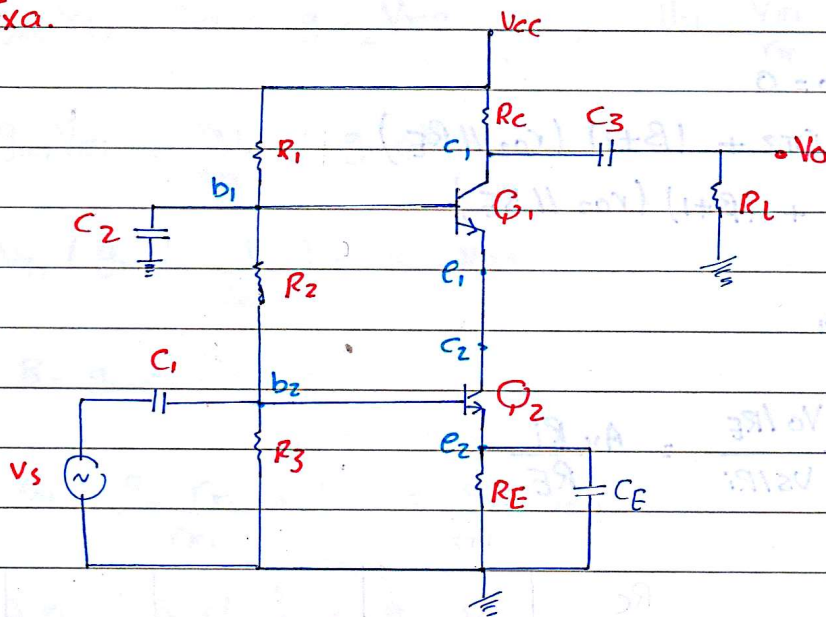


A.C cct  $\rightarrow$

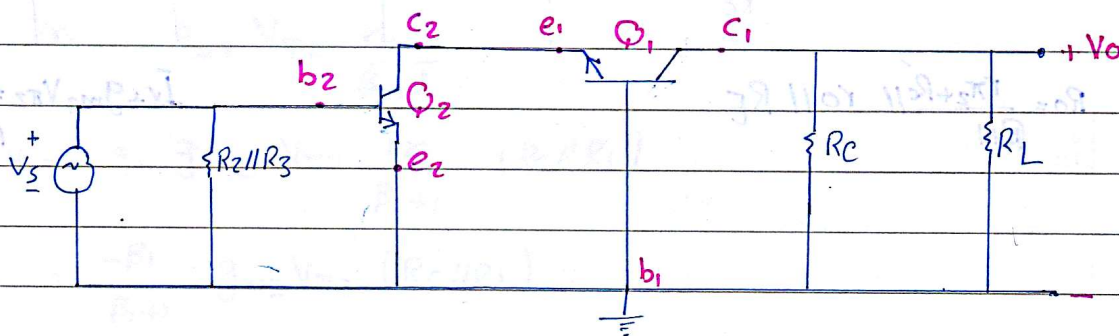

CH6

Thursday 28.7.2016

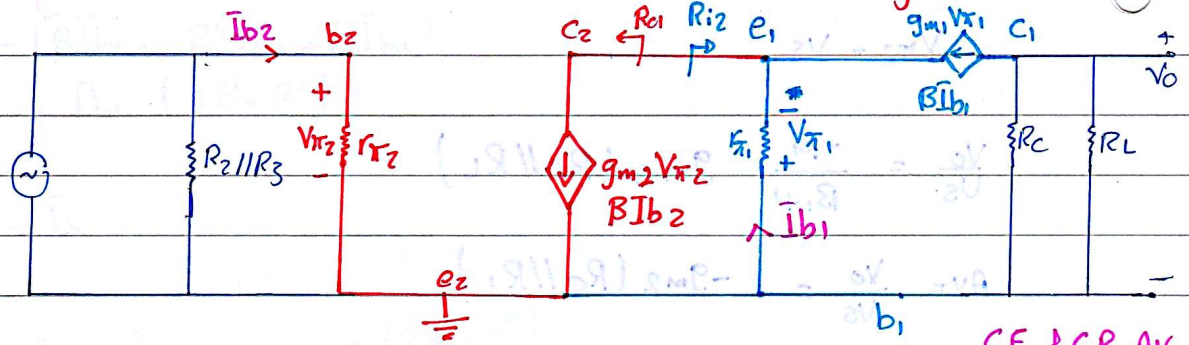

S.S.A.C ↗

↘ C.E & C.B AV

Like AV For ② [C.E]

Because

$I_{e1} = I_{c2}$

& AI For

Common Base

≈ unity

$$A_V = \frac{V_o}{V_s}, \quad V_o = -g_{m1} V_{\pi 1} (R_C \parallel R_L)$$

KCL at  $e_1$ :

$$g_{m1} V_{\pi 1} + \bar{I}_{b1} = g_{m2} V_{\pi 2}, \quad \bar{I}_{b1} = \frac{V_{\pi 1}}{r_{\pi 1}}$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{r_{\pi 1}} = g_{m2} V_{\pi 2}$$

$$V_{\pi 1} \left( g_{m1} + \frac{1}{r_{\pi 1}} \right) = g_{m2} V_{\pi 2}$$

$$\beta = g_{m1} r_{\pi 1}$$

$$V_{\pi 1} \left( \frac{g_{m1} r_{\pi 1} + 1}{r_{\pi 1}} \right) = g_{m2} V_{\pi 2}$$

$$V_{\pi 1} \left( \frac{\beta + 1}{r_{\pi 1}} \right) = g_{m2} V_{\pi 2}$$

$$V_{\pi 1} = g_{m2} V_{\pi 2} \frac{r_{\pi 1}}{\beta + 1}$$

$$V_o = -g_{m1} g_{m2} V_{\pi 2} \frac{r_{\pi 1}}{\beta + 1} (R_C \parallel R_L)$$

$$= \frac{-\beta}{\beta + 1} g_{m2} V_{\pi 2} (R_C \parallel R_L)$$



$$V_{\pi 2} = V_s$$

$$\frac{V_o}{V_s} = \frac{-\beta_1}{\beta_1 + 1} g_{m2} (R_c // R_L)$$

$$A_V = \frac{V_o}{V_s} = -g_{m2} (R_c // R_L)$$

$$A_I = \frac{I_o}{I_s} = \frac{V_o / R_L}{V_s / R_i} = \frac{V_o}{V_s} \cdot \frac{R_i}{R_L} = A_V \frac{R_i}{R_L}$$

$$R_i = R_2 // R_3 // r_{\pi 2}$$


$$R_o = \left. \frac{V_x}{I_x} \right|_{V_s=0} = R_c \Rightarrow V_{\pi 1} = V_{\pi 2} = V_s = 0$$

$$R_{o1} = \infty$$

$$R_{i2} = \frac{r_{\pi 1}}{\beta + 1}$$

. Cascade is used as a wide band Amp to Amplify high Freq. signals.

. Darlington Configuration.

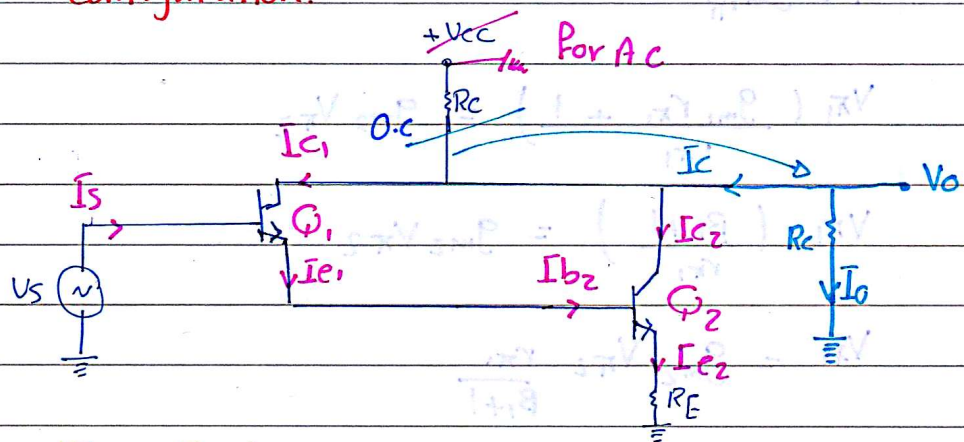

$$I_o = -I_c = -(I_{c1} + I_{c2})$$

$$= -(\beta I_{b1} + \beta I_{b2})$$

$$= -(\beta I_{b1} + \beta(\beta + 1) I_{b1})$$

CH6


Thursday 28.7.2016

$$I_o = -(\beta I_{b1} + \beta^2 I_{b1} + \beta I_{b1})$$

$$I_o = -I_{b1} (2\beta + \beta^2)$$

$$I_{b1} = I_s$$
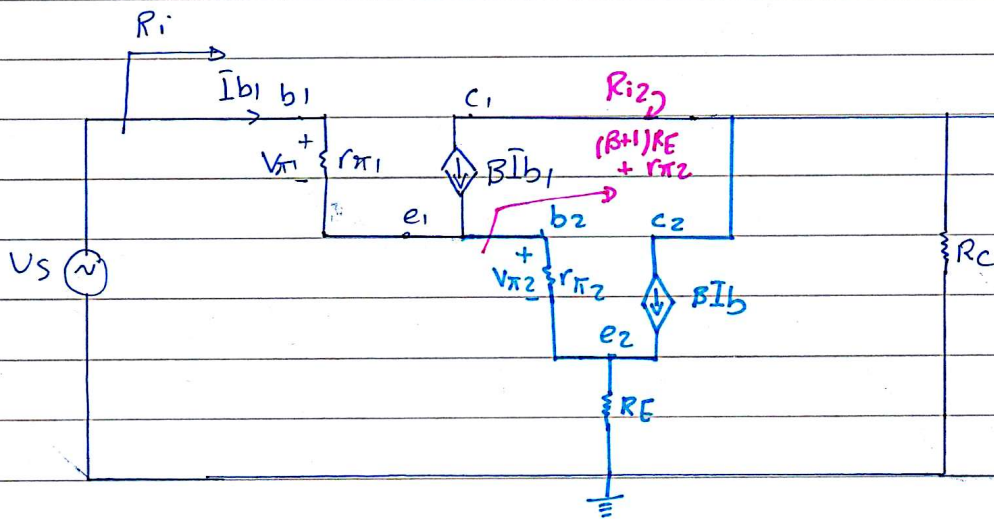
$$\frac{I_o}{I_{b1}} = \frac{I_o}{I_s} = A_I = -(2\beta + \beta^2)$$



$$R_i = [R_E(\beta+1) + r_{\pi 2}] (\beta+1) + r_{\pi 1}$$


using (R.R.R)

$$A_V = \frac{V_o}{V_s} = \frac{I_o R_L}{I_s R_i} = A_I \frac{R_L}{R_i}$$



1) The MOSFET must be biased in saturation Region to be used as an Amplifier.

Ex.

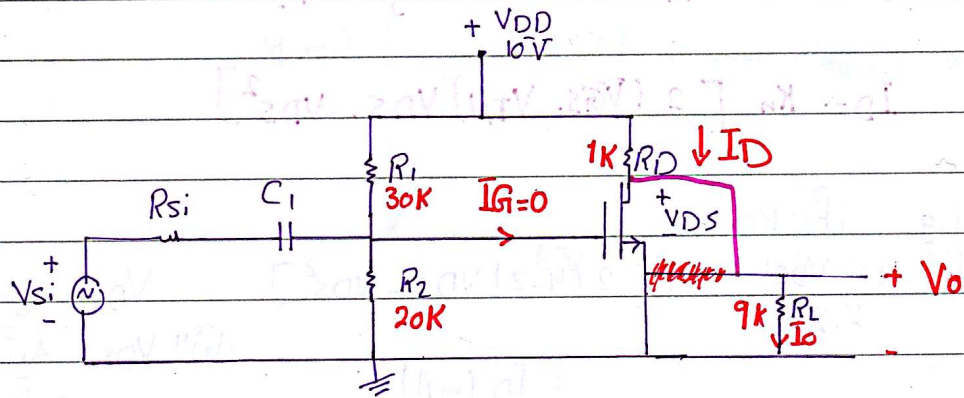

$$K_n = 1 \text{ mA/V}^2$$

$$V_{TN} = 2 \text{ V}$$

Calculate  $I_D$ ,  $V_{DS}$ .

In D.C Analysis Cap  $\rightarrow$  O.C.

Assume the MOSFET in Sat. Region.

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = \frac{10 \times 20}{20 + 30} - 0 = 4 \text{ V}$$

$$I_D = 1(4 - 2)^2 = 4 \text{ mA}$$

$$-V_{DD} + I_D R_D + V_{DS} = 0 \rightarrow V_{DS} = 10 - I_D R_D = 10 - 4 \times 1 = 6 \text{ V}$$

$$V_{DS(sat)} = V_{GS} - V_{TN} = 4 - 2 = 2 \text{ V}$$

Since  $V_{DS} > V_{DS(sat)}$ , then the MOSFET is in Sat. Region

$$P_D = I_D V_{DS} = 4 \times 6 = 24 \text{ mW}$$

CH4

Sunday 31.7.2016

→ In Sat. Region:

$$I_D = K_n (V_{GS} - V_{TN})^2$$


if it was in Linear Region:

$$I_D = K_n [2 (V_{GS} - V_{TN}) V_{DS} - V_{DS}^2]$$

i.g. if  $R_D = 22K \rightarrow$

$$\frac{10 - V_{DS}}{2.2K} = 1 [2(4-2)V_{DS} - V_{DS}^2]$$

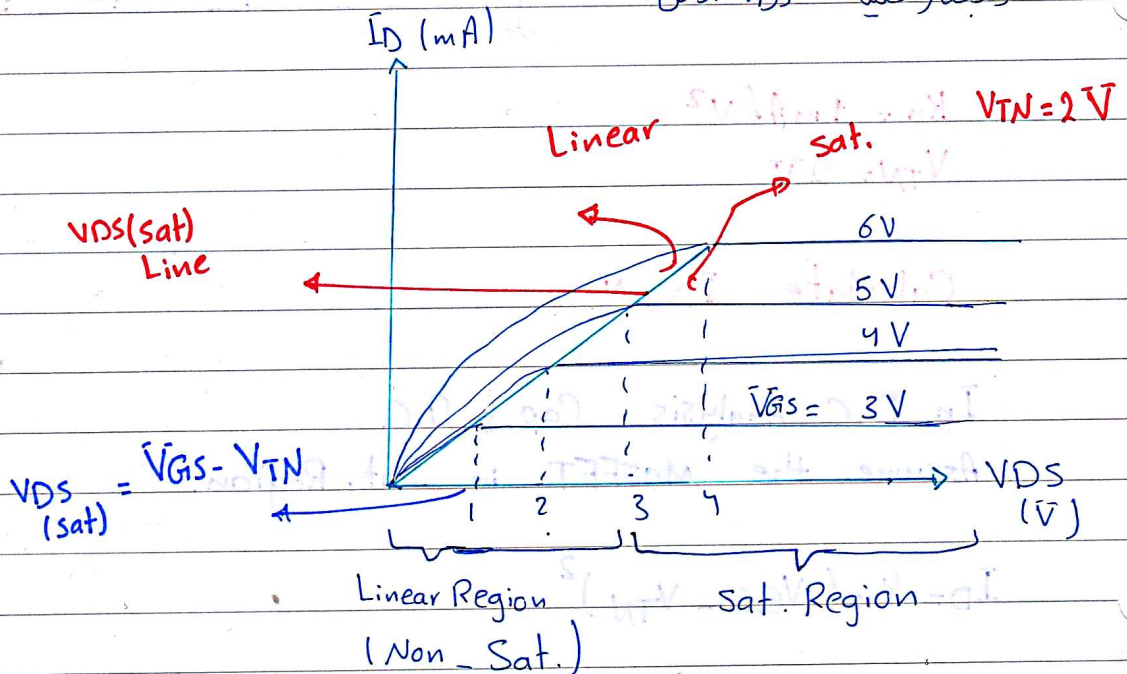$V_{DS}$  بطرح قيمته  
وختار قيمة  $V_{DS}$  الأولى



D.C.L.L.:

$$-V_{DD} + I_D R_D + V_{DS} = 0, \quad V_{DS} = V_{DD} - I_D R_D \rightarrow \text{(D.C.L.L. eqn)}$$


$$\text{slope} = \frac{-1}{R_D}$$

For  $I_D = 0 \rightarrow V_{DS} = V_{DD} = 10V$   $P_1 (10V, 0mA)$



For  $V_{DS} = 0 \rightarrow I_D = 10mA$  ,  $P_2 (0V, 10mA)$

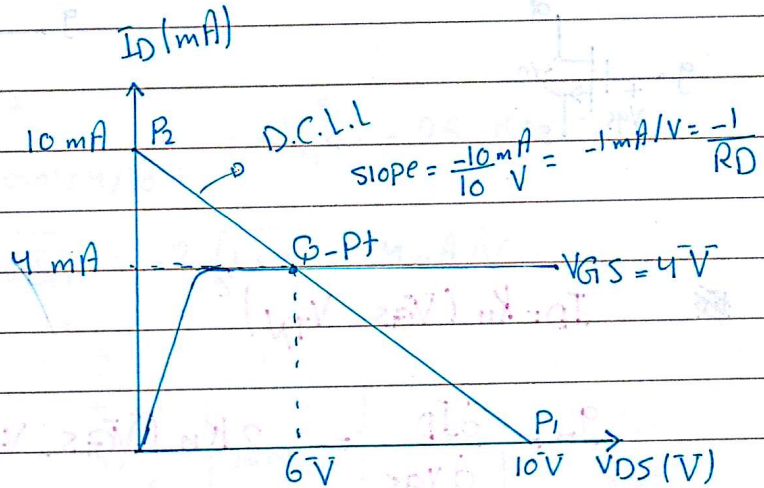Q-pt  $\rightarrow (V_{DSQ}, I_{DQ}) = (6V, 4mA)$







For A.C →

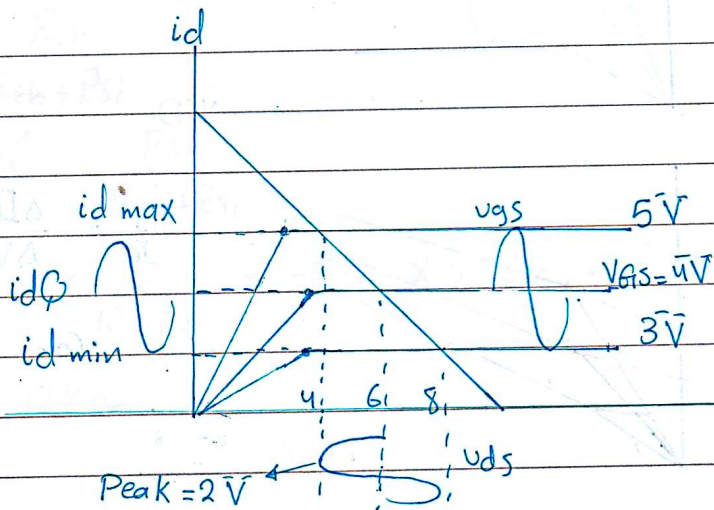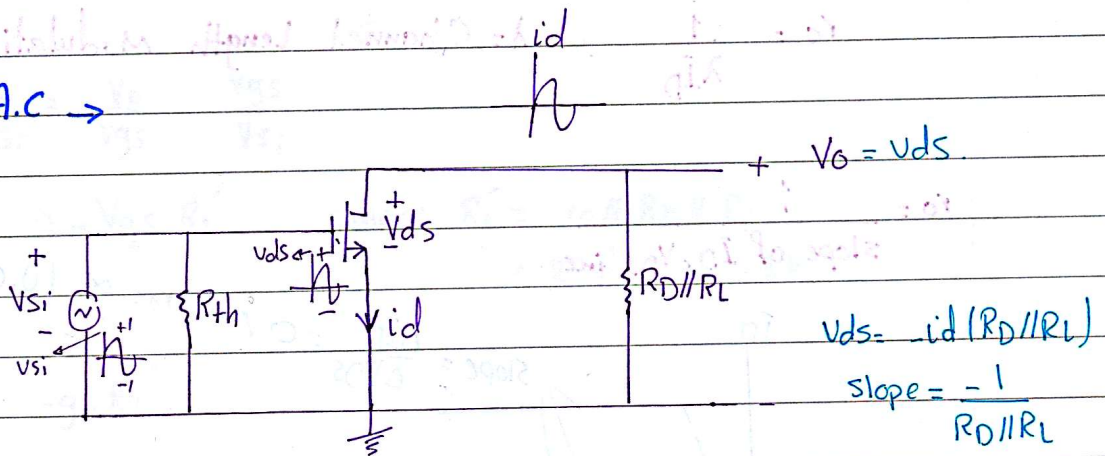

$A_v = \frac{V_{ds}}{V_{si}} = \frac{2}{1} = \frac{4}{2} = 2$

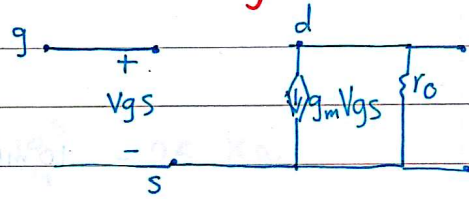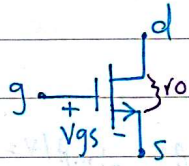$\frac{\text{Peak}}{\text{Peak}} = \frac{\text{Peak to Peak}}{\text{Peak to Peak}}$




$$I_D = K_n (V_{GS} - V_{TN})^2$$


$$g_m = \frac{\partial I_D}{\partial V_{GS}} = 2K_n (V_{GS} - V_{TN}) = 2\sqrt{K_n I_D}$$

$$r_o = \frac{1}{\lambda I_D}, \quad \lambda = \text{Channel length modulation parameter}$$
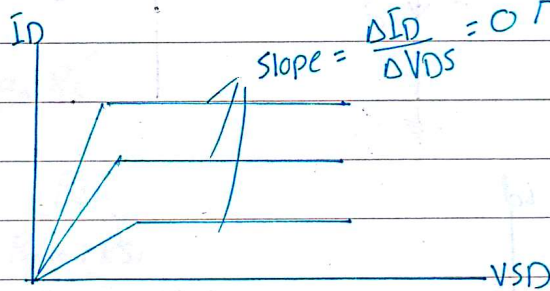
$$r_o = \frac{1}{\text{slope of } I_D, V_{DS} \text{ line}}$$



$r_o = \infty$  (O.C)

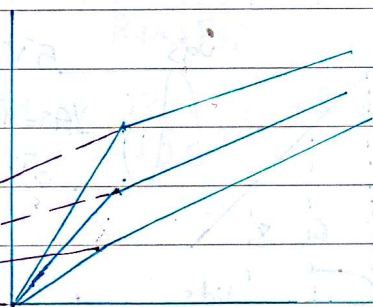


$$\frac{1}{r_o} = \frac{\Delta I_D}{\Delta V_{DS}} = \frac{I_D}{V_A} = \lambda I_D$$

$$r_o = \frac{1}{\lambda I_D}$$

$$V_A = 1/\lambda$$

Ex.

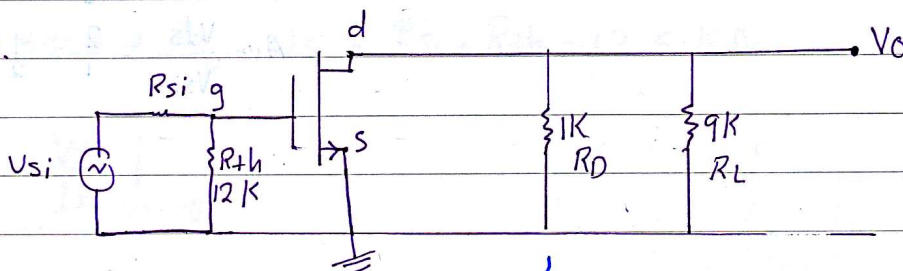

From the previous example.




For  $\lambda = 0.01 \text{ V}^{-1}$

$I_D = 4 \text{ mA}$

$r_o = \frac{1}{0.01 \times 4 \times 10^{-3}} = \frac{10^5}{4} = 25 \text{ k}\Omega$

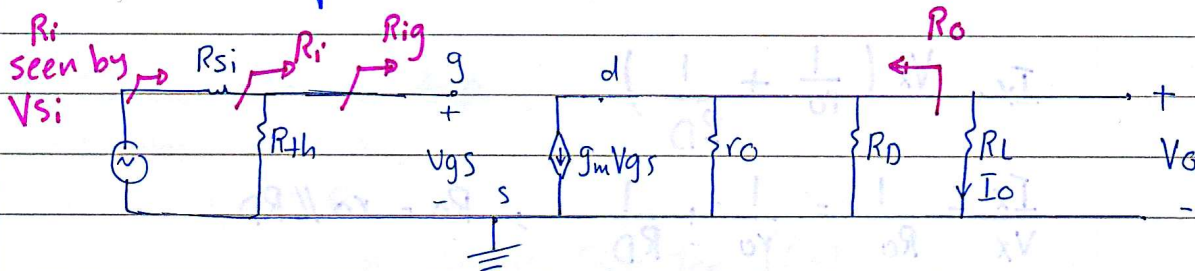$g_m = 2 \sqrt{k_n I_D} = 2 \sqrt{1 \times 4} = 4 \text{ mA/V}$



$A_v = \frac{V_o}{V_{s_i}} = \frac{V_o}{V_{g_s}} \cdot \frac{V_{g_s}}{V_{s_i}}$

$V_o = -g_m V_{g_s} R_i'$  ; where  $R_i' = r_o \parallel R_D \parallel R_L$   
 $= 25 \parallel 1 \parallel 9 = 0.8 \text{ K}$

$\frac{V_o}{V_{g_s}} = -g_m R_i'$

$\frac{V_{g_s}}{V_{s_i}} = \frac{R_{th}}{R_{th} + R_{s_i}}$

$A_v = -g_m R_i' \cdot \frac{R_{th}}{R_{th} + R_{s_i}}$


$= -4 \times 0.8 \times \frac{12}{12 + 0.5} = -3.2 \times 0.96 = -3$

$R_i = R_{th} = 12 \text{ k}\Omega$

$R_{i_g} = \infty$

$R_i \text{ seen by } V_{s_i} = R_{s_i} + R_{th} = 12.5 \text{ k}\Omega$

$R_o = \frac{V_x}{I_x} \Big|_{V_{s_i} = 0}$

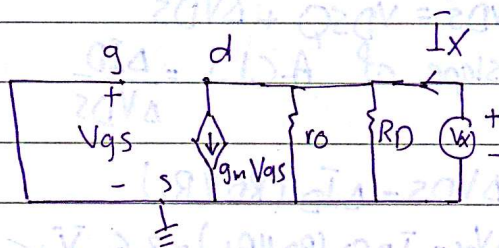

KCL at Node d

$$I_x = g_m V_{GS} + \frac{V_x}{r_o} + \frac{V_x}{R_D}$$


but when  $U_{Si} = 0, V_{GS} = 0$ , dep. s.  $\rightarrow$  O.C

$$I_x = V_x \left( \frac{1}{r_o} + \frac{1}{R_D} \right)$$

$$\frac{I_x}{V_x} = \frac{1}{R_o} = \frac{1}{r_o} + \frac{1}{R_D}, R_o = r_o \parallel R_D$$

The MosFET is a voltage control device  
So  $A_I$  is not needed to be calculated.

A.C.L.L. :

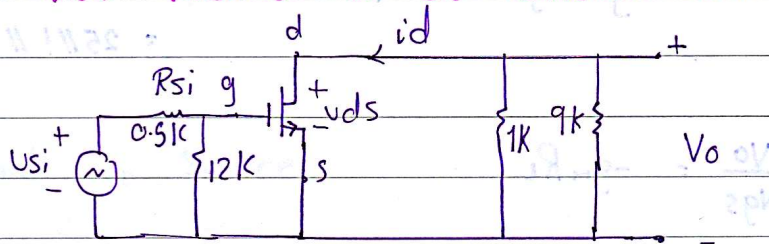

$$V_{ds} + i_d (R_D \parallel R_L) = 0$$

$$V_{ds} = -i_d (R_D \parallel R_L)$$

A.C.L.L. eqn.

$$\text{slope} = \frac{-1}{R_D \parallel R_L}$$

Remark:

The D.C.L.L. eqn was:

$$V_{ds} = 10 - I_D R_D$$


$$V_{DS} = V_{DSQ} + \Delta V_{DS}$$

$$\text{slope of A.C.L.L.} = \frac{\Delta I_D}{\Delta V_{DS}}$$

$$\Delta V_{DS} = \Delta I_D (R_D \parallel R_L)$$

$$\Delta V_{DS} = I_{DQ} (R_D \parallel R_L) = 3.6 \text{ V}$$

$$V_{DS} = 6 + 3.6 = 9.6 \text{ V}$$

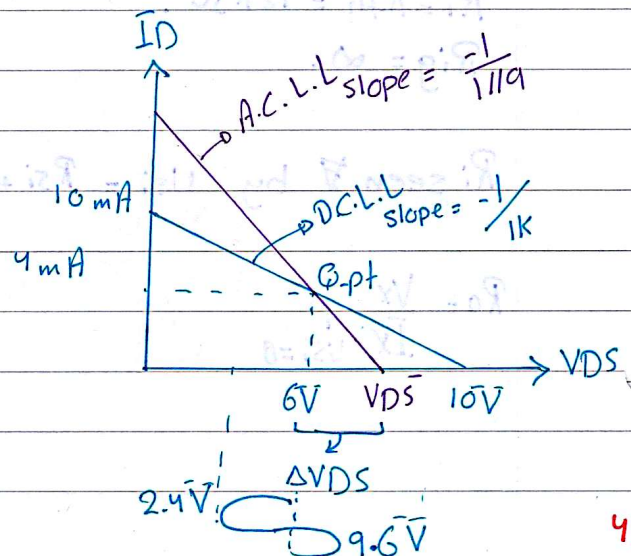



Max peak to peak symmetrical output Voltage:  $V_o$

$$V_o(p-p)_{max} = 2\Delta V_{DS} = 2I_{DQ}(R_D // R_L) = 7.2V$$

MOSFET Amps:-

1) Common Source Amp.

i) Basic C.S Amp.

ii) C.S Amp with  $R_S$

iii) C.S Amp with bypass Capacitor ( $C_S$ )

2) Common Drain Amp (Source Follower)

3) Common Gate Amp


C.S. Amp.

Common Terminal  $\rightarrow$  Source

$V_{in}$  to gate

$V_o$  from drain

i) Basic C.S.

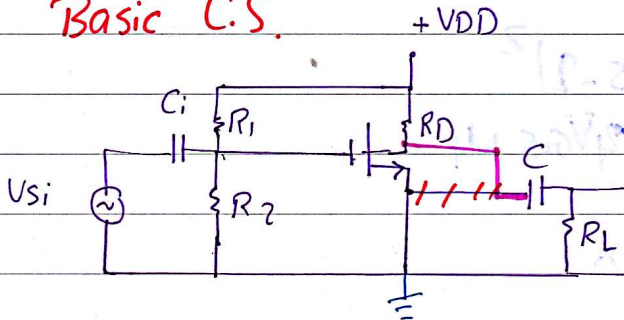


$$A_v = -g_m(R_D // R_L)$$

$$R_o = R_D // R_L$$

$$R_i = R_{th}$$

ii) C.S. with  $R_S$ :

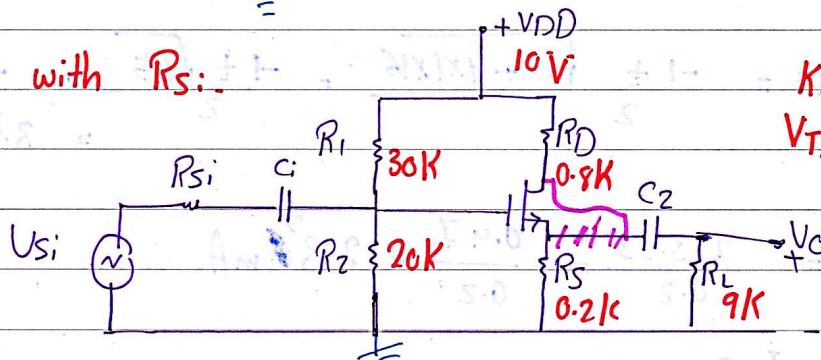

$$K_n = 1 \text{ mA/V}^2$$

$$V_{TN} = 2V$$

$$\lambda = 0.01 \text{ V}^{-1}$$

1) D.C Analysis:.. Cap  $\rightarrow$  O.C.  
 $R_S$  is used to stabilize Q-pt against  $K_n$  parameter variation

Assume The mosFET in Sat. Region:-

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$\Rightarrow V_{GS} = V_G - V_S$$

$$V_G = \frac{10 \times 20}{20 + 30} = 4 \text{ V}$$

$$-V_S + I_D R_S = 0$$

$$V_S = I_D R_S = 0.2 I_D$$

$$V_{GS} = 4 - 0.2 I_D$$

$$\therefore I_D = \frac{4 - V_{GS}}{0.2}$$

$$\frac{4 - V_{GS}}{0.2} = 1 (V_{GS} - 2)^2$$

$$4 - V_{GS} = 0.2 (V_{GS} - 2)^2$$

$$20 - 5V_{GS} = V_{GS}^2 - 4V_{GS} + 4$$

$$V_{GS}^2 + V_{GS} - 16 = 0$$


$$V_{GS} = \frac{-1 \pm \sqrt{1 + 4 \times 1 \times 16}}{2} = \frac{-1 \pm \sqrt{65}}{2} = -4.5 \text{ V} \times$$

$$= 3.53 \text{ V}$$

$$I_D = \frac{4 - 3.53}{0.2} = \frac{0.47}{0.2} = 2.35 \text{ mA}$$

$$-10 + I_D R_S + V_{DS} + I_D R_D = 0$$
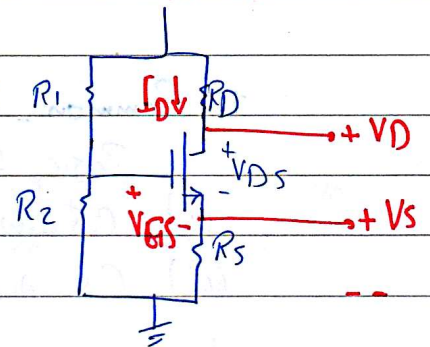
$$V_{DS} = 10 - 2.35(0.8 + 0.2) = 7.65 \text{ V}$$






D.C.L.L

$$-I_0 + I_D R_D + V_{DS} + I_D R_S = 0$$

$$V_{DS} = I_0 - I_D (R_S + R_D)$$

$$\text{slope} = \frac{-1}{R_S + R_D}$$

A.C.L.L , Cap → S.C , D.C → S.C

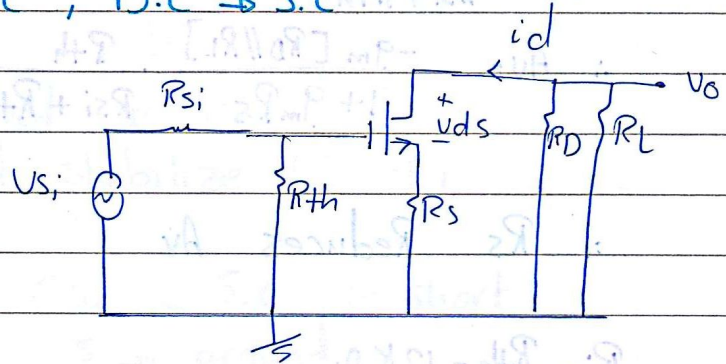


$$V_{DS} + I_D R_S + I_D (R_D // R_L) = 0$$

$$V_{DS} = -I_D (R_S + R_D // R_L)$$

$$\text{slope} = \frac{-1}{R_S + R_D // R_L}$$

S.S.A.C →

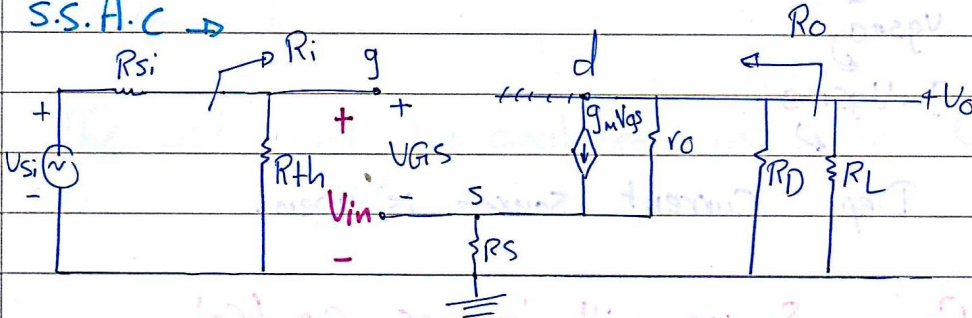

$$A_v = \frac{V_o}{V_{si}} = \frac{V_o}{V_{in}} \cdot \frac{V_{in}}{V_{si}}$$

$$V_o = -g_m V_{gs} [R_D // R_L]$$

Neglecting  $r_o$  →

$$-V_i + V_{gs} + V_s = 0$$

$$V_i = V_{gs} + V_s = V_{gs} + g_m V_{gs} R_S$$

$$v_i = v_{gs} (1 + g_m R_s)$$

$$\frac{v_o}{v_i} = \frac{-g_m [R_D // R_L]}{1 + g_m R_s}$$

$$\frac{v_i}{v_{si}} = \frac{R_{th}}{R_{si} + R_{th}}$$

$$\therefore A_v = \frac{-g_m [R_D // R_L]}{1 + g_m R_s} \cdot \frac{R_{th}}{R_{si} + R_{th}}$$

$\therefore R_s$  Reduces  $A_v$

$$R_i = R_{th} = 12 \text{ k}\Omega$$

$$R_o = \left. \frac{v_x}{i_x} \right|_{v_{si}=0, v_i=0, v_{gs}=0, g_m v_{gs}=0} = R_D = 0.8 \text{ k}\Omega$$

$$v_{si}=0$$


$$v_i=0$$

$$v_{gs}=0$$

$$g_m v_{gs}=0$$

Dep. Current source is open.

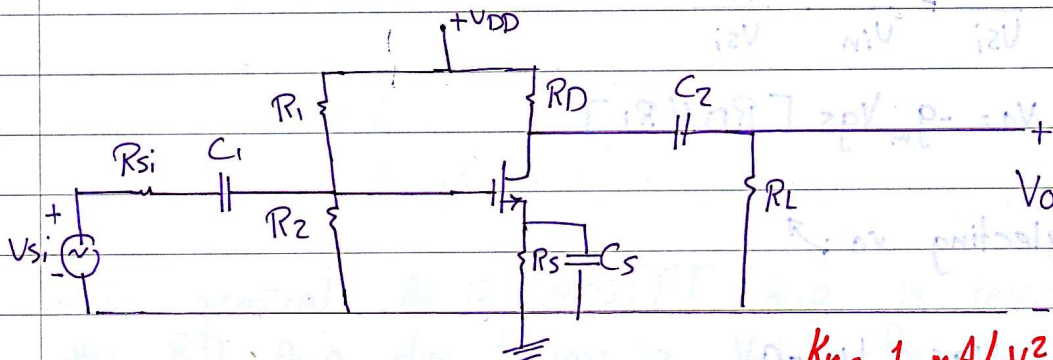iii) Common Source with bypass Cap ( $C_s$ )




$$K_n = 1 \text{ mA/V}^2$$

$$V_{TN} = 2 \text{ V}$$

$$\lambda = 0.01 \text{ V}^{-1}$$




For D.C Analysis  $C_s \rightarrow O.C$

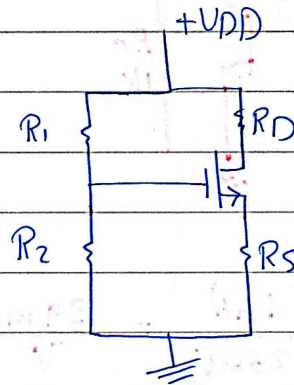

The cct is analyzed as C.S. with  $R_s$ . ( $R_s$  is present and stabilize Q pt)

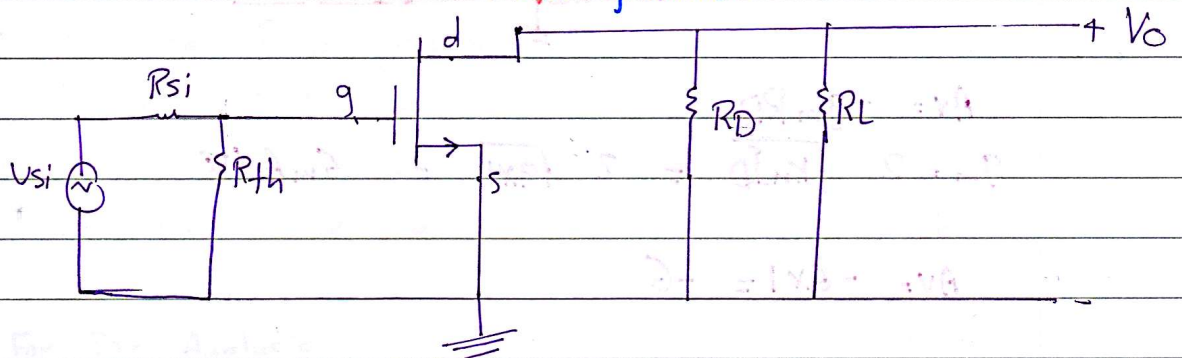For A.C Analysis C.S.  $\rightarrow$  S.C is short  
 $S \rightarrow$  ground.



The cct will be analyzed as Basic C.S. Amp.  
 $A_v \uparrow$


- C.S.  $A_v > 1$
- $R_i = R_{th}$
- $R_o \rightarrow R_D$  or  $R_D // r_o$
- $\phi = 180^\circ$
- $A_I =$  Not important.

$\rightarrow$  In general  $A_v$  in MOSFET Amp is less than  $A_v$  in the BJT Amp due to low  $g_m$  Value for the same Current

CH4

Thursday 4-8-2016

BJT

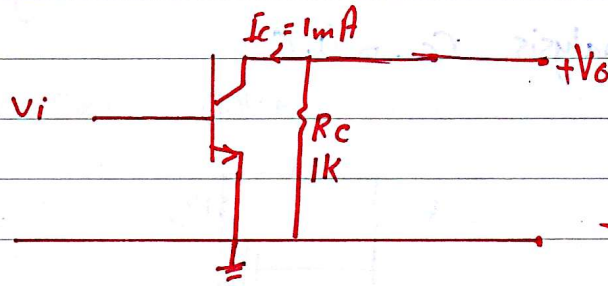


$$A_v = -g_m R_C$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1\text{mA}}{26\text{mV}} = \frac{39\text{mA}}{\text{V}}$$

$$A_v = -39 \times 1 = -39$$

MOSFET

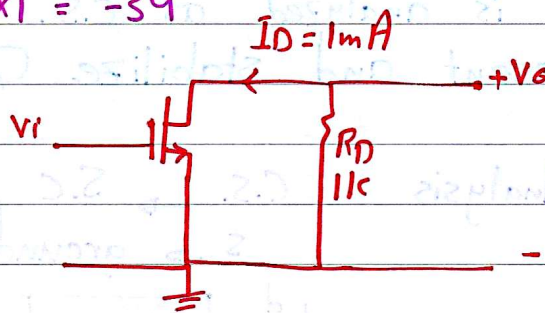

$$A_v = -g_m R_D$$


$$g_m = 2 \sqrt{k_n I_D} = 2 \sqrt{9 \times 1} = 6\text{mA/V}$$

$$A_v = -6 \times 1 = -6$$

$\therefore$  The gain in BJT  $>$  gain in MOSFET




2) Common-Drain Amp (source Follower)

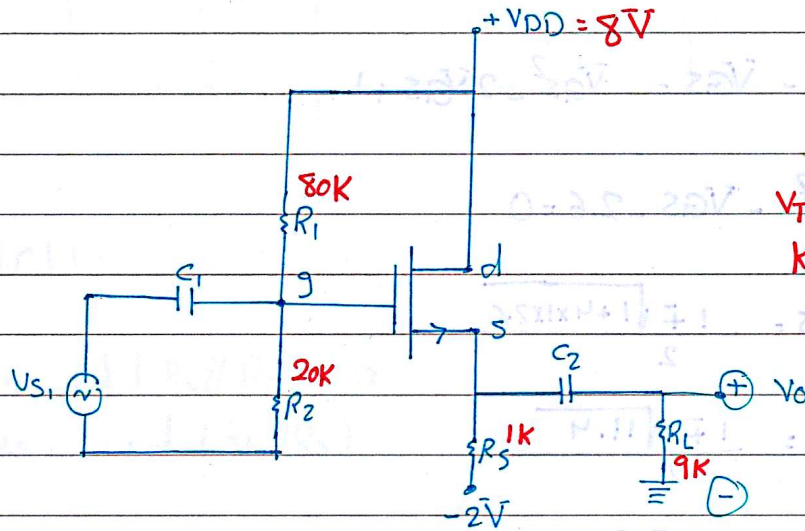

$V_{TN} = 1V$   
 $K_n = 1mA/V^2$   
 $\lambda = 0.01 V^{-1}$

- 1) Calculate  $I_{DQ}$ ,  $V_{DSQ}$ .
- 2) Draw s.s.A.C eqnt cct. & find  $A_v$ ,  $R_i$ ,  $R_o$
- 3) Write A.C.L.L eqn. & find slope.
- 4) Determine Max. peak symmetrical o/p voltage.

→ For Dc Analysis.

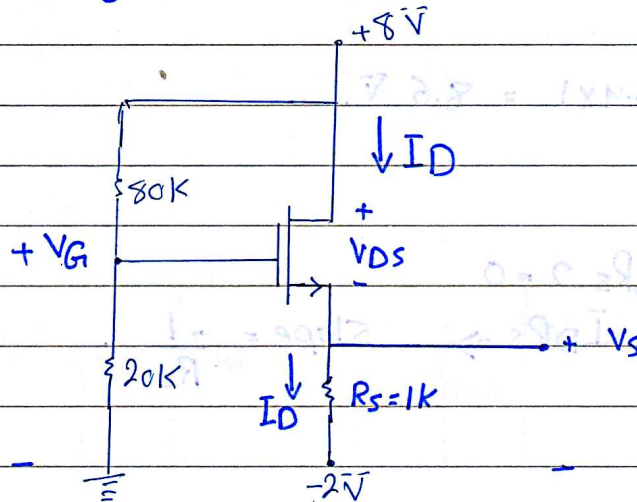

$$-V_S + I_D R_S - 2 = 0 \rightarrow V_S = I_D R_S - 2$$

$$V_{GS} = 1.6 - 1 \times I_D + 2$$

$$\bar{V}_{GS} = 3.6 - I_D$$

$$I_D = \frac{3.6 - V_{GS}}{1} = 3.6 - V_{GS}$$

$$3.6 - V_{GS} = 1 (V_{GS} - 1)^2$$

$$3.6 - V_{GS} = V_{GS}^2 - 2V_{GS} + 1$$

$$V_{GS}^2 - V_{GS} - 2.6 = 0$$

$$V_{GS} = \frac{1 \pm \sqrt{1 + 4 \times 1 \times 2.6}}{2}$$

$$= \frac{1 \pm \sqrt{11.4}}{2}$$

$$= \frac{1 \pm 3.4}{2}$$

$$V_{GS} = 2.2 \text{ V}$$

$$I_D = 3.6 - 2.2 = 1.4 \text{ mA}$$

$$-8 + V_{DS} + I_D R_S - 2 = 0$$

$$V_{DS} = 10 - 1.4 \times 1 = 8.6 \text{ V}$$

D.C.L.L 8.

$$-8 + V_{DS} + I_D R_S - 2 = 0$$

$$V_{DS} = 10 - I_D R_S \Rightarrow \text{slope} = \frac{-1}{R_S}$$


For A.C

D → ground

$V_i$  → gate

$V_o$  → From source.



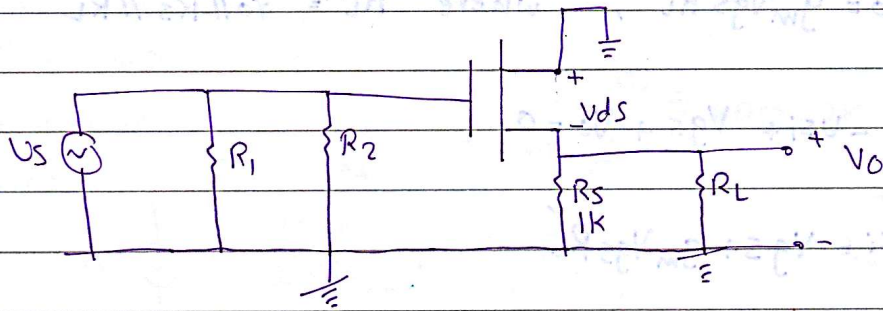


A.C.L.I.:

$$V_{DS} + i_d (R_L // R_S) = 0$$


$$V_{DS} = -i_d (R_L // R_S)$$

$$\text{Slope} = \frac{-1}{R_L // R_S}$$

S.S.A.C

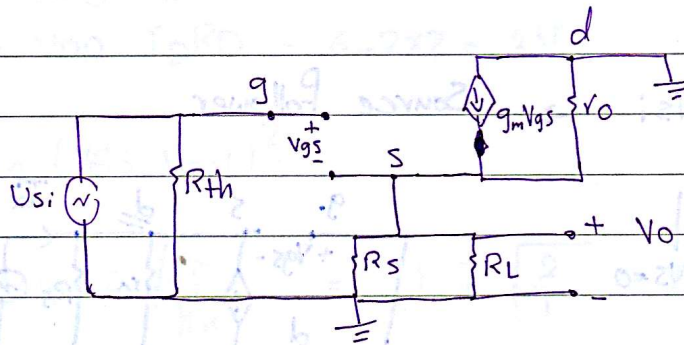

More simple:

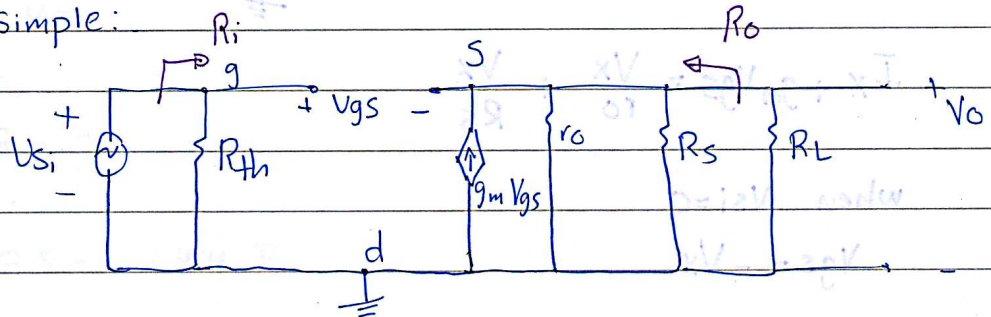

$$R_i = R_{Th} = 80 // 20 = 16 \text{ K}\Omega$$

$$A_V = \frac{V_O}{U_{Si}}$$

CH4

Monday 8-8-2016

$$V_o = g_m V_{gs} R_L', \quad \text{where } R_L' = r_o \parallel R_s \parallel R_L$$

$$-V_{si} + V_{gs} + V_o = 0$$

$$\begin{aligned} V_{si} &= V_{gs} + g_m V_{gs} R_L' \\ &= V_{gs} (1 + g_m R_L') \end{aligned}$$

$$A_v = \frac{g_m V_{gs} R_L'}{V_{gs} (1 + g_m R_L')} = \frac{g_m R_L'}{1 + g_m R_L'}$$

$$A_v < 1, \quad \phi = 0^\circ$$


$$\text{If } g_m R_L' \gg 1$$

$$A_v \approx 1 = \frac{V_o}{V_{si}}$$

$\therefore V_o = V_{si} \rightarrow$  Source Follower.

$$\rightarrow R_o = \frac{V_x}{I_x} \Big|_{V_{si}=0}$$

Kcl at d.

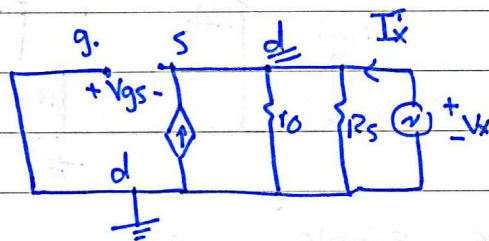

$$I_x + g_m V_{gs} = \frac{V_x}{r_o} + \frac{V_x}{R_s}$$

when  $V_{si} = 0$

$$V_{gs} = -V_x$$

$$I_x = V_x \left[ g_m + \frac{1}{r_o} + \frac{1}{R_s} \right]$$

$$\frac{I_x}{V_x} = \frac{1}{R_o} = g_m + \frac{1}{r_o} + \frac{1}{R_s} \quad \therefore R_o = \frac{1}{g_m} \parallel r_o \parallel R_s$$

,  $R_o \rightarrow$  Low.




### 3) Common-gate Amp

#### C.G. Amp.

G → Common Terminal

$V_i$  → Source

$V_o$  → From Drain

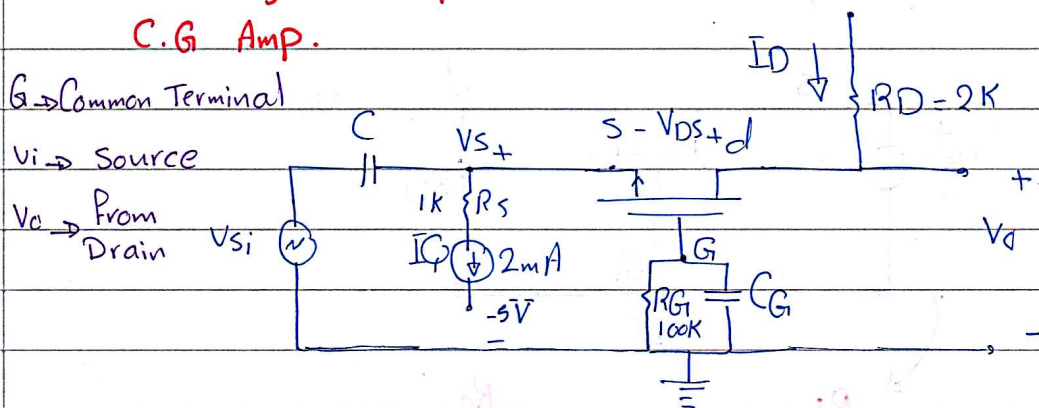

$$V_{TN} = 1 \text{ V}$$

$$K_n = 2 \text{ mA/V}^2$$

$$\lambda = 0$$

1) Find  $V_D, V_S, V_{DS}$

$$-V_{DD} + I_D R_D + V_D = 0$$

$$V_D = V_{DD} - I_D R_D = 6 - 2 \times 2 = 2 \text{ V}$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$V_{GS} - V_{TN} = \sqrt{\frac{I_D}{K_n}} = 1 \sqrt{\frac{2}{1}} = 2.414 \text{ V}$$



$$V_{GS} = V_G - V_S$$

$$V_G = \frac{I_D R_G}{1} = 0$$

$$V_S = -V_{GS} = -2.414 \text{ V}$$

$$V_{DS} = V_D - V_S = 4.414 \text{ V}$$

2) A.C Analysis.

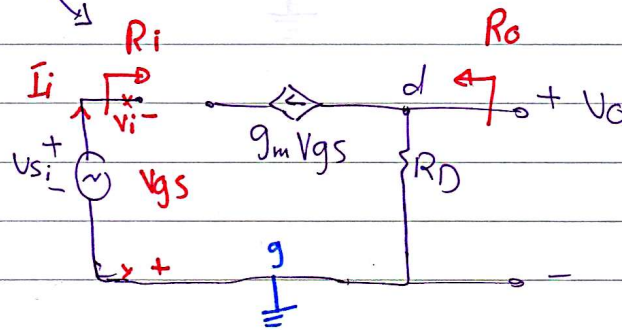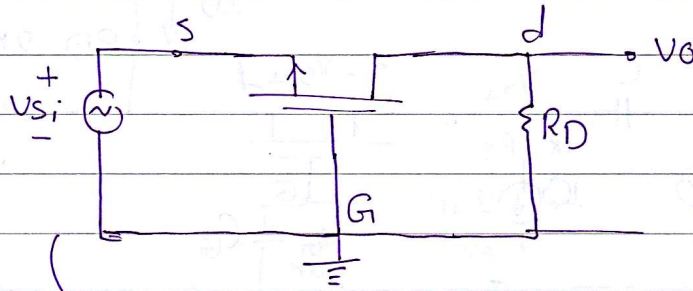

$$A_v = \frac{V_o}{V_{si}} = \frac{-g_m V_{gs} R_D}{-V_{gs}} = g_m R_D$$

$$R_o = \frac{V_x}{I_x} \Big|_{V_{si}=0}$$

when  $V_{si}=0$ ,  $V_{gs}=0$

$$g_m V_{gs}=0, \text{ C.S.} \rightarrow \text{O.C.}$$

$$R_o = R_D$$

$$A_i = \frac{I_o}{I_s} = \frac{-g_m V_{gs}}{-g_m V_{gs}} = 1, \text{ } I_o, I_i \text{ (current Follower)}$$

$$R_i = \frac{v_i}{I_i} = \frac{-V_{gs}}{-g_m V_{gs}} = \frac{1}{g_m} \text{ (Low)}$$




Amp	$A_v$	$A_i$	$\phi$	$R_i$	$R_o$
C.S	$> 1$	-	$180^\circ$	$R_{th}$	moderate to high
C.D	$< 1$	-	0	$R_{th}$	Low
C.G	$> 1$	$< 1$	0	low	moderate to high

→ To achieve certain specifications which can't be obtained from single stage (S.S), multi-stage Amps are used.

1) Cascade Amp (Series Connection).




2) Cascode Amp

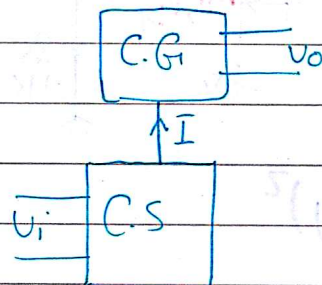
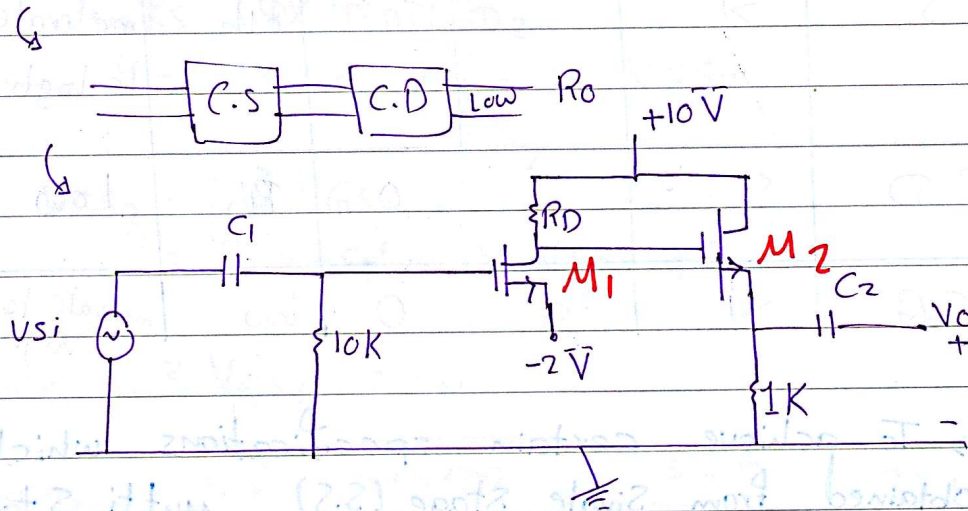
### 1) Cascade Amp.

Ex. It is required to have  $A_v > 1$  & low  $R_o$  &  $180^\circ$




$M_1$  &  $M_2$  are identical with:

$k_n = 2 \text{ mA/V}^2$ ,  $V_{TN} = 1 \text{ V}$ ,  $\lambda = 0.02 \text{ V}^{-1}$

- 1) Find  $I_{DQ1}$ ,  $I_{DQ2}$ ,  $V_{DS1}$ ,  $V_{DS2}$
- 2) Draw S.S.A.C eqnt cct & find  $A_v = \frac{V_o}{V_{si}}$ ,  $R_i$ ,  $R_o$

1) For D.C Analysis:-

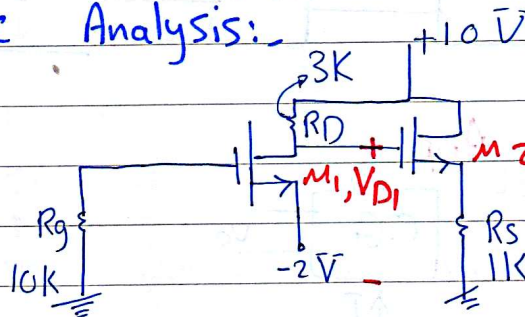

$$I_{D1} = k_n (V_{GS1} - V_{TN})^2$$

$$V_{GS1} = V_{G1} - V_{S1} = 0 - (-2) = 2 \text{ V}$$

$$I_{D1} = 2(2-1)^2 = 2 \text{ mA}$$

$$-10 + I_{D1} R_D + V_{D1} = 0$$

$$V_{D1} = 10 - I_{D1} R_D = 10 - 2 \times 3 = 4 \text{ V}$$

$$V_{DS1} = V_{D1} - V_{S1} = 4 - (-2) = +6 \text{ V}$$



CH4

Tuesday 9-8-2016

$$I_{D2} = K_n (V_{GS2} - V_{TN})^2$$

$$V_{GS2} = V_{G2} - V_{S2} \Rightarrow V_{G2} = V_{D1} = 4V$$

$$V_{S2} = I_{D2} R_S = 1 \times I_{D2} = I_{D2}$$

$$V_{GS2} = 4 - I_{D2} \rightarrow I_{D2} = 4 - V_{GS2}$$

$$4 - V_{GS2} = 2 (V_{GS2} - 1)^2$$


$$= 2 V_{GS2}^2 - 4 V_{GS2} + 2$$

$$2 V_{GS2}^2 - 3 V_{GS2} - 2 = 0$$


$$V_{GS2} = \frac{3 + \sqrt{9 + 4 \times 2 \times 2}}{4} = \frac{3 + 5}{4} = 2V$$

$$= -0.5V \quad \times$$

A.C Analysis:-

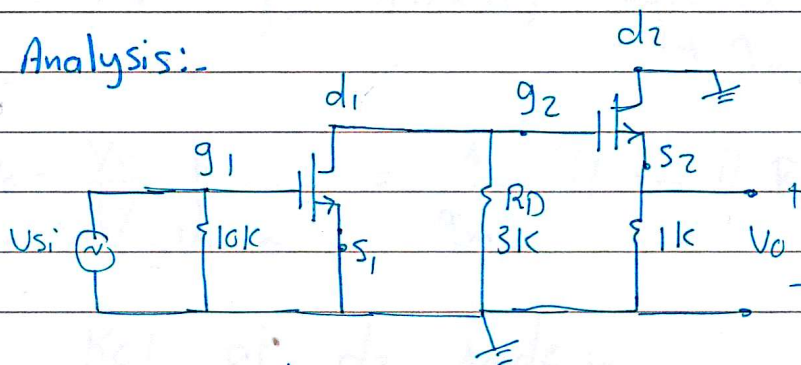

S.S.A.C eqnt cct:-

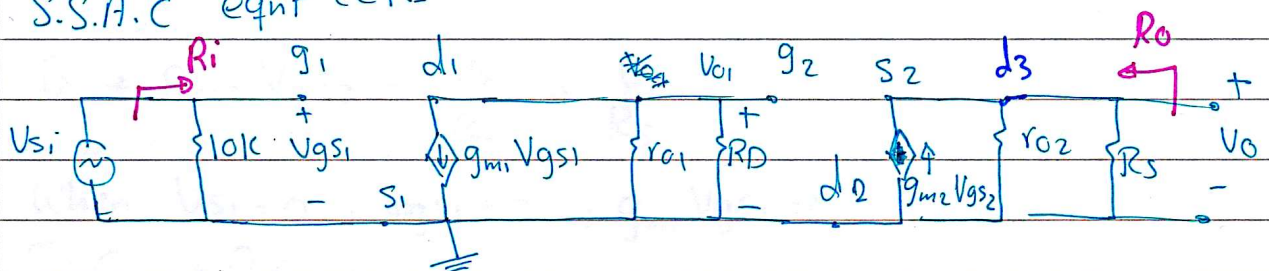

$$R_i = 10K$$

$$A_v = \frac{V_o}{V_{o1}} \times \frac{V_{o1}}{V_{s_i}}$$

$$A_{v2} \quad A_{v1}$$

CH4

Tuesday 9-8-2016

$$V_o = g_{m2} V_{gs2} (r_{o2} \parallel R_s)$$

$$-V_{o1} + V_{gs2} + V_o = 0$$

$$V_{o1} = V_{gs2} + g_{m2} V_{gs2} (r_{o2} \parallel R_s)$$

$$A_{V2} = \frac{V_o}{V_{o1}} = \frac{g_{m2} (r_{o2} \parallel R_s)}{1 + g_{m2} (r_{o2} \parallel R_s)}$$

$$V_{o1} = -g_{m1} V_{gs1} (r_{o1} \parallel R_D)$$

$$V_{gs1} = V_{si}$$

$$\frac{V_{o1}}{V_{si}} = -g_{m1} (r_{o1} \parallel R_D) = A_{V1}$$

$$\therefore A_V = -g_{m1} (r_{o1} \parallel R_D) \cdot \frac{g_{m2} (r_{o2} \parallel R_s)}{1 + g_{m2} (r_{o2} \parallel R_s)}$$

$$R_o = \frac{V_x}{I_x} \Big|_{V_{si}=0} = \frac{1}{g_{m2}} \parallel r_{o2} \parallel R_s$$

or Kcl at  $d_3$  Node :-

$$I_x + g_{m2} V_{gs2} = \frac{V_x}{r_{o2}} + \frac{V_x}{R_s}$$

When  $V_{si} = 0$ ,  $V_{gs1} = 0$ ,  $g_{m1} V_{gs1} = 0$

D.C  $\rightarrow$  O.C


$$(V_{r_{o1} \parallel R_D}) = 0, \quad V_{gs2} = -V_x$$

$$I_x = V_x \left( g_{m2} + \frac{1}{r_{o2}} + \frac{1}{R_s} \right)$$


$$\frac{V_x}{I_x} = R_o = \frac{1}{g_{m2}} \parallel r_{o2} \parallel R_s$$




2) Cascode Amp.:

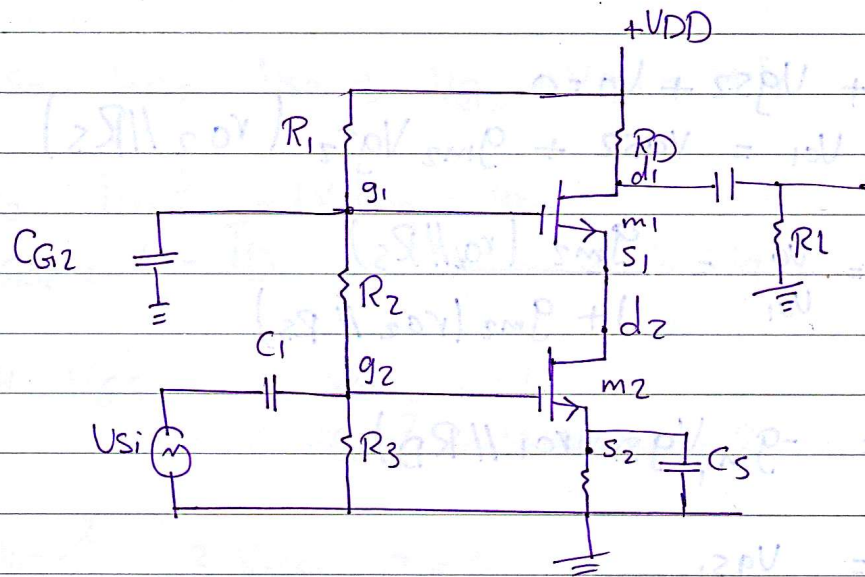

A.C ckt

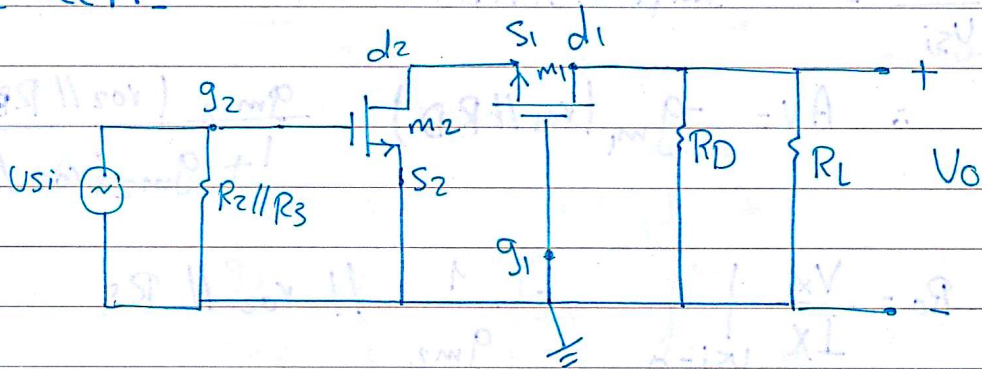

S.S.A.C

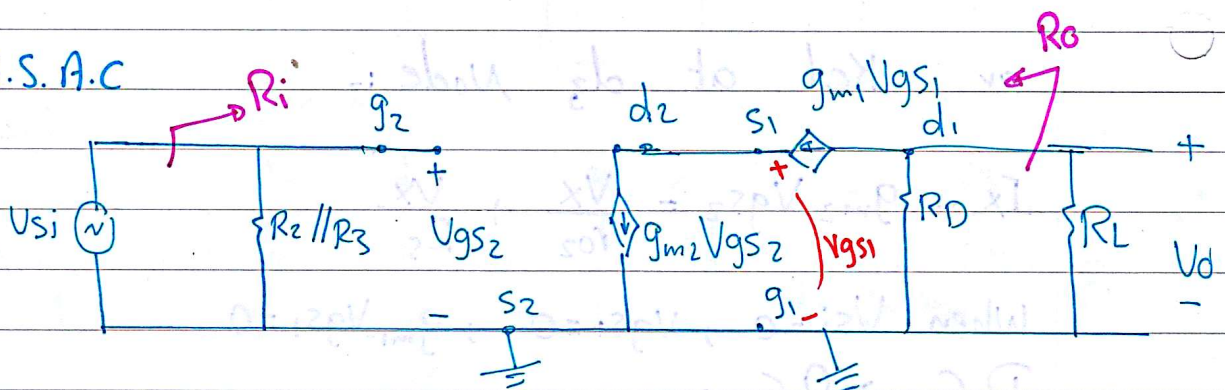


$$R_i = R_2 // R_3$$



$$R_o = R_D$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_{m2} V_{gs2} (R_D // R_L)}{V_{gs2}} = -g_{m2} (R_D // R_L)$$
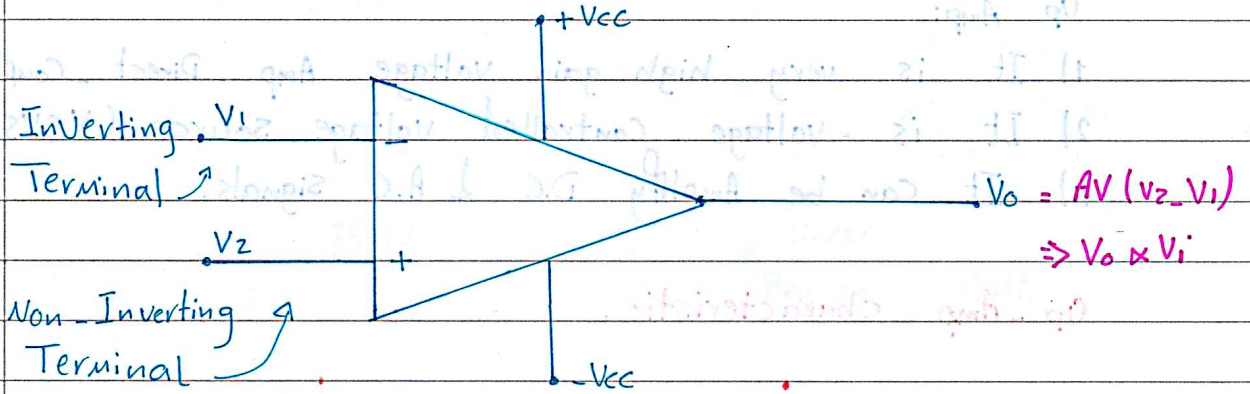
# CH9 Operational Amplifier (Op\_Amp) Thursday 11-8-2016



Block diagram for Simple Op-Amp.

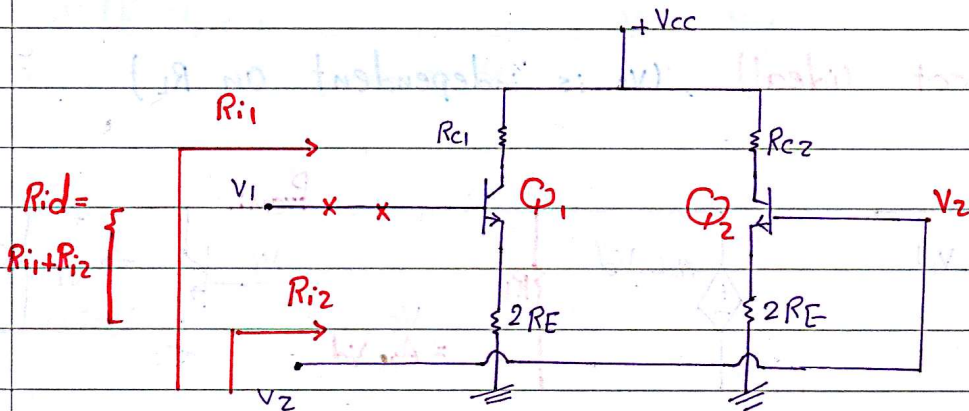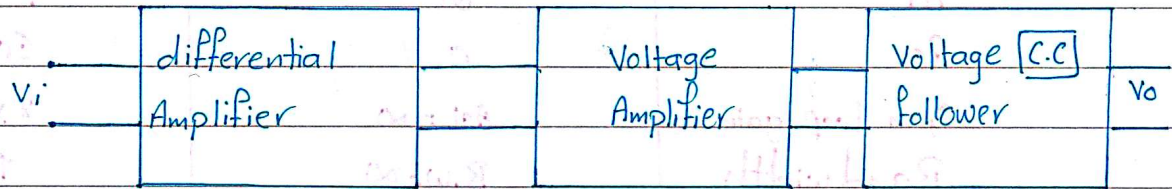


$$R_{i1} = (\beta + 1)2R_E + r_{\pi 1}$$

$$R_{i2} = (\beta + 1)2R_E + r_{\pi 2}$$

$$R_{id} = [4(\beta + 1)R_E + 2r_{\pi}]$$

741

741 Op-Amp.

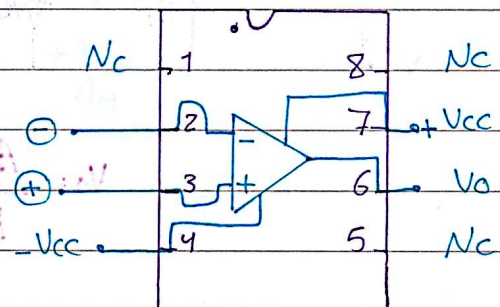




Op Amp:-

- 1) It is very high gain voltage Amp Direct-Coupled.
- 2) It is voltage-Controlled voltage source (VCVS)
- 3) It can be Amplify D.C & A.C signals.


Op - Amp characteristic.

parameter	Ideal Op-Amp	Real Op-Amp (741)
$R_i$	$\infty$	1 M $\Omega$
$R_o$	0	60 $\Omega$
Open Loop gain	$A_{OL} = \infty$	$2 \times 10^5$
Bandwidth	B.W. = $\infty$	1 MHz

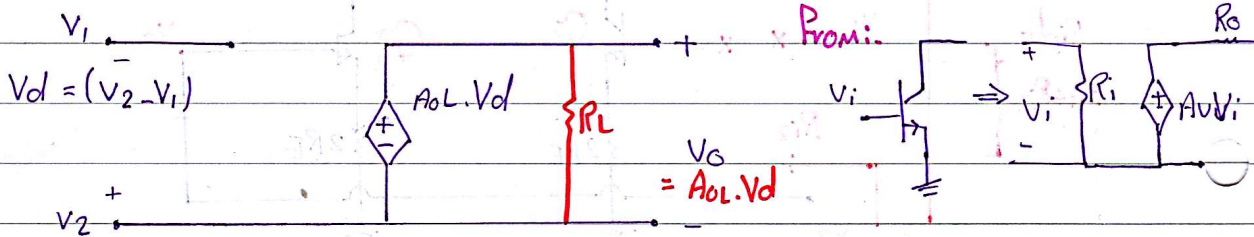Eqnt cct (ideal) , ( $V_o$  is independent on  $R_L$ )




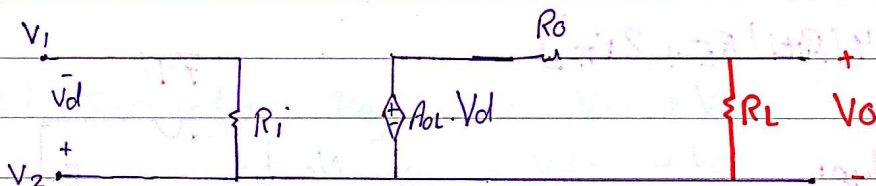Eqnt cct (Real) , ( $V_o$  depends on  $R_L$ )



$$V_o = \frac{A_{OL} \cdot V_d \cdot R_L}{R_L + R_o}$$

Transfer characteristic

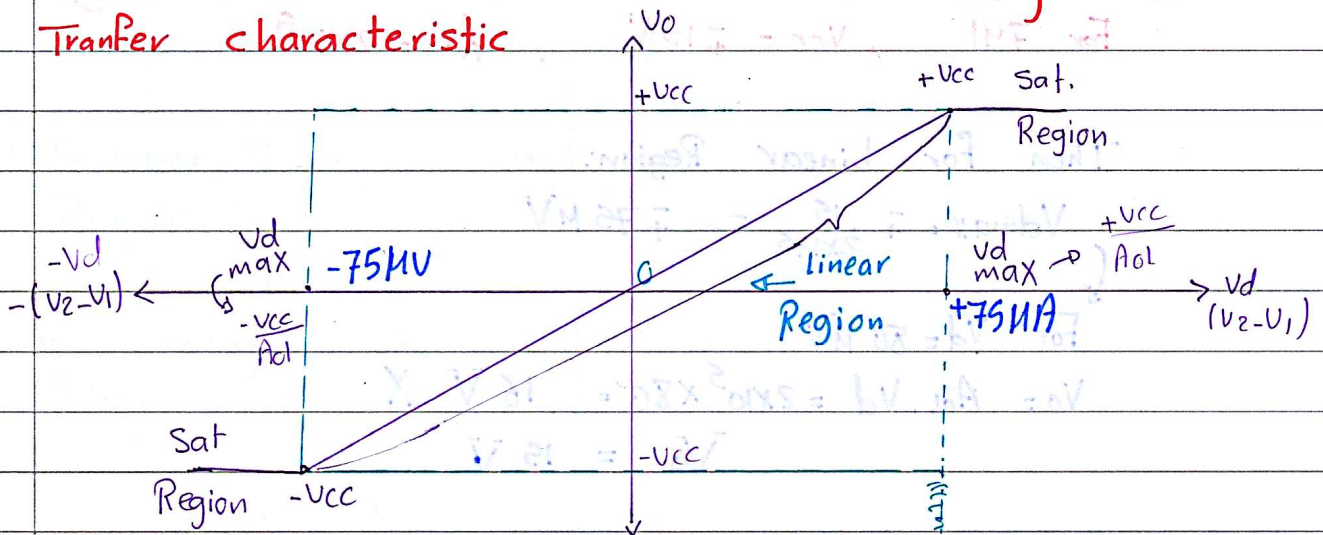

$$V_o = A_{OL} \cdot (V_2 - V_1) = A_{OL} \cdot V_d$$

For ideal op-Amp :  $A_{OL} = \infty$

i) IF  $V_2 > V_1 \rightarrow V_o = \infty ; V_o = +V_{cc}$

ii) IF  $V_2 < V_1 \rightarrow V_o = -\infty ; V_o = -V_{cc}$

$$\therefore V_{o\max} = \pm V_{cc}$$

For  $V_o = V_{cc} \rightarrow V_d = \frac{+V_{cc}}{A_{OL}}$

For  $V_o = -V_{cc} \rightarrow V_d = \frac{-V_{cc}}{A_{OL}}$

Operating Regn.

1) Linear Regn.  $V_o \propto V_d$

$$-\frac{V_{cc}}{A_{OL}} < V_d < \frac{+V_{cc}}{A_{OL}}$$

2) Saturation Regn.  $V_o = \pm V_{cc}$

$$-\frac{V_{cc}}{A_{OL}} > V_d > \frac{+V_{cc}}{A_{OL}}$$



For 741,  $V_{CC} = \pm 15V$ ,  $A_{OL} = 2 \times 10^5$

Then For Linear Region:


$$V_{dmax} = \pm \frac{15}{2 \times 10^5} = \pm 75 \mu V$$

↙

For  $V_d = 80 \mu V$

$$V_o = A_{OL} \cdot V_d = 2 \times 10^5 \times 80 = 16 V \times$$

$$\bar{V}_o = 15 V$$

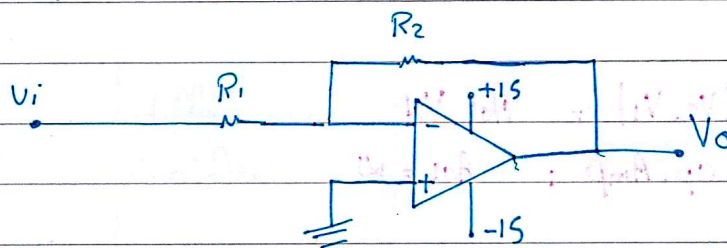

Closed Loop


- For Open-loop made the input signal to be proceed is very small  $\rightarrow V_{dmax} = \pm \frac{V_{CC}}{A_{OL}}$

- To Amplify any signal we must be operating the Op-Amp in closed loop mode.

- In this case  $A_V \neq A_{OL}$ , but  $A_V$  will be a resistor ratio.

A) Linear Applications

1) Inverting Amplifier

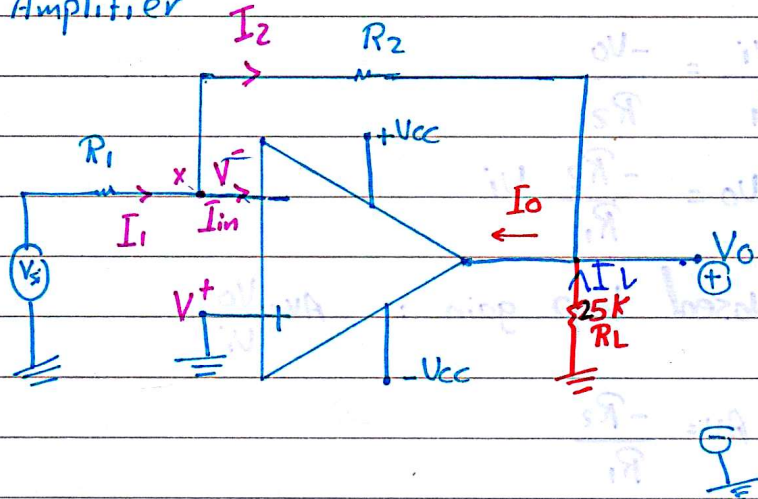

KCL at node x:



$$I_1 = I_2 + I_{in}$$

$$\frac{V_i - V_x}{R_1} = \frac{V_x - V_o}{R_2} + I_{in}$$

but for ideal op. Amp

$$I_{in} = 0$$

$$R_i = \infty$$

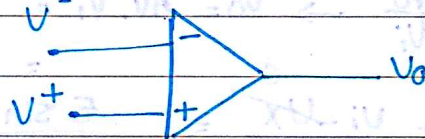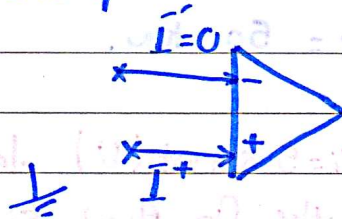

$$V_o = A_{OL} (V^+ - V^-)$$

For ideal op. Amp

$$A_{OL} = \infty$$

$$V^+ - V^- = \frac{V_o}{\infty} = 0$$



CH9

Sunday  
Thursday 14.8.2016

$$V^+ = V^- \text{ (virtual short)}$$

$$V^+ = V^- = V_x = 0 \text{ (virtual ground)}$$

$$\frac{V_i}{R_1} = \frac{-V_o}{R_2}$$

$$V_o = -\frac{R_2}{R_1} V_i$$

closed loop gain :  $A_V = \frac{V_o}{V_i}$

$$A_V = -\frac{R_2}{R_1}$$

$$R_i = \frac{V_i}{I_i} \rightarrow -V_i + I_i R_1 = 0$$

$$\frac{V_i}{I_i} = R_1$$

Ex) 1) Design an I.A to have  $A_V = -10$  and  $R_i = 5k$

$$R_i = R_1 = 5k\Omega$$

$$A_V = -\frac{R_2}{R_1} = -10 = -\frac{R_2}{5}$$

$$\therefore R_2 = 50k\Omega$$

2) For  $V_i = 5 \sin \omega t$  (V) determine  $I_1, I_2, I_L, I_o$ , does the Op. Amp sink or source current.

$$A_V = \frac{V_o}{V_i} \rightarrow V_o = A_V \cdot V_i = -10 \times 5 \sin \omega t$$

$$= -50 \sin \omega t$$



$$I_1 = \frac{V_i - V_x}{R_1} = \frac{5 \sin \omega t}{5k} = 1 \sin \omega t \text{ mA}$$

$$I_2 = \frac{V_x - V_o}{50k} = \frac{0 - (-50) \sin \omega t}{50k} = 1 \sin \omega t \text{ mA}$$

$$I_L = \frac{0 - V_o}{25k} = \frac{50 \sin \omega t}{25k} = 2 \sin \omega t \text{ mA}$$

$$I_o = I_2 + I_L = (1+2) \sin \omega t = 3 \sin \omega t \text{ mA.}$$

The Op-Amp is a sink current.

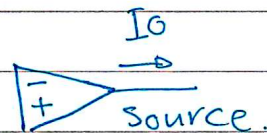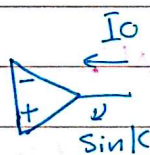


3) Draw  $V_o(t)$  when: i)  $V_{CC} = \pm 60 \text{ V}$


ii)  $V_{CC} = \pm 40 \text{ V}$

From answer 2:

i) For  $V_{CC} = \pm 60 \text{ V}$

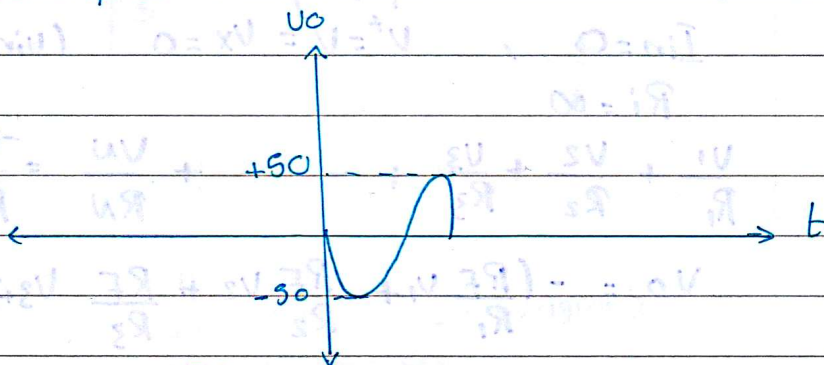


ii) For  $V_{CC} = \pm 40 \text{ V}$

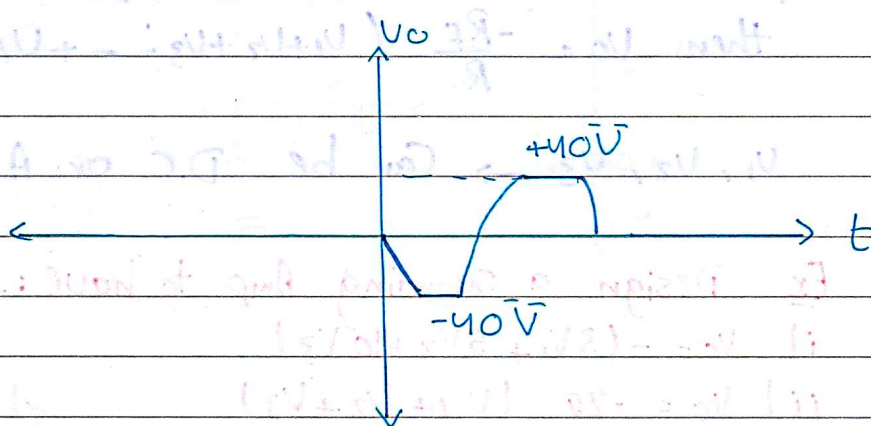



2) Summing Amp.

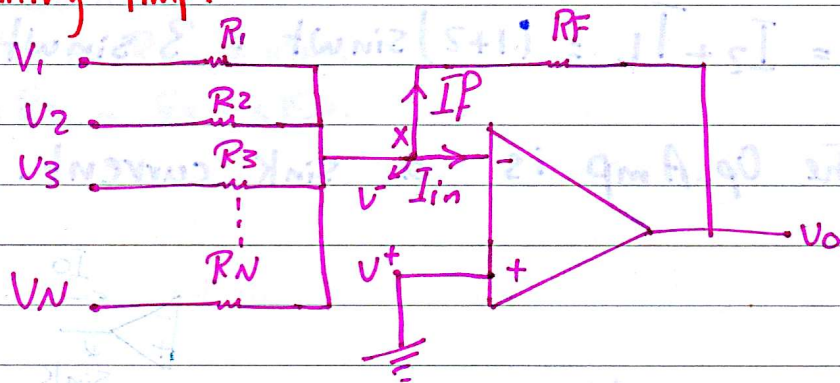

Kcl at node x:

$$I_1 + I_2 + I_3 + \dots + I_N = I_{in} + I_P$$

$$\frac{V_1 - V_x}{R_1} + \frac{V_2 - V_x}{R_2} + \frac{V_3 - V_x}{R_3} + \dots + \frac{V_N - V_x}{R_N} = \frac{0}{R_{in}} + \frac{V_x - V_o}{R_F}$$

Assume ideal Op-Amp

$$I_{in} = 0, \quad V^+ = V^- = V_x = 0 \quad (\text{virtual ground})$$

$$R_i = \infty$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots + \frac{V_N}{R_N} = \frac{-V_o}{R_F}$$

$$V_o = - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 + \dots + \frac{R_F}{R_N} V_N \right)$$

special case: when  $R_1 = R_2 = R_3 = \dots = R_N = R$

$$\text{then } V_o = -\frac{R_F}{R} (V_1 + V_2 + V_3 + \dots + V_N)$$

$V_1, V_2, V_3 \rightarrow$  Can be D.C or A.C signals.

Ex Design a summing Amp to have :-

i)  $V_o = -(3V_1 + 5V_2 + 10V_3)$

ii)  $V_o = -20 (V_1 + V_2 + V_3)$

Soln: i)  $\frac{R_F}{R_1} = 3, \quad \frac{R_F}{R_2} = 5, \quad \frac{R_F}{R_3} = 10$

Let  $R_F = 30 \text{ k}\Omega$ .


$30 = 3R_1 \rightarrow R_1 = 10k\Omega$

$30 = 5R_2 \rightarrow R_2 = 6k\Omega$


$30 = 10R_3 \rightarrow R_3 = 3k\Omega$

2) For  $V_1 = -5V_{d.c}$ ,  $V_2 = 2V_{d.c}$ ,  $V_3 = 0.2 \sin(\omega t)$   
 Find  $V_o(t)$  & draw  $V_o(t)$

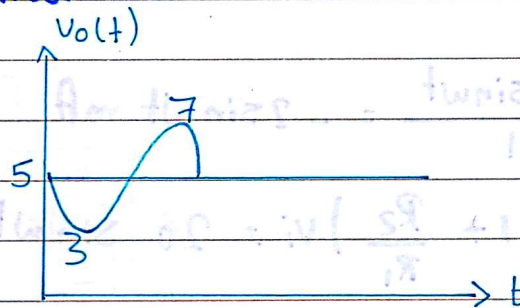i)  $V_o = -(-5 \times 3 + 5 \times 2 + 10 \times 0.2 \sin \omega t)$   
 $= -(-5 + 2 \sin \omega t)$   
 $= 5 - 2 \sin \omega t$



3) Non-Inverting Amp:

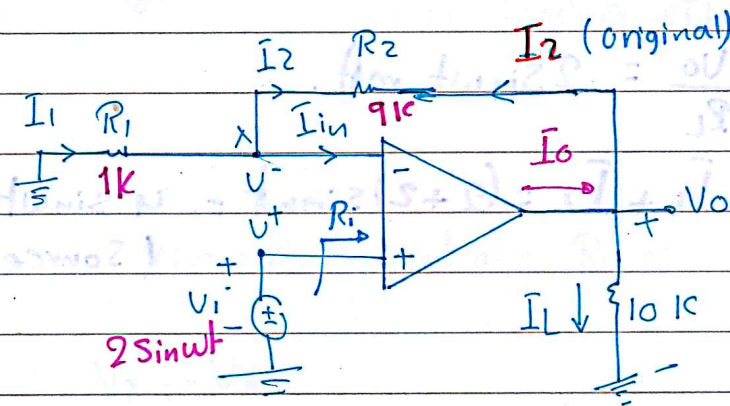

Find  $I_1, I_2, I_L, I_o$ ?

$I_1 = I_{in} + I_2$

$\frac{0 - V_x}{R_1} = \frac{V_x - V_o}{R_2}$



Sunday 14.8.2016

but for ideal op-amp:

$$I_{in} = 0$$

$$V^+ = V^- = V_x = V_i \text{ (Virtual short).}$$

$$\frac{-V_i}{R_1} = \frac{V_i - V_o}{R_2}$$

$$\frac{-V_i R_2}{R_1} = V_i - V_o \rightarrow V_o = V_i \left(1 + \frac{R_2}{R_1}\right)$$

$$A_V = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1} \text{ closed loop gain.}$$

$$R_{in} = \infty$$

$$I_1 = \frac{0 - 2 \sin \omega t}{1} = -2 \sin \omega t \text{ mA}$$


$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i = 20 \sin \omega t \text{ V}$$

$$I_2 = \frac{V_x - V_o}{R_2} = \frac{2 \sin \omega t - 20 \sin \omega t}{9} = \frac{-18 \sin \omega t}{9} \\ = -2 \sin \omega t.$$

$$I_L = \frac{V_o}{R_L} = 2 \sin \omega t \text{ mA.}$$

$$I_o = I_1 + I_2 = (2 + 2) \sin \omega t = 4 \sin \omega t \\ \text{(Source current).}$$

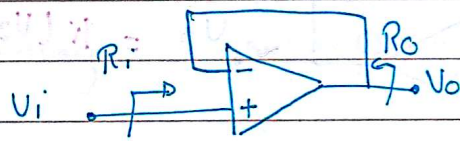41 Voltage Follower  
(special case of Non-Inverting Amp)



used to solve the loading effect problem.


$V_o = V_i \rightarrow A_v = 1$

$R_i = \infty$

$R_o = 0$

$\phi = 0^\circ$

# Ideal voltage follower

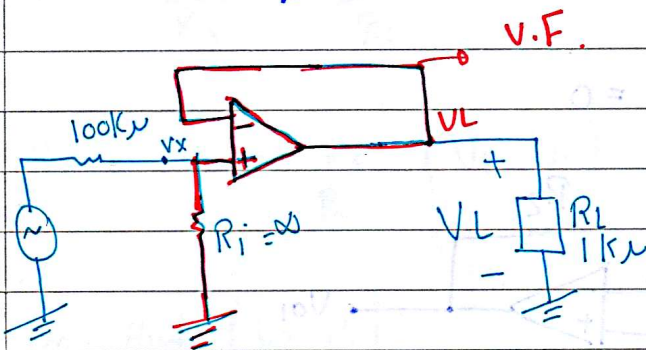

$V_L = \frac{V_s R_L}{R_L + R_s} = \frac{V_s \cdot 1}{101} = 0.01 V_s$

sever loading effect.


with V.F.:

$V_x = \frac{V_s R_i}{R_i + R_s}$ ,  $R_i \gg R_s$  (idealy  $R_i = \infty$ )

$V_x = V_s$

but  $V_L = V_x \therefore A_v = 1$


$\therefore V_L = V_x = V_s = 10 \sin \omega t$

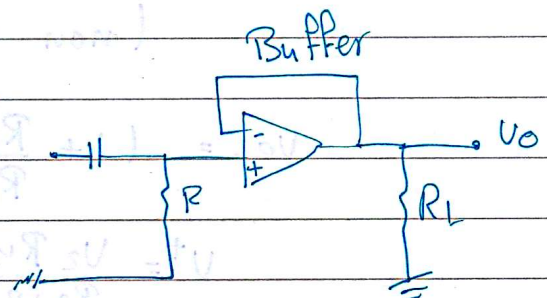



CH9  
5) Difference Amplifier


Monday 15-8-2016

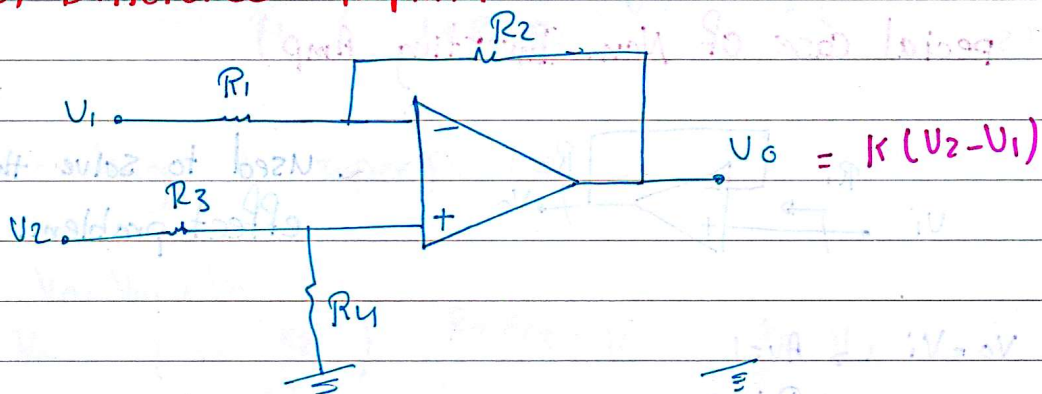

Using Superposition:

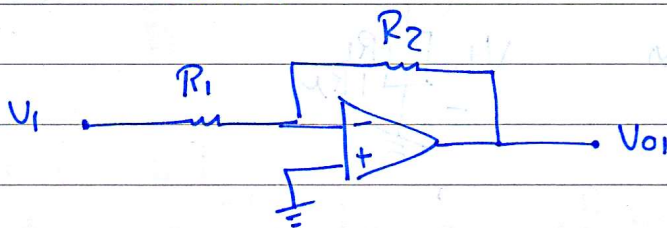
1) effect of  $(V_1)$ :  $V_2 = 0$

$$V^+ = \frac{V_2 \cdot R_4}{R_3 + R_4} = 0$$



$$V_{01} = \frac{-R_2}{R_1} V_1 \quad (\text{inverting Amp})$$

2) For  $V_2$ ,  $(V_1 = 0)$

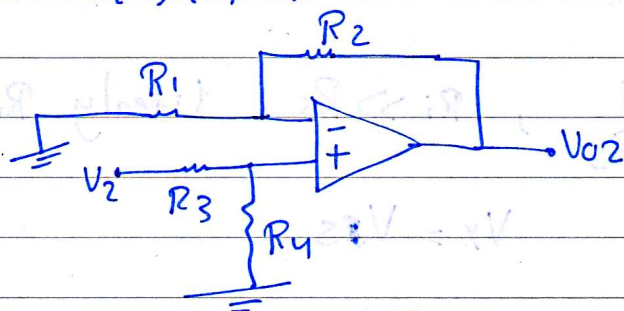

(non inverting Amp)

$$V_{02} = \left(1 + \frac{R_2}{R_1}\right) V^+$$

$$V^+ = \frac{V_2 R_4}{R_3 + R_4} = \frac{R_4 / R_3}{1 + R_4 / R_3} V_2$$

CH9

Monday 15-8-2016

$$V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \frac{R_4/R_3}{1 + R_4/R_3} V_2$$

According to super position :-

$$V_o = V_{o1} + V_{o2}$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \frac{R_4/R_3}{1 + R_4/R_3} V_2 - \frac{R_2}{R_1} V_1$$


For  $\frac{R_4}{R_3} = \frac{R_2}{R_1}$

then:  $V_o = \frac{R_2}{R_1} (V_2 - V_1)$


$$V_o = A_{vd} (V_2 - V_1)$$

$$A_{vd} = \frac{R_2}{R_1} \text{ (Differential gain of the Amp)}$$
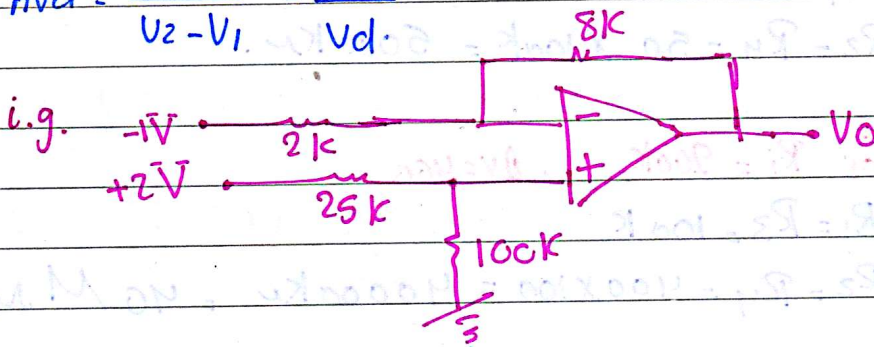
$$A_{vd} = \frac{V_o}{V_2 - V_1} = \frac{V_o}{V_d}$$



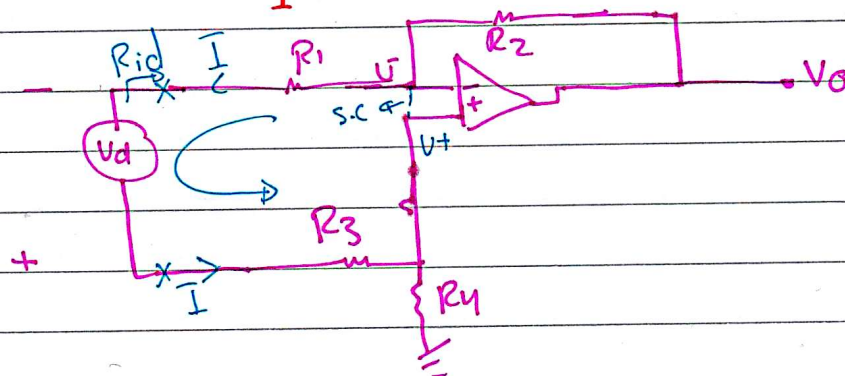To find  $R_{id} = \frac{V_d}{I}$  (input resistance)





$$-V_d + I R_3 + I R_1 = 0$$

$$\rightarrow \frac{V_d}{I} = R_{id} = R_1 + R_3$$

Ex) Design a difference Amp to have:  
1)  $R_i = 20k$  and  $A_{vd} = 50$

$$R_i = R_3 + R_1$$

To satisfy  $\frac{R_4}{R_3} = \frac{R_2}{R_1}$  we can choose

$$R_1 = R_3, R_2 = R_4 \text{ so } R_i = 2R_1 = 2R_3$$

For  $R_i = 20k\Omega$

$$R_1 = R_3 = 10k\Omega$$

$$A_{vd} = \frac{R_2}{R_1} = \frac{R_4}{R_3} \rightarrow 50 = \frac{R_2}{10k} \rightarrow R_2 = 500k\Omega = R_4$$

2)  $R_i = 200k$ ,  $A_v = 50$


$$R_1 = R_3 = 100k\Omega$$


$$R_2 = R_4 = 50 \times 100k = 5000k\Omega$$

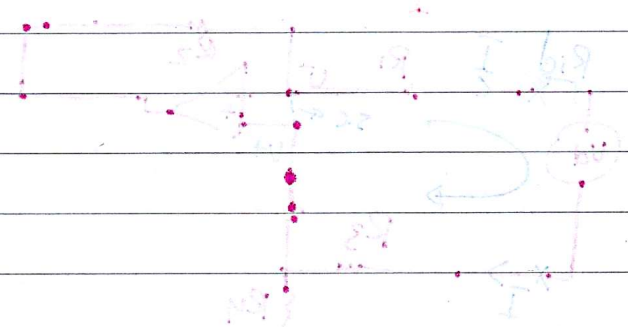3) For  $R_i = 200k$ ,  $A_v = 400$


$$R_1 = R_3 = 100k$$

$$R_2 = R_4 = 400 \times 100 = 40000k\Omega = 40M\Omega$$



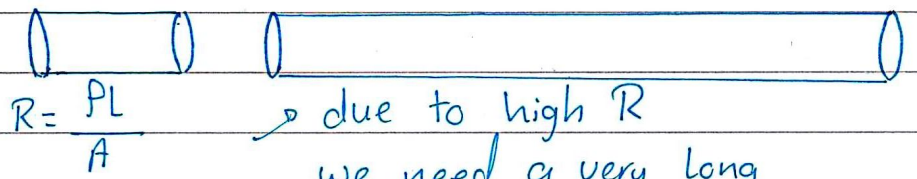

due to high R we need a very long cable.

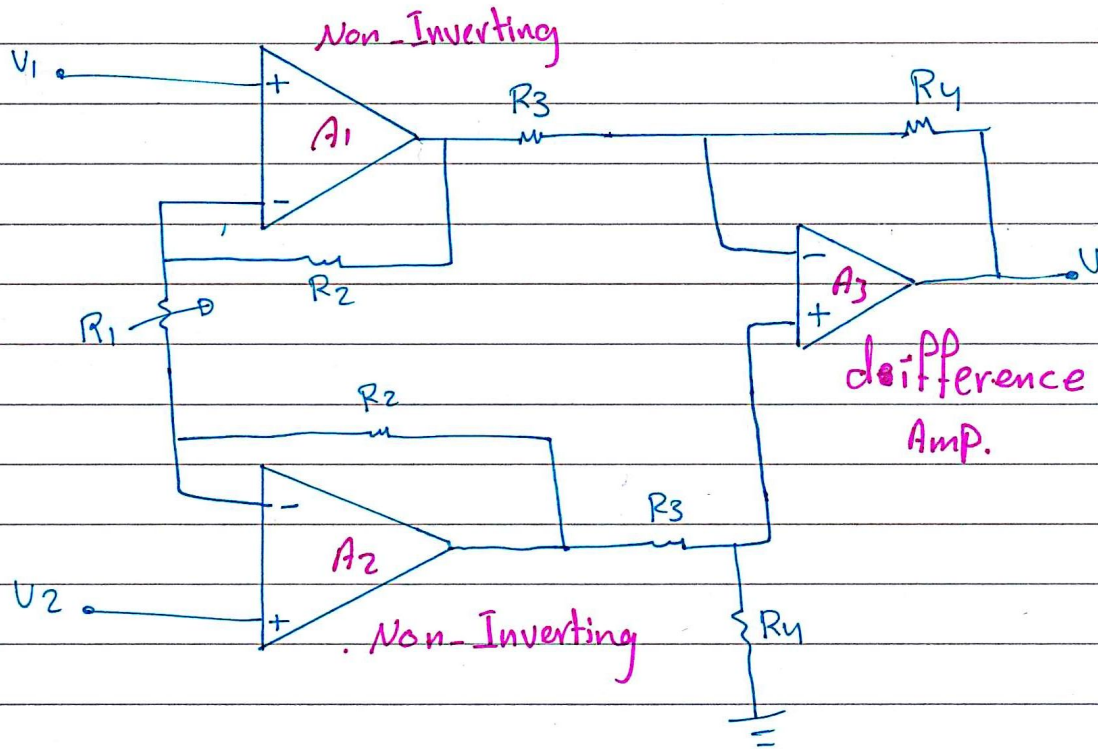

6) Instrumentation Amp


$$V_0 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (V_2 - V_1)$$

Single element dependent device.

$$A_d = \frac{V_0}{V_2 - V_1} = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$

Very high  $R_i, A_V$



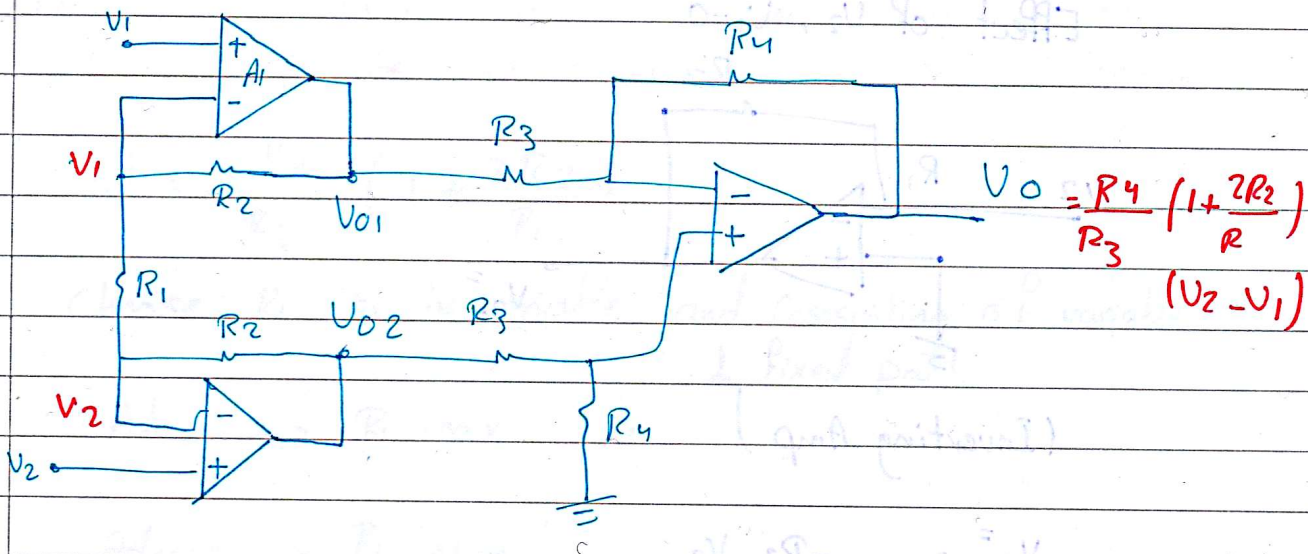

$$V_0 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (V_2 - V_1)$$

Instrumentation Amp.  
Very high I/P resistance.

high, adjustable and single element dependent gain  
using Resonable Resistor. values.


For Diff Amp A3 & with balance condition.

$$V_0 = \frac{R_4}{R_3} (V_{02} - V_{01})$$

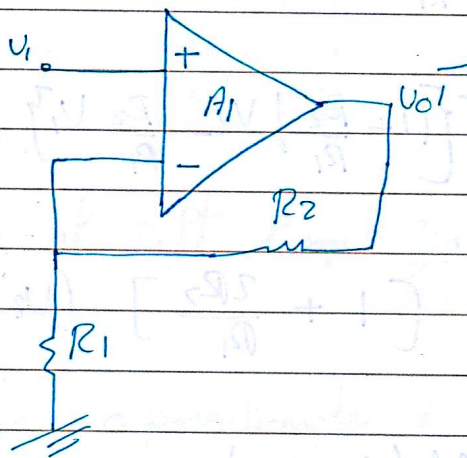
1) For A1 :: Use superposition.

if for V1  
(Non-Inverting)

$$V_{01}' = \left( 1 + \frac{R_2}{R_1} \right) V_1$$



Effect of  $V_2$ ,  $V_1=0$

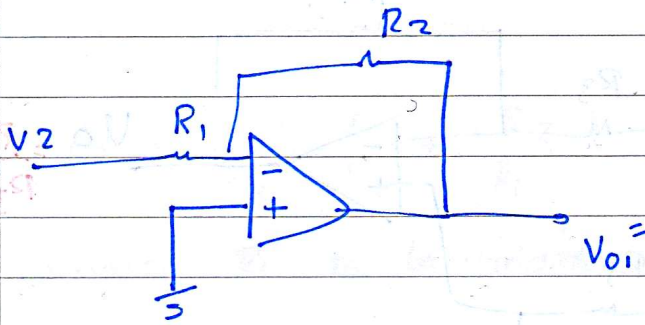


(Inverting Amp)

$$V_{01} = -\frac{R_2}{R_1} V_2$$

$$\begin{aligned} V_{01} &= V_{01}' + V_{01}'' \\ &= \left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2 \end{aligned}$$

2) For  $A_2$ :

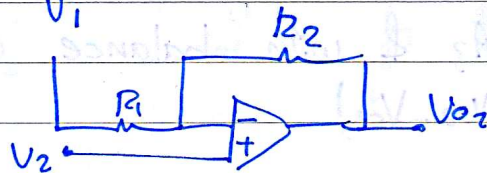

$$V_{02} = \left(1 + \frac{R_2}{R_1}\right) V_2 - \frac{R_2}{R_1} V_1$$

$$V_0 = \frac{R_4}{R_3} \left[ \left(1 + \frac{R_2}{R_1}\right) V_2 - \frac{R_2}{R_1} V_1 \right] - \left[ \left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2 \right]$$

$$= \frac{R_4}{R_3} \left[ 1 + \frac{2R_2}{R_1} \right] (V_2 - V_1)$$

$$V_0 = A_d (V_2 - V_1)$$

$$\text{where } A_d = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) = \frac{V_0}{V_2 - V_1}$$



CH9

Tuesday 16-8-2016




EXA: Design an I.A to have a gain ranging from (100 → 500) The max available resistor is 100kΩ.

$$A_d = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$


Choose  $R_1$  to be variable and consisting of a variable & fixed part.

$A_{dmin} \rightarrow R_1 \text{ max}$

$A_{dmax} \rightarrow R_1 \text{ min}$

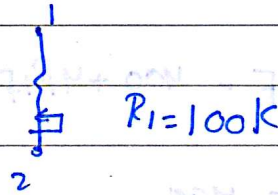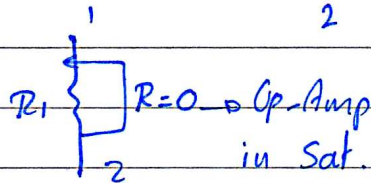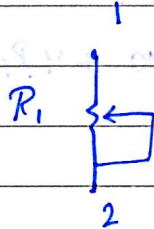

$$R_1 = R_{1V} + R_{1F}$$

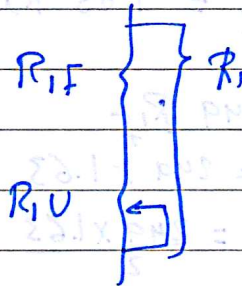

choose the gain of D.F.F Amp  $\frac{R_4}{R_3}$  to be 2,  $\frac{R_4}{R_3}$

Choose  $R_{1V}$  to be a potentiometer of 100 kΩ.

$$R_1 \text{ min} = 0 + R_{1F} = R_{1F}$$

$$R_1 \text{ max} = 100 + R_{1F}$$

CH9

Tuesday 16.8.2016

$$\text{Admin} \rightarrow R_1 \text{ max} \Rightarrow 100 + R_{1F}$$

$$\text{Ad max} \rightarrow R_1 \text{ min} \Rightarrow R_{1F}$$

$$500 = 2 \left( 1 + \frac{2R_2}{R_{1F}} \right) \Rightarrow 250 = 1 + \frac{2R_2}{R_{1F}}$$

$$2R_2 = 249 R_{1F} \quad \text{--- (1)}$$

$$10 = 2 \left( 1 + \frac{2R_2}{100 + R_{1F}} \right)$$

$$4 = \frac{2R_2}{100 + R_{1F}}$$

$$2R_2 = 400 + 4R_{1F}$$

Equate (1) &amp; (2)

$$249 R_{1F} = 400 + 4R_{1F}$$

$$245 R_{1F} = 400$$

$$R_{1F} = \frac{400}{245} = 1.63 \text{ k}\Omega$$

$$\text{From } 2R_2 = 249 R_{1F}$$

$$2R_2 = 249 \times 1.63$$

$$= \frac{249 \times 1.63}{2} = 203 \text{ k}\Omega$$

$$\frac{R_4}{R_3} = 2$$


$$R_4 = 2R_3$$

$$\bullet \text{ Choose } R_3 = 1 \text{ k}\Omega$$

$$R_4 = 2 \text{ k}\Omega$$



7) Current to Voltage Converter.

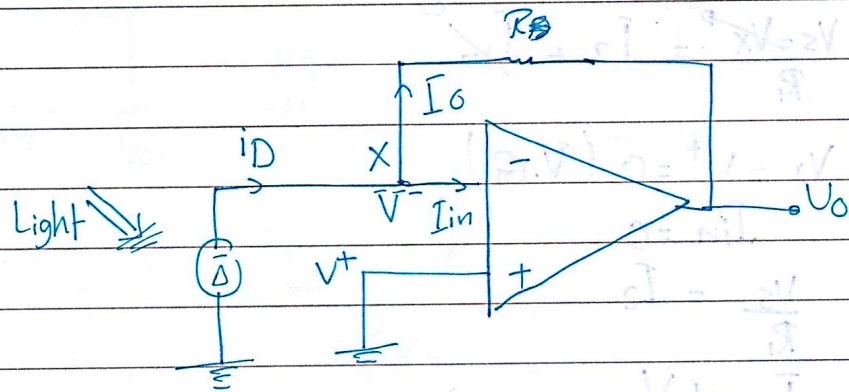

$V_o \propto i_D$   
KCL at Node (X)

$$i_D = I_{in} + I_o$$

$$i_D = I_{in} = \frac{V_x - V_o}{R}$$

For ideal op-Amp


$$I_{in} = 0, R_i = \infty$$

$$V^+ = V^- = V_x = 0 \text{ (V.G.)}$$

$$i_D = \frac{-V_o}{R} \Rightarrow V_o = -i_D R$$

$V_o \propto i_D$

8) Voltage to Current Converter.

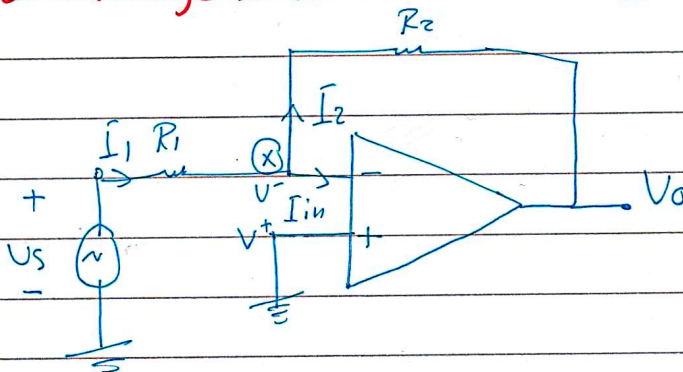

CH9

Tuesday 16.8.2016 16

$$I_1 = I_2 + I_{in}$$


$$\frac{V_s - V_x}{R_1} = I_2 + I_{in}$$

$$V_x = V^+ = 0 \text{ (V.G.)}$$

$$I_{in} = 0$$


$$\frac{V_s}{R_1} = I_2$$

$$I_2 \propto V_s$$

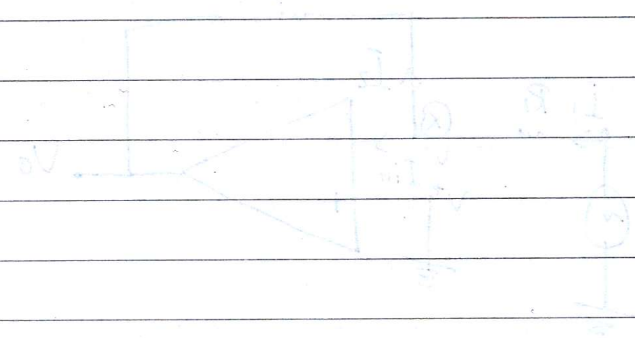



8) Integrator

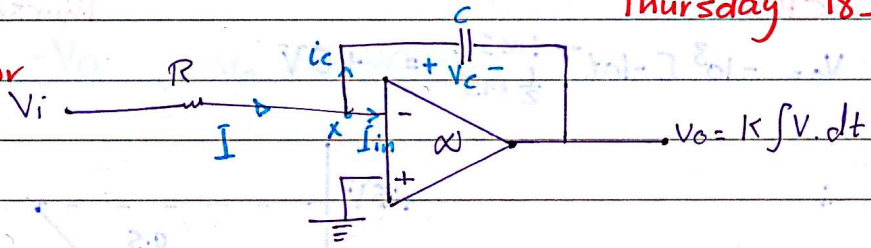

KCL at node (x):

$$I = I_{in} + i_c$$

$$\frac{V_i - V_x}{R} = I_{in} + C \frac{dV_c}{dt} ; \quad V_c = V_x - V_o = -V_o$$

but For Ideal Op Amp:


$$I_{in} = 0, \quad V^- = V^+ = V_x = 0 \quad (\bar{V}.G)$$

$$\frac{V_i}{R} = -C \frac{dV_o}{dt}$$

$$\int \frac{dV_o}{dt} = -\frac{1}{RC} \int V_i dt + K \quad \text{but } K=0 \text{ (initially uncharged)}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

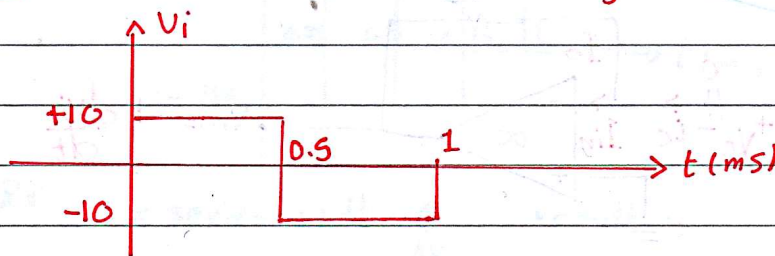Exa: Draw  $V_o(t)$  For the given  $V_i$ ; Given:  $R=1K$



$$C = 1\mu F$$

$$T = \frac{1}{f} = 1ms$$

$$f = 1KHz$$


1) For  $0 < t < \frac{1}{2}ms$ ;  $V_i = 10V$

$$V_o = \frac{-1}{10^3 \times 10^{-6}} \int_0^{0.5ms} 10 dt = -10^3 [10t]_0^{0.5ms}$$


$$= -10^3 \times 10 \times 0.5 \times 10^{-3} = -5V$$

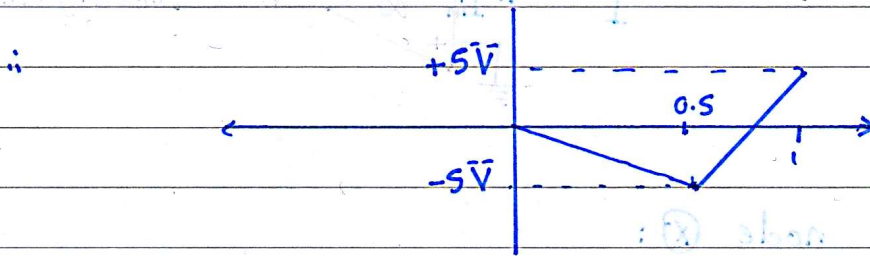2) For  $(\frac{1}{2} < t < 1)ms$ ;  $V_i = -10V$

$$V_o = -10^3 [-10] \frac{1\text{ms}}{\frac{1}{2}\text{ms}} = +5\text{V}$$



Note :-

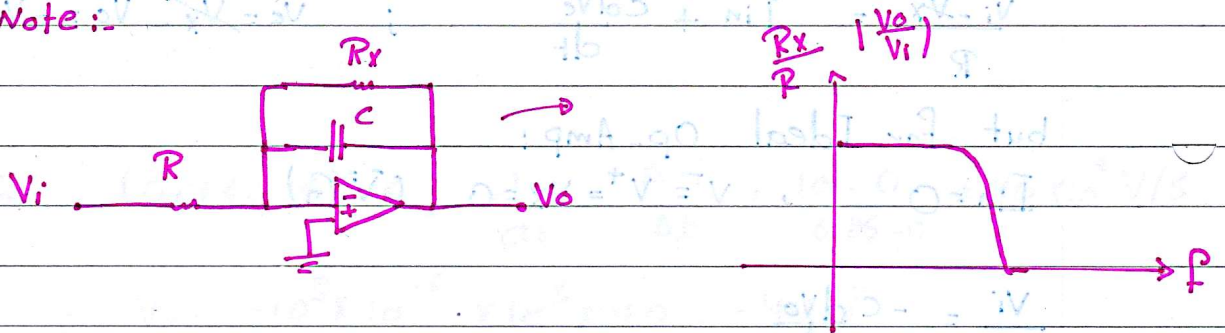


we put  $R_x$  because at Low Freq.  $C$  becomes an B.C. So the Op. Amp becomes Open Loop and works is sat. Regn. So to solve that we put  $R_x$ , it will make it works as an inverting Op. Amp at low Freq.

The same Reason

9) Differentiator

when  $f \rightarrow \infty$

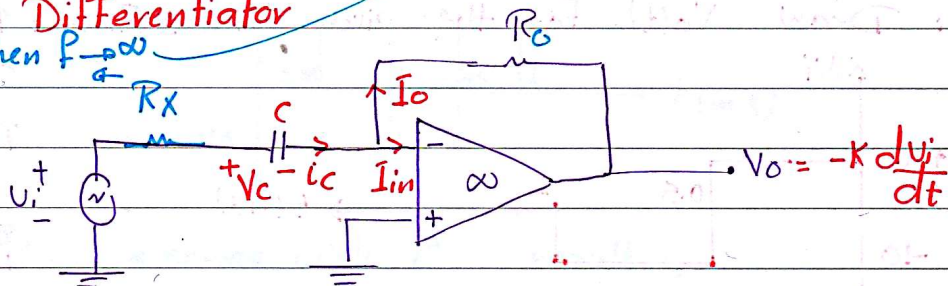

$$i_c = C \frac{dV_c}{dt} ; V_c = V_i - V_x$$

$$I_c = I_{in} + I_o$$


$$C \frac{d(V_i - V_x)}{dt} = I_{in} + \frac{V_x - V_o}{R_o} ; \text{but } I_{in} = 0, V^- = V^+ = V_x = 0 \text{ (V.G)}$$

For ideal Op. Amp.



$$RC \frac{dV_i}{dt} = -V_o \rightarrow V_o = -RC \frac{dV_i}{dt}$$

Ex

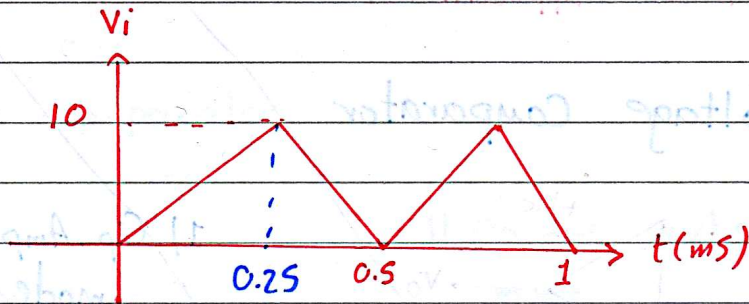


Given :  $R = 1\text{ k}\Omega$ ,  $C = 1\text{ }\mu\text{F}$ .

For  $(0 < t < 0.25)\text{ms}$  ;  $\frac{dV_i}{dt} = \frac{\Delta V_i}{\Delta t} = \frac{10 - 0}{0.25 - 0} = 40 \times 10^3 \text{ V/s}$


$$\therefore V_o = -10^3 \times 10^{-6} \times 40 \times 10^3 = -40 \text{ V}$$

For  $(0.25 < t < 0.5)\text{ms}$  ,  $\frac{\Delta V_i}{\Delta t} = \frac{(0 - 10)\text{V}}{(0.5 - 0.25)\text{ms}} = -40 \times 10^3 \text{ V/s}$
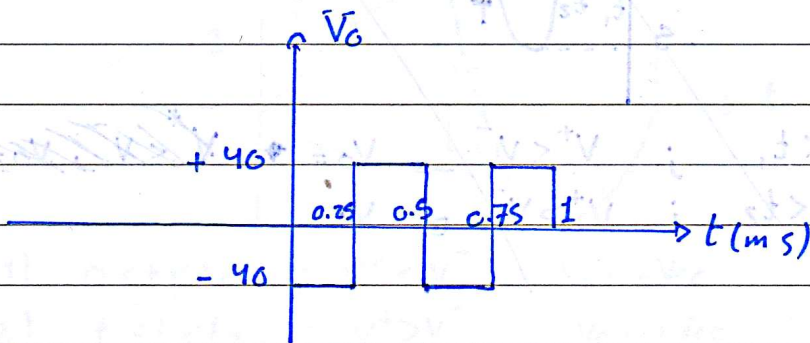
$$\therefore V_o = -10^3 \times 10^{-6} \times -40 \times 10^3 = 40 \text{ V}$$




R<sub>x</sub> in series with C result :-

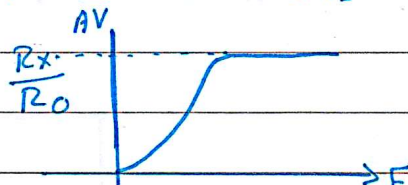


Non-Linear Applications

1] Voltage Comparator

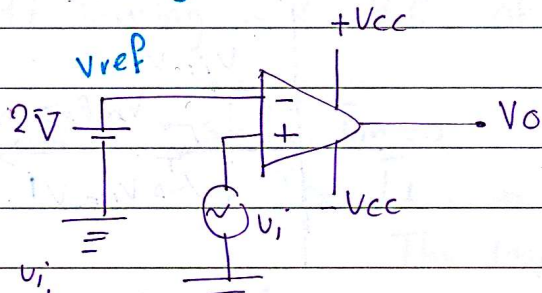

1) Op-Amp works in Open-loop mode

2)  $V_o = +V_{cc}$

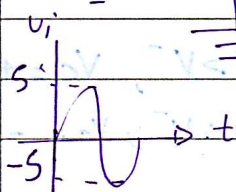


$V_o = A_{OL}(V^+ - V^-)$

For ideal op-Amp,  $A_{OL} = \infty$

1) if  $V^+ > V^- \therefore V_o = +V_{cc}$

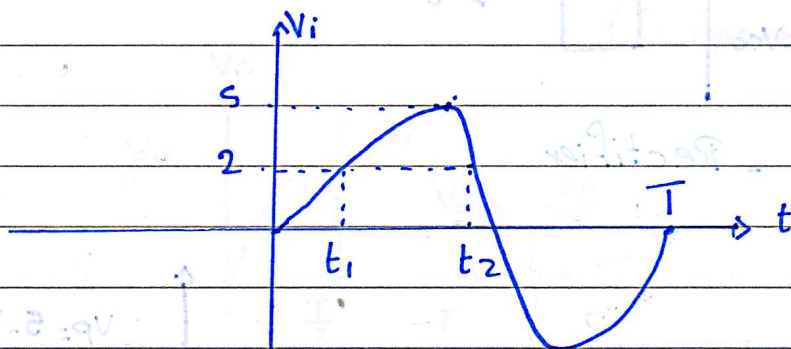
2) if  $V^+ < V^- \therefore V_o = -V_{cc}$



1)  $0 < t < t_1$  ;  $V^+ < V^- \rightarrow V_o = -V_{cc}$

2)  $t_1 < t < t_2$  ;  $V^+ > V^- \rightarrow V_o = +V_{cc}$


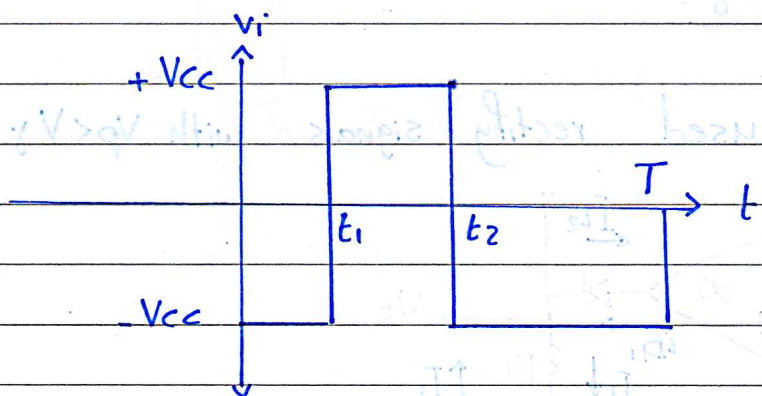
3)  $t_2 < t < T$  ;  $V^+ < V^- \rightarrow V_o = -V_{cc}$






2] Zero crossing detector.

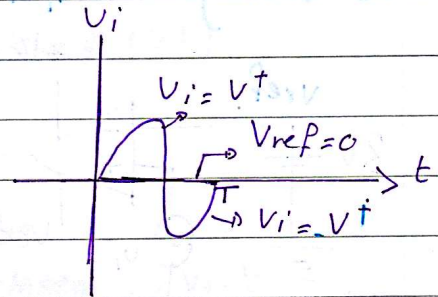
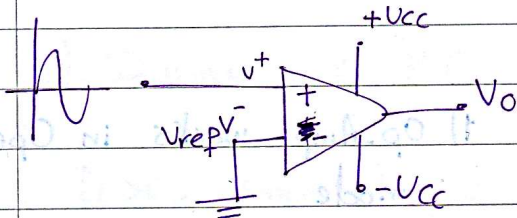
voltage comparator with  $V_{ref} = 0$  and  $V_o$  is symmetrical square wave (sin  $\rightarrow$  square)



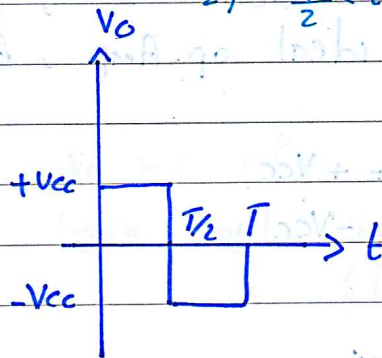- 1)  $0 < t < \frac{T}{2}$ ,  $V^+ > V^-$ ,  $V_o = +V_{cc}$
- 2)  $\frac{T}{2} < t < T$ ,  $V^+ < V^-$ ,  $V_o = -V_{cc}$




3] Precision Rectifier

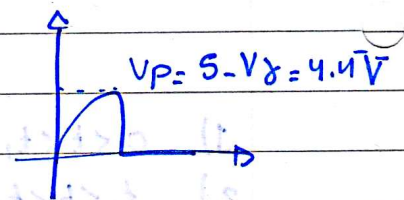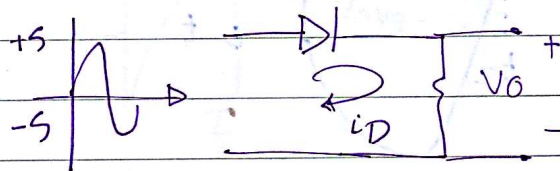


$$V_o = i_D R = \frac{V_i - V_\gamma}{R} \cdot R$$

$$i_D = \frac{V_i - V_\gamma}{R}$$

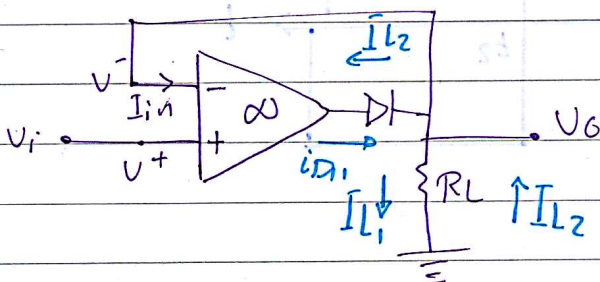Rectifiers used rectify signals with  $V_p < V_\gamma$



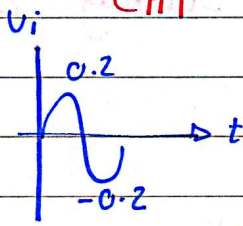



1) During +ve H.C of  $v_i$ ,  $v_o = v_i$  (V.F)



$I_L > 0$ , since  $I_{in} = 0$

$I_D = I_L \rightarrow D$  is On.

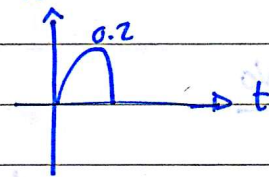The loop is closed  $\rightarrow v_o = v_i$




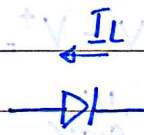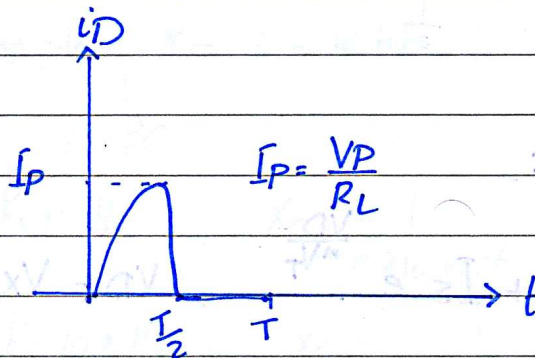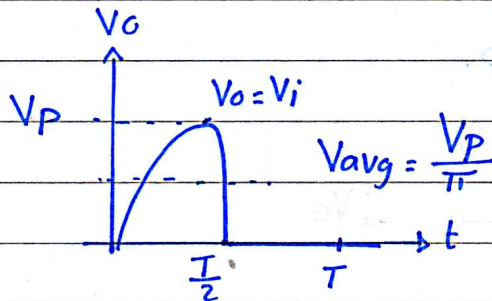2) During -ve H.C of  $v_i$   so diode is off (Open loop)  $v_o = \text{zero}$  ( $I_L$  opposes  $I_D$ )





4] exponential Amp.

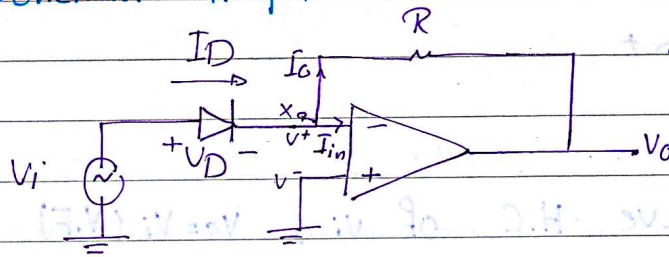

$$i_D = I_{in} + I_o$$


$$I_s e^{\frac{V_D}{nV_T}} = I_{in} + I_o, \quad V_D = V_i - V_x$$

$$I_s e^{\frac{V_i - V_x}{nV_T}} = I_{in} + \frac{V_x - V_o}{R}$$

but  $V_x = V^- = V^+ = \text{Zero}$  (Virtual ground) ideal op-Amp

$$V_o = -I_s R e^{\frac{V_i}{0.026}}$$

5] Logarithmic Amp.

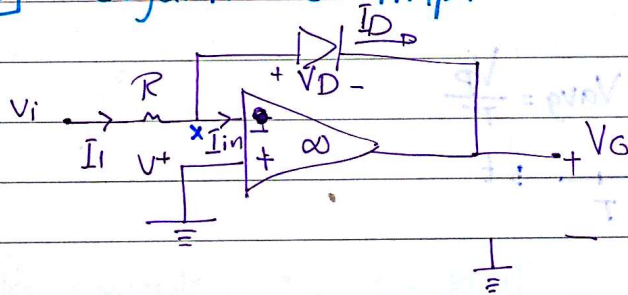

KCL at node X:

$$I_i = I_{in} + I_D$$

$$\frac{V_i - V_x}{R} = I_{in} + I_s e^{\frac{V_D}{nV_T}}, \quad V_D = V_x - V_o$$

but for ideal op-Amp:  $I_{in} = \text{Zero}$ ,  $V_x = V^- = V^+ = \text{Zero}$  (V.G)



$$\frac{V_i}{R} = I_s e^{-V_o/nV_T} \quad ; \quad \frac{V_i}{R I_s} = e^{-\frac{V_o}{nV_T}}$$

$$V_o = -nV_T \ln \frac{V_i}{R I_s} = -0.026 \ln \frac{V_i}{R I_s}$$

CH7

Frequency Response of Amp. Monday 22-8-2016

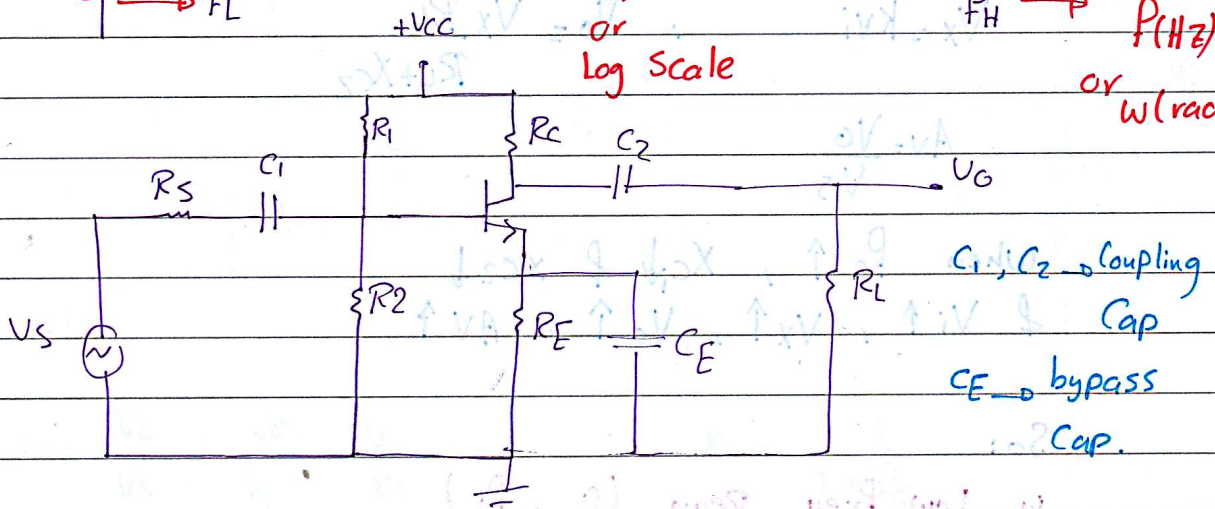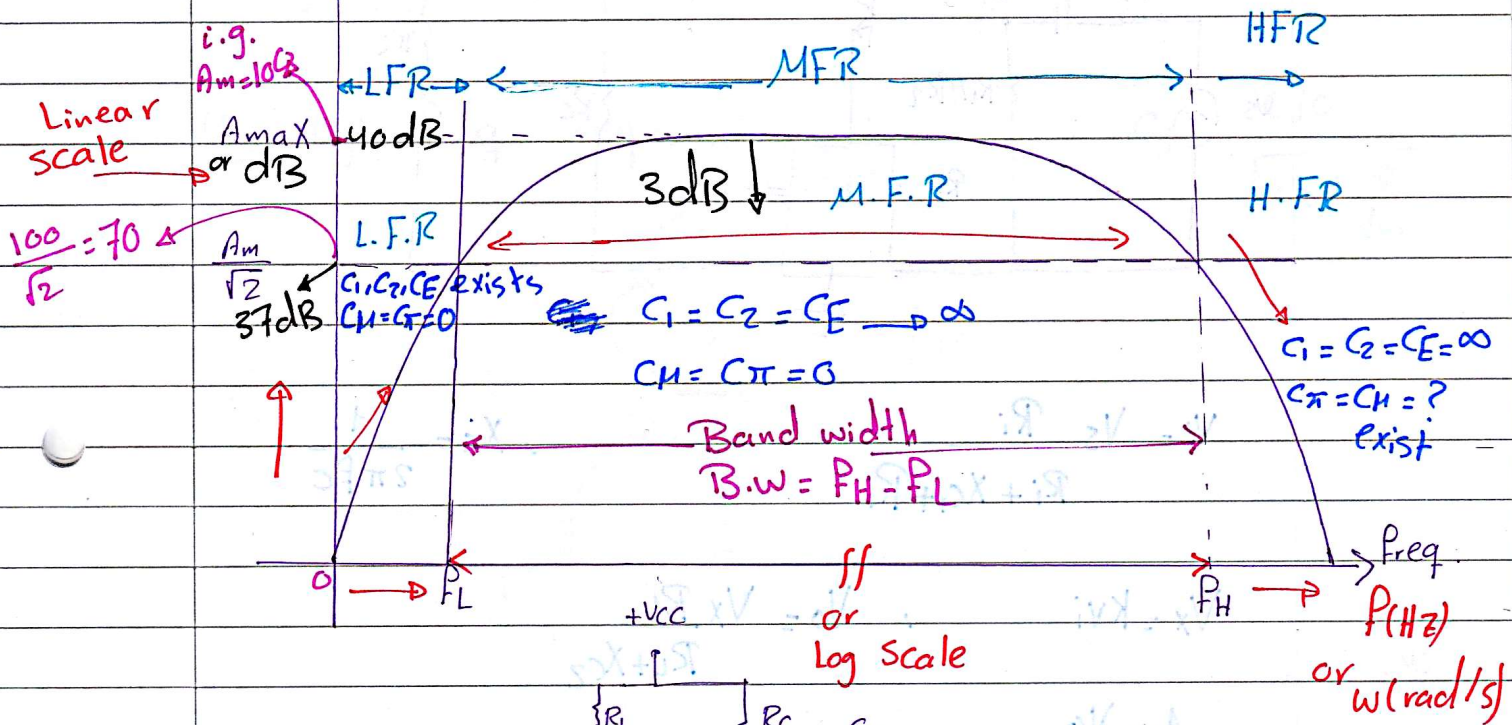$A_V$  or  $A_I \rightarrow$  Unitless or in dB  $\rightarrow$   $A_V(dB) = 20 \log \frac{V_o}{V_s}$   
 $A_I(dB) = 20 \log \frac{I_o}{I_s}$



For example  $C_1 = 10 \mu F$

$X_C = \frac{1}{2\pi f C}$


For  $f = 10 \text{ Hz} \rightarrow X_C = \frac{1}{2\pi \times 10 \times 10^{-6}} = 1.7 \text{ k}\Omega$

For  $f = 10 \text{ kHz} \rightarrow X_C = \frac{1}{2\pi \times 10^4 \times 10^{-6}} = 1.7 \mu\Omega$

For  $f = 100 \text{ kHz} \rightarrow X_C = 0.17 \mu\Omega$



① Low Freq. Regn.

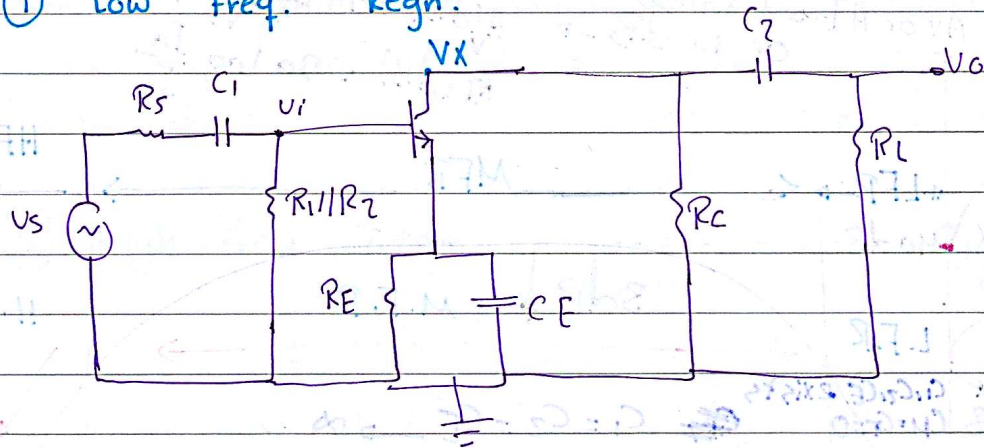

$$V_i = V_s \frac{R_i}{R_i + X_{C1} + R_s} \quad , \quad X_{C1} = \frac{1}{2\pi f C_1}$$

$$V_x = K V_i \quad , \quad V_o = V_x \frac{R_L}{R_L + X_{C2}}$$

$$A_v = \frac{V_o}{V_s}$$

when  $f_c \uparrow$ ,  $X_{C1} \downarrow$  &  $X_{C2} \downarrow$   
 &  $V_i \uparrow$ ,  $V_x \uparrow$ ,  $V_o \uparrow$ ,  $A_v \uparrow$


So:

in Low Freq. Regn ( $0 \rightarrow f_L$ )

In this Regn, the gain is Freq. dependant, such that as  $f \uparrow$ ,  $A \uparrow$ , Due to effect of coupling ( $C_1, C_2$ ) and bypass  $C_E$  capacitor, where as  $f \uparrow$ ,  $X_c \downarrow$  and since they are in series path of signal so  $V_o \uparrow$ ,  $A_v \uparrow$

$$V_s = 5 \sin(2\pi f t)$$

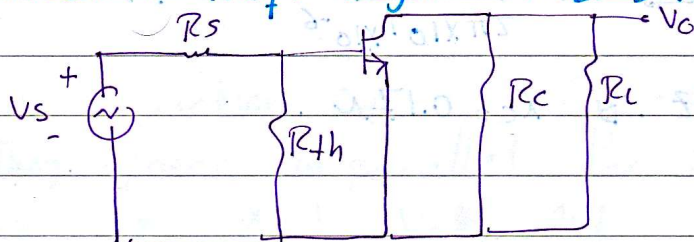② Medium Freq. Regn ( $f_L \rightarrow f_H$ )





$$A_v = \frac{R_i}{R_i + R_s} [g_m (R_c || R_L)]$$

- In this Regn; All capacitors are considered (short ckt)
- The Amp will behave as a pure resistance Amp and the gain will be Freq. independant.

③ High Freq. Regn.
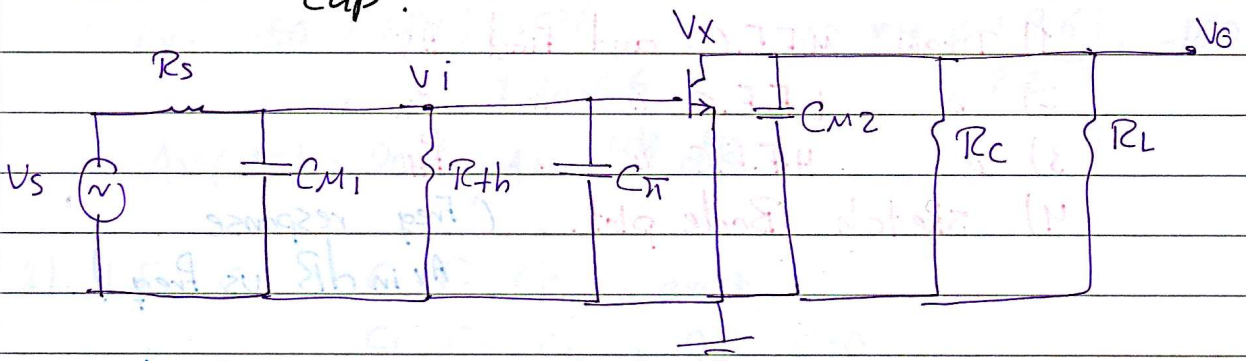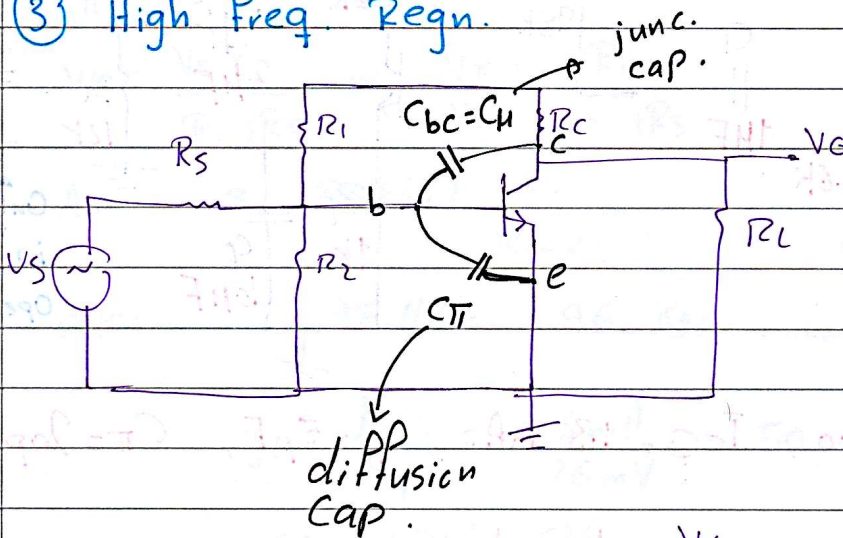
$$C_j = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_{bi}}}}$$



$$A_v = \frac{V_0}{V_s} = \frac{V_0}{V_i} \cdot \frac{V_i}{V_s}, \quad X_c = \frac{1}{2\pi f C}$$

$$V_i = \frac{Z_i \cdot V_s}{Z_i + R_s}, \quad V_0 = K V_i = -g_m V_{\pi} (R_c \parallel R_L \parallel X_{cM2})$$

- In this Regn all Coupling cap and bypass cap are s.c but new stray capacitance appear effectively (No physical existance)


( $C_{\mu} \rightarrow$  junction cap.,  $C_{\pi} \rightarrow$  diff cap.)

They appear in parallel for i/p and O/p side as  $f \uparrow, X_c \downarrow, V_0 \downarrow, A_v \downarrow$

The value of  $C_{\pi}$  and  $C_{\mu}$  at low and Medium Rgn. is = Zero




Freq. response Analysis : C.E. Amplifier

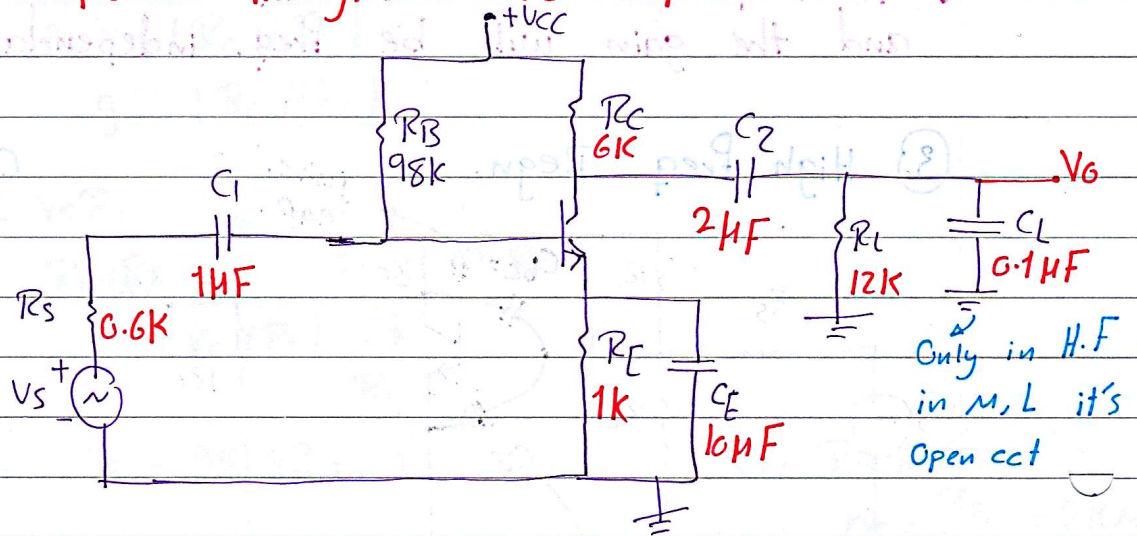

Given  $\beta = 100$ ,  $I_{CQ} = 1.3 \text{ mA}$ ,  $C_{\mu} = 5 \text{ pF}$ ,  $C_{\pi} = 20 \text{ pF}$

- 1) Draw M.F.E.C and find  $A_V$
- 2) " L.F.E.C " "  $P_L$
- 3) " H.F.E.C " "  $P_H$
- 4) sketch Bode plot. ( Freq response  $A_V$  in dB vs Freq )

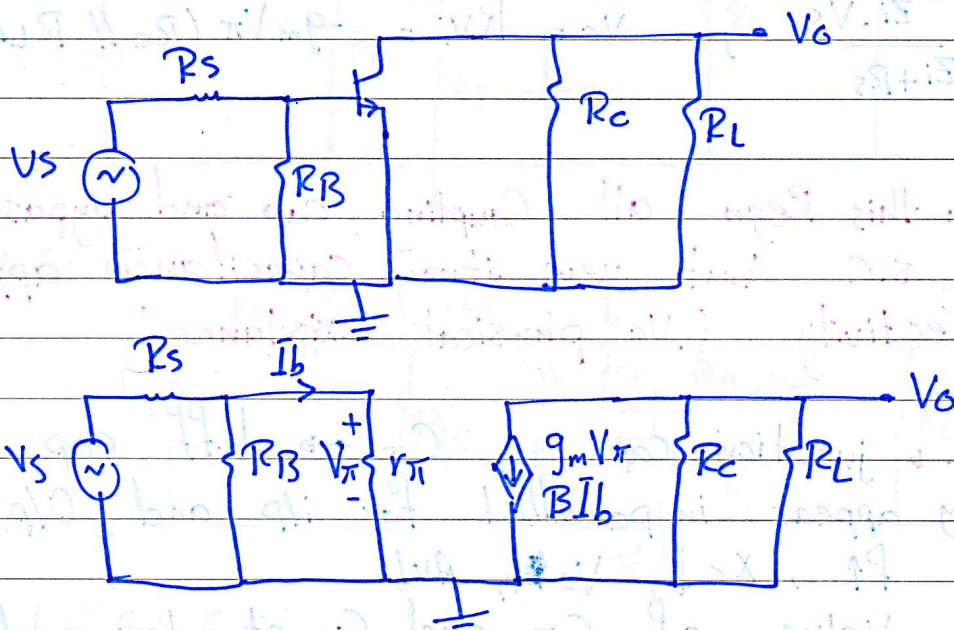1) M.F.E.C,  $C_1, C_2, C_E \rightarrow$  S.C.  
 $C_{\mu}, C_{\pi}$  and  $C_L \rightarrow$  O.C



$$A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{\pi}} \cdot \frac{V_{\pi}}{V_s}$$

$$V_o = -g_m V_{\pi} (R_c \parallel R_L)$$

$$\frac{V_o}{V_{\pi}} = -g_m (R_c \parallel R_L)$$

$$V_{\pi} = \frac{V_s R_i}{R_i + R_s} \Rightarrow \frac{V_{\pi}}{V_s} = \frac{R_i}{R_i + R_s}$$

$$A_v = -g_m (R_c \parallel R_L) \cdot \frac{R_i}{R_i + R_s}$$

~~A\_v~~  $R_i = 98 \parallel 2 = 1.96 \text{ k}\Omega$  ;  $R_i = R_B \parallel r_{\pi}$   
 $r_{\pi} = \frac{\beta V_T}{I_{CQ}} = 2 \text{ k}\Omega$


$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.3 \text{ mA}}{26 \text{ mV}} = 50 \text{ mA/V}$$

$$A_v = -50 (6 \parallel 2) \frac{1.96}{1.96 + 0.6} = -50 \times 4 \times \frac{1.96}{2.5} = -160$$


$$A_v (\text{dB}) = 20 \log A_v = 44 \text{ dB}$$

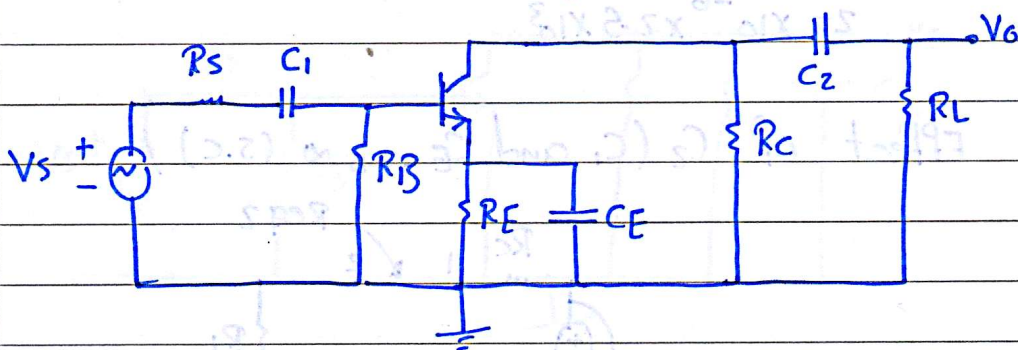2) L.F.E.C  $C_1, C_2, C_E \rightarrow$  exist

$C_L, C_{\pi}, C_{\mu} \rightarrow$  G.C  $C=0$



L.F.E.C :

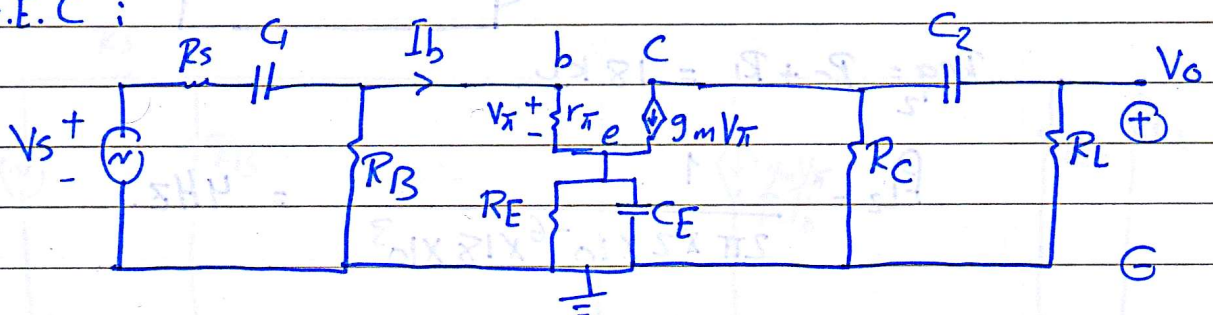

L.F.S.S.E.C




$$f_{L1} = \frac{1}{2\pi C_1 R_{eq1}}, \quad R_{eq1}: R_{th} \text{ seen by } C_1$$

$$f_{L2} = \frac{1}{2\pi C_2 R_{eq2}}, \quad R_{eq2}: R_{th} \text{ seen by } C_2$$

$$f_{LE} = \frac{1}{2\pi C_E R_{eqE}}, \quad R_{eqE}: R_{th} \text{ seen by } C_E$$

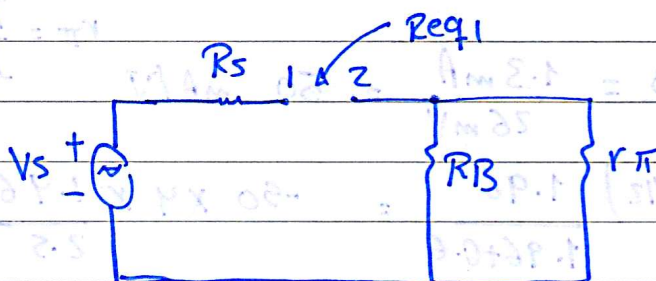
1 Effect of  $C_1 \rightarrow [C_2 \text{ and } C_E \rightarrow \infty]$



$$R_{eq1} = R_{i2} = R_s + R_i = 0.6 + 1.96 = 2.56 \text{ k}\Omega$$

$$f_{L1} = \frac{1}{2\pi \times 10^{-6} \times 2.5 \times 10^3} = 62 \text{ Hz}$$

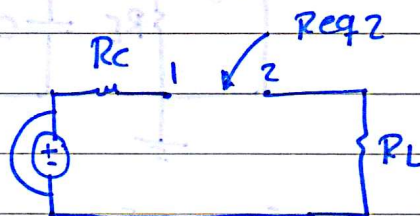
2 Effect of  $C_2 (C_1 \text{ and } C_E \rightarrow \infty \text{ (s.c)})$



$$R_{eq2} = R_c + R_L = 18 \text{ k}\Omega$$

$$f_{L2} = \frac{1}{2\pi \times 2 \times 10^{-6} \times 18 \times 10^3} = 4 \text{ Hz}$$

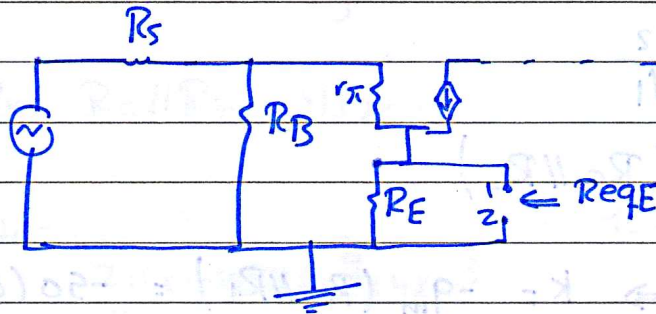3) Effect of  $C_E$  ( $C_1$  and  $C_2 \rightarrow$  S.C.)





$$R_{eqE} = \frac{[(R_s \parallel R_B) + r_{\pi}]}{\beta + 1} \parallel R_E = 24 \Omega$$

$$f_{LE} = \frac{1}{2\pi \times 10 \times 10^{-6} \times 24} = \frac{10^5}{48\pi} = 660 \text{ Hz}$$

$\therefore f_{LE} \text{ (effective)} = 660 \text{ Hz}$  (الانكسر)

$\therefore C_E$  determine  $f_L$  of the Amp.

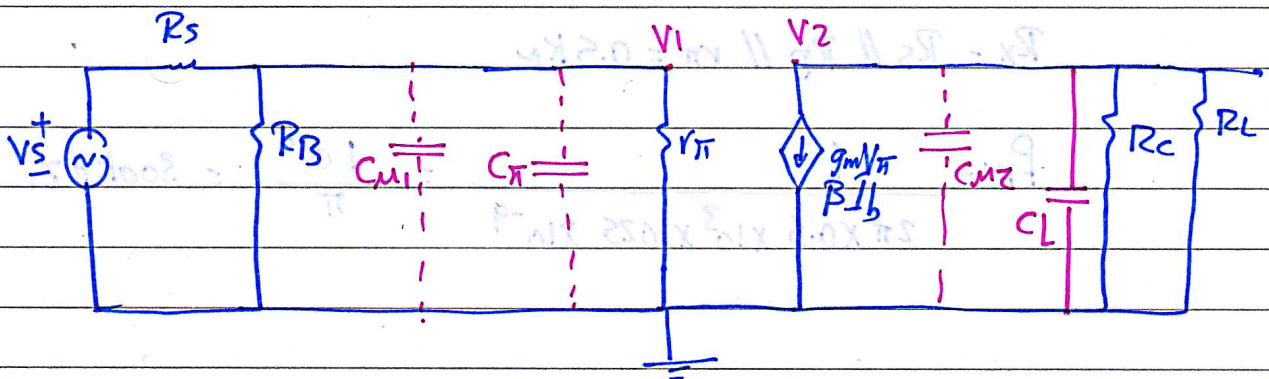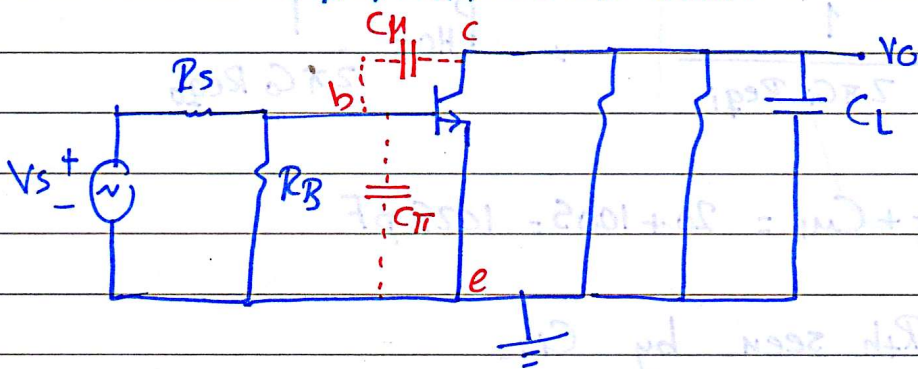3) H.F.R  $C_1, C_2, C_E \rightarrow$  S.C.  
 $C_{\mu}, C_{\pi}, C_L \rightarrow$  Exist.





$$C_{M1} = C_M (1-k) \quad , \quad C_{M2} = C_M \left(1 - \frac{1}{k}\right)$$


where  $k = \frac{V_2}{V_1}$

$$V_2 = -g_m V_\pi (R_C \parallel R_L)$$

$$V_1 = V_\pi \Rightarrow k = -g_m (R_C \parallel R_L) = -50 (6 \parallel 12) = -200$$

$$C_{M1} = 5 (1 + 200) = 1005 \text{ pF}$$
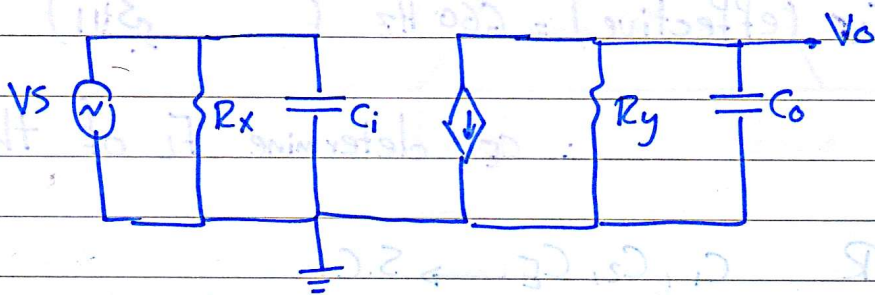
$$C_{M2} = 5 \left(1 - \frac{1}{200}\right) \approx 5 \text{ pF}$$



$$P_{Hi} = \frac{1}{2\pi C_i R_{eqi}} \quad , \quad P_{Ho} = \frac{1}{2\pi C_o R_{eqo}}$$

$$C_i = C_\pi + C_{M1} = 20 + 1005 = 1025 \text{ pF}$$

$R_x = R_{th}$  seen by  $C_i$ :

$$R_x = R_S \parallel R_B \parallel r_\pi = 0.5 \text{ k}\Omega$$

$$P_{Hi} = \frac{1}{2\pi \times 0.5 \times 10^3 \times 1025 \times 10^{-9}} = \frac{10^6}{\pi} = 300 \text{ kHz}$$

CH7.

Tuesday 23.8.2016


$$C_0 = C_{m2} + C_L = 5pF + 1nF = 1005pF.$$

$R_y = R_{th}$  seen by  $C_0$


$$R_y = R_c \parallel R_L = 4k\Omega.$$

$$f_{H0} = \frac{1}{2\pi \times 1.005 \times 10^{-9} \times 4 \times 10^3} = 40kHz.$$


$$\therefore f_H \text{ eff.} = 40kHz.$$

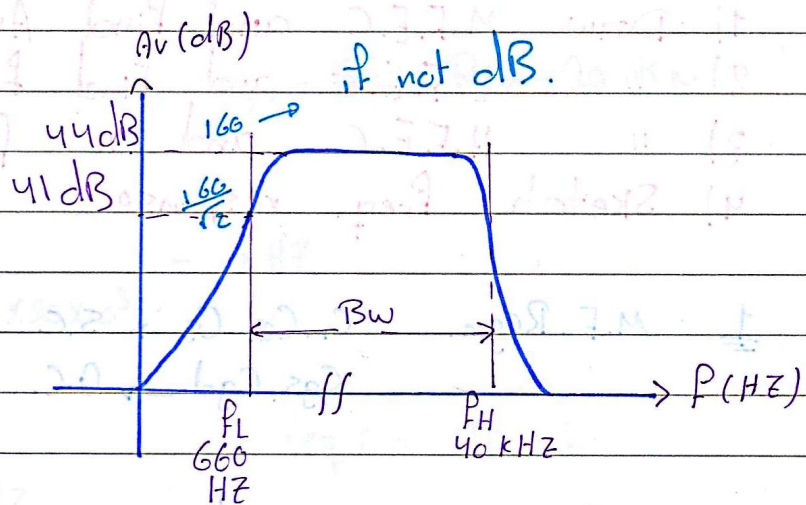

if all  $c \rightarrow \infty$

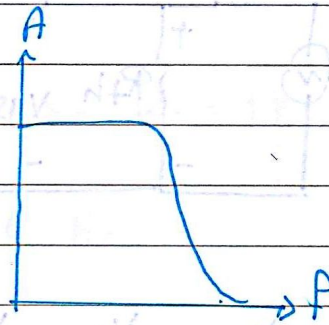





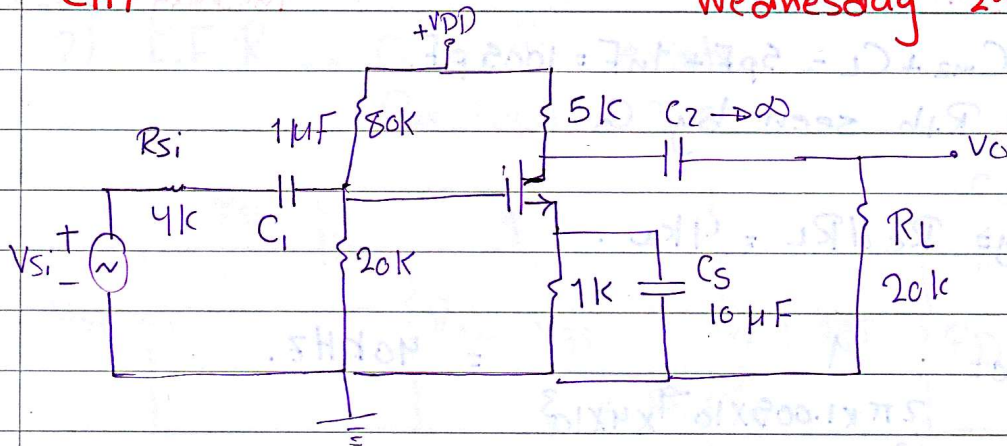

$K_n = 2 \text{ mA/V}^2$   
 $V_{TN} = 1 \text{ V}$   
 $I_{DQ} = 2 \text{ mA}$   
 $C_{gs} = 2 \text{ pF}$   
 $C_{gd} = 100 \text{ pF}$

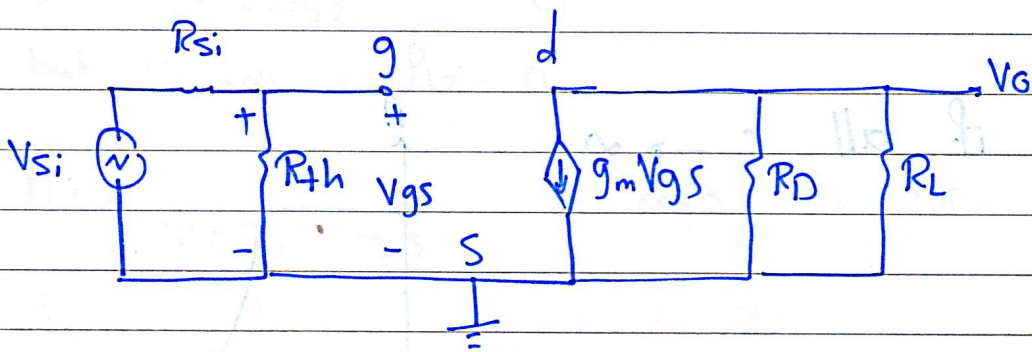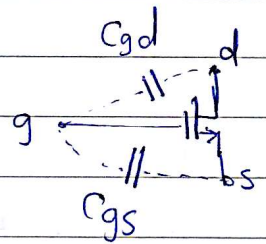- 1) Draw M.F.E.C and find  $A_{vm}$ .
- 2) " L.F.E.C and find  $f_L$
- 3) " H.F.E.C and "  $f_H$ .
- 4) Sketch Freq. response.

1 M.F. Regn.  $C_1, C_2, C_s \rightarrow \text{S.C.}$   
 $C_{gs}, C_{gd} \rightarrow \text{O.C.}$




$$A_v = \frac{V_o}{V_{si}} = \frac{V_o}{V_{gs}} \cdot \frac{V_{gs}}{V_{si}} = -g_m (R_D \parallel R_L) \cdot \frac{R_{th}}{R_{th} + R_{si}}$$

$$g_m = 2 \sqrt{K_n I_D} = 2 \sqrt{2 \times 2} = 4 \text{ mA/V}$$

$$A_v = -4 \times (5 \parallel 20) \left( \frac{16}{16+4} \right) = -16 \times 0.8 = -12.8 \rightarrow A_{vm} = 12.8$$

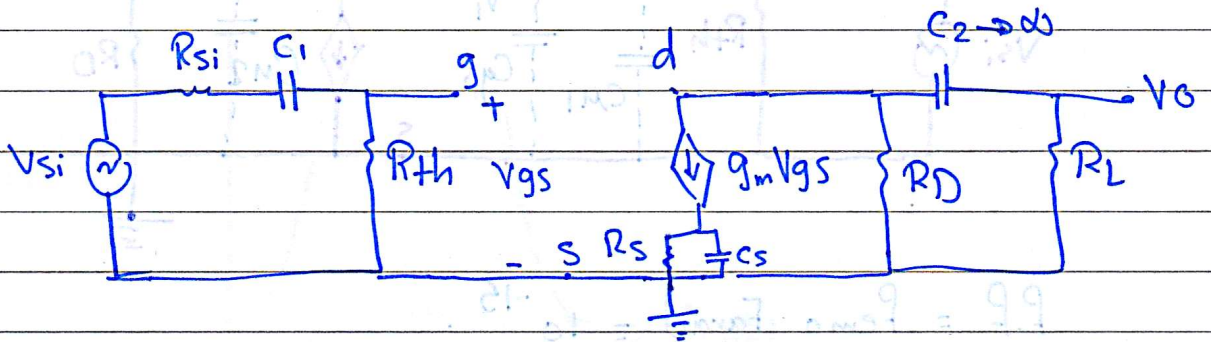2) L.F.R  $\rightarrow C_1, C_2, C_s$  exists.  
 $C_{gs}, C_{gd} \rightarrow O.C.$



$$P_{L1} = \frac{1}{2\pi C_1 \text{Req}_1}, \quad \text{Req}_1 = R_{si} + R_{th} = 20 \text{ K}\Omega$$

$$P_{L1} = \frac{1}{2\pi \times 1 \times 10^{-6} \times 20 \times 10^3} = 8 \text{ Hz}$$

$$P_{L2} = \frac{1}{2\pi C_2 \text{Req}_2}, \quad \text{Req}_2 = R_D + R_L$$


but  $C_2 \rightarrow \infty \therefore P_{L2} = 0$

$$P_{L3} = \frac{1}{2\pi C_s \cdot \text{Req}_s}, \quad \text{Req}_s = R_s = 1 \text{ K}$$


$$P_{L3} = \frac{1}{2\pi \times 10 \times 10^{-6} \times 1 \times 10^3} = 16 \text{ Hz}$$

$\therefore f_L = 16 \text{ Hz}$

3) H.F. Regn.

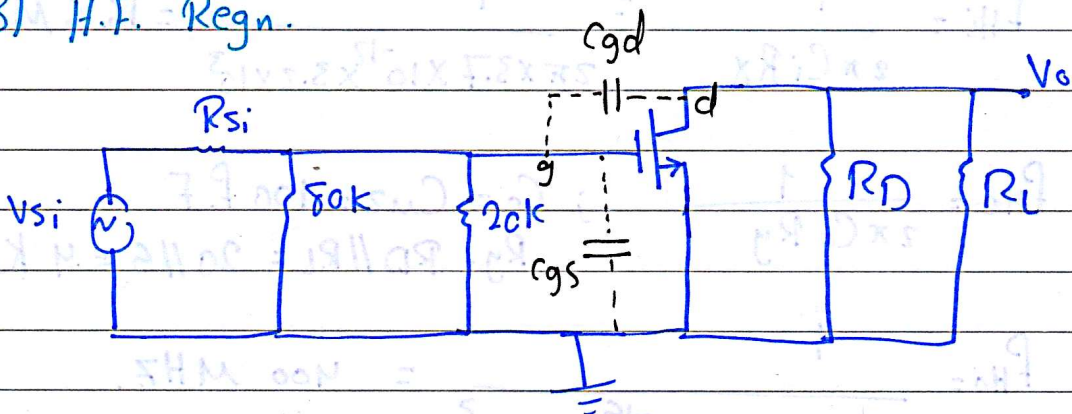



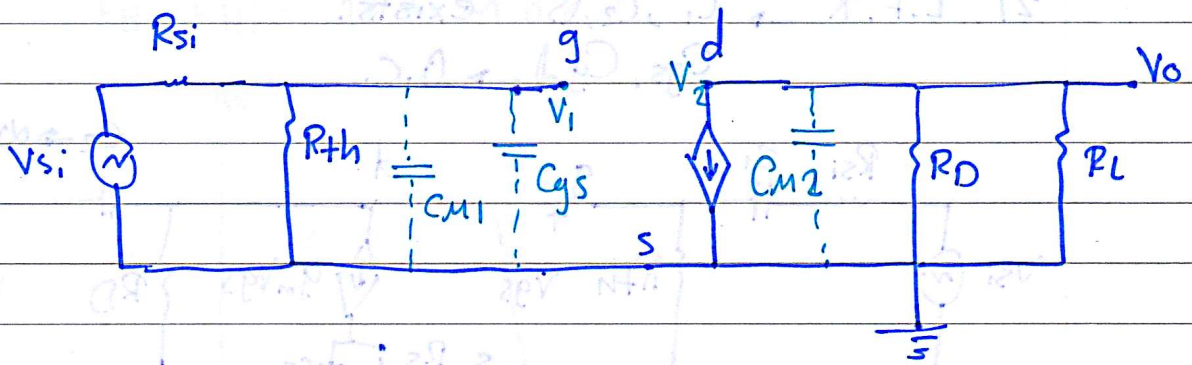


$$P.F = P_{\text{emo}} \text{ Farad} = 10^{-15}$$

$$C_{M1} = C_{gd} (1 - K) \quad ; \quad K = \frac{V_2}{V_1} = \frac{-g_m V_{gs} (R_D \parallel R_L)}{V_{gs}}$$

$$C_{M2} = C_{gd} \left(1 - \frac{1}{K}\right) = -g_m (R_D \parallel R_L) = -4 \times 4 = -16$$

$$C_{M1} = 100 \times 10^{-15} (1 + 16) = 1.7 \text{ pF}$$
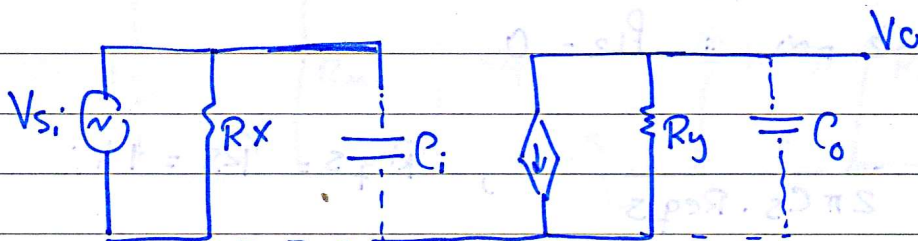
$$C_{M2} = 100 \times 10^{-15} \left(1 + \frac{1}{16}\right) \approx 100 \text{ pF}$$



$$C_i = C_{M1} + C_{gs} = (1.7 + 2) = 3.7 \text{ pF}$$

$$R_x = R_{th} \parallel R_{si} = 4 \parallel 16 = 3.2 \text{ k}\Omega$$



$$f_{Hi} = \frac{1}{2\pi C_i R_x} = \frac{1}{2\pi \times 3.7 \times 10^{-12} \times 3.2 \times 10^3} = 16.6 \text{ MHz}$$

$$f_{Ho} = \frac{1}{2\pi C_o R_y} \quad ; \quad C_o = C_{M2} = 100 \text{ pF}$$


$$R_y = R_D \parallel R_L = 20 \parallel 5 = 4 \text{ k}\Omega$$

$$f_{Ho} = \frac{1}{2\pi \times 100 \times 10^{-15} \times 4 \times 10^3} = 400 \text{ MHz}$$

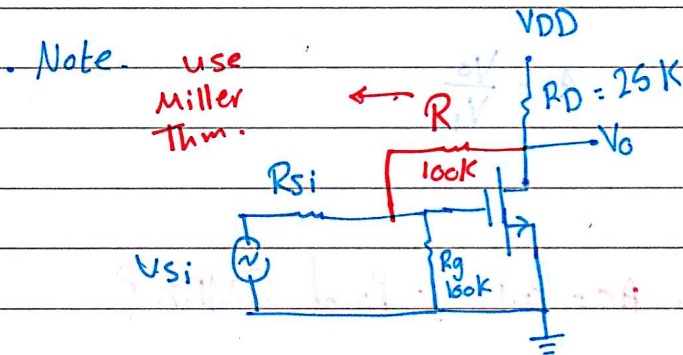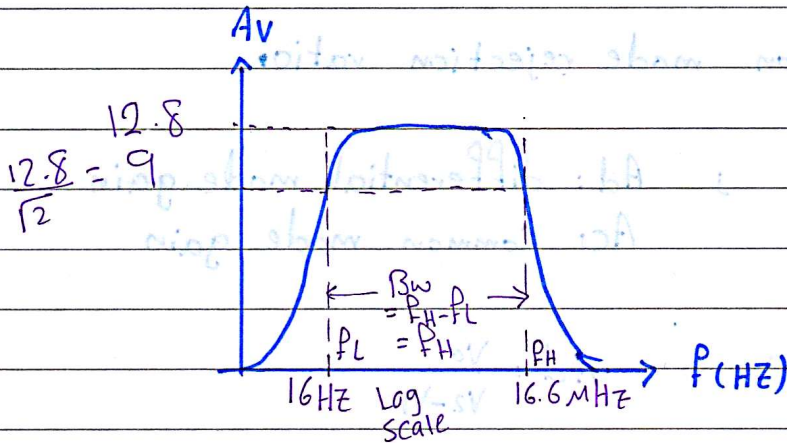$\therefore P_H = P_{Hi} = 16.6 \text{ MHz}$




Find  $A_v, R_o, R_i$

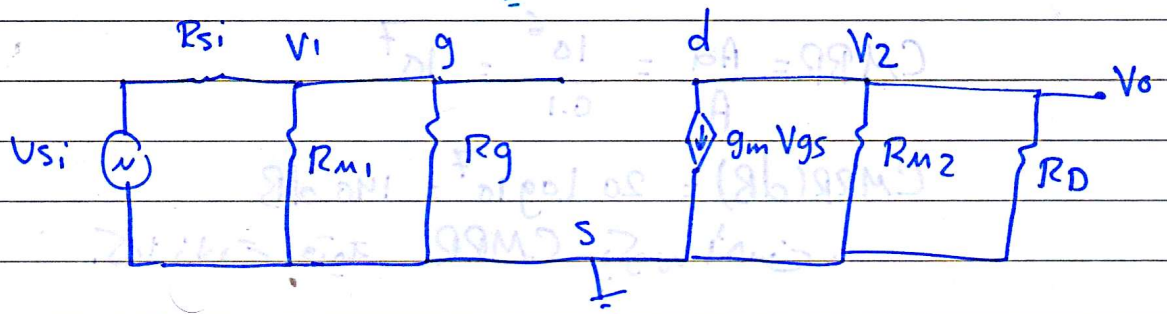

$R_{m1} = \frac{R}{1-k}$  ,  $R_{m2} = \frac{R}{1-1/k}$  ;  $k = \frac{V_2}{V_1}$

Miller Thm:

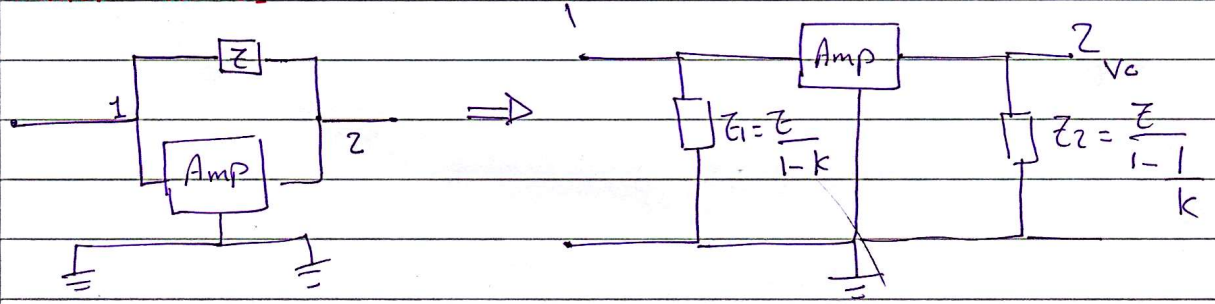





.Note

Wednesday 24-8-2016

Op-Amp

CMRR: Common mode rejection ratio,
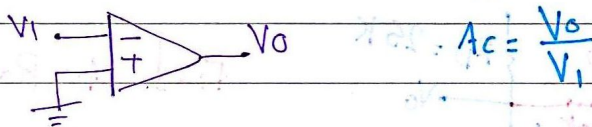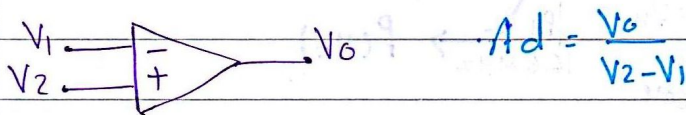
$$CMRR = \frac{A_d}{A_c} \quad ; \quad A_d: \text{differential mode gain} \\ A_c: \text{common mode gain}$$



Ex  $A_d = 10^6$ ,  $A_c = 0.1$ ; Find CMRR?

$$CMRR = \frac{A_d}{A_c} = \frac{10^6}{0.1} = 10^7$$

$$CMRR(\text{dB}) = 20 \log 10^7 = 140 \text{ dB}$$

كلما زادت قيمة CMRR كلما زادت نسبة الإشارة إلى الضوضاء.