

تقدم لجنة EiCoM الأكاديمية

دفتر لمادة:

دوائر كهربائية (1)

من شرح:

د. أشرف العلي

جزيل الشكر للطالب:

عمار أبو الروس



Sir

ایکسپریس

* Units Ohm's Law, ~~formula~~ units

Electrical cct :-

→ Voltage :- is the work needed to have a charge from one point in the cct. to the other [Unit: Volt Symbol (V)]

→ Current :- is the amount of charges that cross certain point in unit time. unit (Amperes) symbol (A)

$$I = \frac{\Delta Q}{\Delta t}$$

-ve charge = $1e = 1.6 \times 10^{-19}$


$i(t) = \frac{dq(t)}{dt} \Rightarrow q(t) = \int i(t) dt$




$$1A = \frac{1C}{1 \text{ second}} = \frac{1.6 \times 10^{-19} e/c}{1 \text{ second}} = \frac{1}{1.6} \times 10^{19} e/sec$$



→ Power :- is the energy dissipated by charge in certain load.

Unit: Watts symbol: W

* Resistor  unit (ohm), symbol Ω

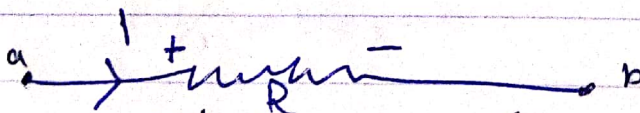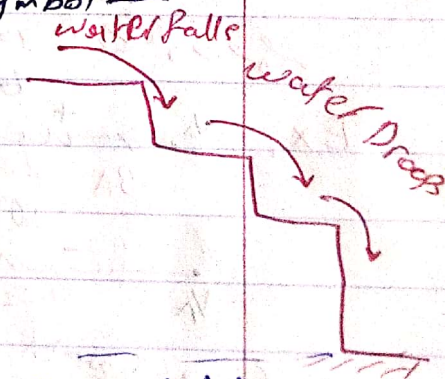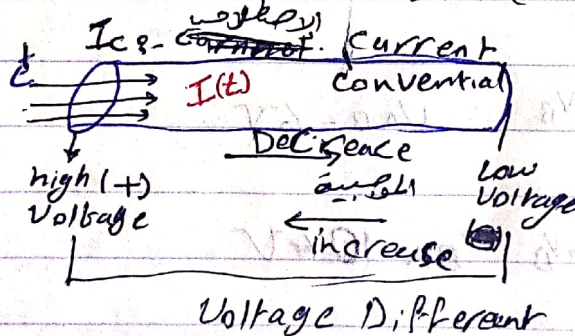


conventional current Technology

$$V_a > V_b \quad (V_{ab} = V_a - V_b) > 0$$

$$(V_{ba} = V_b - V_a) < 0$$

Ground $V=0$
اوپر

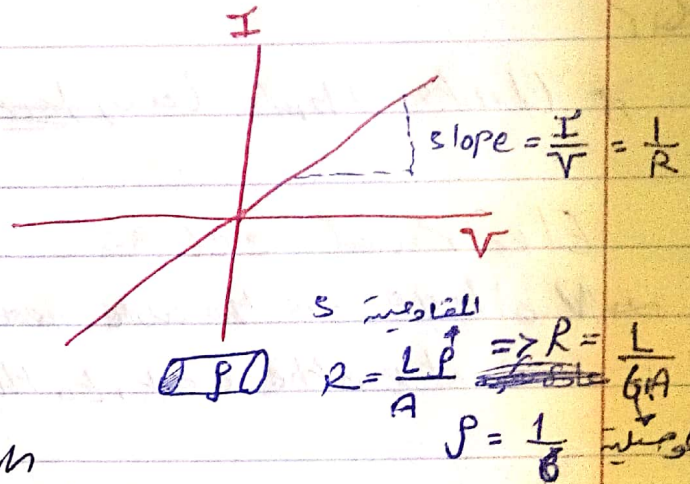
$$I = \frac{V}{R} \Rightarrow V = I \cdot R$$



✱

CCT, Definitions

Loop, Node, Ground, Branch

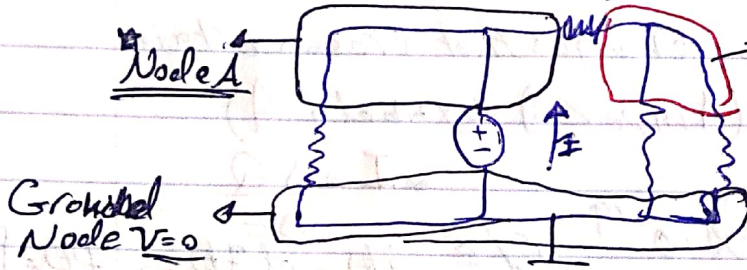

✱ **Ground**:- is part of CCT with zero potential to move charge. (zero volt)


✱ **Node**:- Part of CCT with same voltage value.

Node A $\Rightarrow V_A = ??$, Node B $\Rightarrow V_B = ??$


Ground Node $\Rightarrow V_{ref} = 0$

$V_A > V_B$, $V_A > V_{ref}$, $V_B > V_{ref} \Rightarrow V_A > V_B > V_{ref}$


عن فرق الجهد $I_c > 0$ يكون موجب

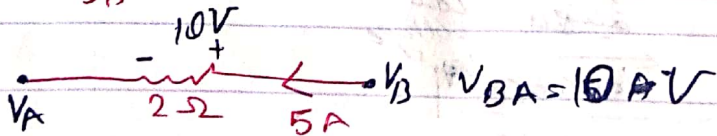

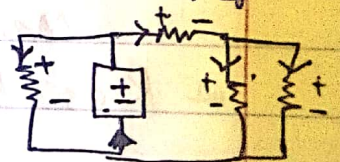إذا طلع I على نفس اتجاه التيار -
 أصغر من 0




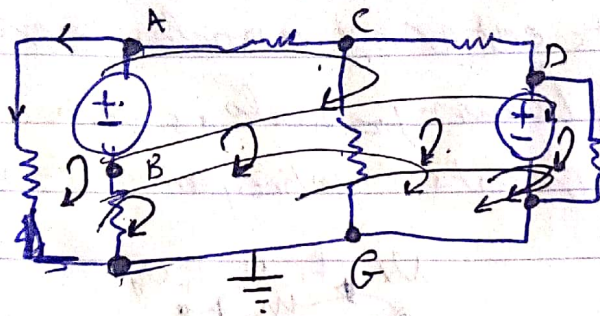Branch - Part of ckt in which the same current flow through it.



Branch 7 is
10 loops
4 MESHES


A.

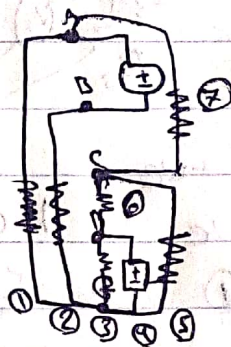


loop 3 - is a closed
Path in a ckt

MESH 3 - is a loop that
has no loops inside it

Circuit's Basics. & KVL laws.

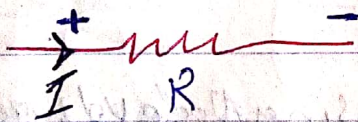
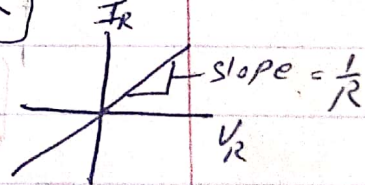
$$I = \frac{V}{R} \Rightarrow R = \frac{V}{I} \Rightarrow \boxed{\frac{I}{V} = \frac{1}{R}} \Rightarrow V = I \cdot R$$




KVL "Kerchhoffs-voltage law"

the sum of voltage differences current. among
loop is zero

$$-V_s + V_{R1} + V_{R2} = 0$$

$$-V_{R3} + V_{R1} + V_{R2} = 0$$

$$-V_s + V_{R3} = 0$$

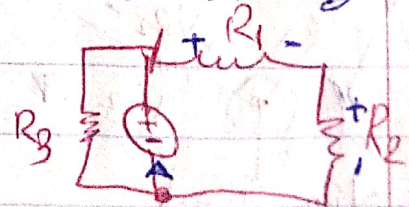


KCL :-

* sum of currents entering a node is zero

* sum of currents leaving a node is zero

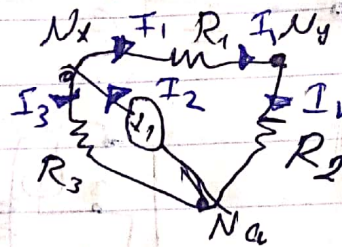Sum of currents entering a node = sum of currents leaving.



KCL @ Node Nx

Current entering \Rightarrow +ve

Leaving \Rightarrow -ve


$$-I_1 + I_2 - I_3 = 0 \quad \text{--- (1)}$$

KCL @ Ny

$$I_1 - I_2 = 0$$

KCL @ Na


$$+I_3 - I_2 + I_1 = 0$$

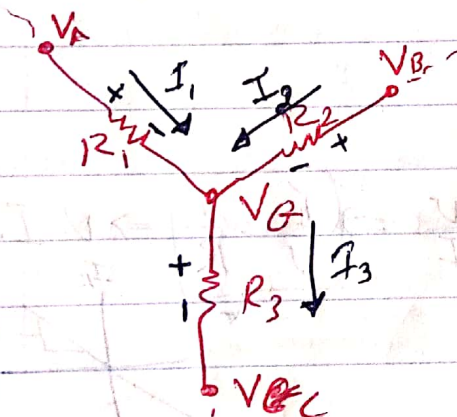


KCL @ VG

Using Node Voltage
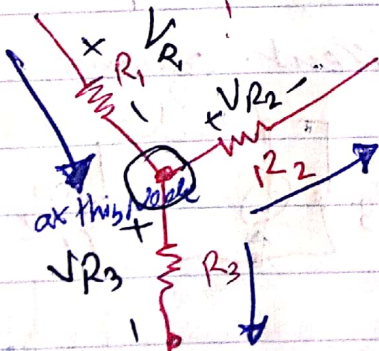
$$+ (I_1 = \frac{V_A - V_G}{R_1}) - (I_2 = \frac{V_B - V_G}{R_2}) - (I_3 = \frac{V_G - V_E}{R_3}) = 0$$



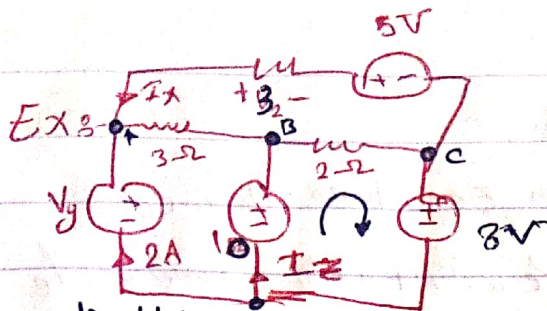
$$\frac{V_{R1}}{R_1} - \frac{V_{R2}}{R_2} - \frac{V_{R3}}{R_3} = 0$$



Find V_x, V_y, I_x, I_z
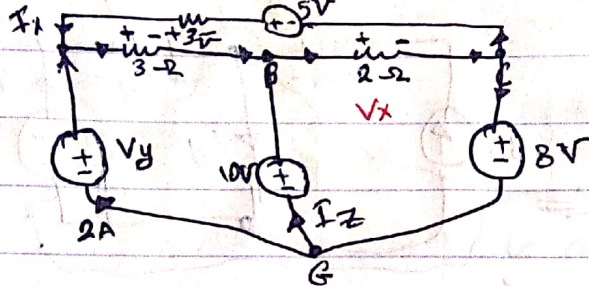
$$\text{KVL } 18 \quad -10 + V_x + 8 = 0 \Rightarrow V_x = +2 \Rightarrow I_z = 1 \text{ A}$$



$$+I_x + 2A -$$

$$\text{KVL } 3- \quad -10 + V_x + 8 = 0 \Rightarrow V_x = +2$$


$$\text{Outer loop } 8- \quad -V_y - 3 + 5 + 8 = 0 \quad V_y = 10 \text{ Volt}$$

$$\text{KVL } 2 \quad -V_y + V_{3\Omega} + V_x + 8 = 0$$


$$-10 + V_{3\Omega} + 2 + 8 = 0$$

$$V_{3\Omega} = 0$$

Final V_x
KVL
KCL
Ω law

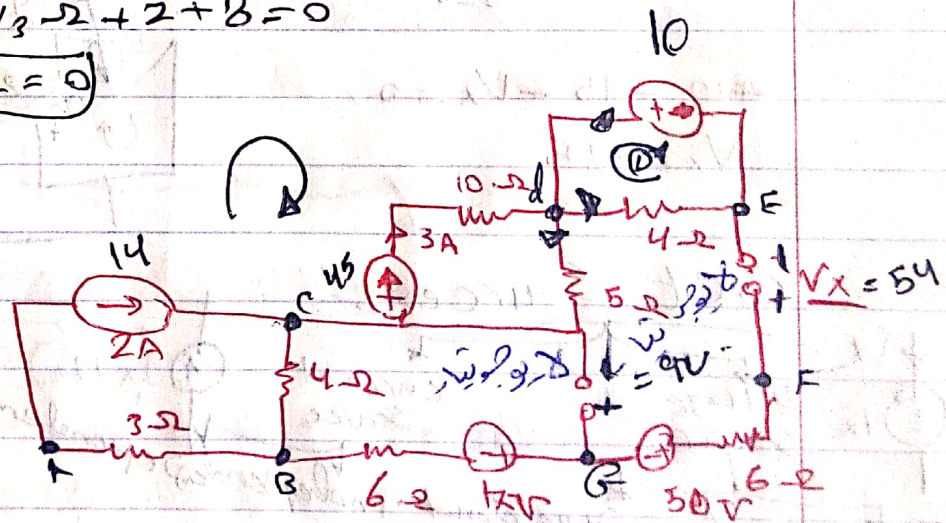


Final V_x

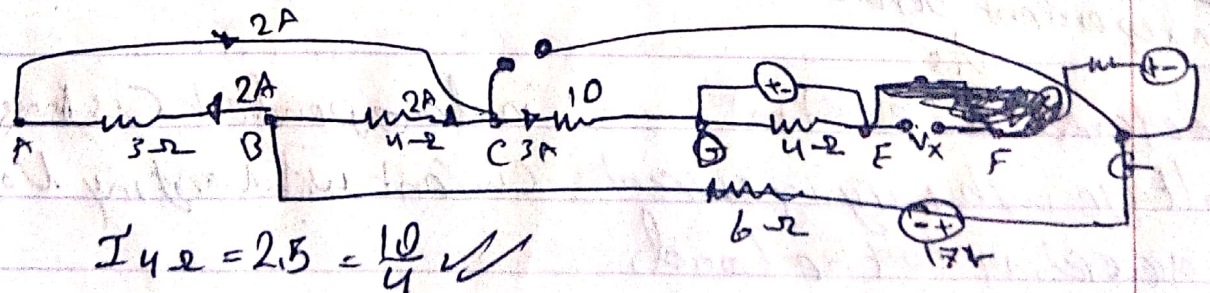



$$I_{4\Omega} = 2.5 = \frac{10}{4} \checkmark$$

Short ckt and open ckt:

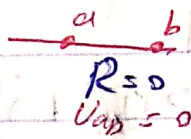Short ckt (S.C) is ckt element with zero Resistance




a and b are within the same node

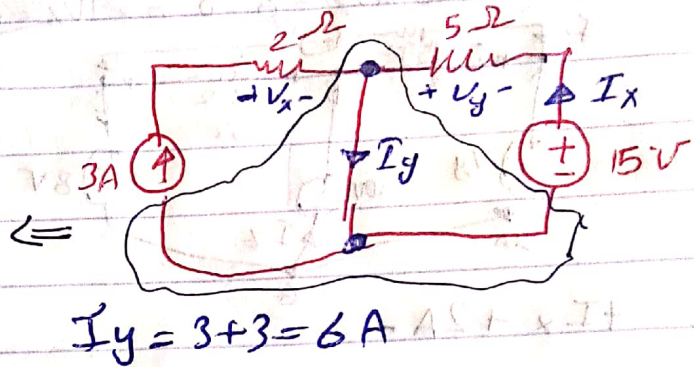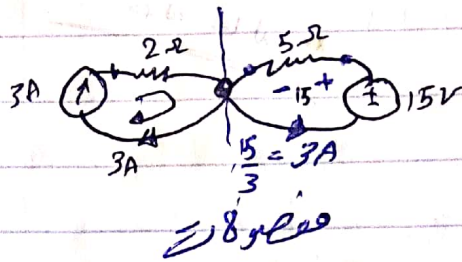


open ckt? (O.C) 2

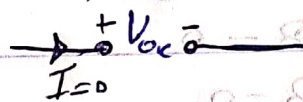ckt element with infinite Resistance $R=\infty$




$$10 - 15 = V_x = 0$$

$$V_x = -25$$

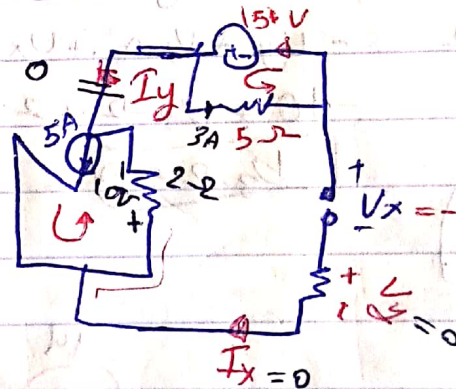


Ckt Sources:

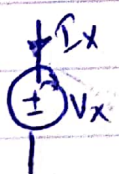

Voltage source

current source

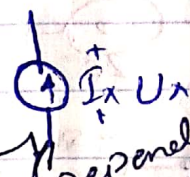


independent

V_s

independent has constant Voltage with varying current according to the load.

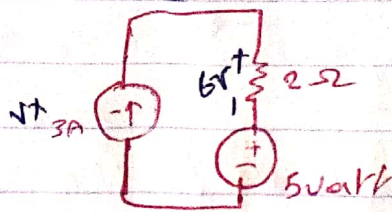independent C.S has constant current with varying Voltage



single loop ckt


$$V_x + 6 + 5 = 0$$

$$V_x = -11V$$

if $2\Omega \rightarrow 3\Omega$

the voltage will change

single node plan

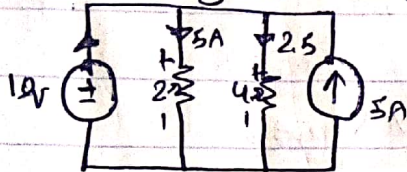


$$I_{10} - 5A + 2.5A + 5A = 0$$

$$I_{10} = 2.5A$$


if $2\Omega \rightarrow 4\Omega$ the voltage will change

voltage source

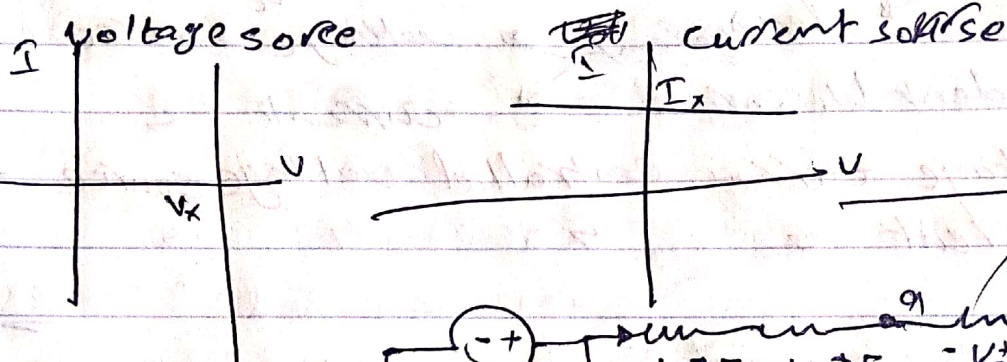

Ex 8

Final V_{R_2}
 V_{ab}

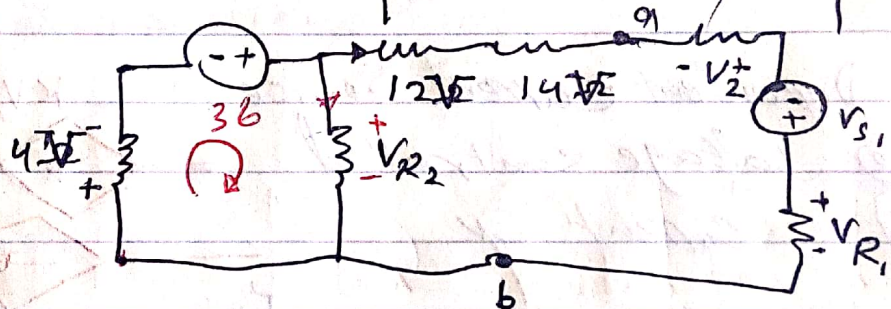



$$V = -4 + 36 - V_{R_2} + V$$

$$V_{R_2} = 32V$$

$$V_{ab} = -4 + 36 - 12 - 14 + V_{ab}$$

$$V_{ab} = +6 \text{ Volt}$$

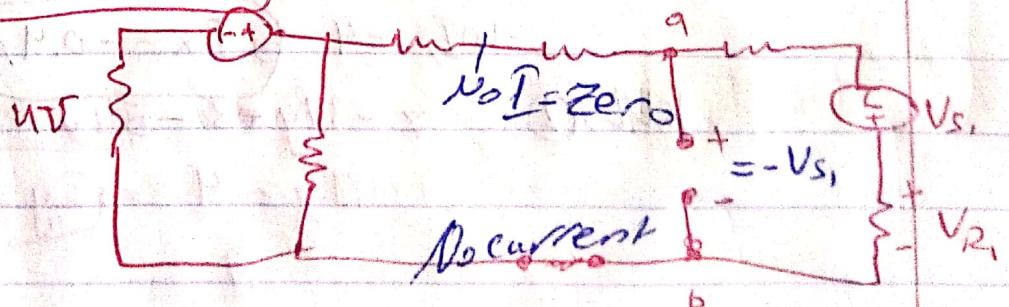

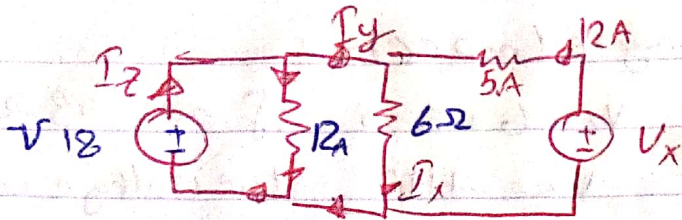

$$I_x = \frac{12}{6} = 2A$$

$$12 - I_y - 3 = 0$$

$$I_y = 9A$$



Sources

- Independent
 - V. Source
 - Current Source
- Dependent
 - Voltage source
 - current

① Dependent V. sources

ⓐ Voltage ~~current~~ controlled voltage source


ⓑ current

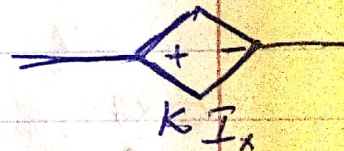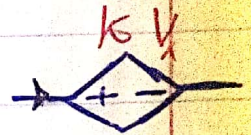


② Dependent current source

ⓐ voltage controlled

ⓑ current

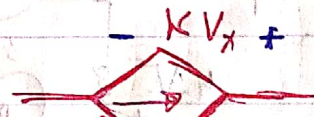

Single loop Ckt.

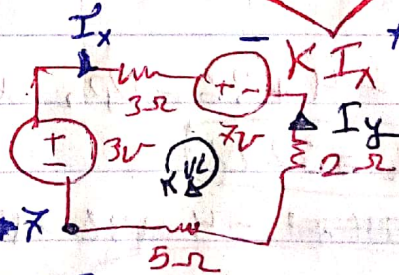


$$KVL: +3 - 3I_x - 7 - 2I_y - 5I_x = 0$$

$$-2I_x - 5I_y = 4$$

$$-10I_x = 4 \Rightarrow I_x = -0.4A$$

$$KVL: 7 - 3I_y - 3 - 5I_y - 2I_y = 0$$

$$10I_y = 4 \Rightarrow I_y = 0.4A$$

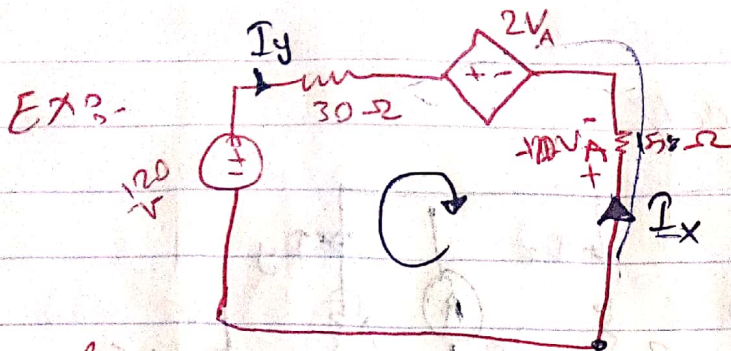

$$I_x = \frac{V_A}{15}$$

$$I_y = 8A$$

Find V_A

$$+V_A - 2V_A + 30 \frac{I_y}{15} + 120 = 0$$

$$V_A = 120V$$


$$I = \frac{-120}{15} = -8A$$

For I_y

$$-120 + 30 I_y + 2V_A + 15 I_y = 0$$


$$I_y = 8A$$

$$V_A = -120V$$

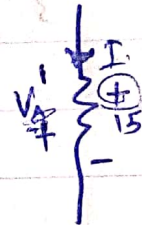


$$15I = -V_A$$

EX 2

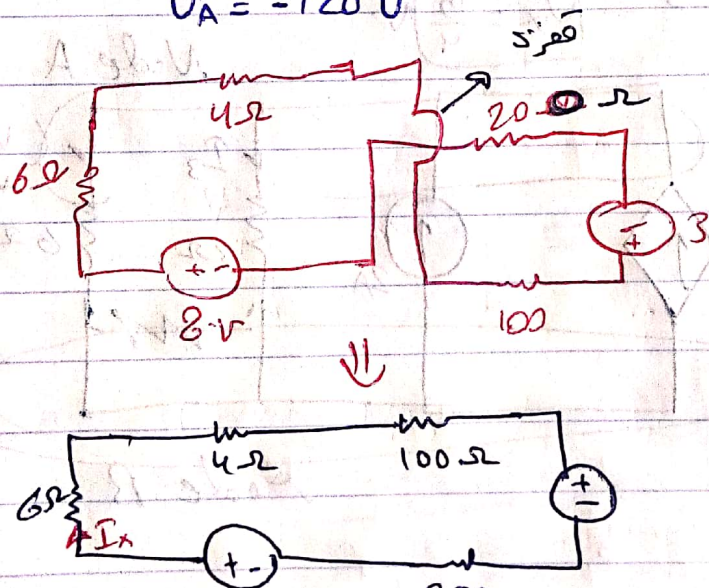

$$60 I_x + 40 I_x + 100 I_x + 200 I_x + 3 + 200 I_x - 8 = 0 \quad \text{--- (1)}$$

Single Node pair ckt

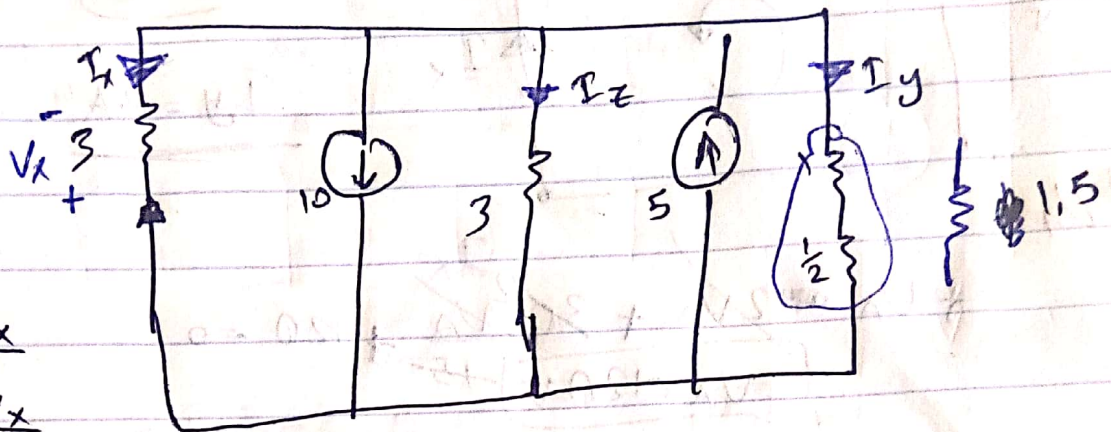

$$I_x = -\frac{V_x}{3}$$

$$I_z = -\frac{V_x}{3}$$

$$I_y = -\frac{2V_x}{3} \text{ kcl}$$


$$-I_x - 10 - I_z - I_y + 5 = 0$$

$$+\frac{V_x}{3} - 10 + \frac{V_x}{3} + \frac{2V_x}{3} + 5 = 0$$

$$\frac{4}{3} V_x = 5$$

$$V_x = \frac{15}{4} \text{ V}$$

Exo-

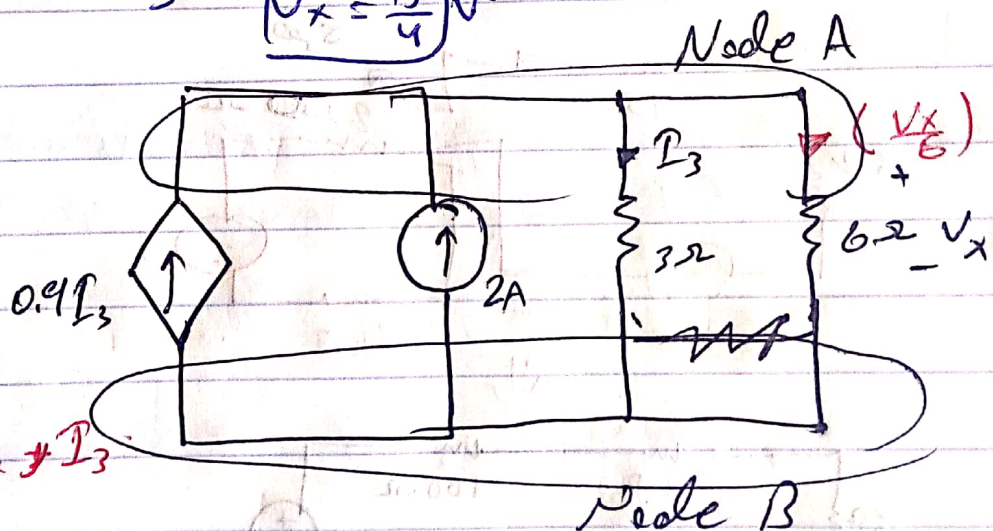

Find V_x & I_3

KCL A-

$$0.9I_3 + 2 - I_3 - \frac{V_x}{6} = 0$$

المسألة

KCL B:-

$$-0.9I_3 - 2 + I_3 + \frac{V_x}{6} = 0$$

$$-0.9 \frac{V_x}{3} - 2 + \frac{V_x}{3} + \frac{V_x}{6} = 0$$

$$I_3 = \frac{V_x}{3}$$


$$\frac{1.2V_x}{6} = 2$$

$$V_x = 10 \text{ V}$$

30/6

9:00 Am

Ex

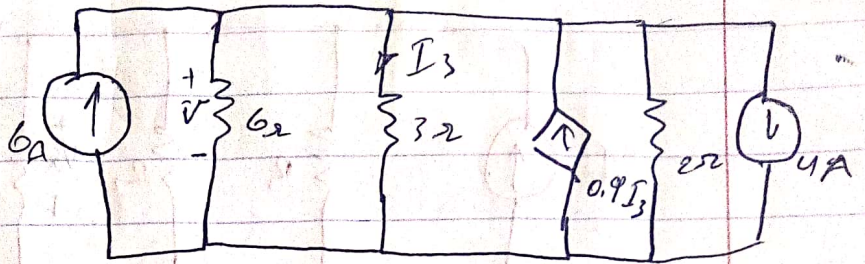Find V, I_3 

$$\text{KCL 2} \rightarrow +6 - \frac{V}{6} - I_3 + 0.9I_3 - \frac{V}{2} - 4 = 0$$

$$6 - \frac{V}{6} - \frac{2V}{6} + 0.3\frac{V}{6} - \frac{V}{2} - 4 = 0$$

$$\boxed{I_3 = \frac{V}{3}}$$


$$-V + 0.3V = -2$$

$$+0.7V = +2$$

$$\boxed{V = \frac{20}{7} \text{ V}}$$

$$\boxed{I_3 = \frac{20}{21} \text{ A}}$$

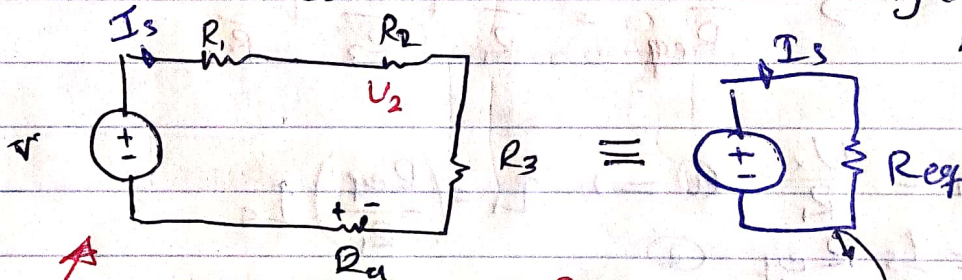Parallel and series Resistances and Voltage/Current Divider Rule.



$$-V_s + I_s R_1 + I_s R_2 + I_s R_3 + I_s R_4 = 0$$

$$-V_s + I_s (R_1 + R_2 + R_3 + R_4) = 0 \quad \text{--- (1)}$$

$$-V_s + I_s (R_{eq}) = 0 \rightarrow$$

$$V_2 = I_s \cdot R_2 \quad \text{--- (2)}$$


$$I_s = \frac{V_s}{R_{eq}}$$

$$\Rightarrow V_2 = \left(\frac{R_2}{R_{eq}} \right) \cdot V_s$$

Voltage Divider Rule

$R_4 \rightarrow$ من السلسلة
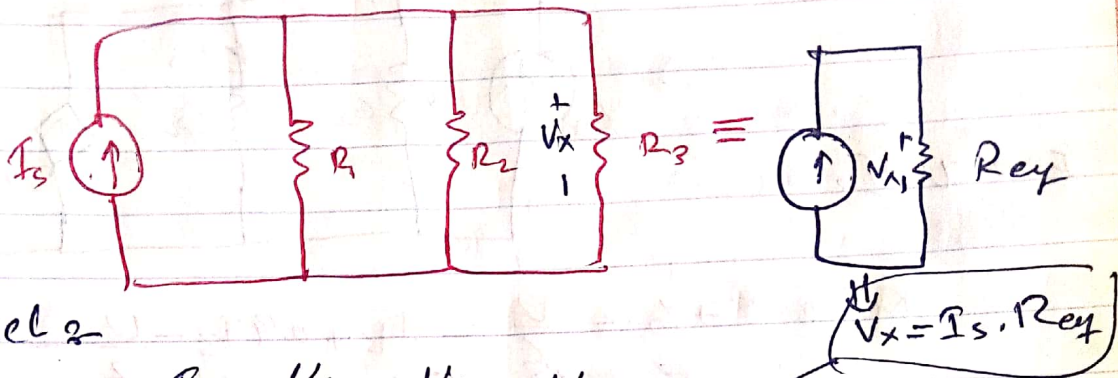
$$V_4 = - \left(\frac{R_4}{R_{eq}} \right) \cdot V_s$$



$$I_s - \frac{V_x}{R_1} - \frac{V_x}{R_2} - \frac{V_x}{R_3} = 0$$

$$I_s = V_x \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$



$$V_x = \frac{I_s}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} \Rightarrow R_{eq} I_s = \frac{I_s}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_1 = \frac{V_x}{R_1} \Rightarrow I_1 = \left(\frac{R_{eq}}{R_1} \right) I_s$$

$$V_x = I_s R_{eq} \quad \text{--- 2}$$

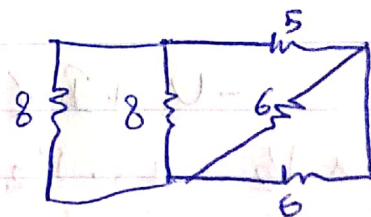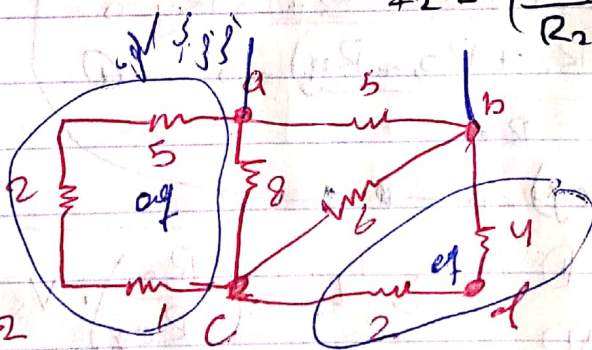
$$I_2 = \left(\frac{R_{eq}}{R_2} \right) I_s$$



R_{ab}

$$R_{ac} = 204 \rightarrow$$

$$R_{bc} = \frac{9}{4} \rightarrow$$

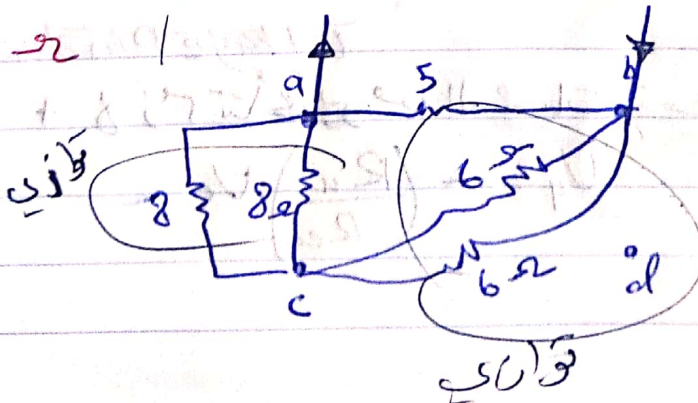


$$R_{ab} = \left[(8 // 8) + (6 // 6) \right] // 3$$

$$= \frac{35}{12} \rightarrow$$


$$R_{AC} = \left[((4+2) \parallel 6) + 3 \right] \parallel 8 \parallel (5+2+1)$$

$$R_{BC} = \left[((5+2+1) \parallel 8) + 3 \right] \parallel (6) \parallel (4+2)$$

Ex

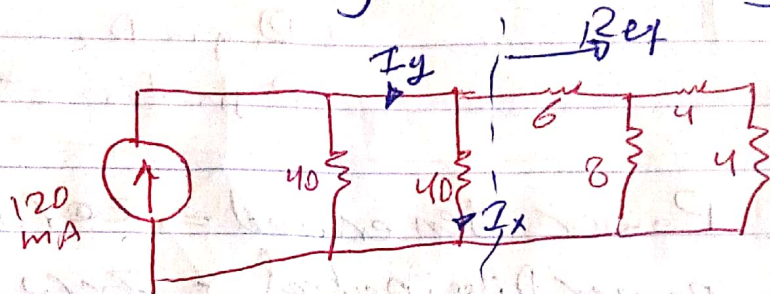
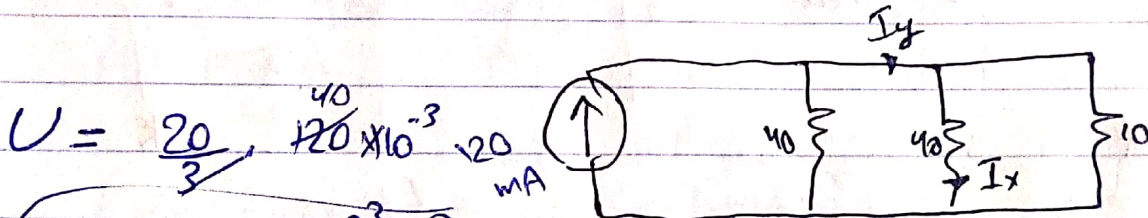
$$R_{eq} = [(4+4) \parallel 8] + 6 = 10 \Omega$$



$$V = \frac{20}{3} \times 120 \times 10^{-3} = 80 \times 10^{-3} V$$


$$R_{eq2} = [10 \parallel 40 \parallel 40] = \frac{20}{3}$$

$$I_x = 80 \times 10^{-3} \left(\frac{20/3}{40} \right)$$

$$I_y = \frac{20/3}{40} \times 80 \times 10^{-3} + \frac{20/3}{10} \times 80 \times 10^{-3} \text{ A}$$

Power Dissipated and Generated

I_s and V_R

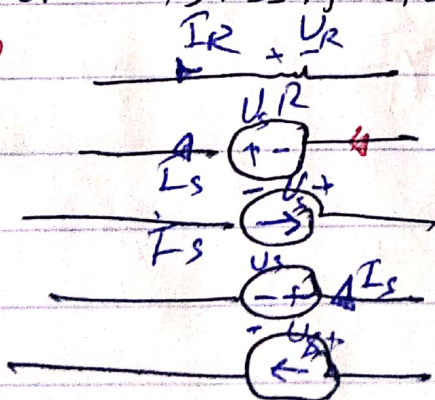


$$\text{power Dissipated} = I_R \cdot V_R (+ve)$$

$$\text{Power} = I_s \cdot (-V_s) (-ve)$$

$$= I_s \cdot (-V_s) (-ve)$$

$$= I_s \cdot (+V_s) (+ve)$$

$$I_s \cdot (+V_s) = +ve$$

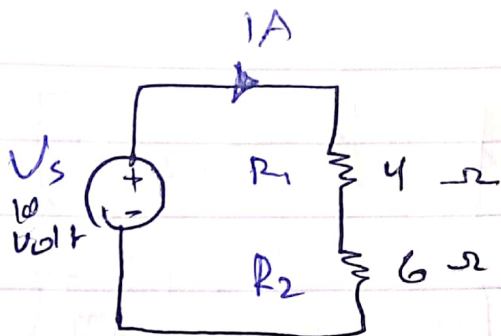

$$P_{\text{diss } R_1} = +4 \text{ W}$$

$$P_{\text{diss } R_2} = +6 \text{ W}$$

$$P_{\text{diss } V_s} = -10 \text{ W}$$

مستهلك

$$P_{\text{gin } R_1} = -4 \text{ W}$$

$$P_{\text{gin } R_2} = -6 \text{ W}$$

$$P_{\text{gin } V_s} = +10 \text{ W}$$

مصدر

$$\infty \quad \sum \text{Power generated} = \text{Zero}$$


$$\sum \text{Power Dissipated} = \text{Zero}$$

$$\sum \text{Power generated} = \sum \text{Power diss} = \text{Zero}$$

~~Handwritten scribbles~~

يوم الثلاثاء (اليوم الخامس) للحاضرة طاعة (25/6)

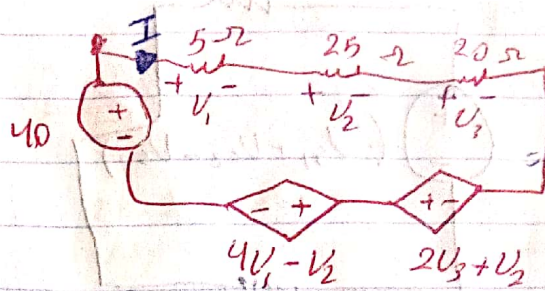Ex:- Find power absorbed (consumed, dissipated) at each element
KVL:-



بقدر نزل
عنه لا
بس 8
نحوه

$$-40 + (2V_3 + V_2) + 4V_1 - V_2 = 0 \Rightarrow -40 - V_3 - V_2 + 5V_1 = 0$$

But $V_1 = 5I$, $V_2 = 25I$, $V_3 = 20I$

then $40 = -20I \Rightarrow I = -2A$

Power diss for (40V) = $(+2)(+40) = +80W$

Power generated (40V) = $-80W$



$P_{diss} = I^2 \cdot R = 25W$ (for 5Ω)

$(40 + (2V_3 + V_2) - (4V_1 - V_2))$



$P_{diss} (2V_3 + V_2) = (+2)(2V_3 + V_2) = 2(2(-20) + (-25)) = -80W$

$P_{diss} (2V_3 + V_2) = -260W$ (هذا هو الجواب generated)

Ex:-

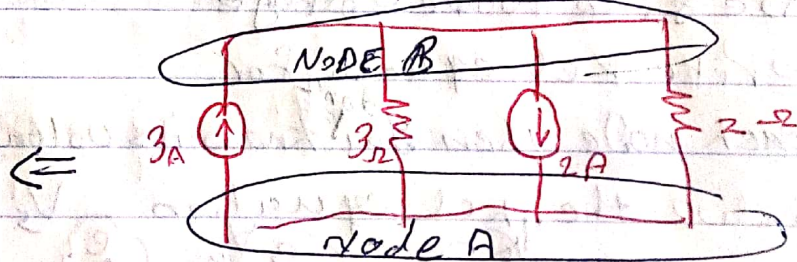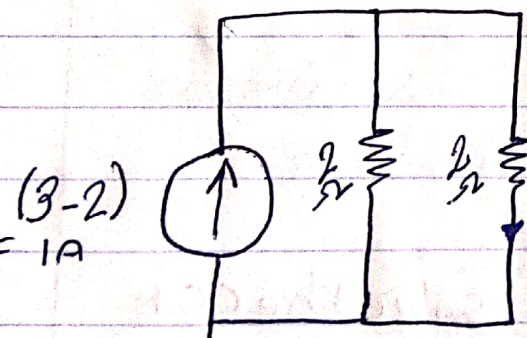

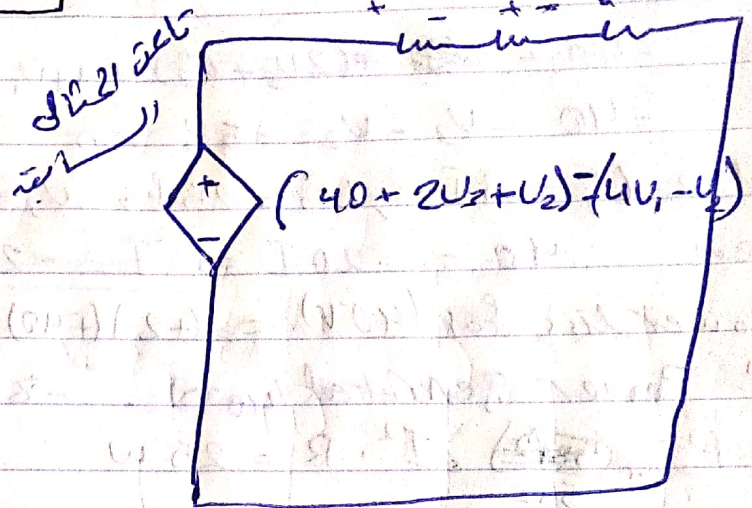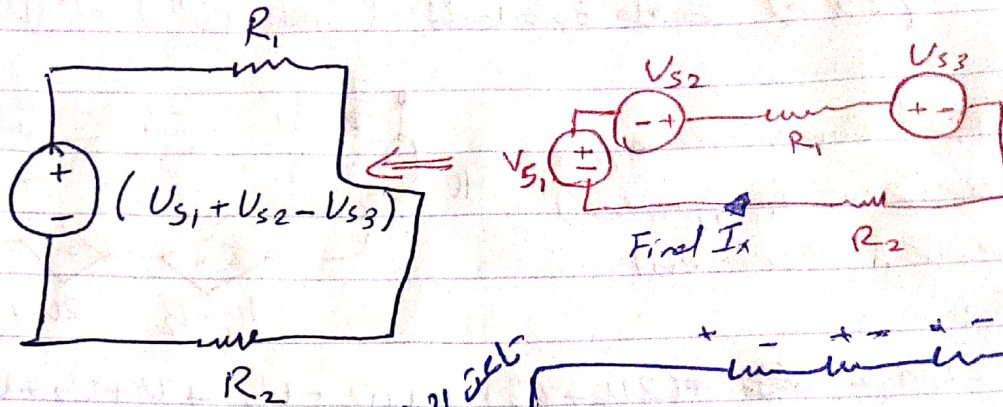
$I = \left(\frac{R_{eq}}{2}\right) \cdot 1 = 0.5A$




No load Analysis

- ① Define the Nodes and the Ground Node
- ② Define Node Voltage
- ③ write KCL equation for each node then you ^{don't} know its voltage
- ④ solve the KCL equation

Ex

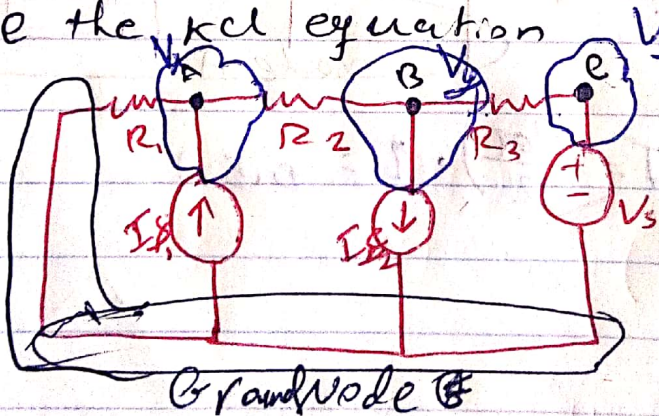

solve the CCT to find All current &.

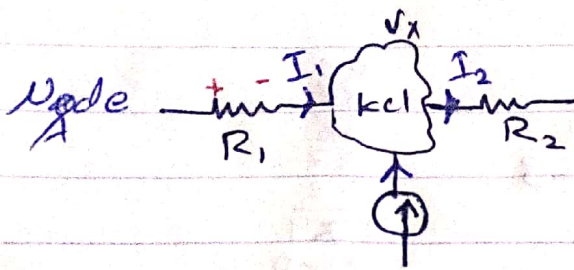

$$KCL @ V_x: +I_1 + I_2 - I_3 = 0$$

$$\textcircled{1} \quad +\left(\frac{0 - V_x}{R_1}\right) + I_{s1} - \left(\frac{V_x - V_y}{R_2}\right) = 0$$

Should be written using node variable

$$\textcircled{1} \Rightarrow \left(-\frac{1}{R_1} - \frac{1}{R_2}\right) V_x + \left(\frac{1}{R_2}\right) V_y = -I_{s1}$$

Node B

بقدر تفرضا اياه البتة، وبين ما بدلك على كمل


$$-I_2 - I_{s2} + I_3 = 0$$

$$\left(\frac{V_y - V_x}{R_2}\right) - I_{s2} + \left(\frac{V_s - V_y}{R_3}\right) = 0$$

$$\left(-\frac{1}{R_2} - \frac{1}{R_3}\right) V_y + \frac{1}{R_2} V_x + \frac{V_s}{R_3} = I_{s2} \quad \textcircled{2}$$

Ex:-

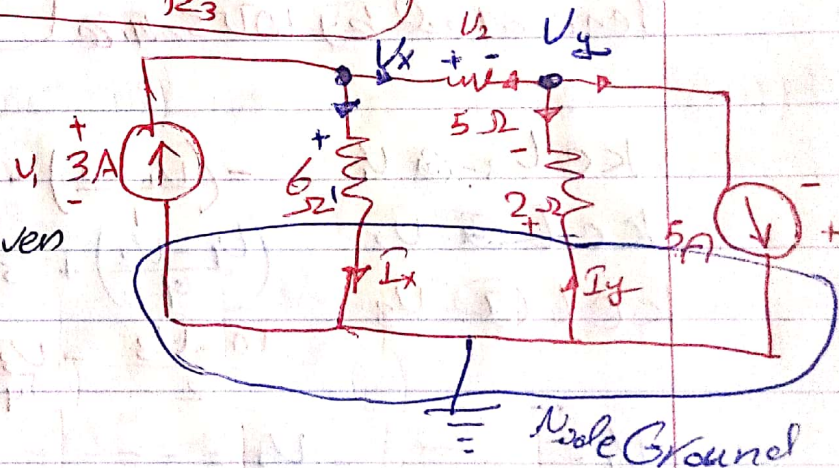the Ground should be given or identified.



KCL @ (a) V_x

$$+3 - \left(\frac{V_x - 0}{6}\right) - \left(\frac{V_x - V_y}{5}\right) = 0$$

$$\left[+3 - \frac{11}{30} V_x + \frac{V_y}{5} = 0 \right] \quad \textcircled{1}$$

KCL @ (a) V_x

$$- \left(\frac{V_y - V_x}{10}\right) - 5 - \left(\frac{V_y - 0}{2}\right) = 0$$

$$\frac{11}{6} * \left[-\frac{7}{10} V_y + \frac{V_x}{5} = 5 \right] \quad \textcircled{2}$$

$$-\frac{77}{60} V_y + \frac{11}{30} V_x = \frac{55}{6}$$

① + ②

$$-\frac{77}{60} U_y + \frac{U_y}{5} = \frac{55}{6} - 3$$

$$-\frac{65}{60} U_y = 37$$

$$U_y = \frac{12}{13} - \frac{444}{13} V$$

$$\begin{array}{r} 12 \\ 13 \\ \hline 37 \\ 12 \\ \hline 124 \\ 370 \\ \hline 444 \end{array}$$

~~the~~


$$U_1 = U_x - 0, I_x = \frac{U_x - 0}{7}$$

$$I_y = \frac{U_y - 0}{2}, U_2 = 0 - \frac{6}{U_y}$$

Ex 2:-

المحل الثاني

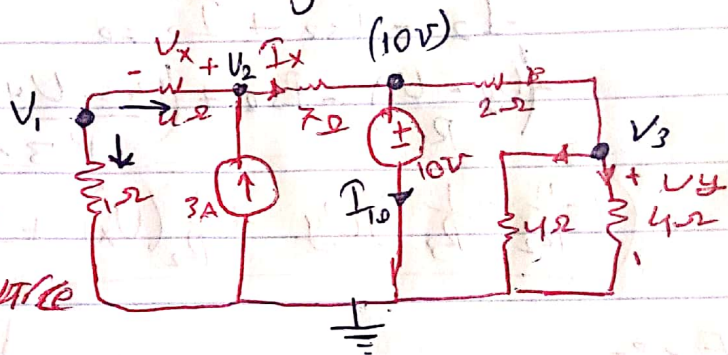Find U_x, U_y, I_x , Power generated by 10V source



KCL @ U_1

KCL @ U_2

KCL @ U_3

$$-(U_1 - 0) - (U_1 - U_2) = 0 \Rightarrow \frac{5U_1}{4} = U_2 \quad \text{①}$$

$$\left(\frac{U_1 - U_2}{4}\right) + 3 - \left(\frac{U_2 - 10}{7}\right) = 0 \Rightarrow \frac{-13}{28} U_2 + \frac{U_1}{4} = -\frac{31}{7}$$

$$\frac{10 - U_3}{2} - \frac{U_3}{4} - \frac{U_3}{4} = 0 \Rightarrow U_3 = 5V$$

$$U_1 = \dots \quad U_2 = \dots \quad U_3 = \dots$$

$$U_x = U_2 - U_1, I_x = \frac{U_2 - 10}{7}, U_y = U_3 - 0$$

Apply KCL @ (10 volts) \neq

$$\left(\frac{U_2 - 10}{7}\right) - I_{10} - \left(\frac{10 - U_3}{2}\right) = 0$$


$$\Rightarrow I_{10} = \frac{U_2}{7} + \frac{U_3}{2} - \frac{45}{7}$$

$$P_{\text{diss}} = I_{10} (+10)$$

$$P_{\text{gen}} = -I_{10} (+10)$$

$$U_1 = \left(\frac{1}{1+4}\right) U_2$$


المسألة

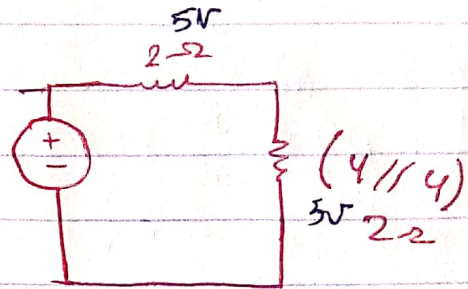

$$V_{2-2} = \frac{2}{4} (10) = 5V$$

Ex 2-

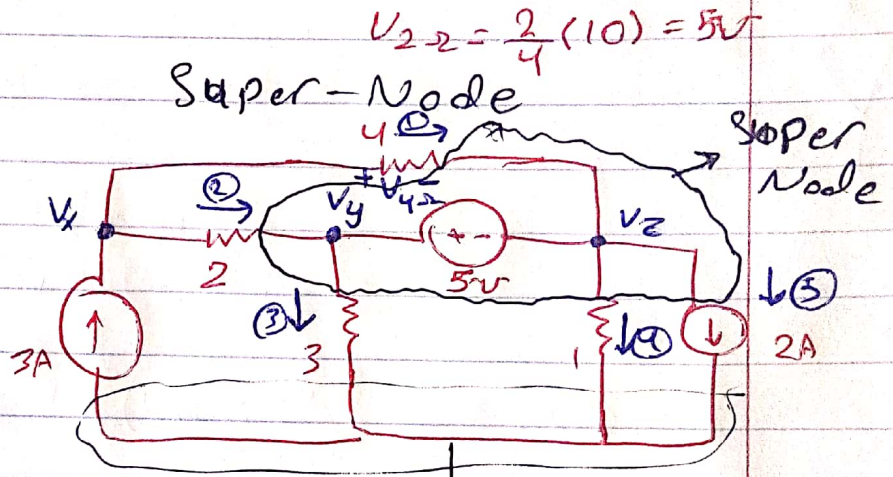* بتقدير خط Ground
 ولقد ما بدت بس
 حاول قطة على يكون فيه
 أقل عدد اطباء هيل



KCL @ V_{x3}

$$3 - \left(\frac{V_x - V_y}{2} \right) - \left(\frac{V_x - V_z}{4} \right) = 0$$

السوبر نود هيل جمع
 ان ثبيت فيه هيل لا نستطيع معرفة التيار
 بينهم (بدالة الجهود)

KCL @ Super Node R


$$\left(\frac{V_x - V_z}{4} \right) + \left(\frac{V_x - V_y}{2} \right) - \frac{V_y}{3} - \frac{V_z}{1} - 2 = 0 \quad (2)$$

Voltage But
source of

$$V_y - V_z = 5V \quad (3)$$




$$\begin{aligned}
 \Rightarrow V_x &= \\
 V_y &= \\
 V_z &= \\
 V_{4-2} &=
 \end{aligned}$$

استخرجان التيارات

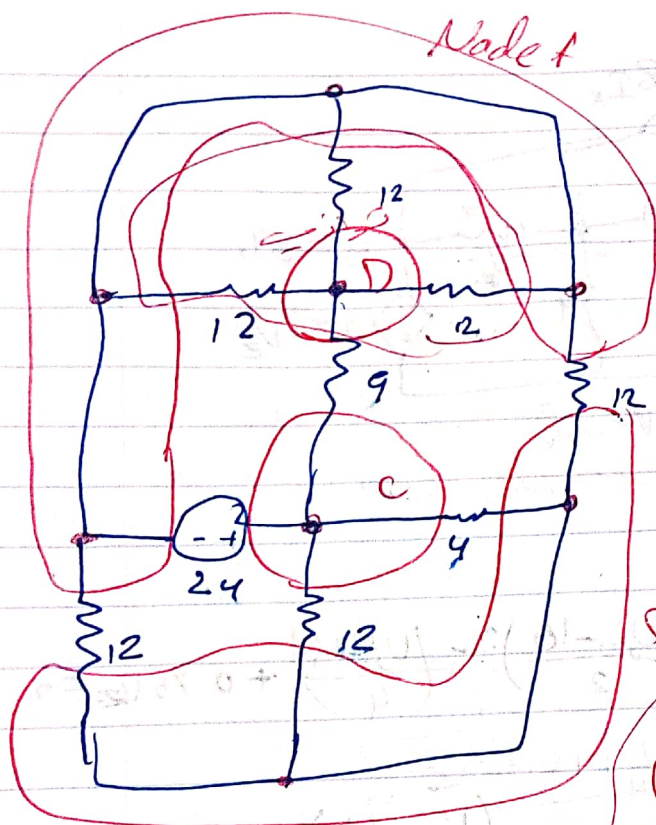

Find R_{eq}

Find the $P_{generator}$ by 24V source

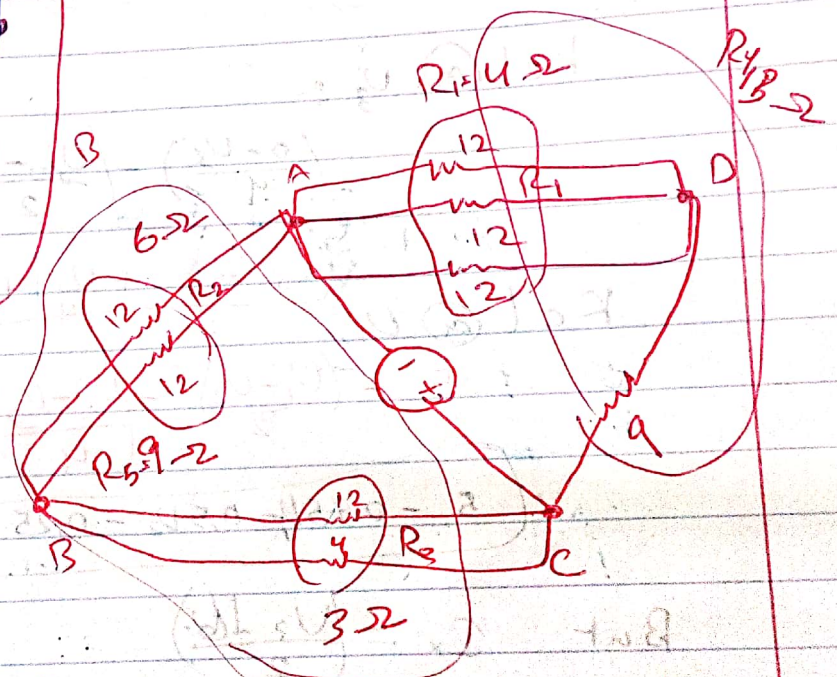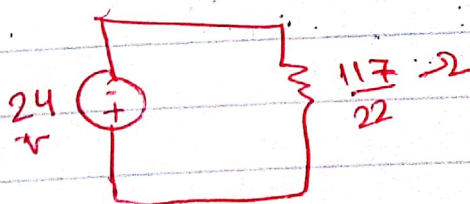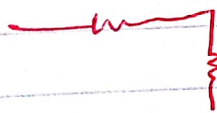

$$R_1 = 12 // 12 // 12 = 4 \Omega$$


$$R_2 = 12 // 12 = 6 \Omega$$

$$R_3 = 12 // 4 = 3 \Omega$$


$$R_4 = 4 + 9 = 13 \Omega$$

$$R_5 = 6 + 3 = 9 \Omega$$
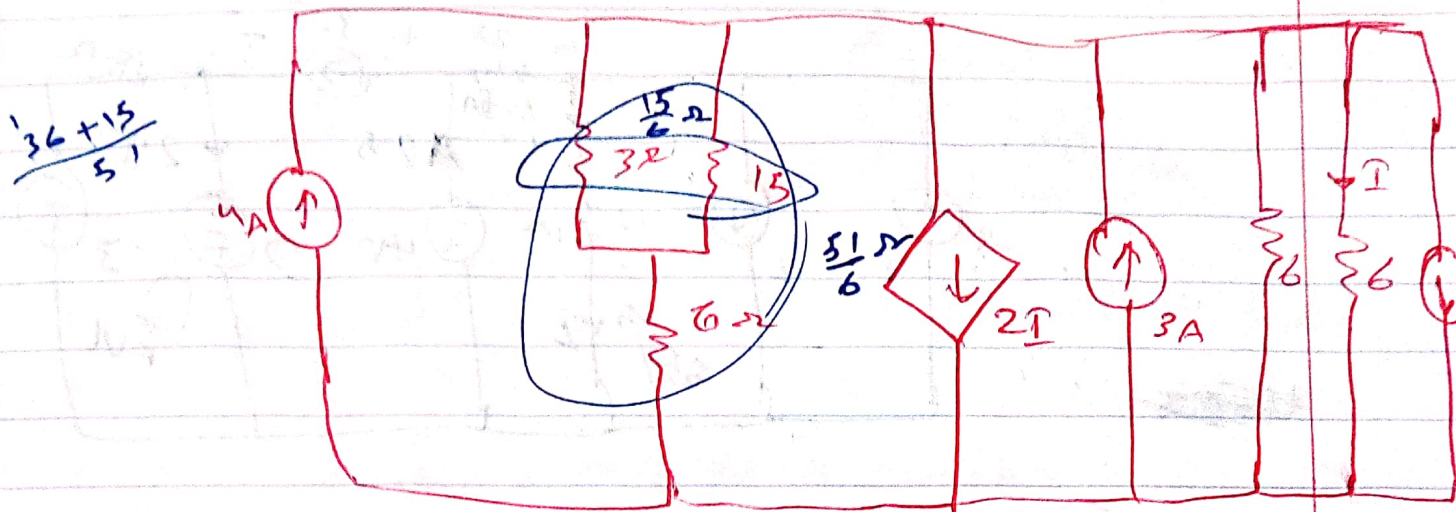
$$R_{eq} = 13 // 9 = \frac{117}{22} \Omega$$



Find I ??

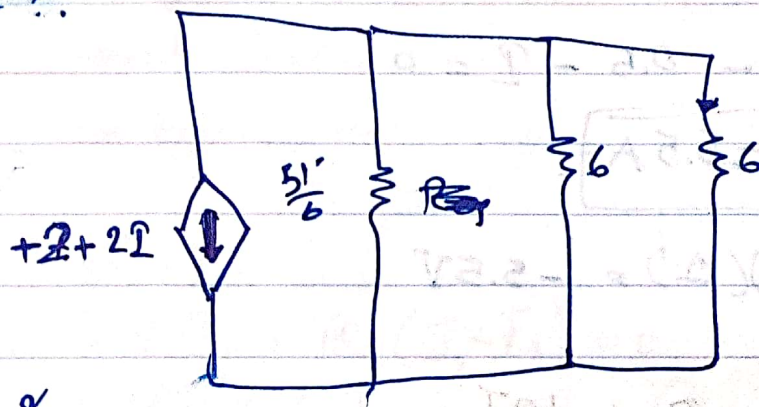


$$\frac{6}{51} + \frac{2}{\cancel{6}}$$

$$\frac{18+51}{153} = \left(\frac{69}{153}\right)$$

$$V = \frac{69}{153} (2+2I)$$
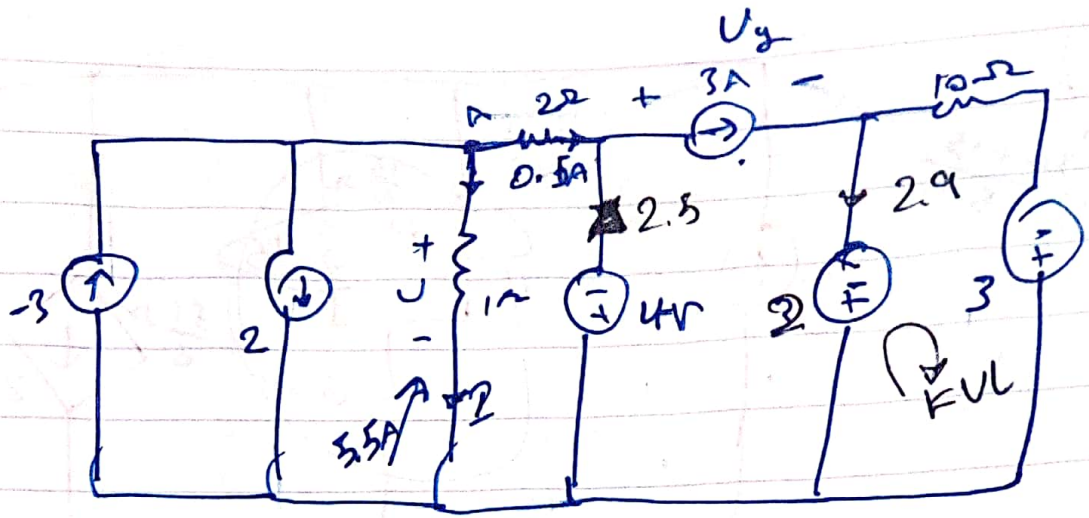
$$\frac{I}{2} = \frac{69}{153} (2+2I) \quad - \quad I = ??$$



KCL @ A

$$-3 + 2 - 0.5 - I = 0$$

$$I = -5.5 \text{ A}$$

$$U = -(5.5)(1) = -5.5 \text{ V}$$



KVL

$$+2 + 3 + 10I = 0$$

$$I = 0.1$$

KCL

$$I_{2V} = +3 - 0.1 = 2.9$$


KVL

$$+U_y + 4 - 2 = 0$$

$$U_y = -2 \text{ V}$$

MECH Analysis

Ex

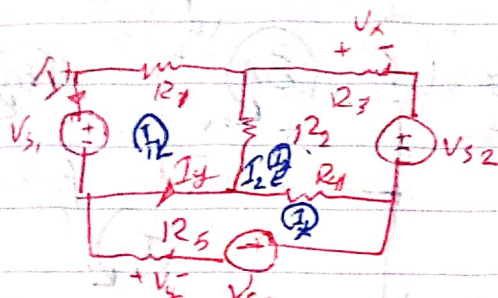

$\left\{ \begin{array}{l} \text{KVL} \\ \text{KCL} \\ \text{current Divider} \\ \text{Voltage Divider} \\ R_{eq} \end{array} \right.$

Systematic Methods to solve ckt

Nodal MECH SUPERPOSITION

جواب المسألة
MECH

- ① Define the Meshes and Mesh currents.
- ② Apply KVL for MESHES that you don't know it's current value.
- ③ Solve the KVL eq.

KVL @ MECH I:

$$-V_{s1} + R_1 I_1 + R_2 (I_1 - I_2) = 0$$

$$(R_1 + R_2) I_1 - R_2 I_2 = V_{s1} \quad \text{--- ①}$$

KVL @ MECH II:

$$R_2 (I_2 - I_1) + R_3 I_2 + V_{s2} + R_4 (I_2 - I_3) = 0$$

$$(R_2 + R_3 + R_4) I_2 - R_2 I_1 - R_4 I_3 = -V_{s2} \quad \text{--- ②}$$

KVL @ MECH III

$$V_{s3} + I_3 R_5 + (I_3 - I_2) R_4 = 0$$

$$(R_5 + R_4) I_3 - I_2 R_4 = -V_{s3} \quad \text{--- ③}$$

$$I_1 = \quad \quad I_2 = \quad \quad I_3 = \quad$$

$$I_x = I_1 \quad I_y = I_3 - I_1$$


$$V_y = -I_3 \cdot R_5$$

$$P_{diss \text{ by } V_{s2}} = I_2 V_{s2}$$

$$P_{gin \text{ by } V_{s3}} = -I_3 \cdot V_{s3}$$

Ex

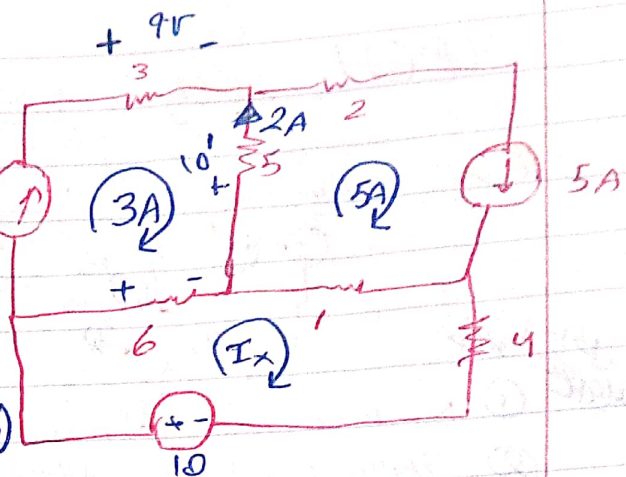Find Power generated by 5A
 $C.S = -(-V_y \cdot 3) V_y 3A$
 Dissipated by 5A
 $=$



KVL @ I_x

$$\begin{aligned} -28 - \frac{5}{33} - 10 + 6(I_x - 3) + 1(I_x - 5) + 4I_x &= 0 \\ 11I_x &= +33 \\ \boxed{I_x = 3A} \end{aligned}$$

KVL.


$$-V_y + 9 - 10 - (I_x - 3) \cdot 6 = 0$$

Ex 8

$$I_1 = -I_x$$

KVL @ M_I

$$\begin{aligned} -6 + 2I_1 + 3(-I_1) + 5I_1 &= 0 \\ 4I_1 &= 6 \\ \boxed{I_1 = 1.5A} \end{aligned}$$

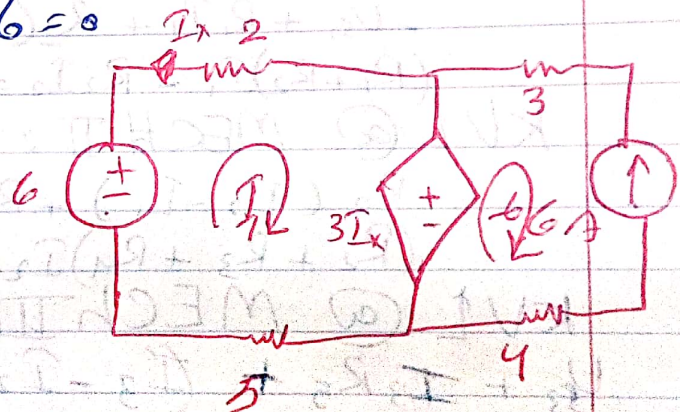

Ex 8-

KVL at M_I


$$V_x = \text{---}$$

$$1(I_1 + 5) \cdot 6 = 3V_x$$

$$\begin{aligned} -3(I_1 + 5) + 2I_1 + (I_1 - I_2) + 10 &= 0 \\ + 6(I_1 + 5) &= 0 \end{aligned} \quad \text{--- (1)}$$

KVL @ M_{II}
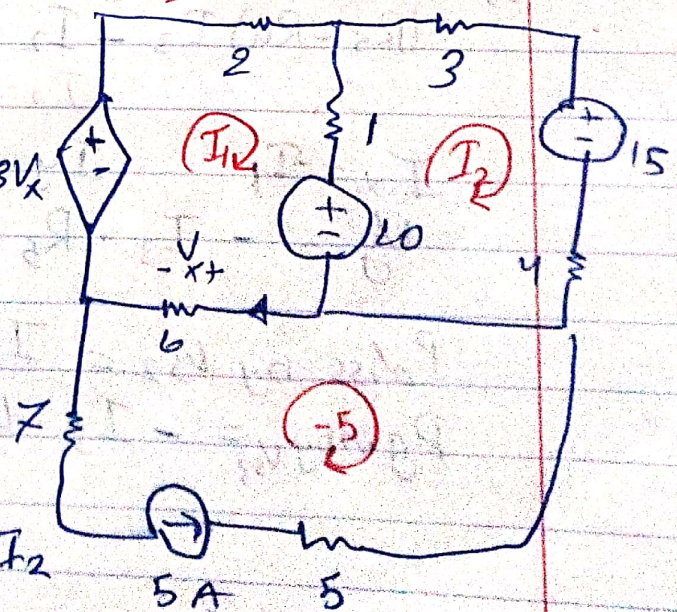
$$\begin{aligned} -10 + (I_2 - I_1) + 3I_2 + 15 + 4I_2 &= 0 \\ &= 0 \end{aligned} \quad \text{--- (2)}$$



* لا يمكن أن يكون الحل الأسهل في بعض الحالات S.m

Ex

KVL @ M1 :- $-10 + I_1 + 2(I_1 - I_2) + V_x + 4(I_1 + 2) = 0$ — (1)

KVL @ M2 :-

$-V_x + 2(I_2 - I_1) + 3I_2 + 5 + 5(I_2 + 2) = 0$ — (2)

Since we have current source between two meshes (I_1, I_2)

$3 = I_2 - I_1$ — (3)

$I_1 = -3 - I_2$
 $V_x = \dots$

we have Super Mesh (if we have a current source between two meshes)

KVL @ S.m

$-10 + I_1 + 3I_2 + 5 + 5(I_2 + 2) + 4(I_1 + 2) = 0$ — (4)

$3 = I_2 - I_1$ — (3)


Ex3-

KVL @ M1 :-

$10(I_1 - 2) + 20(I_1 - 0.2V_x) = 0$ — (1)

But $V_x = 10(2 - I_1)$ — (2)

$I_1 = \dots$ $V_x = \dots$

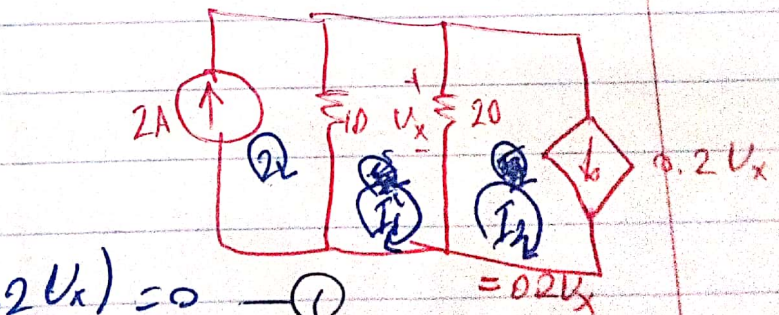


KVL @ M_{12} -

$$2(I_x - 3) + 4I_x + 5 = 0$$

KVL @ M_{23} -

$$-5 + I_y + 3(I_y - 3) = 0$$

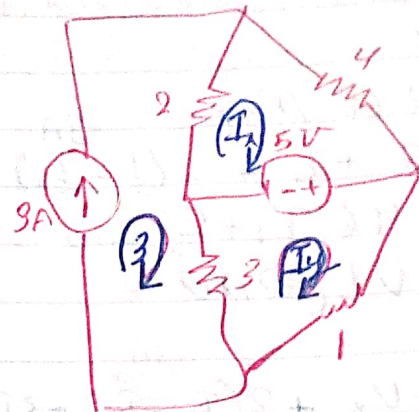

E

KVL @ super super MESH

$$3(I_3 - I_4) + 12 +$$

$$I_1(1) + 4I_2 + 0.2U_x = 0 \quad \text{--- (1)}$$


$$I_2 - I_1 = 14 \quad \text{--- (2)}$$

$$I_3 - I_2 = 0.5U_x \quad \text{--- (3)}$$

But $U_x = -I_1(1)$

KVL @ $-I_4$
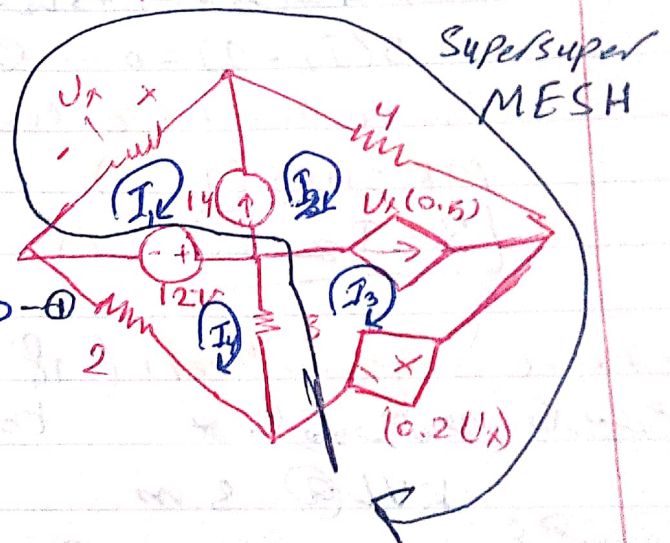
$$2I_4 - 12 + 3(I_4 - I_3) = 0 \quad \text{--- (4)}$$



Super position :-


~~The~~ The value of a response (voltage) or current in a ckt. is a linear sum of Responses (currents, voltages) each one of them is due to our single active source.

لو في source كذا الة في circuit فكل الة في الة




Deal Voltage source




Deal current source

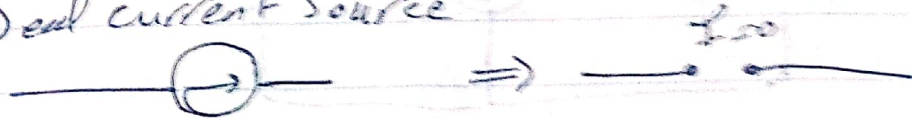

Find V_x using superposition

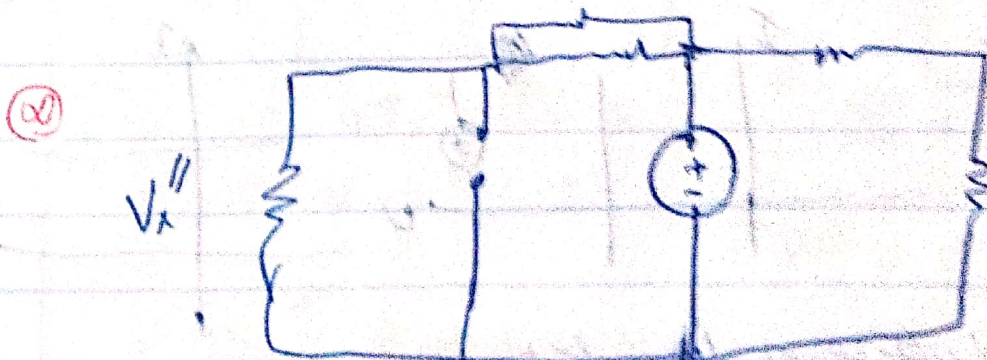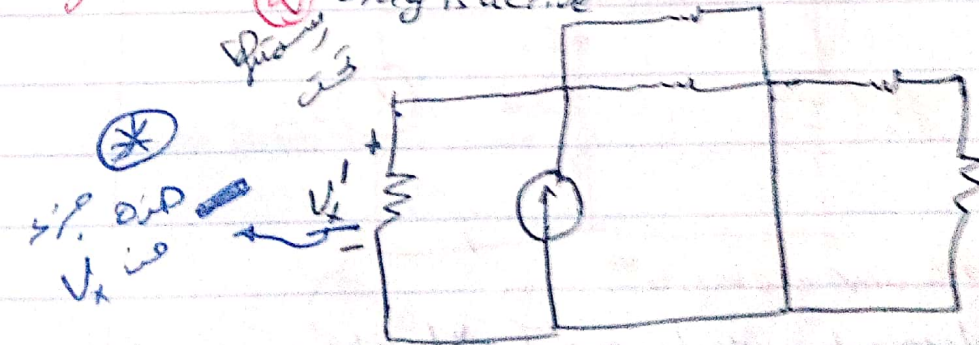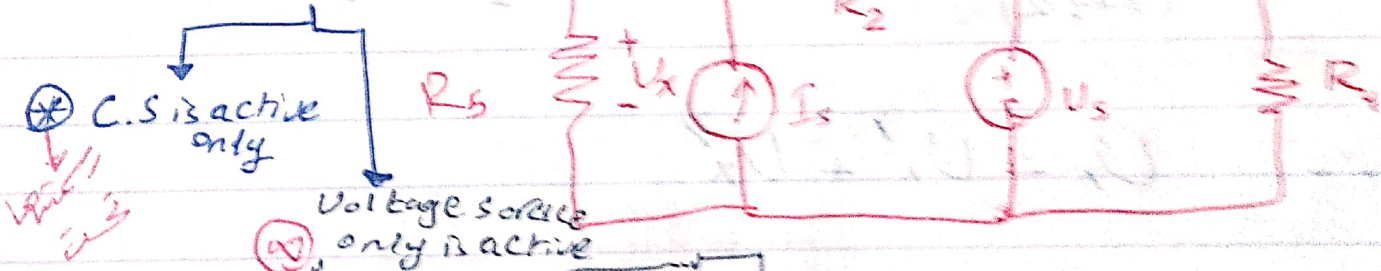

خط *

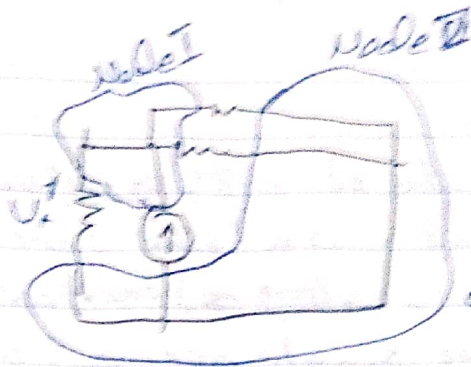


التيار في المقاومة
على التوازي
current distribution
 $R_{eq} = R_1 \parallel R_2 \parallel R_3$

$$U_x' = I_{R_s} \cdot (R_s) =$$

$$\frac{R_{eq}}{R_s} \cdot I_s \cdot R_s = R_{eq} I_s$$

نفس التيار
على التوازي

(∞)

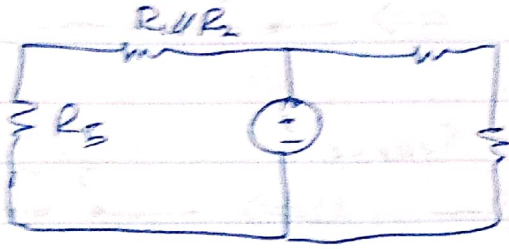


$$U_x'' = \left(\frac{R_2}{R_{eq2}} \right) U_s$$

$$R_{eq2} = R_s \parallel (R_1 \parallel R_2)$$

$$\therefore U_x = U_x' + U_x''$$




Ex:- Find I_x

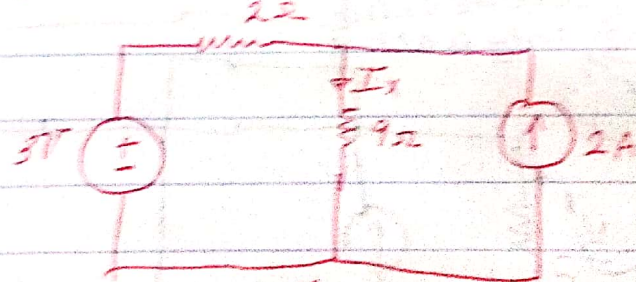we use superposition only
for linear cct.



* linear cct :- is a cct with linear element

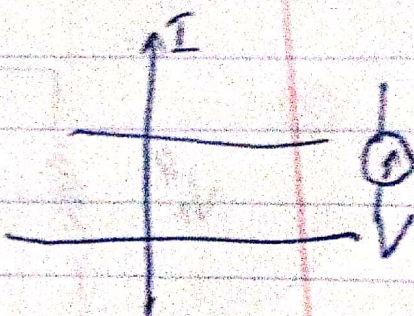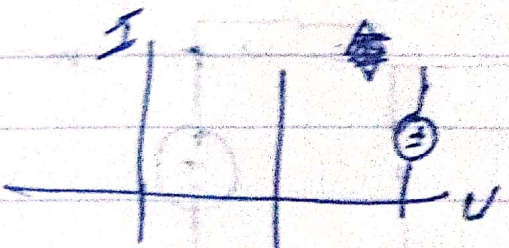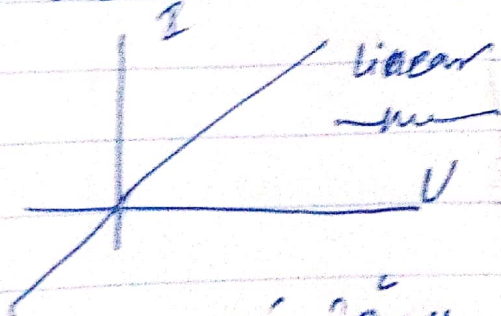as linear element :- is c.c element with linear I-V characteristics



منه
من حاتك يا بدلة اني نبيع

Solve Ex



$$I_x' = \frac{3}{11}$$

$$I_x'' = \left(\frac{2}{11} \cdot 2 \right) = \frac{4}{11}$$

OR $= \left(\frac{R_{eq}}{R_1} \right) \cdot 2$

$$I_x = \frac{7}{11} = \frac{4}{11} + \frac{3}{11}$$


$$R_{eq} = \frac{2(11)}{11}$$

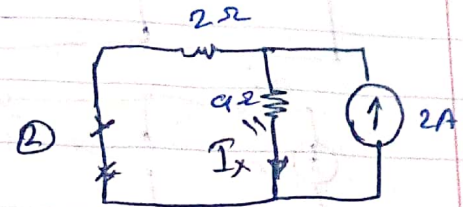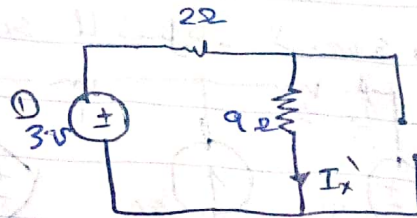


Ex: Find the current in this ckt

this ckt is passive
(Resistive ckt)

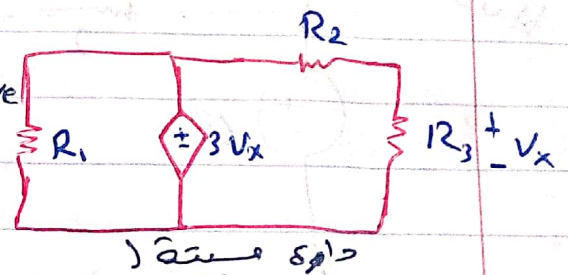
$$V_x = \frac{R_3}{R_2 + R_3} \cdot 3V_x \Rightarrow V_x = 0$$




دائرة سلبية
↓
المكافئ

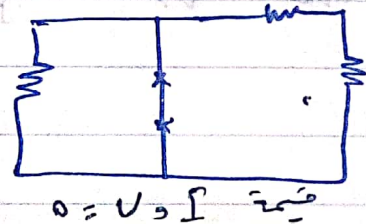

Ex2-

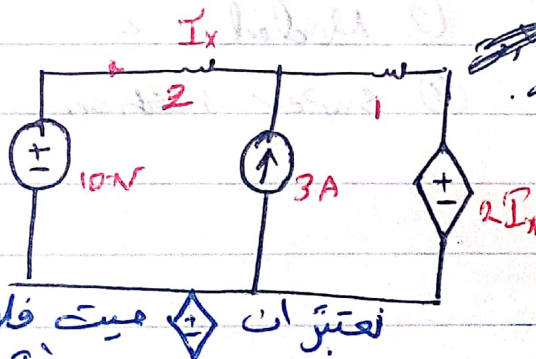

نعتبر ان \diamond ميت فلا \diamond لايه

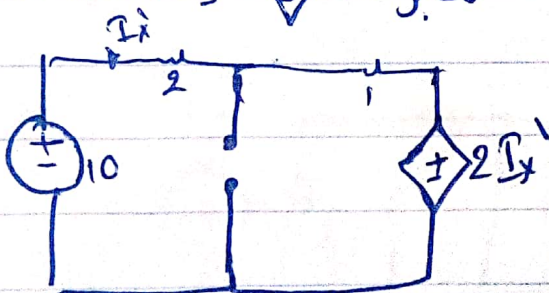


KVL

$$-10 + 2I_x' + I_x' + 2I_x' = 0$$

$$5I_x' = 10 \Rightarrow I_x' = 2A$$

$$\therefore I_x = 2 - 0.6 = 1.4A$$

Find I_x using S.P

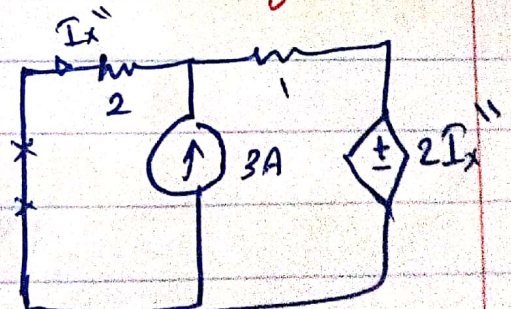

KCL

$$I_x'' + 3 - I_y = 0$$



$$I_y = I_x'' + 3 \quad \text{--- (1)}$$

KVL


$$2I_x'' + I_y + 3 + 2I_x'' = 0$$

$$I_x'' = -0.6A$$

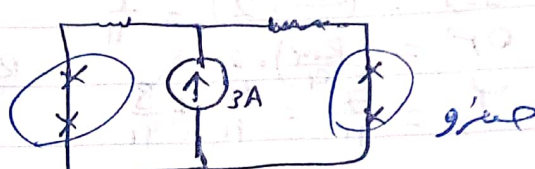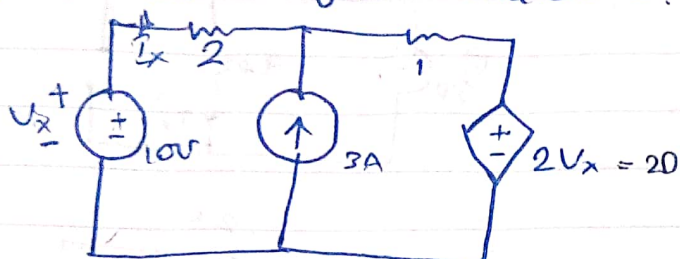اذا خط لا متغير ثابت على source لا نقل هذا ال source ز نقل \pm لا نو
 ز يصر ز




How

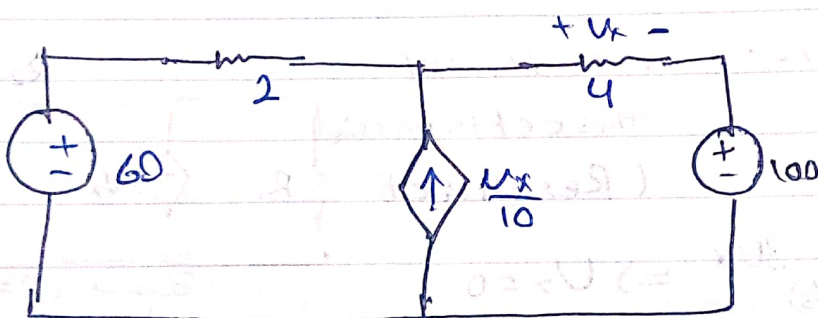

Final V_x using:-


- ① Mesh Analysis
- ② Nodal
- ③ super Position

Source Transformation

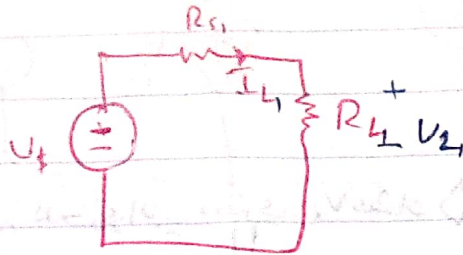

$$I_{L1} = \frac{U_s}{R_{s1} + R_L}$$

$$U_{L1} = I_{L1} \cdot R_L$$

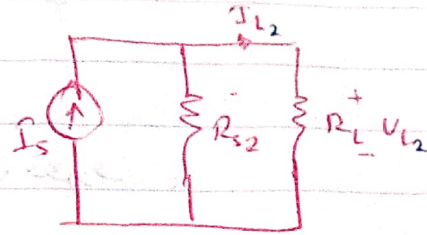

$$I_{L2} = \left[\frac{R_{s2} \cdot R_L}{R_{s2} + R_L} \right] \cdot I_s$$

$$= \left(\frac{R_{s2}}{R_{s2} + R_L} \right) \cdot I_s$$

$$U_{L2} = \left(\frac{R_{s2} \cdot R_L}{R_{s2} + R_L} \right) \cdot I_s$$

when we get $I_{L1} = I_{L2}$?


$$\text{or } U_{L1} = U_{L2}$$

$$\text{if } \frac{U_s}{R_{s1} + R_L} = \frac{R_{s2}}{R_{s2} + R_L} (I_s)$$

$$\text{if } U_s = R_{s2} \cdot I_s \text{ and } R_{s1} = R_{s2}$$



$$U_{L2} = U_{L1} \quad \frac{U_s R_L}{R_{s1} + R_L} = \left(\frac{R_L R_{s2}}{R_{s2} + R_L} \right) I_s \quad \text{if } R_{s2} = R_{s1} \quad U_s = R_{s2} \cdot I_s$$

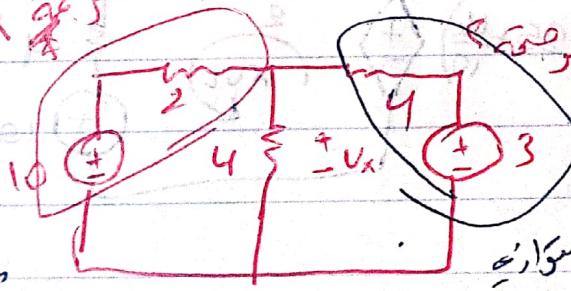Ex.
use source
Transformation
to find U_x



ترجمة (1)
10V source مع

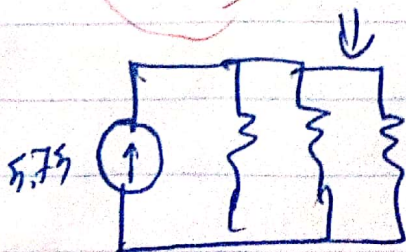
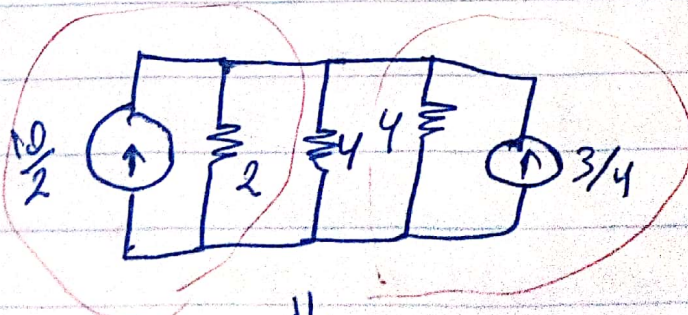
مقاومة بتحويلها
مع نفس المقاومة مع التوازي




$$R_{eq} = 2 \parallel 4 \parallel 4 = 1 \Omega$$

$$U_x = 5.75 V$$

Using S.T.F and V_x

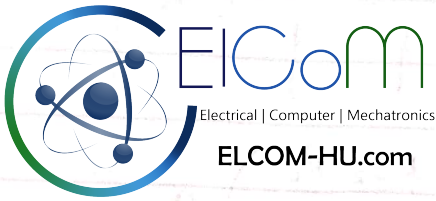
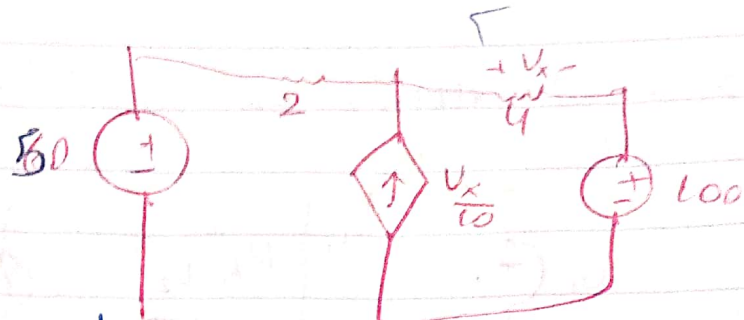


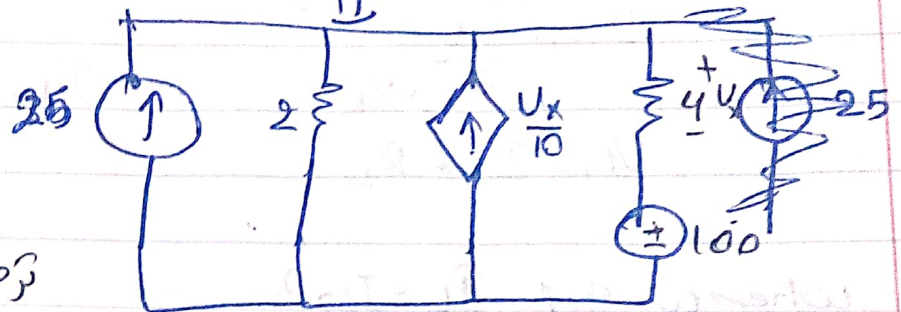غلط نعمل ترجمه للجزيء الذي يحتوي V_x على مشاع V_x بطل معروف




ترجمة ①

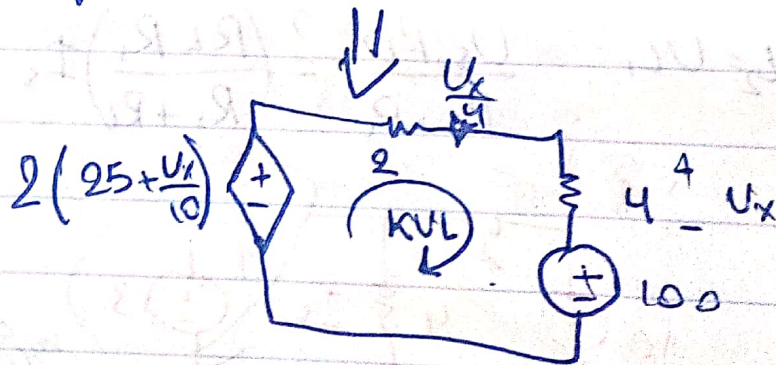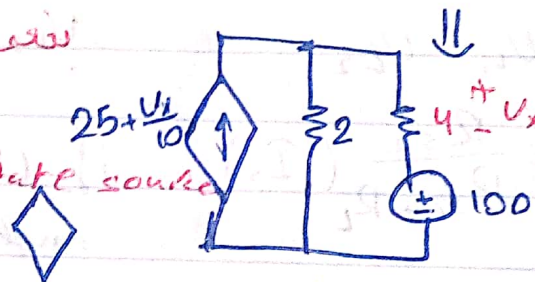نعمل ترجمه بتحويل dependent current source
تواري V_x مصدر V_x voltage source



→ Source Transformation

* maximum power Transfer Theory

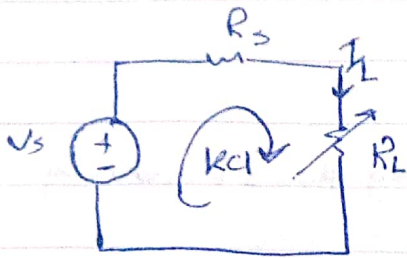

Find the maximum power dissipated in R_L

$$P_L = I_L \cdot V_L = I_L^2 R_L$$

$$-V_s + I_L R_s + I_L R_L = 0$$

$$I_L = \frac{V_s}{R_s + R_L}$$

$$P_L = \frac{V_s^2}{(R_s + R_L)^2} R_L$$

فستقر بـ R_L

$$\frac{\partial P_L}{\partial R_L} = \frac{V_s^2 (R_s + R_L)^2 - V_s^2 R_L (2)(R_s + R_L)}{(R_s + R_L)^4}$$


$$\frac{\partial P_L}{\partial R_L} = 0 \rightarrow \frac{V_s^2 (R_s + R_L)^2 - V_s^2 R_L (2)(R_s + R_L)}{(R_s + R_L)^4} = 0$$

$$(R_s + R_L)^2 - 2R_L(R_s + R_L) = 0$$


نذكر أن التزايد والتناقص

$$(R_s + R_L)^2 = 2R_L(R_s + R_L)$$

$$R_s = R_L$$

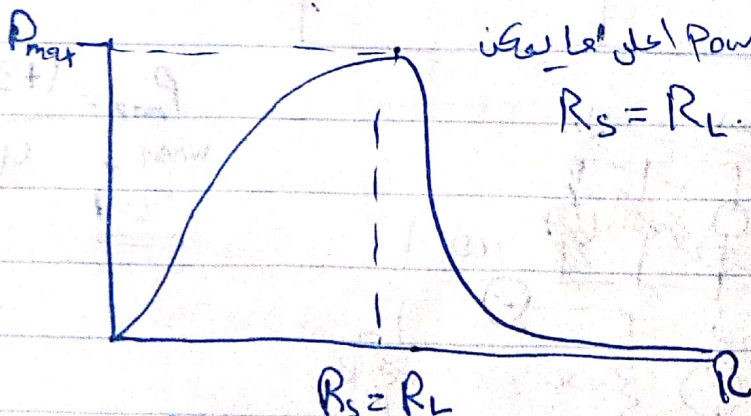


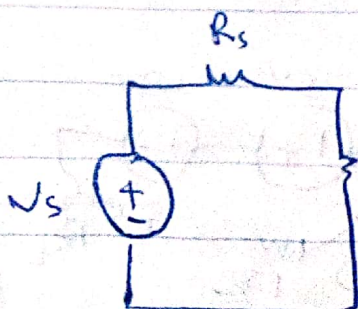يكون ال Power اقل لما يكون
عنه أكبر من $R_s = R_L$





$$R_L = R_s \Rightarrow I_L = \frac{V_s}{2R_s}$$

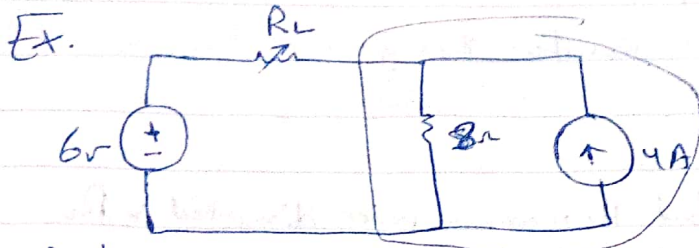
$$P_{\max} = I_L^2 R_L = \frac{V_s^2}{4R_s^2} R_s = \frac{V_s^2}{4R_s}$$



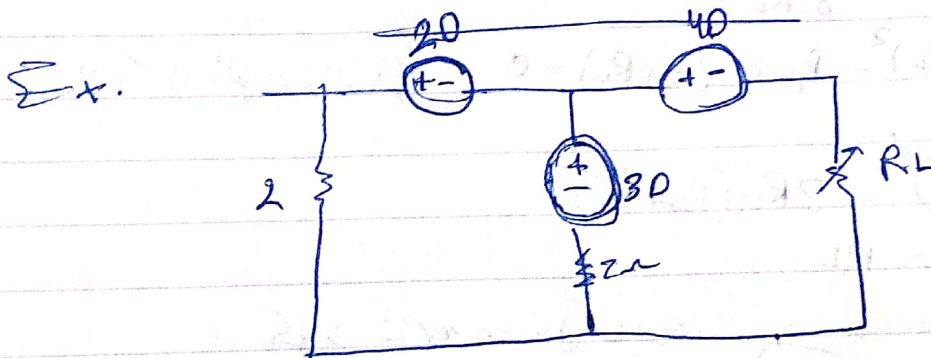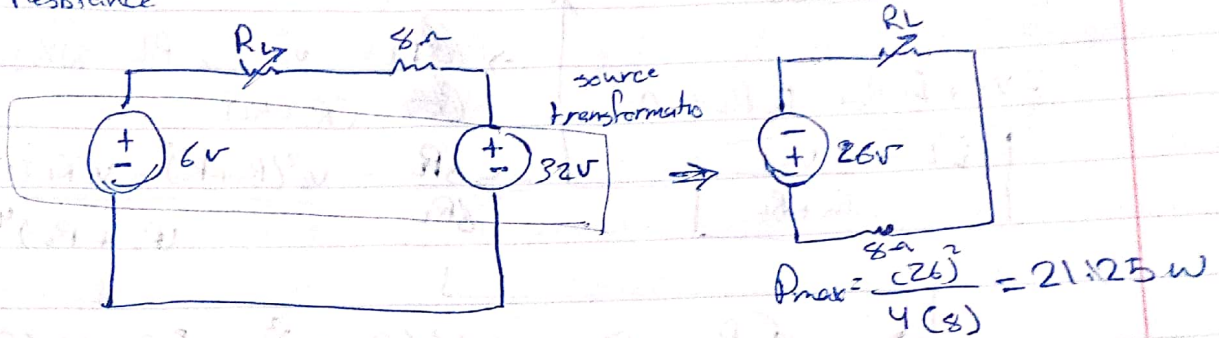→ Find max power delivered to R_L Assuming that R_L is varying Resistance






Find P_{max}

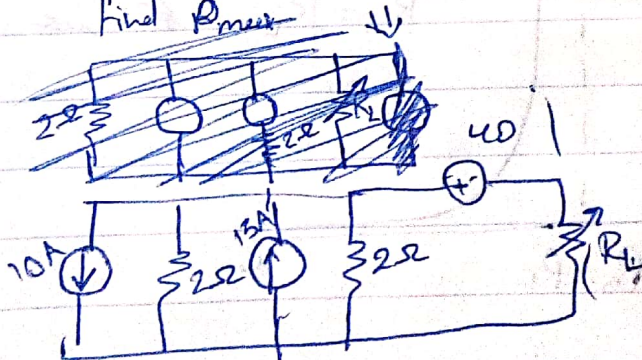

$$P_{max} = \frac{(1+35)^2}{4(1)}$$

when \downarrow
 $R_L = 1$


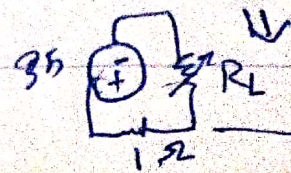
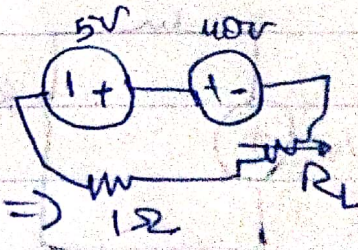
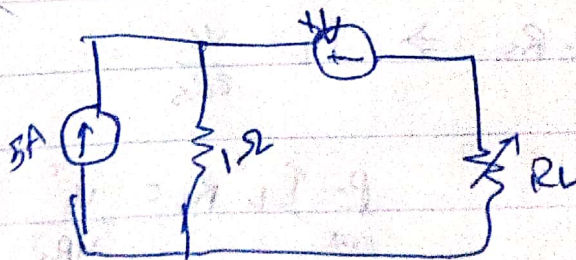


$R_L = 1\Omega$

→ Thevenin & Norton Theory :-


* Thevenin Equivalent Theory : any ckt can be reduced into a single V.S (V_{th}) in series with single Resistance (R_{th})

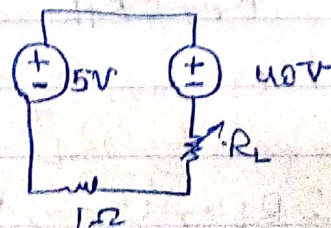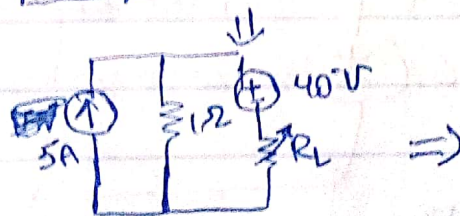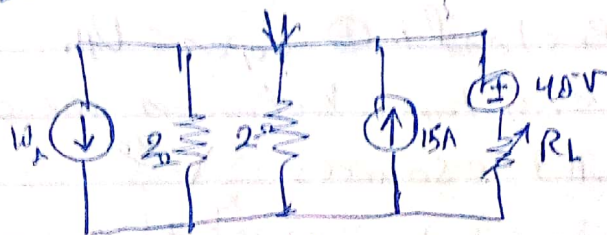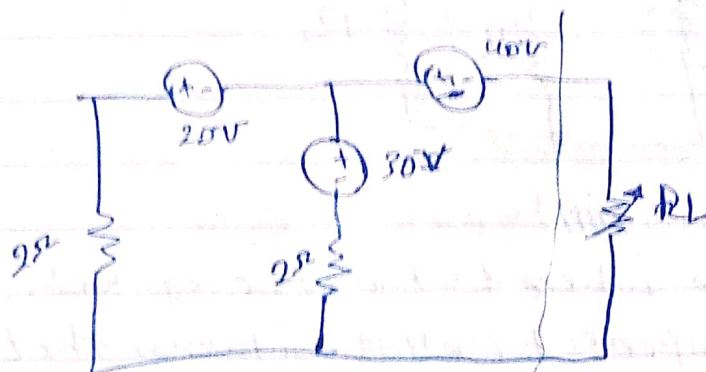* Norton Theory : Any ckt can be reduced into a single current source (I_n) in parallel with Resistance (R_n)



thevenin equivalent


$$V_{th} = -35 \quad R_{th} = 1\Omega$$

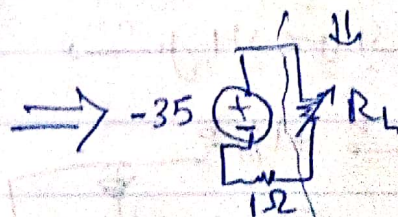

Norton equivalent


$$I_N = \frac{V_{th}}{R_{th}} = -35A$$

$$R_{th} = R_{th} = 1\Omega$$

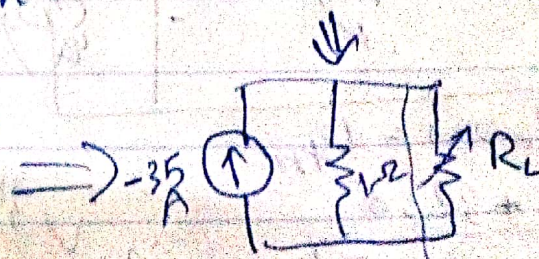

$$V_{th} = I_N \cdot R_N$$


$$I_N = \frac{V_{th}}{R_{th}}$$

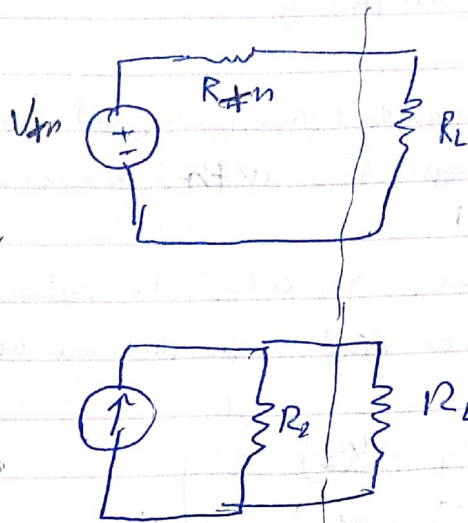


how to Find the ~~min~~ Equivalent ckt.

- ① Determine where to find the eq. ckt.
- ② Find the open ckt voltage between the two points you picked in ① $V_{open} = V_{th}$
- ③ Find the eq. Resistance between the same two points. After you kill the sources $R_{eq} = R_{th}$

Find the ~~min~~ eq ckt as seen by R_L

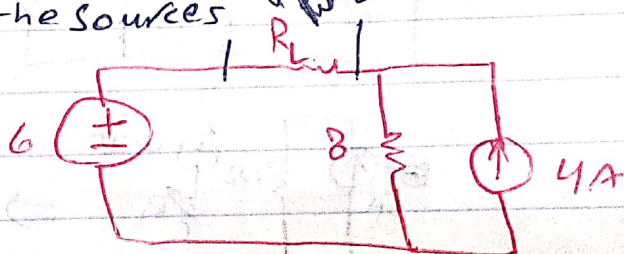

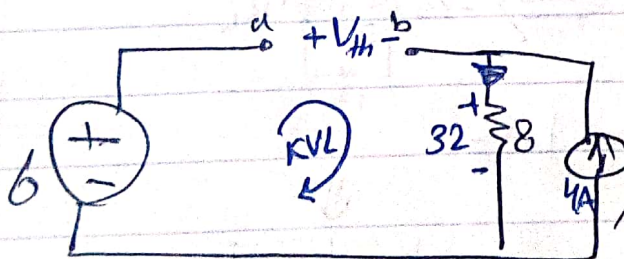جواب زي كانو R_L بتجرب
بشكل اللى انا اقدر أقوف فيه




$$V_{open} = V_{th}$$

$$-6 + V_{th} + 32 = 0$$




$$V_{th} = -26V$$

بشكل اللى انا اقدر أقوف فيه
بشكل اللى انا اقدر أقوف فيه

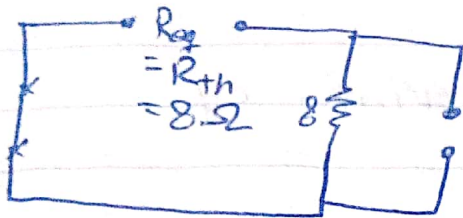Assum
Source
Transformation
~~should not be used~~
should not be used



$$R_{th} = 8$$

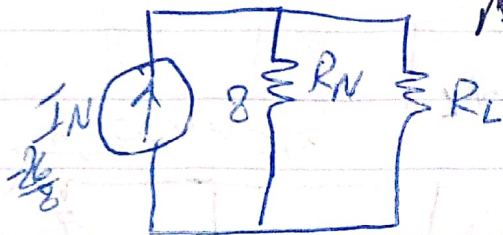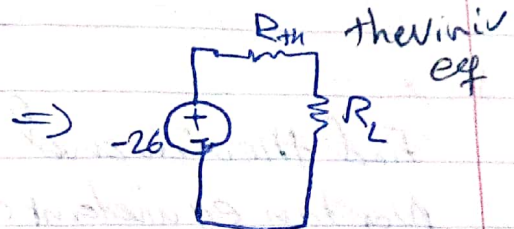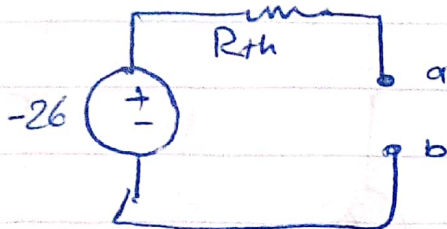


Norton eq

$$I_N = \frac{V_{th}}{R_{th}}$$

هوت يعرف thevenin

To find Norton eq.

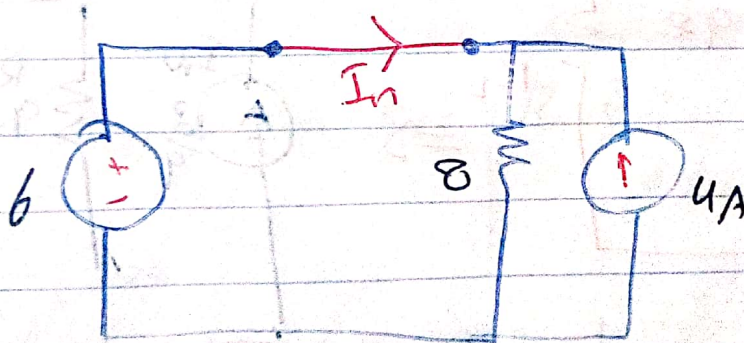
- ① determine the two point a, b in which you find the effect.
- ② Find the short ckt current between (a, b) $I_{s.c} = I_N$
- ③ Find R_{eq} similar to R_{th} $R_{th} = R_N$




$$I_{8\Omega} = \frac{6}{8} = \frac{3}{4}$$

$$I_N + 4 - \frac{3}{4} = 0 \Rightarrow I_N = -\frac{13}{4} A$$



$$R_N = R_{th}$$

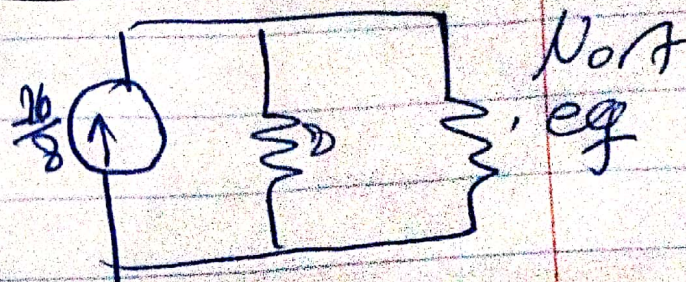

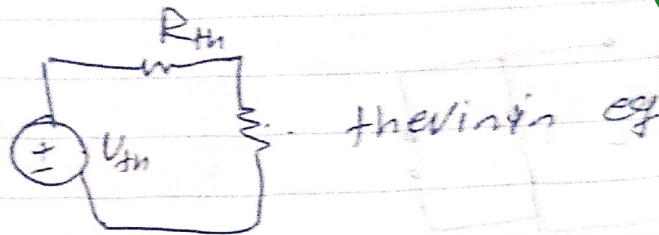


Ex

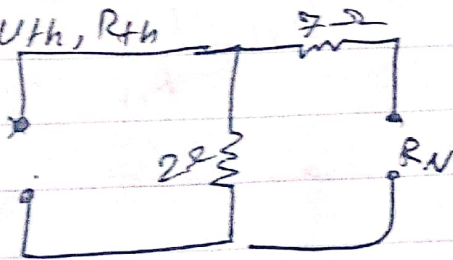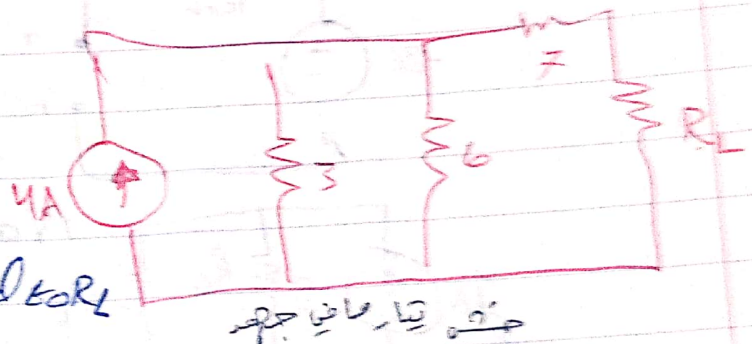Find thevenin and Norton equivalent circuit and find max power that can be delivered to R_L to find V_{th} , R_{th}





$$R_N = 9 \Omega$$

$$= (3 \parallel 6) + 7 = 9 \Omega$$

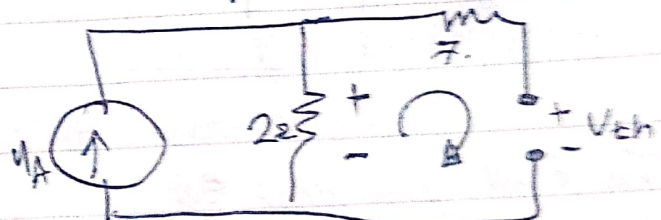

$$V_{th} = 8V = 2 \times 4 =$$

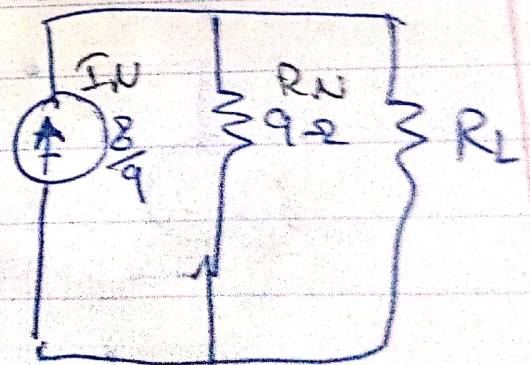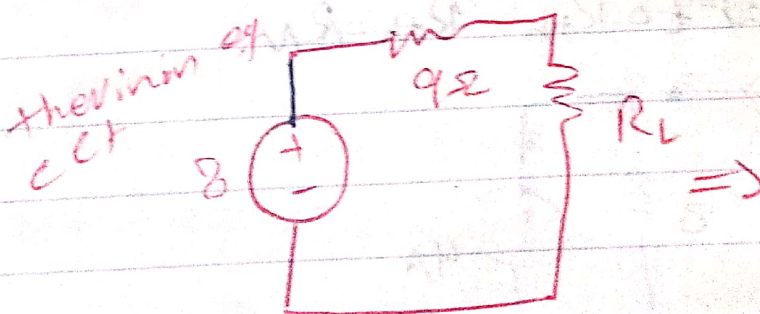

To find R_N, I_N


جول واربع دوائر

$$R_{eq} = 3 // 6 // 7$$


$$= \frac{14}{9}$$

$$I_N = I_{7\Omega} = \frac{14/9}{7} (4)$$


$$= \frac{8}{9} A$$

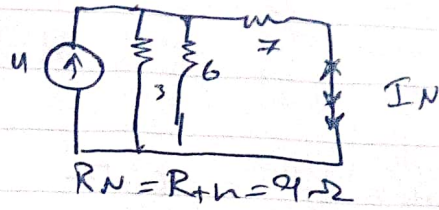

Norton current source

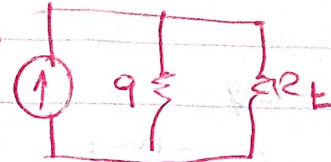

thevenin voltage source

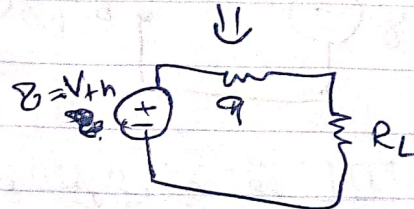

What is β :-

- ① Dependent and independent
- ② Dependent β

Case I :- ckt with independent source

Case II :- ckt with dependent and independent source

Case III :- ckt, with dependent source only

cases :- $V_{op} = V_{th}$ $R_{eq} = R_{th}$ $I_N = \frac{V_{th}}{R_{th}}$ $R_N = R_{th}$
 $I_N = I_{s.c}$

case II

Ex Find thevenineg as seen by a, b

$$V_{th} = V_{0.2} = V_{ab} = X_x$$


$$KVL \rightarrow -4 - \frac{V_x}{2} + 0 + V_x = 0$$

$$V_x = 8V$$

$$R_{th} = R_{eq}$$


$$\left(R_{th} = \frac{V_{th}}{I_N} \right)$$

كيف نجد R_{th} β تغير

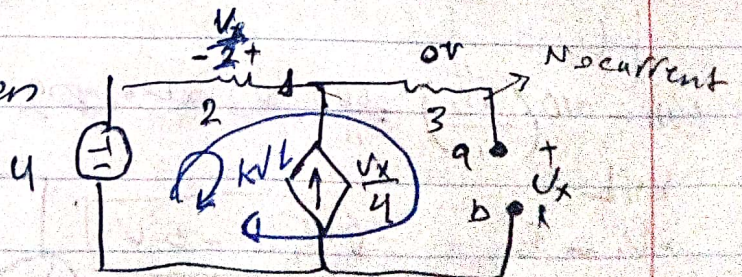

I_{N0}

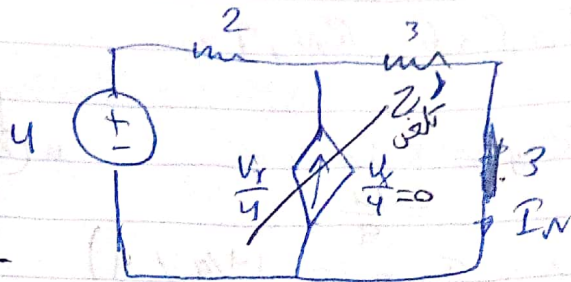
$$R_{th} = \frac{U_{th}}{I_N} = 10 \Omega$$





↓ V_x shorted \rightarrow صفر

↓ $R_{eq} = 2 + 3$

Thévenin eq

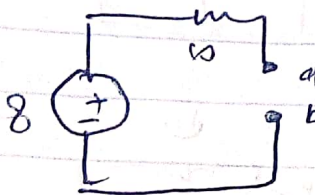

Norton eq

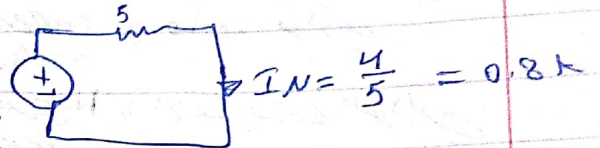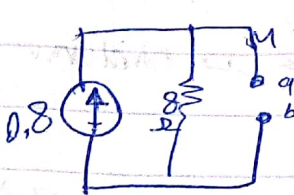

* case III \rightarrow يكون I_N يكون V_{th} يكون قيمة المتغير فيه

$$V_{open} = U_{th} = \text{Zero}$$

$$I_N = \text{Zero}$$

صفر

حالة

حالة

(indep) source

Ex case II

$$-5 - V_i + U_{th} = 0$$

$$U_{th} = 5 + V_i \rightarrow ①$$

$$U_{th} = -10V_i \rightarrow ②$$

$$U_i = \frac{-5}{11}$$

$$U_{th} = -10 \left(\frac{-5}{11} \right) = \frac{50}{11}$$

KVL



$$-V_i = 5 = 0 \Rightarrow V_i = -5V$$



KVL

$$-50 + 2I_N = 0$$

$$I_N = 25A$$

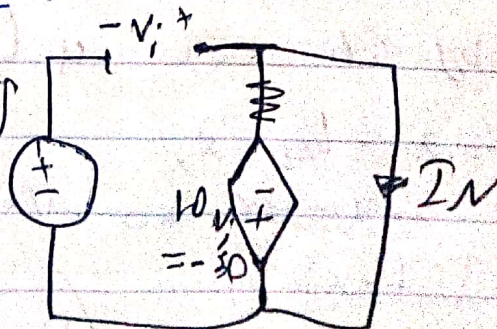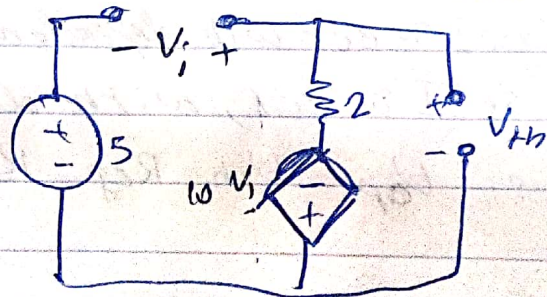
$$R_{th} = \frac{50}{\frac{25}{11}} = \frac{2}{11} \Omega$$



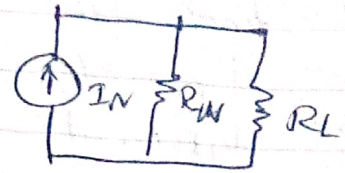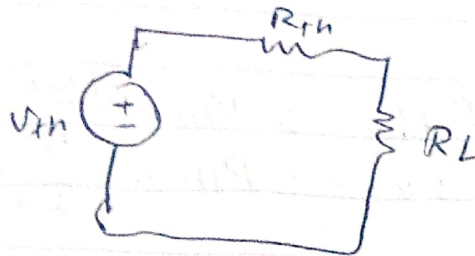


Ex for case III

Find thevenin and Norton as seen by R_L

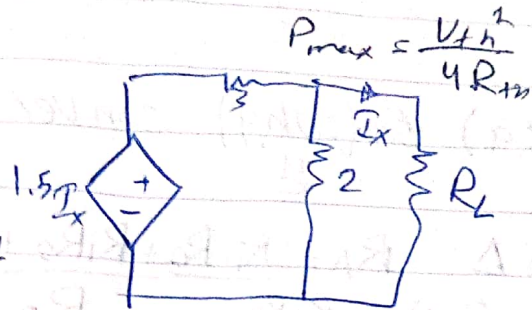

$$R_{eq} = (3 \parallel 2) = \frac{6}{5}$$

$$R_{th} = \frac{V_{oc}}{I}$$

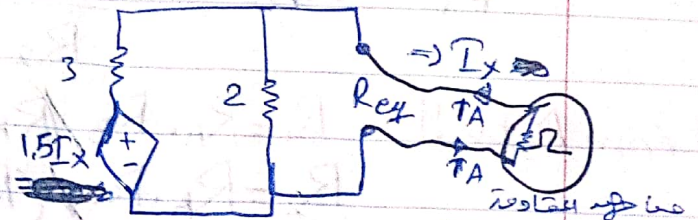



$V_{th} = V_{open\ circuit}$

I_{NCO}


عند ادمية نوعين

واحد بطرح واحد ادمية وحسب فولت



الآخر حله فقيده واحد فولت ويطرح الباقي

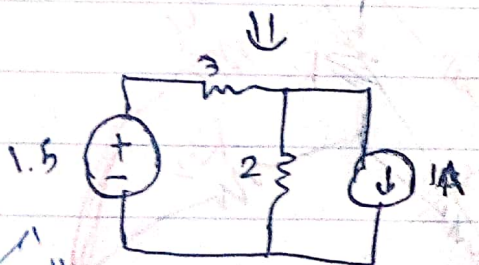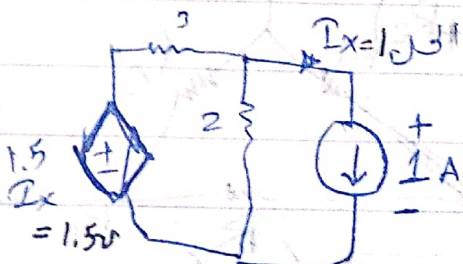

تقريباً

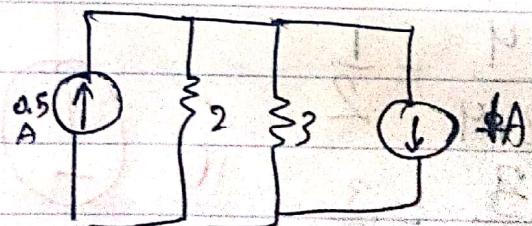
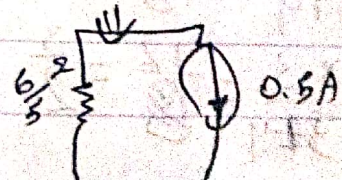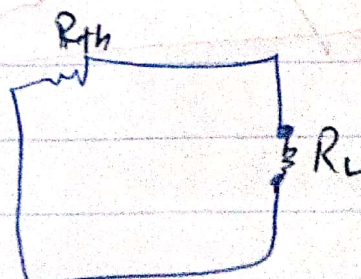
$$R_{eq} = \frac{1}{0.6} = \frac{10}{6} = \frac{5}{3} \Omega$$



$$V = \frac{6}{5} \cdot 0.5 = 0.6V$$


To find $R_{th} = \frac{0}{0}$?
 بقی $I_{test} = 1A \Rightarrow \text{Find } U_{oc} \Rightarrow R_{th} = \frac{U_{oc}}{1}$
 فیصل $U_{test} = 1V \Rightarrow \text{Find } I_{sc} \Rightarrow R_{th} = \frac{1}{I_{sc}}$

* (Delta) to (why) conversion

From Y to Δ $R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$
 $R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$
 $R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$

From Δ to Y $R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$
 $R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$
 $R_3 = \frac{R_B R_C}{R_A + R_B + R_C}$

Ex 8- Find I_{30}

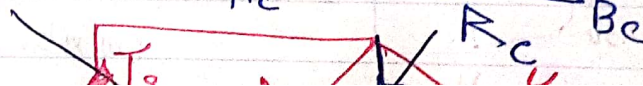

Ex 3 Find I_s

$$R_1 = \frac{1 \times 4}{1 + 3 + 4} = \frac{4}{8} = \frac{1}{2}$$


$$R_2 = \frac{1 \times 3}{1 + 3 + 4} = \frac{3}{8}$$

$$R_3 = \frac{3 \times 4}{1 + 3 + 4} = \frac{12}{8} = \frac{3}{2}$$



$$R_{eq} = \left(\frac{3}{2} + 5 \right) \parallel \left(\frac{3}{8} + 2 \right) + \frac{1}{2}$$

$$= 2.239 \Omega$$

$$I_s = \frac{10}{2.239} = 4.46 A$$

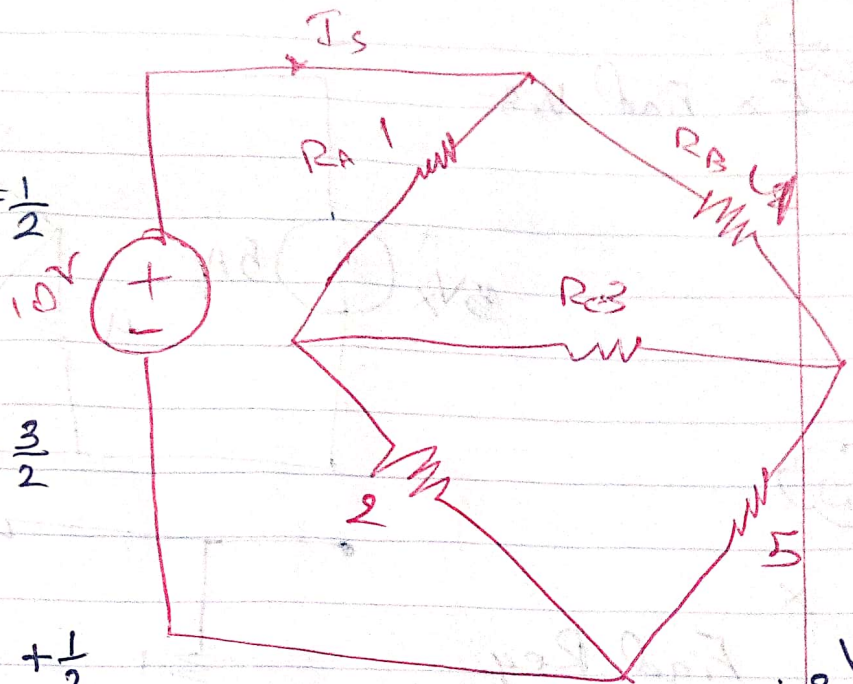


حولات
مقاومت

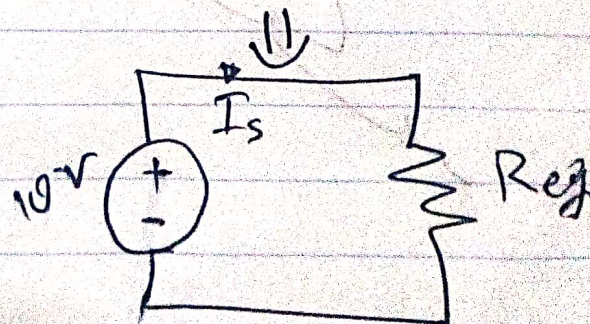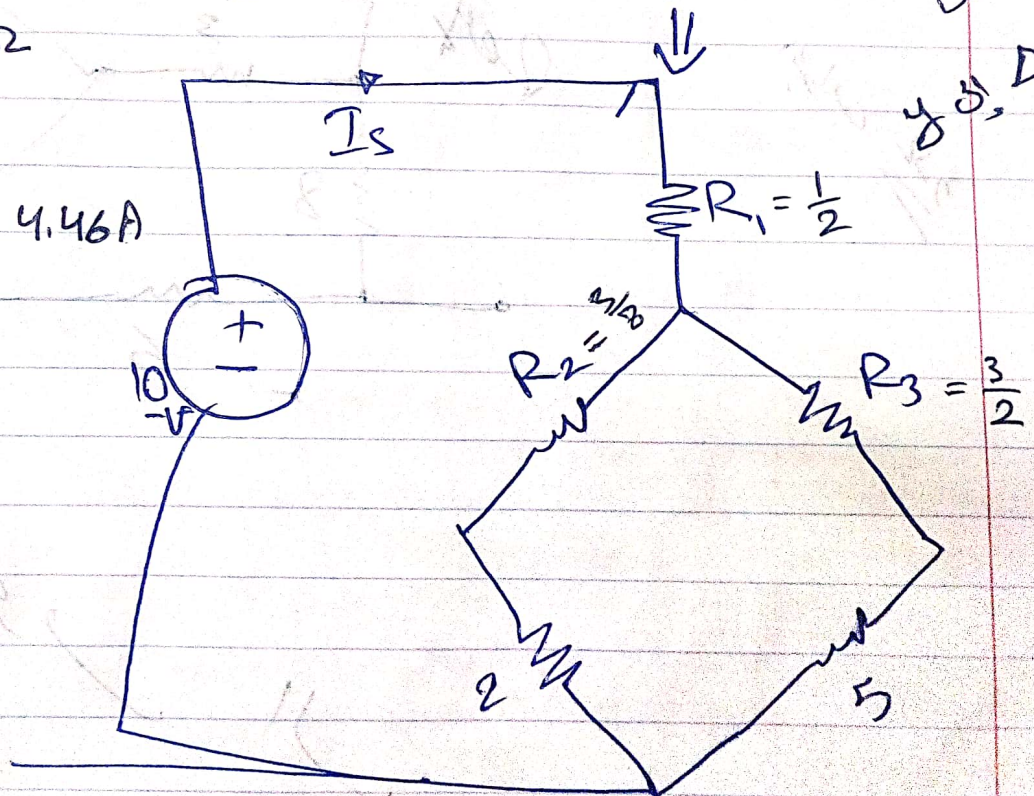

Ex


Find V_{12}

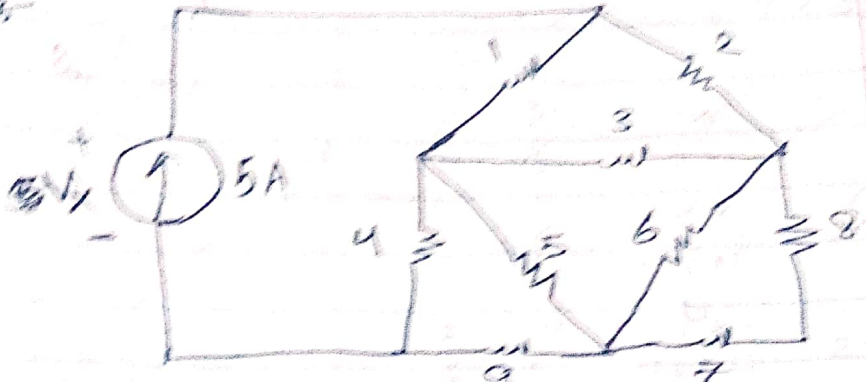

Ex

Find Req

Find Req

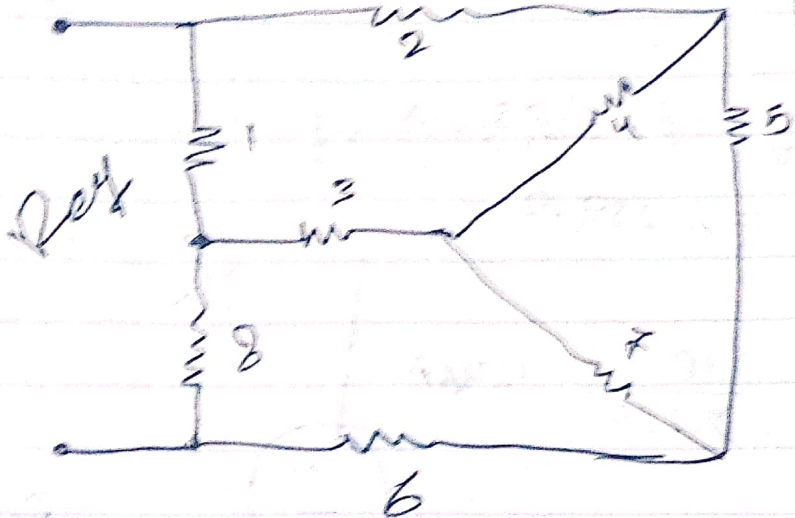

السؤال

✱ Final ✱


Inductors and Capacitors

✱ energy store in elements (Active elements)


Passive elements (Resistance) (can't store energy)

Capacitors ^{تخزين} $I_{discharge}$

$$I_c(t) = C \frac{dV_c(t)}{dt}$$


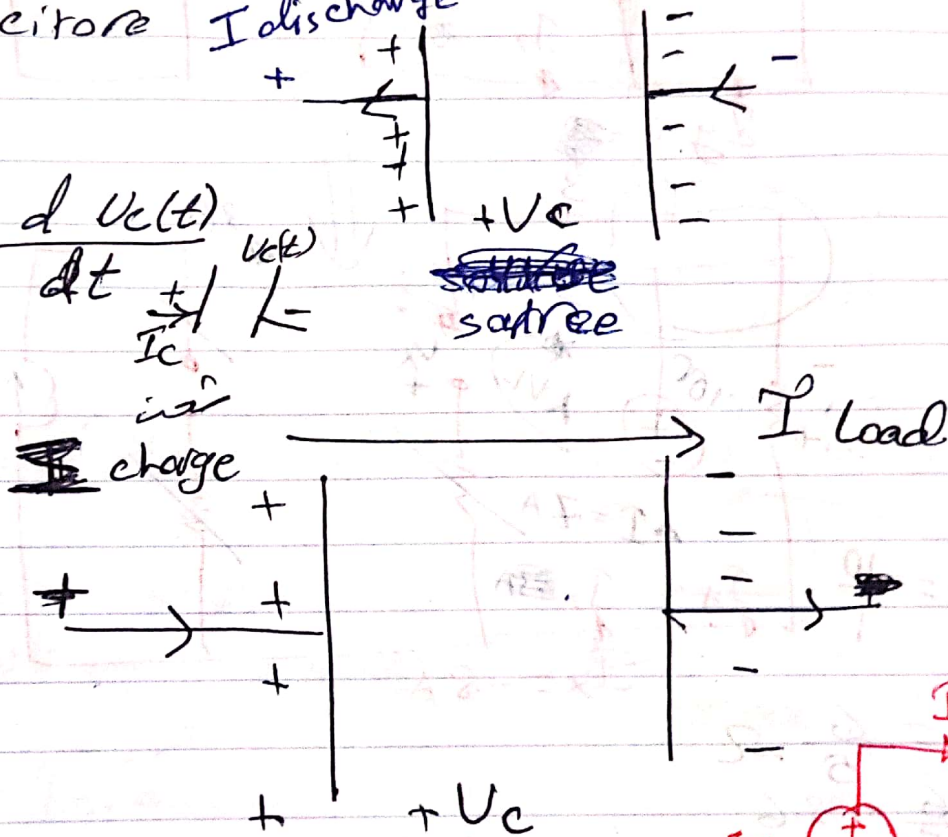


✱ $C \Rightarrow$ open ckt

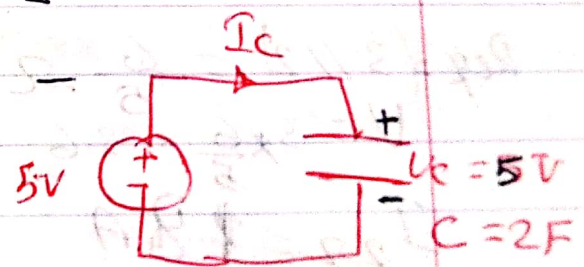

$$\begin{aligned} -5 + V_c &= 0 \\ \boxed{V_c = 5V} \end{aligned}$$

$$I_c = \frac{2d(5)}{dt} = \text{zero}$$

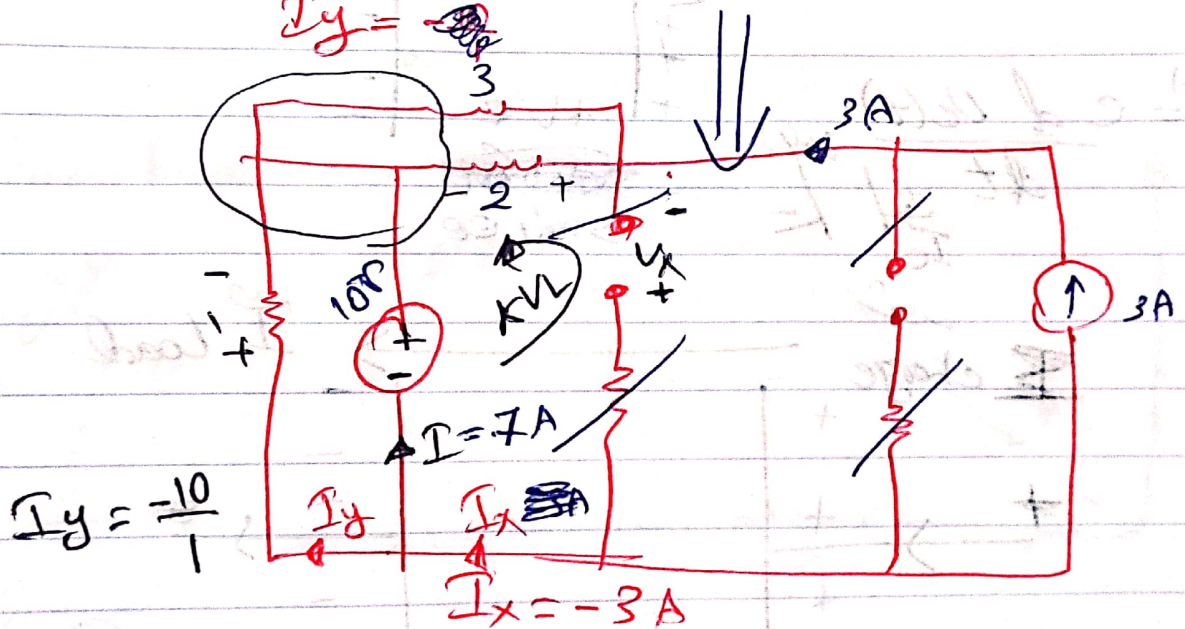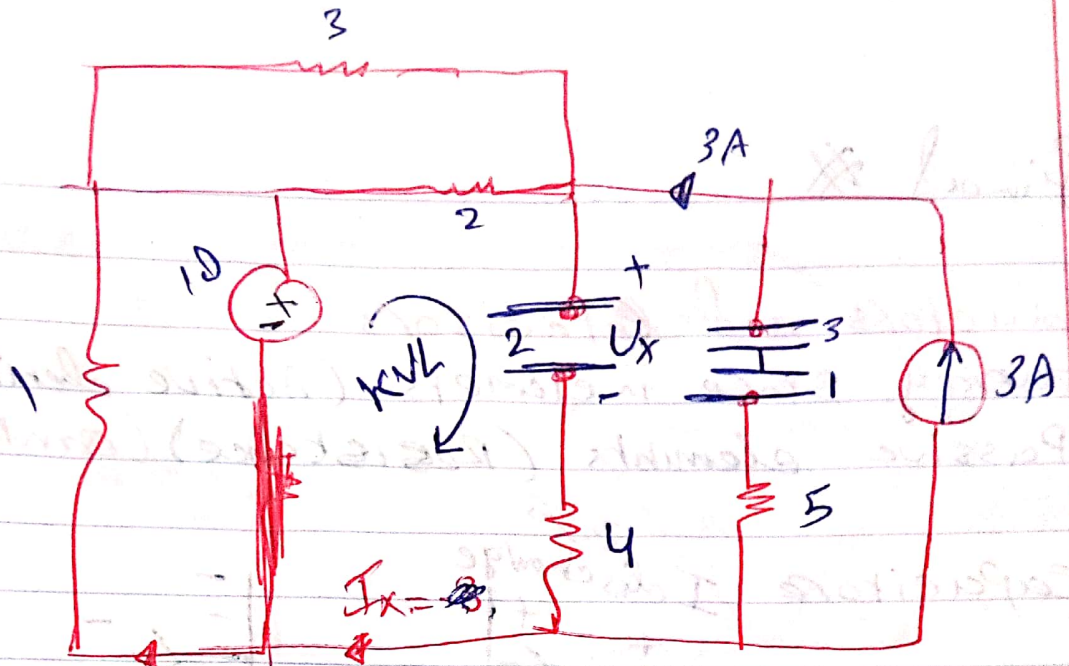

$$R_{eq} = (3 \parallel 2) = \frac{6}{5} \Omega$$

$$U = 3 \times \frac{6}{5} = 3.6$$

$$I_{2\Omega} = 1.8 A$$

$$+U + 2 \times 1.8 + 10 = 0$$

$$U = -13.6 V$$

الإحداثيات للـ V_c


$$V_c(t) \\ \rightarrow I_c(t) C$$

V_c is constant


$$I_c = \text{zero}$$

$$I_c = C \cdot \frac{dV_c}{dt}$$

Ex 8-

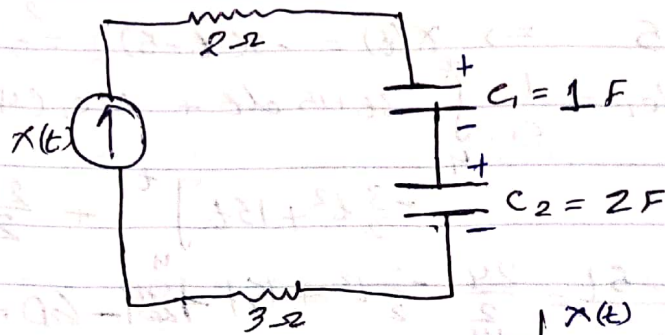

Find and plot V_{C1}, V_{C2}

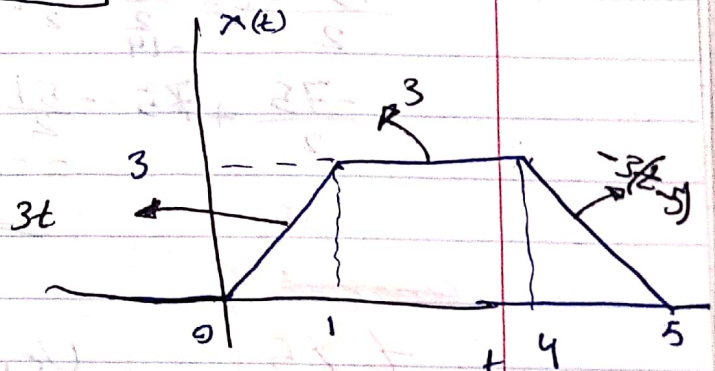

$$V_c(t) = \frac{1}{C} \int_{-\infty}^t I_c(t) dt$$

$$x(t) = I_{C1} = I_{C2}$$

$$V_{C1} = \frac{1}{C_1} \int_{-\infty}^t x(t) dt$$

$$mt + b = fx \\ \begin{aligned} 5m + b &= 0 \\ 4m + b &= 3 \\ \hline m &= -3 \\ b &= -15 \end{aligned} \quad \begin{aligned} & (5, 0) \\ & (4, 3) \end{aligned} \\ V_{C2} &= \frac{1}{C_2} \int_{-\infty}^t x(t) dt$$

$$\therefore 0 < t < 1 \quad x(t) = 3t$$

$$1 < t < 4 \quad x(t) = 3$$

$$4 < t < 5 \quad x(t) = 3(5-t)$$

$$\text{if } t < 0 \quad V_{C1} = 0, V_{C2} = 0$$

$$\text{if } 0 < t < 1 \quad V_{C1} = \frac{1}{C_1} \int_{-\infty}^t 3t dt$$

$$= \frac{1}{C_1} \left(\int_{-\infty}^0 0 dt + \int_0^t 3t dt \right) = \frac{1}{C_1} \cdot \frac{3}{2} (t^2 - 0) = \frac{3}{2} t^2$$

$$U_{C2} = \frac{1}{C_2} \int_{-\infty}^t 3t \, dt = \int_0^t 3t \, dt = \frac{3}{2} t^2$$

$$1 < t < 4 \quad x(t) = 3$$

$$U_{C1}(t) = \frac{1}{C_1} \int_1^t 3 \, dt + U_{C1}(1) = \frac{3}{2} + 3t \Big|_1^t = \frac{3}{2} + 3t - 3 = 3t - \frac{3}{2}$$

$$4 < t < 5 \Rightarrow x(t) = -3(t-5) = -3t + 15$$

$$U_{C1} = \frac{1}{C_1} \int_4^t (-3t + 15) \, dt + U_{C1}(4)$$

$$= \left[-\frac{3}{2} t^2 + 15t \right]_4^t + \frac{21}{2}$$


$$\frac{75 - 51}{2} = \frac{24}{2} = 12 \quad -\frac{3}{2} t^2 + 15t + 12 - 60 + \frac{21}{2}$$

$$= -\frac{3}{2} t^2 + 15t - \frac{51}{2}$$

$$\begin{array}{r} 72 \\ 21 \\ 51 \\ 510 \\ 60 \\ -24 \\ \hline 36 \end{array}$$

~~Current~~
 $t > 5$
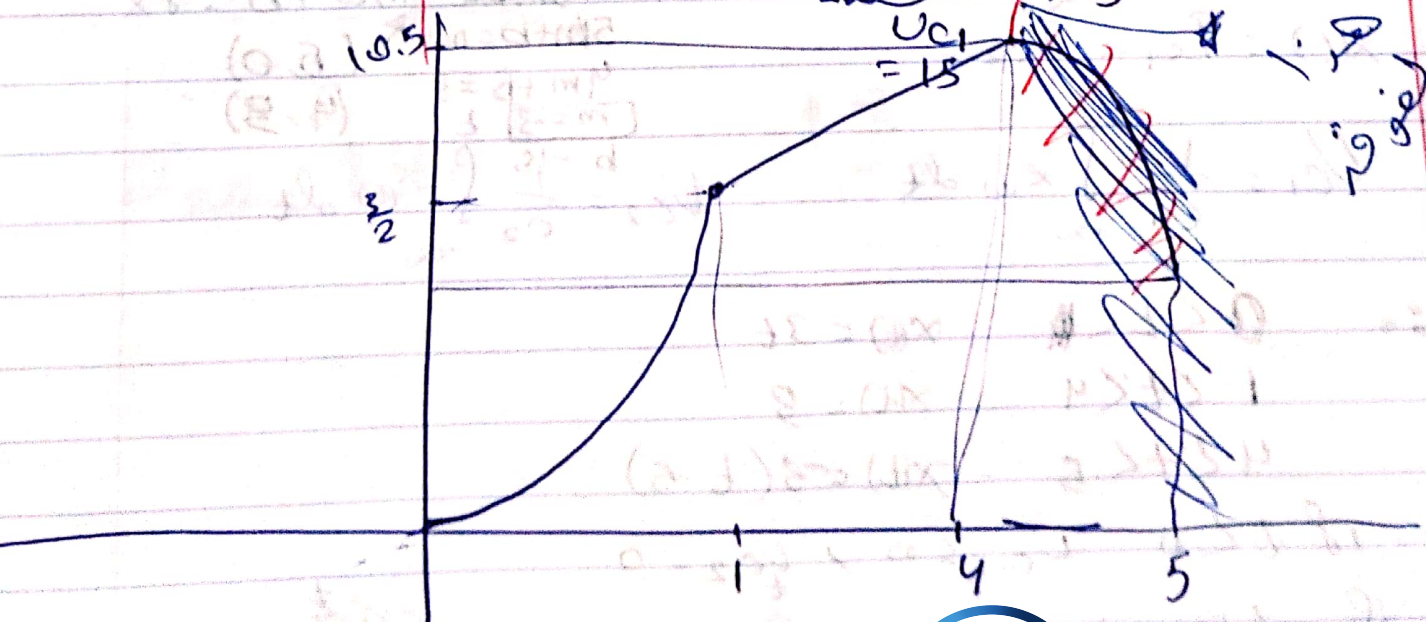
$$U_{C1} = \frac{1}{C_1} \int_{-\infty}^5 x(t) \, dt + \int_5^t x(t) \, dt$$



General rule

$$V_c(t) = \frac{1}{C} \int_{t_0}^t I_c(t) dt + V_c(t_0)$$

+ $V_c(t)$

LP & Ji

$$V_c(t) = \frac{1}{C} \int_{-\infty}^t I_c(t) dt$$


capacitor current is always continuous function

$$I_c(t_0^-) = I_c(t_0) = I_c(t_0^+)$$



من قبل من بعد

$$I_c(t) = C \frac{dV_c(t)}{dt}$$

Ex :-

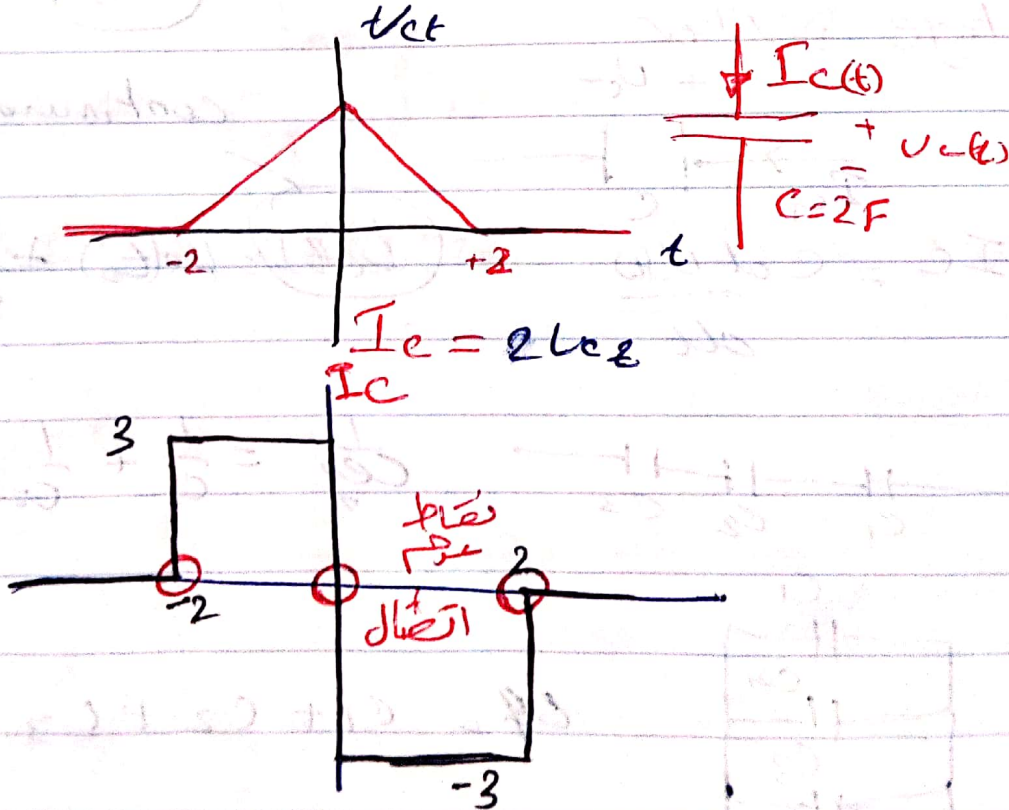

Eg. equivalent capacitance

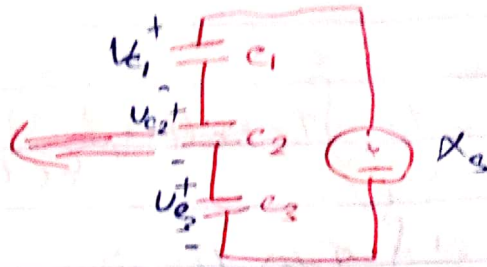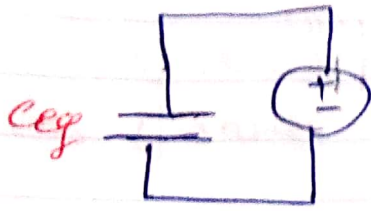

For series capacitor

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

For Parallel capacitor

$$C_{eq} = C_1 + C_2 + C_3$$

KVL

$$+U_{e1} + U_{e2} + U_{e3} - X_s = 0$$

$$X_s = \frac{1}{C_1} \int I_e dt + \frac{1}{C_2} \int I_e dt + \frac{1}{C_3} \int I_e dt$$

$$X_s = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) \int I_e dt$$


$$X_s = \frac{1}{C_{eq}} \int I_e dt$$

Can we apply current and Voltage Divider


$$I_e = C \frac{dU_e(t)}{dt}$$

continuous in time
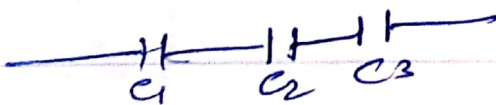
$$U_e(t) = U_e(t_0) + \frac{1}{C} \int_{t_0}^t I_e dt$$



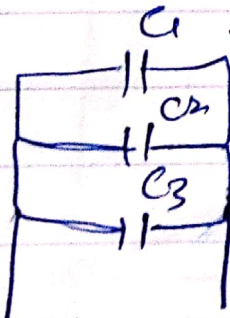
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



$$C_{eq} = C_1 + C_2 + C_3$$

Ex 3

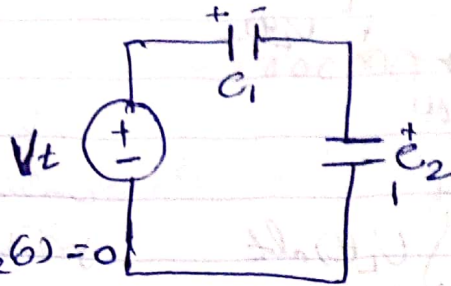

$$U_{C1}(0) = U_{C2}(0) = 0$$

$$U_{C1}(t) = \overset{\text{zero}}{U_{C1}(0)} + \frac{1}{C_1} \int_0^t I_C(t) dt$$

$$U_{C2}(t) = \overset{\text{zero}}{U_{C2}(0)} + \frac{1}{C_2} \int_0^t I_C(t) dt$$

KVL :-

$$-U(t) + \frac{1}{C_1} \int_0^t I_C(t) dt + \frac{1}{C_2} \int_0^t I_C(t) dt = 0$$


$$U(t) = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \int_0^t I_C(t) dt$$

$$U(t) = \frac{1}{C_{eq}} \cdot \int_0^t I_C(t) dt \Rightarrow \int_0^t I_C(t) dt = U(t) C_{eq}$$


$$U_C(t) = \frac{1}{C_1} * U(t) C_{eq} = \frac{C_{eq}}{C_1} U(t) \quad \text{Voltage divider}$$

مكثفات الأخر

لا يكونوا متوازيين مع current source

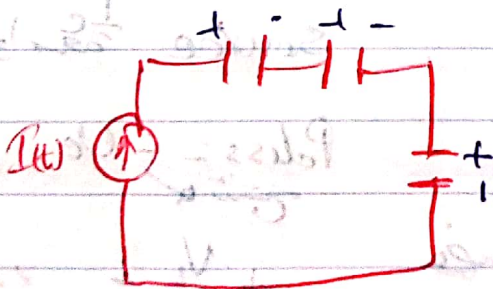

كون بتطلع الفولتية
مستقيمة بس

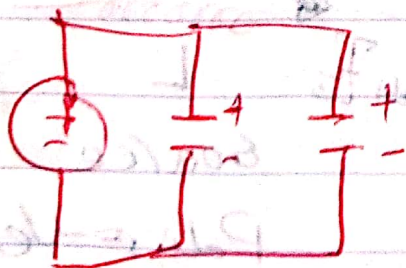


هون بتطلع البنية
بسهولة

يعاقل زيف



$$V_L(t) = L \frac{dI_L(t)}{dt}$$

$$I_L(t) = I_L(t_0) + \frac{1}{L} \int_{t_0}^t V_L(t) dt$$

رسمه ان تكون
متصلة (continuous)
مع الزمن

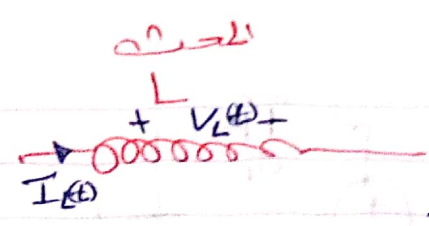

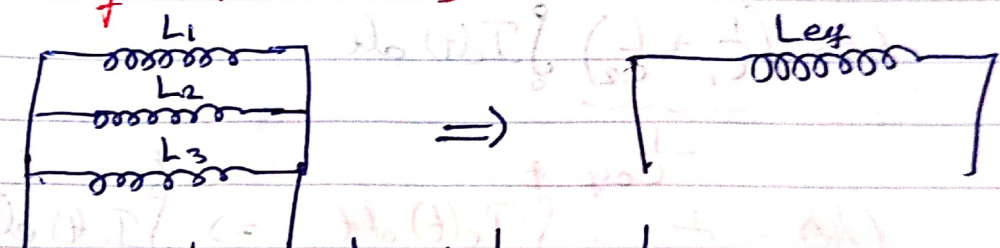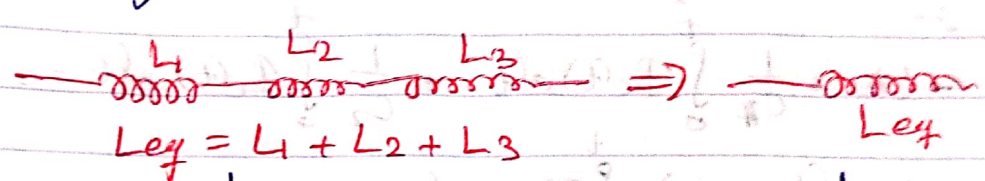
لا يكون عليها تيار
علا، جبر يتكون بتسلسل
حالتها بطارية فلا يتصل
التيار الخارجية يتحول
المحس، ان كانو
source فيبدي بطا
تيا.



$$\frac{1}{Leq} = \frac{1}{L1} + \frac{1}{L2} + \frac{1}{L3}$$

خارجية


Note

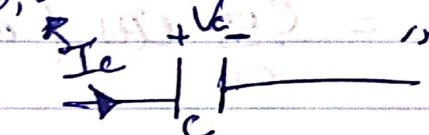

with local


$$P_{diss} = +U_c$$

فصلنا عن المصدر

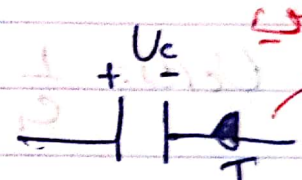

Source هذا المواجهة


$$P_{diss} = -U_c$$

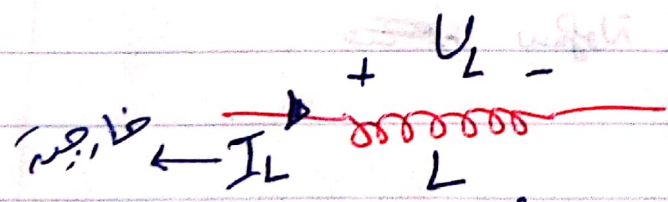

Local

$$P_{diss} = +U_L$$

فصلنا

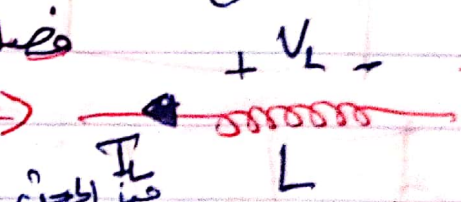

Source

$$P_{diss} = -U_L$$

For capacitor

Energy $W_c(t) = \int_{t_0}^t P(t) dt = \int_{t_0}^t e \frac{dV_c(t)}{dt} \cdot V_c(t) dt$

$= \int_{t_0}^t e V_c(t) dV_c(t)$

$W_c(t) = \frac{1}{2} C (V_c(t))^2 - W_c(t_0)$


$\frac{C \cdot (V_c(t))^2}{2} \Big|_{t_0}^t = \frac{1}{2} C (V_c(t))^2 - \frac{1}{2} C (V_c(t_0))^2$

If the initial energy is zero $W_c(t) = \frac{1}{2} C V_c^2(t)$

(EX) Find the total Energy stored inside the capacitor

Sol: $W_c(t) = \int_{t_0}^t P(t) dt = \int_{t_0}^{\infty} P(t) dt$

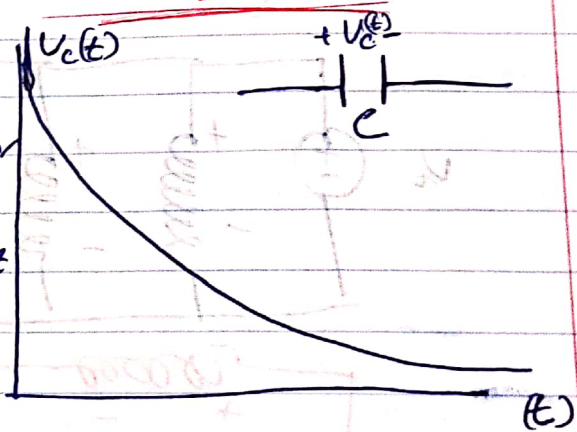$= W_c(\infty) = \frac{1}{2} C (V_c(\infty))^2 = \text{zero}$




هذا الزخم يتجهب إلى الصفر

فقدت الطاقة

$W_L = \frac{1}{2} L (I_L(t))^2 - W_L(t_0)$

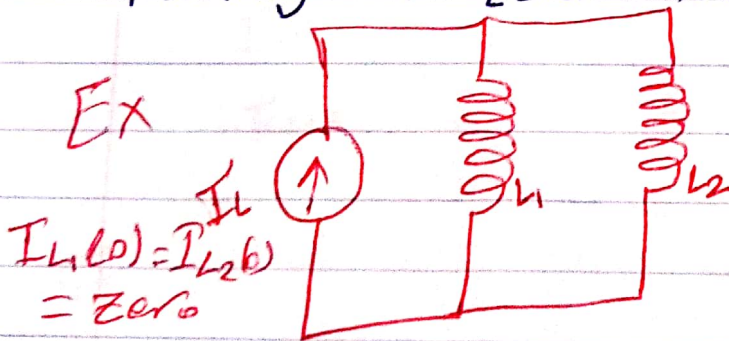Assuming that $W_L(t_0) = 0$ then $W_L = \frac{1}{2} L (I_L(t))^2$



$I_{L1} = \frac{1}{L_1} \int_0^t V_{L1}(t) dt + I_{L1}(0)$

$I_{L2} = \frac{1}{L_2} \int_0^t V_{L2}(t) dt + I_{L2}(0)$

$I_{L2} = \frac{1}{L_2} \int_0^t V_{L2}(t) dt + I_{L2}(0)$

Kcl

$I(t) - I_{L1} - I_{L2} = 0$

$$I(t) = \frac{1}{L_1} \int_0^t U_L(t) dt + \frac{1}{L_2} \int_0^t U_L(t) dt \quad U_{L1}(t) = U_{L2}(t) = U_L(t)$$


$$I(t) = \left(\frac{1}{L_1} + \frac{1}{L_2} \right) \int_0^t U_L(t) dt$$

$$I(t) = \frac{1}{L_{eq}} \int_0^t U_L(t) dt \Rightarrow \int_0^t U_L(t) dt = I(t) L_{eq}$$


$$I_{L1} = \frac{1}{L_1} \cdot L_{eq} \int_0^t I(t) dt = \frac{L_{eq}}{L_1} I(t) \quad (\text{current divider})$$

$$U_L(t) = L_{eq} \frac{dI(t)}{dt} \quad I(0) = 0 \text{ A}$$
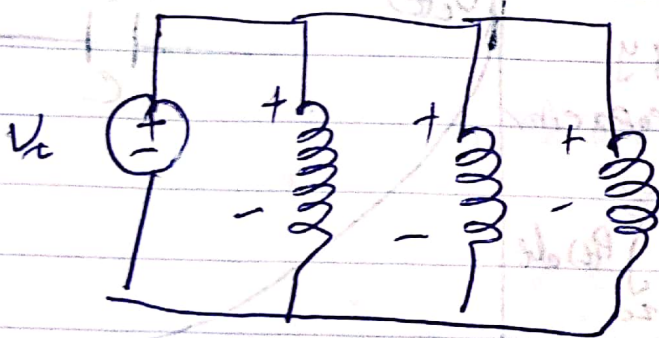
$$\int_0^t U_L(t) dt = \int_0^t L_{eq} \frac{dI(t)}{dt} dt = L_{eq} (I(t) - \underbrace{I(0)}_{\text{zero}})$$



جهد مشترك
التيار، فيه

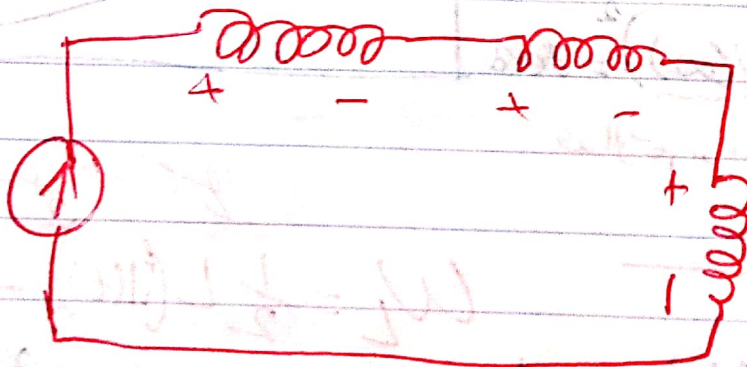


جهد مشترك
التيار، فيه

Source free RC and RL ckt

$$+V_L + V_R = 0$$

$$L \frac{di(t)}{dt} + R i(t) = 0$$

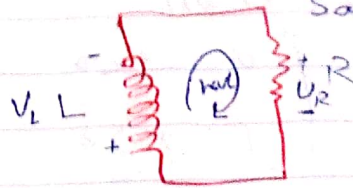

Source free RL ckt.

$$L \frac{di(t)}{dt} + R i(t) = 0 \quad \text{FODE}$$

يقتضي المعاد اذ كان
هو بطن التيار. وفي المعاد وعاد في بطن
فهو د اوتيا اذ

$$i(t) = A \cdot e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R} \quad \therefore \text{time constant}$$

To find A we need initial conditions $i(0) = ?? = A \cdot I_0$

$$i(t) = I_0 e^{-t/\tau}$$

$$I(0^-) = I(0) = I(0^+) \quad \text{continuously}$$

Plot


$$I(\tau) = I_0 e^{-1} = 0.87 I_0$$

$$I(2\tau) = I_0 e^{-2} = 0.94 I_0$$

$$I(3\tau) = I_0 e^{-3} = 0.96 I_0$$

$$I(4\tau) = I_0 e^{-4} = 0.98 I_0$$

$$I(5\tau) = I_0 e^{-5} = 0.99 I_0$$

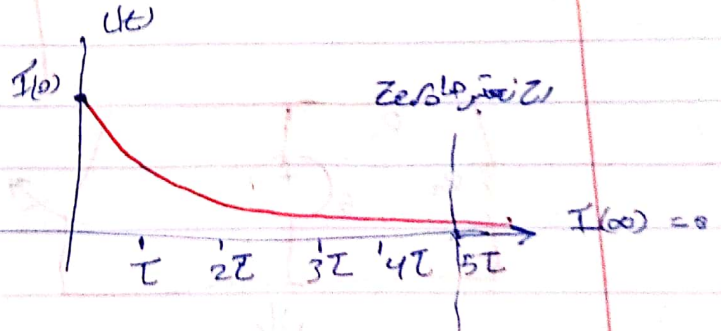


Source free RC ckt

KVL

$$+ (I(t) \cdot R) - \frac{1}{C} \int_{-\infty}^t I(t) dt$$

new

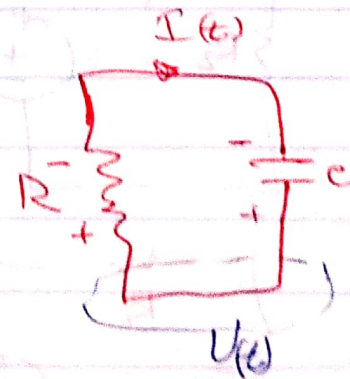

$$I \cdot R - \frac{1}{C} I(t) = 0 \quad \text{FODE}$$

$$I(t) =$$

KCL

$$+ \frac{V(t)}{R} + V_C \cdot C = 0 \quad \text{FODE}$$



$$V(t) = V_0 e^{-t/\tau}$$

$$\tau = RC \quad \text{time constant}$$


$$V_C(0) = V_0$$

unit step function

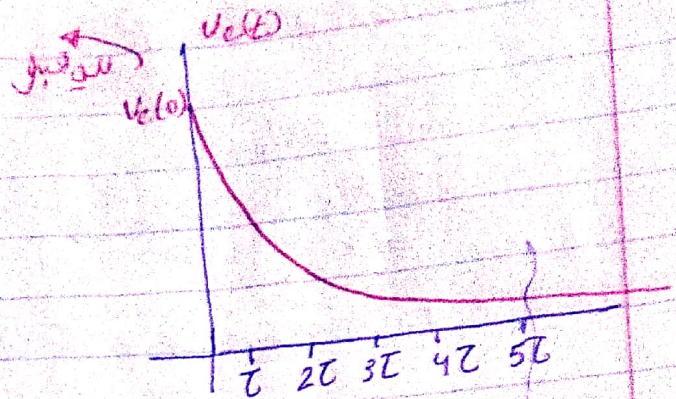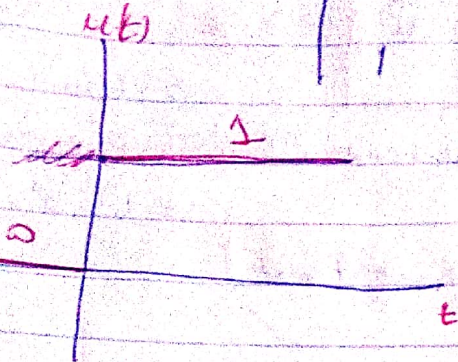
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$



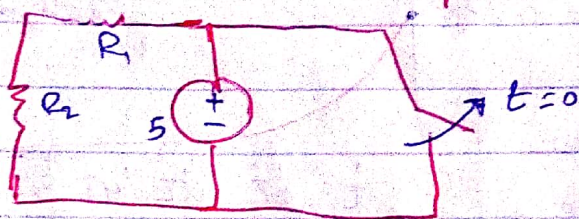
$$u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$$




Switch opens @ $t=0$

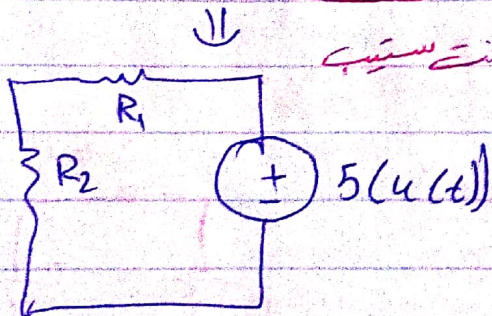


جولہ الحثا ح ر یونے سٹیپ
U.S.F

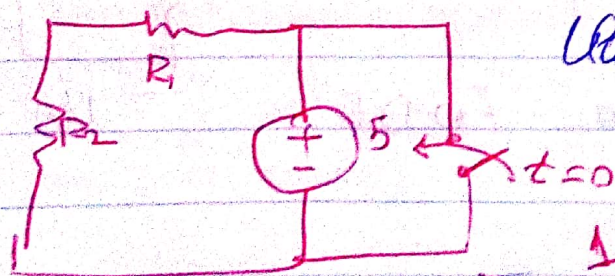

ح ر یونے سٹیپ $u(t) = 5u(-t)$

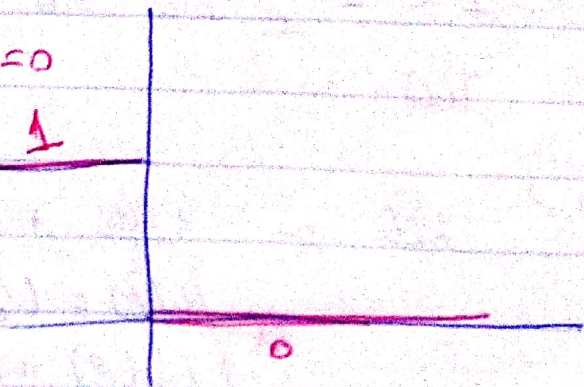


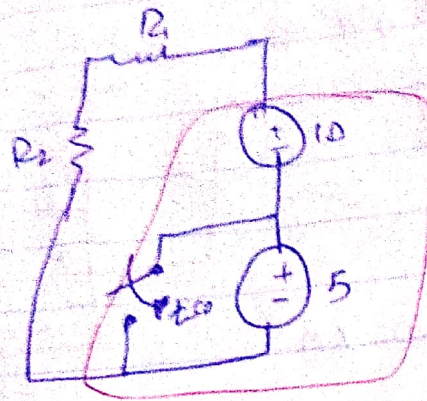


$$V(t) = 10 + 5 u(-t)$$

دالة الجهد


Ex 3

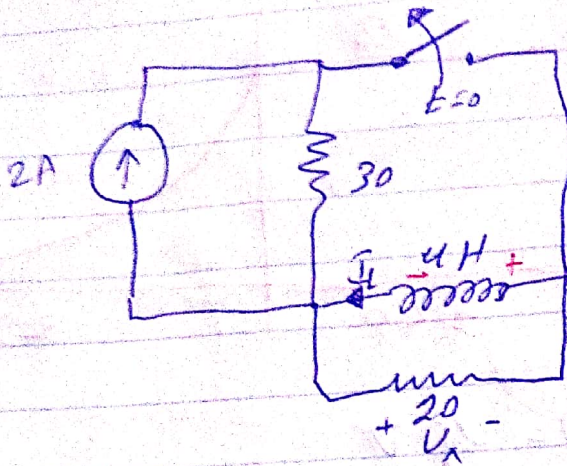

Sketch the ckt for $t < 0$ and $t > 0$

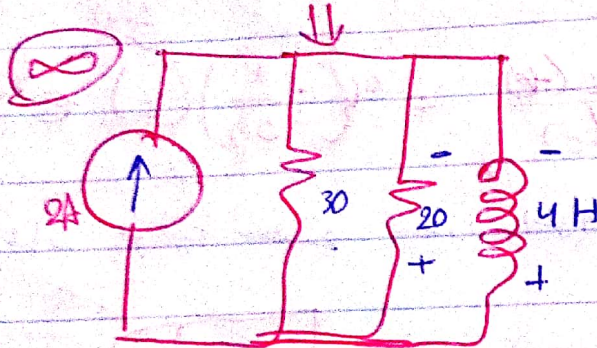

$t < 0$

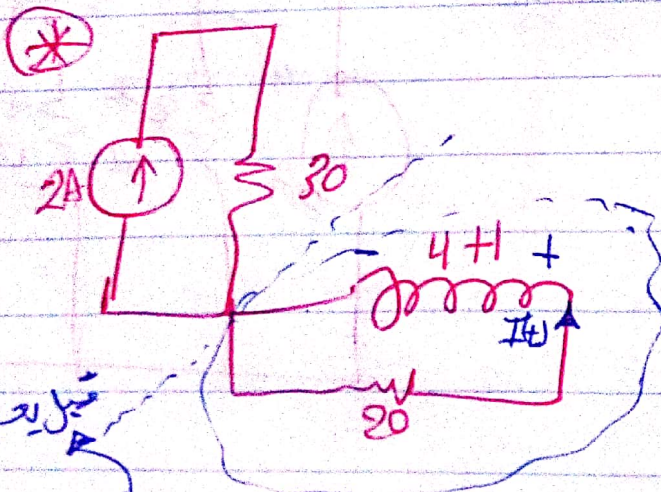

source free RL ckt


$$I(t) = I(0) e^{-t/\tau}$$

$$\tau = \frac{L}{R} = \frac{4}{20} = \frac{1}{5} = 0.2 \text{ sec}$$

قبل الفتح


$$I(0) = I(0^-) = I(0^+)$$

We Find $I_L(t)$ from graph (∞)

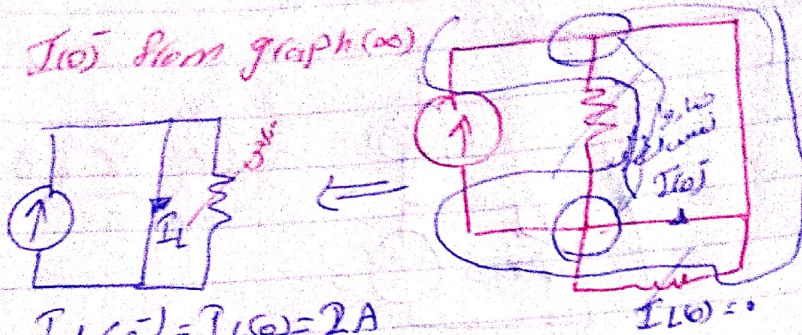

$$I_L(0^-) = I_L(0) = 2A$$

$$I(t) = 2e^{-t/0.2}$$

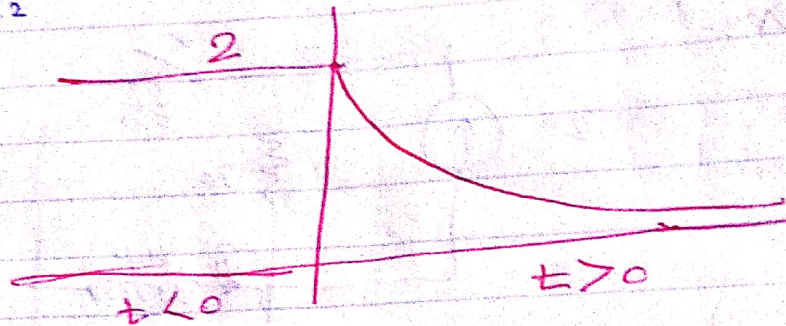


$$V_x = 2 \cdot 20 = 40V$$

$$V_L = L \frac{dI_L(t)}{dt} = 4 \left(-\frac{1}{0.2} \right) (2) e^{-t/0.2}$$

بعد إيجاد فولتية الحث بتقدير نحول إلى $-+$ ونحل السؤال


Find V_x Parallel time value

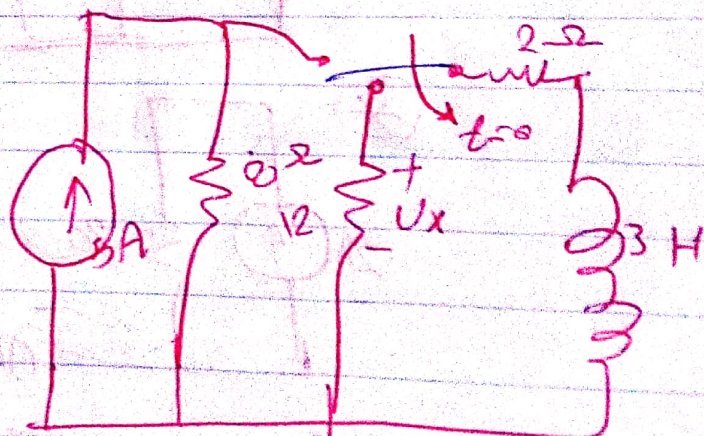

جریان در شاخه سلف


current divider
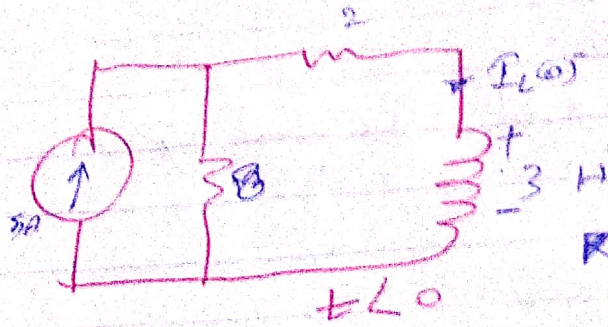
$$I_L(0) = \frac{(2/8) \cdot 5}{2} = 4A$$



$$I_L(t) = 4e^{-t/\tau}$$

$$V_x = I_L(t) \cdot R = 4e^{-t/\tau}$$

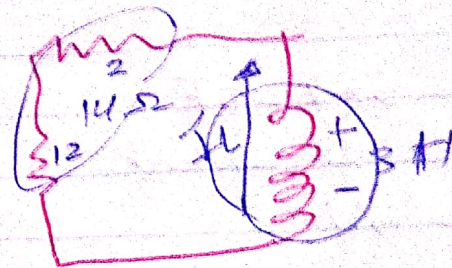


$$I_L(t) = I_L(0)e^{-t/\tau}$$

$$\tau = \frac{L}{R_{eq}} = \frac{3}{14} \text{ sec}$$


* Source free RLC:-
Source free RLC circuit.
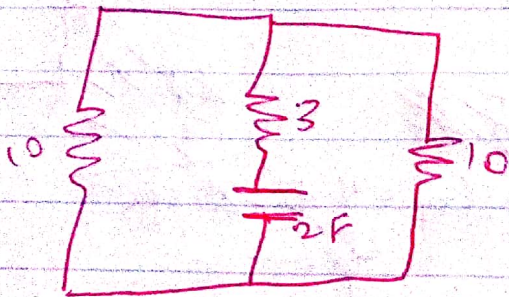
$$V_C(t) = V_C(0)e^{-t/\tau} \quad \tau = RC$$



$$V_C(t) = 2e^{-t/\tau} \quad I(0) = I(0^-) = 4A$$


جریان در شاخه سلف

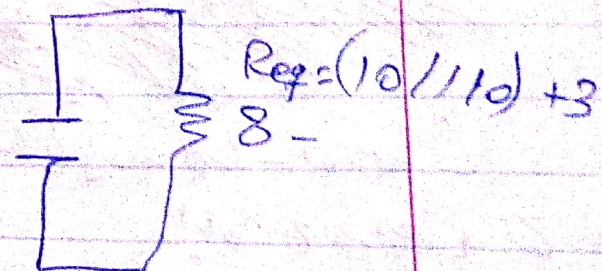


$$V_C(0) = 2V$$

Find $V_C(t)$

$$\tau = 8 \cdot 2 = 16 \text{ sec}$$

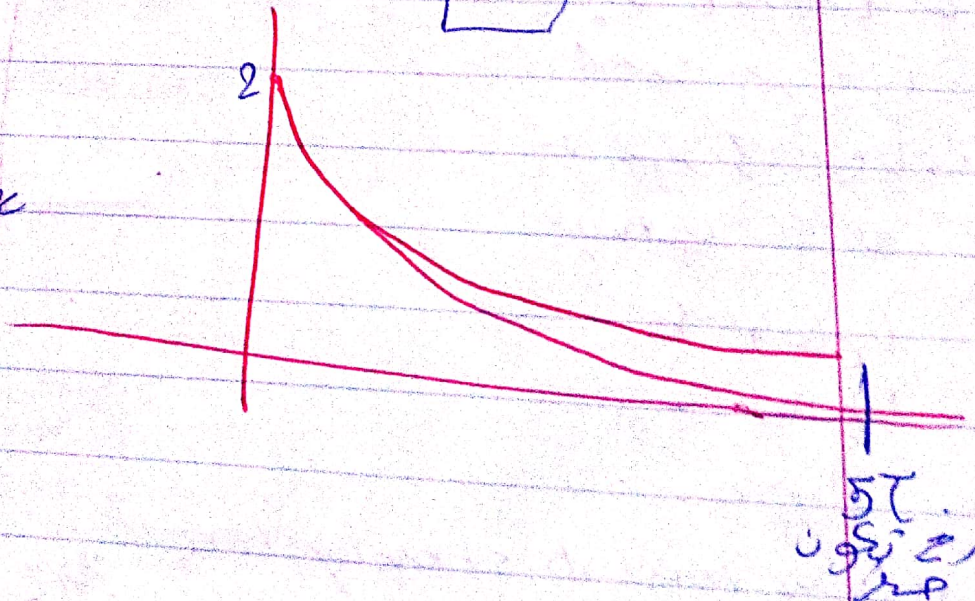


Switch
Ex: Find I_x and V_x


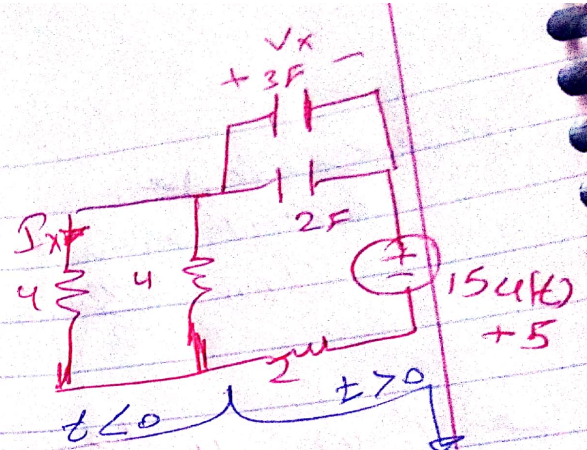


$$C_{eq} = 3 + 2 = 5F$$

XVL: No current
 $V_x = 5V$

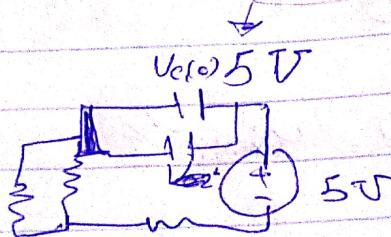

$$R_{eq} = (4/4) + 2 = 4\Omega$$

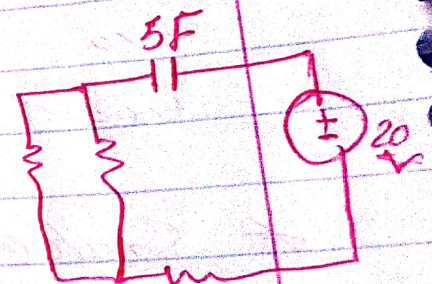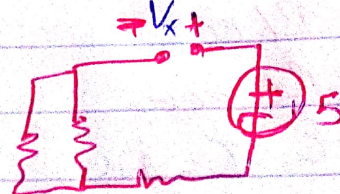


Driven Response (step.
(RC)

$$V(t) = V(\infty) - e^{-t/\tau} = V(\infty) - V(\infty)e^{-t/\tau}$$

$$= 5 - 5e^{-t/\tau}$$
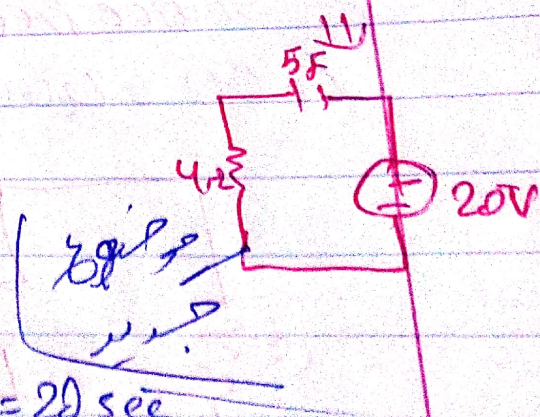
$$\tau = R_{eq} \cdot C_{eq} = 4 \cdot 5 = 20 \text{ sec}$$




Driven Response (step Response)

$$V_C(t) = V_{C(\infty)} + V_{C(0)} [1 - e^{-t/\tau}]$$

general

$$V_C(t) = V_{C(\infty)} + [V_{C(0)} - V_{C(\infty)}] e^{-t/\tau}$$


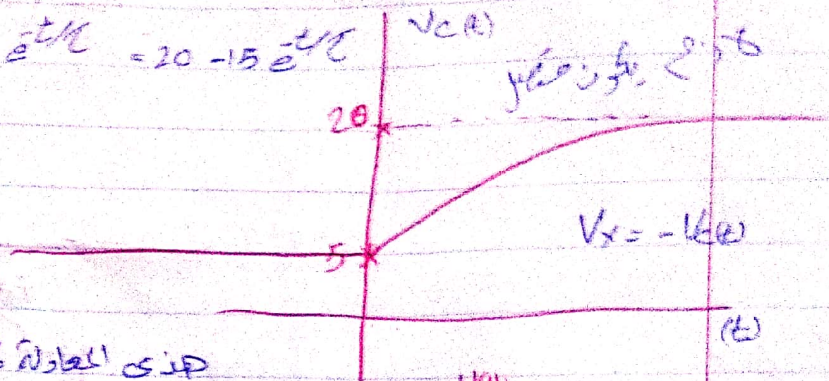
$$V_C(t) = 20 + (5 - 20) e^{-t/\tau} = 20 - 15 e^{-t/\tau}$$




source voltage calculation

$$V_y = [15u(t) + 5 - V_C(t)] \left(\frac{2}{2+2} \right) \text{ for all } t$$

$$I_x = \frac{V_y}{4} \text{ A}$$

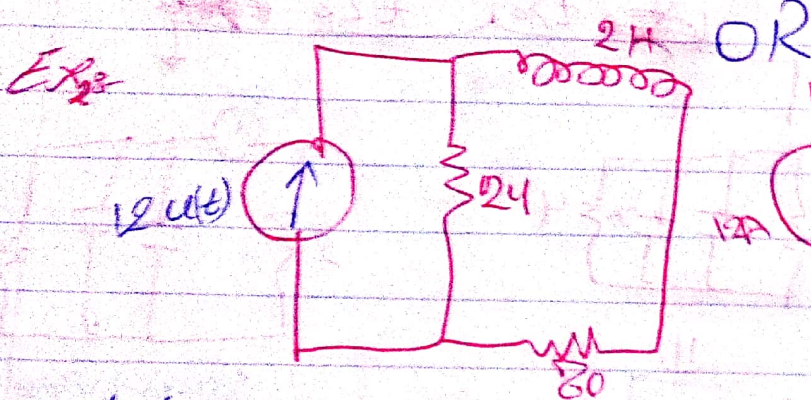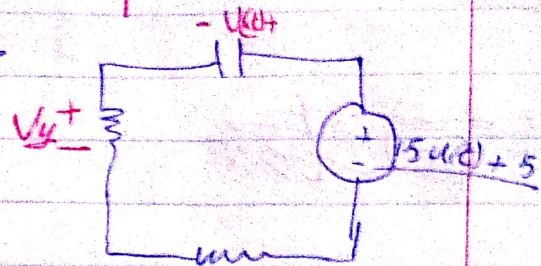


$t < 0$

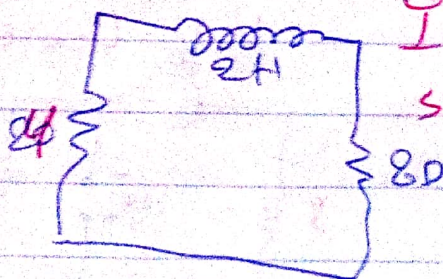


$$I_L(0^-) = 0$$

source free

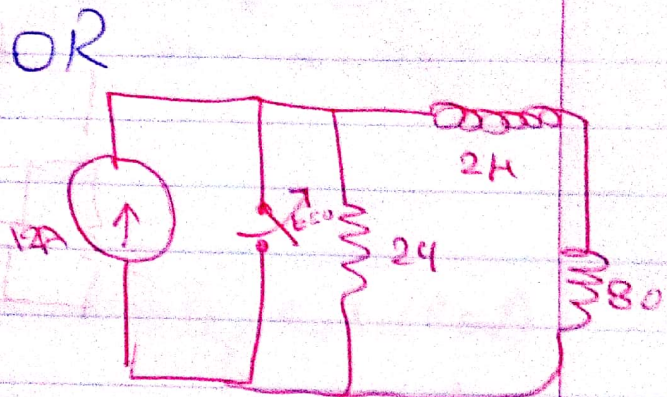

Driven (step Response) RL

$t > 0$

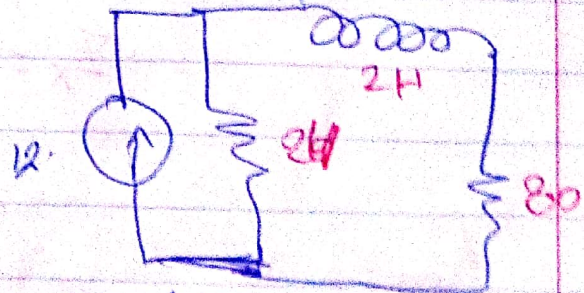


$$I_L(t) = I_L(\infty) + [I_L(0) - I_L(\infty)] e^{-t/\tau}$$

$$I_L(\infty) = \frac{12}{24 + 80} = 12$$

$R_{eq} = R_{th}$


at $t = \infty$ the capacitor is fully charged

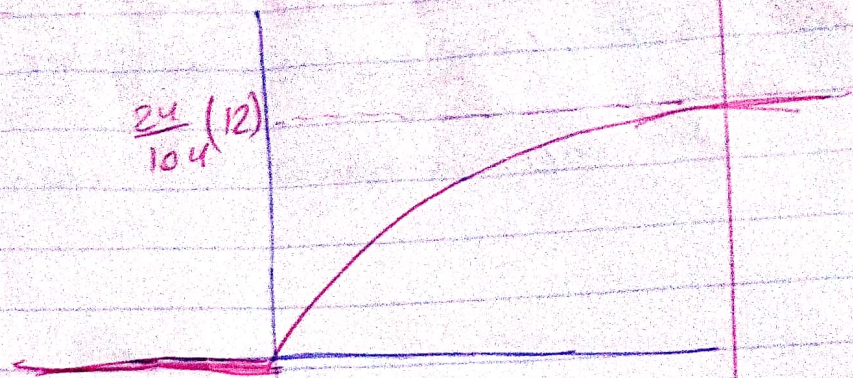بسطح R_{eq} من طرف R_{th} بعد ما قلنا ان $R_{eq} = 24/1180 = \dots$
 $T = \frac{L}{R_{eq}}$





Ex

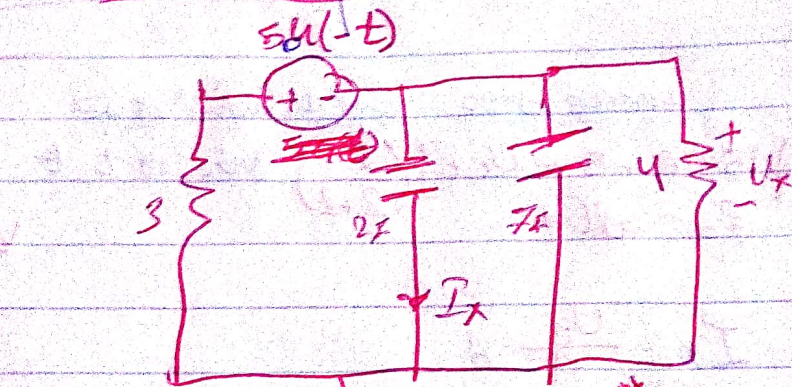
$$\frac{1}{60} = \frac{1}{50} + \frac{1}{40}$$



~~t > 0~~ ~~t < 0~~

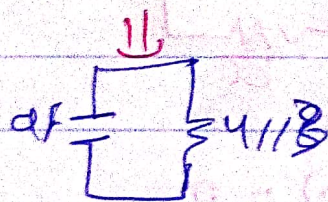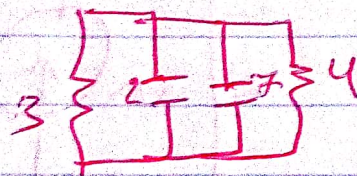


$$I_x = V_c(t) e^{-t/25}$$

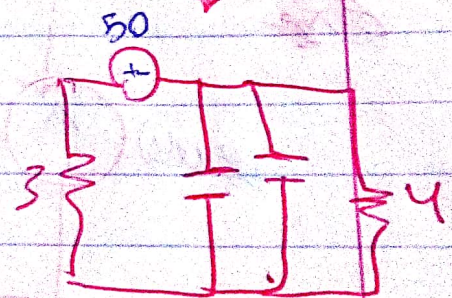

Source free
RC ckt


$$V_c(t) = V_c(0) e^{-t/\tau}$$

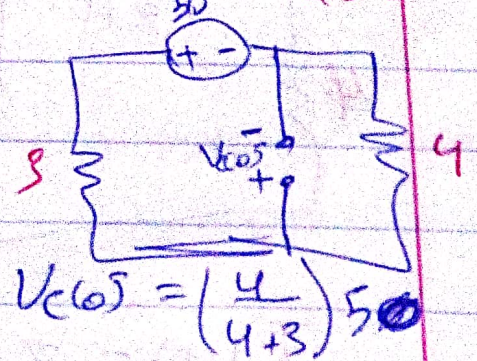

$$V_c(0) = \left(\frac{4}{4+3} \right) 50$$

$$\tau = RC = (3000) \cdot 4$$

Source free RLC ckt

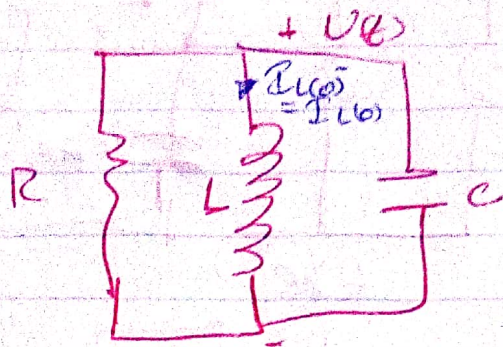

1st & 2nd order

$$U(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$U(0) = A_1 + A_2 \quad \text{--- (1)}$$

من الكولاج $U_c(\infty) = U_c(0)$

$$I_L = \frac{1}{L} \int_{-\infty}^t U(t) dt \Rightarrow I_L(t) = \frac{1}{L} \left[\frac{A_1 e^{s_1 t}}{s_1} + \frac{A_2 e^{s_2 t}}{s_2} \right]_{-\infty}^t$$

$$= \frac{1}{L} \left[\frac{A_1 e^{s_1 t}}{s_1} + \frac{A_2 e^{s_2 t}}{s_2} \right] \Rightarrow I_L(0) = \frac{1}{L} \left(\frac{A_1}{s_1} + \frac{A_2}{s_2} \right) \quad \text{--- (2)}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega^2}$$

$$U(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\alpha = \frac{1}{2Rc}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

Case I $\alpha > \omega$ OVERDAMPED s_1, s_2 (Real)

Case II $\alpha = \omega$ $s = s_1 = s_2 = -\alpha$ $\left\{ s_1 = \dots, s_2 = \dots \right\}$

$U(t) = A(e^{st})$ Critical Damped

Case III $\alpha < \omega$
under DAMPED

$$s_1 = -\alpha + j\sqrt{\omega^2 - \alpha^2}$$



$$s_2 = -\alpha - j\sqrt{\omega^2 - \alpha^2}$$

$$s_1 = -\alpha + j\omega_d$$



$$s_2 = -\alpha - j\omega_d \quad \omega_d = \sqrt{\omega^2 - \alpha^2} \text{ (Real)}$$

$$i = \sqrt{-1}$$
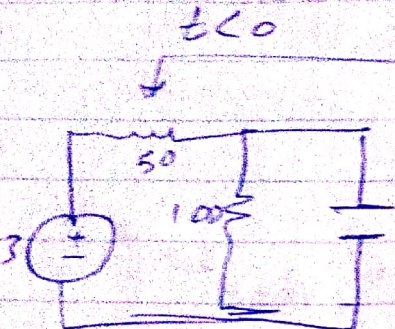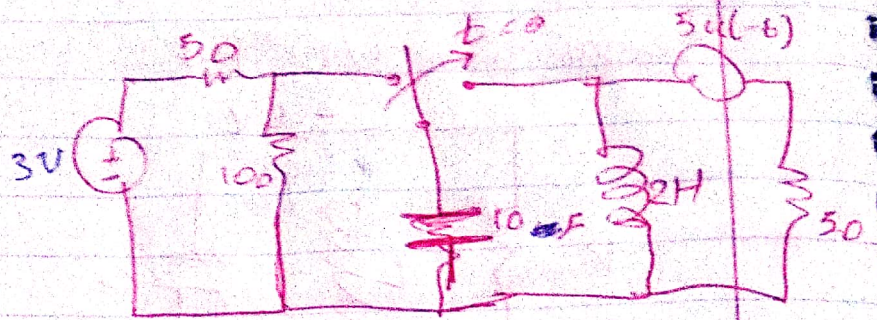
$$U(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$


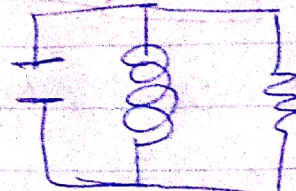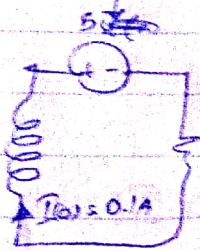
$$U_0 = \left(\frac{100}{150} \right) 3$$




$$\alpha = \frac{1}{R \times 50 \times 10} = \frac{1}{1000} = 0.001$$

$$\omega = \frac{1}{\sqrt{2 \times 10}} = \frac{1}{\sqrt{20}} \approx 0.22$$

$$U_0 = A_1 \cos \omega t + A_2 \sin \omega t$$

$U_0 = A_1$
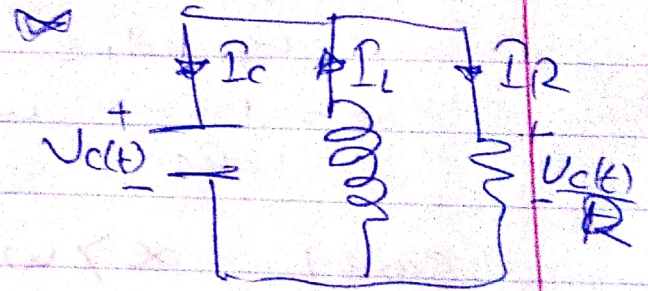
$$U(t) = e^{-\alpha t} [A_1 \cos \omega t + A_2 \sin \omega t]$$



$$I_C = C \frac{dU(t)}{dt}$$

$$KCL: I_C + I_R = I_L$$

THE END