



THE HASHMITE UNIVERSITY
ELECTRICAL ENGINEERING DEPARTMENT
ELECTRICAL MACHINES LAP

LAP REPORT # 6
DC-Shunt Excited Generator

Instructor :Dr. Mohamed Al-Wedyan

Lap supervisor : Eng.Majid Al - Briqi

Bahaa Ishaq 833150

"Mohammad Baraa" Hamawi 830677

Akram Al-Serrawi 836658

Ahmad Jamel Zahran 730255

Musabb Zyood


Objectives :

The objective of this experiment is determine both the no load characteristics and the full load characteristics of the DC-Shunt Excited Generator and to understand the external voltage characteristics and control characteristics.

Theoretical Background :

In the shunt excited generator the field circuit is directly connected across the armature circuit, an initial voltage is a result from residual flux within the core of the generator.

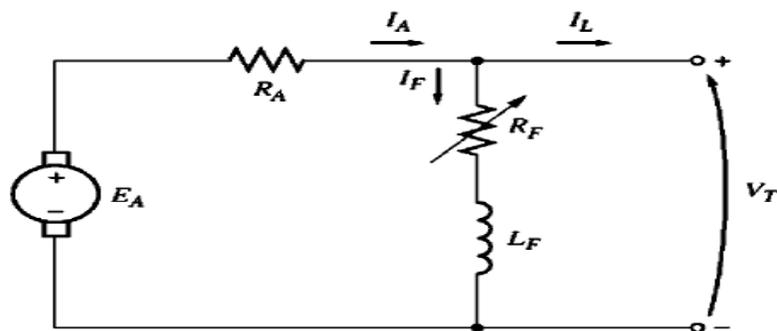The equivalent circuit of the generator is shown next:



$$\begin{aligned} I_A &= I_F + I_L \\ V_T &= E_A - I_A R_A \\ I_F &= \frac{V_T}{R_F} \end{aligned}$$

In this circuit the current I_f depends on the terminal voltage, and as the load decreases (i.e. load resistance decreases) the field current also decreases and the internal generated voltage decreases which will result a further drop in terminal voltage , the reasons for the decrease of the terminal voltage as the load increases are summarized :

- The drop voltage across the armature resistance.
- Armature reaction will reduce the effective flux that will affect the internal generated voltage.
- E_a will be less due to the previous reasons and the terminal will voltage will decrease further.

There are two ways to control the voltage of a shunt generator:

- 1. Change the speed of rotation.*
- 2. Change the resistance of the circuit which will change the field current.*

If a shunt generator is started and no voltage builds up, there are three reasons for this problem, the reasons and solutions are :

- There may be no residual flux in the core, the solution is simply to connect external DC source across the field circuit so it will produce a residual flux in the core, and this process is called “Flushing”.*
- The direction of rotation is reversed or the connection of the field is reversed, flux will produce E_a and E_a will produce flux in opposite direction to residual flux and no voltage build up will result.*
- Field resistance may be too large, and voltage build up will not occur because steady state is at residual flux level, the solution is to simply decrease field resistance.*

Equipments :

We used a motor as prime mover , and a set of millimeters to measure currents and voltages a variable load , a torque measuring unit to measure the speed of the prime mover and of course the DC shunt excited generator .

Procedure :

1.The No load characteristics :

We first noted the rating plate and saw the values that we should not exceed in our experiment , then we used the practical diagram to connect the generator , we used torque measuring unit to measure the speed of the prime mover , this speed had to be constant in our experiment , then we used the variable resistance R_f (rheostat) to control the field current , and we took measurements on the internal terminal voltage of the generator we set the speed of the prime mover to 1200 rpm and we started to increase the rheostat until we obtained zero and measured the terminal voltage, it was 12 V , this voltage is due to residual flux , then we started to decrease the rheostat (i.e. increase I_f) and take measurements of E_a as shown in the table:

1200 RPM								
Increasing I_f								
I_f	0	.1	.2	.3	.4	.5	.6	.7
E_a	10	63	106	127	139	147	156	160

The we started increasing the rheostat (i.e. decreasing I_f) and take measurements of E_a as shown in the table:

1200 RPM								
decreasing I_f								
I_f	0	.1	.2	.3	.4	.5	.6	.7
E_a	10	63	110	130	163	151	156	160


We repeated this process for 1400 RPM:

1400 RPM								
Increasing I_f								
I_f	0	.1	.2	.3	.4	.5	.6	.7
E_a	12	74	125	148	164	174	181	190

1400 RPM								
decreasing I_f								
I_f	0	.1	.2	.3	.4	.5	.6	.7
E_a	12	74	126	153	165	176	185	190

Questions and Answers for the No load characteristics:

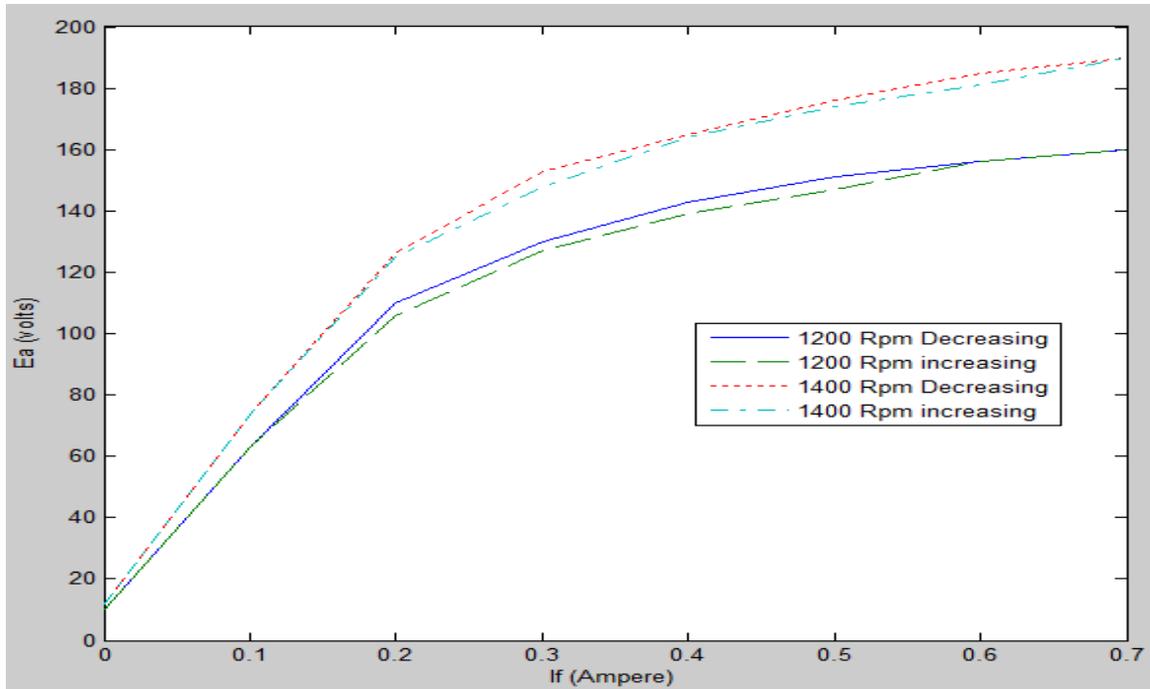1. Draw the No load characteristics for increasing and decreasing I_f on (x) axis at 1400 RPM and 1200 RPM on the same graph.




2.The load characteristics :

Now we adjusted the motor to 1400 RPM and maintained this value through the experiment, and we adjusted the rheostat until we had an excitation current of .8 Ampere , then we connected the load (the load was adjusted at a very high resistance when we connected it , so it doesn't get over heated because of the high current) and took measurements of I_a , V_t , and I_L as shown in the table :

I_m	.8	.71	.69	.69
I_L	0	2	4	6
V_t	191	181	178	172

Questions and Answers For the load characteristics:

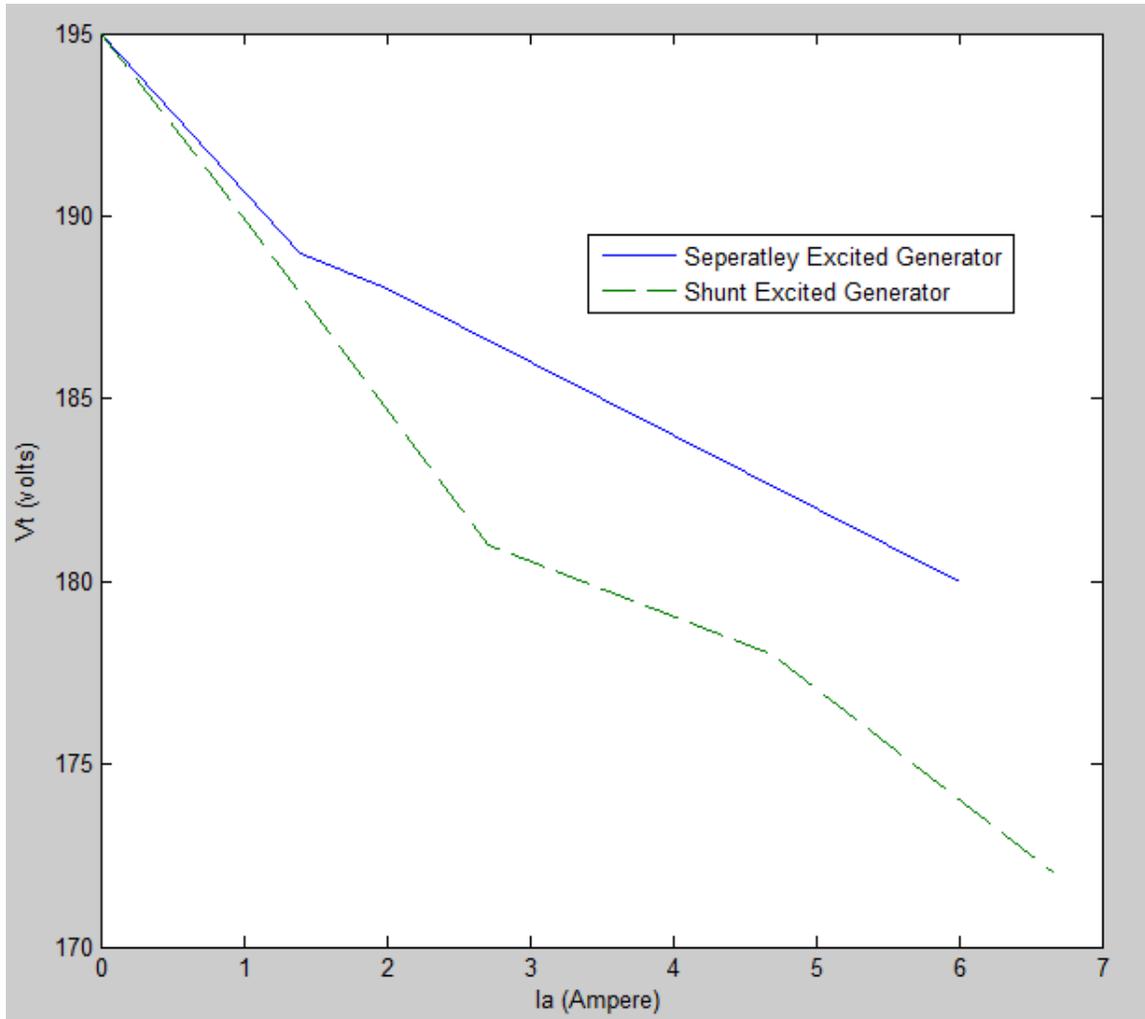1. Draw the external voltage characteristics separately and shunt excitation in the same graph with I_a on (x) axis ?



(Note : lowest Point on the (y) axis is 170 for accuracy)

2. Why does V_t decrease with increase I_a ?

Because of the drop voltage over the internal resistance (R_a) of mathematically :

$$V_t = E_a - I_a * R_a .$$

3. Why does V_t decrease more with shunt than with separately excited ?

In the Shunt DC Generator when V_t decreases, the field current in the machine decreases with it. This causes the flux in the machine to decrease, decreasing EA. Decreasing EA causes a further decrease in the terminal voltage $V_t = EA - I_a R_a$ (E_a is lowered) .

the voltage drop-off is steeper than just the $I_a R_a$ drop in a separately excited generator. In other words, the voltage regulation of this generator is worse than the voltage regulation of the separately excited generator .

4. Why does the generator not take up voltage in measurement if the field is wrongly connected?

the residual flux will produce an internal generated voltage EA, The voltage EA produces a field current which produces a flux opposing the residual flux , in other words residual flux decreases and the generator doesn't build up voltage .

The solution is to reverse connection.

Conclusions :

1. We learned how to connect the prime mover to the shunt excited generator and how loads and millimeters are connected and how to take measurements on this generator .

2. we used different values for the excitation current to obtain different values of terminal voltage , and from plotting these values we have been able to obtain the magnetization curve .

3. We saw how loads are connected to the generator , and how changing the load would change the armature current .

4. We learned how to control voltage obtained from the generator.