




تلخيص منطق رقمي ميكاترونكس

للطالب المبدع
محمود المجدلاني

إرادة - ثقة - تغيير

Numbers system

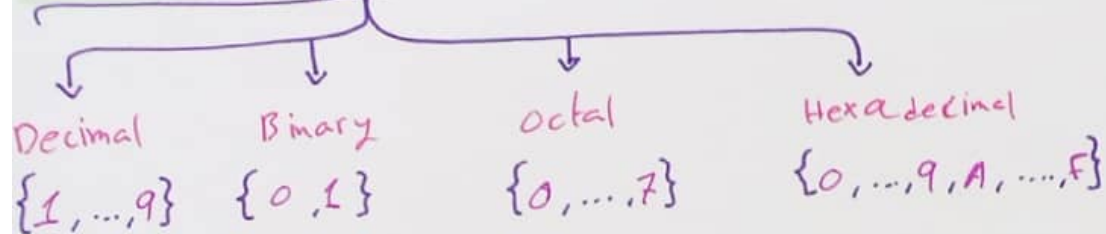

Conversions between systems

$\diamond$ Decimal $\xrightarrow[\text{* Base}]{\div \text{Base}}$ Binary
 $\xrightarrow[\text{* Base}]{\div \text{Base}}$ Octal
 $\xrightarrow[\text{* Base}]{\div \text{Base}}$ Hexa.

$\downarrow$ fraction
 $\uparrow$ Integer

$\diamond$ Octal $\Rightarrow$ Binary $\Rightarrow$ Hexa

BCD	DECIMAL
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9

BINARY	OCTAL
000	0
001	1
010	2
011	3
100	4
101	5
110	6
111	7

BINARY	HEXA
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	B
1100	C
1101	D
1110	E
1111	F

1st Complement

$1 \xrightarrow{\text{NOT}} 0$
 $0 \xrightarrow{\text{NOT}} 1$

فقط حول من

2nd complement

2nd compl. = 1st compl. + 1

GRAY	DECIMAL
0000	0
0001	1
0011	2
0010	3
0110	4
0111	5
0101	6
0100	7
1100	8
1101	9
1111	10
1110	11
1010	12
1011	13
1001	14
1000	15

$$\begin{array}{r} 0_{(2)} + \\ 0_{(2)} + \\ \hline 0_{(2)} \end{array}$$

$$\begin{array}{r} 0_{(2)} + \\ 1_{(2)} + \\ \hline 1_{(2)} \end{array}$$

$$\begin{array}{r} 1_{(2)} + \\ 1_{(2)} + \\ \hline 10_{(2)} \end{array}$$

$$\begin{array}{r} 1_{(2)} + \\ 1_{(2)} + \\ \hline 11_{(2)} \end{array}$$

$$\begin{array}{r} 1_{(2)} + \\ 1_{(2)} + \\ \hline 11_{(2)} \end{array}$$

Basic Binary Gate

* NOT Gate $\Rightarrow$ 1st complement

OR

$\oplus$



A	B	F
0	0	0
1	0	1
0	1	1
1	1	1

AND

$\odot$



A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

NOT

1st compl.



A	F
0	1
1	0

$F = \bar{A}$

Buffer

No change



A	F
0	0
1	1

$F = A$

بختب ال 1

بختب ال 0

بختب ال 0


بختب ال 1

بختب ال 0

بختب ال 1

$$X + \bar{X} = 1 \rightarrow X + 0 = X \rightarrow X + 1 = 1$$
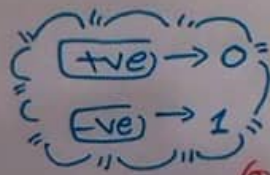
$$X \cdot \bar{X} = 0 \rightarrow X \cdot X \cdot X \cdot X = X$$



من بعد العدد 8

Number representation

significal magnitude

1st complement representation

2nd complement representation

+ve

as is

-ve


1st compl.

+ve







as is

-ve

2nd compl.

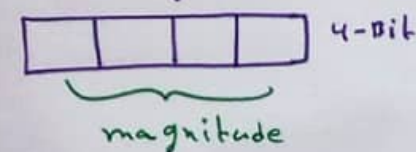

Logical Gate

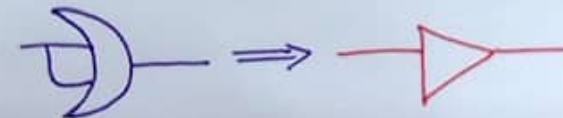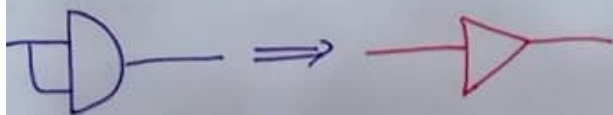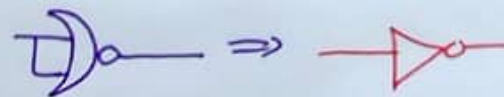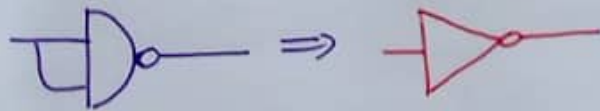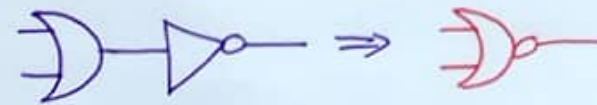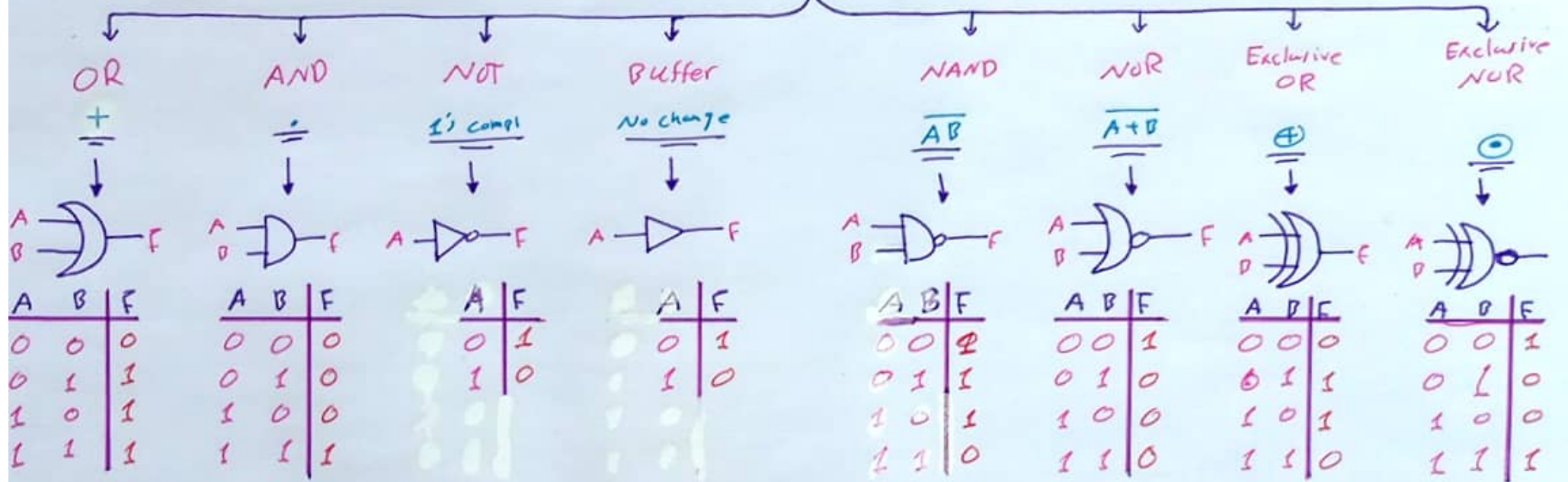

Range

sign-magnitude
1st compl. rep. $\rightarrow -(2^{n-1}-1) : +(2^{n-1}-1)$

2nd compl. rep. $\rightarrow -(2^{n-1}) : (2^{n-1}-1)$

Bits	1 st compl. sign-mag	2 nd compl.
4	-7 : +7	-8 : +7
8	-127 : +127	-128 : +127

* Bit $\rightarrow$ for Binary Digit

()
AND $\doteq$
OR $\pm$

$$2^0 \rightarrow 1$$

$$2^1 \rightarrow 2$$

$$2^2 \rightarrow 8$$

$$2^3 \rightarrow 16$$

$$2^4 \rightarrow 32$$

$$2^5 \rightarrow 64$$

$$2^7 \rightarrow 128$$

$$2^8 \rightarrow 256$$

$$2^9 \rightarrow 512$$




$$2^{10} \rightarrow 1024$$

$$k \rightarrow 10^3 \rightarrow 2^{10} = 1024$$

$$M \rightarrow 10^6 \rightarrow 2^{20} = (1024)^2$$

$$G \rightarrow 10^9 \rightarrow 2^{30} = (1024)^3$$

NUMBER	X	Y	Z	MIN TERMS		MAX TERMS	
				TERM	DESIGNATION	TERM	DESIGNATION
0	0	0	0	$\bar{x} \cdot \bar{y} \cdot \bar{z}$	m_0	$x + y + z$	M_0
1	0	0	1	$\bar{x} \cdot \bar{y} \cdot z$	m_1	$x + y + \bar{z}$	M_1
2	0	1	0	$\bar{x} \cdot y \cdot \bar{z}$	m_2	$x + \bar{y} + z$	M_2
3	0	1	1	$\bar{x} \cdot y \cdot z$	m_3	$x + \bar{y} + \bar{z}$	M_3
4	1	0	0	$x \cdot \bar{y} \cdot \bar{z}$	m_4	$\bar{x} + y + z$	M_4
5	1	0	1	$x \cdot \bar{y} \cdot z$	m_5	$\bar{x} + y + \bar{z}$	M_5
6	1	1	0	$x \cdot y \cdot \bar{z}$	m_6	$\bar{x} + \bar{y} + z$	M_6
7	1	1	1	$x \cdot y \cdot z$	m_7	$\bar{x} + \bar{y} + \bar{z}$	M_7

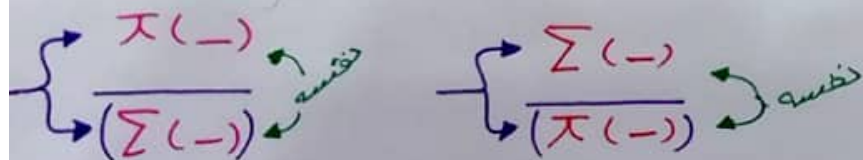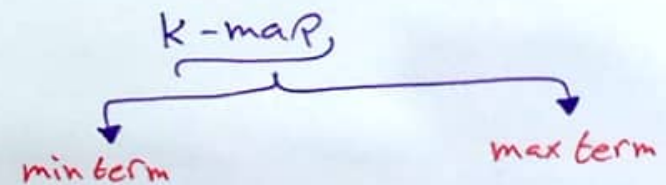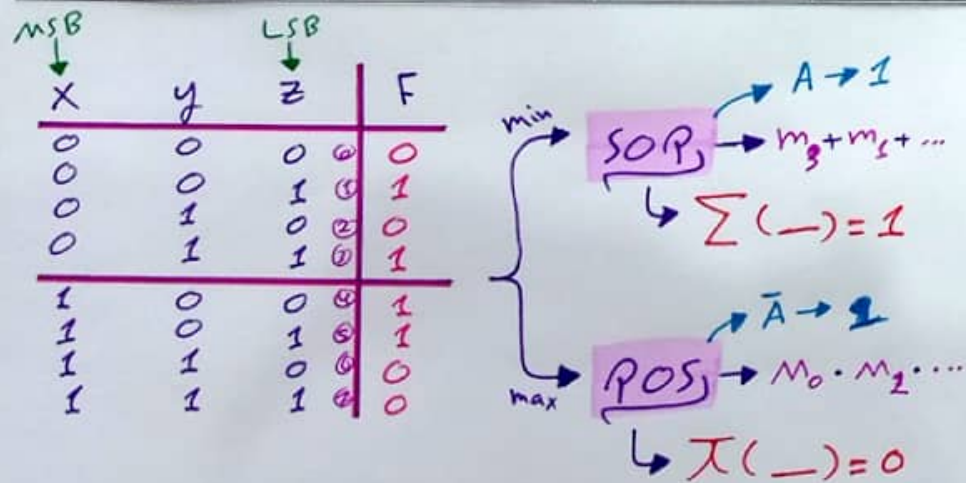

k-map

2-variable

B

m_0	m_1
m_2	m_3

A |

3-variable

اس عنوان

B

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

A |

C

4-variable

کرے

C

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

A |

D

5-variable

کرتے بقیہ
بعض

D

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

E

A

D

D

m_{16}	m_{17}	m_{19}	m_{18}
m_{20}	m_{21}	m_{23}	m_{22}
m_{28}	m_{29}	m_{31}	m_{30}
m_{24}	m_{25}	m_{26}	m_{27}

E

Rule for minimization

1) cover all ones using Σ 's
 → circles and non-zero ←

2) circles are 1, 2, 4, 8 → Σ 's

3) minimize → the number of circles

4) maximize → the size of each circle

$$\overline{(A \odot B)} = A \oplus B \quad \diamond \quad \overline{(A \oplus B)} = A \odot B$$

* بظنر أحده على الآخر جينا سيني من
 k-map لنظمت { minterm, max term }

ولكن وأنا فاحد ربي السؤال على أنو أحده
 له بحله على الذي فيها دوائر أفك أو انقطه مع أسهل رسيه

* إذا كان جوجو بران kmap ← Symmetric


لـ يعرف انه فيه
 XOR
 XAOR

How to Design (1, 2, 3, ...) Bit up/down or both

1) Find state table (truth table) $\begin{array}{c|c} A, B & F_1, F_2 \\ \hline 1 & 1 \end{array}$

2) find state Diagram 

3) find the function By k-map

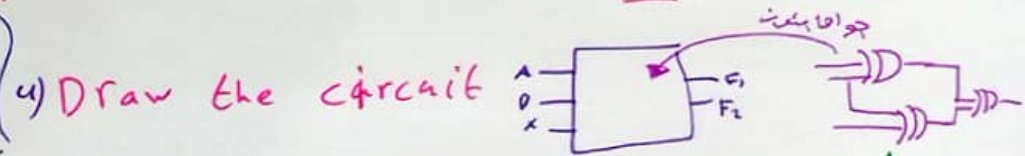


* If I have 2 variable → 2 output F_1, F_2 ← أرسو حيزون

3 variable → 3 output F_1, F_2, F_3
 variable
 → (A, B, C, D)
 له بدون انه


يعني عدد المتغيرات = عدد output

* XOR ← 8 يقابل 2 في 2 map

Half Adder (H.A)

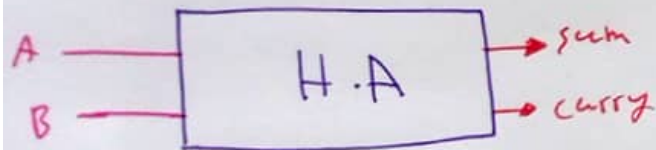


Full Adder (F.A)


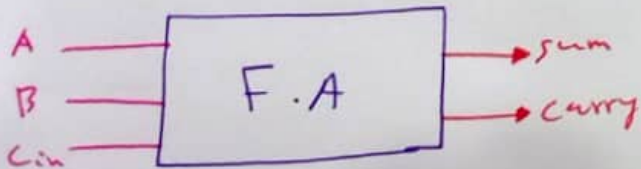


4-Bit Adder


4-Bit Adder subtractor

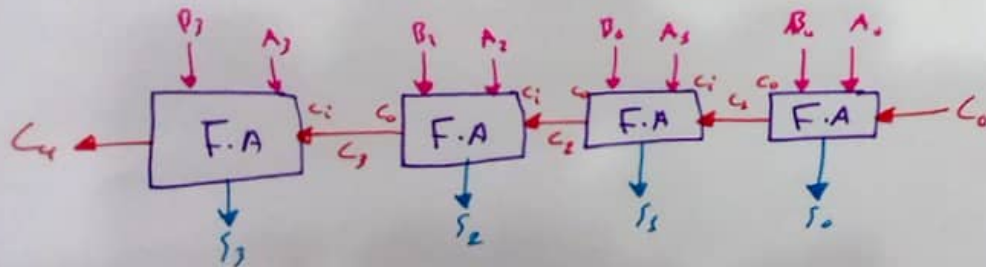

4-Bit Adder

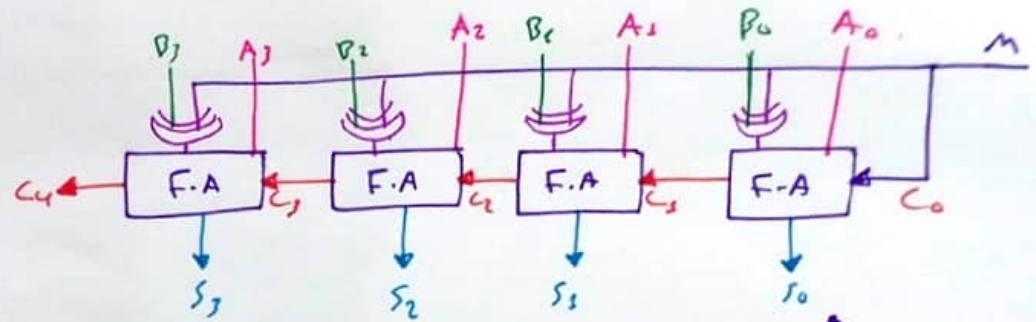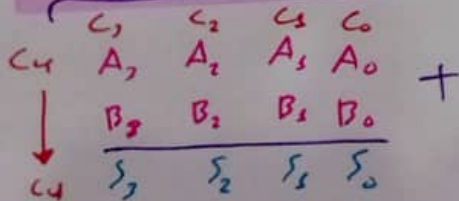

4-Bit Adder subtractor

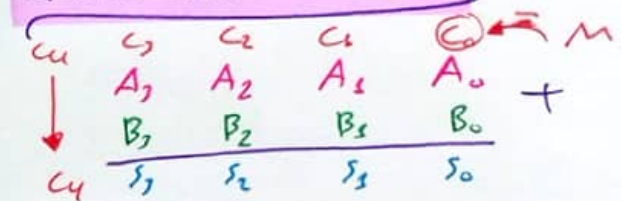

$$* B \oplus M \begin{cases} B \oplus 0 \rightarrow B \\ B \oplus 1 \rightarrow \bar{B} \end{cases}$$



* $M=0$

$\rightarrow A+B$ Addition.



* $M=1$

$\rightarrow A + \bar{B} + 1$ subtractor.
2nd compl.



Decoder

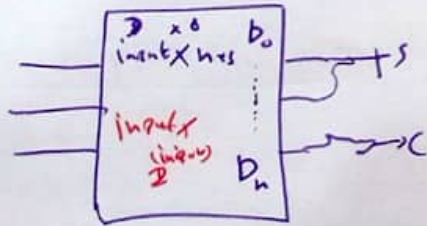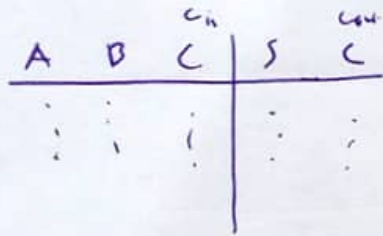

Multiplexer (mux)

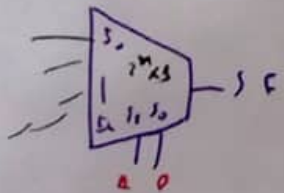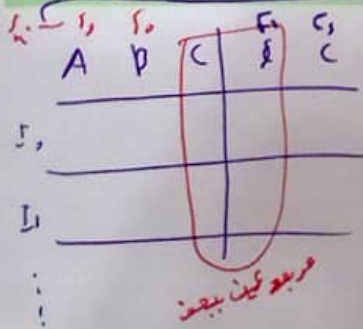

	Input	selection lines	output
2x1	2	1	1
4x1	4	2	1
8x1	8	3	1
16x1	16	4	1

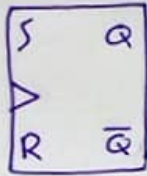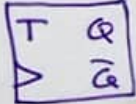Name	Symbol	Truth Table	chara. equ.	excitation table																																			
SR f/f		<table border="1"> <thead> <tr> <th>S</th> <th>R</th> <th>Q⁺</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>Q</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>X</td></tr> </tbody> </table>	S	R	Q ⁺	0	0	Q	0	1	0	1	0	1	1	1	X	_____	_____																				
S	R	Q ⁺																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	X																																					
JK f/f		<table border="1"> <thead> <tr> <th>J</th> <th>K</th> <th>Q⁺</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>Q</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>$\bar{Q}$</td></tr> </tbody> </table>	J	K	Q ⁺	0	0	Q	0	1	0	1	0	1	1	1	$\bar{Q}$	$Q^+ = J\bar{Q} + \bar{K}Q$	<table border="1"> <thead> <tr> <th>Q</th> <th>Q⁺</th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>X</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>X</td></tr> <tr><td>1</td><td>0</td><td>X</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>X</td><td>0</td></tr> </tbody> </table>	Q	Q ⁺	J	K	0	0	0	X	0	1	1	X	1	0	X	1	1	1	X	0
J	K	Q ⁺																																					
0	0	Q																																					
0	1	0																																					
1	0	1																																					
1	1	$\bar{Q}$																																					
Q	Q ⁺	J	K																																				
0	0	0	X																																				
0	1	1	X																																				
1	0	X	1																																				
1	1	X	0																																				
T f/f		<table border="1"> <thead> <tr> <th>T</th> <th>Q⁺</th> </tr> </thead> <tbody> <tr><td>0</td><td>Q</td></tr> <tr><td>1</td><td>$\bar{Q}$</td></tr> </tbody> </table>	T	Q ⁺	0	Q	1	$\bar{Q}$	$Q^+ = T \oplus Q$	<table border="1"> <thead> <tr> <th>Q</th> <th>Q⁺</th> <th>T</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	Q	Q ⁺	T	0	0	0	0	1	1	1	0	1	1	1	0														
T	Q ⁺																																						
0	Q																																						
1	$\bar{Q}$																																						
Q	Q ⁺	T																																					
0	0	0																																					
0	1	1																																					
1	0	1																																					
1	1	0																																					
D f/f		<table border="1"> <thead> <tr> <th>D</th> <th>Q⁺</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	D	Q ⁺	0	0	1	1	$Q^+ = D$	<table border="1"> <thead> <tr> <th>Q</th> <th>Q⁺</th> <th>D</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	Q	Q ⁺	D	0	0	0	0	1	1	1	0	0	1	1	1														
D	Q ⁺																																						
0	0																																						
1	1																																						
Q	Q ⁺	D																																					
0	0	0																																					
0	1	1																																					
1	0	0																																					
1	1	1																																					

Region	V _{BE}	V _{CE}	current relationship
cut off	< 0.6	0.1	$I_B = I_C = 0$
Active	0.6 - 0.7	> 0.7	$I_C = h_{FE} I_B$
saturation	0.7 - 0.8	0.2	$I_B \geq \frac{I_C}{h_{FE}}$