

تقدم لجنة EICoM الاكاديمية

دفتر لمادة:

المنطق الرقمي

من شرح:



د. انس المجالي

جزيل الشكر للطالب:

نمر عودة



- Analog
- Digital
- Number Systems

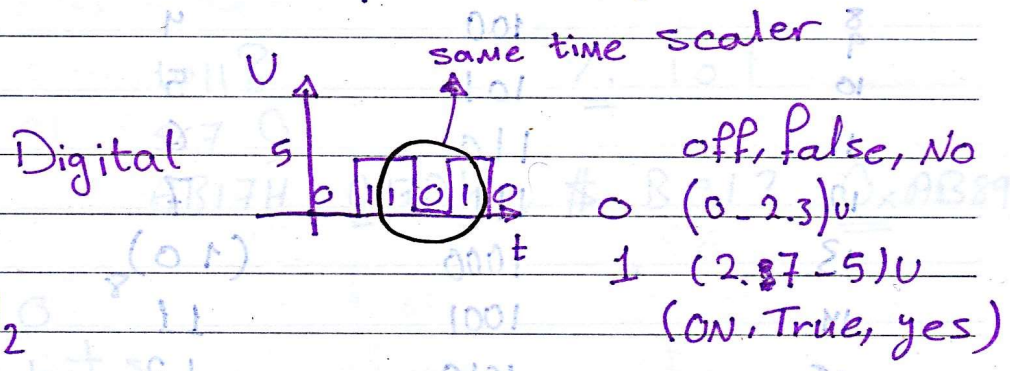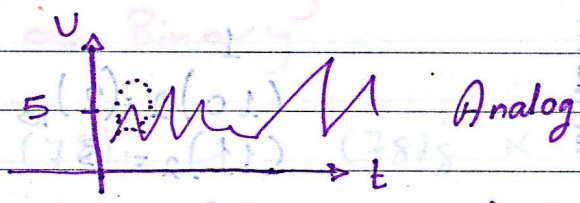

$(5)_{10} = (101)_2$

ADC → Analog to Digital Converter
 DAC → Digital to Analog Converter

Number Systems:

1. Decimal	2. Binary	3. Octal	4. Hexadecimal
0-9	0-1	0-7	0-9, A-F ₁₀₋₁₅
base = 10	base = 2	base = 8	base = 16

Decimal Binary Octal hexadecimal

Digital logic

PAGE 2


DATE 29.9.2015
Tuesday

Decimal Binary Octal hexadecimal

0	0	0	0
1	1	1	1
2	$(10)_2 = (2)_{10}$	2	2
3	$(11)_2 = 3$	3	3
4	100	4	4
5	101	5	5
6	110	6	6
7	111	7	7
8	1000	$(10)_8$	8
9	1001	11	9
10	1010	12	A
11	1011	13	B
12	1100	14	C
13	1101	15	D
14	⊙ 1110	16	E
15	⋮	17	$(F)_{16} = (15)_{10}$
16	⋮	$(20)_8 = (16)_{10}$	$(10)_{16} = 16$
17	⋮		عبر مثال في

عبر مثال في

77
↓ Octal
100

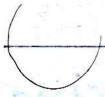

Thursday

class 2

Basic Definition

conversion Decimal \Leftrightarrow any systemconversion Octal \Leftrightarrow Binary
hex \Leftrightarrow Binarye.g. $(1011)_2 \leftarrow (78)_{16} \leftarrow (78)_8 \times$

B (Binary)

1011B

= 101

Q (Octal)

567Q

H (Hexa)

AB17H, 017Dh, #BC12, 0xAB89

* Bit = 1 0

Nibble = 4 bits

Byte = 8 bits

word = 16 bits = 2 byte

 $2^{10} = 1 \text{ Kilo} = 1024$ $2^{20} = 1 \text{ Mega} = 1024 \times 1024$ $2^{30} = 1 \text{ Giga}$ $2^{40} = 1 \text{ Tera}$

* LSB = Least Significant Bit

MSB = Most Significant Bit

eg: $(10110)_2$
MSB \leftarrow \rightarrow LSB $(9101)_{10}$
MSB \leftarrow \rightarrow LSB

Class 2

Thursday

Binary }
Octal } → Decimal // weighted sum
hexa }

e.g. $(195)_{10}$

10^2	10^1	10^0	weight	= $10^0 * 5 + 10^1 * 9 + 1 * 10^2$
1	9	5	Factor	

b = 10

e.g. $(167)_8 \Rightarrow b = 8$

8^2	8^1	8^0	weight
1	6	7	Factor

$$7 * 8^0 + 6 * 8^1 + 1 * 8^2 = 7 + 48 + 64 = (119)_{10}$$

e.g. $(150)_6 \Rightarrow$ Decimal

$$6^0 * 0 + 5 * 6^1 + 1 * 6^2$$

$$= 30 + 36 = (66)_{10}$$

e.g. $(FC7)_{16} \quad b = 16$

$$= 7 * 16^0 + 12 * 16^1 + 15 * 16^2 = (4039)_{10}$$

\downarrow \downarrow
 C F

e.g. $(17.52)_8$

Radix Pt

$$= 1 * 8^1 + 7 * 8^0 + 5 * 8^{-1} + 2 * 8^{-2}$$

$$= (15.65625)_{10}$$

Class 2

e.g. $(101.01)_2 \Rightarrow$ Decimal

$$1 * 2^2 + 0 * 2^1 + 1 * 2^0 + 0 * 2^{-1} + 1 * 2^{-2}$$

$$= 4 + 0 + 1 + 0 + \frac{1}{4} = 5 + \frac{1}{4} = (5.25)_{10}$$

Decimal \rightarrow $\left\{ \begin{array}{l} \text{Binary} \\ \text{hex} \\ \text{Octal} \end{array} \right.$

① Integer: ① Divide by the base (Repeated)
② look for the remainder

② Fraction: ① multiplication by the base (Repeated)
② look for the integer part

e.g. $(8)_{10} \Rightarrow$ Binary

	Result	Reminder	
8 / 2	4	0	LSB
4 / 2	2	0	
2 / 2	1	0	
1 / 2	0	1	MSB

$$(8)_{10} = (1000)_2$$

Class 2

eg (80)₁₀ → Octal

base 8

$$80 / 8 = 10 \rightarrow 0 \text{ LSB}$$

$$10 / 8 = 1 \rightarrow 2$$

$$1 / 8 = 0 \rightarrow 1 \text{ MSB}$$

$$(80)_{10} = (120)_8$$

eg (500)₁₀ → hex

$$500 / 16 = 31 \text{ LSB}$$

$$31 / 16 = 1 \text{ 15}$$

$$1 / 16 = 0 \text{ 1 MSB}$$

$$(1F4)_{16}$$

eg (50)₁₀ → binary

$$50 / 2 \rightarrow 25 \quad 0$$

$$25 / 2 \rightarrow 12 \quad 1$$

$$12 / 2 \rightarrow 6 \quad 0$$

$$6 / 2 \rightarrow 3 \quad 0$$

$$3 / 2 \rightarrow 1 \quad 1$$

$$1 / 2 \rightarrow 0 \quad 1$$

$$(110010)_2$$

Class 3

Conversion → Fraction - Decimal → binary
hex
Octal (8) = (2)

Sunday

→ On the Fly Conversion

→ Octal ⇔ binary

hex ⇔ binary

Octal ⇔ hex

Ex (0.3)₁₀ → Binary

Sol →

0.3 * 2 = 0.6

i.p

0 → MSB

* 0.6 * 2 = 1.2

1

0.2 * 2 = 0.4

0

0.4 * 2 = 0.8

0

0.8 * 2 = 1.6

1

* 0.6 * 2 = 1.2

1

→ LSB

(0.3)₁₀ = (0.010011)₂

e.g (0.3)₁₀ ⇒ Octal

5 digits

b = 8

i.p

0.3 * 8 = 2.4

2

→ MSB

0.4 * 8 = 3.2

3

0.2 * 8 = 1.6

1

0.6 * 8 = 4.8

4

0.8 * 8 = 6.4

6

→ LSB

(0.3)₁₀ = (0.23146)₈

(10011.11001)₂ = (18.01)₁₀

Class 3

Sunday

e.g. $(0.3)_{10} \Rightarrow$ hex $b=16$

$$(0.3)_{10} = (??)_{16}$$

$$0.3 * 16 = 4.8$$

$$0.8 * 16 = 12.8$$

$$0.8 * 16 = 12.8$$

⋮

$$(0.3)_{10} = (0.4CC\text{---})_{16}$$

e.g. $(0.75)_{10} \Rightarrow$ Binary

$$0.75 * 2 = 1.5 \rightarrow \text{MSB}$$

$$0.5 * 2 = 1.0$$

$$0.0 * 2 = 0.0 \rightarrow \text{LSB}$$

$$(0.75)_{10} = (0.11)_2$$

e.g. $(19.81)_{10} \Rightarrow$ binary $b=2$

Integer part

$$19 / 2 = 9 \rightarrow \text{MSB}$$

$$9 / 2 = 4$$

$$4 / 2 = 2$$

$$2 / 2 = 1$$

$$1 / 2 = 0.1 \rightarrow \text{LSB}$$

Fraction part

$$= (10011)_2$$

$$(0.81) * 2 = 1.62 \rightarrow \text{MSB}$$

$$0.62 * 2 = 1.24$$

$$0.24 * 2 = 0.48$$

$$0.48 * 2 = 0.96$$

$$0.96 * 2 = 1.92 \rightarrow \text{LSB}$$

Related to the radix pt.

$$(19.81)_{10} = (10011.11001)_2$$

CLASS 3

Decimal \rightarrow Binary On the Fly

$(8)_{10} \rightarrow$

2^3	2^2	2^1	2^0
1	0	0	0

$(4)_{10} \rightarrow$

2^2	2^1	2^0
1	0	0

$(2)_{10} \rightarrow$

2^1	2^0
1	0

e.g. $(9)_{10} \rightarrow (1001)_2$
 $8 + 1 = 9$

On the Fly \rightarrow look for the greatest or equal digit \Leftrightarrow (equal or less than the given number)

e.g. $(23)_{10}$

2^4	2^3	2^2	2^1	2^0
16	8	4	2	1
1	0	1	1	1

$(23)_{10} = (10111)_2$

e.g. $(37)_{10}$

2^5	2^4	2^3	2^2	2^1	2^0
32	16	8	4	2	1
1	0	0	1	0	1

$(37)_{10} = (100101)_2$

Class 3

Sunday

Octal \leftrightarrow Binary

① Binary \rightarrow Octal

- start from the radix pt.

- divide the binary number to groups of 3

- (convert each group)

e.g. $001 \mid 101 \mid 1001 \mid 110$
 1 5 5 6

$(1101101.110)_2 = (155.6)_8$

e.g.

octal binary

0 000

1 001

2 010

3 011

4 100

5 101

6 110

7 111

$2^3 = 8$

② Octal \rightarrow Binary

e.g. $(517.2)_8 \rightarrow$ binary

divide to groups of 3

sol $\rightarrow (101001111.010)_2$

$(19.81)_{10} = (10011.11001)_2$

Class 3

hex \Leftrightarrow BinarySame method
but 4 groups

Sunday

hex	binary
0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1
A	1 0 1 0
B	1 0 1 1
C	1 1 0 0
D	1 1 0 1
E	1 1 1 0
F	1 1 1 1

Class 4

hex \leftrightarrow binary
Octal \leftrightarrow hex

Tuesday

Eg $(F701.3)_{16} \rightarrow$ Binary

Sol $(1111011100000001.0011)_2$

eg $(0010111011011100.11011000)_2$ hex

$= (176E.D8)$

Octal \leftrightarrow hex passing binary
 \downarrow
 binary

eg $(F701.3)_{16} \rightarrow$ Octal

Sol $\rightarrow (1111011100000001.0011)_2$

to Octal $\rightarrow 00111101100000001.001100$

$= (173401.14)_8$

e.g $(732.5)_8 \rightarrow$ hex

Sol \rightarrow to binary $= (111011010.101)_2$

to hex $\rightarrow 000111011010.1010$

$= (1DA.A)_{16}$

Class 4

Arithmetic Operation,

"Tuesday"

e.g

operands

8 1 0 0 0

9 1 0 0 1

result

| | | |

Must
be the same
number of blocks.

* Finite precision

Numbers can be:

1. unsigned

2. Signed \rightarrow Magnitude \rightarrow 1's complement \rightarrow 2's Complement

Binary Codes: sequences of bits that refers to a certain values.

9 \rightarrow 1001

n: # of digits

	decimal, n=2	n=3	
# of values	100	1000	10^n
Maximum Value	99	999	$10^n - 1$
range	0-99	0-999	

Class 4


	Binary, $n=2$ $2^2 = 4$	$n=3$ $2^3 = 8$	2^n
# of values دائماً ثابت			
Max values تقريباً النظام	3	7	$2^n - 1$
Range	0-3 (0-11)	0-7	0- $(2^n - 1)$

* Signed Magnitude


One digit reserved to the sign

0 → +ve
1 → -ve] MSB


$n=4$

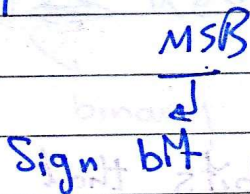

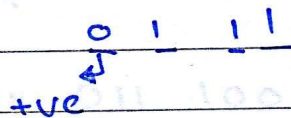
eg → $n=4$, $(7)_{10} \Rightarrow$ Signed magnitude.



$(-3)_{10} \Rightarrow$

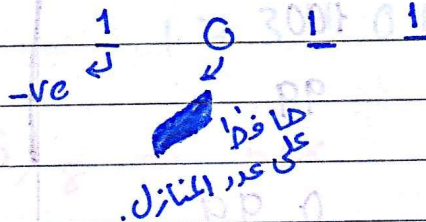

$(+1)_{10} \Rightarrow$

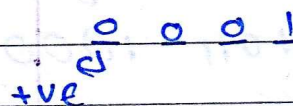

Class 4

$n=4$

+ve $\leftarrow \underline{0} \ 0 \ 0 \ 0 = +0$

-ve $\leftarrow \underline{1} \ \underline{0 \ 0 \ 0} = -0$
 \downarrow
 mag

# of values	$n=3$ $2^3=8$	$n=4$ $2^4=16$	2^n
Max	$2^2-1=3$ 0 1 1	$2^3-1=7$ 0 1 1 1	$2^{n-1}-1$
Min	$-(2^2-1)=-3$ 1 1 1	$-(2^3-1)=-7$ 1 1 1 1	$-(2^{n-1}-1)$
# of zero's	0 0 0 1 0 0	0 0 0 0 1 0 0 0	<u>2</u>

Class 5

Thursday

- unsigned

- signed mag

- signed 1's complement

2's

complement

} Binary System.

1. Diminished Radix Complement:

$$B + (-B) = \underline{\underline{r^n - 1}}$$

↓

Complement
of B

e.g. $n=2, r=10$
 $10^2 - 1 = \underline{\underline{99}}$

e.g. $n=2, r=10, B=51$ Radix - B
 $99 - 51 = 48$

e.g. $n=3, r=2$ Radix $010 = (2)_{10}$
 $r^n - 1 = 2^3 - 1 = 7 = (111)_2$
 $7 - 2 = \underline{\underline{5}}$

$$2 = 010$$

$$5 = \underline{101} \Rightarrow (22)$$

$$7 = 111$$

- MSB represent the sign

0 \Rightarrow +ve

1 \Rightarrow -ve

e.g) Find $(-3)_{10} \Rightarrow$ 1's complement, $n=5$

Sol +ve 00011 \Rightarrow 3

-ve 11100 \Rightarrow -3
 ← 1's complement

e.g) what is the number PP(101101) 1's complement

(010010) = 18

\therefore (101101) 1's complement = -18

* To Find 1's complement convert 1 \rightarrow 0
 0 \rightarrow 1

e.g) write +17 in 1's complement, $n=8$

00010001

e.g) write zero 1's complement $n=4$.

0000 +ve zero

1111 -ve zero

eg) Find 1's complement 10110.101

sol → (01001.010)

signed 1's complement

# of values	$n=3$ $2^3=8$	$n=4$ $2^4=16$	rule 2^n
Min	-3 → 100	-7	$-(2^{n-1}-1)$
Max	+3 → 011	+7	$+(2^{n-1}-1)$
# of zeros	000 111 <u>2</u>	2	2

Range = [Min - Max]

2's complement → $B + (-B) = r^n$
 complement of B

e.g) $n=2, r=10, 10^2=100$

e.g) $B=51, (-B)=?, n=2, r=10$

$-B=49$

MSB at least for the sign
 0 → +ve
 1 → -ve

Find 2's complement :-

- Find 1's comp. then add 1
- Start from LSB then move to the left until you find first 1, then convert the remaining.

e.g) Find 2's complement for 001101

[1] 001101 → 13

-13 ∈ 110010 ✓ 1's comp.

1+
110010
-13 → 110011
2's complement

[2] 001101

-13 in 2's

complement

e.g) 10100 Find 2's complement

[1] 10100

1+
00100
1+1=10

[2] 10100

2's complement

e.g) write 01100

e.g) write binary's complement then
that after with 1's
until you find 1

class 5

Thursday

e.g) write -5 in 2's complement, n=4

$$\begin{aligned} +5 &= 0101 \\ \underline{-5} &= 1011 \\ &\text{is complement.} \end{aligned}$$

e.g) write +7 in 2's complement, n=5

Sol \rightarrow (00111) 2's complement \neq

e.g) zero, n=4

$$\begin{array}{r} 0000 \\ 0000 \\ \hline 1111 \\ \hline 1+ \\ \hline \cancel{0000} \end{array}$$

1 zero

فوق ال Σ

CLASS 6

2's Complement, Arithmetic operation Sunday

unsigned, signed, 1's complement, 2's complement.

eg) $n=4$, 2's Complement system.

-ve $\Rightarrow 1000$ ↓

$1000 = -8$

$n=5, 10000 = -16$

$n=3, 100 = -4$

$n=2, 10 = -2$

2's complement system :

	$n=3$	$n=4$	rule
# of values	$2^3 = 8$	2^4	2^n
Min	100, = -4	1000, = -8	-2^{n-1}
Max	011, = 3	0111, = 7	$2^{n-1} - 1$
Zero's	$\frac{1}{0000}$	0000	1

$n=3 \rightarrow \# \text{ of values} = 8 \Rightarrow 2^3$

Binary Code :

↓	unsigned	signed Mag.	1's comp.	2's Comp.
0 0 0	0	+ve zero	+ve zero	0
0 0 1	1	+1	+1	1
0 1 0	2	+2	+2	2
0 1 1	3	+3	+3	3
1 0 0	4	-ve zero	-3	-4
1 0 1	5	-1	-2	-3
1 1 0	6	-2	-1	-2
1 1 1	7	-3	-ve zero	-1

class 6

Sunday

e.g) which of the following equal (11111010) is comp.

a) +5 b) -5 c) (1011) 's comp. d) (1111011) 's

e) (1000101) unsigned f) (10101) signed mag.

Sol $\rightarrow (11111010) \rightarrow (00000101) = (-5)$

Arithmetic Operation:

steps: 1) Fix size of the operands

(sign extension)

2) Perform the operation (+)

if subtraction, then convert to addition

3) Check for overflow.

if (overflow) then the result is wrong.

e.g) +5, $n=7$ unsigned
0000101 (sign extension)

e.g) 00010 1's comp, $n=8$
00000010 = +2

e.g) 1010 = -5, 1's comp, $n=8$
1111010 = -5

e.g) 10010, 2's comp, $n=8$
1110010 = -14

e.g) 0101, 2's, $n=8$
00000101

class 6

Sunday

e.g) (10110110) , Signed Mag, $n=8$

$$\begin{array}{r} \swarrow \\ 10110110 \\ \hline 10000110 \\ \hline \text{Mag} \end{array}$$

Always extend using Zero's in Signed Mag.

e.g) i's comp 01010

e.g) (5-2), $n=5$ in i's complement

$$\begin{array}{r} \text{Cin} \\ 5 + (-2) \Rightarrow (00101) \quad 5 \\ (11101) \quad (2-) \end{array}$$

Carry Out $\leftarrow 100010$

e.g)
$$\begin{array}{r} 1111 \\ + 1011 \\ \hline 11010 \end{array}$$

Carry in \Rightarrow Cin = 0/1
Carry Out \Rightarrow Cout = 0/1 } MSB

e.g)
$$\begin{array}{r} \text{Cin} \\ 011 \\ \hline 001 \end{array}$$

Cout = 0 $\leftarrow 01100$

e.g)
$$\begin{array}{r} 1000 \\ + 1000 \\ \hline \text{Cout} \leftarrow 0000 \end{array}$$

CLASS 7

Tuesday

Overflow \rightarrow Ov
 if Ov then the result is wrong.
 (Result is out of the range that can be represented by the given # of bits.)

eg) $n=3 \rightarrow$ range in 1's complement $(-3, +3)$
 $-3 - 3 = -6 \rightarrow$ Out of the range.

* Unsigned numbers Ov (Addition)

Ov if $cout = 1$

eg) $n=5, 16+8=24$

$$\begin{array}{r}
 10000 \\
 01000 \\
 \hline
 11000 \\
 \leftarrow \text{Cin} = 1
 \end{array}$$

* Signed 1's Complement
 if $Cin \neq Cout$ then Ov (result is wrong)
 else if $Cin = Cout = 1$
 then discard $Cout \rightarrow$ Add 1 to the result.

eg) Find $-5 - 7, n=5, 1's$ Complement.

$$\begin{array}{l}
 +5 \rightarrow 00101 \rightarrow 11010 \text{ (-5)} \\
 +7 \rightarrow 00111 \rightarrow 11000 \text{ (-7)}
 \end{array}$$

$$\begin{array}{r}
 11010 \\
 + 11000 \\
 \hline
 10010
 \end{array}$$

$Cin = Cout$

$$\begin{array}{r}
 10010 \\
 \times \quad 1 + \\
 \hline
 10011
 \end{array}$$

Class 7

Tuesday

e.g)
$$\begin{array}{r} 1001 \\ 1000^+ \\ \hline 11001 \end{array}$$
 1's Complement
 $0110 \rightarrow 6 \rightarrow -6$
 $0111 \rightarrow 7 \rightarrow -7^+ = -13$
 $[-7, +7]$

$C_{in} \neq C_{out} \Rightarrow \text{OV}$

Not in Range

e.g)
$$\begin{array}{r} 01011 \\ 10100^+ \\ \hline 11111 \end{array}$$
 11
 $(-11) = 0$

$11111 \rightarrow 0$

OV signed 2's Complement

if $C_{in} \neq C_{out}$ then OV \rightarrow result is wrong
 else if $C_{in} = C_{out} = 1$ then discard C_{out}

e.g)
$$\begin{array}{r} 10110 \\ 11011 \\ \hline 110001 \end{array}$$
 2's Complement
 $C_{in} = C_{out} = 1 \rightarrow \text{No OV}$

\therefore Ans: $10001 = -15$
 $01111 = 15$

$10110 \rightarrow 01010 = 10 = -10$

$011011 \rightarrow 00101 = 5 = -5$
 $-10 - 5 = -15$

e.g)
$$\begin{array}{r} 1000 \\ 1000 \\ \hline 1000 \end{array}$$

Class 8

Sunday

ASCII →

n: # of bits

of possible values or character = 2^n

e.g) n=7 For Ascii

$$2^7 = 128$$

e.g) $A = (65)_{10} = (41)_{16} = (01000001)$

7 bits

Binary Codes

Parity Check

e.g) $B = (66)_{10} = (42)_{16} = (0100\ 0010)_2$

e.g) x = # of character = 76 Find n?

Sol → $x = 76 = 2^n$

$$\log 76 = n \log 2 \Rightarrow n = \frac{\log 76}{\log 2} = 6.24$$

∴ $n = 7$ The ceiling

OR → $2^6 < 76 < 2^7$
 $64 < 76 < 128$

$n = 7$

class 9

Tuesday

- BCD, Gray Code, Logic gates:-

Eg) $(1998)_{10} \rightarrow (0001\ 1001\ 0111\ 1000)_{BCD}$

BCD \rightarrow Binary Coded Decimal, A-F Not exist X
* Groups of 4

* BCD \rightarrow Decimal

Eg) 1011 0111

Can't be B.C.D, Wrong Code x

Ex) $(1001\ 1000\ 0011)_{BCD} \rightarrow$ Decimal
 $(9\ 8\ 3)_{10}$


1] 1 Byte stores 2 BCD digits 8 bits (packed)

2] 1 Byte store 1 BCD (unpacked)
LSB
MSB 0000

* Gray Code	Value	Binary	Gray
	0	000	000
	1	001	001
	2	010	011
	3	011	010
	4	100	110
	5	101	111
	6	110	101
	7	111	100

To convert

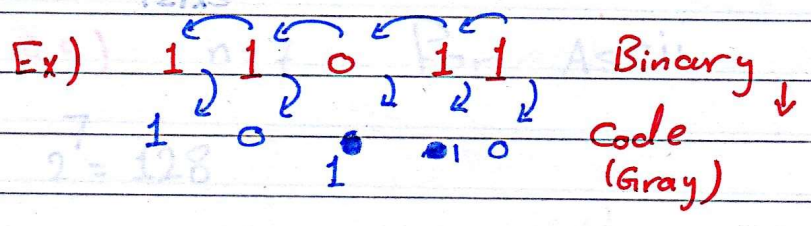1) Start from LSB
if the next bit is 1 then convert the current else (if=0) do nothing



XOR $\rightarrow P = x \oplus y$; $P = 1$ if we have odd # of 1's.

x	y	P
0	0	0
0	1	1
1	0	1
1	1	0

2) Copy MSB
for each smaller

$$G[i] = B[i] \oplus B[i+1]$$

Ex) $i = 4 \rightarrow$

i	4	3	2	1	0
B	1	1	0	1	1

- $i = 4$ $G[4] = 1$
 - $i = 3$ $G[3] = B[3] \oplus B[4] = 1 \oplus 1 = 0$
 - $i = 2$ $G[2] = B[2] \oplus B[3] = 0 \oplus 1 = 1$
 - $i = 1$ $G[1] = B[1] \oplus B[2] = 1 \oplus 0 = 1$
 - $i = 0$ $G[0] = 1 \oplus 1 = 0$
- $\therefore G = 10110$

Tuesday

CLASS 9

* Gray \rightarrow Binary

- Start from MSB

$$B[i] = B[i+1] \oplus G[i]$$

Ex)	i	4	3	2	1	0
	G	1	0	1	1	0

B = ?

$$i=4 \quad B[4] = 1$$

$$i=3 \quad B[3] = B[4] \oplus G[3] = 1 \oplus 0 = 1$$

$$i=2 \quad B[2] = B[3] \oplus G[2] = 1 \oplus 1 = 0$$

$$i=1 \quad B[1] = B[2] \oplus G[1] = 0 \oplus 1 = 1$$

$$i=0 \quad B[0] = B[1] \oplus G[0] = 1 \oplus 0 = 1$$

$$B = 11011$$

NAND: Not AND, In U.A.M.A

$$\overline{A \cdot B} = \overline{A} \cdot \overline{B} \quad \overline{A} = \text{NOT gate}$$

$$\overline{A \cdot B} = \overline{A} \cdot \overline{B} \quad \text{2 gates}$$

Class 10

AND, OR, NOT/INV, NAND, NOR, XOR, XNOR

AND: The Output is 1 if all inputs are 1

$P = A \cdot B = AB$




Truth Table :-

	A	B	P
# of inputs = 2 ⁿ	0	0	0
	0	1	0
	1	0	0
	1	1	1

n = 2

Timing diagram :-

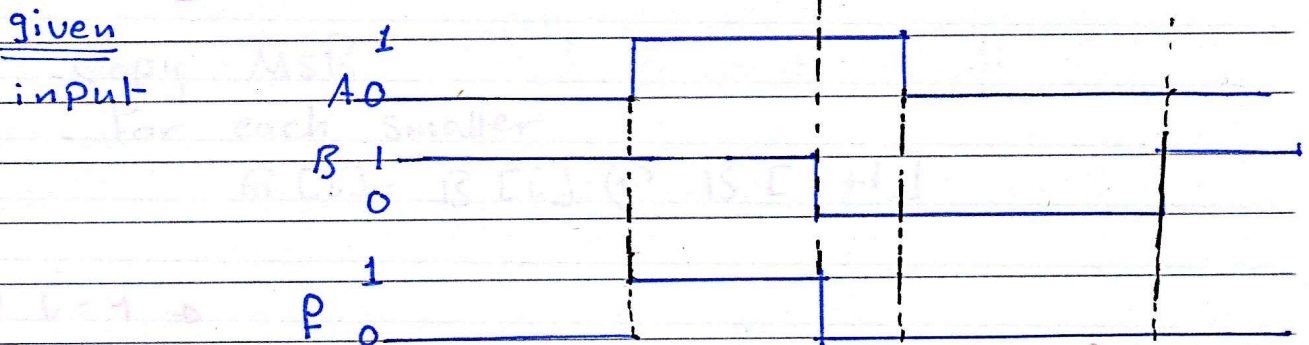


0, 1 = 0
 And


Class 10

OR: The Output is 1 if any of the inputs



is 1

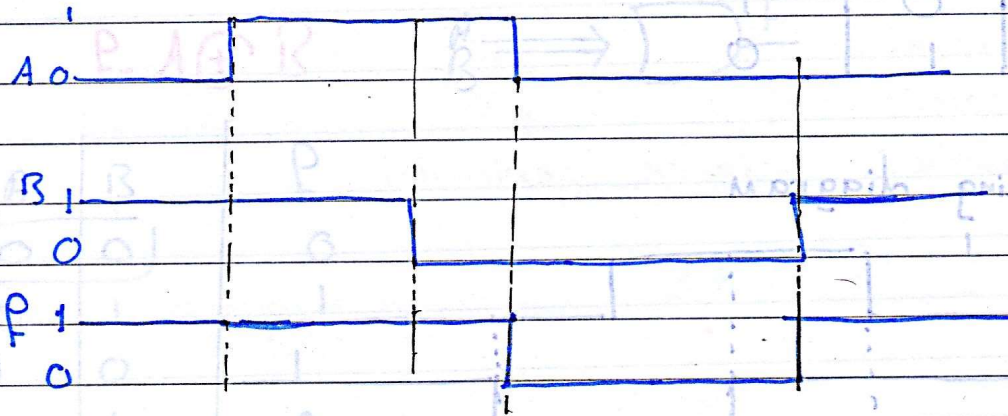

Inverter (One input)


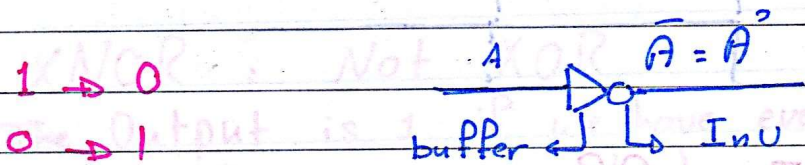


1 → 0
0 → 1

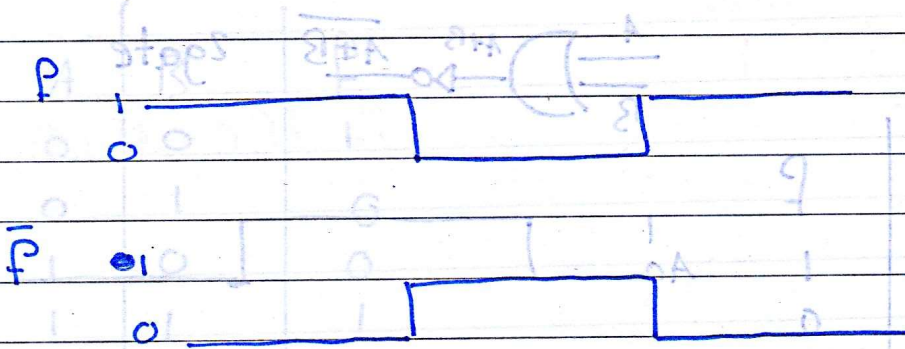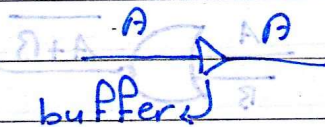

NAND: Not AND, In U. AND


$P = A \uparrow B = \overline{A \cdot B} = \overline{AB}$

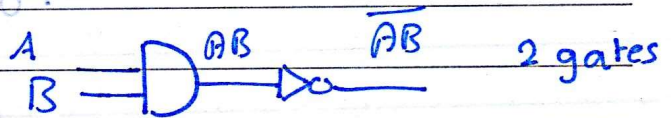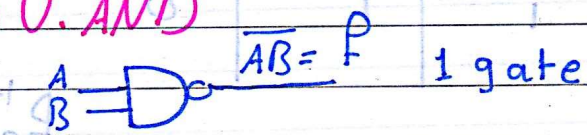

Class 10



A	B	$P = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

* Timing diagram

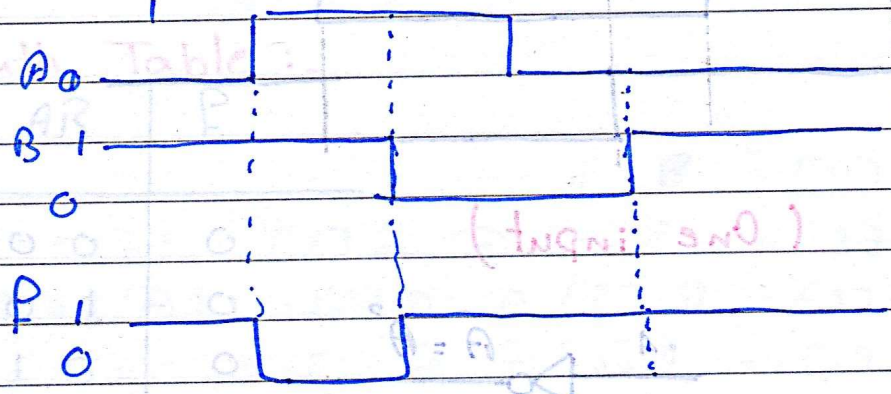


NOR: NOT OR / InV OR

$P = A \downarrow B = \overline{A+B}$

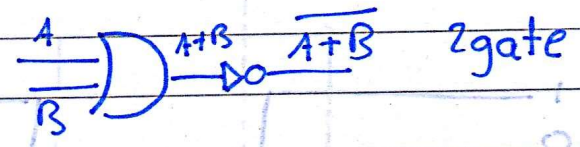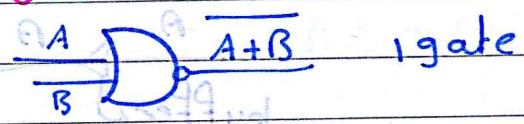

A	B	P
0	0	1
0	1	0
1	0	0
1	1	0

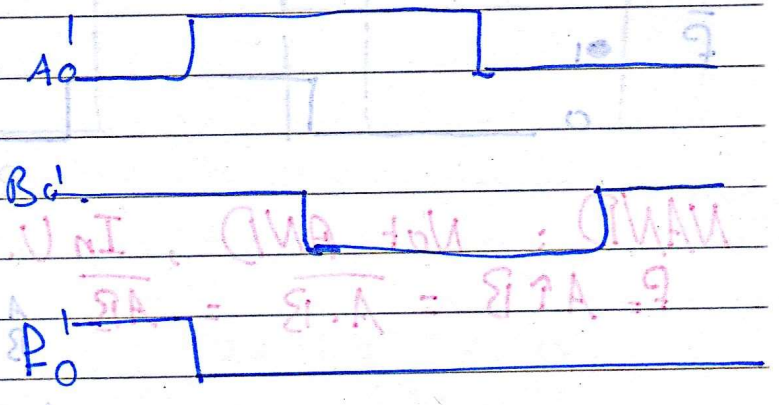


CLASS 10

- Exclusive OR (XOR)

∴ Output is 1 if we have odd # of 1's in the input.

$$P = A \oplus B$$

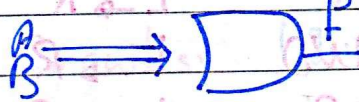

A	B	P
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR : Not XOR


The Output is 1 if we have even # of 1's

(Comperator)

$$P = \overline{A \oplus B}$$

$$P = \overline{A \oplus B}$$




A	B	P
0	0	1
0	1	0
1	0	0
1	1	1

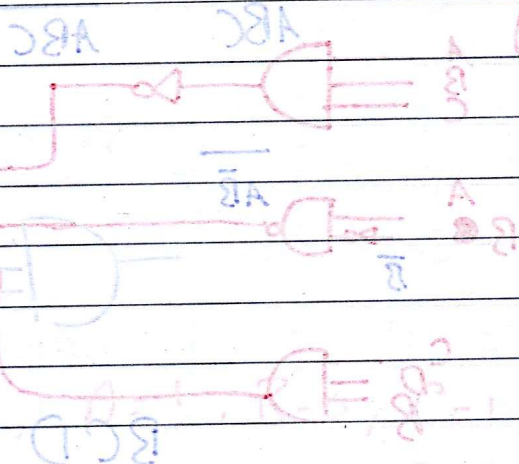

* Describing logic circuits → gives me the circuit and I give him $F = ?$

Steps:

- ① Start by INV $L \rightarrow R$
- ② Implement AND $L \rightarrow R$
- ③ Implement OR $L \rightarrow R$
- ④ Paranthesis enforce periority.

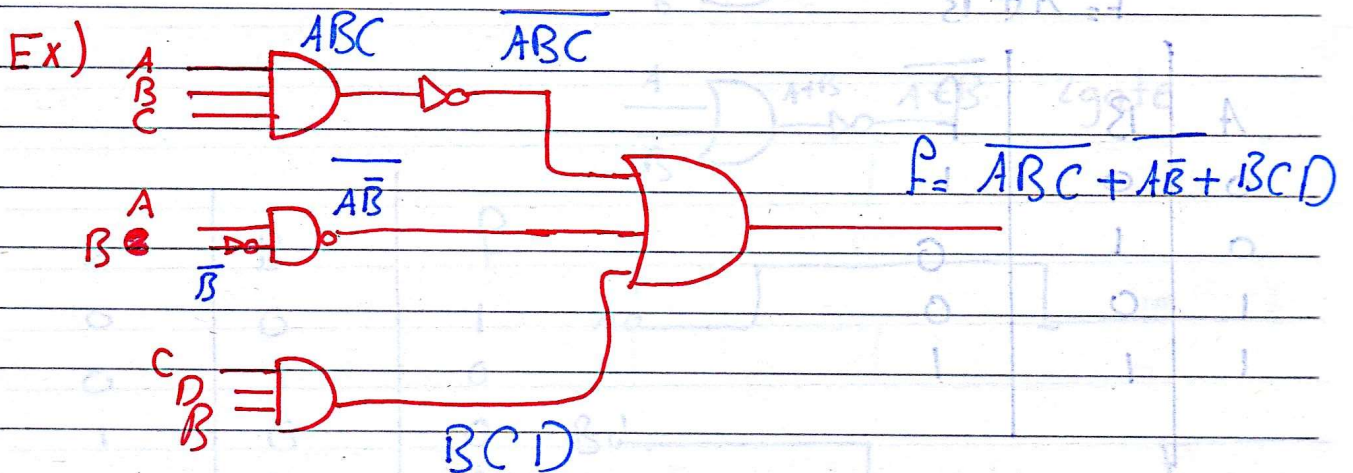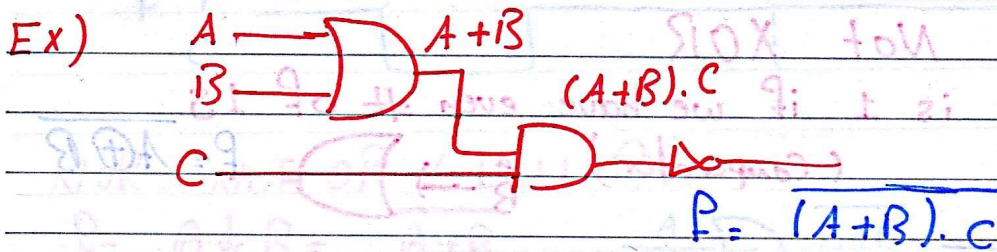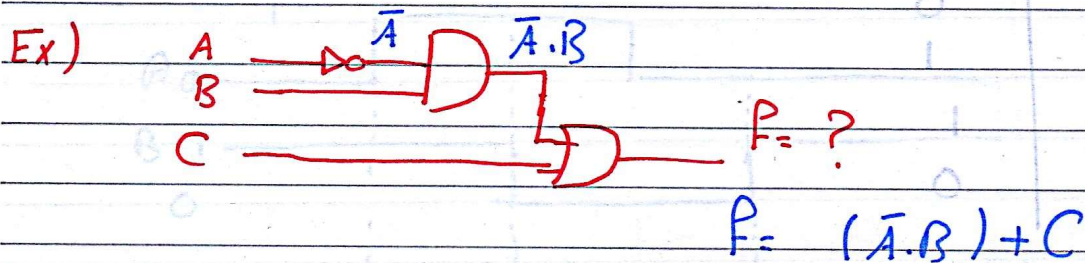

class 11

- Evaluating boolean expression
- Implementing logic Circuit
- Extending gates to multiple inputs.

* Evaluating logic Circuits: (given boolean expression)

① Evaluate all inversions (INV)

② " " AND operations

③ " " OR "



④ Peranthesis have the priority.

Ex) $F = \bar{A}BC (A+D)$, $A=0$, $B=1$, $C=1$, $D=1$

$F = ?$


$$F = (\bar{0})(1)(1)(0+1)$$

$$= (1)(1)(1)(1) = \underline{1}$$

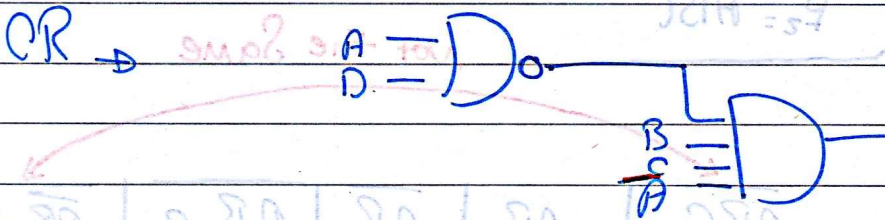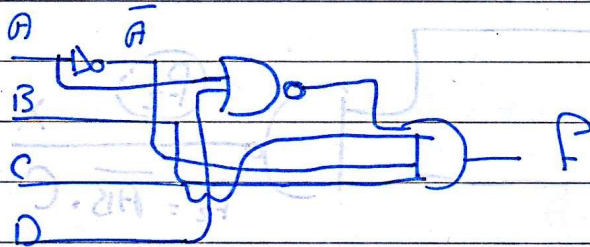



Ex) $F = AC + \bar{B}C + \bar{A}BC$, $A=1$, $B=0$, $C=1$

$$F = 1(1) + 0(0) + (0)(0)(1) = 1 + 0 + 0 = 1$$

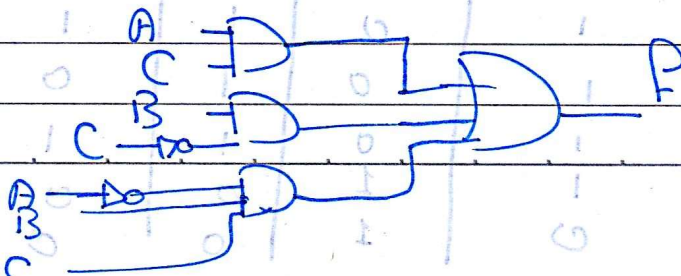



class 11

* Extension to multiple Inputs.

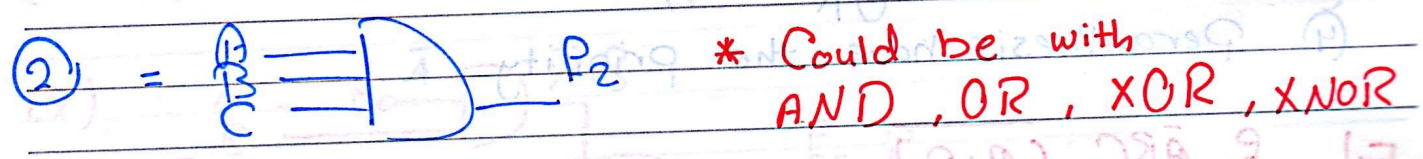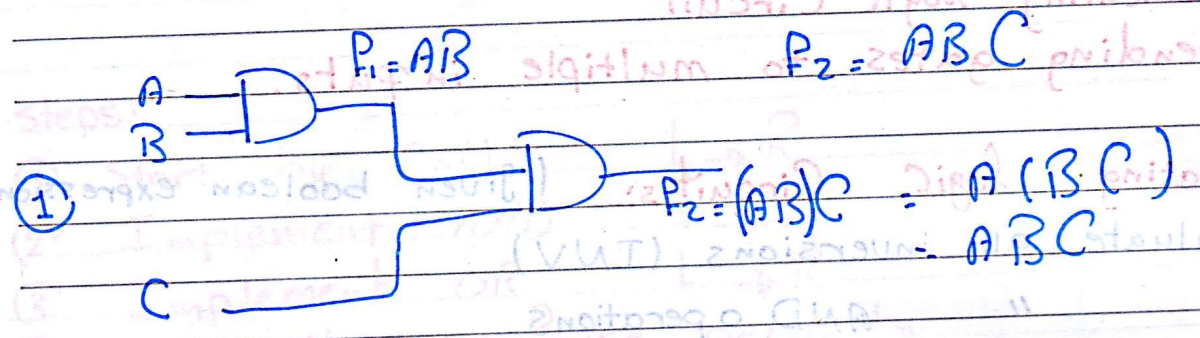

* NAND, NOR

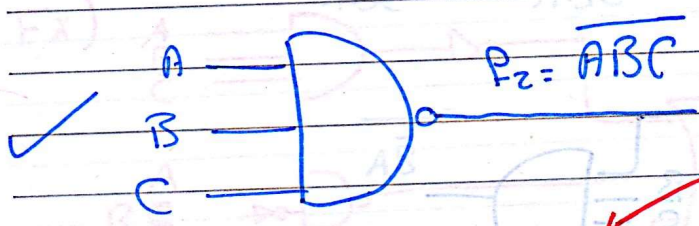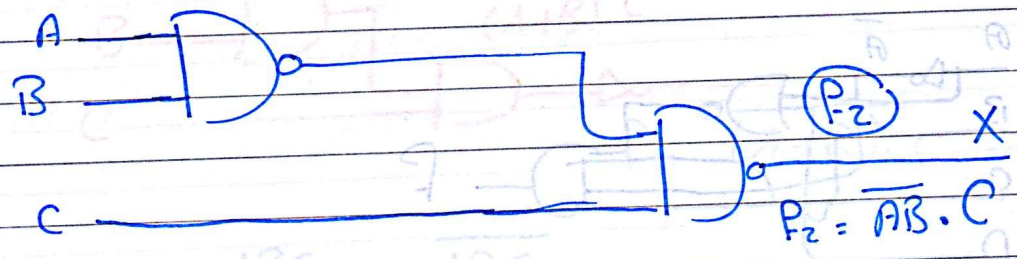$P_1 = \overline{AB}$, $P_2 = \overline{ABC}$




Not the Same

A	B	C	\overline{ABC}	AB	\overline{AB}	$AB \cdot C$	$\overline{AB \cdot C}$
0	0	0	1	0	1	0	1
0	0	1	1	0	1	0	1
0	1	0	1	0	1	0	1
0	1	1	1	0	1	0	1
1	0	0	1	0	1	0	1
1	0	1	1	0	1	0	1
1	1	0	0	1	0	0	1
1	1	1	0	1	0	1	0


Class 11

H.w) Does $F = \overline{(\overline{A+B})} + C$ equal $\overline{A+B} + C$


to build the following circuit

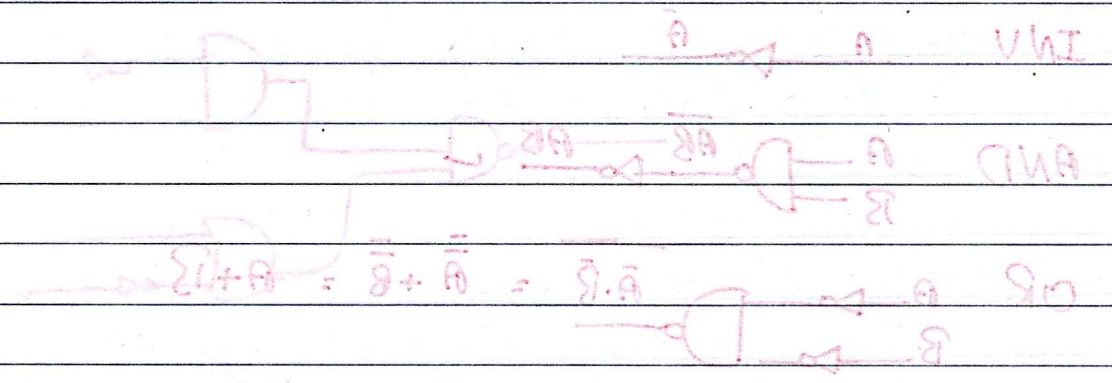

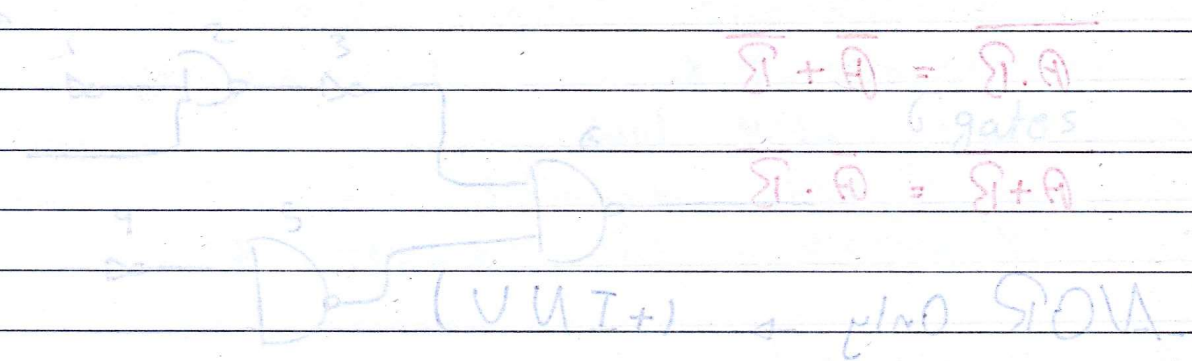De Morgan's law: $\overline{A+B} = \overline{A} \cdot \overline{B}$





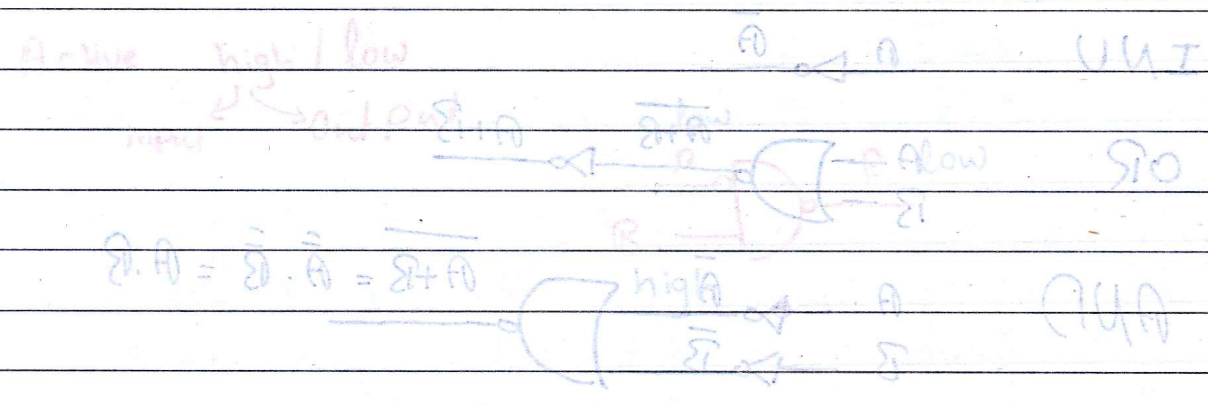$\overline{A+B} = \overline{A} \cdot \overline{B}$
 6 gates
 $\overline{A+B} = \overline{A} \cdot \overline{B}$



$\overline{A+B} = \overline{A} \cdot \overline{B} = \overline{A+B}$

NAND Only $\rightarrow (+ INU)$


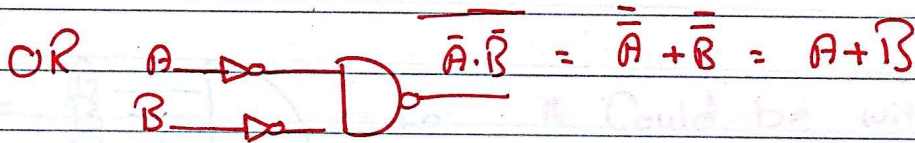
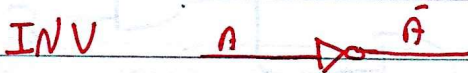


DeMorgan's law:-

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$



NOR Only $\rightarrow (+ INU)$

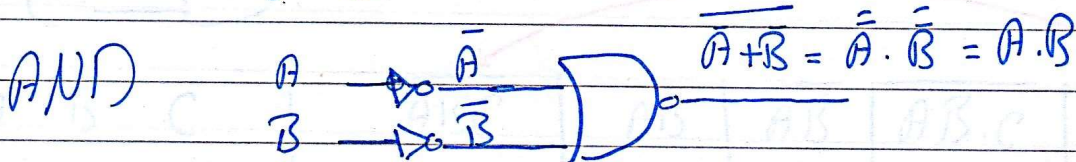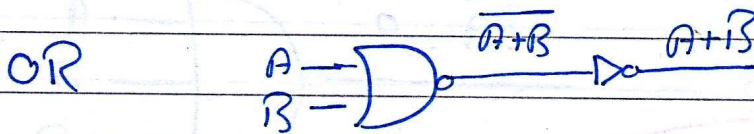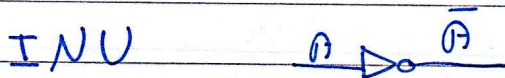


Class 11

Sunday

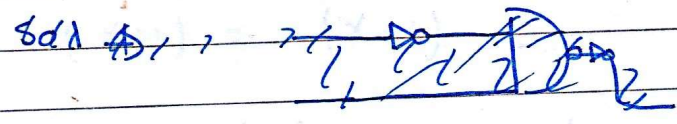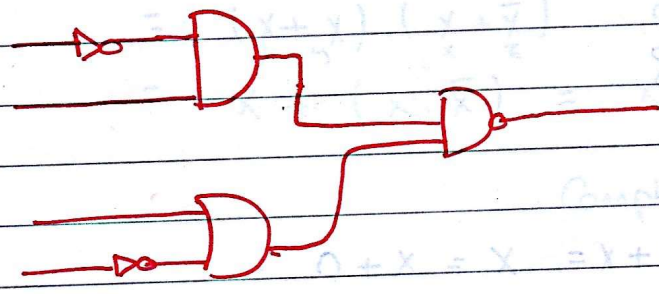Ex) How many gates using NAND Only to build the following circuit.




Sol →

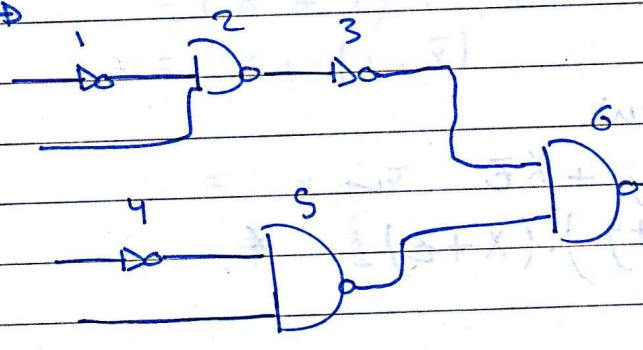

6 gates

- Active high / low input → output

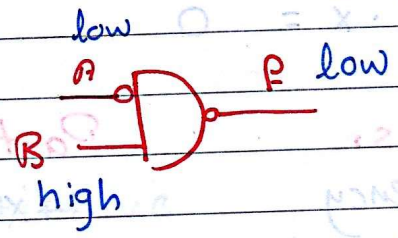

$$\bar{A} + X = \bar{A} \cdot X$$

$$X = (A + X) \cdot X$$

$$\bar{A} \cdot X = X + \bar{A}$$

$$X + X = X$$

$$\bar{A} \cdot \bar{A} = \bar{A}$$

$$\bar{A} \cdot A = 0$$

* - Absorption

SN
Class 12 →

Tuesday

Postulates, Theorems, Examples

$x, y \in B = \{0, 1\}$

1. Closure

$x+y \in B$
 $x \cdot y \in B$

2. Identity

$0+x = x = x+0$
 $1 \cdot x = x = x \cdot 1$

3. Commutative

$x+y = y+x$
 $x \cdot y = y \cdot x$

* 4. Distributive law

$x(y+z) = xy + xz$
 $x+(y \cdot z) = (x+y) \cdot (x+z)$ *

5. Complement

$x + \bar{x} = 1$
 $x \cdot \bar{x} = 0$

* Theorems:

	Part A	Part B
1. Idempotency	$x+x = x$	$x \cdot x = x$
2. NULL Element	$x+1 = 1$	$x \cdot 0 = 0$
3. Involution	$\bar{\bar{x}} = x$, (x') ' = x	
4. Associative	$(x+z)+y =$ $x+(z+y)$	$(x \cdot y) \cdot z =$ $x \cdot (y \cdot z)$
5. DeMorgan's law	$\overline{x+y} = \bar{x} \cdot \bar{y}$	$\overline{x \cdot y} = \bar{x} + \bar{y}$
* 6. Absorption	$x + xy = x$	$x \cdot (x+y) = x$

Tuesday

Ex) $x + x = x$, Prove

$$(x+x) = (x+x) \cdot 1 \quad \text{identity}$$

$$= (x+x) \cdot (x+\bar{x}) \quad \text{Complement, distributive}$$

$$= x + (x \cdot \bar{x}) = x + 0 = x$$

Complement Identity

Ex) $x+1 = 1$, Prove

$$(x+1) = (x+1) \cdot 1 \quad \text{Identity}$$

$$= (x+1) \cdot (x+\bar{x}) \quad \text{Complement}$$

$$= x + (1 \cdot \bar{x}) \quad \text{Distributive}$$

$$= x + \bar{x} \quad \text{Identity}$$

$$= 1 \quad \text{Complement.}$$

Ex) $x + xy = x$, Prove

$$x(1+y) = x \cdot 1 = x$$

OR

$$\text{Identity} \leftarrow x \cdot 1 + xy = x$$

$$= x(1+y) \rightarrow \text{Distributive}$$

$$= x \cdot 1 \rightarrow \text{Null}$$

$$= x \rightarrow \text{Identity}$$

Ex) $\overline{A \cdot B \cdot C} = \bar{A} + \bar{B} + \bar{C}$

Ex) $\overline{A \cdot B + \bar{C} \cdot D} = \overline{AB} \cdot \bar{C} \cdot \bar{D} = \overline{AB} \cdot C \cdot \bar{D}$
 $= (\bar{A} + \bar{B}) \cdot C \cdot \bar{D}$

Class 12

Ex) $(\bar{A} + B) \cdot C \cdot D$

= $(\bar{A} + B) + \bar{C} + \bar{D}$

= $A \cdot \bar{B} + \bar{C} + \bar{D}$

* Simplification:

① Reduce circuit size

② Equivalency proof

- Techniques

① Combining terms \rightarrow

Literal $x \cdot y + x \cdot \bar{y} = x \rightarrow x \cdot (y + \bar{y}) = x \cdot 1 = x$
 $x \cdot y + x \cdot y \cdot z = x \cdot y$

Ex) $ab\bar{c} + abc$
 $ab(\bar{c} + c) = \underline{ab}$

② Adding Redundant terms \rightarrow

$a\bar{b}c + abc + \bar{a}bc$
 $= a\bar{b}c + abc + abc + \bar{a}bc$
 $= ac(\bar{b} + b) + bc(a + \bar{a})$
 $= ac + bc$

③ Eliminating terms.

$x + x \cdot y = x$ $\square + \square \dots = \square$

"Class 13"

$$\text{Ex) } \bar{a}b\bar{c} + bc\bar{d} + bd + \bar{a}b$$

$$bd + \bar{a}b$$

[4] Eliminating Literal

$$x + \bar{x}y = x + y = (\bar{x} + x) \cdot (x + y) = x + y$$

$$\bar{x} + xy = \bar{x} + y$$

$$\text{Ex) } \bar{A}B + \bar{A}\bar{B}\bar{C}\bar{D} + ABC\bar{D}$$

$$= \bar{A}(B + \bar{B}\bar{C}\bar{D}) + ABC\bar{D}$$

$$= \bar{A}(B + \bar{C}\bar{D}) + ABC\bar{D}$$

$$= \bar{A}B + \bar{A}\bar{C}\bar{D} + ABC\bar{D}$$

$$= B(\bar{A} + AC\bar{D}) + \bar{A}\bar{C}\bar{D}$$

$$= B(\bar{A} + C\bar{D}) + \bar{A}\bar{C}\bar{D}$$

$$= \bar{A}B + Bc\bar{D} + \bar{A}\bar{C}\bar{D}$$

* Canonical Forms.

- How to represent Boolean Functions?

Standard Form (2 Levels)

1) Sum of Product (ANDing → ORing)
 Sum of minterms (Canonical form)
 a term that contains all input


2) Product of Sum (ORing → ANDing)
 Product of Maxterms (an ORed term that contains all inputs)

Non Standard.


"Class 13"

Ex)
$$P_1 = xy + z$$
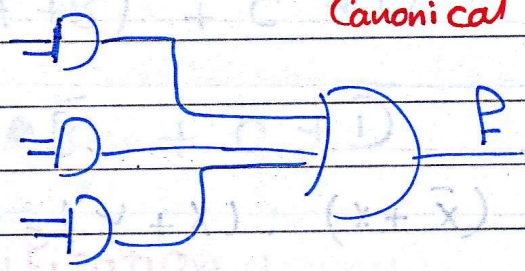
$$P_2 = xyz + \bar{x}\bar{y}z$$
 Canonical 2 levels





Sum of Product

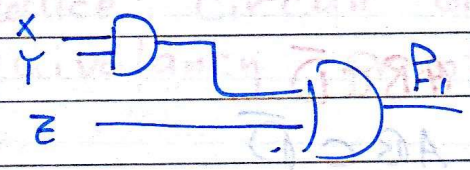

Ex)
$$P_1 = (x + y)(z)$$
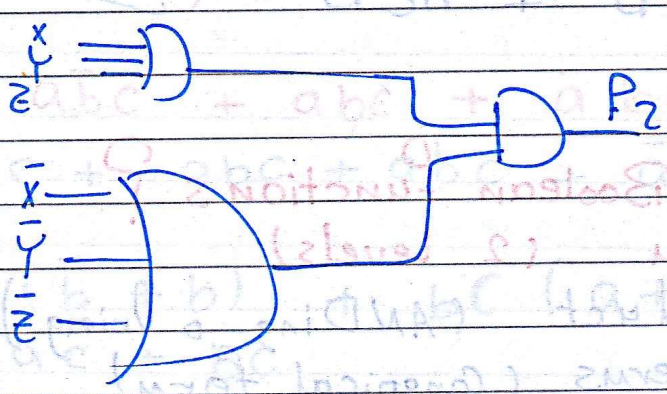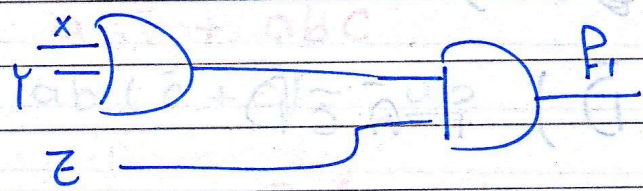
$$P_2 = (x + y + z) \cdot (\bar{x} + \bar{y} + \bar{z})$$



• Class 13,

* Non standard

Ex) $F = (X + Y) \cdot Z + \bar{X}$

- Sum of Minterms

Given $F(x, y, z)$

$x y z \rightarrow F$

	x	y	z	F
m_0	0	0	0	0
m_1	0	0	1	1 ✓
m_2	0	1	0	1 ✓
m_3	0	1	1	0
m_4	1	0	0	0
m_5	1	0	1	1 ✓
m_6	1	1	0	0
m_7	1	1	1	0

- Look for 1s in F

- Find the corresponding Minterms

- Convert Minterm to variables (Inputs)

- i.e. (x, y, z)

$$F = m_1 + m_2 + m_5$$

$$= \bar{x} \cdot \bar{y} \cdot z + \bar{x} \cdot y \cdot \bar{z} + x \cdot \bar{y} \cdot z$$

Class 14

$F = \Sigma(1, 2, 5)$

$F(x, y, z) = \Sigma(1, 2, 5)$

* Product of Maxterms:

- 1) Look for zeroes in P.
- 2) Find corresponding Maxterms.
- 3) Write Maxterm as x, y, z.

Ex) Given 13:1

Max	x	y	z	P
M ₀	0	0	0	0
M ₁	0	0	1	1
M ₂	0	1	0	1
M ₃	0	1	1	0
M ₄	1	0	0	0
M ₅	1	0	1	1
M ₆	1	1	0	0
M ₇	1	1	1	0

write P as product of Maxterms.

$P = M_0 \cdot M_3 \cdot M_4 \cdot M_6 \cdot M_7$

$= (x + y + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z) \cdot (\bar{x} + \bar{y} + \bar{z})$

$= \Pi(0, 3, 4, 6, 7)$

Class 14

Ex) $F_1(x, y, z) = \Sigma(0, 1, 2, 7)$

$F_2(x, y, z) = \Pi(0, 3; 4)$

$F_3 = (F_1 + F_2)$

Find \bar{F}_3 as product of Maxterms?

$$F_3 = \Pi(\dots) ?$$

	x	y	z	F_1	F_2	$F_3 = F_1 + F_2$	\bar{F}_3
0	0	0	0	1	0	1	0
1	0	0	1	1	0	1	0
2	0	1	0	1	0	1	0
3	0	1	1	0	0	0	1
4	1	0	0	0	0	0	1
5	1	0	1	0	1	1	0
6	1	1	0	0	1	1	0
7	1	1	1	1	1	1	0

$$\bar{F}_3 = \Pi(0, 1, 2, 5, 6, 7)$$

$$\bar{F}_3 = (x+y+\bar{z}) \cdot (x+\bar{y}+z) \cdot (\bar{x}+y+\bar{z}) \cdot (\bar{x}+y+z) \cdot (\bar{x}+\bar{y}+z) \cdot (\bar{x}+\bar{y}+\bar{z})$$

Ex) Find \bar{F} if $F = \Sigma(1, 6)$.

$$F = \Sigma(0, 2, 3, 4, 5, 7)$$

$$\bar{F} = \Pi(1, 6)$$

OR $\Rightarrow F = \bar{x}\bar{y}z + x y \bar{z}$
 $\bar{F} = (\bar{x}\bar{y}z + x y \bar{z})'$

$$= \overline{\bar{x}\bar{y}z} \cdot \overline{x y \bar{z}} = (x+y+\bar{z}) \cdot (\bar{x}+\bar{y}+z)$$

$$= \Pi(1, 6)$$

Class 14

Duality Principle \rightarrow

Convert $+$ \rightarrow \cdot
 \cdot \rightarrow $+$

Convert 0 \rightarrow 1
 1 \rightarrow 0

If this is done then the equality is still valid.

A. Identity $x+0=x$ (a) $x \cdot 1=x$ (b)

B. Commutative $x+y=y+x$ $x \cdot y=y \cdot x$

C. Distributive $x(y+z) = xy+xz$ $x+y \cdot z = (x+y) \cdot z$

D. Complement $\bar{x}+x=1$ $x \cdot \bar{x}=0$

$$x \oplus y = x\bar{y} + \bar{x}y$$

$$\overline{x \oplus y} = \overline{x\bar{y} + \bar{x}y} = \bar{x} \oplus y = \pi x \oplus \bar{y}$$

$$x \oplus 0 = x$$

$$x \oplus 1 = \bar{x}$$

$$x \oplus x = 0$$

$$x \oplus \bar{x} = 1$$

$$x \oplus y = y \oplus x$$

$$x(y \oplus z) = xy \oplus xz$$

class 15

Ex) $F = xy + \bar{z}$, write it in canonical form

$$= xy \cdot 1 + \bar{z}$$

$$= xy(z + \bar{z}) + \bar{z}$$

$$= xyz + xy\bar{z} + \bar{z}$$

$$\bar{z} \Rightarrow \bar{z} \cdot 1 \cdot 1 = \bar{z} \cdot (x + \bar{x}) \cdot (y + \bar{y})$$

$$= (x\bar{z} + \bar{x}\bar{z}) \cdot (y + \bar{y})$$

$$= xy\bar{z} + x\bar{y}\bar{z} + \bar{x}y\bar{z} + \bar{x}\bar{y}\bar{z}$$

$$F = xyz + xy\bar{z} + x\bar{y}\bar{z} + \bar{x}y\bar{z} + \bar{x}\bar{y}\bar{z}$$

$$F = \Sigma(7, 6, 4, 2, 0)$$

$$= \Sigma(0, 2, 4, 6, 7)$$

Ex) $F = (x+y) \cdot z$

POS, write F in canonical form.

$$\rightarrow (x+y) \Rightarrow x+y+0 = (x+y) + z \cdot \bar{z}$$

$$= (x+y+z) \cdot (x+y+\bar{z})$$

$$z = (x+y+z) \cdot (\bar{x}+y+z) \cdot (x+\bar{y}+z) \cdot (\bar{x}+\bar{y}+z)$$

$$F = \Pi(0, 2, 4, 6, 1)$$

$$= \Pi(0, 1, 2, 4, 6)$$

Ex) Prove $(x + y) \cdot (\bar{x} + z) = xz + \bar{x}y$

	x	y	z	$x+y$	$\bar{x}+z$	$(x+y) \cdot (\bar{x}+z)$	xz	$\bar{x}y$	$A+B$
0	0	0	0	0	1	0	0	0	0
1	0	0	1	0	1	0	0	0	0
2	0	1	0	1	1	1	0	1	1
3	0	1	1	1	1	1	0	1	1
4	1	0	0	1	0	0	0	0	0
5	1	0	1	1	0	0	1	0	1
6	1	1	0	1	0	0	0	0	0
7	1	1	1	1	1	1	1	0	1

∴ Eq 4.1 proved by truth table.

$$F = \pi(0, 1, 4, 6)$$

$$= \sum(2, 3, 5, 7)$$

$$\bar{F} = \pi(2, 3, 5, 7)$$

$$\bar{F} = \sum(0, 1, 4, 6)$$

class 15

Other sol -


$$\begin{aligned}
 (x+y) \cdot (\bar{x}+z) &= x \cdot \bar{x} + x \cdot z + y \bar{x} + y z \\
 &= x \cdot z + \bar{x} y + y z \cdot 1 \\
 &= x \cdot z + \bar{x} y + y z \cdot (x + \bar{x}) \\
 &= x \cdot z + \bar{x} y + x y z + \bar{x} y z \\
 &= x z (1+y) + \bar{x} y (1+z) \\
 &= x z + \bar{x} y
 \end{aligned}$$

Ex) ~~xy~~ $\bar{x} y \oplus z w$ * simplify
* write

$$\begin{aligned}
 \overline{\bar{x} y} \oplus z w &= x y \oplus z w \\
 &= x y \cdot \bar{z} \bar{w} + \bar{x} \bar{y} \cdot z w \\
 &= x y \cdot (\bar{z} + \bar{w}) + (\bar{x} + \bar{y}) \cdot z w \\
 &= x y \bar{z} + x y \bar{w} + \bar{x} z w + \bar{y} z w
 \end{aligned}$$

SOP

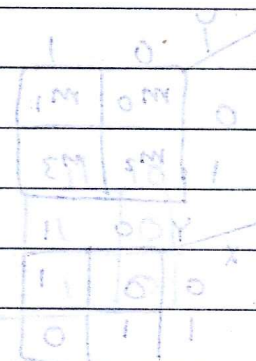
Handwritten notes in red ink, including "Karnaugh map" and "simplify".




Handwritten notes in red ink, including "Karnaugh map" and "simplify".

"Lecture 6"

Kmap

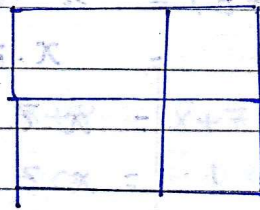

2 inputs

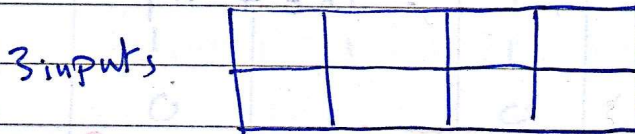

3 inputs

K-maps:-



1. How to construct k-map
2. Mapping the function
"Filling kmap with function values,"
3. Simplification using k-map

* Each k-map should have:-

1. 2^n cells
2. each cell represent 1 minterm
Or 1 maxterm
3. in each row or col. adjacent cells
differs by one literal

* 2-inputs kmap

i	x	y	F (given)
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	0

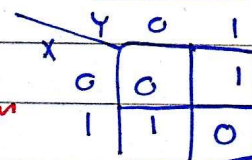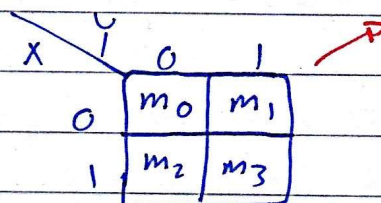

$F = x \oplus y \rightarrow$ evaluate function

$F = x\bar{y} + \bar{x}y \rightarrow$ Canonical

Sunday

Ex) $F(x, y) = x$
create the K-map

4) Standard

$$m_0 = \bar{x}\bar{y}$$

$$m_2 = x\bar{y}$$

$$m_3 = x\bar{y}$$

$$m_3 = x\bar{y}$$

		0	1
0	0	0	0
1	1	1	1

3 inputs Kmap

	X	Y	Z	P given
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

		00	01	11	10
0	m ₀	m ₁	m ₃	m ₂	
1	m ₄	m ₅	m ₇	m ₆	

$$m_1 = \bar{x}\bar{y}z$$

$$m_3 = \bar{x}yz$$

$$m_0 = \bar{x}\bar{y}\bar{z}$$

$$m_2 = \bar{x}y\bar{z}$$

		00	01	11	10
0	m ₀	m ₁	m ₅	m ₄	
1	m ₂	m ₃	m ₇	m ₆	

		00	01	11	10
0	0	1	1	0	
1	1	0	1	0	

$$F = m_1 + m_3 + m_4 + m_7$$

$$\text{OR } F = M_0 \cdot M_2 \cdot M_5 \cdot M_6$$

$$F = x\bar{y}\bar{z} + \bar{x}z + yz$$

Class 16

		00	01	11	10
0	0	0	1	1	0
1	1	1	0	1	0

4 Variables

X	Y	Z	W	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0


	00	01	11	10
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

	00	01	11	10
00	0	1	0	1
01	0	0	1	1
11	1	0	0	1
10	1	1	0	0

$f = x + y + z + w$
 $f = x + y + z + w$
 $f = x + y + z + w$

class 17

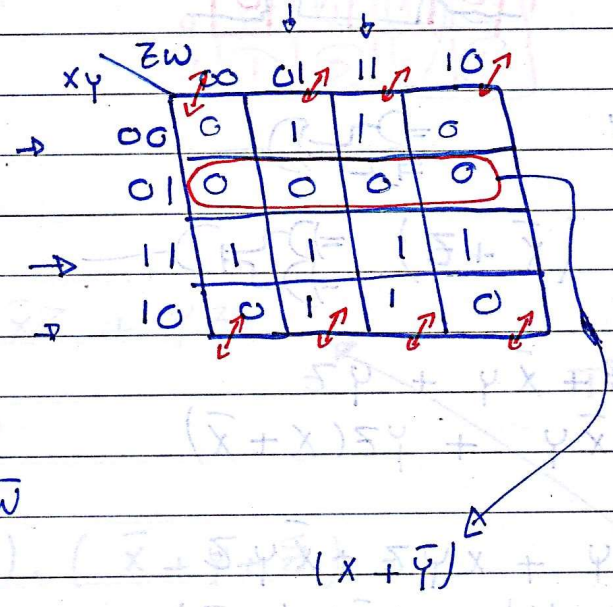Ex) $F(x, y, z, w) = xy + \bar{y}w$
 map \rightarrow k-map



$m_8 = x\bar{y}\bar{z}\bar{w}$
 $m_0 = \bar{x}\bar{y}\bar{z}\bar{w}$

* Simplification \rightarrow


Grouping in k-map SOP

1. Only combine cells that have 1 in them
2. you can combine 1, 2, 4, 8, 16... cells (2^n)
3. Each group will be 1 term (Anding) \rightarrow SOP
 (ORing) \rightarrow POS

* 4. As possible each cell must participate in 1 group
 Only, unless necessary


* 5. Start by grouping cells that have only 1 option.
 (group)

Ex) Simplify:

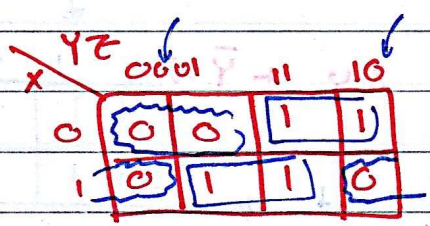

SOP

$F = xz + \bar{x}y$

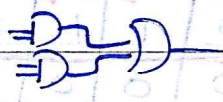

POS

$F = (x+y)(\bar{x}+z)$

$$= x \cdot \bar{x} + xz + \bar{x}y + yz$$

$$= xz + \bar{x}y + yz(x + \bar{x})$$

$$= xz + \bar{x}y + xyz + \bar{x}y\bar{z}$$


$$= xz(1+y) + \bar{x}y(1+z)$$

$$= xz + \bar{x}y$$

* After grouping check:

1. Cover all 1's ??
2. Maximize group size ??
3. Minimize # of groups ??

Ex) Simplify

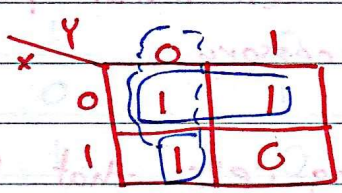


group size = 1 cell
∴ # 2 variable


P = ?
SOP = ?

group size = 2 cells
1 variable

$P = \bar{x} + x\bar{y}$

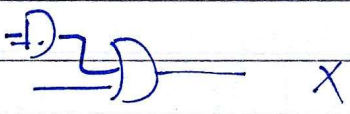

$P = \bar{x} + \bar{y}$

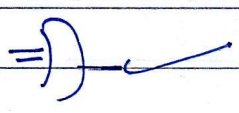

class 18

Ex)

	x \ yz	00	01	11	10
0		0	1	0	0
1		1	0	0	1

Find F as SOP, POS

SOP →

$$F = \bar{x}\bar{y}z + x\bar{z}$$

POS →

$$F = (x+z) \cdot (\bar{y}+\bar{z}) \cdot (\bar{x}+\bar{z})$$

Ex)

	x \ yz	00	01	11	10
0		1	1	1	1
1		0	1	1	0

Find F as SOP, POS

$$F = \bar{x} + z \rightarrow \text{SOP}$$

$$F = \bar{x} + z \rightarrow \text{POS}$$

2 inputs K-map

group size # of literals

1 cell

2

2 cells

1

4 cells

0 ∴ F=1 or F=0

3 inputs K-map

group size # of literals

1 cell

3

2 cells

2

4 cells

1

8 cells

0

4 inputs K-map

group size # of literals

1 cell

4

2 cells

3

4 cells

2

8 cells

1

16 cells

0

This one is not necessary X

Ex)

$xy \backslash zw$	00	01	11	10
00	1	1	1	0
01	1	1	0	0
11	1	0	0	1
10	1	0	1	1

Find F as SOP, POS

$$F = \bar{x}\bar{z} + x\bar{w} + \bar{y}zw \rightarrow \text{SOP}$$

$$F = (x+z+\bar{w}) \cdot (\bar{y}+\bar{z}+\bar{w}) \cdot (x+\bar{z}+w)$$

Ex)

$xy \backslash zw$	00	01	11	10
00	1	1	1	0
01	1	1	0	0
11	1	1	1	1
10	1	1	1	0

Find F as SOP, POS

$$F = \bar{z} + \bar{y}w + xy \rightarrow \text{SOP}$$

$$F = (x+\bar{y}+\bar{z}) \cdot (y+\bar{z}+w)$$

Ex)

$xy \backslash zw$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	0

Find F as SOP, POS

$$F = \bar{x} + y + w + \bar{z} \rightarrow \text{SOP}$$

$$F = \bar{x} + y + w + \bar{z} \rightarrow \text{POS}$$

Class 18

* Don't Care

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	X
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

X → (I don't Care about it's value)

Ex)

YZ	00	01	11	10
X=0	1	1	X	1
X=1	0	0	0	0

$F = \bar{x}\bar{y} + \bar{x}z$
 Suppose $x=1$ $F = \bar{x}$
 if $x=0$ X

* I don't have to cover all X's

Ex)

xy \ zw	00	01	11	10
00	X	1	0	0
01	X	0	0	0
11	1	0	X	X
10	1	1	0	0

$F = \bar{z}\bar{w} + \bar{z}\bar{y}$ → SOP
 $F = \bar{z} \cdot (\bar{y} + \bar{w})$

F as SOP, POS

class 19

- Analysis of boolean circuit

Analysis \rightarrow Given circuit


\swarrow Boolean expression of this circuit

\searrow Truth Table

\searrow IF possible Describe the function of the circuit.

Design \rightarrow Given Description of the function \rightarrow Circuit.

Analysis of combinational circuits

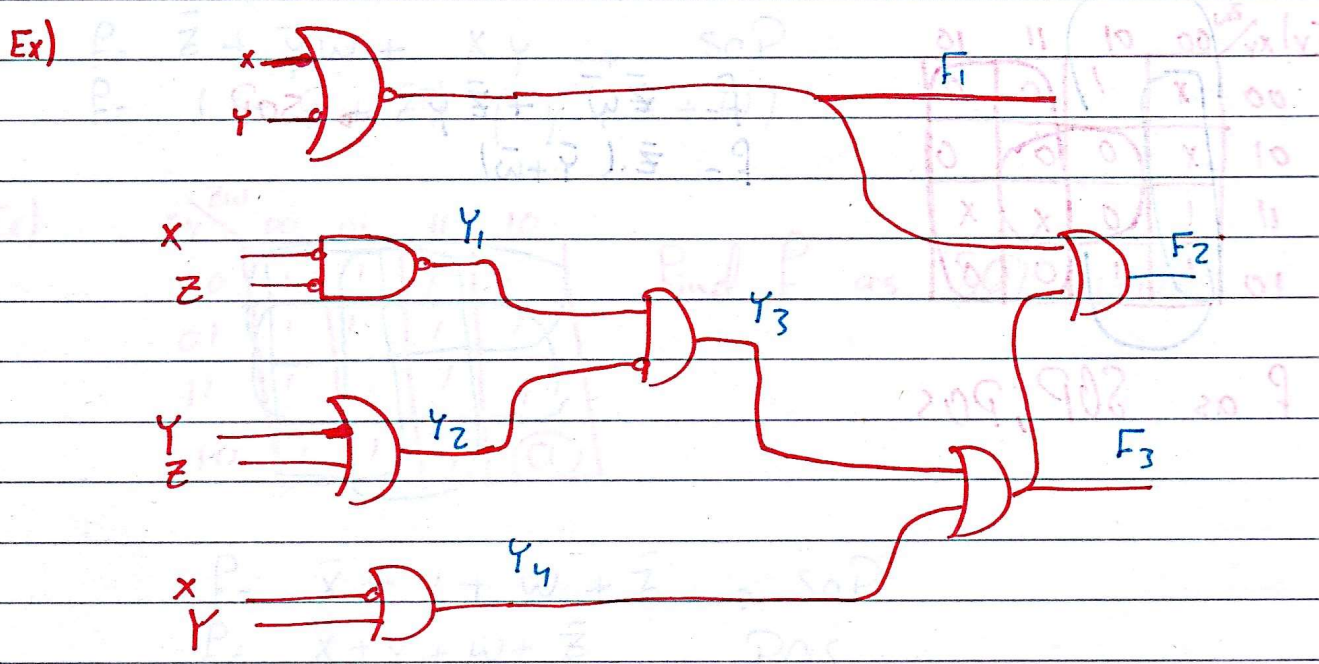

Class 19

Sunday

$$F_1 = \overline{x+y} = \bar{x} \cdot \bar{y}$$

$$Y_1 = \overline{\bar{x} \cdot \bar{z}} = x+z$$

$$Y_2 = \overline{y+z}$$

$$Y_3 = Y_1 \cdot Y_2 = (x+z) \cdot (y+z)$$

$$Y_4 = \bar{x} + y$$

$$F_3 = Y_3 + Y_4 = \dots$$

of row = $2^n = n$

of possible functions
= $2^m = 2^{(2^n)}$



$$F_2 = F_1 + F_3$$

x	y	z	F ₁	Y ₁	Y ₂	Y ₃	F ₂	F ₃	Y ₄
0	0	0	0	0	1	0	1	1	1
0	0	1	0	1	0	1	1	1	1
0	1	0	1	0	0	0	1	1	1
0	1	1	1	1	0	1	1	1	1
1	0	0	0	1	1	0	0	0	0
1	0	1	0	1	0	0	1	1	0
1	1	0	0	1	0	1	1	1	0
1	1	1	0	1	0	1	1	1	0

Design of combinational circuits →

1/ Limitation →


- The available logic gates, e.g. NAND, NOR Only
- Restrictions on the number of inputs.
e.g., you only have 2 inputs OR 2 gates, $F = x+y+z+w$

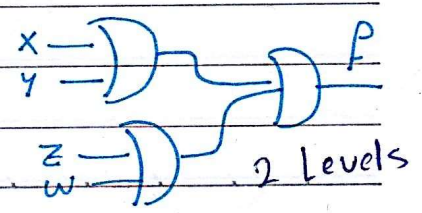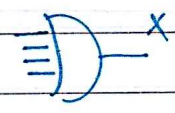

Class 19


3. Propagation Delay

e.g., Delay should be $\leq 2d$

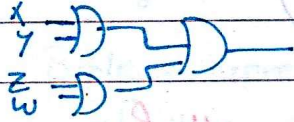

$d + d = 2d$

4. Driving Capability

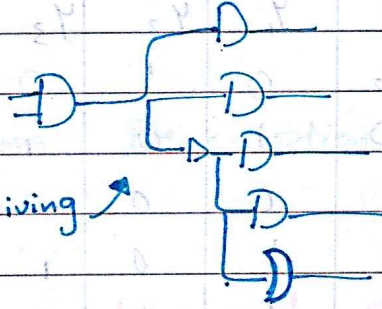

e.g. 3 Driving


Ex) Design 3bit Binary to Gray Code Converter.

x	b ₂	P ₂
y	b ₁	P ₁
z	b ₀	P ₀

① Find Truth table

② Find boolean expression of outputs

③ Draw the circuit.

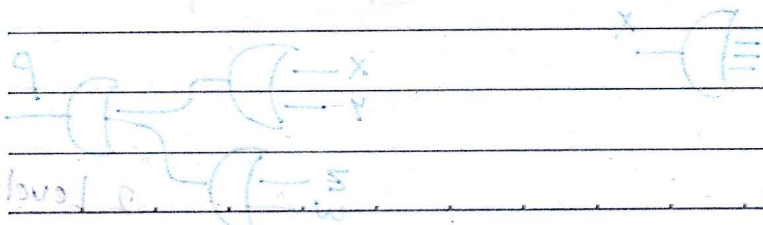

class 20

Gray Code

Binary			Gray		
x	y	z	g_2	g_1	g_0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

$g_2 = x$


	yz	00	01	11	10
x	0	0	0	0	0
	1	1	1	1	1

$g_1 = x\bar{y} + \bar{x}y$
 $= x \oplus y$

	yz	00	01	11	10
x	0	0	0	1	1
	1	1	1	0	0



$g_0 = \bar{y}z + y\bar{z}$
 $= y \oplus z$

	yz	00	01	11	10
x	0	0	1	0	1
	1	0	1	0	1

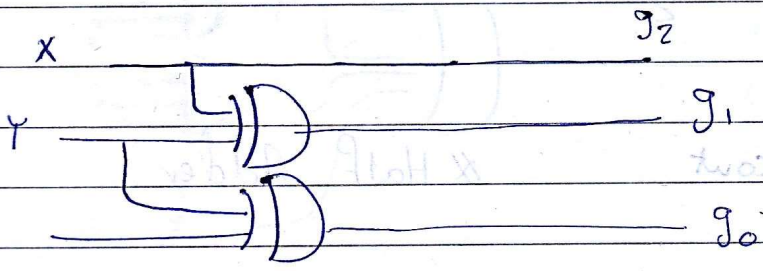


Adder

↳ Half Adder
↳ Full Adder

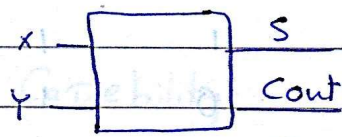
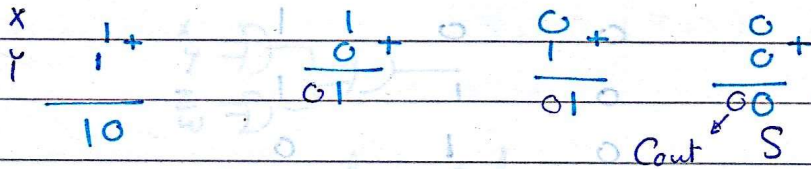


X	Y	cout	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$S = X \oplus Y$
 $cout = X \cdot Y$

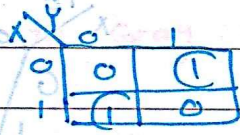

$X\bar{Y} + \bar{X}Y$

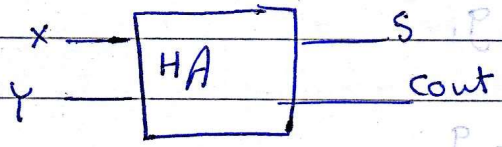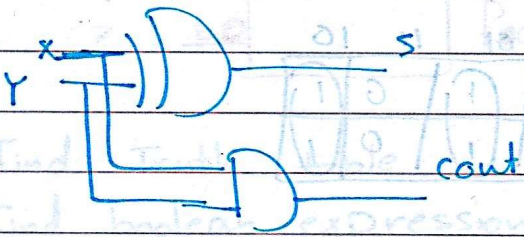

* Half Adder

Class 20

Full Adder.

Cin	X	Y	Count	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S →



Cin \ XY	00	01	10	11
0	0	1	0	1
1	1	0	1	1

$$S = C_{in} \bar{x} \bar{y} + C_{in} x y + \bar{C}_{in} \bar{x} y + \bar{C}_{in} x \bar{y}$$




Count →

Cin \ XY	00	01	10	11
0	0	0	1	0
1	0	1	1	1

$$Count = x y + C_{in} y + C_{in} x$$

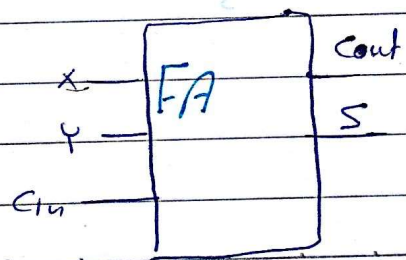
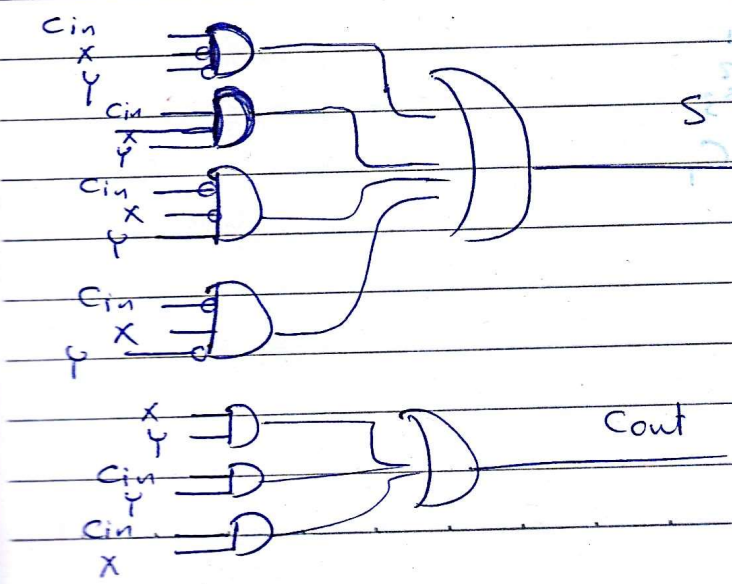


Ex)

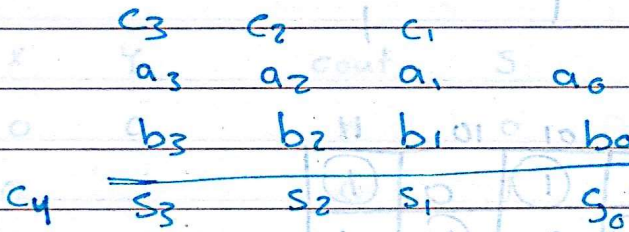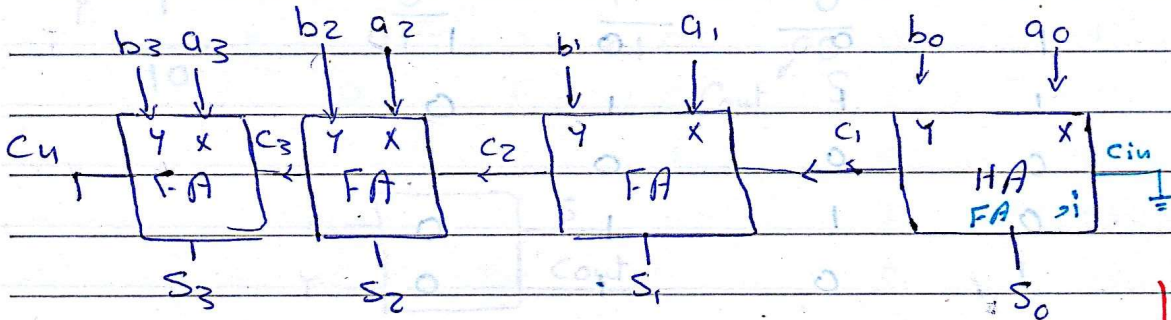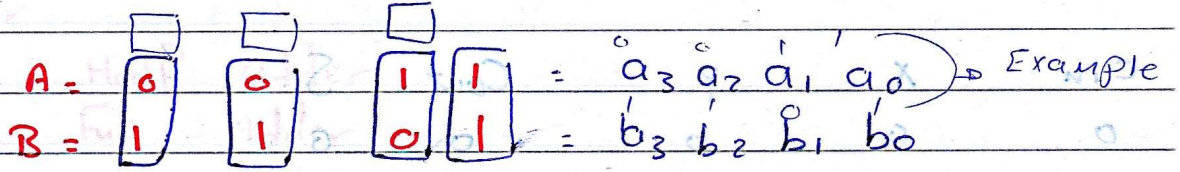

Binary Ripple Carry Adder

4 bit Adder

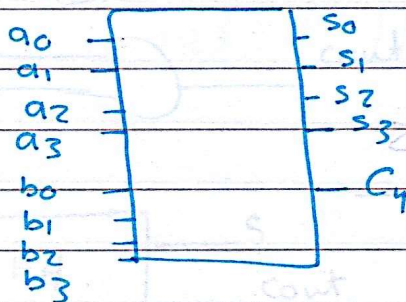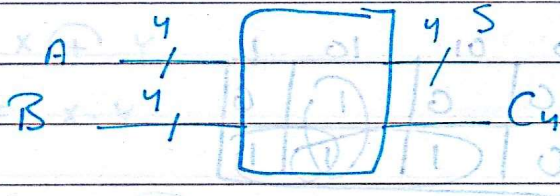

2

two

"Class 21"

Carry Look ahead adder

- Subtractor
- Add/sub.

$$S_1 = a_1 \oplus b_1 \oplus C_1 = a_1 \bar{b}_1 \bar{C}_1 + a_1 b_1 C_1 + \bar{a}_1 b_1 C_1 + \bar{a}_1 \bar{b}_1 \bar{C}_1$$

$$C_1 = a_0 \cdot b_0$$

$$S_1 = \bar{a}_1 \bar{b}_1 \bar{a}_0 b_0 + a_1 b_1 a_0 b_0 + \bar{a}_1 \bar{b}_1 a_0 b_0 + \bar{a}_1 b_1 \bar{a}_0 b_0$$

$$C_2 = a_1 b_1 + a_1 C_1 + b_1 C_1$$

$$= a_1 b_1 + a_1 a_0 b_0 + b_1 a_0 b_0$$

- Subtractor 2's

$$A - B = A + (-B)$$

Ex) $A = 1010$

$B = 0011$


$$\begin{array}{r} 1100 \\ + \\ 1101 \\ \hline \end{array}$$

2's

$$A - B = A + \bar{B}$$

$$\begin{array}{r} 0011 \\ \downarrow \downarrow \downarrow \downarrow \\ 1100 \end{array}$$

$$1010 +$$

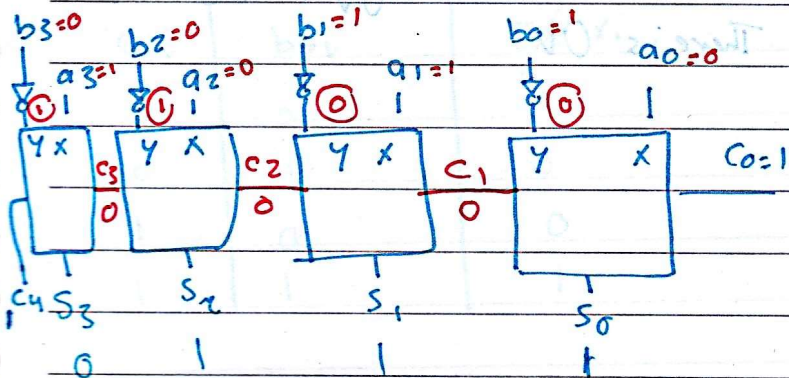


class 21
 Add / Sub

I need one control signal

$M=0 \Rightarrow$ Addition

$M=1 \Rightarrow$ Sub

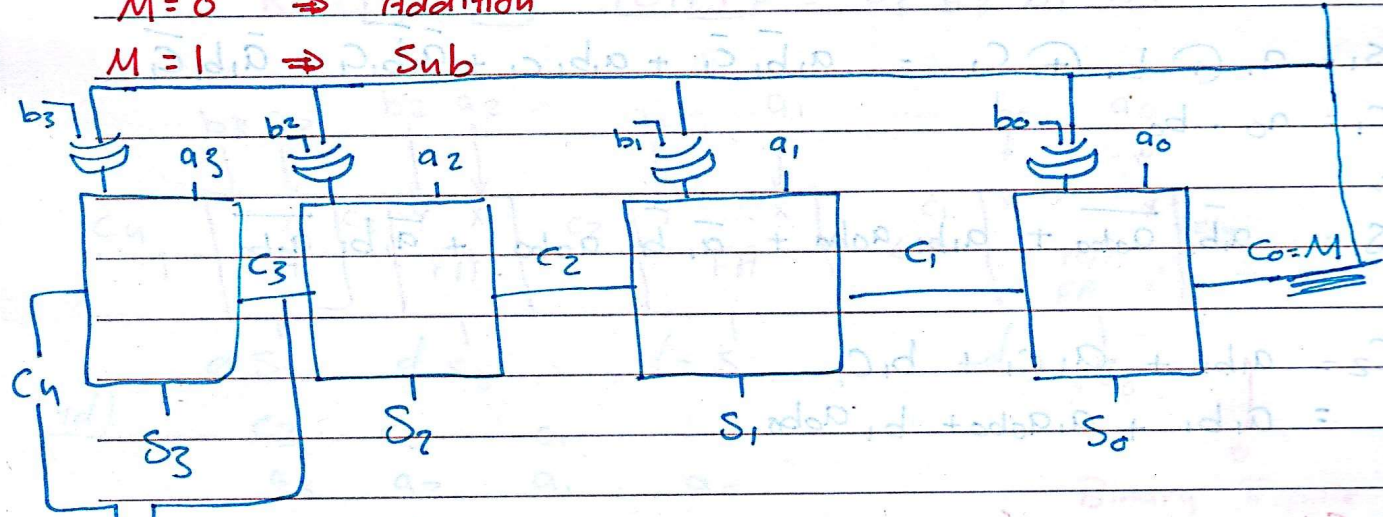

	M	b_i	b_i^*
OV	0	0	0
	0	1	1
	1	0	1
	1	1	0

$b_i^* = M \oplus b_i$

P for	OV \rightarrow
C_3	C_4
0	0
0	1
1	0
1	1

no OV
 There is OV

$OV = C_3 \oplus C_4$

class 21

Ex) $M=1$, $A=1011$, $B=0001$ find $S=?$

$C_4=??$

$OV=??$


$A + (-B)$

$$\begin{array}{r} 1 \quad 1 \quad 1 \quad 1 \\ 1 \quad 0 \quad 1 \quad 1 \\ \underline{1 \quad 1 \quad 1 \quad 1} \quad + \\ 1 \quad 1 \quad 0 \quad 0 \quad 1 \quad 0 \end{array}$$


$S = 1010$

$C_4 = 1$


$OV = 0$

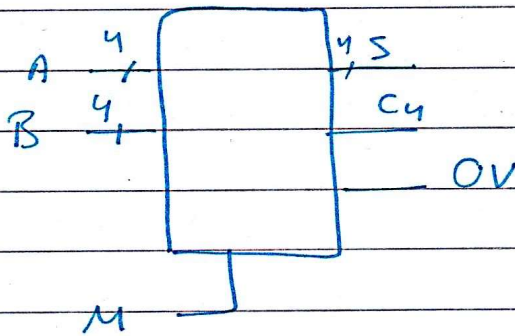


Magnitude Comperator

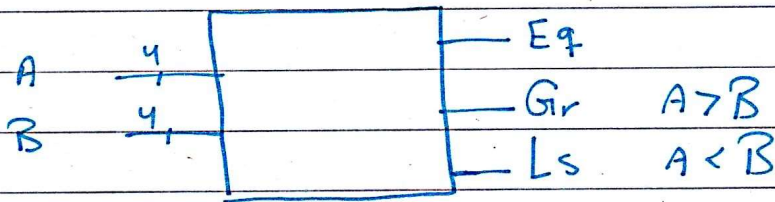

a_i	b_i	$Eq \quad x_i$
0	0	1
0	1	0
1	0	0
1	1	1

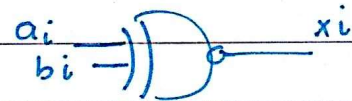

Magnitude Comparator

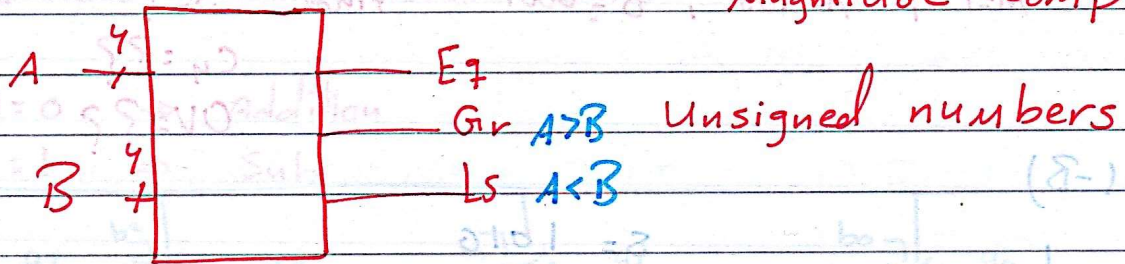


$$A = a_3 a_2 a_1 a_0$$

$$B = b_3 b_2 b_1 b_0$$

a_i	b_i	x_i
0	0	1
0	1	0
1	0	0
1	1	1

$i = 0, 1, 2, 3$
 $x_i = a_i \oplus b_i$

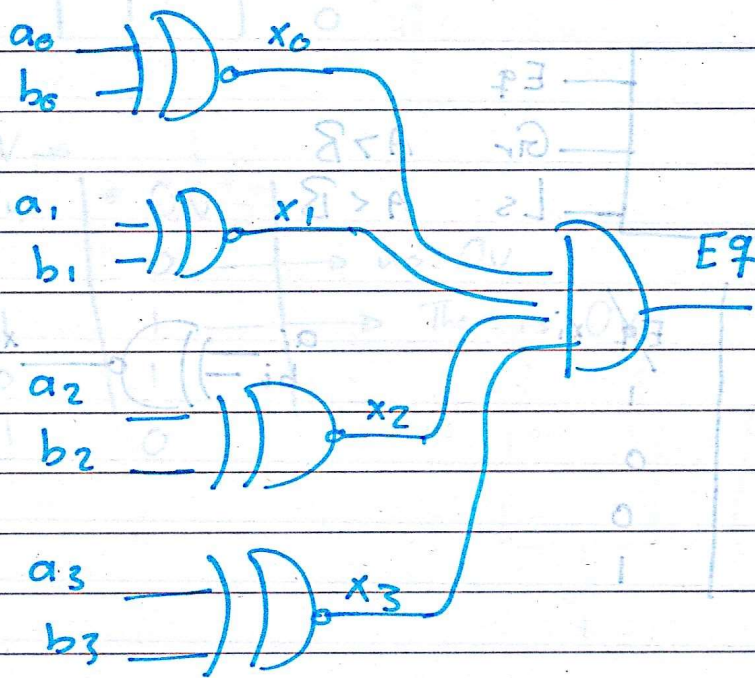

class 226

Ex) 2 bits numbers

$$A = 10 \quad G_r = 1$$

$$B = 00$$

$$\text{Ex) } A = 01$$

$$G_r = 0$$

$$B = 11$$

$$\text{Ex) } A = 11$$

$$G_r = 1$$

$$B = 10$$

$$\text{Ex) } A = 00$$

$$G_r = 0$$

$$B = 01$$

Boolean Expression

$$G_r = (a_3 \bar{b}_3) + (a_3 a_2 \bar{b}_2) + (x_3 x_2 a_1 \bar{b}_1) + (x_3 x_2 x_1 a_0 \bar{b}_0) \quad \text{SOP}$$

A > B

$$A = a_3 a_2 a_1 a_0$$

$$B = b_3 b_2 b_1 b_0$$

$$L_s = \bar{E}_g \cdot \bar{G}_r \quad A < B$$

Z	Y	X	Y	X
0	0	0	0	0
1	0	0	0	0
1	0	0	1	0
0	1	0	1	0
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1

PF
 Class 22

How to build FA From 2 HA


FA → $S = X \oplus Y \oplus C_{in}$
 $C_{out} = XY + XC_{in} + YC_{in}$ "FA"

HA → $S = X \oplus Y$
 $C_{out} = XY$

* Build FA From two half Adders

~~*/~~
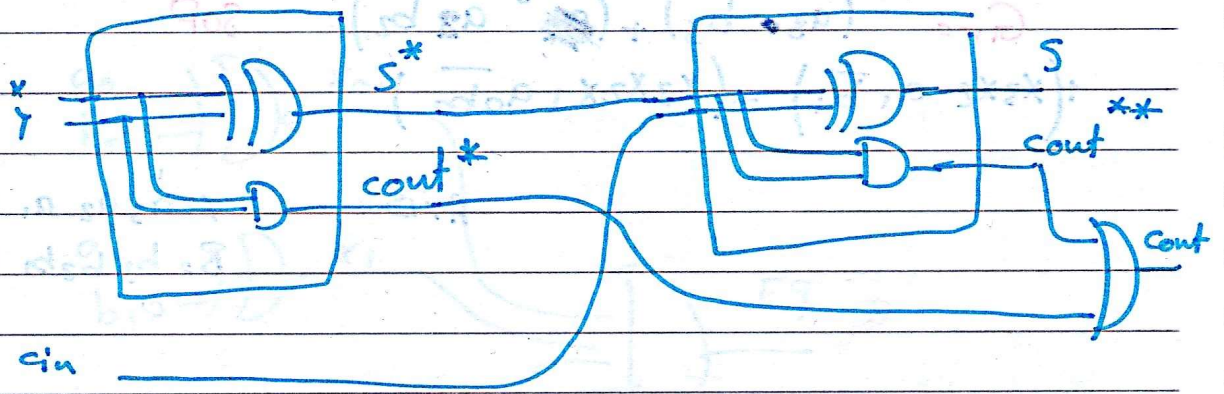
$$\begin{array}{r} X \\ + \\ Y \\ \hline S^* \\ + \\ C_{in} \\ \hline S \end{array}$$



X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

«class 23»

Decoder - Combinational circuit that convert a binary code to a binary value.

n - to - m Decoder

n: # of inputs, m = 2ⁿ (Max)

القسم الثاني

- Active high } decoder
 - Active low }


- without Enable }
 - with Enable }

- Enable active high }
 - Enable active low }


2 - to - 4 Decoder

Active - Low


Active high

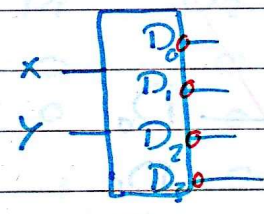

X	Y	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

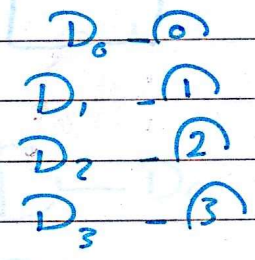

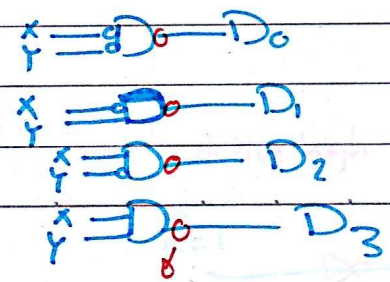$D_0 = \bar{X} \cdot \bar{Y}$, $D_1 = \bar{X} \cdot Y$, $D_2 = X \cdot \bar{Y}$, $D_3 = X \cdot Y$



Active high

bubbles in Active low

class 23,

Active Low

Active Low


X	Y	D ₀	D ₁	D ₂	D ₃
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

with enable active high 2 to 4

IF E=0 then decoder

→ inactive

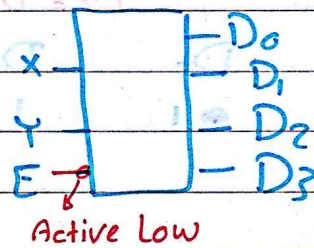
IF E=1 then decoder should work normally (active)



inactive decoder

E	X	Y	D ₀	D ₁	D ₂	D ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1


active decoder

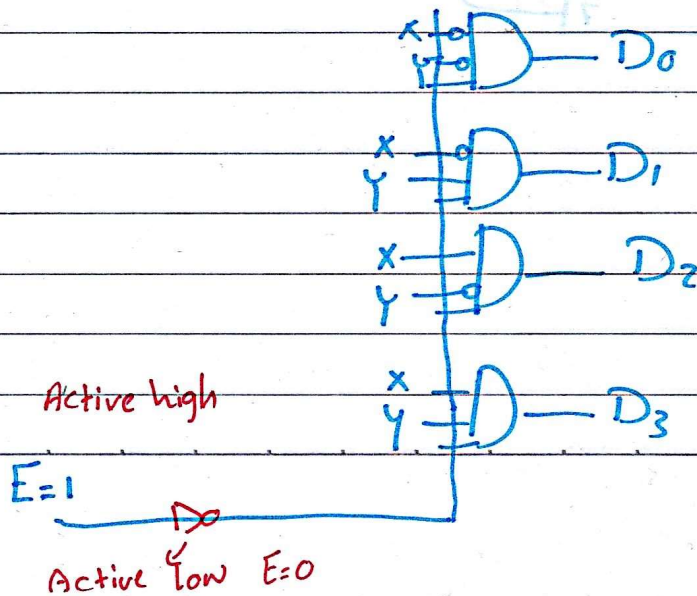

Class 23

Ex) IF $X=1, Y=0$

a) $E_1=1, E_2=1$

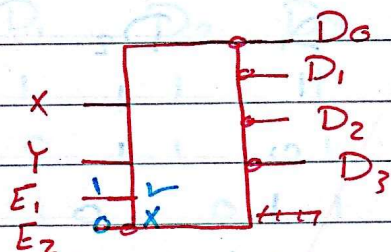


Find D_0, D_1, D_2, D_3 → inactive low

b) $E_1=1, E_2=0$ → active Low

X	Y	D_0	D_1	D_2	D_3
1	0	1	1	0	1

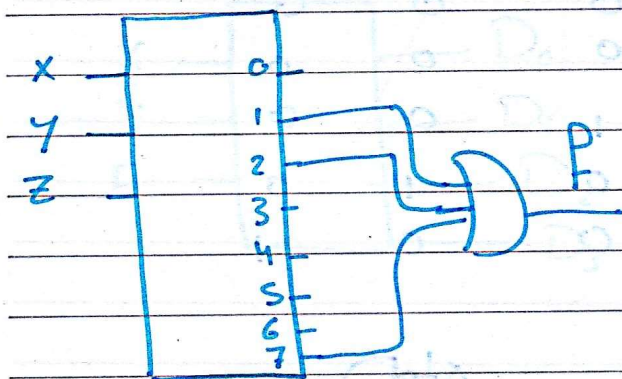
Ex) $F(x, y, z) = \sum(1, 2, 7)$ Use 3-to-8 Decoder



08
class 24



Ex) $S = \sum(1, 2, 4, 7)$ * represent Adder #
 $Count = \sum(3, 5, 6, 7)$ From decoder.

Cin	x	y	count	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1

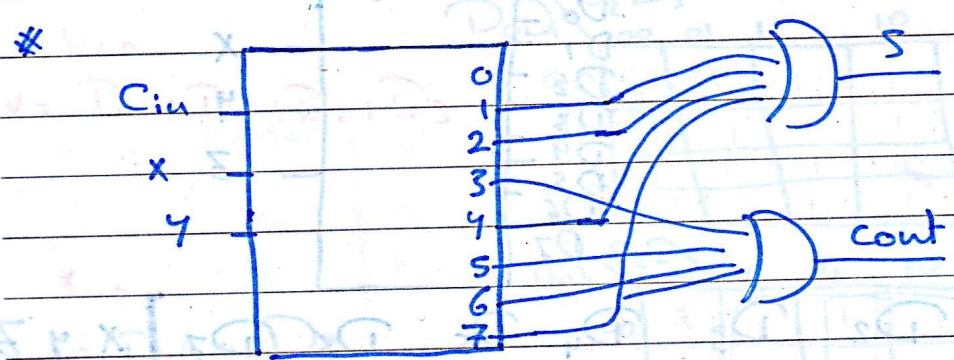

Ex) $F(x, y, z) = xy$ 3-to-8 Decoder

$F = xy\bar{z} + xyz$
 $F = \sum(6, 7)$

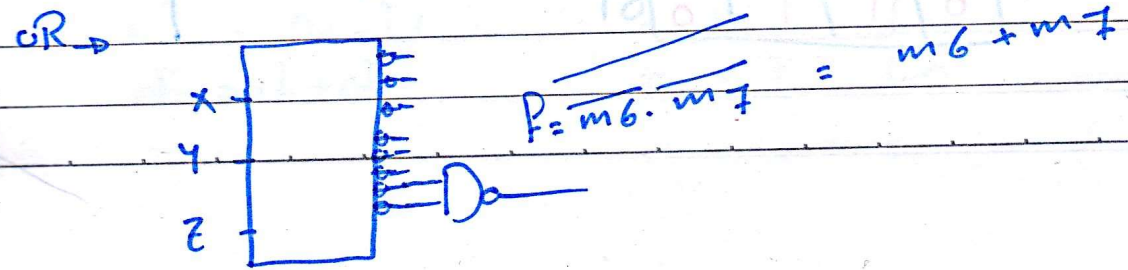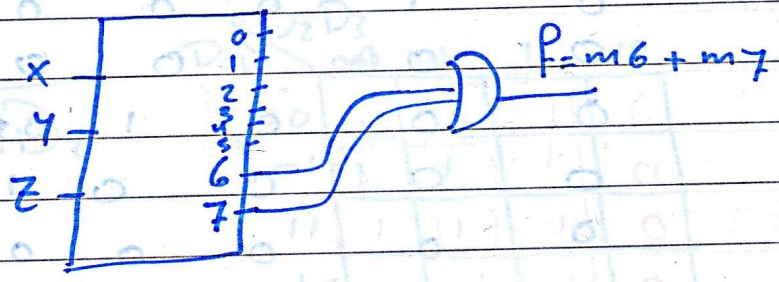


IF decoder active high
combine minterms using OR gates

IF decoder active low
Combine minterms using NAND gates

IF \bar{P} put inverter after P.

Encoder → A combinational circuit that converts a binary value to a binary code

M-to-n Encoder

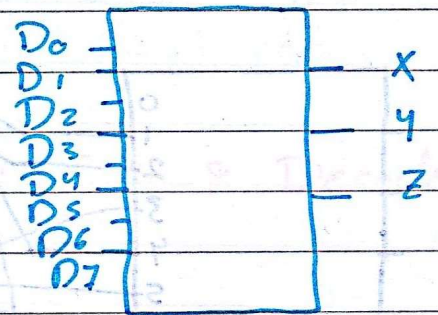

D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Class 24

$$X = D_4 + D_5 + D_6 + D_7$$

$$Y = D_3 + D_4 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

4 to 2 Encoder (Priority Encoder)

D_0	D_1	D_2	D_3	X	Y	V	Valid if $V=0$ then discard input (X, Y)
0	0	0	0	X	X	0	
1	0	0	0	0	0	1	(X, Y)
\bar{x}	1	0	0	0	1	1	
X	X	1	0	1	0	1	IF $V=1$ then take (X, Y)
X	X	X	1	1	1	1	

$V \rightarrow$
 $V = D_0 + D_1 + D_2 + D_3$

$D_0 D_1$	$D_2 D_3$	00	01	11	10
00	0	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1


$X \rightarrow$
 $X = D_2 + D_3$

$D_0 D_1$	$D_2 D_3$	00	01	11	10
00	X	1	1	1	1
01	0	1	1	1	1
11	0	1	1	1	1
10	0	1	1	1	1

$Y \rightarrow$
 $Y = D_3 + D_1 \bar{D}_2$


$D_0 D_1$	$D_2 D_3$	00	01	11	10
00	X	1	1	1	0
01	1	1	1	1	0
11	1	1	1	1	0
10	0	1	1	1	0

18
"Class 24"

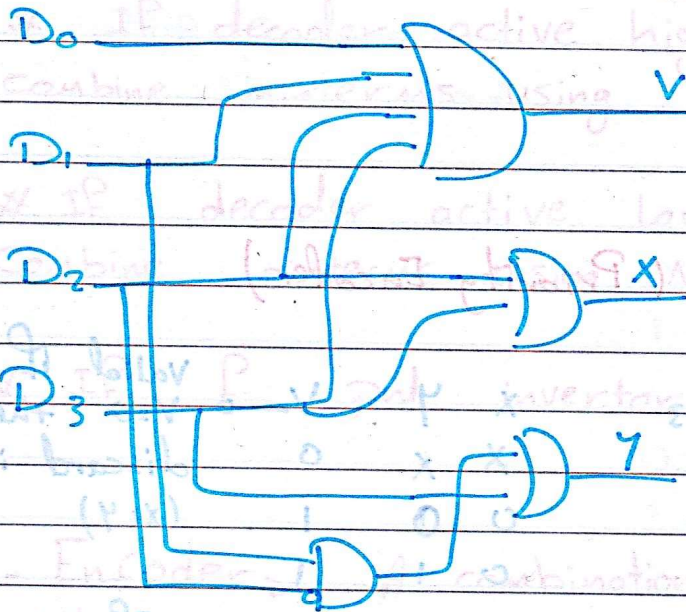


Multiplexers (MUX)

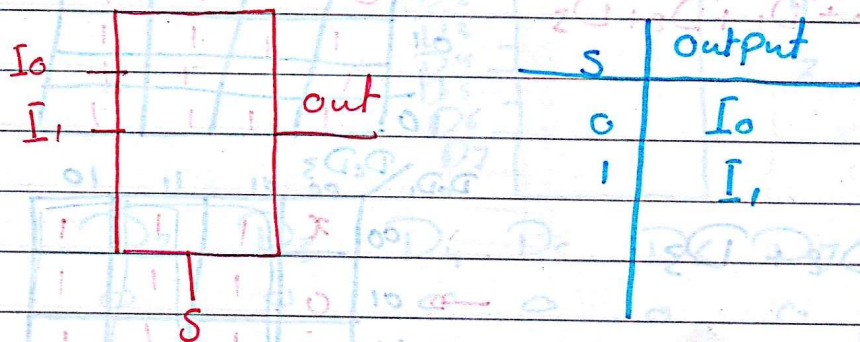Combinational circuit that selects one of the input to be directed to the Output.



$I_0 = f(x, y, z)$

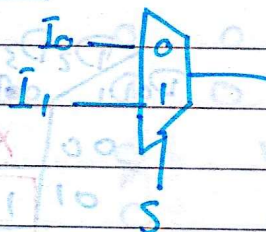


$Out = \bar{S} I_0 + S I_1$

$S=0 \rightarrow out = 0 I_0 + 0 I_1 = 1 I_0 + 0 = I_0$

$S=1 \rightarrow out = 1 I_0 + 1 I_1 = 0 I_0 + I_1 = I_1$


class 25

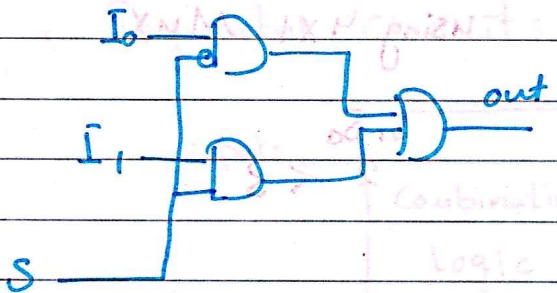

2x1 MUX

* 4x1 MUX

S_1	S_0	output
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

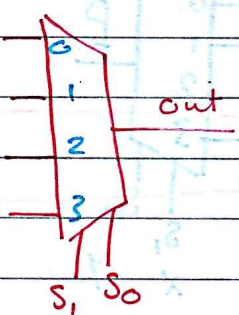

Select One input

$$out = \frac{\bar{S}_1 \bar{S}_0}{m_0} I_0 + \frac{\bar{S}_1 S_0}{m_1} I_1 + \frac{S_1 \bar{S}_0}{m_2} I_2 + \frac{S_1 S_0}{m_3} I_3$$


* How to use Mux to represent boolean function:

① If # of variables in the function = # of selector lines → Connect input to the select lines

② If # of variables > # of selector lines

Ex) $(x, y, z) \rightarrow Z$, use 8x1 MUX

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

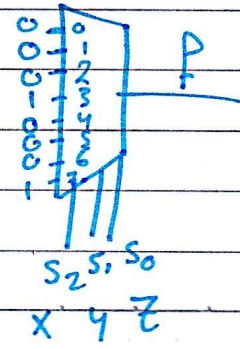

CLASS 25


Ex) given

	X	Y	Z	P
X ₄ =00	0	0	0	0
X ₄ =01	0	1	0	0
X ₄ =10	1	0	0	0
X ₄ =11	1	1	0	0

Using 4x1 Mux

S₁, S₀
2 < 3


For 2x1

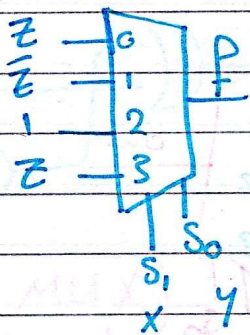



1) Connect MSB to the available Selector line

2) Write inputs as function of remaining variables.


Using 2x1 Mux

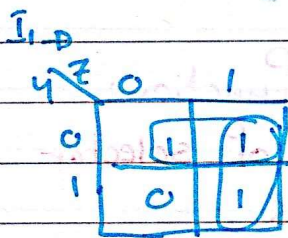


$P = \bar{Y}Z + Y\bar{Z} + YZ$

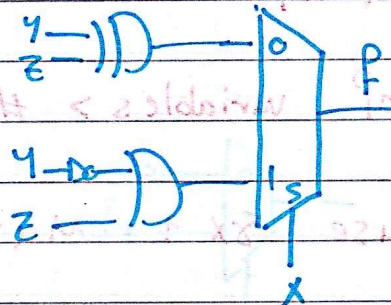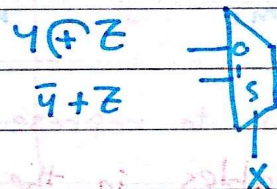


Sequential Circuits

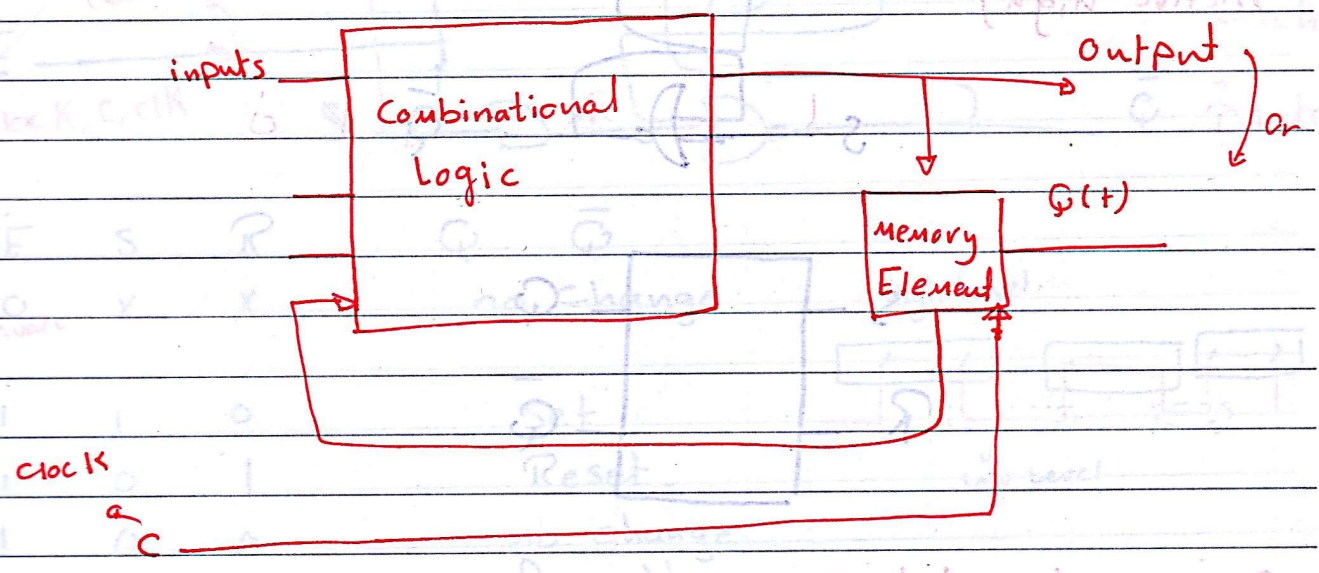

$Q(t)$	$Q(t+1)$
Current State	next state


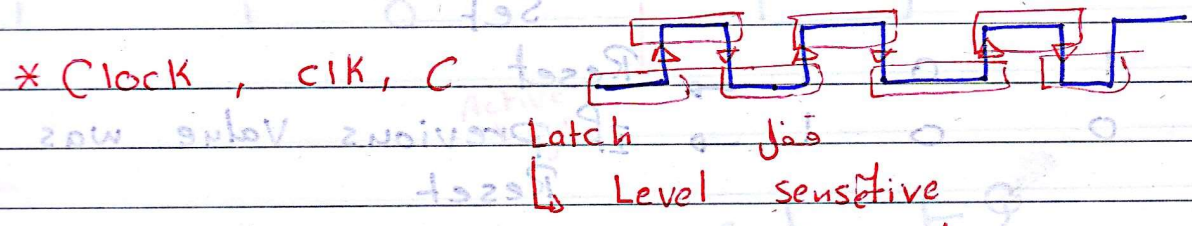


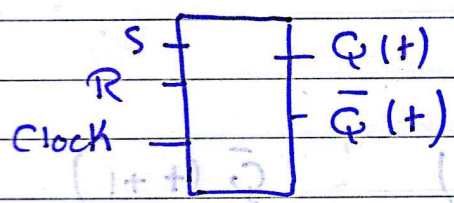Latch
Jas
Level sensitive
- High Level
- Low Level



Flip Flop
- +ve edge
- -ve edge

SR Latch
 (Active high)

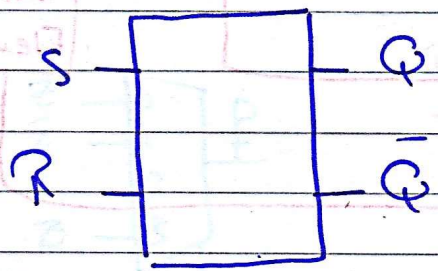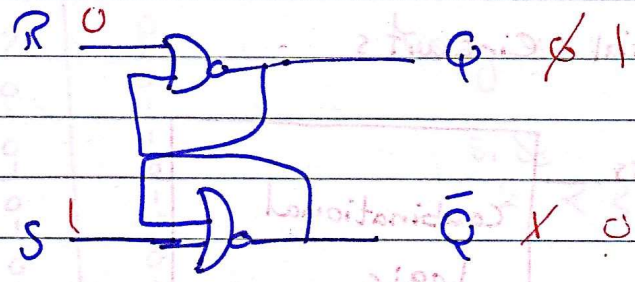


S: Set / 1 / high
 R: Reset / 0 / low

S	R	Q	Q̄	
Set ← 1	0	1	0	→ Set
no change ← 0	0	1	0	→ if previous value was Set
Reset ← 0	1	0	1	→ Reset
no change ← 0	0	0	1	→ if previous value was Reset
Forbidden cell	1	1	0	0


Ex) inputs

S	R	Q(t)	Q̄(t)	Q(t+1)	Q̄(t+1)
1	0	0	1	1	0
0	0	1	0	1	0

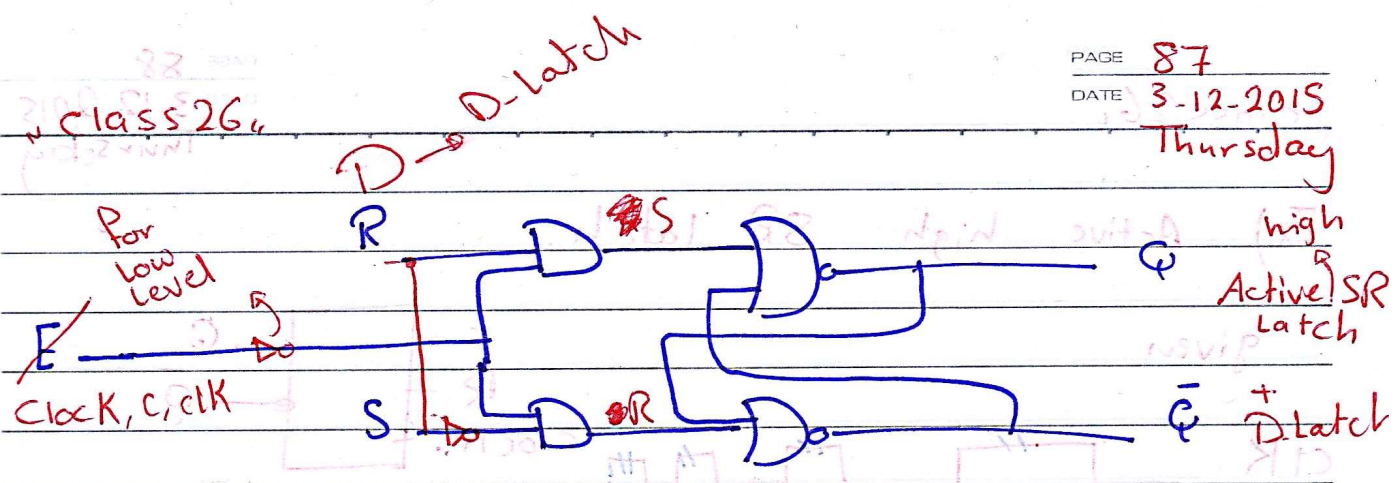


E	S	R	Q	Q̄
0 (deactivate)	x	x	no change	

1	1	0	Set	
1	0	1	Reset	
1	0	0	no change	
1	1	1	for bidden	

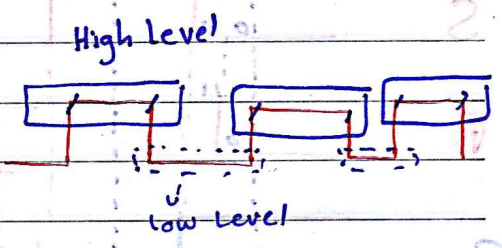


activate SR

D	Q(t)	Q̄
0	0	1
1	1	0

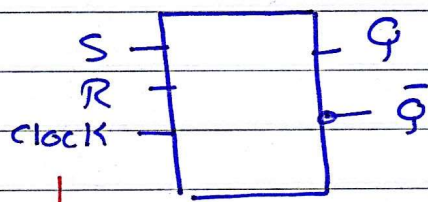



Active high

Active Low & CLK

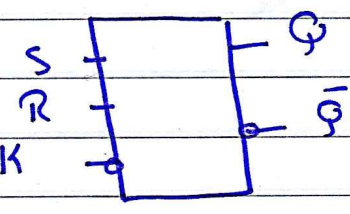

Active low SR latch




S	R	Q	Q̄
0 (set)	1	1	0 (if after set)
1 (no change)	1	1	0
1 (Reset)	0	0	1 (if after reset)
1 (no change)	0	0	1
0	0	for bidden	

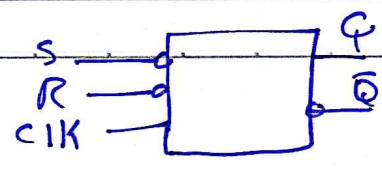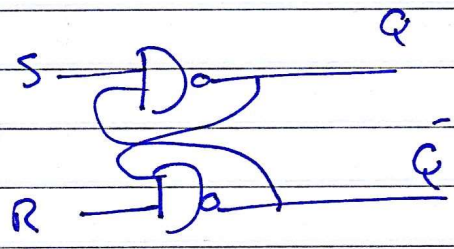



class 264

Ex) Active high SR latch.



given

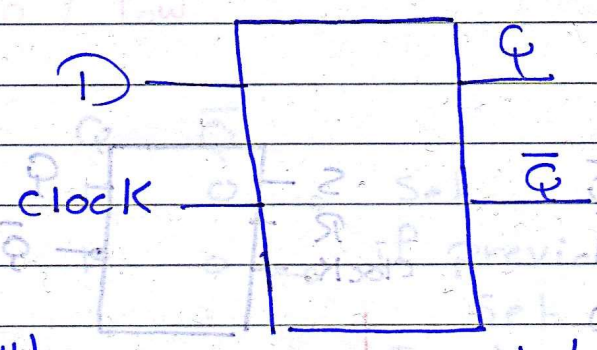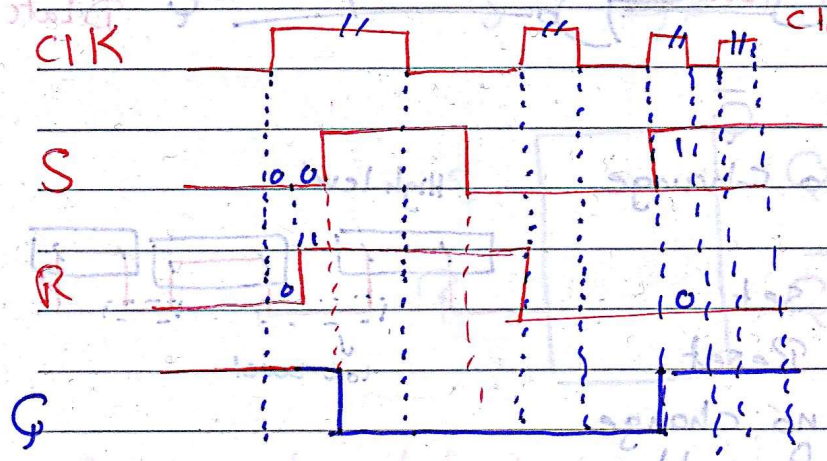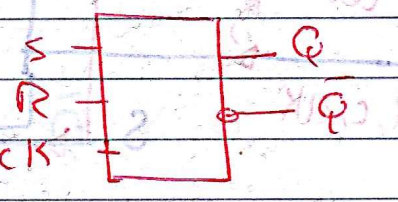

D	Q(+1)	Latch
0	0	transparent
1	1	

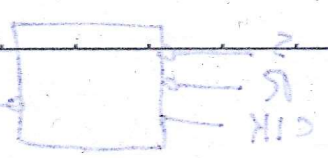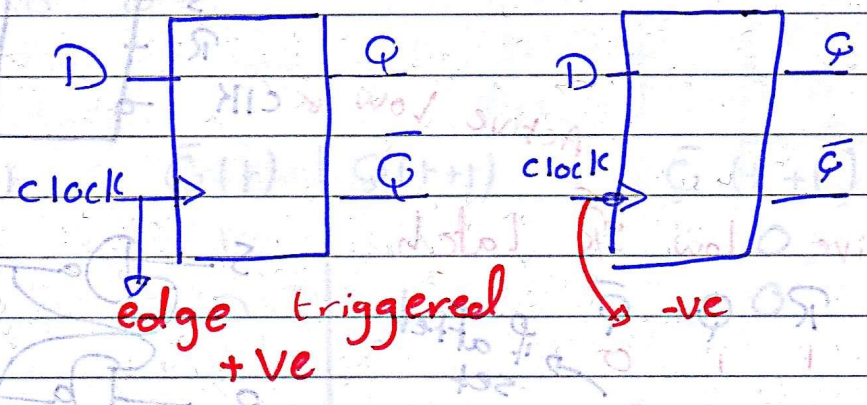

Class 27

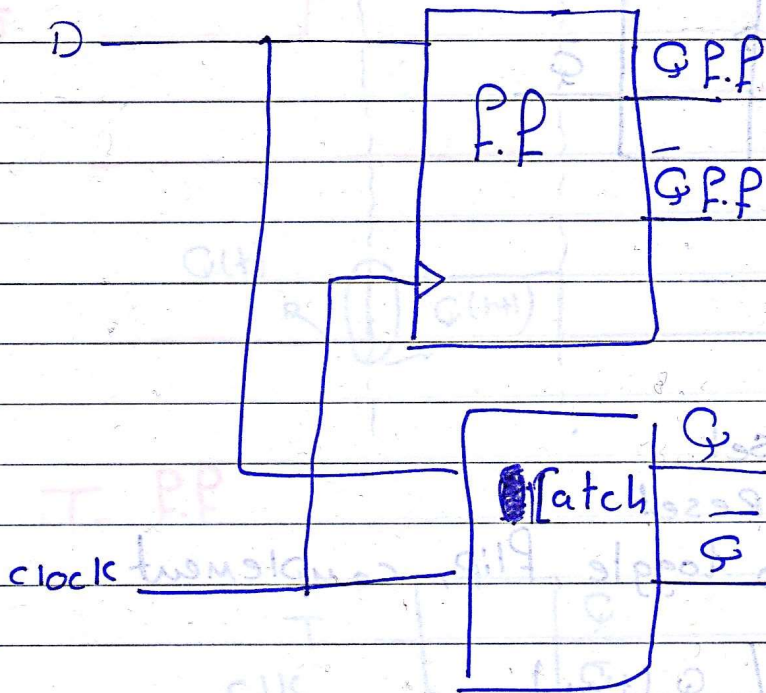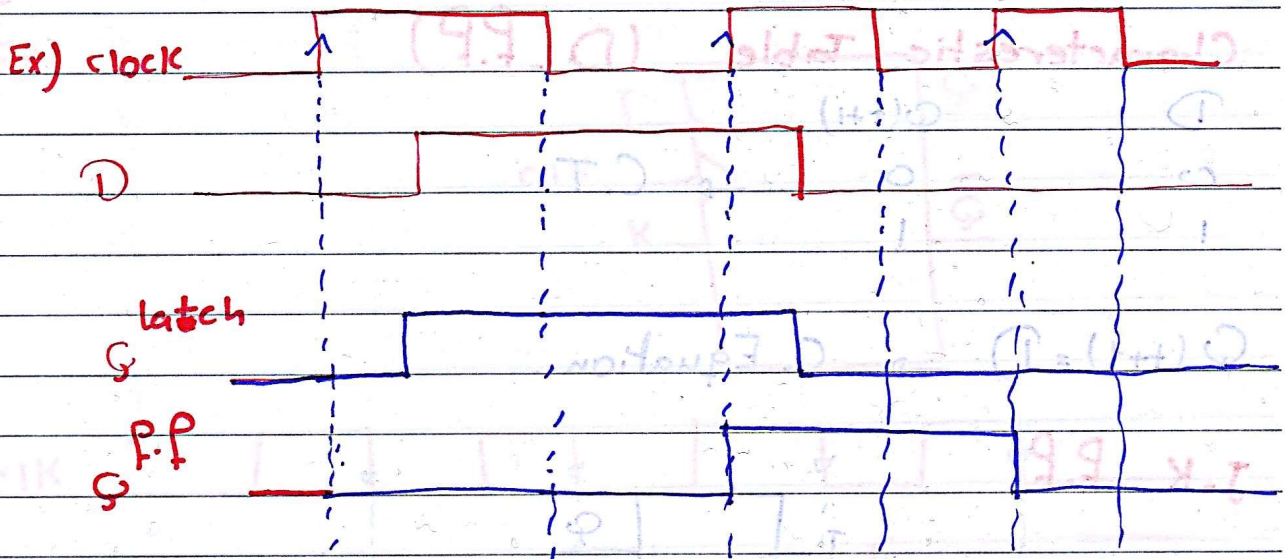

- Flip Flops → D.F.F.
JK.F.F.
T.F.F.

- ① Characteristic Flip Table
- ② Characteristic equation


Characteristic Table (D.P.F)

D	Q(t+1)
0	0
1	1

→ C.T

$Q(t+1) = D$ → C. Equation

J-K P.F

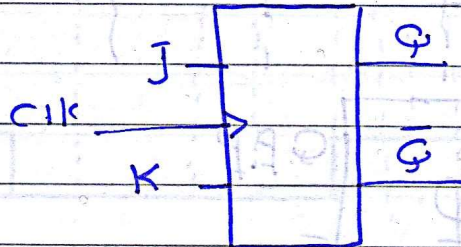


C. Table

J	K	Q(t+1)
0	0	Q(t)
1	0	1 → Set
0	1	0 → Reset
1	1	$\bar{Q}(t)$ → toggle, Flip, complement

no change

J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0



no change
Reset
Set
Toggle

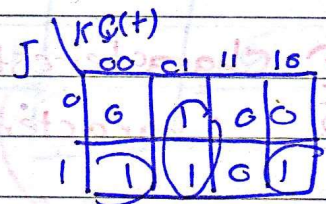


$Q(t+1) = \bar{K}Q(t) + J\bar{Q}(t)$

"class 27"

Ex)

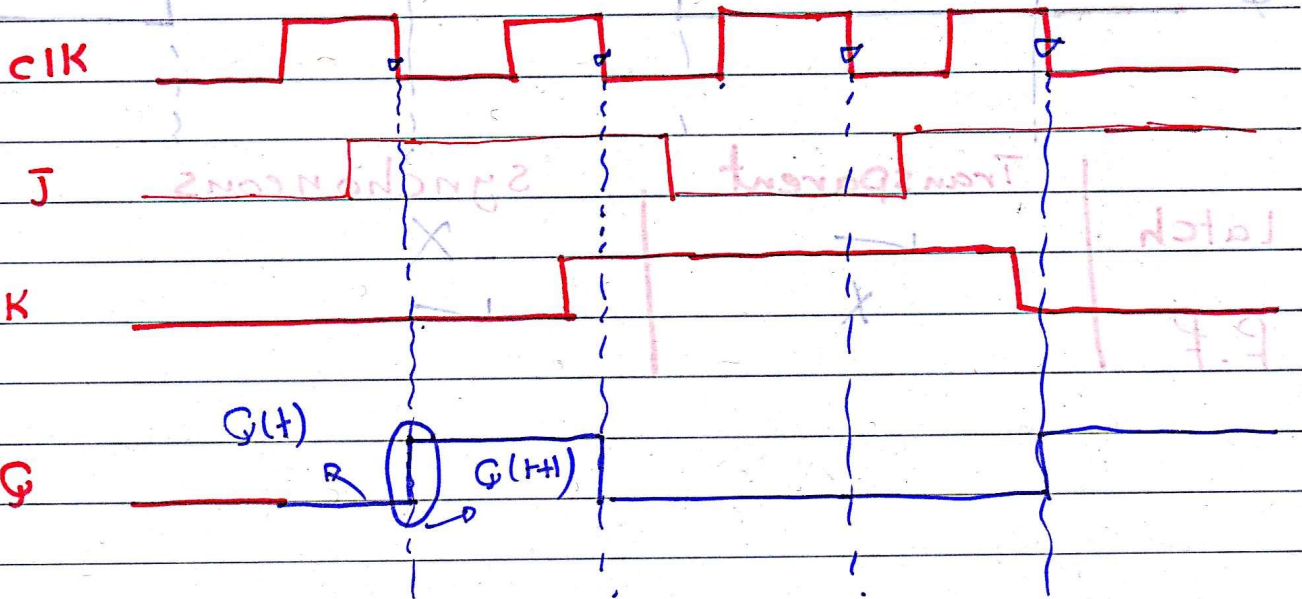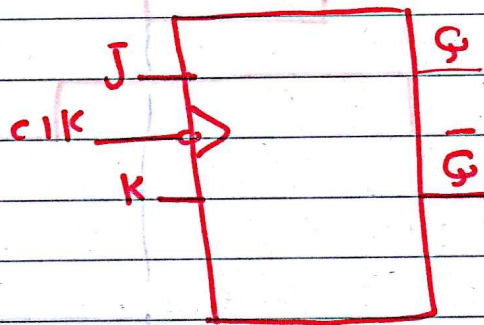

→ T. P.F

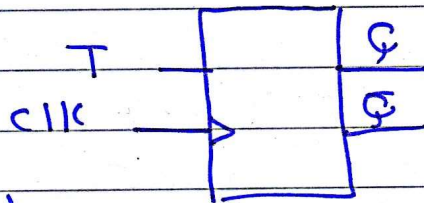


T	Q(t+1)
0	Q(t) → no change
1	$\bar{Q}(t)$ → Toggle

T	Q	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = T \oplus Q$$

$$= T\bar{Q} + \bar{T}Q$$

class 27

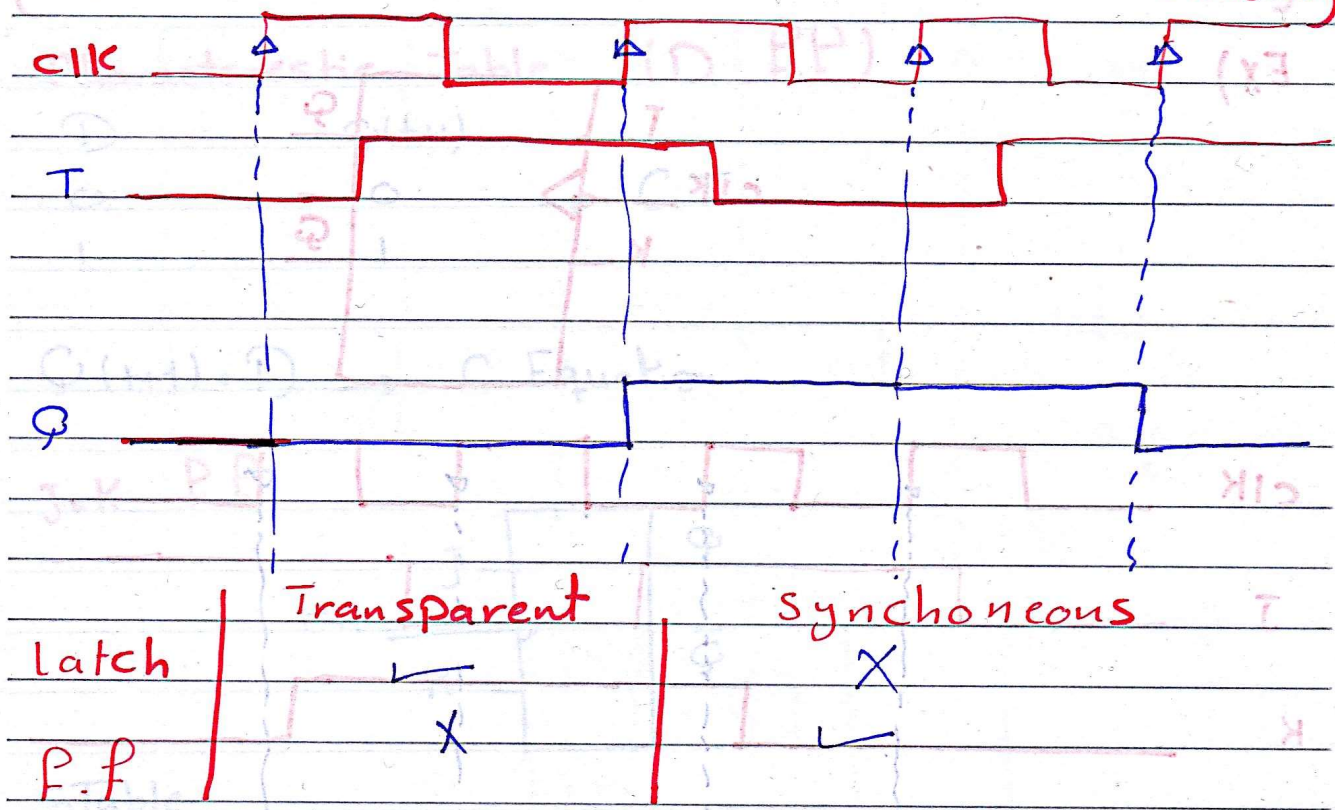

JK Flip-flop truth table and characteristic equation:


J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

no change (0,0) → Q(t+1) = Q(t)
 toggle (1,1) → Q(t+1) = $\bar{Q}(t)$
 set (0,0) → Q(t+1) = 1
 reset (1,1) → Q(t+1) = 0


Characteristic equation: $Q(t+1) = KQ(t) + J\bar{Q}(t)$

Class 28

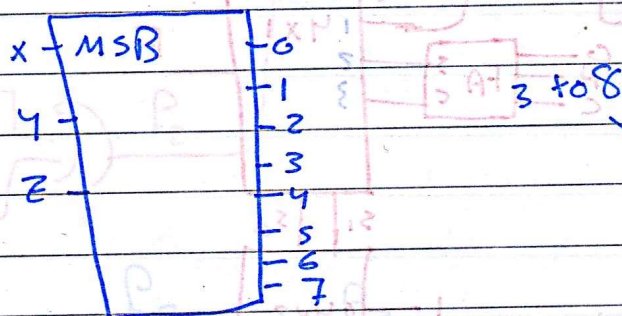Ex) Design 3 to 8 Decoder From 2 to 4 decoders with Enable.




X	Y	Z	D_0	D_1	D_2	D_3
MSB		LSB				
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	0	1

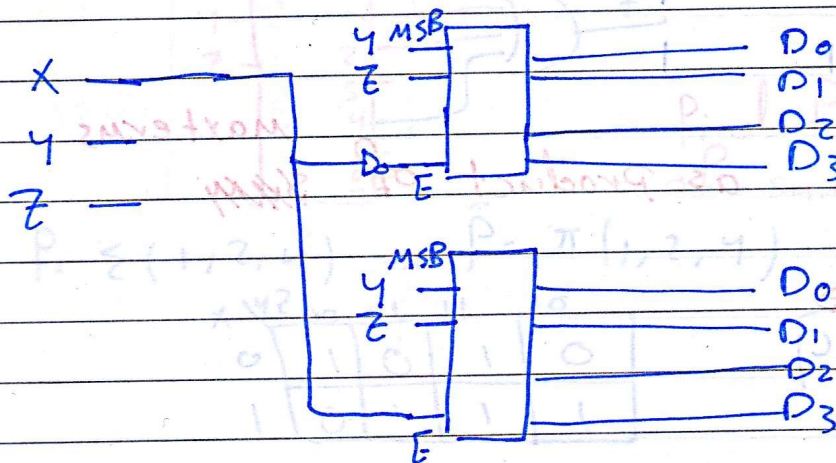

Class 28


Ex) write F as SOP

Sum of Minterms

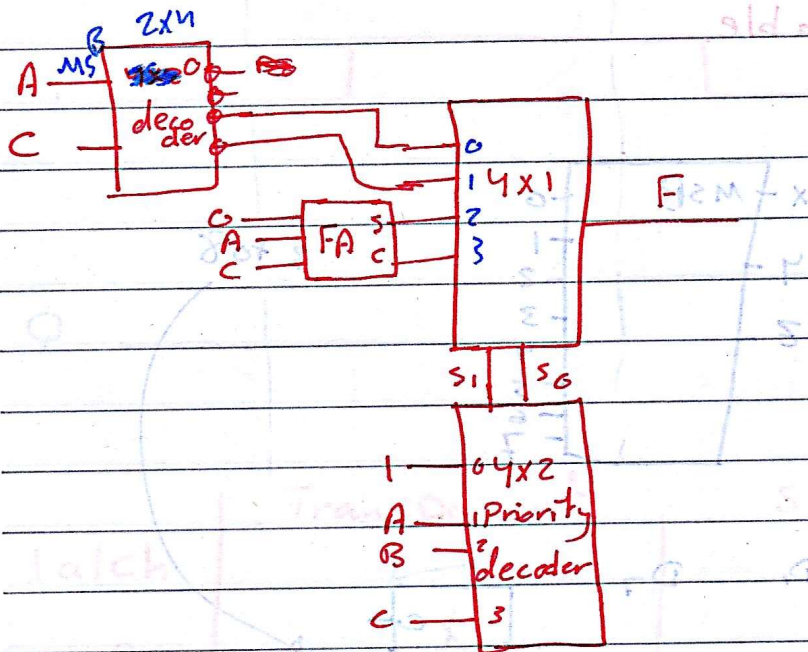


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Ex) Find F_3 as product of maxterms

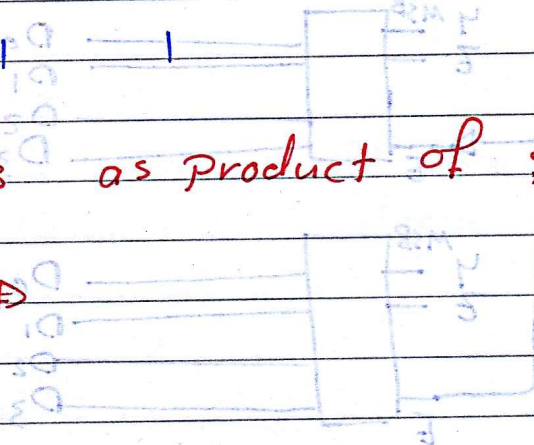


class 28

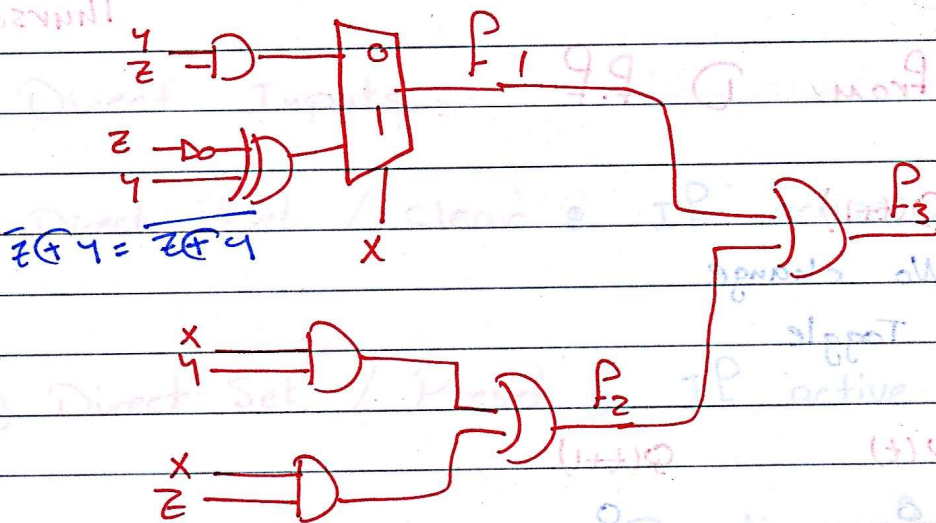

x	y	z	F ₁	F ₂	F ₃
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	1	0	1
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	1	1	1

$$F_3 = \pi(0, 1, 2)$$

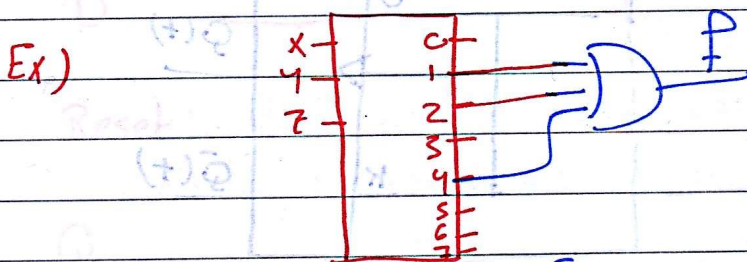

find \bar{F} as Product of sums (simplified)

$$F = \Sigma(1, 2, 4) \Rightarrow \bar{F} = \pi(1, 2, 4)$$

x \ yz	00	01	11	10
0	1	0	1	0
1	0	1	1	1

$$\bar{F} = (\bar{x} + y + z) \cdot (\bar{x} + \bar{y} + \bar{z}) \cdot (x + \bar{y} + \bar{z})$$


2P
 "Class 29"

T.P.P From D.P.P.

T $Q(t+1)$
 0 No change
 1 Toggle


T	$Q(t)$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

$Q(t+1) = Q \oplus T$
 $Q(t+1) = D$

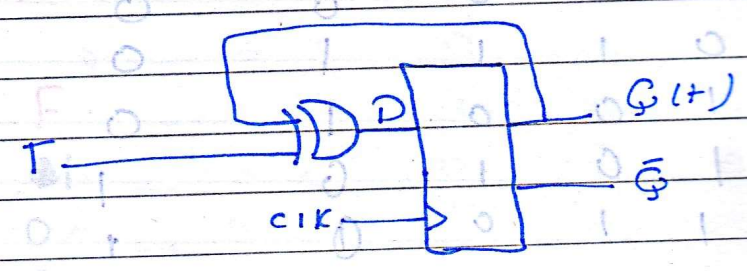

T.P.P From JK.P.P

T JK
 no change 0 0 0
 Toggle 1 1 1

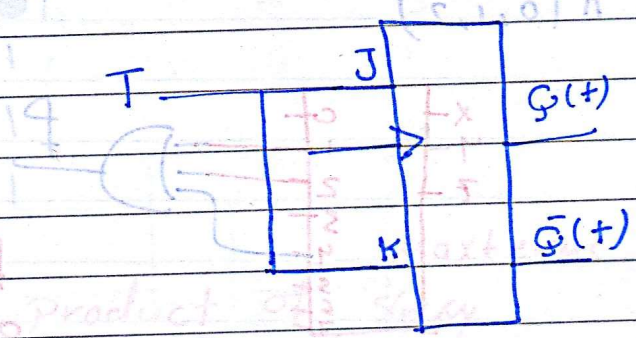

$Q(t+1) = J\bar{Q} + \bar{K}Q$
 $Q(t+1) = J\bar{Q} + \bar{K}Q$


0	1	0	1	0
1	1	1	0	1

Direct Inputs →

① Direct Reset / clear & IP active then $Q = 0$

② Direct Set / Preset & IP active then $Q = 1$


Regardless of the CLK.

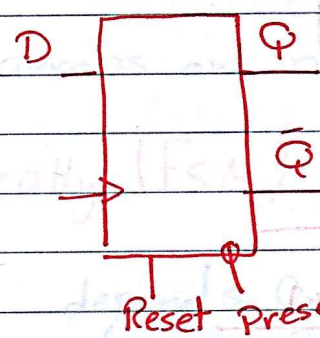

Reset	D	Q
1	X	0
0	0	0
0	1	1

Ex) D P.P


بیشترین سیگنال

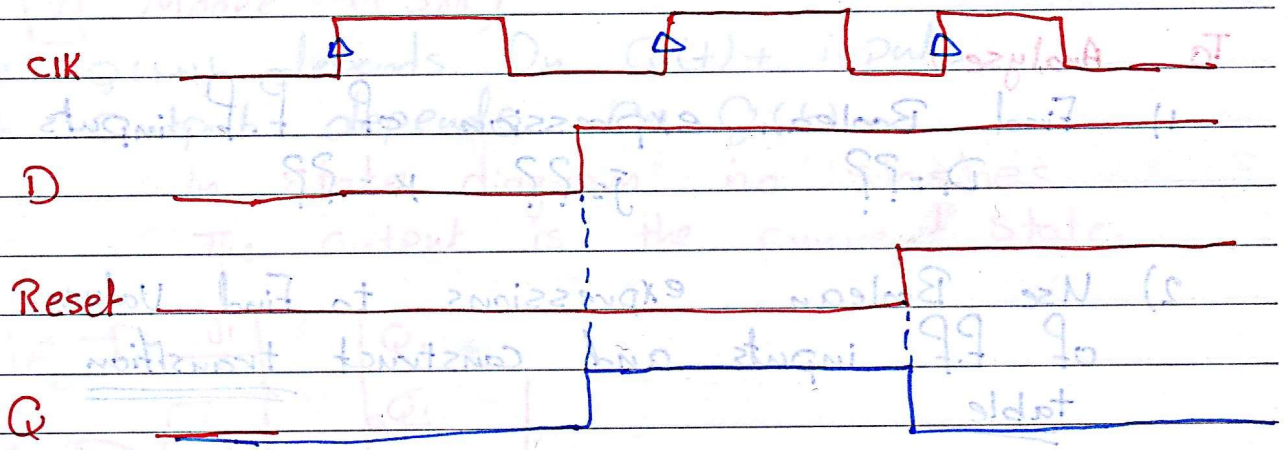

Active law

Preset	D	Q
0	X	1
1	0	0
1	1	1

Analysis of sequential circuits

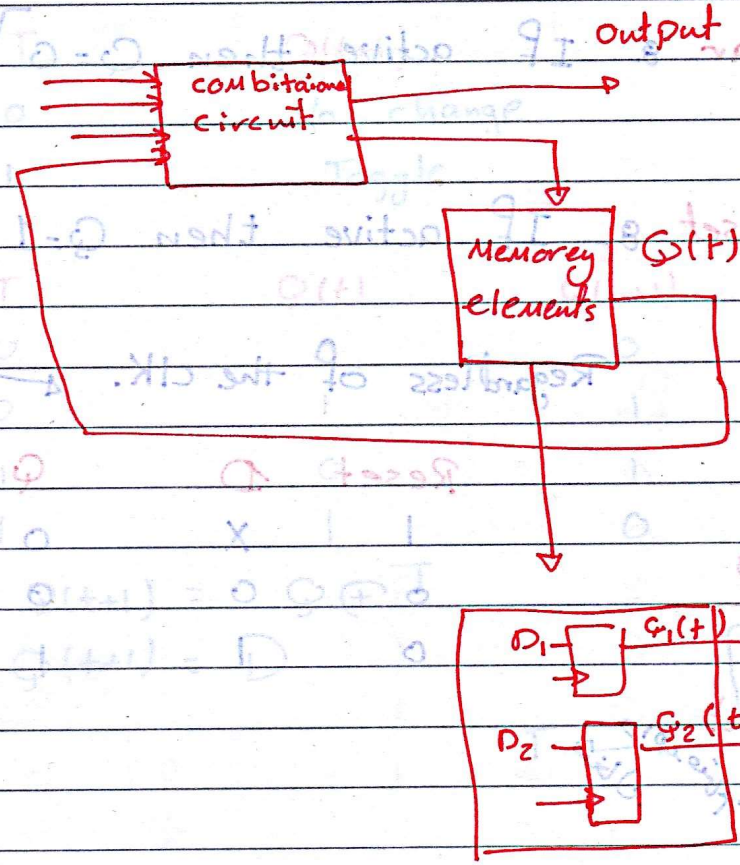

To Analyse:

1) Find Boolean expression of P.F inputs
 $D_1 = ??$ $J = ??$ $K = ??$

2) Use Boolean expressions to Find values of P.F inputs and construct transition table


Current state	# of P.F = M	inputs (external) n	nextstate	Output
<p># of rows = 2^{n+M}</p>				

Class 29

3. Find next state using Characteristic table or equation + Output.

Types of state diagrams

① Finite state Machine (FSM)

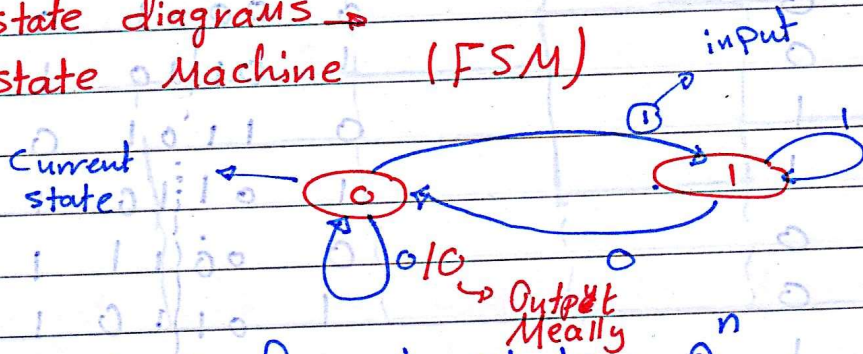

of arrows out of each state = 2^n
of states $\leq 2^M$


① Mealy (FSM)

$Q(t+1)$ depends on $Q(t) + \text{inputs}$
Output depends on $Q(t) + \text{inputs}$

② Moore (FSM)

* $Q(t+1)$ depends on $Q(t) + \text{inputs}$
* Output depends on $Q(t)$

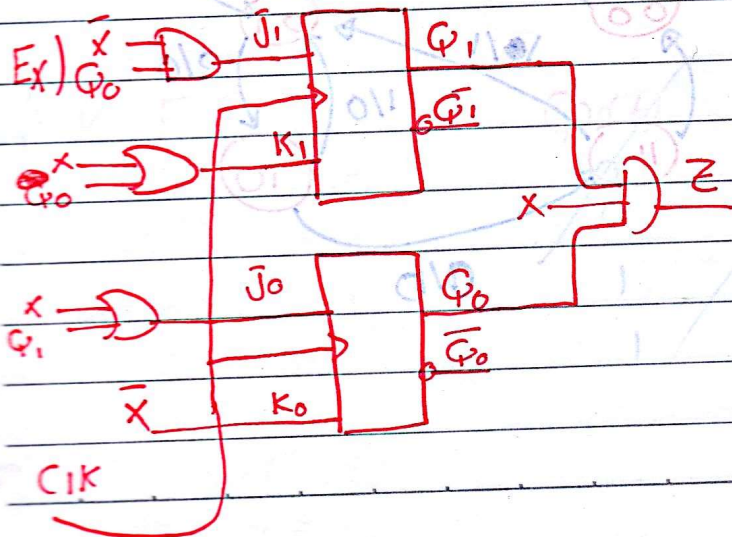in state diagram no slashes
The output is the current state.



next state

Current state Inputs

Q_1	Q_0	X	J_1, K_1	J_0, K_0	$Q_1(t+1)$	$Q_0(t+1)$	Z
0	0	0	0 0	0 0	0	0	0
0	0	1	0 1	1 0	1	0	0
0	1	0	1 1	0 1	0	1	0
0	1	1	0 1	1 0	1	0	0
1	0	0	0 0	1 1	1	1	0
1	0	1	0 1	1 0	1	0	0
1	1	0	1 1	1 0	0	0	0
1	1	1	0 1	1 0	0	1	1

$J_1 = \bar{x} \cdot Q_0$

$K_1 = x + Q_0$


$J_0 = x + Q_1$

$K_0 = \bar{x}$


JK $Q(t+1)$
 00 no change
 01 Reset
 10 set
 11 Toggle

$Z = x \cdot Q_1(t) \cdot Q_0(t)$

Q_1, Q_0

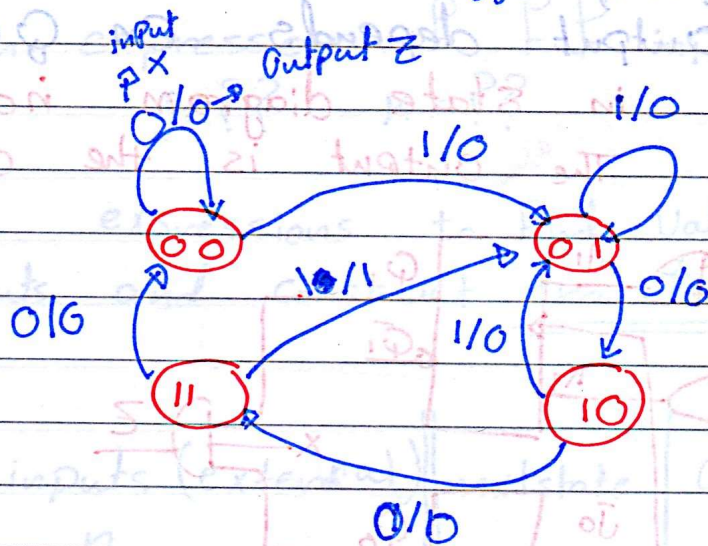

Class 30

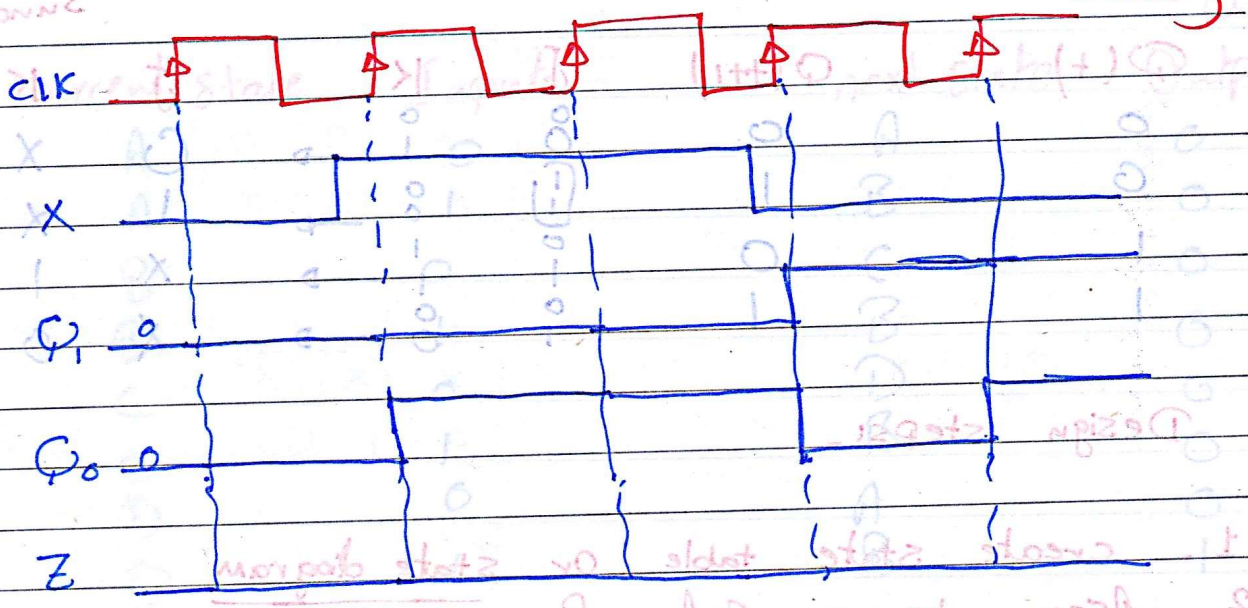

Excitation table

D, P, P	Q(t)	Q(t+1)	D = ?
0	0	0	0
0	0	1	1
1	0	0	0
1	0	1	1

T, F, F	Q(t)	Q(t+1)	T
0	0	0	0
0	0	1	1
1	0	0	0
1	0	1	1

J, K, F, F	Q(t)	Q(t+1)	J	K
0	0	0	0	0
0	0	1	1	0
1	0	0	0	1
1	0	1	1	0

no change

class 30

Q(+)	Q(++1)	J	K	J	K
0	0	0	0	0	X
0	1	0	0	1	X
1	0	0	1	X	1
1	1	0	0	X	0


Design steps

1. create state table or state diagram
2. Assign binary code for each state
I know # of P.F
3. Generate Find F.F Inputs From excitation table (value)
4. Find simplified expression of P.F inputs (K map)
5. Build the circuit.

Ex) Sequence Recognizer

input: 00001110010001
Output: 000000001000

Pattern = "1001"
Output = 1 (start end)

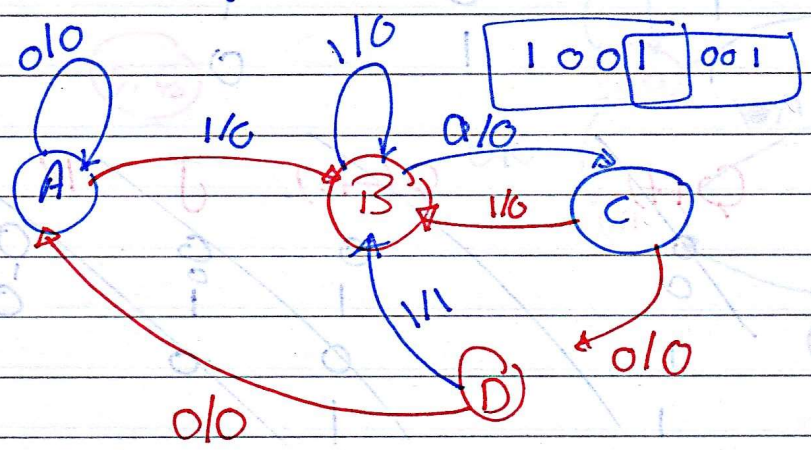

A: none of the desired pattern bits appeared. "0"
 B: We have already seen the first bit of the pattern
 C: Second bit of the pattern appeared
 D: Third bit of the pattern appeared

C. class 31,,

current state

Inputs

next state = Output

A
A
B
B
C
C
D
D0
1
0
1
0
1
0
1A
B
C
B
D
B
A
B0
0
0
0
0
0
0
1

	Q_1	Q_0
A	0	0
B	0	1
C	1	0
D	1	1

P.P Inputs

current state

Inputs J_K J_K next state

Output

 Q_1 Q_0

X

J_KJ_K Q_1 Q_0

Z

A	0	0	0	0X	0X	0	0	0
	0	0	1	0X	1X	0	1	0
B	0	1	0	1X	X1	1	0	0
	0	1	1	0X	X0	0	1	0
C	1	0	0	X0	1X	1	1	0
	1	0	1	X1	1X	0	1	0
D	1	1	0	X1	X1	0	0	0
	1	1	1	X1	X0	0	1	1

class 31,,

$$J_1 = Q_0 \bar{X}$$

	$Q_0 X$	00	01	11	10
Q_1	0	0	0	0	1
	1	X	X	X	X


$$K_1 = Q_0 + X$$

	$Q_0 X$	00	01	11	10
Q_1	0	X	X	X	X
	1	0	1	1	1

$$\bar{J}_0 = X + Q_1$$

	$Q_0 X$	00	01	11	10
Q_1	0				
	1				

$$K_0 = \bar{X}$$

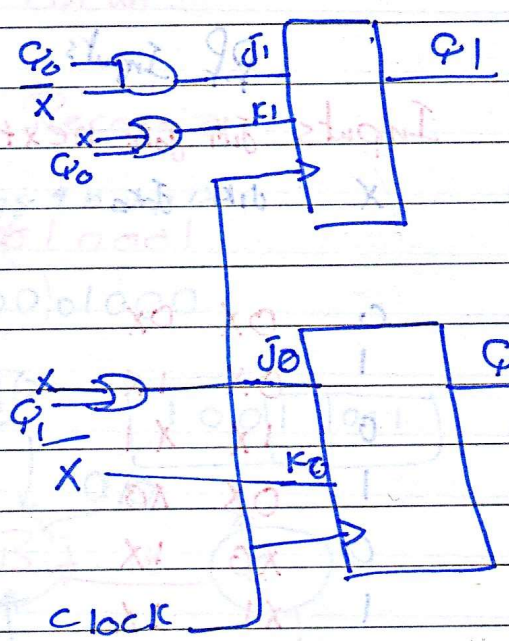


Current state "100"
 Output: 100
 Desired pattern 778
 appeared "00"
 Q0 & Q1 have played
 over the first
 bit of the input
 and second bit
 of the pattern
 appeared
 D. Third bit of
 the pattern
 appeared

Registers

Parallel in / Parallel Out
 4 bits Register.

Input
 1011
 ↓
 MSB

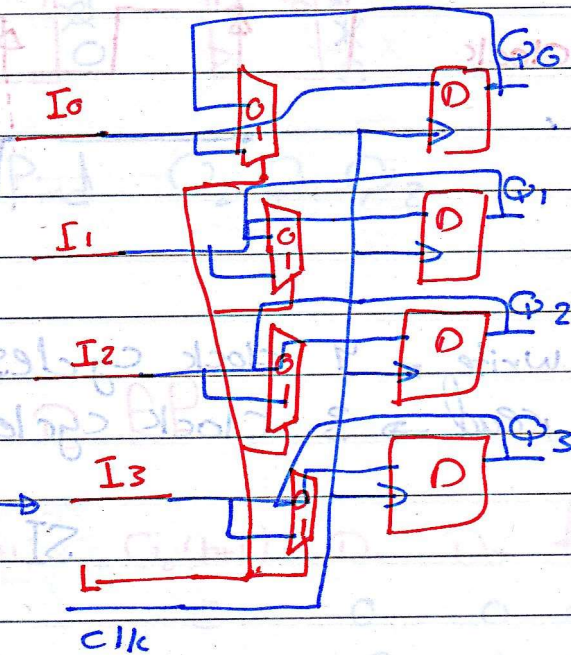


write → 1 clock cycle

read → 0 clock cycle

Selector →
 L


0 → no change

1 → load new data

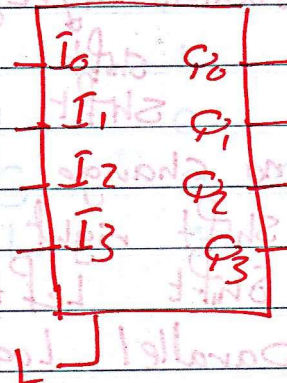


Serial in / Serial Out


1011
 ↓
 MSB

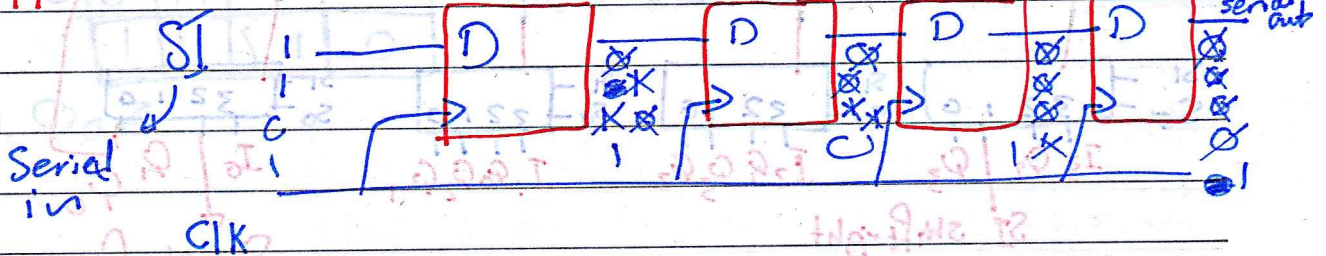

Registers

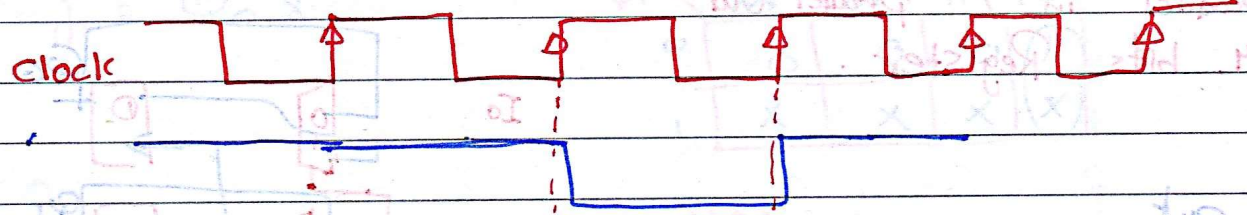

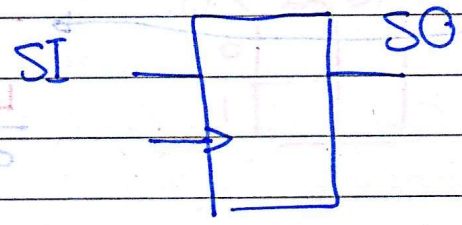
write → 4 clock cycles
read → 3 clock cycles



* Universal register

- 1) no change (same)
- 2) shift right
- 3) shift left
- 4) parallel load

S_1	S_0
0	0
0	1
1	0
1	1

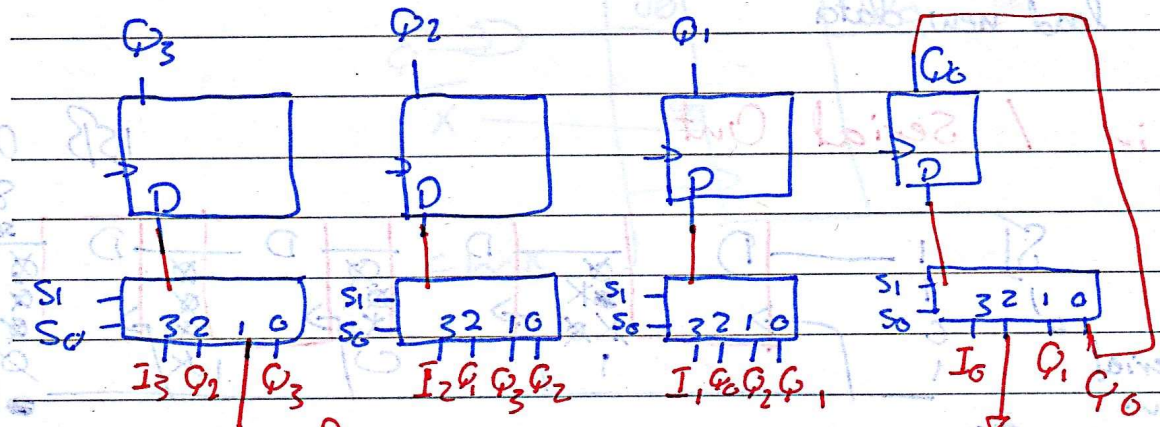


SI shift right
Parallel in (4)
Serial in shift left
Serial in shift right

SI shift left

Registers

Ex)

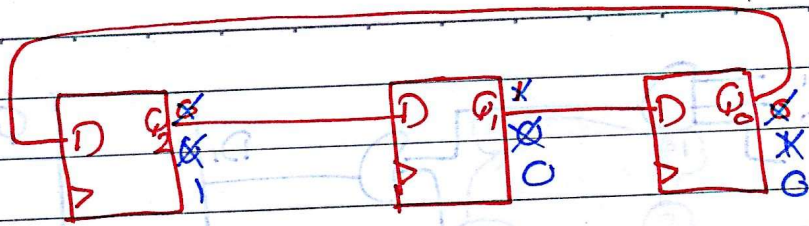

After 2 clock cycles Find Q_2, Q_1, Q_0

= 100

Ex) Designing pattern using D.F.F

Q_1	Q_0	x	$Q_1(t+1)$	$Q_0(t+1)$	D_1	D_0	F
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	0	1	0	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	0	0	1	1

$D_1 \rightarrow$

Q_1	Q_0	x		
0	0	0	0	1
1	1	0	0	0

$$D_1 = Q_1 \bar{Q}_0 \bar{x} + \bar{Q}_1 Q_0 \bar{x}$$


$D_0 \rightarrow$

Q_1	Q_0	x		
0	0	1	1	0
1	1	1	1	0


$$D_0 = x + Q_1 \bar{Q}_0$$

$$Z = Q_1 Q_0 Z$$

Class 32u

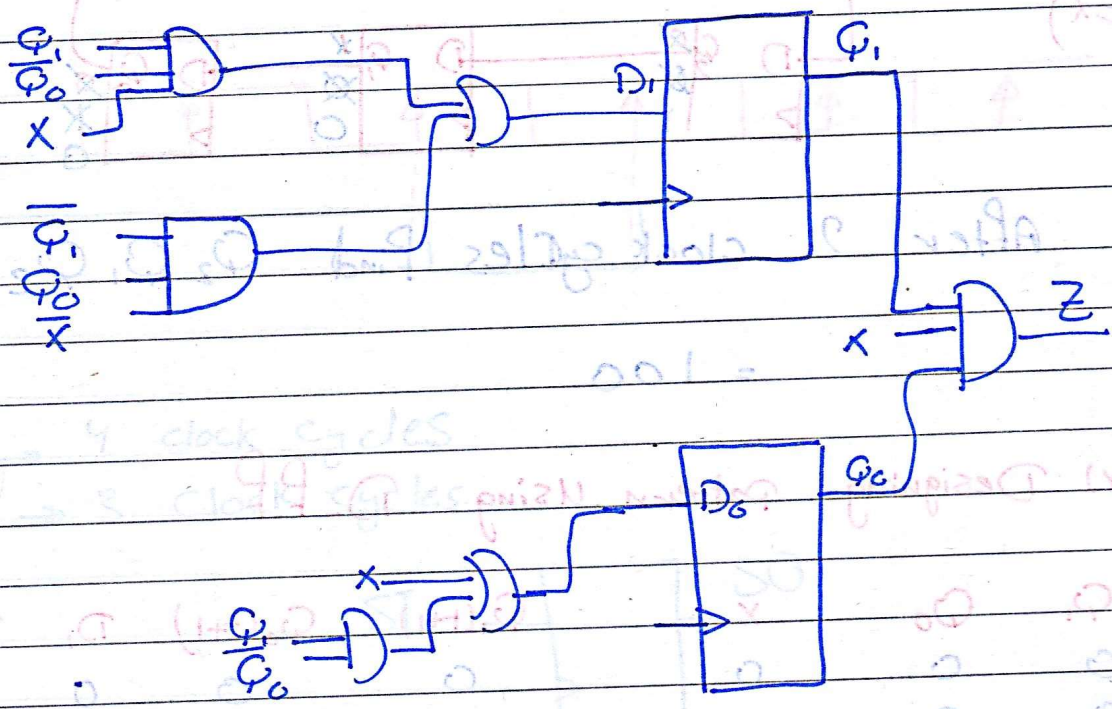

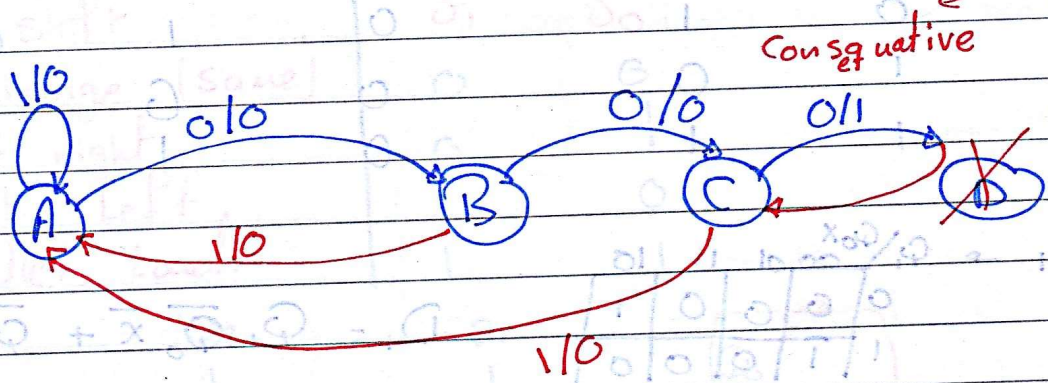Ex) Design A sequence detector that recognizes the occurrence of 3 or more Zero's




- A: I'm receiving 1's
- B: "0"
- C: "00"
- D: "000"


Parallel in (S)
 Serial in shift left
 Serial in shift right

Class 334


Ex) 0-3

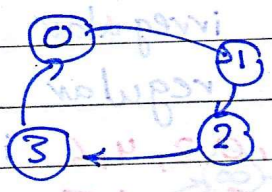

Moore.

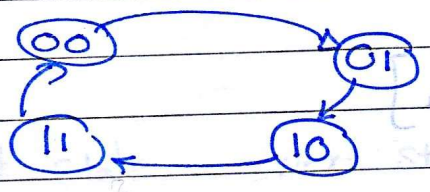

Types of counters:

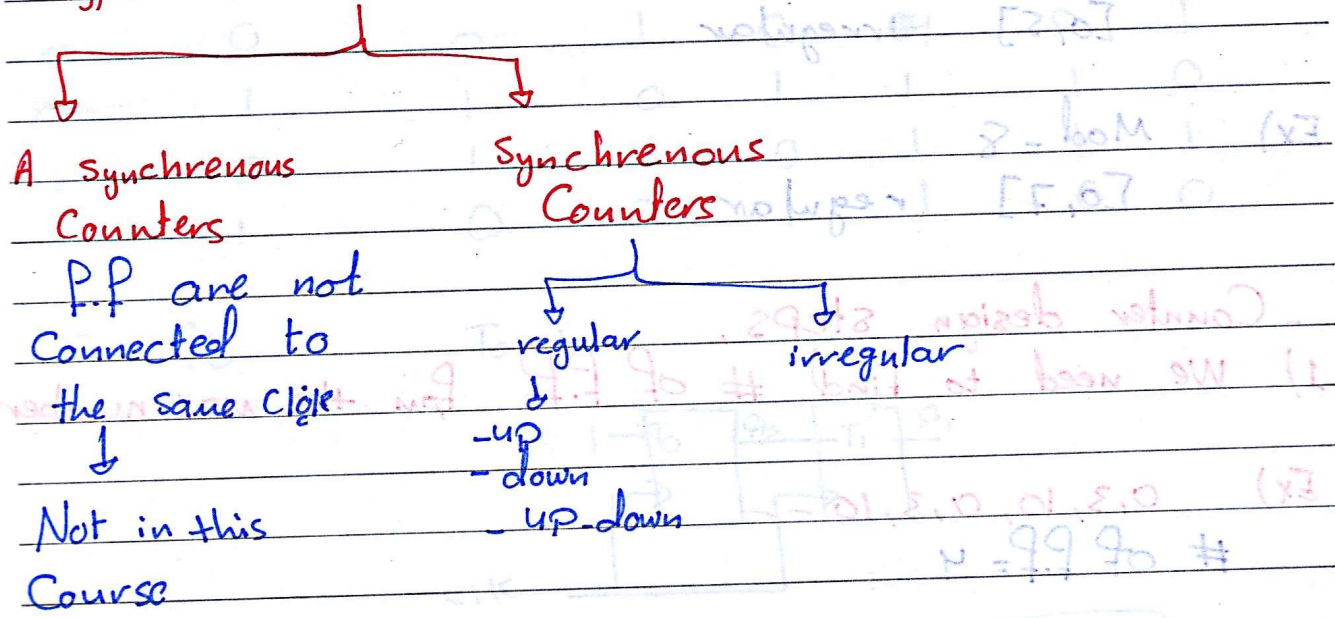

* Up Counter → initial state 0
 Final state $2^n - 1$ → $n = \# \text{ of P.F}$
 Step width 1
 next state = current state + 1

down Counter → initial state $2^n - 1$ → $n = \# \text{ of P.F}$
 Final state 0
 step width 1
 next state = current state - 1

up-down → x → counter behaviour
 0 → up
 1 → down

POI
class 32

- e.g) 0-4 irregular
- 0-7 regular
- 0, 2, 4, 6, 0, 2, 4, 6 irregular
- 0, 1, 2, 3, 5, 4, 6, 7, 0 irregular

* Modulus n } $[0, n-1]$
Mod n }

Ex) Mod 6
[0, 5] irregular

Ex) Mod 8
[0, 7] regular

Counter design steps,

1) We need to find # of P.F for the max number

Ex) 0, 3, 10, 0, 3, 10 --
of P.F = 4

Ex) (7, 0) # of P.F = 3

2) Determine P.F Type

T, JK

3) Determine if P.F are positive or negative edge


4) Determine the initial state and the final state of the P.F.

C class 33

e.g) 0.3 Counter

(00-11)₂

of P-P = 2

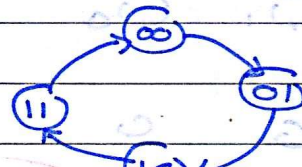


P.P. inputs Use Anyone.

Current state		Next state		T ₁	T ₀	D ₁	D ₀
Q ₁	Q ₀	Q ₁	Q ₀				
0	0	0	1	0	1	0	1
0	1	1	0	1	1	1	0
1	0	1	1	0	1	1	1
1	1	0	0	1	1	0	0


T₁ = Q₀

T₀ = 1

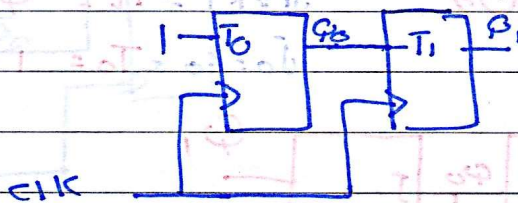

D₁ = Q₁ ⊕ Q₀

D₀ = Q₀

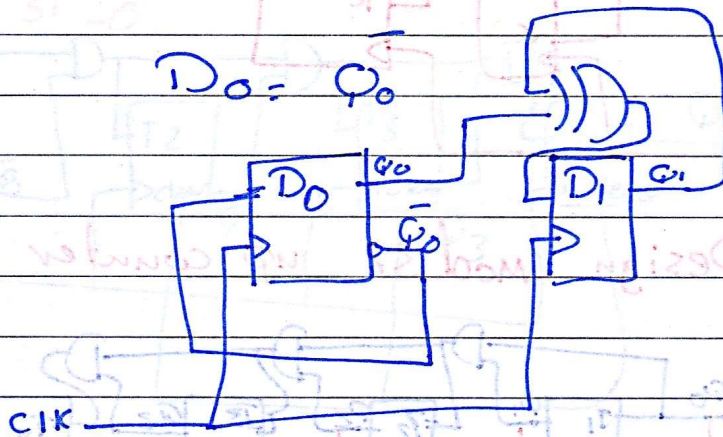

Ex) 0-7 counter


current state			next state			T ₂	T ₁	T ₀
Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀			
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	0	1	0	1	1
1	1	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	1

T₂ = Q₀ Q₁

T₃ = Q₀ Q₁ Q₂


J_i = K_i = T_i = Q_{i-1} · Q_{i-2} · ... · Q₀

J₀ = K₀ = T₀ = 1

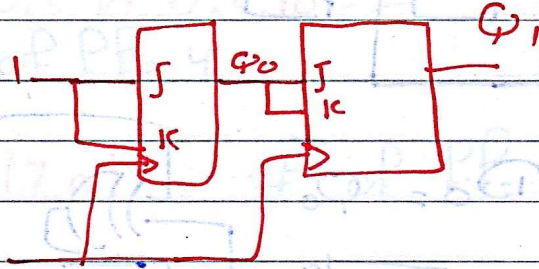


Ex) Design mod 32 up counter using T P.F.

0-31

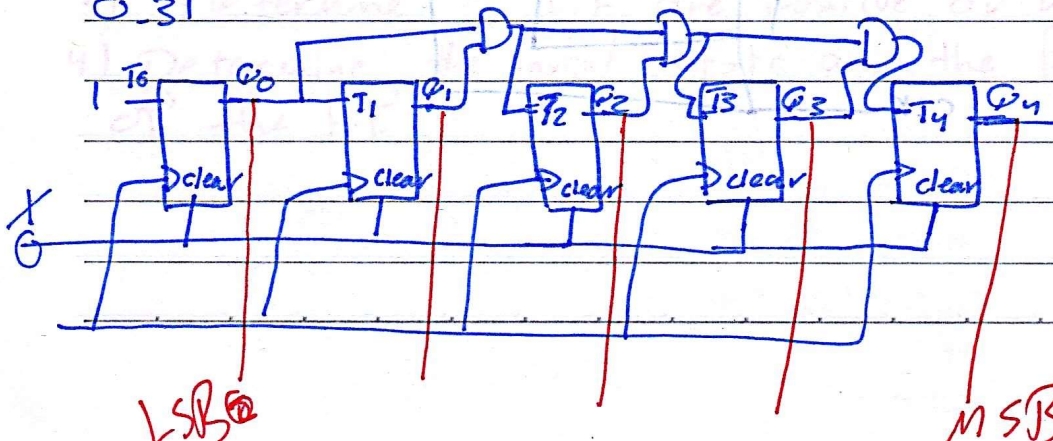


Down counter 3-0

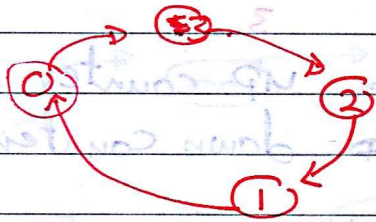


Current state		next state		P.P Inputs	
Q_1	Q_0	Q_1	Q_0	T_1	T_0
0	0	1	1	1	1
0	1	0	0	0	1
1	0	0	1	1	0
1	1	1	0	0	0

$T_0 = 1$

$T_1 = \overline{Q_0}$

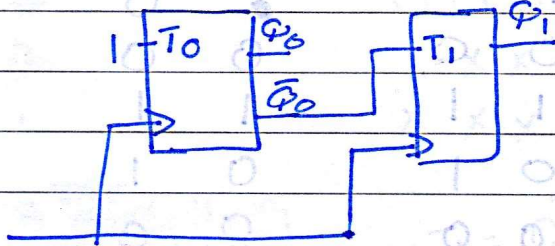

Ex) Design 31-0

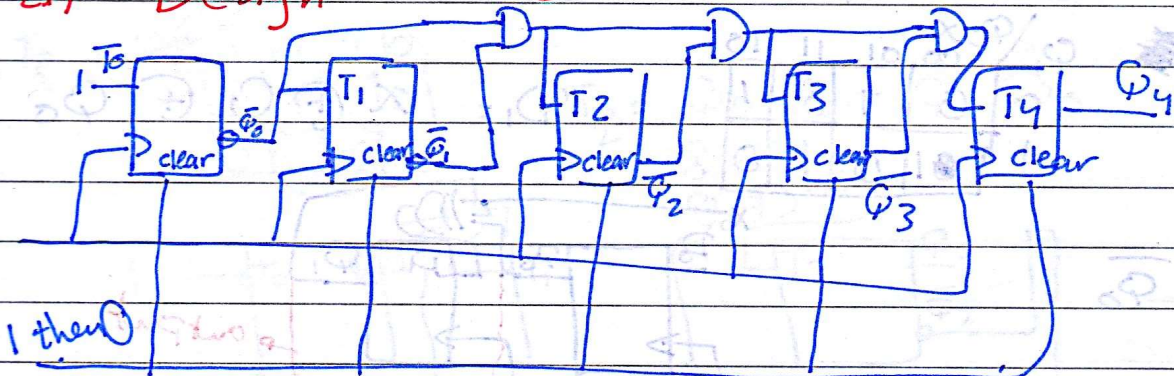


1 then 0

class 34

Ex) design up-down count 0-3

of P.F = 2

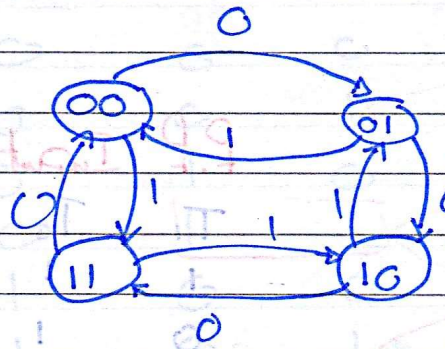PP $x=0 \rightarrow$ up counter
PP $x=1 \rightarrow$ down counter.




Current state	Inputs	next state	P.F
Q_1, Q_0	X	Q_1, Q_0	D_1, D_0
0 0	0	0 1	0 1
0 0	1	1 1	1 1
0 1	0	1 0	1 0
0 1	1	0 0	0 0
1 0	0	1 1	1 1
1 0	1	0 1	0 1
1 1	0	0 0	0 0
1 1	1	1 0	1 0

Q_1	Q_0	X	01	11	10
0	0	0	0	1	1
0	0	1	1	1	0

$D_1 = X \oplus Q_1 \oplus Q_0$

$D_0 = \overline{Q_0}$

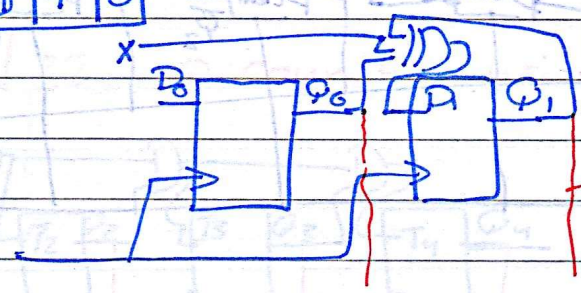


MSB

output




class 34

Irregular →

Ex) Design Mod_6 counter 0-5

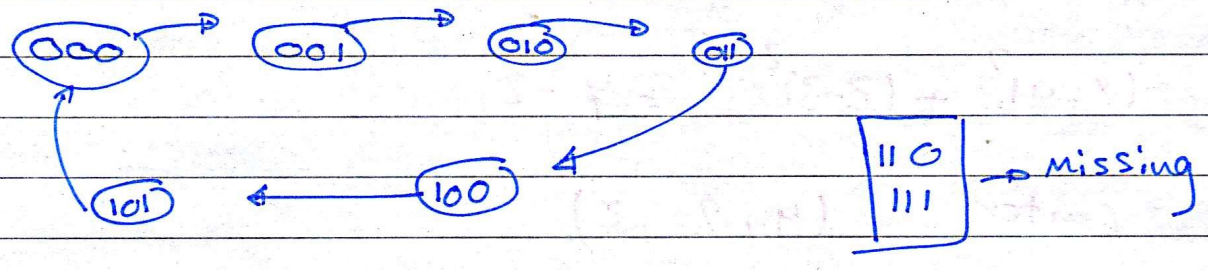


current state	Next state	F.F Inputs
$Q_2 Q_1 Q_0$	$Q_2 Q_1 Q_0$	$T_2 T_1 T_0$
0 0 0	0 0 1	0 0 1
0 0 1	0 1 0	0 1 1
0 1 0	0 1 1	0 0 1
0 1 1	1 0 0	1 1 1
1 0 0	1 0 1	0 0 1
1 0 1	0 0 0	1 0 1
1 1 0	X X X	X X X
1 1 1	X X X	X X X

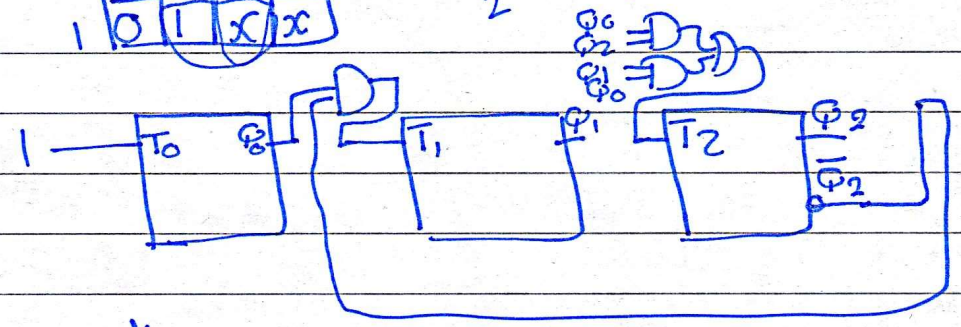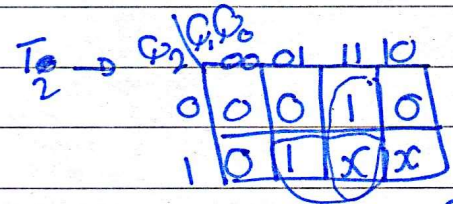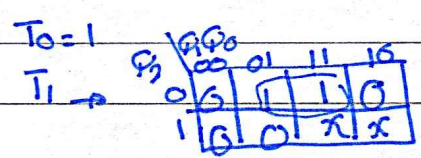


with clock.

class 34

For simplify →

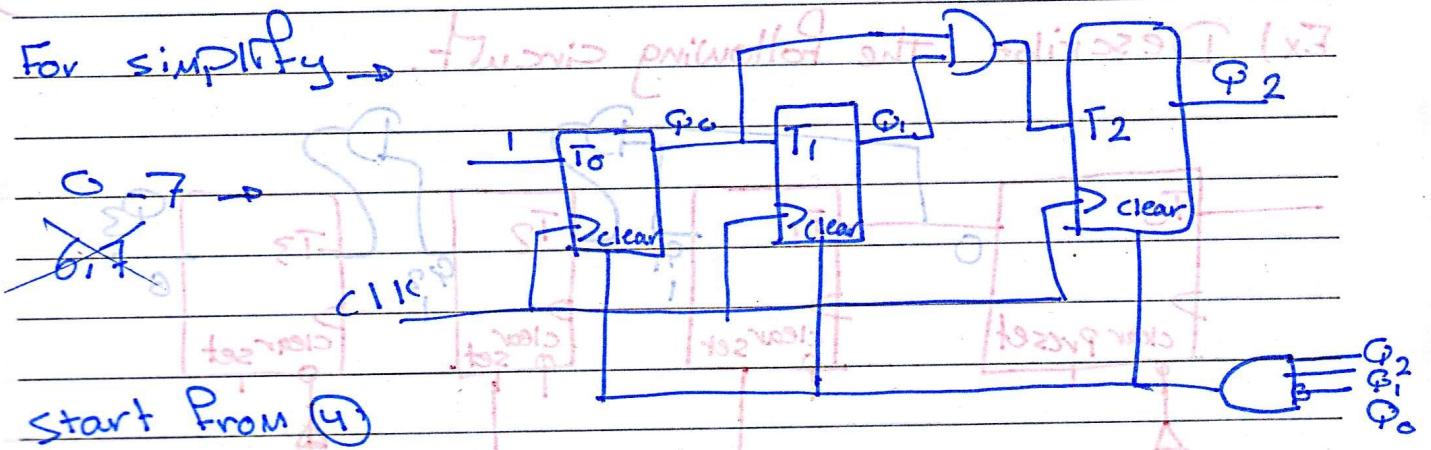


Start From (4)
 100

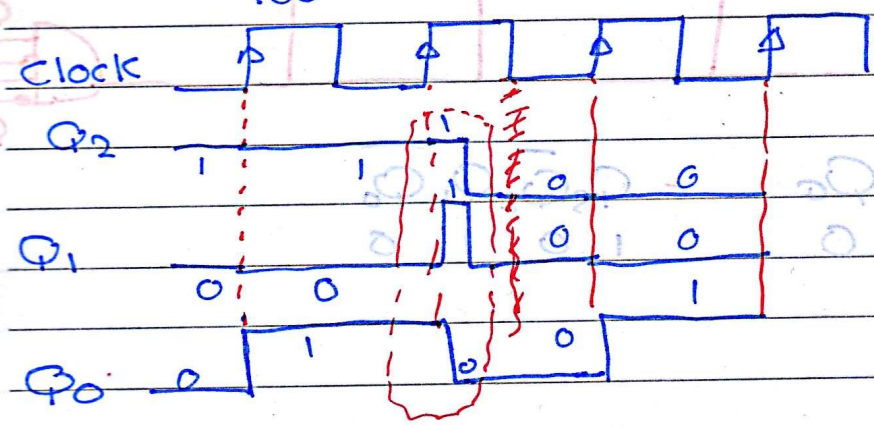


Conditions for simplifying irregular counters:

- ① The count must be up or down but not both.
 - ② Stop wdt must be $\frac{1}{2}$
- $NS = PS + 1$
 $= PS - 1$

Ex) 7.3

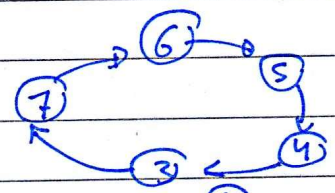


Preset On 2

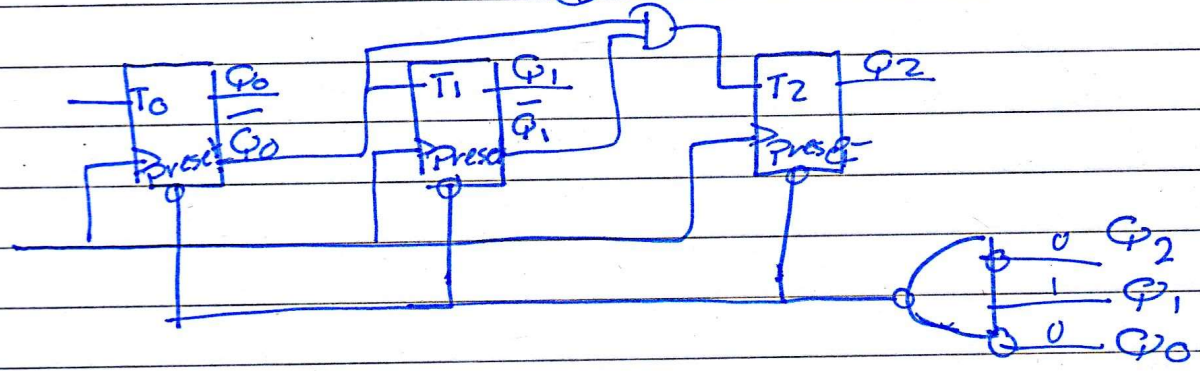

class 34

Ex) Describe the following circuit.

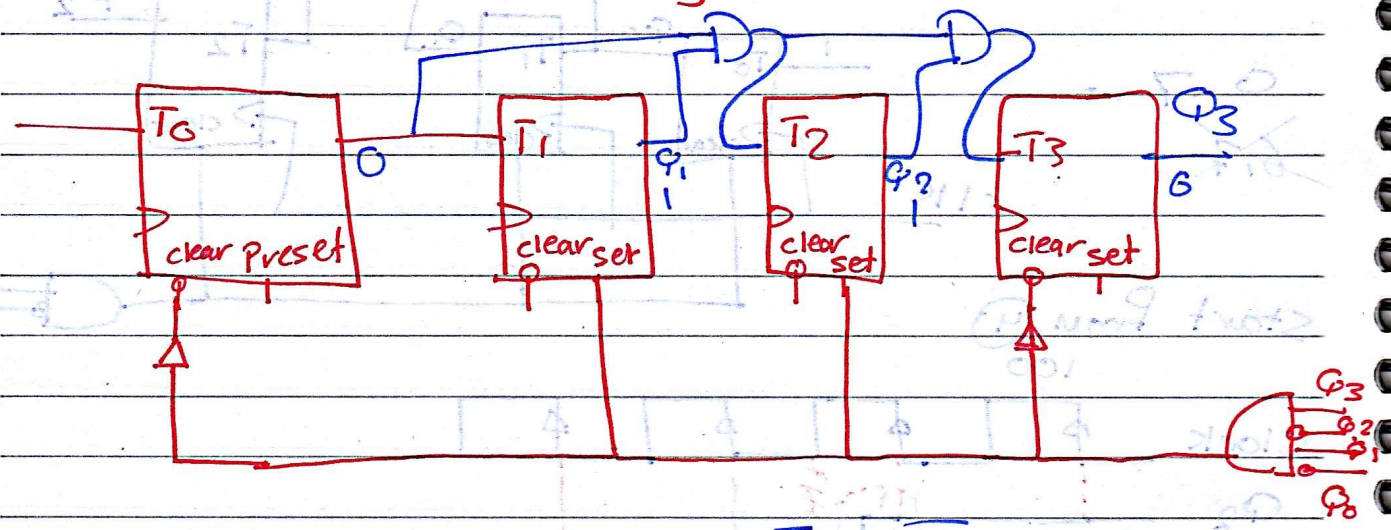

$Q_3 \quad Q_2 \quad Q_1 \quad Q_0$ $\overline{Q_3} \quad \overline{Q_2} \quad \overline{Q_1} \quad \overline{Q_0}$
 0 1 1 0 1 0 1 0

[3_9]

