

CPE 408330

Assembly Language and Microprocessors

Chapter 8: THE 8088 AND 8086 MICROPROCESSORS AND THEIR MEMORY AND INPUT/OUTPUT INTERFACES

[Computer Engineering Department,
Hashemite University, © 2008]

Lecture Outline

- ▶ 8.1 The 8088 and 8086 Microprocessors
- ▶ 8.2 Minimum-Mode and Maximum-Mode System
- ▶ 8.3 Minimum-Mode Interface
- ▶ 8.4 Maximum-Mode Interface
- ▶ 8.5 Electrical Characteristics
- ▶ 8.6 System Clock
- ▶ 8.7 Bus Cycle and Time States
- ▶ 8.8 Hardware Organization of the Memory Address Space

Lecture Outline

- ▶ 8.9 Memory Bus Status Codes
- ▶ 8.10 Memory Control Signals
- ▶ 8.11 Read and Write Bus Cycles
- ▶ 8.12 Memory Interface Circuits
- ▶ 8.13 Programmable Logic Arrays
- ▶ 8.14 Types of Input/Output
- ▶ 8.15 An Isolated Input/Output Interface
- ▶ 8.16 Input/Output Data Transfer
- ▶ 8.17 Input/Output Instructions
- ▶ 8.18 Input/Output Bus Cycles

8.1 The 8088 and 8086 Microprocessors

- The 8086, announced in 1978, was the first 16-bit microprocessor introduced by Intel Corporation.
- 8086 and 8088 are internally 16-bit MPU. However, externally the 8086 has a 16-bit data bus and the 8088 has an 8-bit data bus.

8.1 The 8088 and 8086 Microprocessors


- 8086 and 8088 both have the ability to address up to 1 Mbyte of memory and 64K of input/output port.
- The 8088 and 8086 are both manufactured using *high-performance metal-oxide semiconductor (HMOS) technology*.
- The 8088 and 8086 are housed in a 40-pin dual inline package and many pins have multiple functions.

8.1 The 8088 and 8086 Microprocessors

- **CMOS, Complementary Metal–Oxide–Semiconductor**, is a major class of integrated circuits used in chips such as microprocessors, microcontrollers, static RAM, digital logic circuits, and analog circuits such as image sensors.
- Two important characteristics of CMOS devices are **high noise immunity** and **low static power** supply drain. Significant power is only drawn when its transistors are switching between on and off states; consequently, CMOS devices **do not produce as much heat as other forms of logic such as TTL**. CMOS also allows a high density of logic functions on a chip.

 8.1 The 8088 and 8086 Microprocessors

- Pin functions
- Most pins are independent and serve a single function
- Examples:
 - CLK—clock
 - INTR—interrupt request
 - READY—bus ready
- Some multi-functions pins—different times/different mode
- Examples:
 - AD₀–AD₁₅– multiplexed address/data lines at different times
 - A₁₆/S₃—multiplexed address and status line at different times
 - IO/M* or S₂* Control line in one mode or bus



Pin layout of the 8086 and 8088 microprocessor

8.2 Minimum-Mode and Maximum-Mode Systems

- The 8086 and 8088 microprocessors can be configured to work in either of two modes:
 - The minimum mode - $MN/MX' = 1$
 - The maximum mode - $MN/MX' = 0$
- The mode selection feature lets the 8088 or 8086 better meet the needs of a wide variety of system requirement.
- Minimum mode 8088/8086 systems are typically smaller and contain a single processor.
- Depending on the mode of operation selected, the assignment for a number of the pins on the microprocessor package are changed.

8.2 Minimum-Mode and Maximum-Mode Systems

Common signals		
Name	Function	Type
AD7-AD0	Address/data bus	Bidirectional, 3-state
A15-A8	Address bus	Output, 3-state
A19/S6- A16/S3	Address/status	Output, 3-state
MN/ $\overline{\text{MX}}$	Minimum/maximum Mode control	Input
$\overline{\text{RD}}$	Read control	Output, 3-state
$\overline{\text{TEST}}$	Wait on test control	Input
READY	Wait state control	Input
RESET	System reset	Input
NMI	Nonmaskable Interrupt request	Input
INTR	Interrupt request	input
CLK	System clock	Input
V _{CC}	+5 V	Input
GND	Ground	

(a)

Signals common to both minimum and maximum mode

- 8088 signals/pins categorized as
 - Common—same function both modes
Examples: Pin 9 (AD₇)– pin 16 (AD₀)
 - Minimum Mode—special minimum mode operations
Examples: pins 26–28 are DEN*, DT/R*, and IO/M*
 - Maximum Mode—special maximum mode operations
Example: pins 26–28 are S₀*, S₁*, and S₂*

8.2 Minimum-Mode and Maximum-Mode Systems

Minimum mode signals ($MN/\overline{MX} = V_{CC}$)		
Name	Function	Type
HOLD	Hold request	Input
HLDA	Hold acknowledge	Output
\overline{WR}	Write control	Output, 3-state
IO/\overline{M}	IO/memory control	Output, 3-state
DT/\overline{R}	Data transmit/receive	Output, 3-state
\overline{DEN}	Data enable	Output, 3-state
\overline{SSO}	Status line	Output, 3-state
ALE	Address latch enable	Output
\overline{INTA}	Interrupt acknowledge	Output

(b)

Maximum mode signals ($MN/\overline{MX} = GND$)		
Name	Function	Type
$\overline{RQ}/\overline{GT1}, 0$	Request/grant bus access control	Bidirectional
\overline{LOCK}	Bus priority lock control	Output, 3-state
$\overline{S2} - \overline{S0}$	Bus cycle status	Output, 3-state
QS1, QS0	Instruction queue status	Output

(c)

(b) Unique minimum-mode signals (c) Unique maximum-mode signals

8.2 Minimum-Mode and Maximum-Mode Systems


▶ EXAMPLE

Which pins provide different signal functions in the minimum-mode 8088 and minimum-mode 8086?

▶ Solution:


- (a) Pins 2 through 8 on the 8088 are address lines A_{14} through A_8 , but on the 8086 they are address/data lines AD_{14} through AD_8 .
- (b) Pin 28 on the 8088 is IO/M' output and on the 8086 it is the M/IO' output.
- (c) Pin 34 of the 8088 is the SSO' output, and on the 8086 this pin supplies the BHE'/S_7 .

8.3 Minimum-Mode Interface

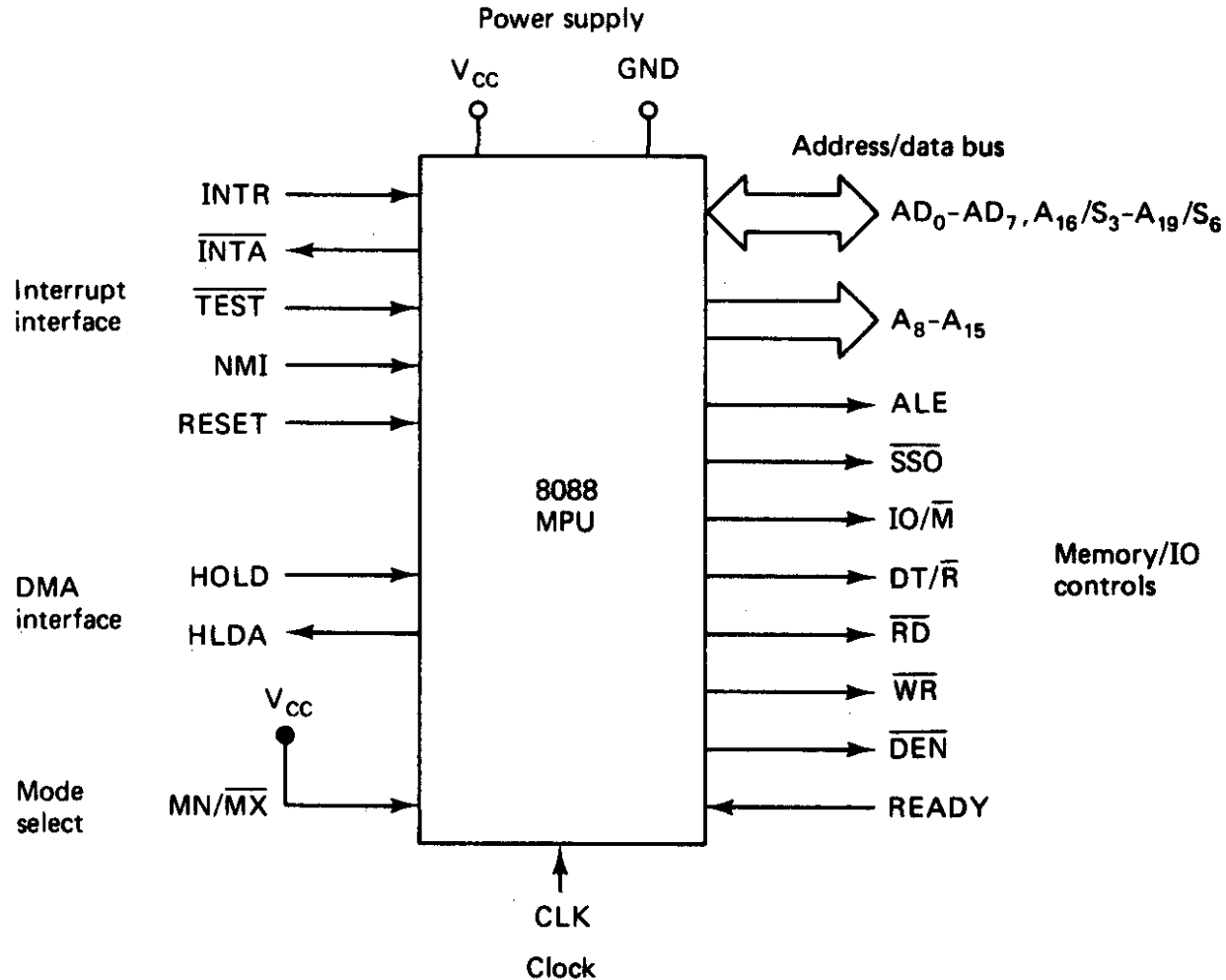

Block diagram of the minimum-mode 8088 MPU

8.3 Minimum-Mode Interface-Differences

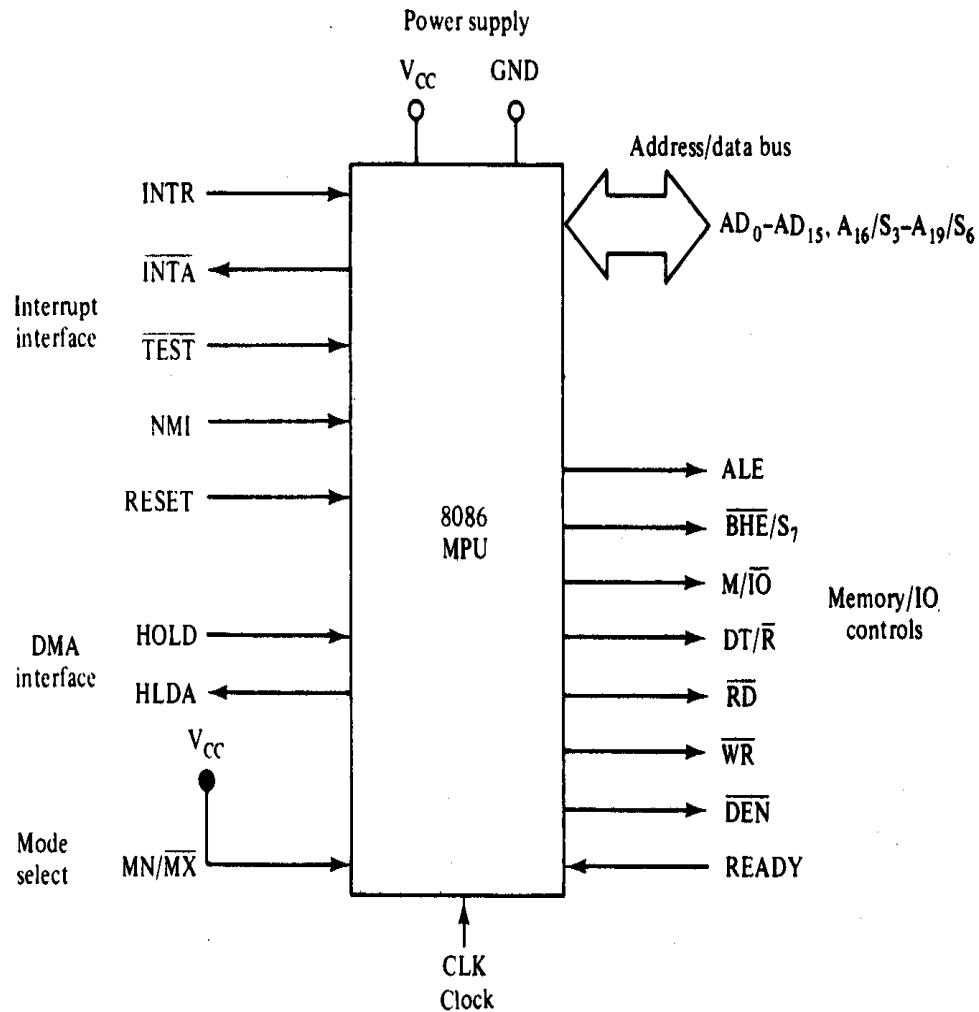

Block diagram of the minimum-mode 8086 MPU

- Data bus
 - 16-bit wide
 - D₁₅-D₀
 - Multiplexed with A₁₅ through A₀
 - Allows 3 types of data transfers
 - Word—over D₁₅-D₀
 - Low byte—over D₇-D₀
 - High byte—over D₁₅-D₈
- Memory/IO Controls
 - SSO* → BHE* (bank high enable)
 - Used to signal external circuitry whether or not a byte transfer is taking place over the upper 8 data bus lines
 - A₀ now does the same for a byte transfer over the lower 8 data bus line

8.3 Minimum-Mode Interface

- The minimum-mode signals can be divided into the following basic groups:
 - Address / Data bus
 - Status signals
 - Control signals
 - Interrupt signals
 - DMA interface signals

8.3 Minimum-Mode Interface

- Address / Data bus
 - The address bus is used to carry address information to the memory and I/O ports.
 - The address bus is 20-bit long and consists of signal lines A_0 through A_{19} .
 - A 20-bit address gives the 8088 a 1 MByte memory address space.
 - Only address line A_0 through A_{15} are used when addressing I/O. This give an I/O address space of 64 Kbytes.
 - The 8088 has 8 multiplexed address/data bus lines ($A_0 \sim A_7$) while 8086 has 16 multiplexed address/data bus lines ($A_0 \sim A_{15}$).

8.3 Minimum-Mode Interface

S6 S5 S4 S3

- Status signals
 - The four most significant address, A_{19} through A_{16} are multiplexed with *status signal* S_6 through S_3 .
 - Bits S_4 and S_3 together form a 2-bit binary code that identifies which of the internal segment registers was used to generate the physical address. S_5 is the logic level of the internal interrupt flag. S_6 is always at the 0 logic level.

S_4	S_3	Address Status
0	0	Alternate (relative to the ES segment)
0	1	Stack (relative to the SS segment)
1	0	Code/None (relative to the CS segment or a default of zero)
1	1	Data (relative to the DS segment)

8.3 Minimum-Mode Interface

- Control signals
 - The *control signals* are provided to support the memory and I/O interfaces of the 8088 and 8086.
 - ALE – Address Latch Enable
 - IO/M' – IO/Memory (8088)
 - M/IO' – Memory/IO (8086)
 - DT/R' – Data Transmit/Receive (8088/8086)
 - SSO' – System Status Output (8088)
 - BHE' – Bank High Enable (8086)
 - RD' – Read (8088/8086)
 - WR' – Write (8088/8086)
 - DEN' – Data Enable (8088/8086)
 - READY – Ready (8088/8086)

8.3 Minimum-Mode Interface

□ Interrupt signals

- The *interrupt signals* can be used by an external device to signal that it needs to be serviced.
 - INTR' – Interrupt Request
 - INTA' – Interrupt Acknowledge
 - TEST' – Test (can be use to synchronize MPU)
 - NMI – Nonmaskable Interrupt
 - RESET – Reset (hardware reset of the MPU)

8.3 Minimum-Mode Interface

- DMA interface signals
 - When an external device wants to take control of the system bus, it signals this fact to the MPU by switching HOLD to the 1 logic level.
 - When in the hold state, signal lines AD₀ through AD₇, A₈ through A₁₅, A₁₆/S₃ through A₁₉/S₆, SSO', IO/M', DT/R', RD', WR', DEN', and INTR are all put into high-Z state.
 - The 8088 signals external devices that the signal lines are in the high-Z state by switching its HLDA output to the 1 logic level.


8.4 Maximum-Mode Interface

- The maximum-mode configuration is mainly used for implementing a ***multiprocessor/coprocessor system environment***.
- Global resources and local resources
- In the maximum-mode, facilities are provided for implementing allocation of global resources and passing bus control to other microprocessors sharing the system bus.

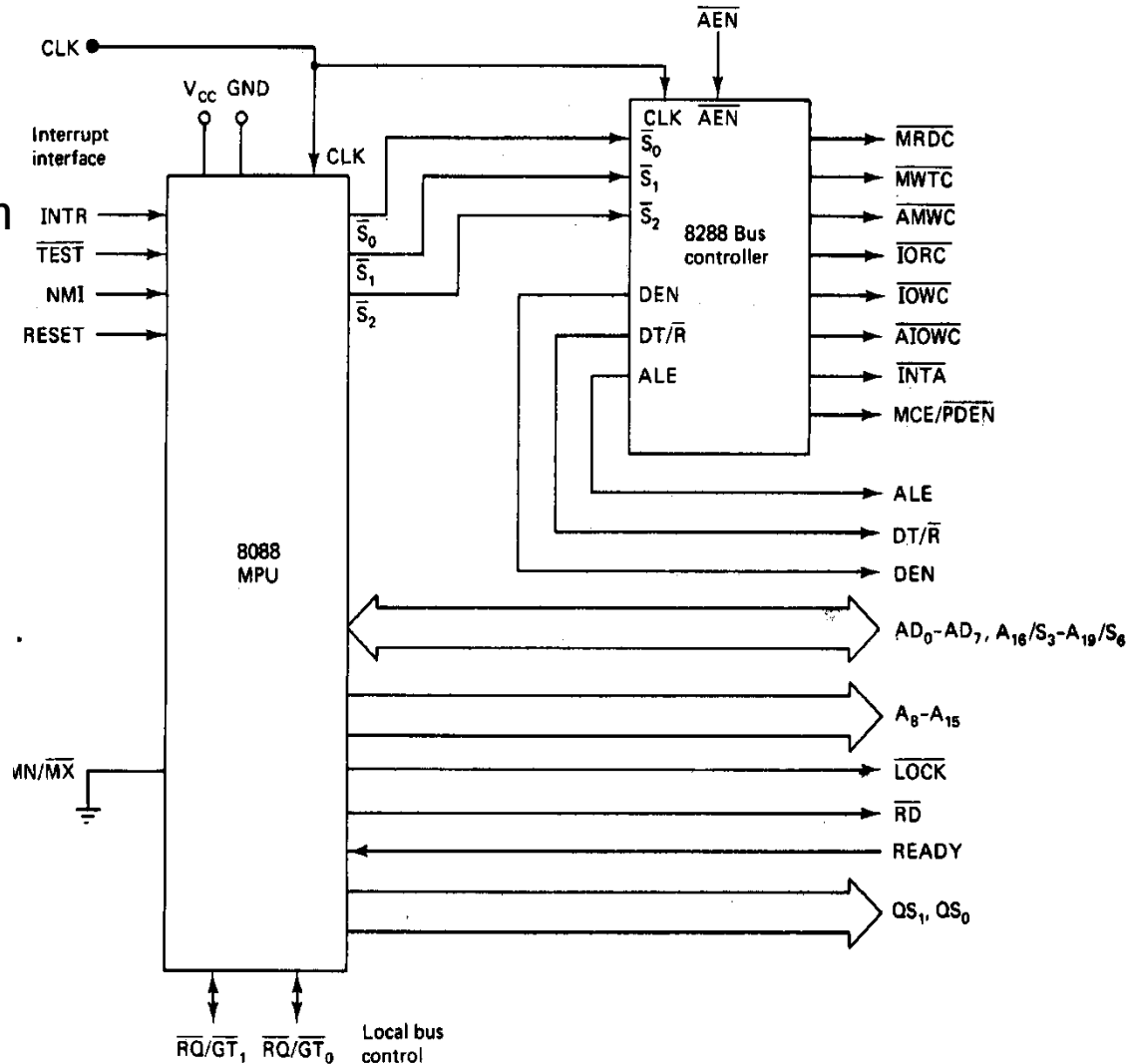8.4 Maximum-Mode Interface

8288 bus controller:

- Maximum-mode configuration
 - MN/MX* pin = 0 → GND
 - Most memory, IO, and interrupt interface outputs produced by an external 8288 bus controller




8088 maximum-mode block diagram

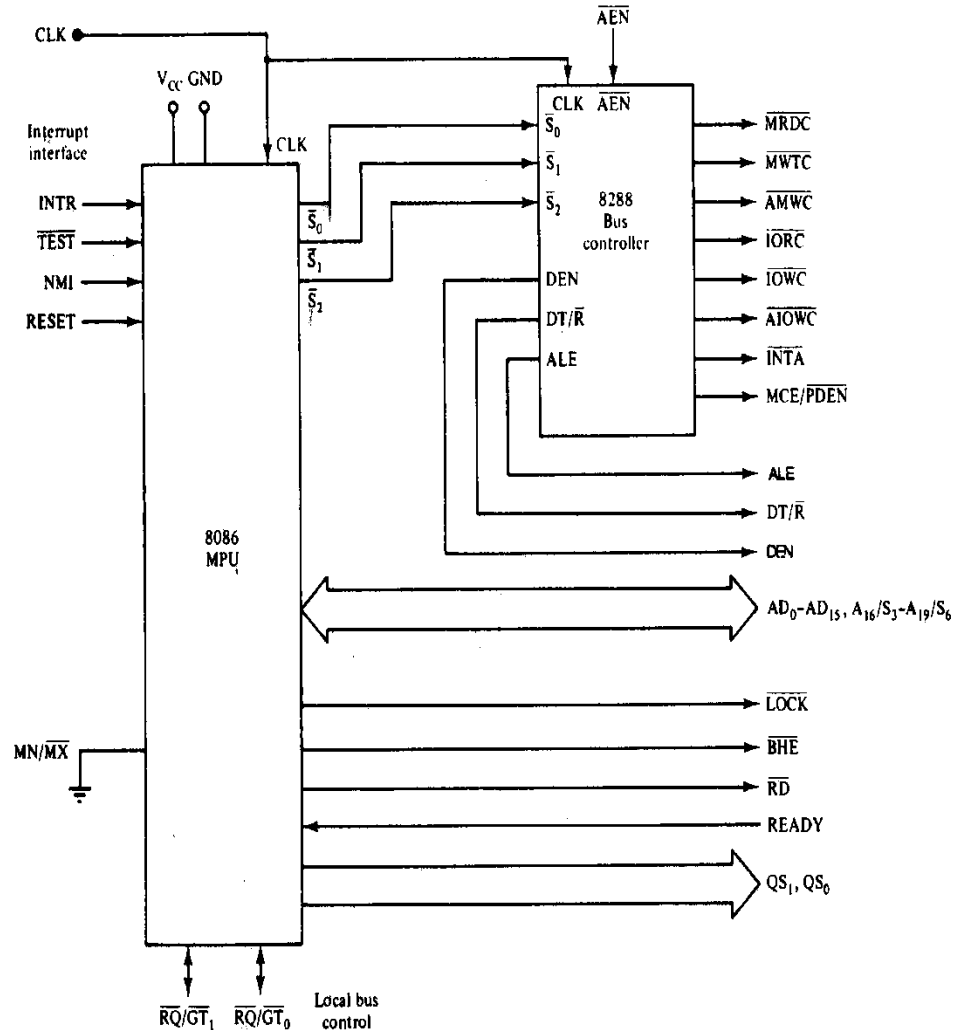8.4 Maximum-Mode Interface

8288 bus controller:

- Differences from 8088 Maximum mode interface
 - 16-bit multiplexed data bus
 - BHE* output



8086 maximum-mode block diagram

8.4 Maximum-Mode Interface

- 8288 bus controller
 - In the maximum-mode, 8088/8086 outputs a status code on three signal line, S_0 , S_1 , S_2 , prior to the initialization of each bus cycle.
 - The 3-bit bus status code identifies which type of bus cycle is to follow and are input to the external bus controller device, 8288.
 - The 8288 produces one or two command signals for each bus cycle.

8.4 Maximum-Mode Interface


□ *8288 bus controller:*

Status Inputs			CPU Cycle	8288 Command
$\overline{S2}$	$\overline{S1}$	$\overline{S0}$		
0	0	0	Interrupt Acknowledge	\overline{INTA}
0	0	1	Read I/O Port	\overline{IORC}
0	1	0	Write I/O Port	$\overline{IOWC}, \overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction Fetch	\overline{MRDC}
1	0	1	Read Memory	\overline{MRDC}
1	1	0	Write Memory	$\overline{MWTC}, \overline{AMWC}$
1	1	1	Passive	None

Bus status code

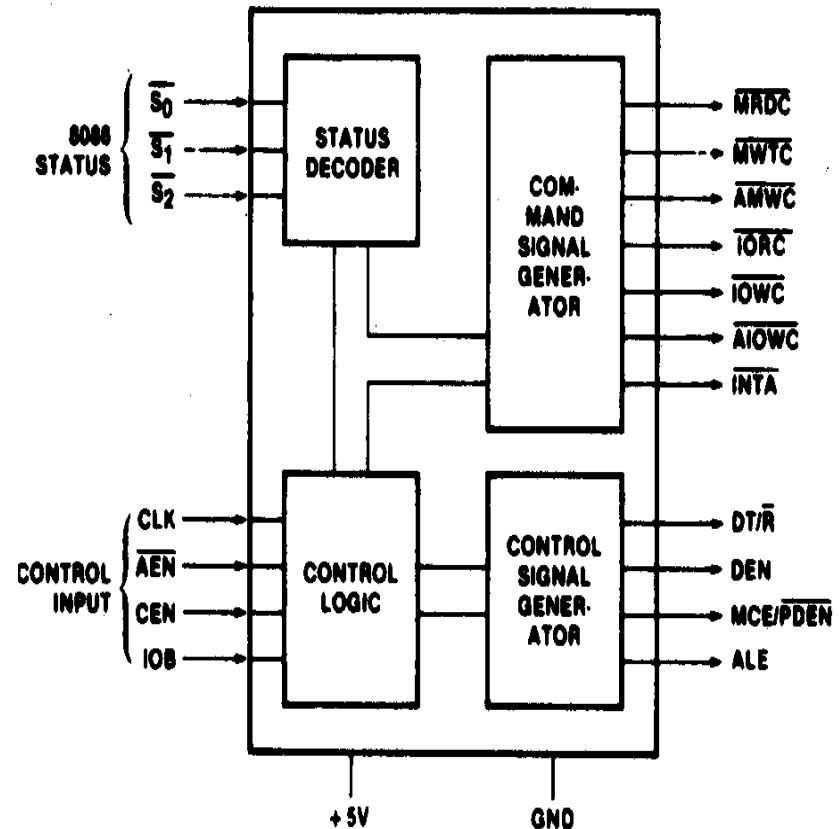8.4 Maximum-Mode Interface

- 8288 bus controller connection
 - Inputs are codes from the 3-bit bus status lines $S_2^*S_1^*S_0^*$ = bus status code
 - Outputs produced by 8288 instead of 8088
 - Based on bus status code \rightarrow active 0
- MRDC* = Memory read command
- MWTC* = Memory write command
- AMWC* = Advanced memory write command
- IORC* = I/O read command
- IOWC* = I/O write command
- AIOWC* = advanced I/O write command
- Produced for all bus cycles
 - ALE = Address latch enable
 - DT/R* = Data transmit/receive
 - DEN = Data enable (complement)
 - INTA* = Interrupt acknowledge



Block diagram of 8288

8.4 Maximum-Mode Interface

□ Lock signal

□ The lock signal (LOCK') is meant to be output (logic 0) whenever the processor wants to lock out the other processor from using the bus.

□ Local bus control signals

□ The request/grant signals (RQ'/GT'₀, RQ'/GT'₁) provide a prioritized bus access mechanism for accessing the local bus.

8.4 Maximum-Mode Interface

- Queue status signals
 - The 2-bit queue status code QS_0 and QS_1 tells the external circuitry what type of information was removed from the queue during the previous clock cycle.

QS1	QS0	Queue Status
0 (low)	0	No Operation. During the last clock cycle, nothing was taken from the queue.
0	1	First Byte. The byte taken from the queue was the first byte of the instruction.
1 (high)	0	Queue Empty. The queue has been reinitialized as a result of the execution of a transfer instruction.
1	1	Subsequent Byte. The byte taken from the queue was a subsequent byte of the instruction.

Queue status code

8.4 Maximum-Mode Interface

▶ EXAMPLE

If the bus status code $S'_2S'_1S'_0$ equals 101, what type of bus activity is taking place? Which command output is produced by the 8288?

▶ Solution:

Looking at the bus status table, we see that bus status code 101 identifies a read memory bus cycle and causes the MRDC' output of the bus controller to switch to logic 0.

8.5 Electrical Characteristics

- Power is applied between pin 40 (Vcc) and pins 1 (GND) and 20 (GND) (pin1 and 20 are connected together).
- The nominal value of Vcc is specified as +5V dc with a tolerance of $\pm 10\%$ (4.5V~5.5V will work correctly)
- Both 8088 and 8086 draw a maximum of 340mA from the supply.


Symbol	Meaning	Minimum	Maximum	Test condition
V_{IL}	Input low voltage	-0.5 V	+0.8 V	
V_{IH}	Input high voltage	+2.0 V	$V_{cc} + 0.5 V$	
V_{OL}	Output low voltage		+0.45 V	$I_{OL} = 2.0mA$
V_{OH}	Output high voltage	+2.4 V		$I_{OH} = -400 \mu A$

8.6 System Clock

- The time base for synchronization of the internal and external operations of the microprocessor in a microcomputer system is provided by the *clock (CLK)* input signal.
- **8088 is available in two speeds.** The standard 8088 operates at 5 MHz and the 8088-2 operates at 8 MHz.
- The 8086 is manufactured in three speeds: 5-MHz 8086, 8-MHz 8086-2, and the 10-MHz 8086-1.
- The CLK is externally generated by the 8284 clock generator and driver IC.

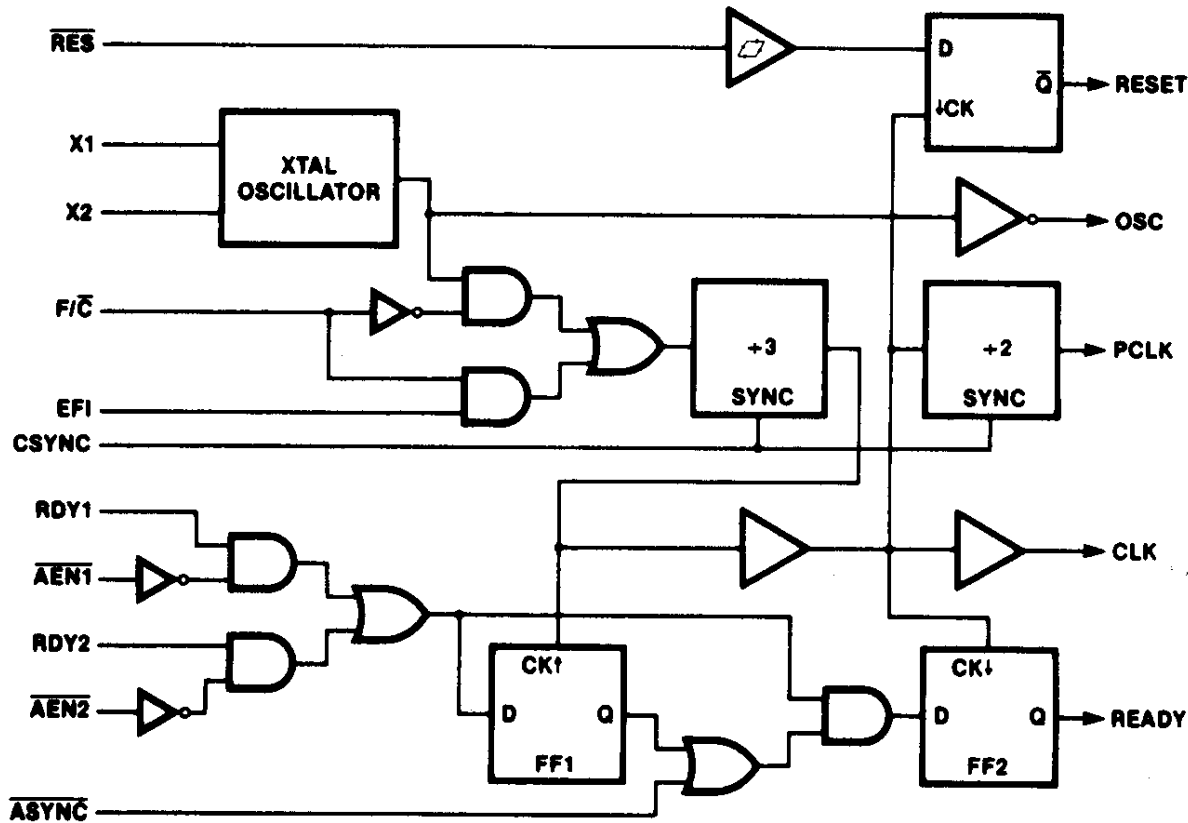
8.6 System Clock

- Block diagram of the 8284 clock generator




8.6 System Clock

- Connecting the 8284 to the 8088

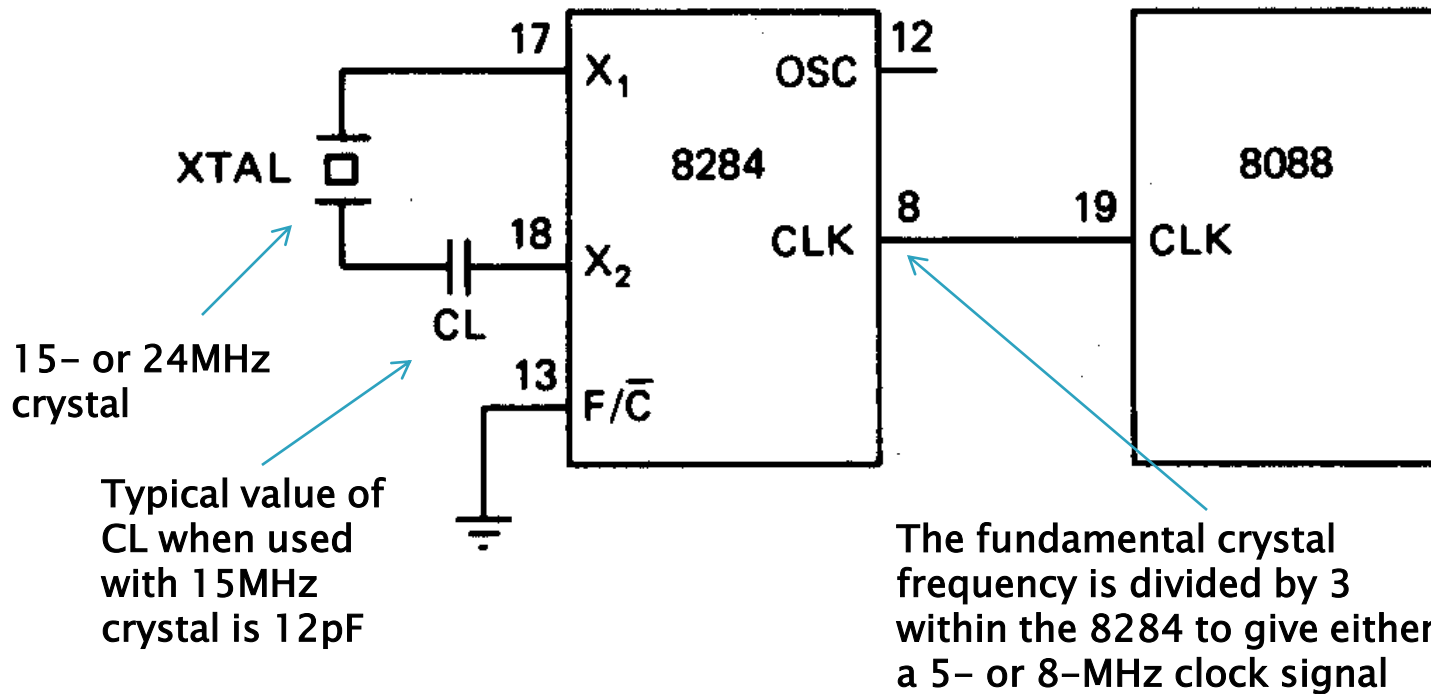

 
8.6 System Clock

- CLK waveform
 - The signal is specified at Metal Oxide Semiconductor (MOS)–compatible voltage level (rather than TTL)
 - The period of the 5-MHz 8088 can range from 200 ns to 500 ns, and the maximum rise and fall times of its edges equal 10 ns.



 8.6 System Clock

- PCLK and OSC signals
 - The peripheral clock (PCLK) and oscillator clock (OSC) signals are provided to drive peripheral ICs.
 - The clock output at PCLK is half the frequency of CLK. The OSC output is at the crystal frequency which is three times of CLK.



8.6 System Clock

▶ EXAMPLE

If the CLK input of an 8086 MPU is to be driven by a 9-MHz signal, what speed version of the 8086 must be used and what frequency crystal must be attached to the 8284

▶ Solution:


The 8086-1 is the version of the 8086 that can be run at 9-MHz. To create the 9-MHz clock, a 27-MHz crystal must be used on the 8284.

8.7 Bus Cycle and Time States

- A bus cycle defines the basic operation that a microprocessor performs to communicate with external devices.
- Examples of bus cycles are the memory read, memory write, input/output read, and input/output write.
- The bus cycle of the 8088 and 8086 microprocessors consists of at least **four clock periods**.
- If no bus cycles are required, the microprocessor performs what are known as *idle states*.
- When READY is held at the 0 level, *wait states* are inserted between states T₃ and T₄ of the bus cycle.
- For write cycle, at T₁ the address is prepared, data is ready at T₂ and maintained during T₃ and T₄.
- For read cycle, at T₁ the address is prepared, at T₂ the bus is at Z state, and the data is ready at T₃ and maintained at T₄.

 8.7 Bus Cycle and Time States


- Multiplexed address/data transfer operation
 - Address output during T1
 - Bus lines in high-Z state in T2
 - Data transfer takes place during states T3 and T4



Bus cycle clock periods

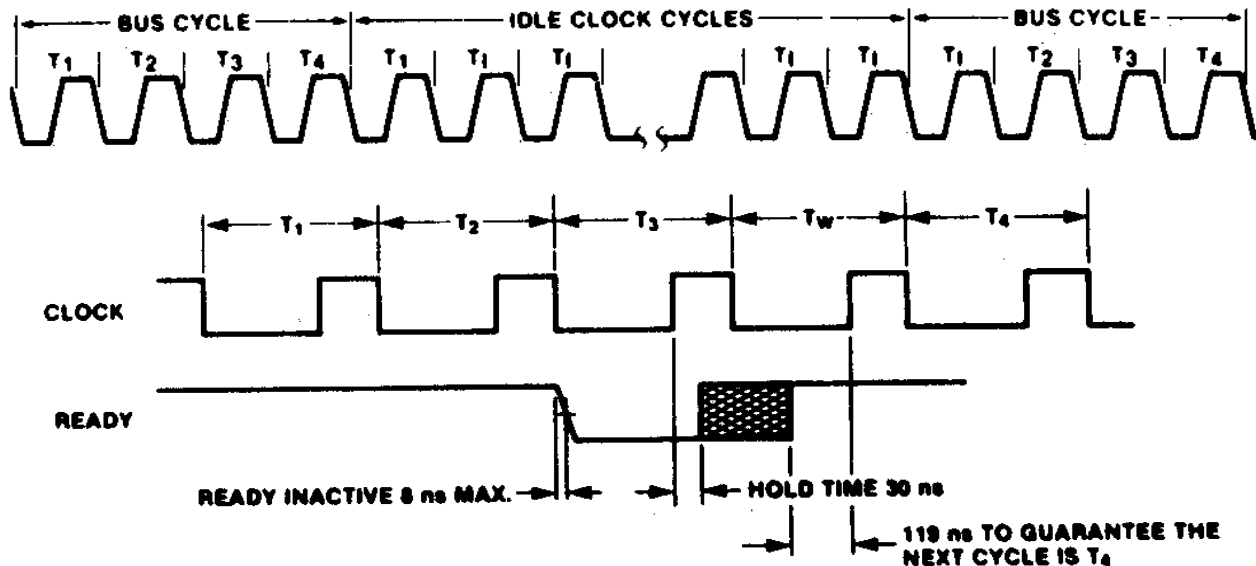8.7 Bus Cycle and Time States

- Bus cycle with idle
 - If no bus activity is necessary, microprocessor inserts idle states between bus cycles
 - Identified as T1
 - May be due to the fact that the instruction queue is already full so no instructions need to be fetched
- Bus cycle with wait states
 - If the memory or I/O device is not able to respond in the duration of a bus cycle (500ns @8MHz) (slow I/O and memory) , it must make READY 0 during T3 to extend the bus cycle
 - Wait states (T_w) are inserted to extend the bus cycle until READY returns to 1



Bus cycle with idle state, and wait state

8.7 Bus Cycle and Time States

▶ EXAMPLE

What is the duration of the bus cycle in the 8088-based microcomputer if the clock is 8 MHz and the two wait states are inserted.

▶ Solution:


The duration of the bus cycle in an 8 MHz system is given by

$$t_{\text{cyc}} = 500 \text{ ns} + N \times 125 \text{ ns}$$

In this expression the N stands for the number of wait states. For a bus cycle with two wait states, we get

$$\begin{aligned} t_{\text{cyc}} &= 500 \text{ ns} + 2 \times 125 \text{ ns} = 500 \text{ ns} + 250 \text{ ns} \\ &= 750 \text{ ns} \end{aligned}$$

 8.8 Hardware Organization of the Memory Address Space




- 8088 memory hardware is organized as a single byte-wide memory bank
 - Size—1 M X 8 bits
 - Physical address range— 0H-FFFFFH
 - Address/data bus de-multiplexed in external hardware
 - Input:
 - 20-bit address bus— A₁₉ through A₀
 - Input/output:
 - 8-bit data bus—D₇ Through D₀

Memory size = 2^{number of address lines}
→ 1M = 2²⁰ (needs 20 address line)

1Mx8 memory bank of the 8088

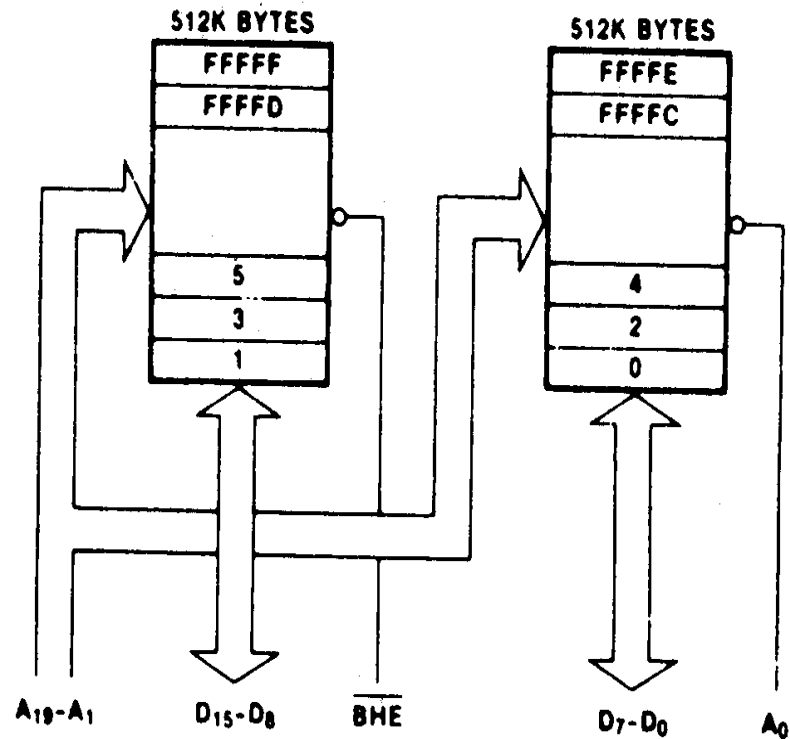8.8 Hardware Organization of the Memory Address Space




- 8086 memory hardware is organized as a two byte-wide memory bank
- Bank size—512K X 8 bits
- Low-bank holds even addressed bytes—0H through FFFEH
- High-bank holds odd addressed bytes—1H through FFFFH
- Address/data bus demultiplexed in external hardware
- Input:
 - 20-bit+ address bus— A19 through A0, and BHE*
 - A1-A19 = selects storage location
 - A0 = 0 enables low bank
 - BHE* = 0 enables high bank
- Input/Output:
 - 16-bit data bus—D15 Through D0
 - D7-D0 → even addressed byte accesses
 - D15-D8 → odd addressed byte

High and low memory banks of the 8086

Memory size = $2^{\text{number of address lines}}$

→ $512K = 2^{19}$ (needs 19 address line)

 
8.8 Hardware Organization of the Memory Address Space



Byte transfer by the 8088

- Byte access bus cycle
 - MPU applies address of storage location to be accessed over address lines $A_{19}-A_0$
 - A_{19} —most significant bit
 - A_0 —least significant bit
 - Byte of data written into or read from address X transferred over data lines D_0 through D_7
 - D_7 —most significant bit
 - D_0 —least significant bit
 - Byte access takes a minimum of one bus cycle of duration
 - @5MHz—800ns
 - @8MHz—500ns

 8.8 Hardware Organization of the Memory Address Space




- Word access bus cycles
 - MPU must access two consecutive storage locations in memory—X and X+1
 - Requires two bus cycles
 - Address X accessed during cycle 1
 - Address X+1 accessed during cycle 2
 - Word access duration is a minimum of two bus cycle
 - @5MHz—2 X 800ns = 1600ns
 - @8MHz—2 X 500ns = 1000ns

Word transfer by the 8088

8.8 Hardware Organization of the Memory Address Space


- Low bank byte access bus cycle
 - MPU applies even address X to both banks over address lines $A_{19}-A_0$
 - MPU enables just the low bank $BHE^*A_0 = 10 \rightarrow$ enables low bank
 - Byte of data written into or read from address X transferred over data lines D_0 through D_7
 - High bank access bus cycle differences
 - Odd address $X+1$ applied to both banks
 - High bank enabled $BHE^*A_0 = 01 = \rightarrow$ enable high bank
 - Byte-wide data transfer takes place over data line D_8 through D_{15}
 - Word access bus cycle differences
 - Even word address X applied to both banks
 - MPU enables both banks $BHE^*A_0 = 00 = \rightarrow$ enable low and high bank
 - Word-wide data transfer takes place over D_0 through D_{15}
 - All accesses takes a minimum of one bus cycle of duration
- @5MHz—800ns
@8MHz—500ns

 8.8 Hardware Organization of the Memory Address Space



- (a) Even address byte
- (b) Odd address byte transfer by the 8086
- (c) Even address word transfer

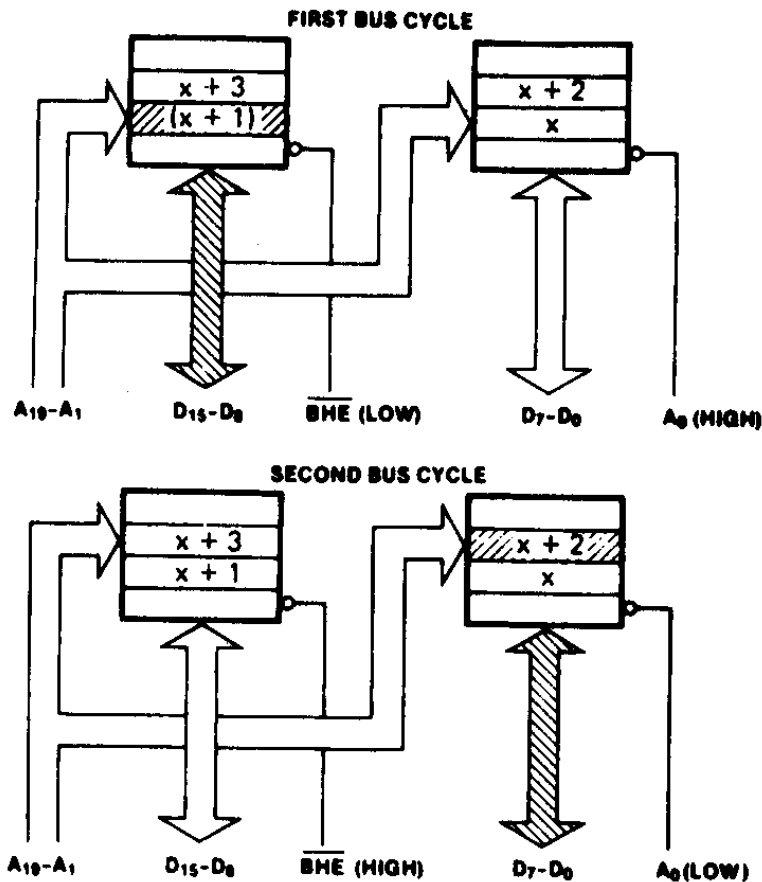8.8 Hardware Organization of the Memory Address Space



(d)

- Misaligned-word access bus cycles
 - Word starting at address $X+1$ is misaligned
 - Requires two bus cycles
 - Access byte at address $X+1$ during cycle 1
 $A_{19}-A_0 = X+1$
 $BHE * A_0 = 01 \rightarrow$ enables high bank
 $D_{15}-D_8 \rightarrow$ carries data
 - Access byte at address $X+2$ during cycle 2
 $A_{19}-A_0 = X+2$
 $BHE * A_0 = 10 \rightarrow$ enables low bank
 $D_7-D_0 \rightarrow$ carries data
 - Word access duration is a minimum of two bus cycle
 - @5MHz— $2 \times 800ns = 1600ns$
 - @8MHz— $2 \times 500ns = 1000ns$
- Impact on performance—software should minimize accessing

Odd address word transfer by the 8086

8.8 Hardware Organization of the Memory Address Space

▶ EXAMPLE

Is the word at memory address 01231_{16} of an 8086-based microcomputer aligned or misaligned? How many cycle are required to read it from memory?

▶ Solution:


The first byte of the word is the second byte at the aligned-word address 01230_{16} . Therefore, the word is misaligned and required two bus cycles to be read from memory.

8.9 Address Bus Status Codes

- Whenever a memory bus cycle is in progress, an address bus status code S_4S_3 is output by the processor.
- S_4S_3 identifies which one of the four segment register is used to generate the physical address in the current bus cycle:
 - $S_4S_3 = 00$ identifies the extra segment register (ES)
 - $S_4S_3 = 01$ identifies the stack segment register (SS)
 - $S_4S_3 = 10$ identifies the code segment register (CS)
 - $S_4S_3 = 11$ identifies the data segment register (DS)
 - **Since each combination of S_4S_3 leads to select different memory segment,** the memory address reach of the microprocessor can thus be expanded to 4 Mbytes.

8.10 Memory Control Signals

- Minimum-mode memory control signals

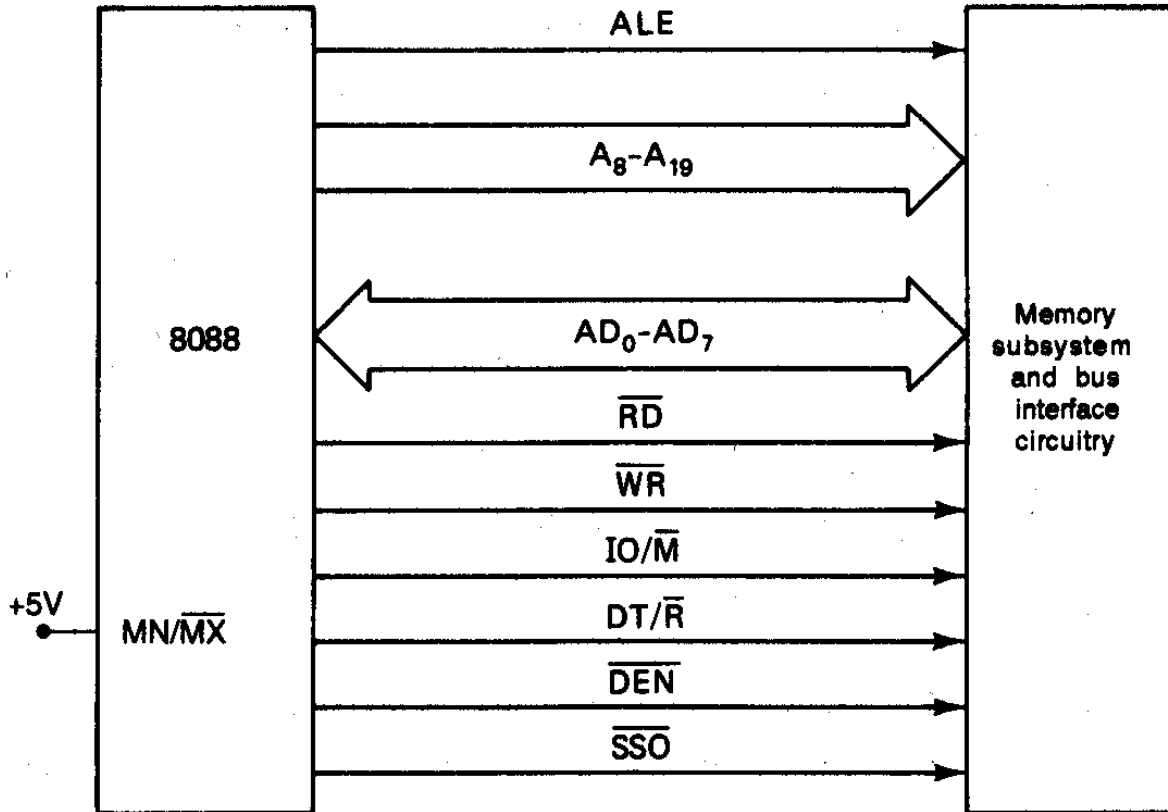

8.10 Memory Control Signals

- **Minimum-mode memory control signals**
 - **ALE – Address Latch Enable** – used to latch the address in external memory (valid address on the bus).
 - **IO/M’ – Input-Output/Memory** – signal external circuitry whether a memory or I/O bus cycle is in progress.
 - **DT/R’ – Data Transmit/Receive** – signal external circuitry whether the 8088 is transmitting or receiving data over the bus.
 - **RD’ – Read** – identifies that a read bus cycle is in progress.
 - **WR’ – Write** – identifies that a write bus cycle is in progress.
 - **DEN’ – Data Enable** – used to enable the data bus.
 - **SSO’ – Status Line** – identifies whether a code or data access is in progress.

8.10 Memory Control Signals


- The control signals for the 8086's minimum mode memory interface differs in three ways:
 - IO/M signal is replaced by M/IO signal.
 - The signal SSO is removed from the interface.
 - BHE (bank high enable) is added to the interface and is used to select input for the high bank of memory in the 8086's memory subsystem.

8.10 Memory Control Signals

- Maximum-mode memory control signals
 - MRDC – Memory Read Command
 - MWTC – Memory Write Command
 - AMWC – Advanced Memory Write Command

Status Inputs			CPU Cycle	8288 Command
\bar{S}_2	\bar{S}_1	\bar{S}_0		
0	0	0	Interrupt acknowledge	\overline{INTA}
0	0	1	Read I/O port	\overline{IORC}
0	1	0	Write I/O port	$\overline{IOWC}, \overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction fetch	\overline{MRDC}
1	0	1	Read memory	\overline{MRDC}
1	1	0	Write memory	$\overline{MWTC}, \overline{AMWC}$
1	1	1	Passive	None


8.11 Read and Write Bus Cycle

 

Minimum-mode memory read bus cycle of the 8088

- Read bus cycle timing diagram—shows relationship between signals relative to times states
- T1 state—read cycle begins
 - Address output on A0–A19
 - Pulse produced at ALE—address should be latched in external circuitry on trailing edge of ALE
 - IO/M* set to 0 → memory bus cycle
 - DT/R* set to 0 → set external data bus control circuitry for receive mode (read)
- T2 state
 - Status code output on S3–S6
 - AD0 through AD7 tri-stated in preparation for data bus operation
 - RD* set to 0 → read cycle
 - DEN* set to 0 → enable external data bus control circuitry
- T3 state
 - Data on D0–D7 read by the MPU
- T4 state—read cycle finishes
 - RD* returns to 1 → inactive level
 - Complete address/data bus tristate
 - IO/M* returned to 1 → IO bus cycle
 - DEN* returned to 1 → inactive level
 - DT/R* returns to 1 → transmit level

8.11 Read and Write Bus Cycle

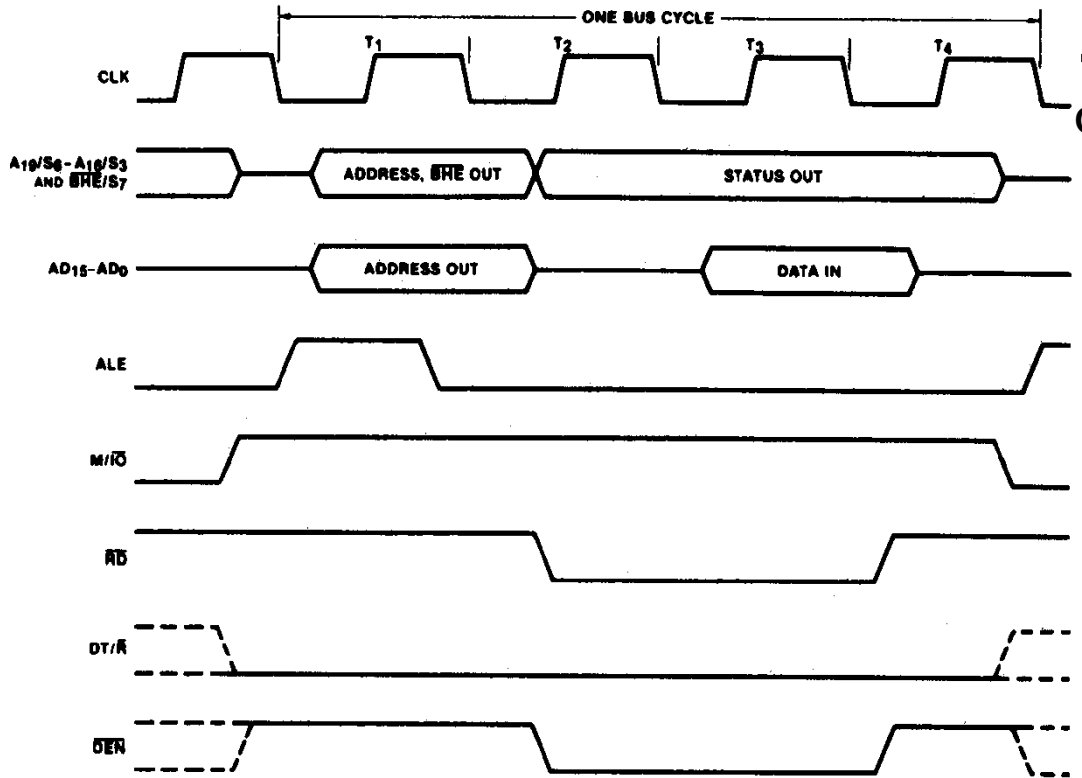


• Differences of 8086 read bus cycle

- BHE* is output along with the address in T1
- Data read by the MPU can be carried over all 16 data bus lines
- M/IO*—which replaces IO/M*—switches to 1 instead of 0 at the beginning of T1
- SSO* signals is not produce

Minimum-mode memory read bus cycle of the 8086

8.11 Read and Write Bus Cycle

□ Read cycle

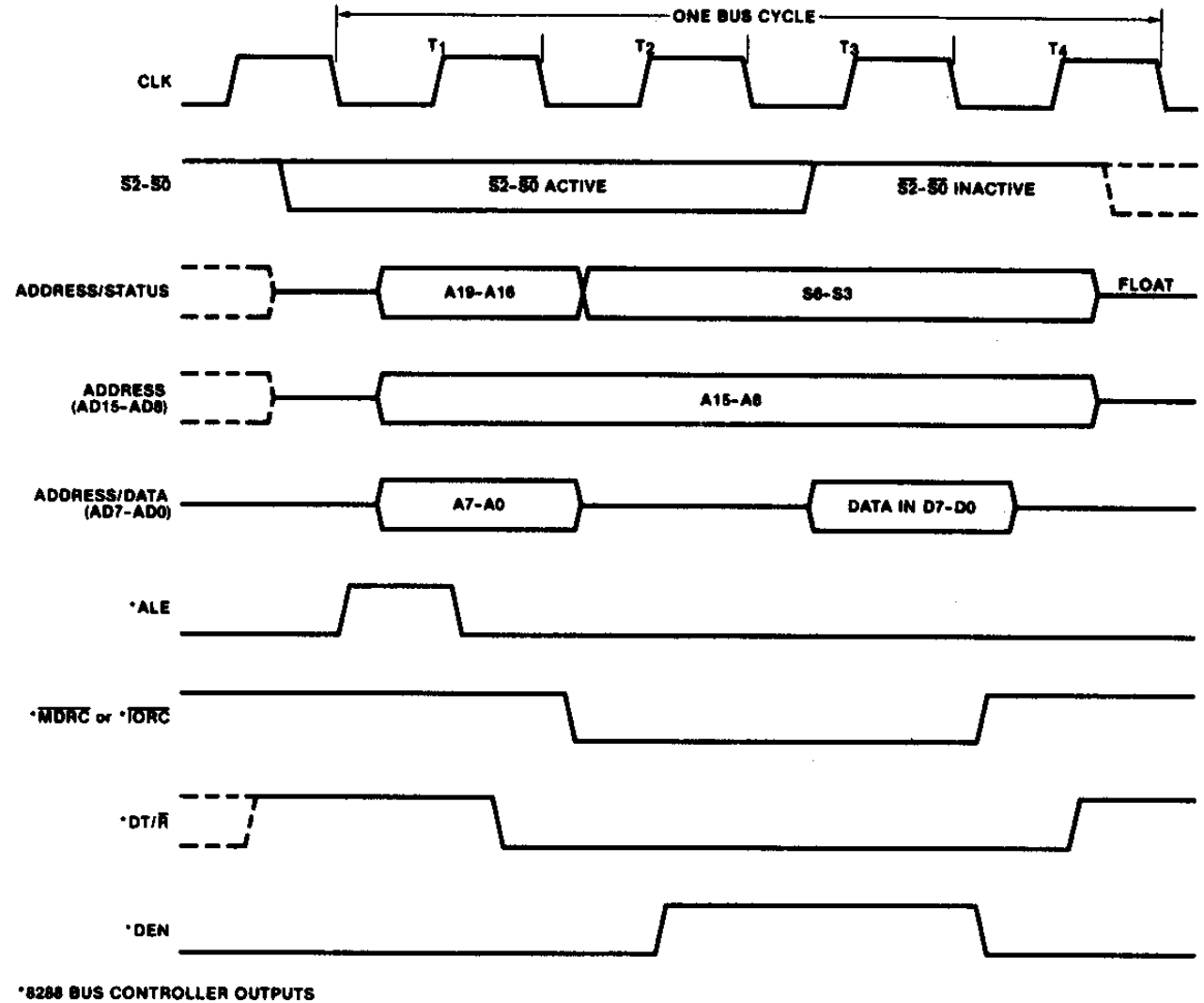

Maximum-mode memory read bus cycle of the 8086

8.11 Read and Write Bus Cycle

• Write bus cycle timing diagram—shows relationship between signals relative to times states

• T1 state—write cycle begins

- Address output on A0–A19
- Pulse produced at ALE and address latched in external circuitry on trailing edge of ALE
- IO/M* set to 0 → memory bus cycle
- DT/R* remains at 1 → external data bus control circuitry for transmit mode (write)

• T2 state


- Status code output on S3–S6
- AD0 through AD7 transitioned to data bus and write data placed on bus
- DEN* set to 0 → enable external data bus control circuitry
- WR* set to 0 → write cycle

• T3 or T4 state

- Data on D0–D7 written into memory (memory decides when!)


• T4 state—write cycle finishes

 - WR* returns to 1 → inactive level
- Complete address/data bus tri-stated
- IO/M* returned to 1 → IO bus cycle
- DEN* returned to 1 → inactive level



Minimum-mode memory write bus cycle of the 8088


8.11 Read and Write Bus Cycle

 

- Similar to 8088/8086 minimum-mode write bus cycle
 - Address and data transfer operation identical
 - Transfer may be a high-byte, low-byte, word
- Differences is the 8288 produces the bus control signals—ALE, DEN, AMWC*, and MWTC*
 - Bus status code S2*–S0* output prior to T1 and held through T2
 - AMWC* and MWTC* replace WR* (Note timing difference)
 - DEN =1 produced instead of DEN* =0 (change in external circuitry!)

Maximum-mode memory write bus cycle of the 8088

8.12 Memory Interface Circuit

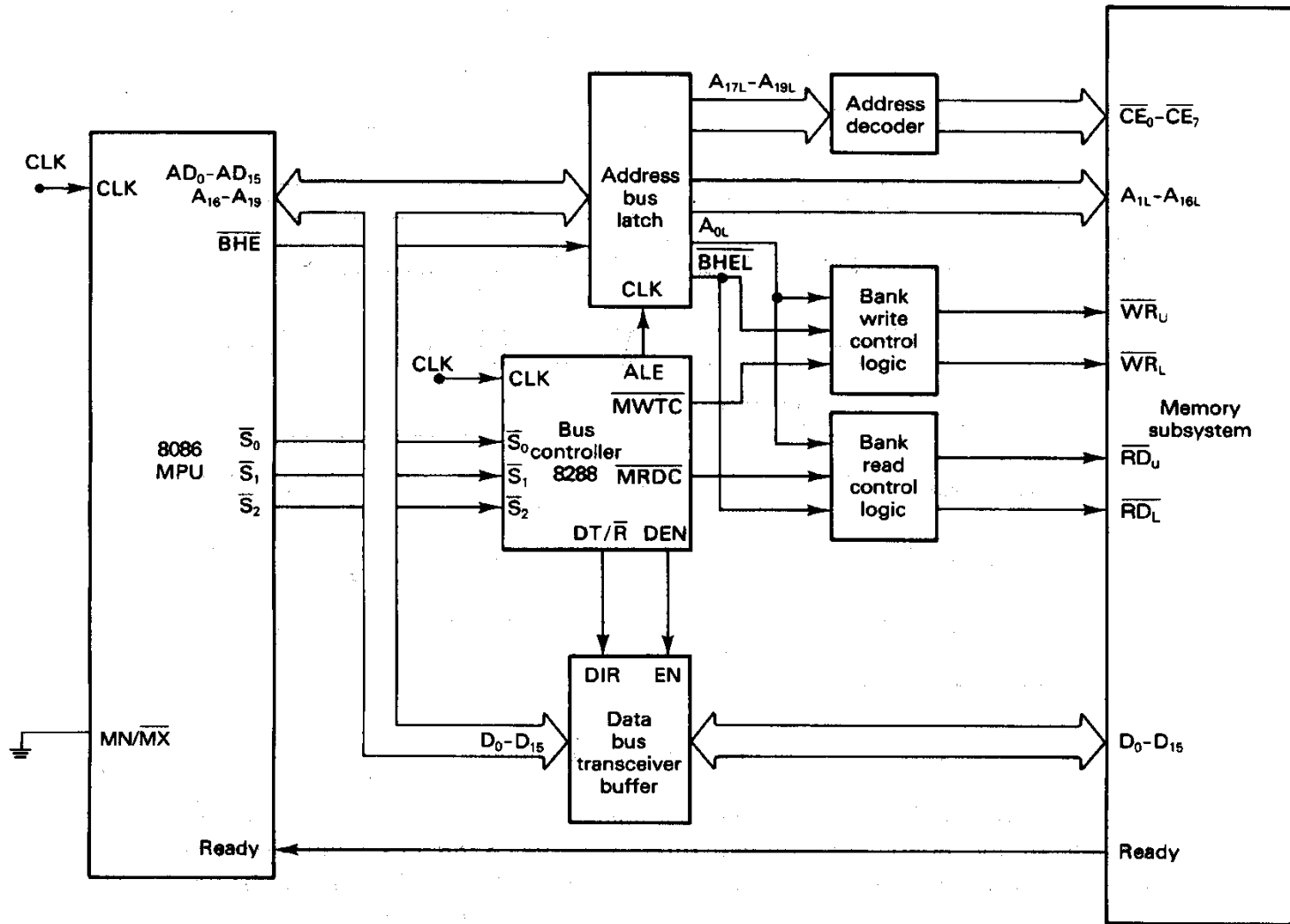


Memory interface block diagram

8.12 Memory Interface Circuit

- Address bus latches and buffers
- Bank write and bank read control logic
- Data bus transceivers/buffers
- Address decoders

8.12 Memory Interface Circuit

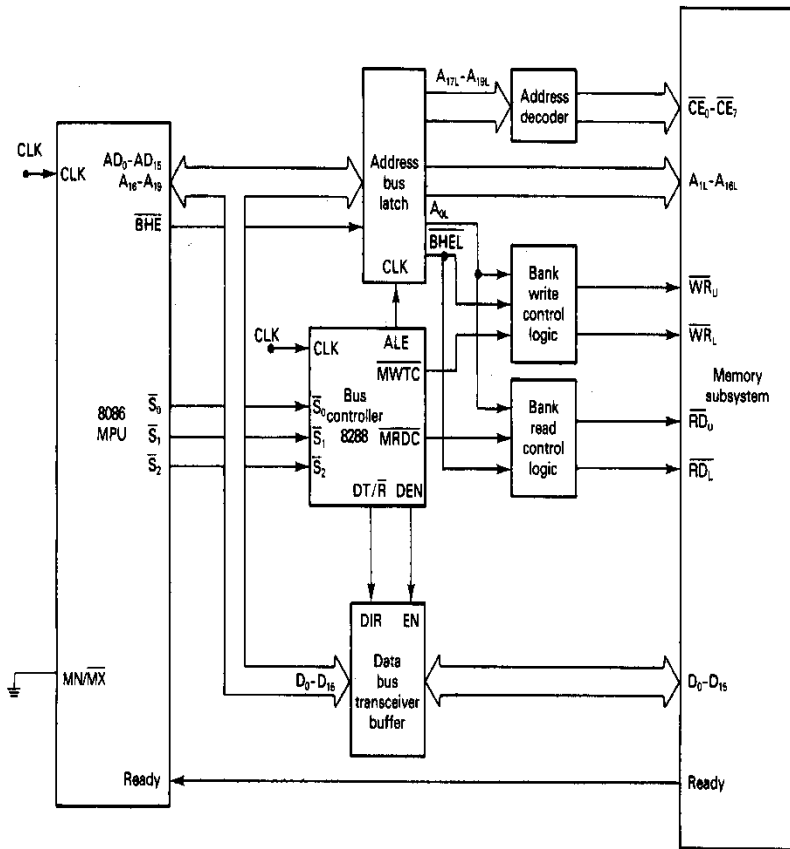


Memory interface block diagram


- Overview of the memory access
 - Bus status code for type of memory access output to 8288 on S₂*-S₀*
 - 8288 decodes to produce the command and control signals need to coordinate the data transfer
 - Address is latched, buffered, and decoded to:
 - Produce chip enable signals for the memory array
 - Select a specific memory location
 - Select upper, lower, or both banks of the memory array
 - MWTC* and MRDC* combined with A_{0L} and BHEL* to set the appropriate bank(s) of the memory array for write or read, respectively
 - DT/R* and DEN are used to enable the data bus transceiver/buffer and set it for the transmit (write) or receive (read) direction

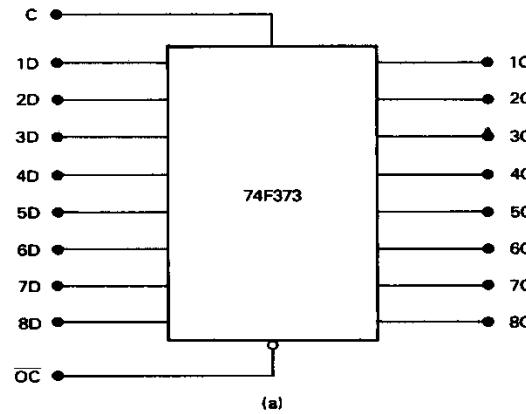8.12 Memory Interface Circuit

- Roles of the address latch
 - Latch address signals A₀–A₁₉ and BHE*
 - Buffer signals so that they may be used to drive a large memory system, IO peripherals, and other interfaces
- Requirements
 - 21 bit wide latch/buffer
 - Low propagation delay– allows use of slower memories
- 74F373—Octal D-type latch
 - 8 independent buffered D-type flipflops (latches)
 - Enable to output propagation delay = 13 ns
 - Outputs sink 24 mA (buffering)
 - Output Control (OC*) = 0 enables latch circuits



Block diagram of a D-type latch

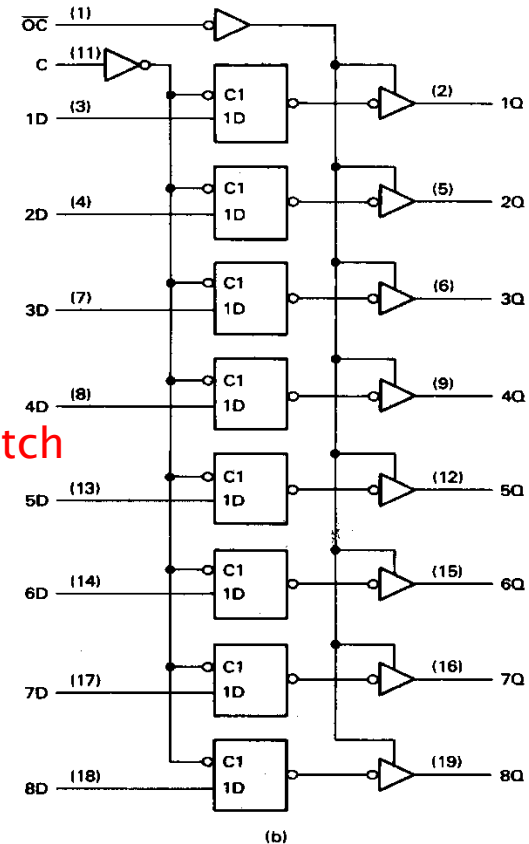

Circuit diagram of the 74F373


Operation of the 74F373

Inputs			Output
\overline{OC}	Enable C	D	Q
L	H	H	H
L	H	L	L
L	L	X	Q _o
H	X	X	Z

Address bus latches and buffers (c)

8.12 Memory Interface Circuit

□ Address bus latches and buffers

 


Address latch circuit

- Implemented with 3 74F373 Octal-D-type latches
 - Inputs AD₀-AD₁₅, A₁₆-A₁₉, and BHE* from MPU
 - All devices permanently enabled by fixing the OC* inputs at logic 0
 - All latches clocked in parallel with pulse at ALE from 8288
 - Latched and buffered outputs are: A_{0L}-A_{19L}, and BHEL*
 - Parts of address applied to the address inputs of memory subsystem, address decoder, and read/write control logic

 8.12 Memory Interface Circuit


- Role of write control logic
- Memory array is organized in upper and lower banks
- Types of data writes that may take place:
 - Byte to a storage location in the upper (odd) bank
 - Byte to a storage location in the lower (even) bank
 - Word to storage locations in both banks
- Write control logic must decode A_{0L} , $BHEL^*$, and $MWTC^*$ to produce independent write signals— WRU^* and WRL^*
- 7432—2-input OR gate solution
- $MWTC^*(MWRC^*) = 0$ enables both gates



Bank write control logic

$BHEL^*$	A_{0L}	WRU^*	WRL^*	Result
0	0	0	0	Both banks enabled
1	0	1	0	Lower (even) bank enabled
0	1	0	1	Upper (odd) bank enabled

8.12 Memory Interface Circuit

 



Bank read control logic

\overline{BHEL}^*	A_{0L}	$\overline{RD_U}^*$	$\overline{RD_L}^*$	Result
0	0	0	0	Both banks enabled
1	0	1	0	Lower (even) bank enabled
0	1	0	1	Upper (odd) bank enabled

- Role of read control logic
 - Types of data reads that may take place:
 - Byte from the lower (even) bank
 - Byte from upper (odd) bank
 - Word of data from both banks or an instruction fetch
 - Read control logic must decode A_{0L} , \overline{BHEL}^* , and \overline{MRDC}^* to produce independent read signals— $\overline{RD_U}^*$ and $\overline{RD_L}^*$
 - 7432-based solution is similar to bank write control logic
 - $\overline{MRDC}^* = 0$ enables both gates

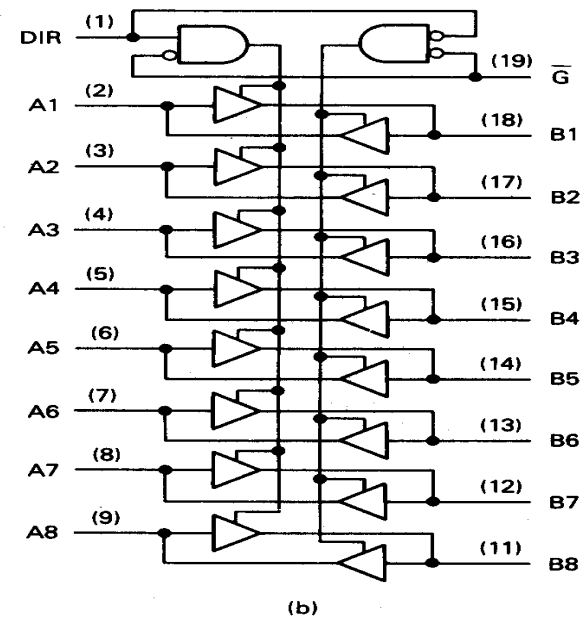 
8.12 Memory Interface Circuit

- Roles of the data bus transceiver/buffer
 - Set the direction of the data path between memory and the MPU bus
 - Appropriately time the enabling of the transceivers to coincide with the read/write data transfer
 - Buffer the data bus lines so that they may be used to drive a large memory system, IO peripherals, and other interfaces
- Requirements
 - 8/16 bit wide bi-directional transceiver
 - Low propagation delay- allows use of slower memories
- 74F245—Octal bi-directional bus transceiver
 - 8 independent bus transceivers
 - DIR input selects direction of data transfer
 - 0 = B to A → read
 - 1 = A to B → write
 - $G^* = 0$ enables all transceivers
 - Outputs sink 64 mA (buffering)



Block diagram and circuit diagram of the 74F245 octal bus transceiver


8.12 Memory Interface Circuit

 

Data bus transceiver circuit

- Implemented with 2 74F245 Octal bi-directional bus transceivers
 - A inputs/outputs are D₀-D₁₅ directly from MPU
 - Direction of both devices set by logic level of DT/R*
 - Both devices enabled at appropriate time for data transfer by DEN=1
 - B inputs/outputs are the buffered data bus lines DB₀ through DB₁₅
 - Buffered data bus lines applied directly to the memory subsystem

8.12 Memory Interface Circuit


 


Address bus configuration with address decoding

- **Role of address decoder**
 - Part of the buffered/latched address is decoded to create chip enables
 - Address inputs A_{19L} A_{18L} A_{17L} is decoded to produce 8 independent chip enable outputs \overline{CE}_0^* through \overline{CE}_7^*

  8.12 Memory Interface Circuit

- Requirements of Address Decoder
 - Requires standard decoder/multiplexer functions
 - 2-input 4-output—74F139
 - 3-input 8-output—74F138
 - 74F139 decoder/multiplexer
 - Dual 2-input 4-output decoder/multiplexer
 - Two-bit input BA
 - Four independent outputs Y0 through Y3
 - G^* input enables the associated decoder
- Operation
 - $G^* = 1$ forces all outputs to 1
 - $G^* = 0$ enables circuit and the Y output associated with the input code switches to the active 0 level



INPUTS			OUTPUTS			
ENABLE	SELECT		Y0	Y1	Y2	Y3
\bar{G}	B	A	Y0	Y1	Y2	Y3
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H	L	H
L	H	H	H	H	H	L


(c)

Block diagram, operation and circuit diagram of the 74F139 decoder

 8.12 Memory Interface Circuit

□ Address decoder


- 3-input 8-output address decoder made with two 2-input 4-output decoder/multiplexer circuits
 - $A_{19L} = 0$ makes $1G^* = 0$ and $2G^* = 1$ and enables outputs $CE_0^* - CE_3^*$
 - $A_{19L} = 1$ makes $1G^* = 1$ and $2G^* = 0$ and enables $CE_4^* - CE_7^*$
 - Code at A_{18L} A_{17L} applied to the BA inputs of both multiplexers in parallel
 - Output associated with the input code on the enabled decoder becomes active




Address decoder circuit using 74F139

8.12 Memory Interface Circuit

- Address decoder

 

 Block diagram, operation and circuit diagram of the 74F138 decoder




ENABLE INPUTS			SELECT INPUTS			OUTPUTS							
G1	G2A	G2B	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	X	H	H	H	H	H	H	H	H
X	X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	L	L	H	H	H	L	H	H	H	H	H
H	L	L	L	L	L	H	H	H	H	L	H	H	H
H	L	L	L	L	H	H	H	H	H	L	H	H	H
H	L	L	L	L	L	H	H	H	H	H	L	H	H
H	L	L	L	L	H	H	H	H	H	H	L	H	H
H	L	L	L	L	L	H	H	H	H	H	H	L	L

(c)

8.12 Memory Interface Circuit

- Address decoder

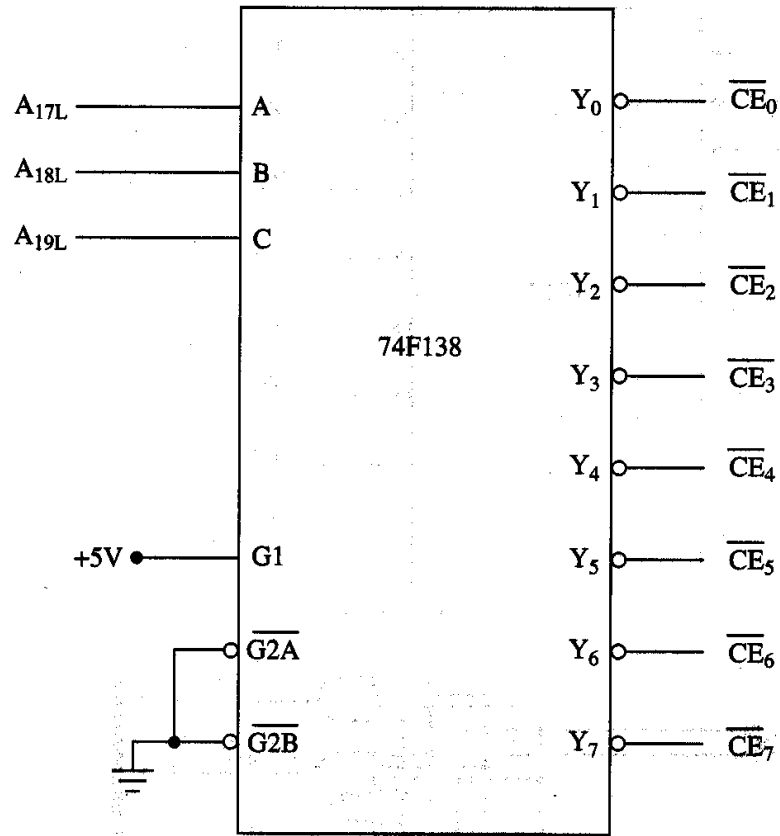

Address decoder circuit using 74F138

8.13 Programmable Logic Arrays

- **Programmable logic array, PLA,** are general purpose logic devices that have the ability to perform a wide variety of specialized logic functions.
- A PLA contains a general-purpose AND-OR-NOT array of logic gate circuits.
- The process used to connect or disconnect inputs of the AND gate array is known as programming, which leads to the name programmable logic array.

8.13 Programmable Logic Arrays

- Major types of programmable logic architecture
 - Simple Programmable Logic Devices (SPLDs)
 - PAL, GAL, PLA, EPLD
 - Complex Programmable Logic Devices (CPLDs)
 - EPLD, PEEL, EEPLD, MAX
 - Field Programmable Gate Arrays (FPGAs)
 - LCA, pASIC, FLEX, APEX, ACT, ORCA, Virtex, pASIC
 - Field Programmable InterConnect (FPICs)




8.13 Programmable Logic Arrays

- PLAs, GALs, and EPLDs
 - Early PLA devices were all manufactured with the bipolar semiconductor process.
 - Bipolar devices are programmed with an interconnect pattern by burning out fuse links within the device.
 - PLAs made with bipolar technology are characterized by slower operating speeds and higher power consumption.
 - Two kinds of newer PLA, manufactured with the CMOS process, are in wide use today: the **GAL** and **EPLD**.

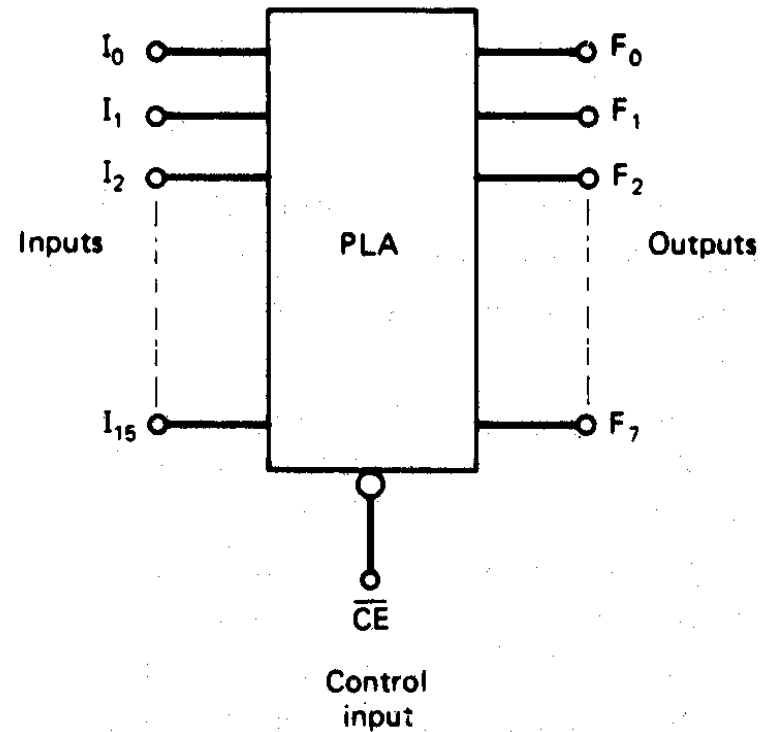8.13 Programmable Logic Arrays


- ▶ Block diagram of a PLA
 - The logic levels applied at inputs I_0 through I_{15} and the programming of the AND array determine what logic levels are produced at outputs F_0 through F_{15} .
 - The capacity of a PLA is measured by three properties: the number of inputs, the number of outputs, and the number of product terms (P-terms)




Block diagram of a PLA

8.13 Programmable Logic Arrays

► Architecture of a PLA

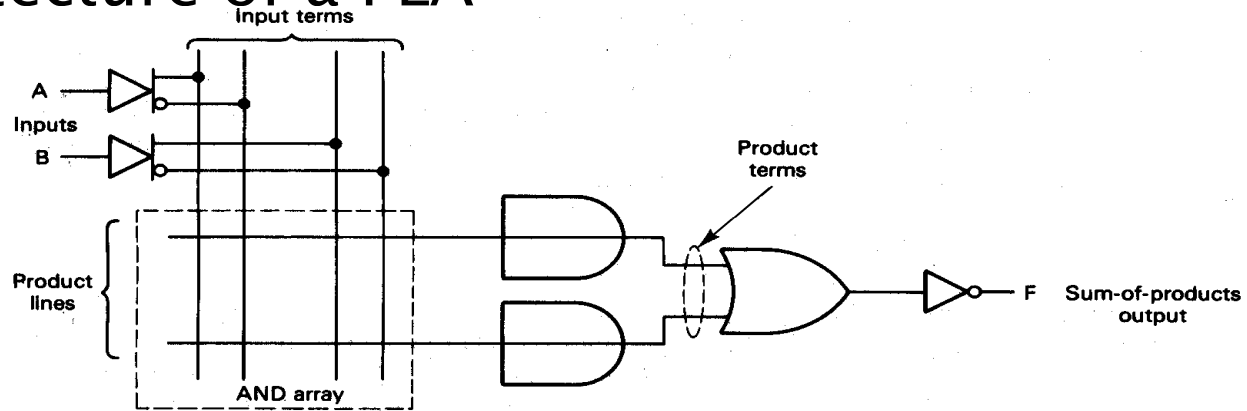



(a)

 

(b)

8.13 Programmable Logic Arrays

▶ Architecture of a PLA

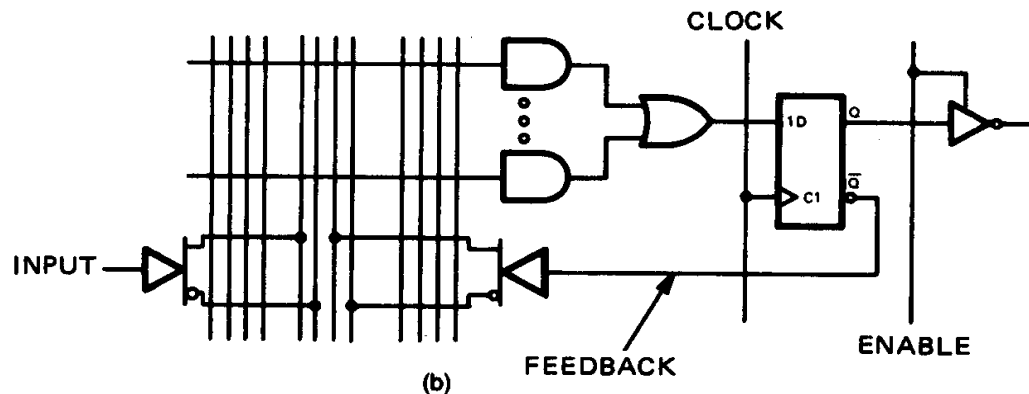 



(a) Typical PLA architecture. (b) PLA with output latch

8.13 Programmable Logic Arrays

- Standard PAL™ device
 - A PAL, programmable array logic, is a PLA in which the OR array is fixed; only the AND array is programmable.
 - The 16L8 is a widely used PAL IC. It is housed in a 20-pin package. It has 10 dedicated input, 2 dedicated outputs, and 6 programmable I/O lines.
 - The 16L8 is manufactured with bipolar technology. It operates from a $+5V \pm 10\%$ dc power supply and draw a maximum of 180mA.
 - The 20L8 has 20 inputs, 8 outputs and 64 P-terms.
 - The 20R8 is the register output version of 20L8.

8.13 Programmable Logic Arrays

□ Standard PAL™ device

  


16L8 circuit diagram and pin layout

8.13 Programmable Logic Arrays

- Standard PAL™ device

20L8 circuit diagram and pin layout

 


(a)


8.13 Programmable Logic Arrays

- Expanding PLA capacity

Expanding output word length

 

Expanding input word length

 


8.14 Types of Input/Output

- Isolated input/output
 - When using isolated I/O in a microcomputer system, the I/O device are treated separate from memory.
 - The memory address space contains 1 M consecutive byte address in the range 00000H through FFFFFH; and that the I/O address space contains 64K consecutive byte addresses in the range 0000H through FFFFH.
 - All input and output data transfers must take place between the AL or AX register and I/O port.

8.14 Types of Input/Output


- Isolated input/output

 

8088/8086 memory and I/O address spaces

8.14 Types of Input/Output

□ Isolated input/output

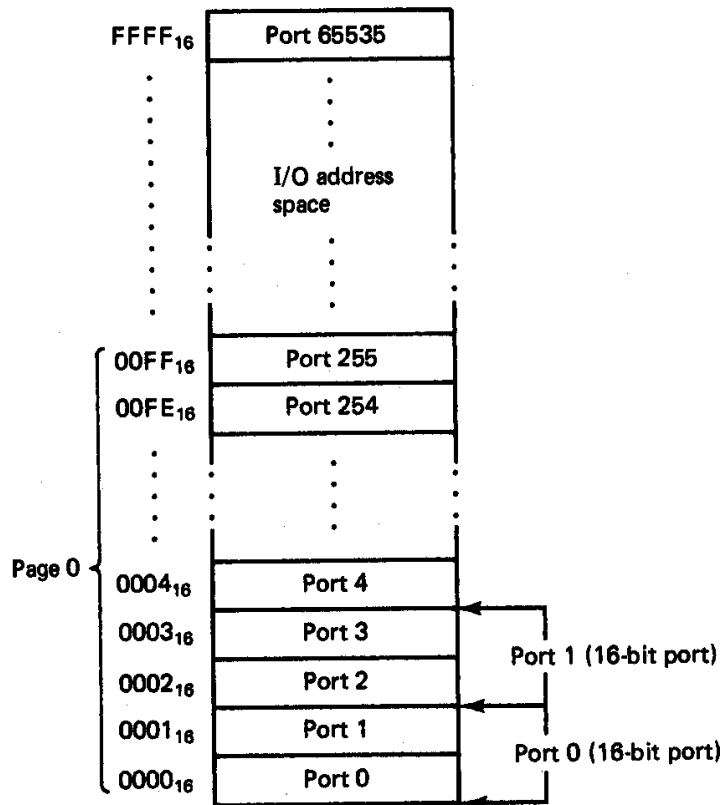

Isolated I/O ports

- Input/output data organization
 - Supports byte and word I/O ports
 - 64K independent byte-wide I/O ports
 - 32K independent aligned word-wide I/O ports
 - Word ports may also be misaligned
 - Examples:
 - Byte ports 0,1,2 → addresses 0000H, 0001H, and 0002H
 - Word ports 0,1,2 → addresses 0000H, 0002H, 0004H
 - Advantages of isolated I/O
 - Complete memory address space available for use by memory
 - I/O instructions tailored to maximize performance
 - Disadvantage of Isolated I/O
 - All inputs/outputs must take place between an I/O port and accumulator register (A)

8.14 Types of Input/Output

□ Isolated input/output

▪ Input/output data organization

- All I/O accesses take either one or two bus cycles

- Byte input/output = 1 bus cycle
- Aligned word input/output = 1 bus cycle—on 8086


- Misaligned word input/output = 2 bus cycles

▪ Page 0

- First 256 byte addresses → 0000H – 00FFH

- Can be accessed with direct or variable I/O instructions

- Ports F8H through FFH reserved

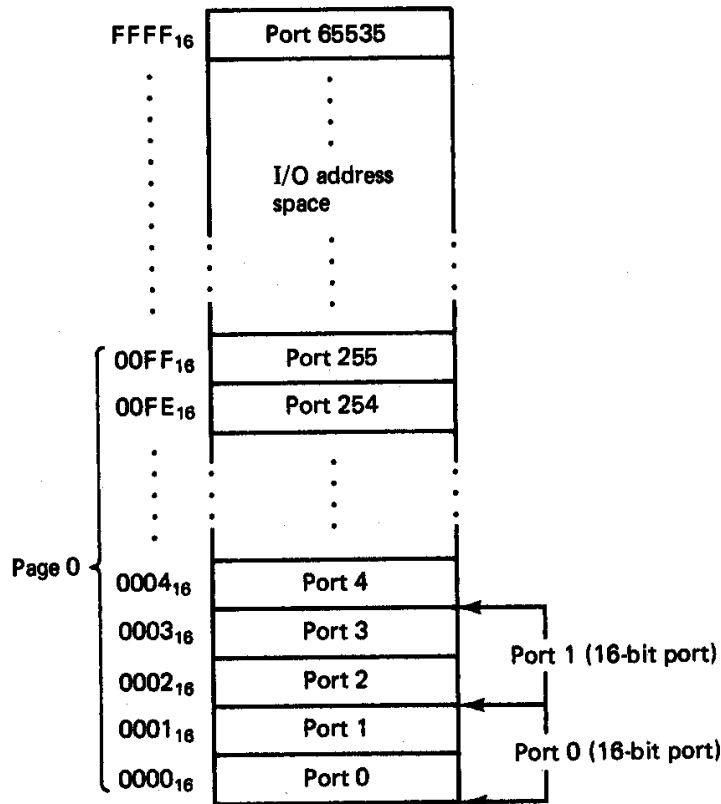


Isolated I/O ports

8.14 Types of Input/Output

- Memory-mapped input/output
 - In the case of memory-mapped I/O, MPU looks at the I/O port as though it is a storage location in memory.
 - Some of the memory address space is dedicated to I/O ports.
 - Instructions that affect data in memory are used instead of the special I/O instructions.
 - The memory instructions tend to execute slower than those specifically designed for isolated I/O.

8.14 Types of Input/Output

□ Memory-mapped input/output

 

Memory mapped I/O ports

- Example:
 - E0000H–E0FFFH → 4096 memory addresses assigned to I/O ports
 - E0000H, E0001H, and E0002H correspond to byte-wide ports 0,1, and 2
 - E0000H and E0001H correspond to word-wide port 0 at address E0000H
- Advantages of memory mapped I/O
 - Instructions that affect data in memory (MOV, ADD, AND, etc.) can be used to perform I/O operations
 - I/O transfers can take place between and I/O port and any of the registers
- Disadvantage of memory mapped I/O
 - Memory instructions perform slower
 - Part of the memory address space cannot be used to implement memory

8.15 Isolated Input/Output Interface

- I/O devices:
 - Keyboard (input)
 - Printer (output)
 - Mouse (input)
 - 82C55A, etc. (PPI section .13)
- Functions of interface circuit:
 - Select the I/O port
 - Latch output data
 - Sample input data
 - Synchronize data transfer
 - Translate between TTL voltage levels and those required to operate the I/O devices.


8.15 Isolated Input/Output Interface

□ Minimum-mode interface:

- Similar in structure and operation to memory interface
 - I/O devices—can represent LEDs, switches, keyboard, serial communication port, printer port, etc.
 - I/O data transfers take place between I/O devices and MPU over the multiplexed-address data bus
 - AD0–AD7
 - A8–A15
- Control signal review
 - ALE = pulse to logic 1 tells bus interface circuitry to latch I/O address
 - RD* = logic 0 tells the I/O interface circuitry that an input (read) is in progress
 - WR* = logic 0 tells the I/O interface circuitry that an output (write) is in progress
 - IO/M* = logic 1 tells I/O interface circuits that the data transfer operation is for the IO subsystem
 - DT/R* = sets the direction of the data bus for input (read) or output (write) operation
 - DEN* = enables the interface between the I/O subsystem and MPU data bus

8.15 Isolated Input/Output Interface


- Minimum-mode interface:

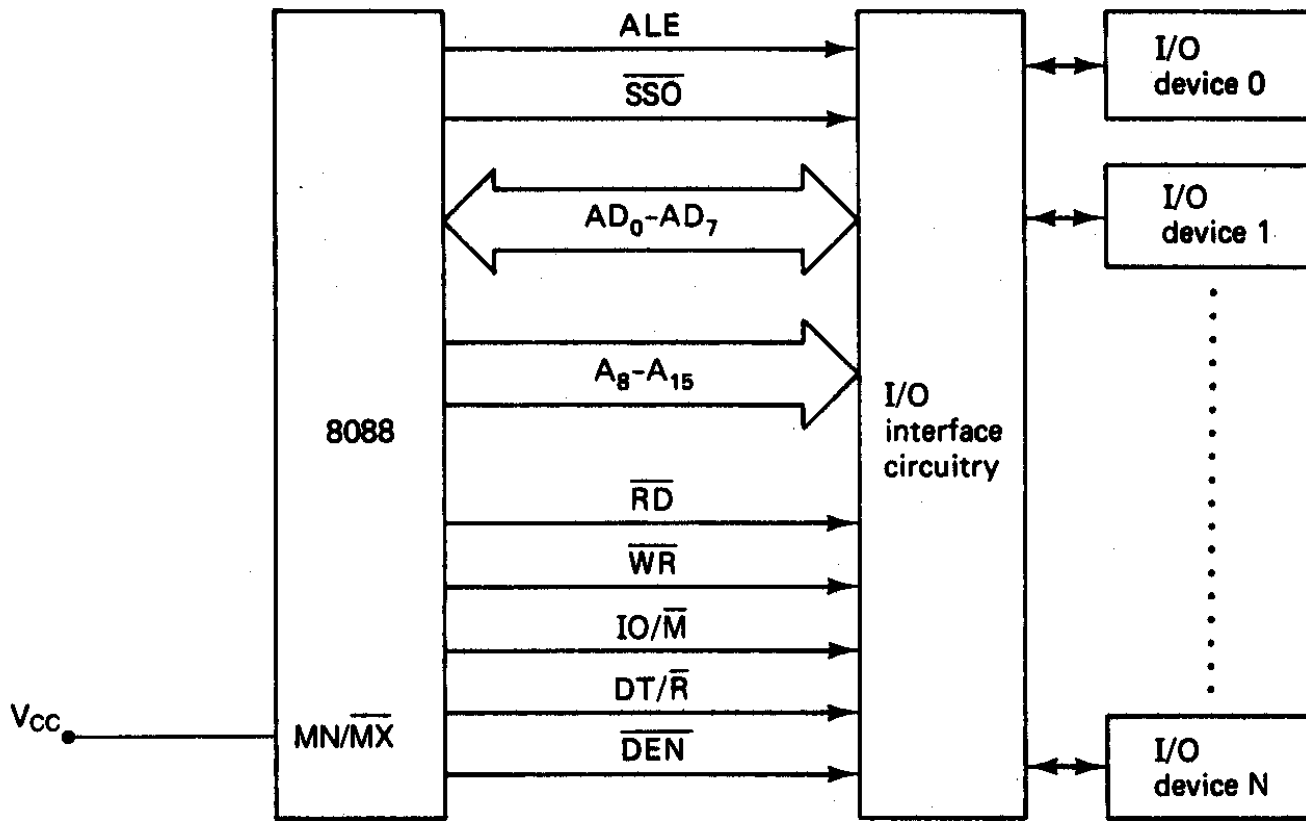

Minimum-mode 8088 system I/O interface

8.15 Isolated Input/Output Interface


- Minimum-mode interface:

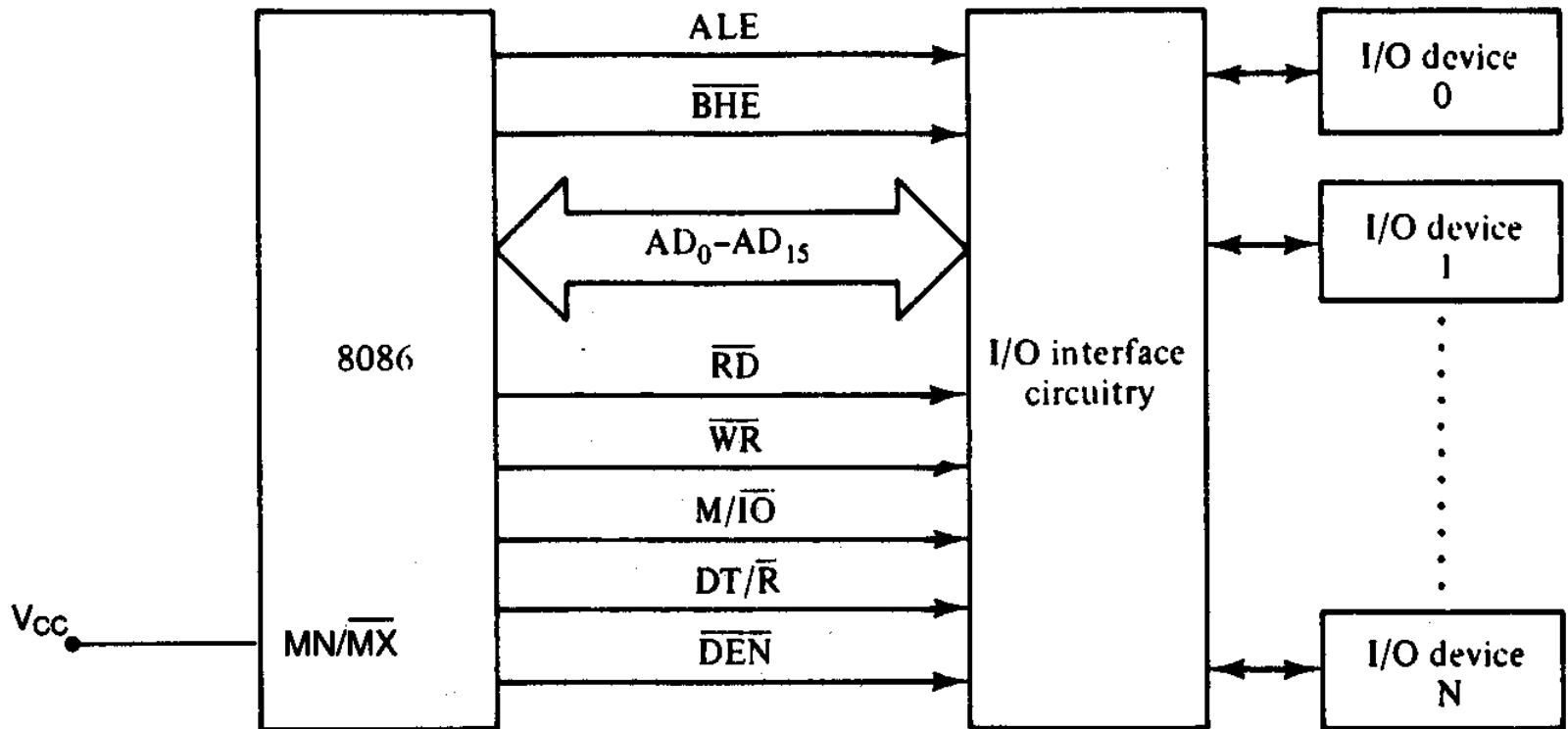

Minimum-mode 8086 system I/O interface

8.15 Isolated Input/Output Interface

- Maximum -mode interface:

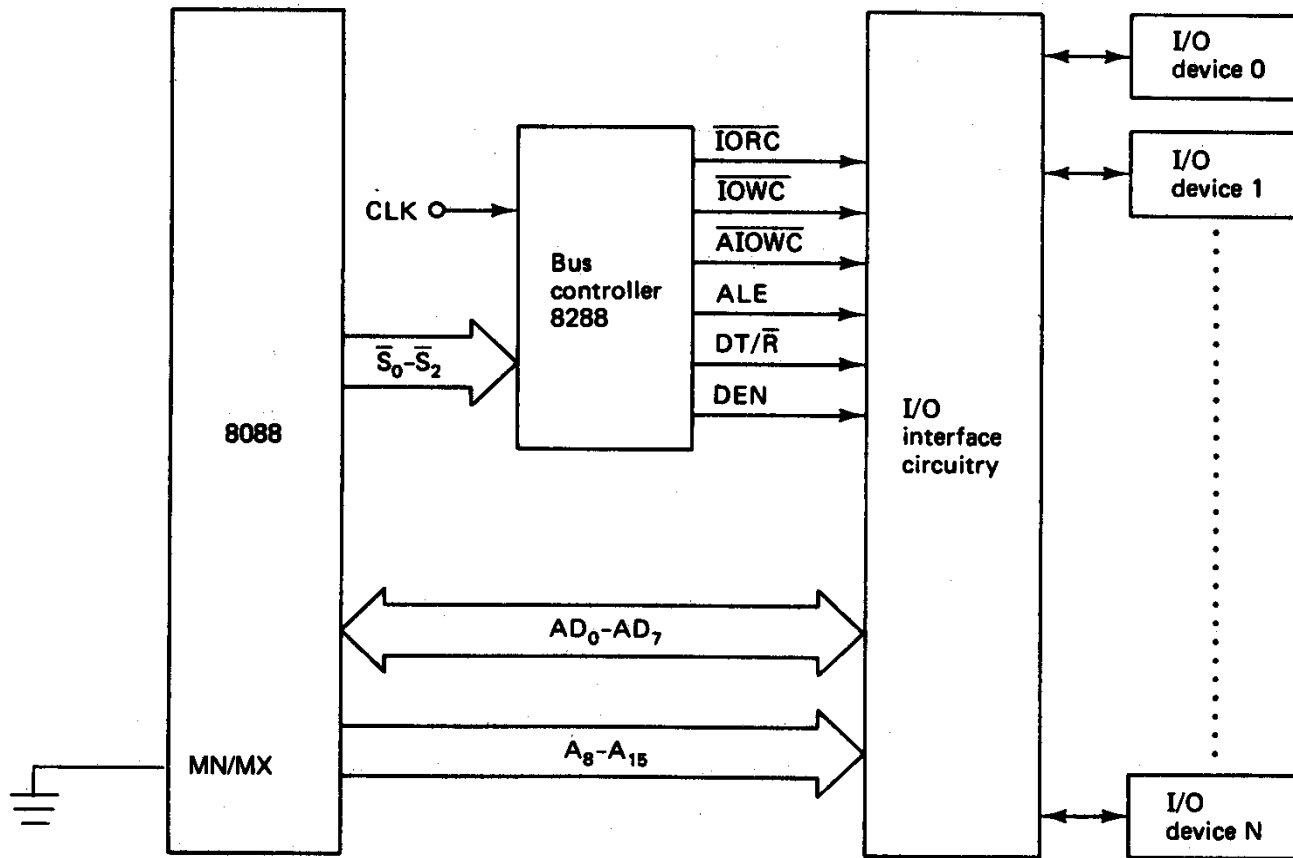


Maximum-mode 8088 system I/O interface

8.15 Isolated Input/Output Interface

- Maximum –mode interface:
 - 8288 bus controller produces the control signals
 - Signal changes
 - IORC* replaces RD*
 - IOWC* and AIOWC* replace WR*
 - DEN is complement of DEN*
 - IO/M* no longer needed (bus controller creates separate IO read/write controls)
 - SSO* no longer part of interface

8.15 Isolated Input/Output Interface

- Maximum -mode interface:

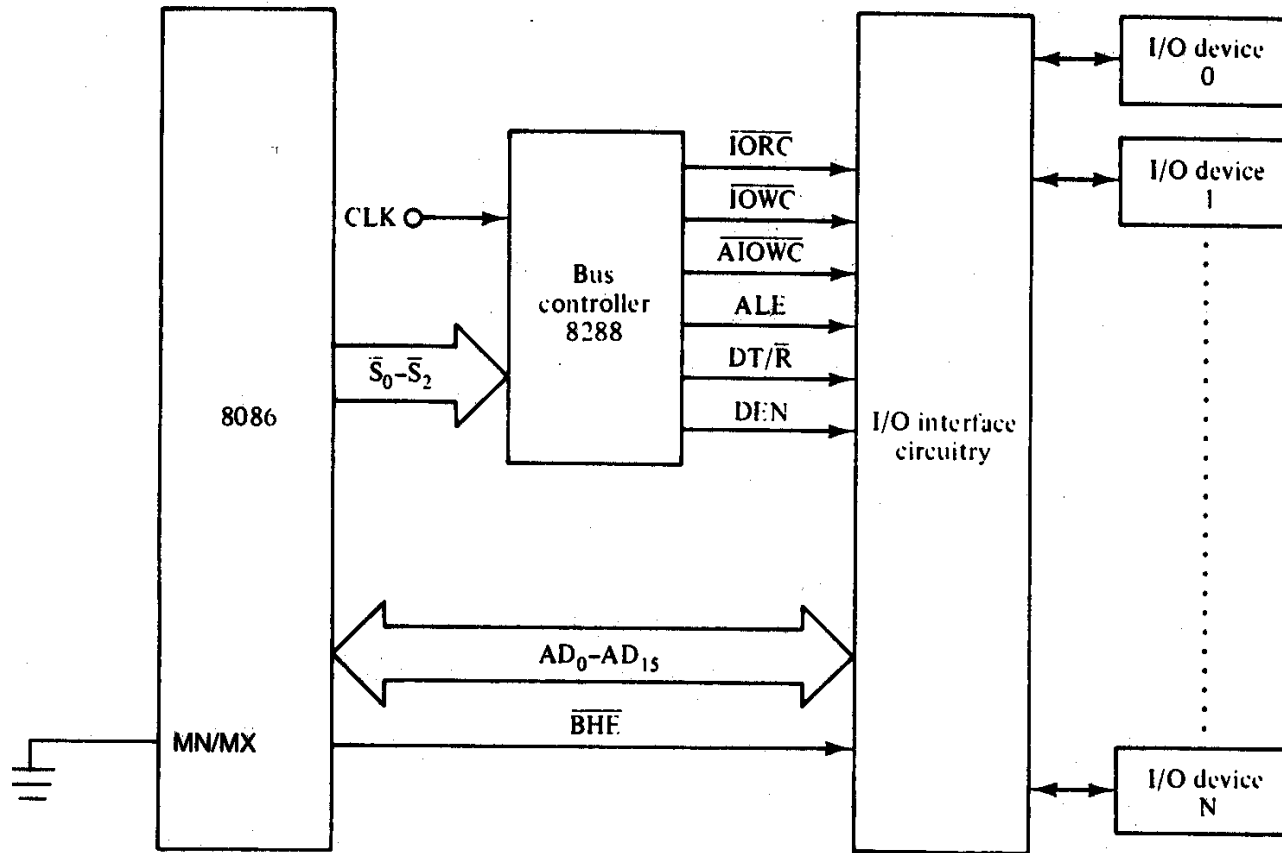

Maximum-mode 8086 system I/O interface

8.15 Isolated Input/Output Interface

□ Maximum –mode interface:

Status inputs			CPU cycle	8288 command
\bar{S}_2	\bar{S}_1	\bar{S}_0		
0	0	0	Interrupt acknowledge	\overline{INTA}
0	0	1	Read I/O port	\overline{IORC}
0	1	0	Write I/O port	$\overline{IOWC}, \overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction fetch	\overline{MRDC}
1	0	1	Read memory	\overline{MRDC}
1	1	0	Write memory	$\overline{MWTC}, \overline{AMWC}$
1	1	1	Passive	None

I/O bus cycle status codes

- Bus status code review
 - During all I/O accesses one of two bus cycle status code are output by the MPU
 - Read I/O port
 - Write I/O port
 - 8288 decodes to produce appropriate control command signals
 - $IORC^* \rightarrow$ input (read I/O)
 - $IOWC^* \rightarrow$ output (write I/O)
 - $AIOWC^* \rightarrow$ output (write I/O)

8.16 Input/Output Data Transfers

- Input/output data transfers in the 8088 and 8086 microcomputers can be either **byte-wide** or **word-wide**.
- **The port that is to be addressed is specified by the IO address.**
- I/O addresses are 16 bits in length and are output by the 8088 to the I/O interface over bus lines AD₀ through AD₇ and A₈ through A₁₅.**why?**
- In 8088, the word transfers is performed as two consecutive byte-wide data transfer and takes two bus cycle.
- In 8086, the word transfers can takes either one or two bus cycle.
- Word-wide I/O ports should be aligned at even-address boundaries **to ensure that one cycle is enough to complete the word operation.**

8.17 Input/Output Instructions

- Types of instructions
 - Direct I/O instructions—only allow access to ports at page 0 addresses
 - Variable I/O instructions—allows access of ports anywhere in the I/O address space
- Direct I/O instructions

IN Acc,Port

OUT Port,Acc

- Port = 8-bit direct address—limited to 0H through FFH (page 0)
- Acc = accumulator register AX (word transfer); AH or AL (byte transfer)
- Example:

IN AL, 0FEH

(FE) → AL (byte input operation)

- Also known as accumulator I/O—because source or destination must always be in accumulator (Acc) register

Mnemonic	Meaning	Format	Operation
IN	Input direct	IN Acc,Port	(Acc) ← (Port) Acc = AL or AX
	Input indirect (variable)	IN Acc,DX	(Acc) ← ((DX))
OUT	Output direct	OUT Port,Acc	(Port) ← (Acc)
	Output indirect (variable)	OUT DX,Acc	((DX)) ← (Acc)

8.17 Input/Output Instructions

- Types of instructions
 - Direct I/O instructions—only allow access to ports at page 0 addresses
 - Variable I/O instructions—allows access of ports anywhere in the I/O address space
- Variable I/O instructions

IN Acc,DX

OUT DX,Acc

- DX = 16-bit indirect address—allows access to full I/O address space
- Acc = accumulator register AX (word transfer); AH or AL (byte transfer)
- Example:

MOV DX,A000H ;load I/O address

IN AL,DX ;input value to AL

MOV BL,AL ;copy value to BL

(A000H) → BL (byte input operation)

Mnemonic	Meaning	Format	Operation
IN	Input direct	IN Acc,Port	(Acc) ← (Port) Acc = AL or AX
	Input indirect (variable)	IN Acc,DX	(Acc) ← ((DX))
OUT	Output direct	OUT Port,Acc	(Port) ← (Acc)
	Output indirect (variable)	OUT DX,Acc	((DX)) ← (Acc)

8.17 Input/Output Instructions

▶ EXAMPLE

Write a sequence of instructions that will output the data FFH to a byte-wide output port at address ABH of the I/O address space.

▶ Solution:

First, the AL register is loaded with FFH as an immediate operand in the instruction

MOV AL, FFH

Now the data in AL can be output to the byte-wide output port with the instruction

OUT ABH, AL

8.17 Input/Output Instructions

▶ EXAMPLE

Write a series of instructions that will output FFH to an output port located at address B000H of the I/O address space.

▶ Solution:

The DX register must first be loaded with the address of the output port. This is done with the instruction

```
MOV DX, B000H
```

Next, the data that are to be output must be loaded into AL with the instruction

```
MOV AL, FFH
```

Finally, the data are output with the instruction

```
OUT DX, AL
```

8.17 Input/Output Instructions

- ▶ EXAMPLE

Data are to be read in from two byte-wide input ports at addresses AAH and A9H and then output as a word-wide output port at address B000H. Write a sequence of instructions to perform this input/output operation.

- ▶ Solution:

First read in the byte at address AAH into AL and move it into AH.

```
IN AL, AAH  
MOV AH, AL
```

Now the other byte can be read into AL by the instruction


```
IN AL, A9H
```

And to write out the word of data

```
MOV DX, B000H  
OUT DX, AX
```

8.18 Input/Output Bus Cycle

- Input bus cycle of the 8088

 


8.18 Input/Output Bus Cycle

□ Input bus cycle of the 8088

- Input (I/O read) bus cycle timing diagram—shows relationship between signals relative to time states
 - T1 state—input cycle begins
 - Address output on A0–A15
 - Pulse produced at ALE—address should be latched in external circuitry on trailing edge of ALE
 - IO/M* set to 1 → I/O bus cycle
 - DT/R* set to 0 → set external data bus control circuitry for receive mode (input)
 - T2 state
 - Status code output on S3–S6
 - AD0 through AD7 tri-stated in preparation for data bus operation
 - RD* set to 0 → input cycle
 - DEN* set to 0 → enable external data bus control circuitry
 - T3 state
 - Data on D0–D7 input (read) by the MPU
 - T4 state—input cycle finishes
 - RD* returns to 1 → inactive level
 - Complete address/data bus tri-stated
 - IO/M* returned to 0 → memory bus cycle
 - DEN* returned to 1 → inactive level
 - DT/R* returns to 1 → transmit level

8.18 Input/Output Bus Cycle

□ Output bus cycle of the 8088

 


8.18 Input/Output Bus Cycle

□ Output bus cycle timing diagram of the 8088

- T1 state—output cycle begins
 - Address output on A0–A15
 - Pulse produced at ALE and address latched in external circuitry on trailing edge of ALE
 - IO/M* set to 1 → I/O bus cycle
 - DT/R* set to 1 → external data bus control circuitry for transmit mode (output)
- T2 state
 - Status code output on S3–S6
 - AD0 through AD7 transitioned to data bus and output data placed on bus
 - DEN* set to 0 → enable external data bus control circuitry
 - WR* set to 0 → output cycle
- T3 or T4 state
 - Data on D0–D7 output (write) into I/O port (I/O device decides when!)
- T4 state—output cycle finishes
 - WR* returns to 1 → inactive level
 - Complete address/data bus tri-stated
 - IO/M* returned to 0 → memory bus cycle
 - DEN* returned to 1 → inactive level


8.18 Input/Output Bus Cycle

□ Input bus cycle of the 8086

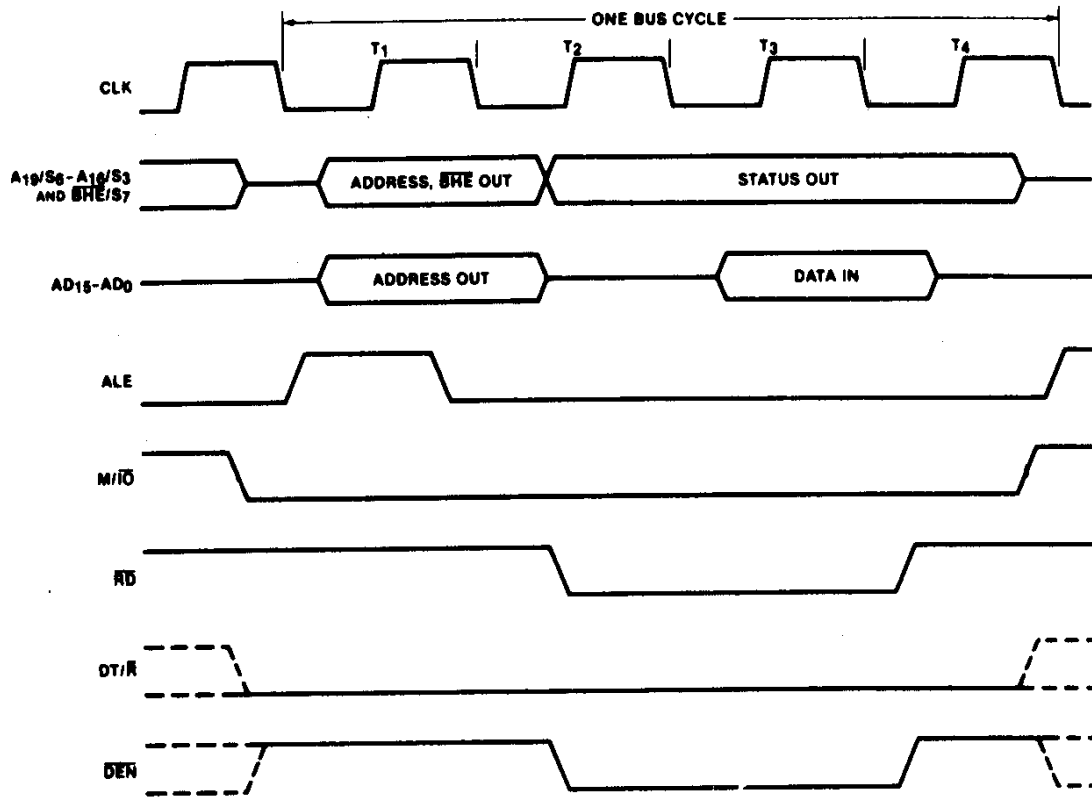

8.18 Input/Output Bus Cycle

- Output bus cycle of the 8086

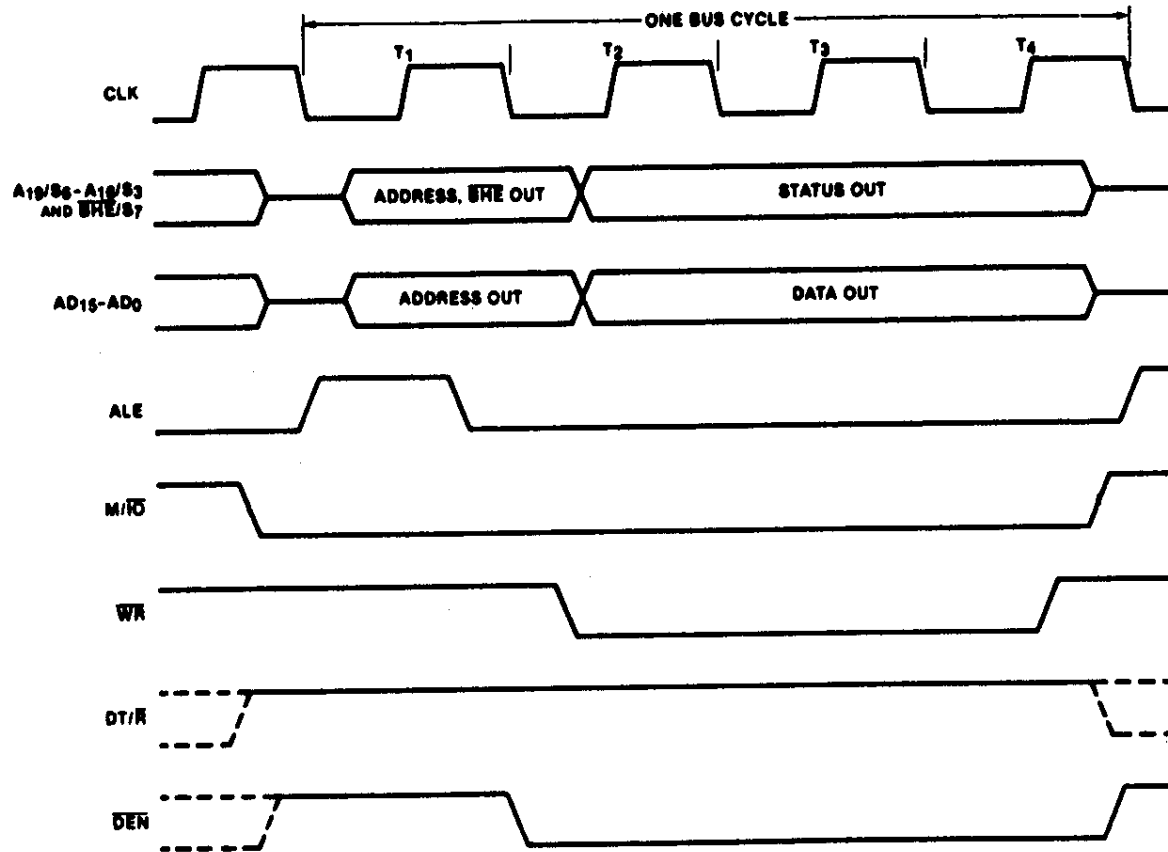

H.W. #8

- Solve the following problems from Chapter 8 from the course textbook:
8, 22, 26, 35, 39, 49, 55, 59, 66, 86, 89, 99,
101, 107