

تلخيص دوائر كهربائية 2

للطالب المبدع
محمود مجدلاني

إرادة - ثقة - تغيير

Chapter 11

* We have 3 different ways to calculate RMS values

$$1) I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) \cdot dt}$$

$$2) I_{rms} = \sqrt{(I_{rms1})^2 + (I_{rms2})^2 + \dots} \leftarrow \text{Different frequency}$$

3) Same frequency $\rightarrow$ add with phaser

* Power calculation

$$* P(t) = V(t) i(t)$$

$$V(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$P(t) = \frac{P_{avg}}{2} + \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)$$

$$\frac{V_m I_m}{2} \cos(\theta - \phi) \quad V_{rms} I_{rms} \cos(\theta - \phi)$$

$$* V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$* I_{rms} = \frac{I_m}{\sqrt{2}}$$

Apparent Power

$$P_{app} = S = \frac{V_m I_m}{2} = V_{rms} I_{rms} \quad (\underline{VA})$$

Power factor

$$P_f = \cos(\theta - \phi) \quad (\text{ليست موجبة})$$

Note

$$\begin{array}{c} \uparrow I \\ \downarrow V \end{array} \quad P_g = VI, \quad P_d = -VI$$

$$\begin{array}{c} \downarrow I \\ \uparrow V \end{array} \quad P_g = -VI, \quad P_d = VI$$

Power avg في حسابات الـ

1) average power

2) active

3) Real power

4) consumed

5) dissipated // generated

Chapter 11

$$\theta_z = \theta - \phi$$

+

* load $\rightarrow$ inductive

* $\underline{I}$ lags $\underline{V}$

$\hookrightarrow$ lagging power factor

-

* capacitive load

* $\underline{I}$ leads $\underline{V}$

$\hookrightarrow$ leading power factor

0

* pure resistive

* $\underline{I}$ in phase $\underline{V}$

$\hookrightarrow \theta = \phi$

$$0 \leq P_f = \cos(\theta - \phi) \leq 1$$

1

for pure (R)

$$\cos(\theta - \phi) = 1$$

$$\theta = \phi$$

$$P_{avg} = \frac{V_m I_m}{2} * \cos(0^\circ)$$

$$\therefore P_{avg} = \frac{V_m I_m}{2} = P_{app}$$

$$P_{avg} = P_{app}$$

$$V_{rms} I_{rms}$$

$$I_{rms}^2 R$$

$$\frac{V_{rms}^2}{R}$$

$$\frac{V_m I_m}{2}$$

$$\frac{I_m^2 R}{2}$$

$$\frac{V_m^2}{2R}$$

$$\frac{1}{2}$$

avg. V_{rms} & I_{rms}

$$\frac{1}{2}$$

avg. phase $\cos$

0

for pure reactance

$$\cos(\theta - \phi) = 0$$

$$\theta - \phi = \pm 90^\circ$$

- capacitive

+ inductive

$$* P_{avg}(C, L) = 0$$


Chapter 11

* AC Power


* Average value for any periodic function:-

$$Y_{avg} = \frac{1}{T} \int_0^T y(t) \cdot dt$$


→ half symmetry function ($Y_{avg} = 0$)

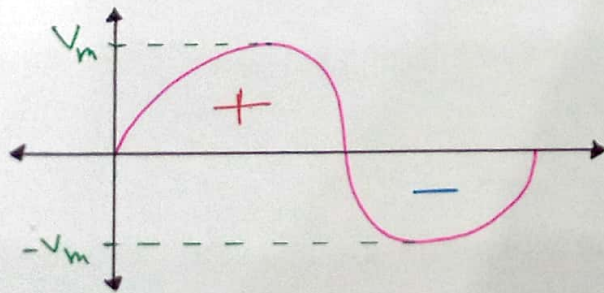


$$Y_{avg} = 0$$

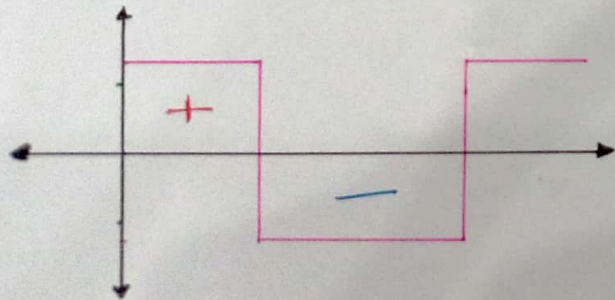

$$Y_{avg} \neq 0$$

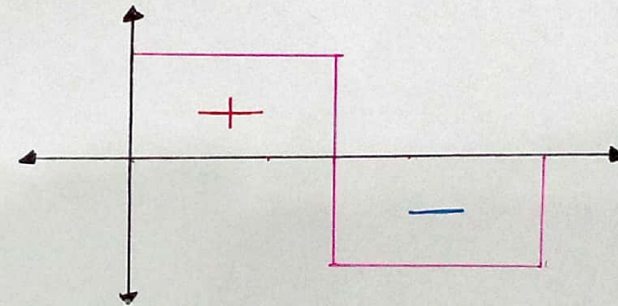

$$Y_{avg} = 0$$

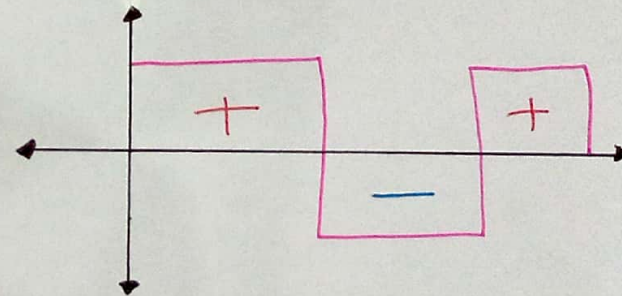

$$Y_{avg} \neq 0$$


$$\sin \cos = 0$$

← (avg) 0 *

* RMS

↳ Root Mean square value


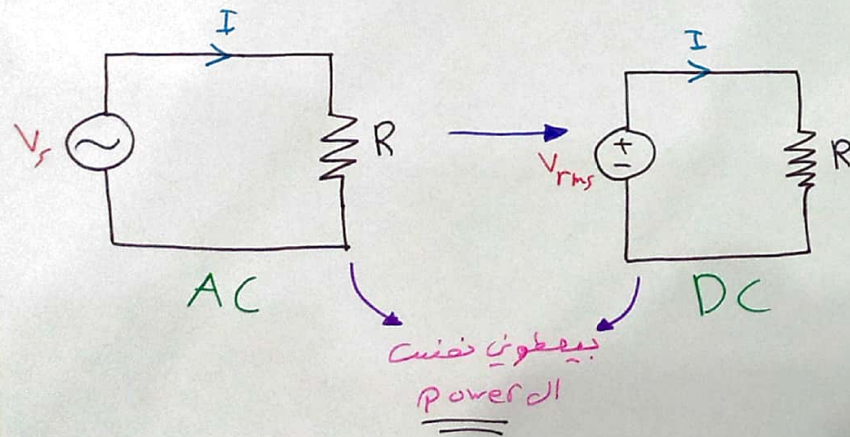
$$Y_{Rms} = Y_{eff} = \sqrt{\frac{1}{T} \int_0^T y^2(t) \cdot dt}$$




$$* V(t) = V_m \cos(\omega t + \theta)$$

$$\rightarrow V_{avg} = 0$$

$$\rightarrow V_{rms} = V_{eff} = \frac{V_m}{\sqrt{2}}$$

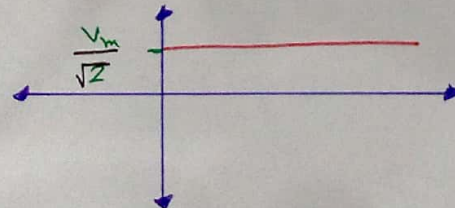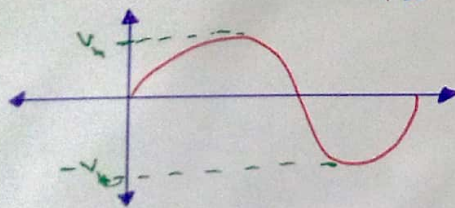


Chapter 15

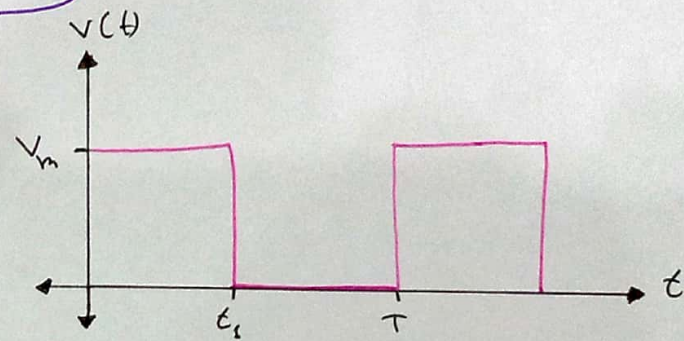

$$* V_{avg} = \frac{V_m \cdot t_1}{T}$$

$$* V_{rms} = V_m \sqrt{\frac{t_1}{T}}$$

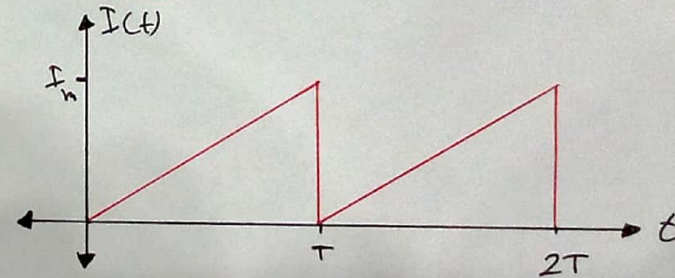

$$* I(t) = \frac{I_m t}{T}$$

$$* I_{rms} = \frac{I_m}{\sqrt{3}}$$

Complex Power (S)

$$S \begin{cases} V_{rms} I_{rms} \cos(\theta - \phi) + (V_{rms} I_{rms} \sin(\theta - \phi)) i \\ P_{avg} + Q i \\ V_{rms} I_{rms}^* \rightarrow \frac{V_m I_m^*}{2} \\ P_{app} \angle \theta - \phi \end{cases}$$

$$\begin{cases} P_{avg} = P_{app} \cos(\theta - \phi) \\ Q = P_{app} \sin(\theta - \phi) \\ P_{app} = \sqrt{(P_{avg})^2 + (Q)^2} \rightarrow |S| = P_{app} \\ \theta - \phi = \tan^{-1}\left(\frac{Q}{P_{avg}}\right) \end{cases}$$

* $S \rightarrow$ Complex power $\rightarrow$ VA

* $Q \rightarrow$ Reactive power $\rightarrow$ VAR

* $P_{avg} \rightarrow$ Average power $\rightarrow$ W

* for pure R)



$$\begin{cases} \theta = \phi \quad \text{In phase} \\ P_f = 1 \\ P_{avg} = V_{rms} I_{rms} \\ Q_R = 0 \\ S_R = P_{avg} = P_{app} \end{cases}$$

* for pure Reactive


$$\begin{cases} \theta - \phi = 90^\circ \\ P_f = 0 \\ P_{avg} = 0 \\ Q_L = V_{rms} I_{rms} \\ Q_C = -V_{rms} I_{rms} \\ S_L = (V_{rms} I_{rms}) i \\ S_C = -(V_{rms} I_{rms}) i \end{cases}$$

$$S = P_{app} \angle \cos^{-1}(P_f)$$


Poly Phase

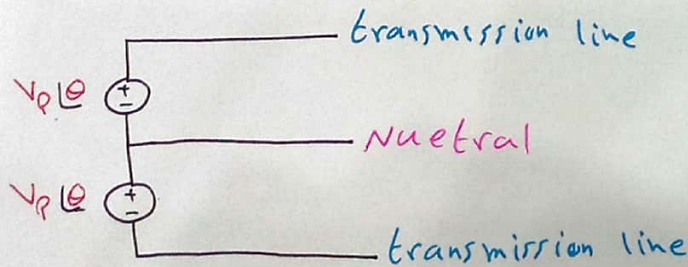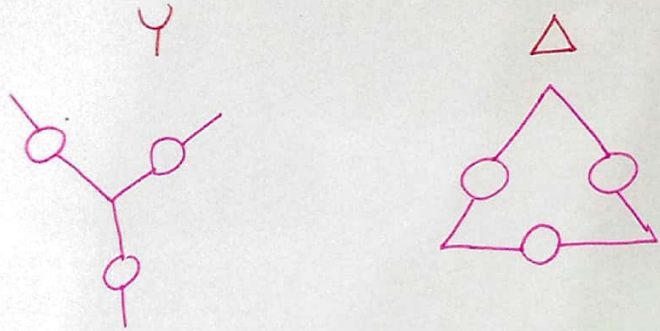

balanced (symmetry) system

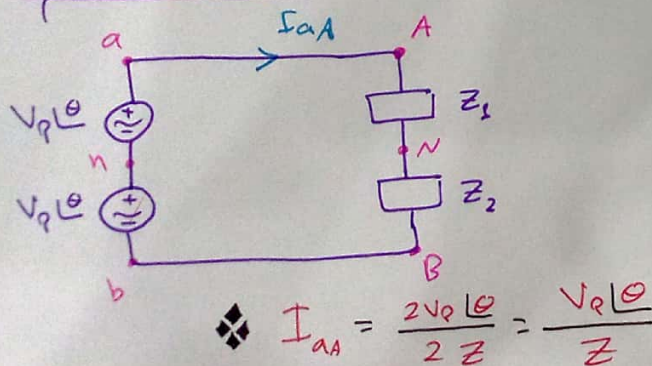

Single Phase in 3 wires

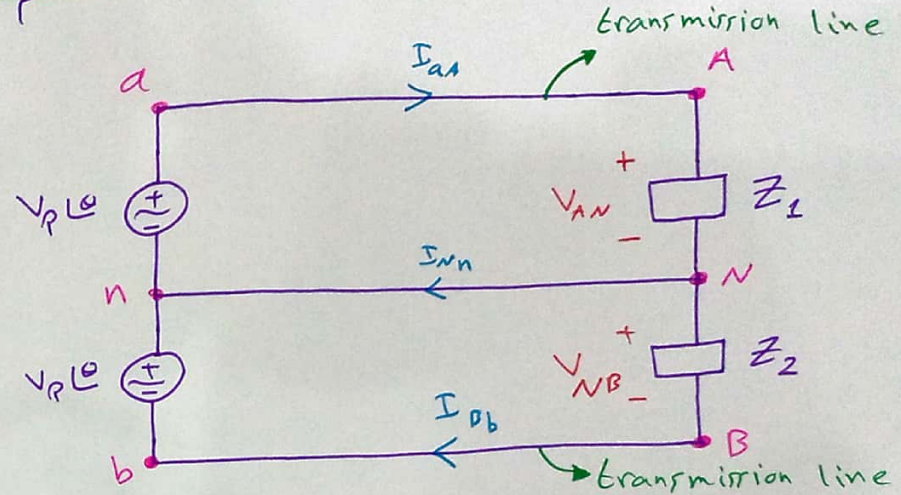

$$V_{AN} = V_{an} = V_{p\angle\theta}$$

$$I_{aA} = \frac{V_{an}}{Z_1} = \frac{V_{nN}}{Z_1} = \frac{V_{p\angle\theta}}{Z_1}$$

$$V_{NB} = V_{nb} = V_{p\angle\theta}$$

$$I_{bB} = \frac{V_{nb}}{Z_2} = \frac{V_{nN}}{Z_2} = \frac{V_{p\angle\theta}}{Z_2}$$

$$I_{nn} = I_{bB} - I_{aA}$$


$$* Z_1 = Z_2$$

$$I_{aA} = I_{bB}$$

$$I_{nn} = 0$$

Load $\rightarrow$ (---, ---, ---)
المصادر الثلاثة

Chapter 12

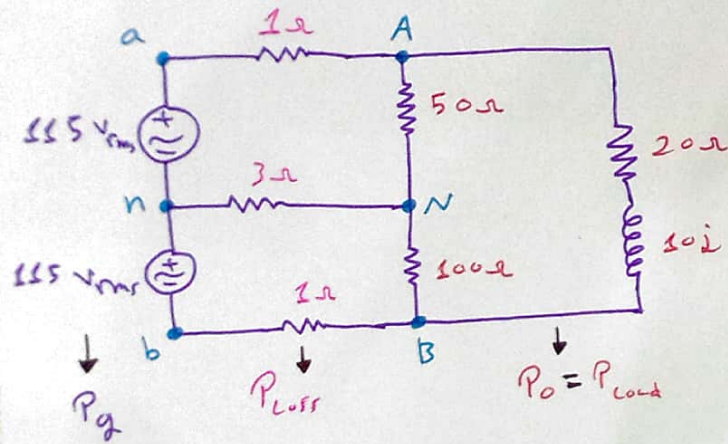

$$P_g = P_{in} = P_{loss} + P_o$$

* note

generating power come from sources (ϕ, ϕ)

loss power come from Resistance (Ω)

efficiency

$$\eta = \frac{P_o}{P_i} \times 100\%$$

* If $P_{loss} = 0 \rightarrow P_o = P_i \rightarrow \underline{\eta = 100\%}$

* Phase voltage

Between Line - neutral

* line voltage

Between two lines

⊕ seq

-120

⊖ seq

+120

هذا هو فقط مجموعهم بال (توت)

$$\left\{ \begin{array}{l} \diamond S_t = S_1 + S_2 + \dots = P_{app_1} \cos \theta - \phi + P_{app_2} \cos \theta - \phi + \dots \\ \diamond Q_t = Q_1 + Q_2 + \dots \\ \diamond P_{avg_t} = P_{avg_1} + P_{avg_2} + \dots \end{array} \right.$$

* note

$$P_g \rightarrow \phi \phi \rightarrow P_{in}$$


$$P_o \rightarrow \text{Load} \rightarrow P_{load}$$

$$P_{loss} \rightarrow R_w$$

Chapter 12

Three Phase

Y - connective

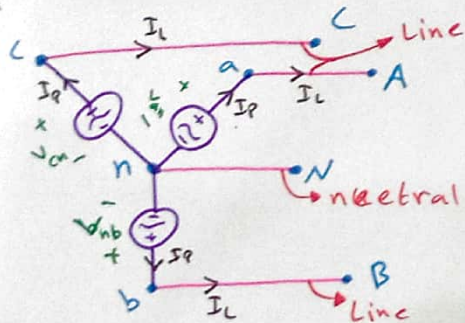

$$I_P = I_L$$

$$V_L = \sqrt{3} V_P \angle 0$$

line lag
Phase by 30°
for $\ominus$ seq

$$* |V_{an}| = |V_{bn}| = |V_{cn}| = V_P$$

$$\checkmark V_{an} + V_{bn} + V_{cn} = 0$$

$$\blacklozenge V_L > V_P$$

Phase voltage

$$V_{an} = V_P \angle 0$$

$$V_{bn} = V_P \angle 120$$

$$V_{cn} = V_P \angle 240$$

$\oplus$ seq

Line voltage


$$V_{ab} = \sqrt{3} V_P \angle -30$$

$$V_{bc} = \sqrt{3} V_P \angle 90$$

$$V_{ac} = \sqrt{3} V_P \angle 240$$

$\oplus$ seq

Δ - connective

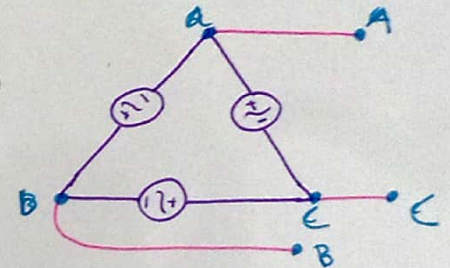

$$I_L = \sqrt{3} I_P \angle 0$$

$$V_P = V_L$$

line lag
phase by
for $\oplus$ seq

$$* |I_{bc}| = |I_{ab}| = |I_{ac}| = I_P$$

$$\checkmark I_{bc} + I_{ab} + I_{ac} = 0$$

$$\blacklozenge I_L > I_P$$

Phase current

$$I_{ab} = I_P \angle 0$$

$$I_{ac} = I_P \angle -120$$

$$I_{bc} = I_P \angle -240$$

$\oplus$ seq




Line current

$$I_{aA} = \sqrt{3} I_P \angle -30$$

$$I_{bB} = \sqrt{3} I_P \angle -150$$


$$I_{cC} = \sqrt{3} I_P \angle -270$$

$\oplus$ seq

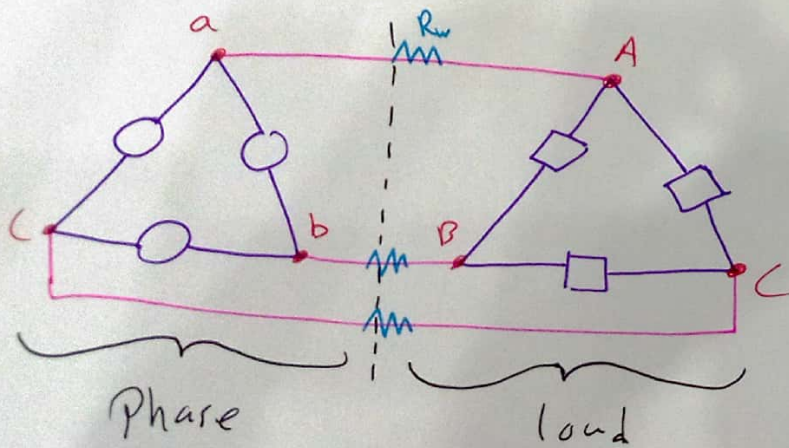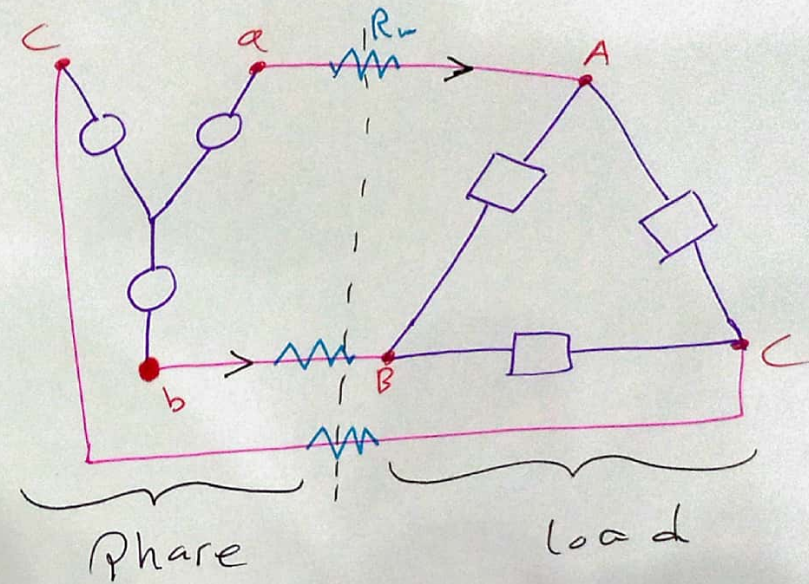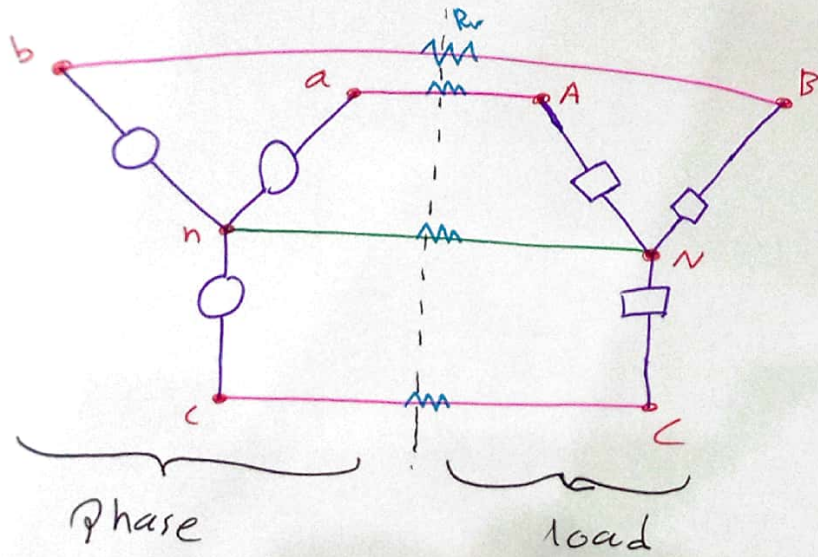


دائماً التيار من (Phase) إلى (load) ✖

Coupling circuit

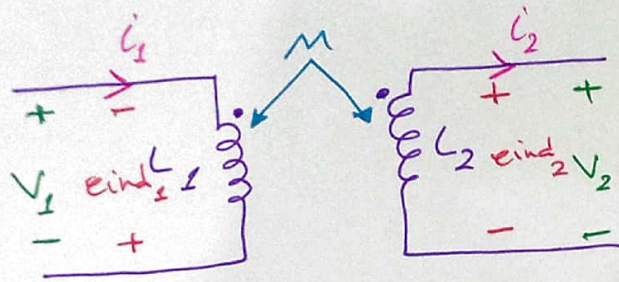


$$V_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = \omega L_1 I_1 + \omega M I_2$$

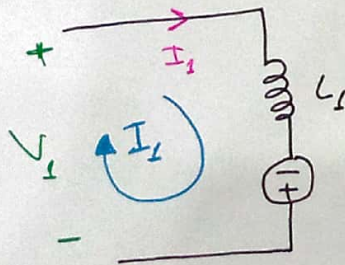

Chapter 13

Linear Transformer

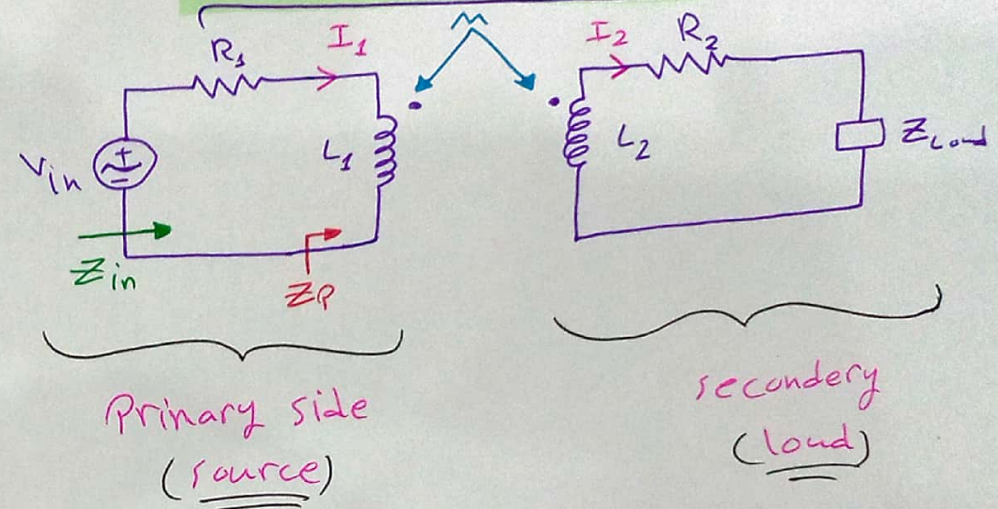

$$* Z_{in} = \frac{V_{in}}{I_1} = Z_p + \frac{\omega^2 M^2}{Z_s}$$

impedance eqn

impedance eqn

stored energy in coupling ckt

$$W_L(t) = \frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) \pm M i_1(t) i_2(t) \geq 0$$

$$M = k \sqrt{L_1 L_2}$$


coupling coefficient

$$0 \leq k = \frac{M}{\sqrt{L_1 L_2}} \leq 1$$




$M=0$
no coupling

lightly coupled

Linear Transformer

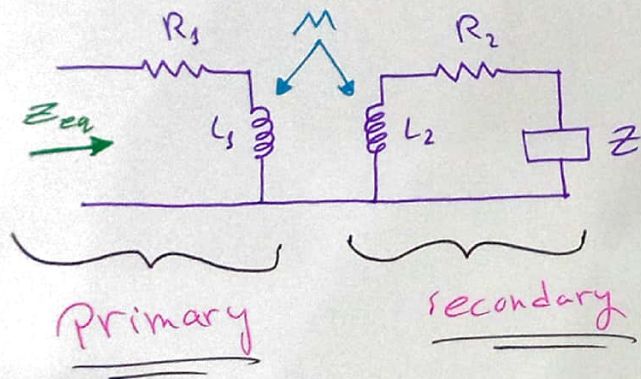
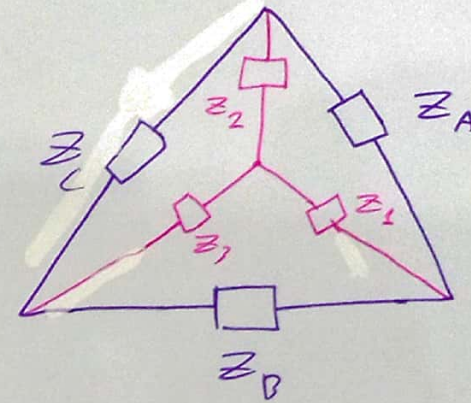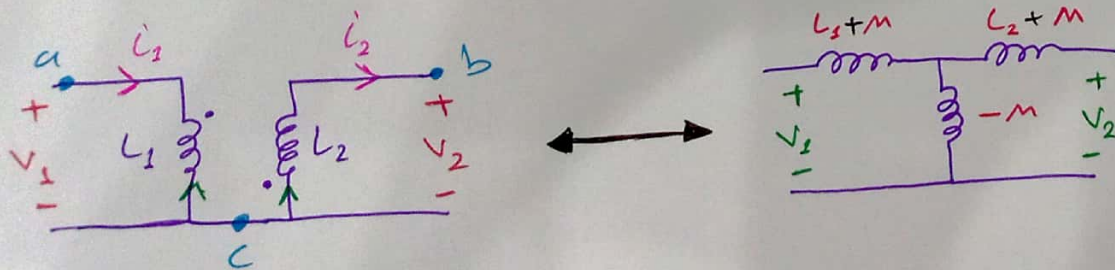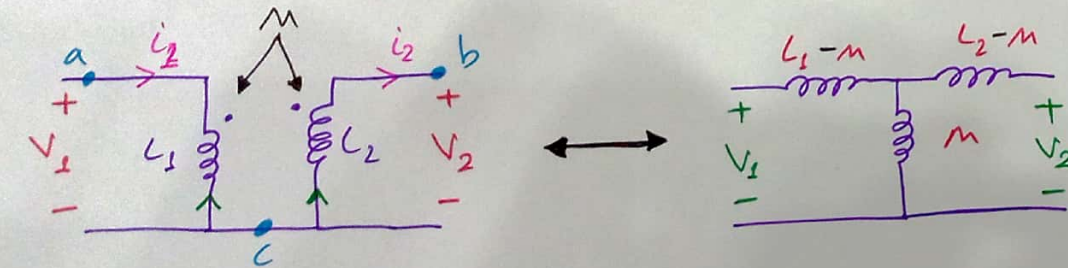
$$\rightarrow Z_{eq} = Z_P + \frac{\omega^2 M^2}{Z_s} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + Z + j\omega L_2}$$



Y-Δ

$$Z_A = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_3}$$

Δ-Y

$$Z_1 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$$

$$\left\{ * Z_{\Delta} = 3 Z_Y \right\}$$

Chapter 16

Transfer function

Ratio between two quantities $H(s)$

Voltage gain
 $H(s) = \frac{V_o(s)}{V_{in}(s)}$

Current gain
 $H(s) = \frac{I_o(s)}{I_{in}(s)}$

$H(s) = \frac{V_o(s)}{I_{in}(s)}$

$H(s) = \frac{I_o(s)}{V_{in}(s)}$

$H(s)$ has Zero

صفر
Zero

at $s = s_0 \Rightarrow$ If $H(s_0) = 0$


$H(s)$ has Pole

قطب
Pole


at $s = s_0 \Rightarrow$ If $H(s_0) = \infty$

Bode Plot


$H(j\omega) = A \angle \phi$

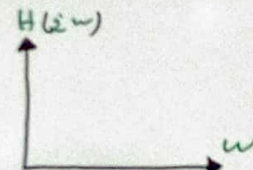


magnitude
Bode plot

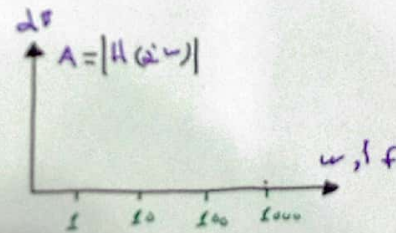

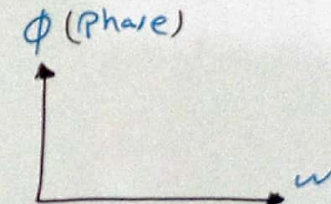a $\rightarrow$ cut of frequency
 $\rightarrow$ critical frequency
 $\rightarrow$ 3dB frequency




Phase
Bode plot

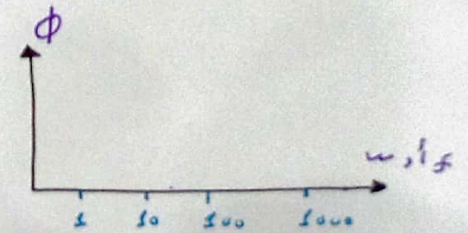


$H_{dB} = 20 \log |H(j\omega)|$


$H(s) = k$

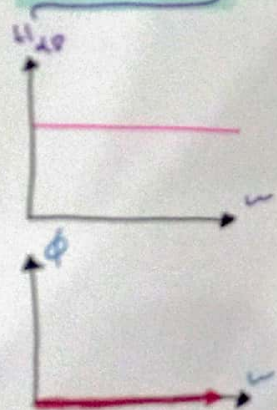


$H(s) = s^N$

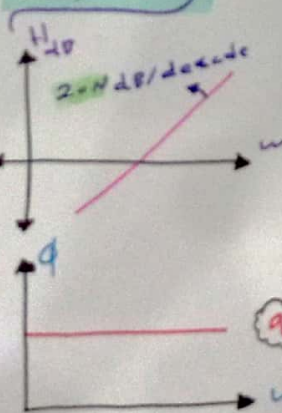


$H(s) = \frac{1}{s^N}$

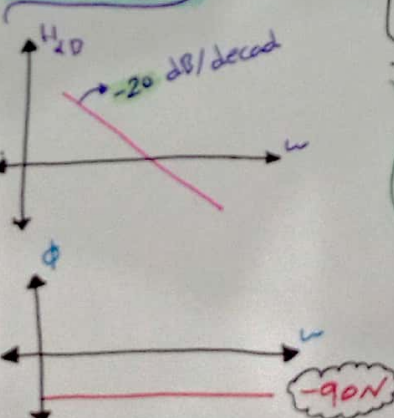

$H(s) = (1 + \frac{s}{a})^N$

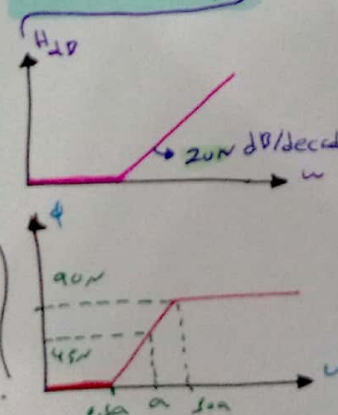



$H(s) = (1 + \frac{s}{a})^{-N}$

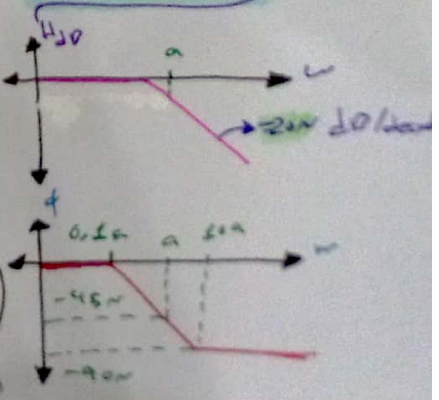



Filters

Types of filters according of frequency band



Low Pass filter (LPF)

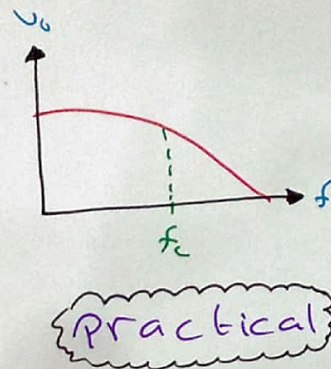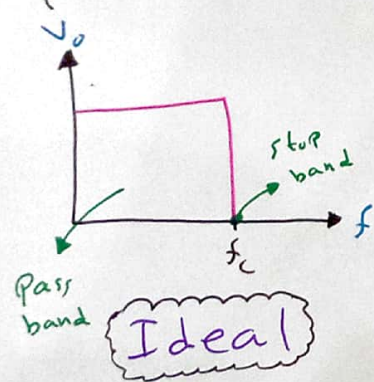



High Pass filter (HPF)

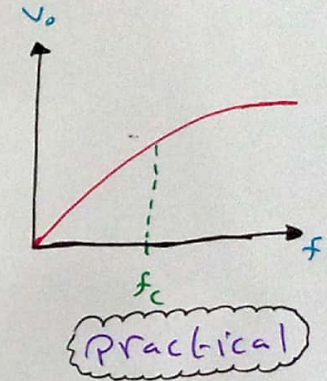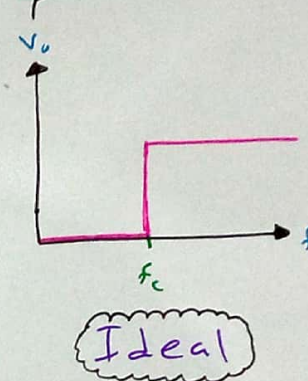

Band Pass filter (BPF)

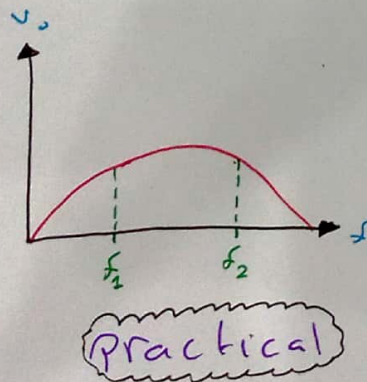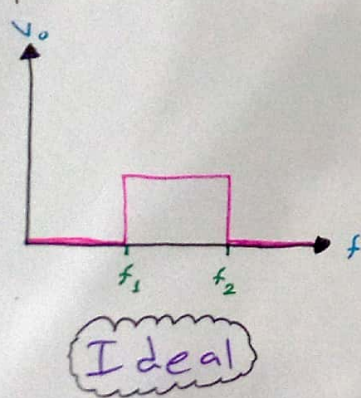

Band stop filter (BSF)

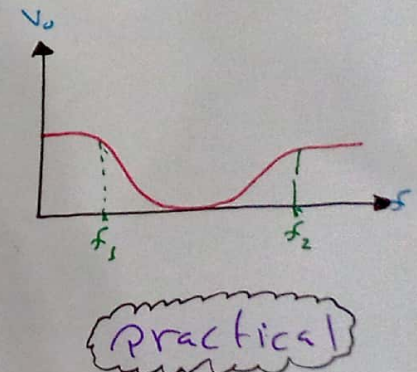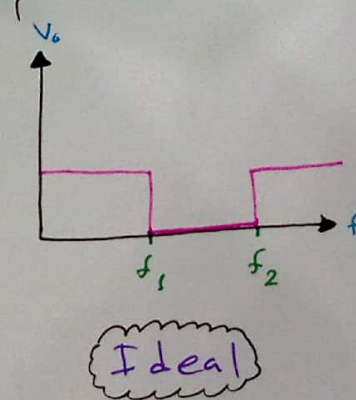


Chapter 10

RC circuit

$$V_o = \frac{Z_c}{Z_c + R} * V_{in}$$
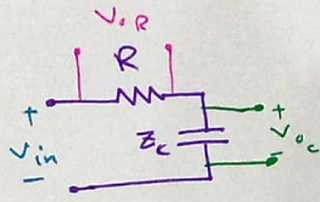
$$\frac{V_o}{V_{in}} = H(\omega) = \frac{1}{1 + j\omega RC}$$



$$\omega = 0 \Rightarrow V_{oc} = V_{in} \quad (Z_c)$$

$$\omega = \infty \Rightarrow V_{oc} = 0$$

$$\omega = 0 \Rightarrow V_{or} = 0 \quad (R)$$


$$\omega = \infty \Rightarrow V_{or} = V_{in}$$

$$\omega_c = \frac{1}{RC}$$


$$f_c = \frac{1}{2\pi RC}$$

$$V_o = \frac{1}{\sqrt{2}} V_{in}$$


for C

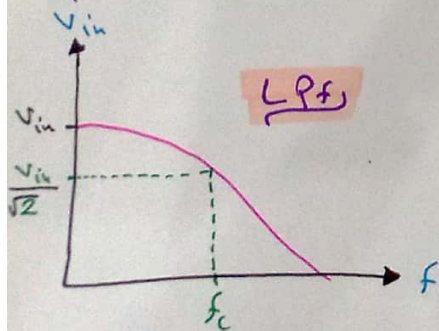

for R

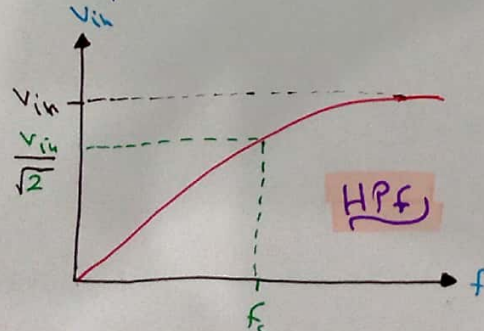

RL circuit

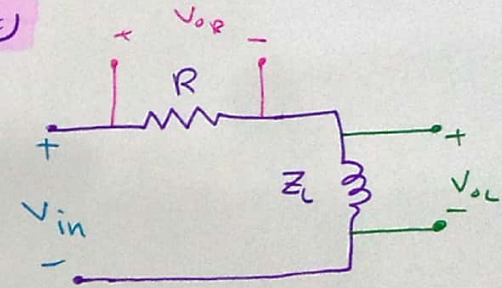

$$\omega = 0 \Rightarrow V_{ol} = 0$$

$$\omega = \infty \Rightarrow V_{ol} = V_{in}$$


$$\omega = 0 \Rightarrow V_{or} = V_{in}$$

$$\omega = \infty \Rightarrow V_{or} = 0$$


$$\omega_c = \frac{R}{L}$$

$$f_c = \frac{R}{2\pi L}$$


$$V_o = \frac{1}{\sqrt{2}} V_{in}$$

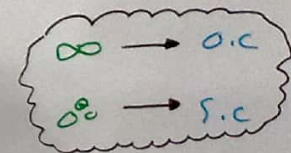

for L

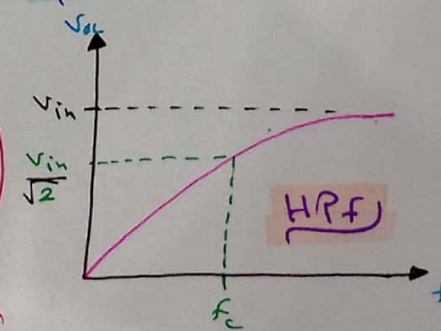



for R

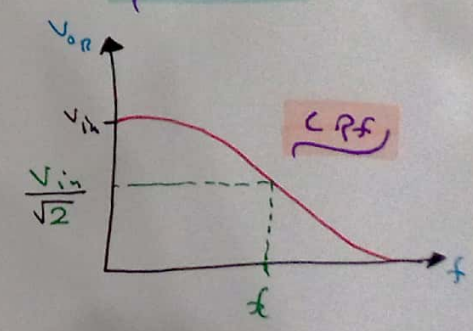

$$Z \begin{cases} \frac{L}{R} \\ RC \end{cases}$$

ثابت زمنية
و بنية ما اخذنا
بالنسبة لـ RC



Band Pass filter

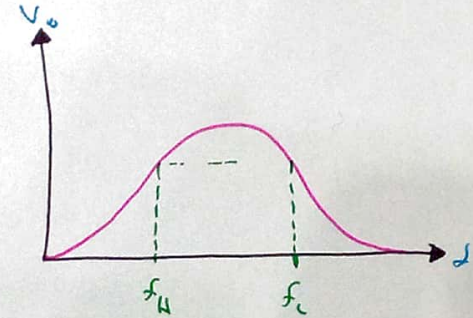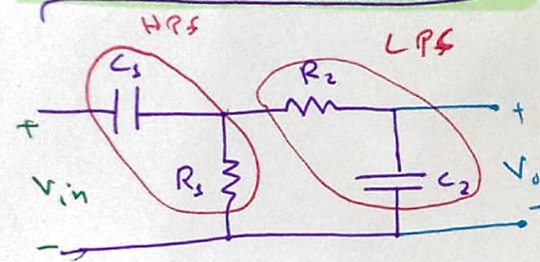

$$f_L = \frac{1}{2\pi R_2 C_2}$$

$$f_H = \frac{1}{2\pi R_1 C_1}$$


Series RLC

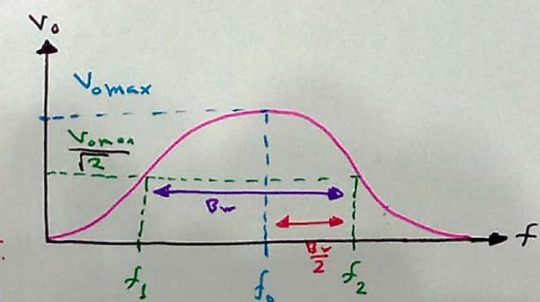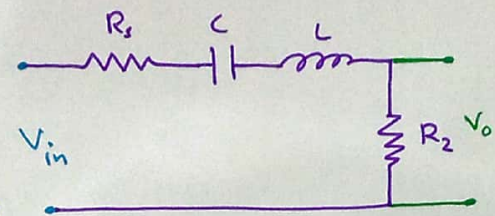

$$\begin{cases} f_1 = f_0 - \frac{B_w}{2} \\ f_2 = f_0 + \frac{B_w}{2} \end{cases}$$

$$B_w = \frac{R}{L} \text{ (rad/s)} \rightarrow B_w = \frac{\omega_0}{Q}$$
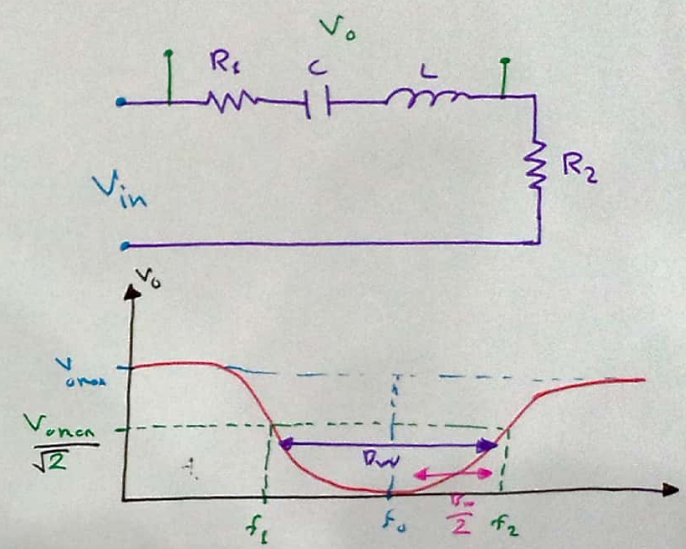
$$B_w = \frac{R}{2\pi L} \text{ (Hz)} \rightarrow B_w = \frac{f_0}{Q}$$



Series and Parallel RLC

Resonant circuit

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$



$$V_o = V_{0\max} = \frac{R_2}{R_1 + R_2} \cdot V_n$$

$$V_o = \frac{1}{\sqrt{2}} V_{0\max}$$

* Quality factor

$$Q = \frac{X_L}{R_{eq}} = \frac{\omega_0 L}{R_{eq}}$$

Parallel RLC

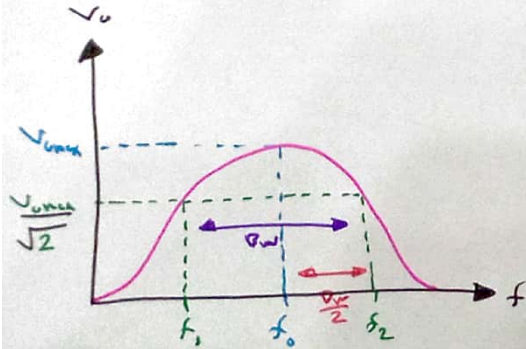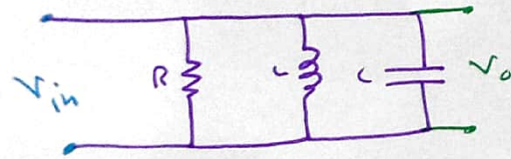

$$\left\{ \begin{array}{l} f_1 = f_0 - \frac{B_w}{2} \\ f_2 = f_0 + \frac{B_w}{2} \end{array} \right\} V_o = \frac{1}{\sqrt{2}} V_{max}$$

$$* f_0 = \frac{1}{2\pi \sqrt{LC}} \quad * \omega_0 = \frac{1}{\sqrt{LC}}$$

بالنسبة لـ
الدارة
فانضوا شانهين

$$\left\{ \begin{array}{l} B_w = \frac{1}{Rc} = \frac{\omega_0}{Q} \text{ (rad/s)} \\ B_w = \frac{1}{2\pi Rc} = \frac{f_0}{Q} \text{ (Hz)} \end{array} \right.$$

* Quality factor

$$Q = \omega_0 R C$$

Chapter 14

Complex frequency

$$s = \sigma + j\omega$$

$s \rightarrow$ complex frequency $\rightarrow s^{-1}$
 $\sigma \rightarrow$ neper frequency $\rightarrow$ neper/s
 $\omega \rightarrow$ Angular frequency $\rightarrow$ rad/s

$$\omega = 2\pi f$$

$$f = \frac{1}{T} \quad (s^{-1} \equiv \text{Hz})$$

$$f(t) = k e^{st} = k e^{\sigma t} e^{j\omega t} = k \angle \phi$$



constant $\rightarrow$ complex frequency

$$1) s = 0$$

$$f(t) = k \quad (\text{constant})(\text{DC source})$$

$$2) s = \sigma$$

$$f(t) = k e^{\sigma t} \quad (\text{exponential})$$

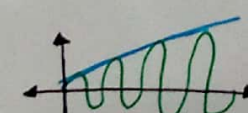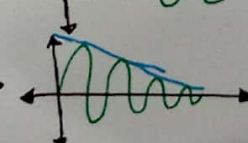$+\sigma \rightarrow$ Inc exp $\rightarrow$ 
 $-\sigma \rightarrow$ Dec exp $\rightarrow$ 

$$3) s = j\omega$$

$$f(t) = k(\cos \omega t + \sin \omega t) \quad (\text{sinusoidal})$$

$$4) s = \sigma + j\omega \quad (\text{Damped sinusoidal})$$

$$f(t) = k e^{\sigma t} (\cos \omega t + \sin \omega t)$$

* Note

$$e^{j\omega t} \rightarrow \phi_{\text{phase}} = \omega t$$

$$e^{\sigma t} \rightarrow \sigma = \text{neper/s}$$

$$e^{j\omega t} \rightarrow \omega = \text{rad/s}$$

$$e^{\sigma t} \rightarrow \text{constant}$$

$$v(t) = e^{\sigma t} \cos(\omega t + \theta)$$

$$s = \sigma \pm j\omega$$

Chapter 34)


Laplace Transform

Time Domain	Frequency Domain
$A u(t)$	$\frac{A}{s}$
$A u(t - t_0)$	$\frac{A e^{-s t_0}}{s}$
$A e^{-at} u(t)$	$\frac{A}{s + a}$
$A t u(t)$	$\frac{A}{s^2}$
$A t e^{-at} u(t)$	$\frac{A}{(s + a)^2}$
$u(t) \sin(\omega t)$	$\frac{\omega}{s^2 + \omega^2}$
$u(t) \cos(\omega t)$	$\frac{s}{s^2 + \omega^2}$
$A \delta(t)$	A
$A \delta(t - t_0)$	$A e^{-s t_0}$

$$\rightarrow \mathcal{L} \frac{df}{dt} = s f(s) - f(0)$$


$$\rightarrow \mathcal{L} \frac{d^2 f}{dt^2} = s^2 f(s) - s f(0) - f'(0)$$

$u(t)$ unit step function

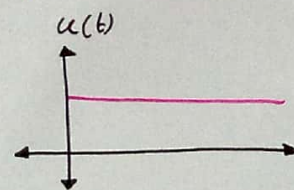


$$u(t) = \begin{cases} 1 & , t \geq 0 \\ 0 & , t < 0 \end{cases}$$
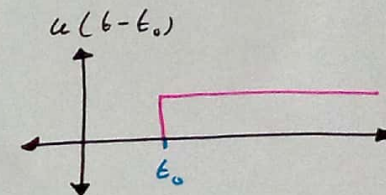
$$u(t) = \begin{cases} 1 & , t \geq t_0 \\ 0 & , t < t_0 \end{cases}$$



* Note

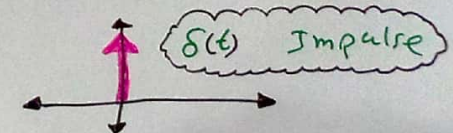$N \geq D \rightarrow$ long division
 $N < D \rightarrow$ partial fraction
 $\frac{N}{D}$



Initial Value

$$\blacklozenge f(0) = \lim_{t \rightarrow 0} f(t)$$

$$\blacklozenge F(0) = \lim_{s \rightarrow \infty} s F(s)$$

Final Value

$$\blacklozenge f(\infty) = \lim_{t \rightarrow \infty} f(t)$$

$$\blacklozenge F(\infty) = \lim_{s \rightarrow 0} s F(s)$$