

تقدم لجنة EiCoM الاكاديمية

دفتر لمادة:

الالكترونيات الاتصالات

من شرح:

د.هادي العيثاوي

جزيل الشكر للطالب:

عدنان حوراني



Oscillators :- (Signal Generators)

[Sinusoidal Oscillators]

1) Circuits generate A.C periodic output

Signal without any input Signal, Only

DC voltage is required to bias the amplifier.


2) Oscillator Circuit Contains amplifier

to give the required gain and phase


Shift Circuit (RC, LC, LR) to give the

required phase Shift.

BJT, FET, OP-Amp.

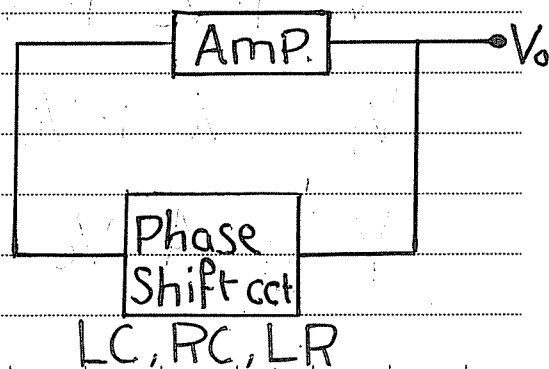

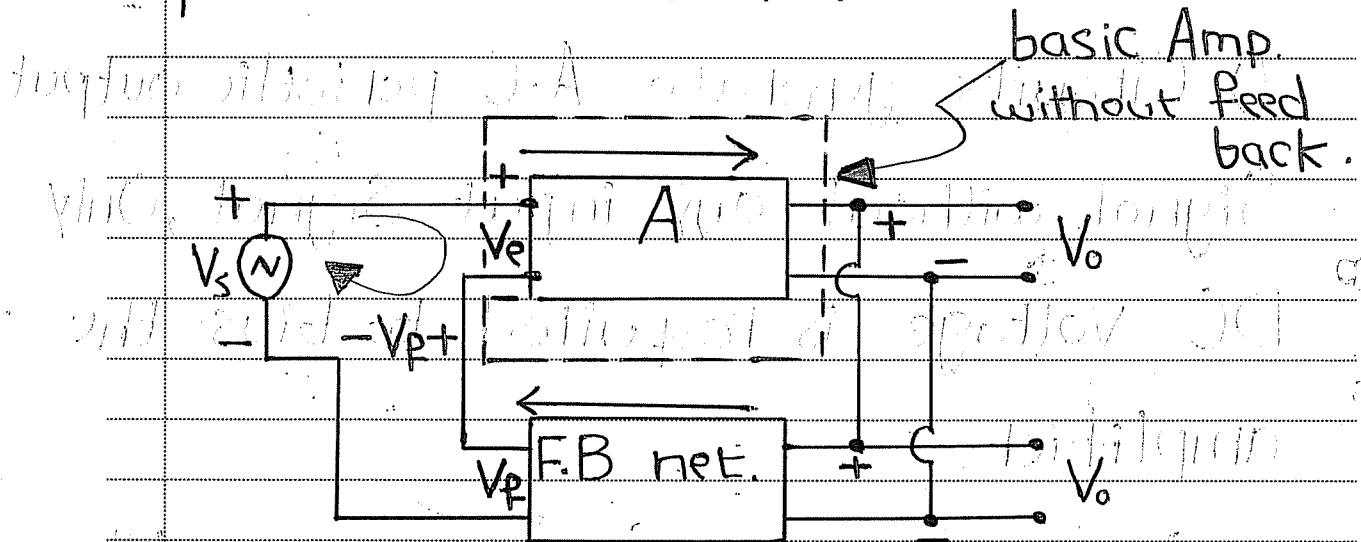3) It is a feedback amplifier use
Positive feedback.



$$B = \frac{V_f}{V_o}$$

$$V_e = V_s \mp V_f \begin{cases} V_e = V_s - V_f \text{ (-ve feedback)} \\ V_e = V_s + V_f \text{ (+ve feedback)} \end{cases}$$

→ assume -ve feedback:

$$-V_s + V_e + V_f = 0$$

$$V_s = V_e + V_f$$

$$V_o = A \cdot V_e$$

$$V_e = V_s - V_f$$

$$V_f = B V_o$$

$$V_o = A (V_s - B V_o)$$

$$V_o (1 + BA) = A V_s$$


$$\frac{V_o}{V_s} = \frac{A}{1 + BA}$$

↳ gain of Feedback Amp.

$$\text{If } BA = -1, \frac{V_o}{V_s} = \infty ;$$

either $V_o = \infty$ (is not correct, because V_o has a certain value)

or $V_s = 0$ (No input signal).

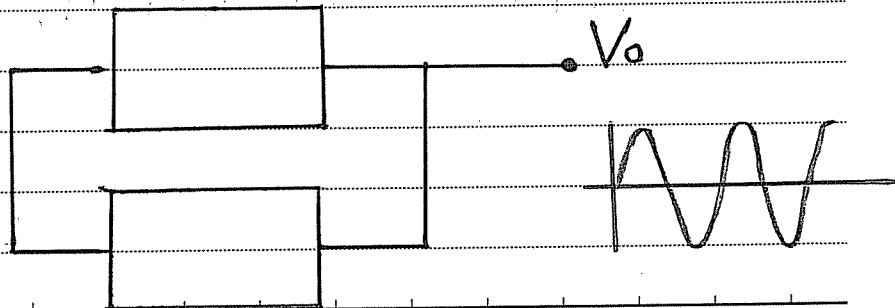

* $V_s = 0$, it's mean that the CCT. will give a Certain O/p without AC input signal.

* gain is function of f_{req} .

* The value of A and B depends on f_{req} .

* The Conditions will be Satisfy at the Certain value of ω .


Oscillators

↓
Non Sinusoidal
(relaxation oscillator)

based on Charging
and discharging of Cap.

↓
Sinusoidal

based on
Oscillation
Condition.

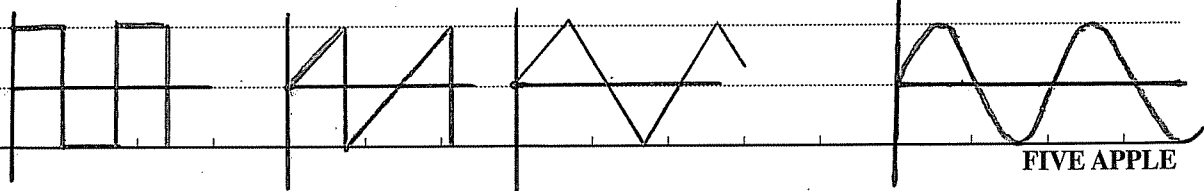

Sinusoidal Oscillator

RC-Oscillator LC-Oscillator

(Amp. + RC-Ckt.) (Amp. + LC-Ckt.)



Wien-bridge Oscillator Phase-Shift Oscillator

$\angle A = 0^\circ$ $\angle A = 180^\circ$

$\angle B = 0^\circ$ $\angle B = 180^\circ$

Hartley Oscillator Colpitts Oscillator Crystal Oscillator

Wien-Bridge Oscillator :-

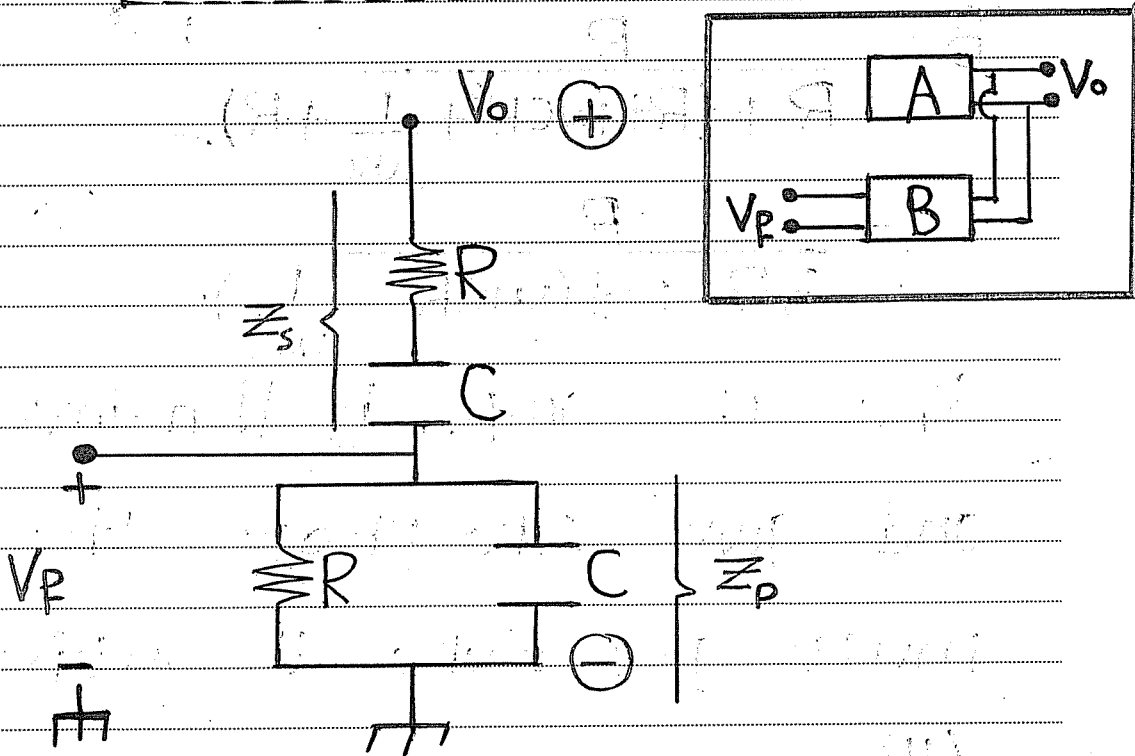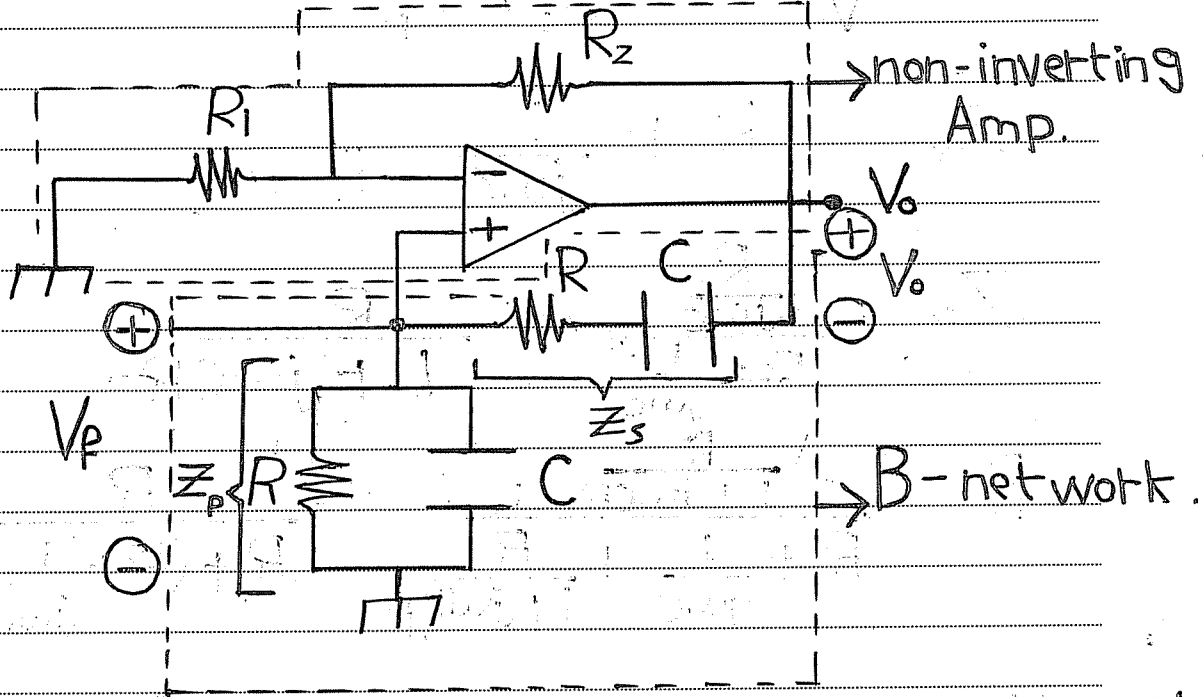

$$B = \frac{V_e}{V_o} = \frac{Z_p}{Z_s + Z_p}$$

Build up work

$$Z_s = R + \frac{1}{j\omega C}$$

$$Z_p = \frac{R}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega CR}$$

$$|B| = \frac{\frac{R}{1 + j\omega CR}}{R + \frac{1}{j\omega C} + \frac{R}{1 + j\omega CR}} = \frac{R}{R + (R + \frac{1}{j\omega C})(1 + j\omega CR)}$$

$$|B| = \frac{R}{R + (R + \frac{1}{j\omega C})(1 + j\omega CR)}$$

$$= \frac{R}{3R + j(\omega CR^2 - \frac{1}{\omega C})}$$

Since the amp. is Non-inverting and give zero phase, the B.net must give zero to satisfy

$$\angle B = 0^\circ$$

$|B| = 0^\circ$ when j -terms = 0 ,

$$\omega CR^2 - \frac{1}{\omega C} = 0$$

$$\omega^2 C^2 R^2 = 1$$

when $\omega_0 = \frac{1}{RC}$

$\therefore f_0 = \frac{1}{2\pi RC}$ (Freq. of Oscillation)

At this freq. :

$$|B| = \frac{1}{3}$$

To satisfy $|BA| = 1$, $A_{\min} = 3$.


$$A = 1 + \frac{R_2}{R_1} = 3 \rightarrow \text{For non-inverting amp.}$$

$$\therefore \left(\frac{R_2}{R_1}\right)_{\min} = 2$$

$$\boxed{R_2 = 2R_1}$$



يمكن استخدام OP-AMP في:
 Common base
 Common gate
 two Stages Common Source or
 Common Emmitter.

(نموذجي في الامتحان)

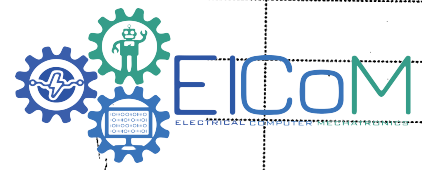




Phase Shift Oscillator

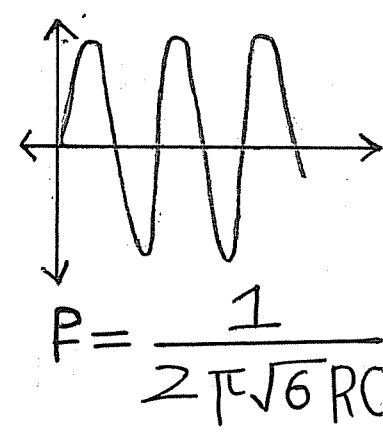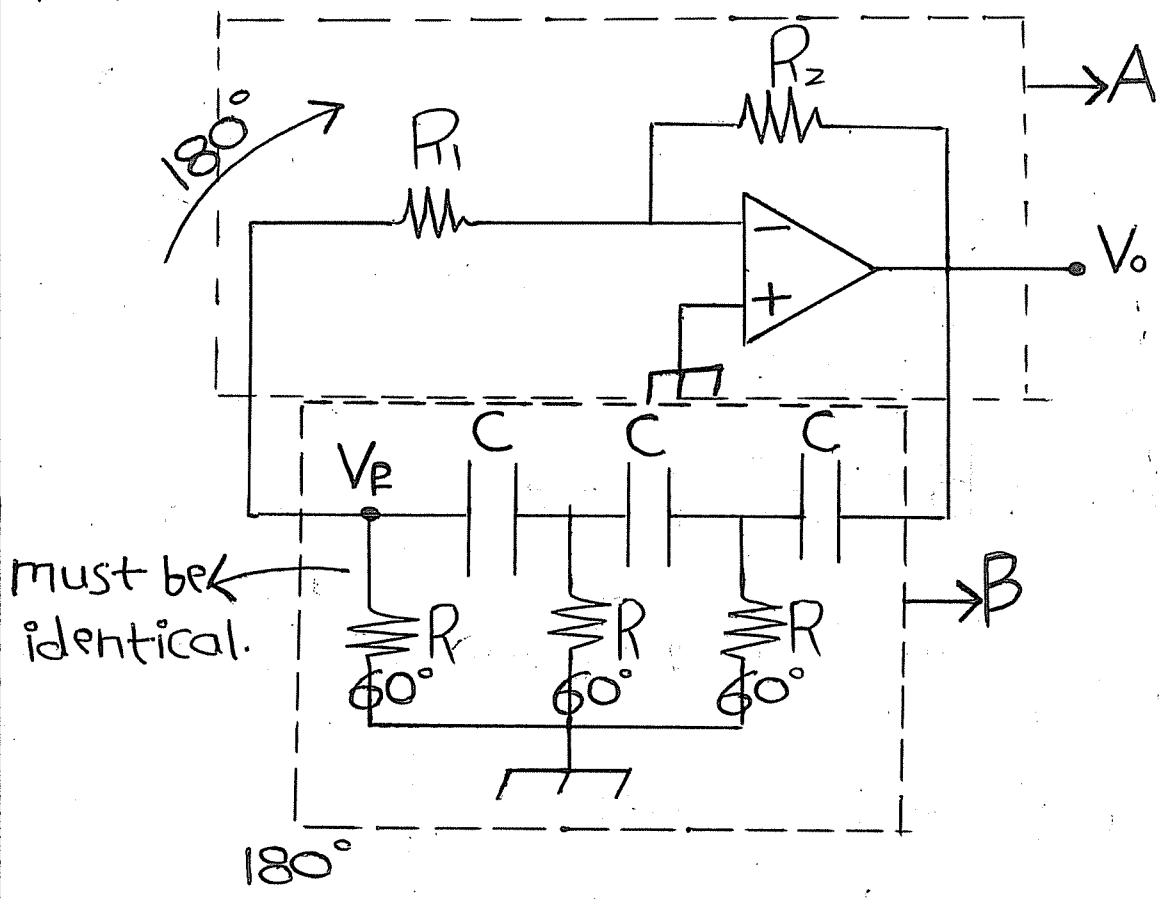

each RC section gives 60° , So the B-Net gives 180° .

Inverting Amp. $\rightarrow 180^\circ$.

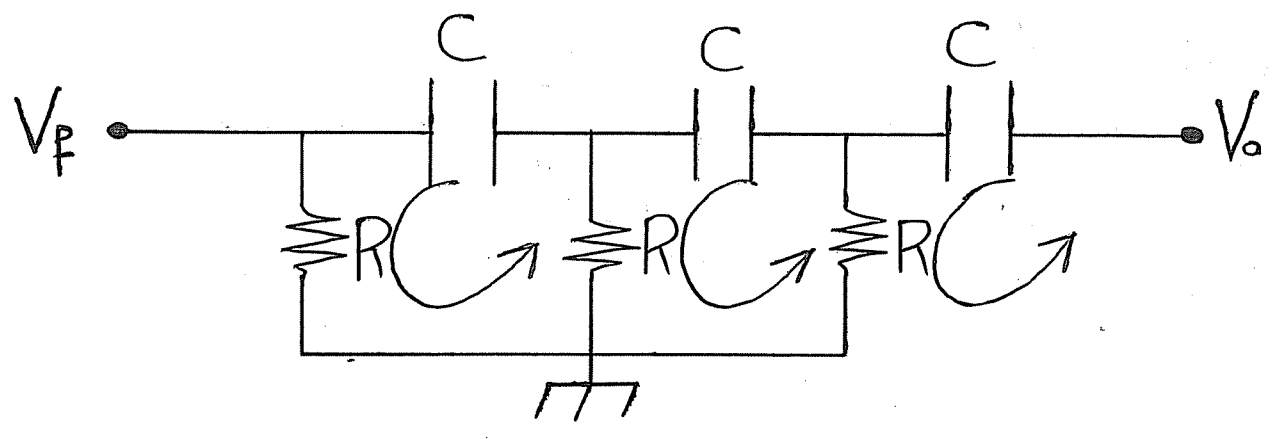So $\angle A.B = \angle A + \angle B = 360^\circ$.



$$B = \frac{V_f}{V_o} = \dots$$

$$\omega_o = \frac{1}{\sqrt{6} RC}$$

$$f_o = \frac{1}{2\pi\sqrt{6} RC} \quad \text{freq. of Oscillation.}$$

at this freq. : $B = \frac{-1}{29} \rightarrow |B| = \frac{1}{29}$

To satisfy $|BA| = 1$, $A_{min} = 29$


For inverting Amp. : $|A| = \frac{R_2}{R_1}$

So, we must Choose $\frac{R_2}{R_1} = 29$.

$$R_2 = 29 R_1$$

note :

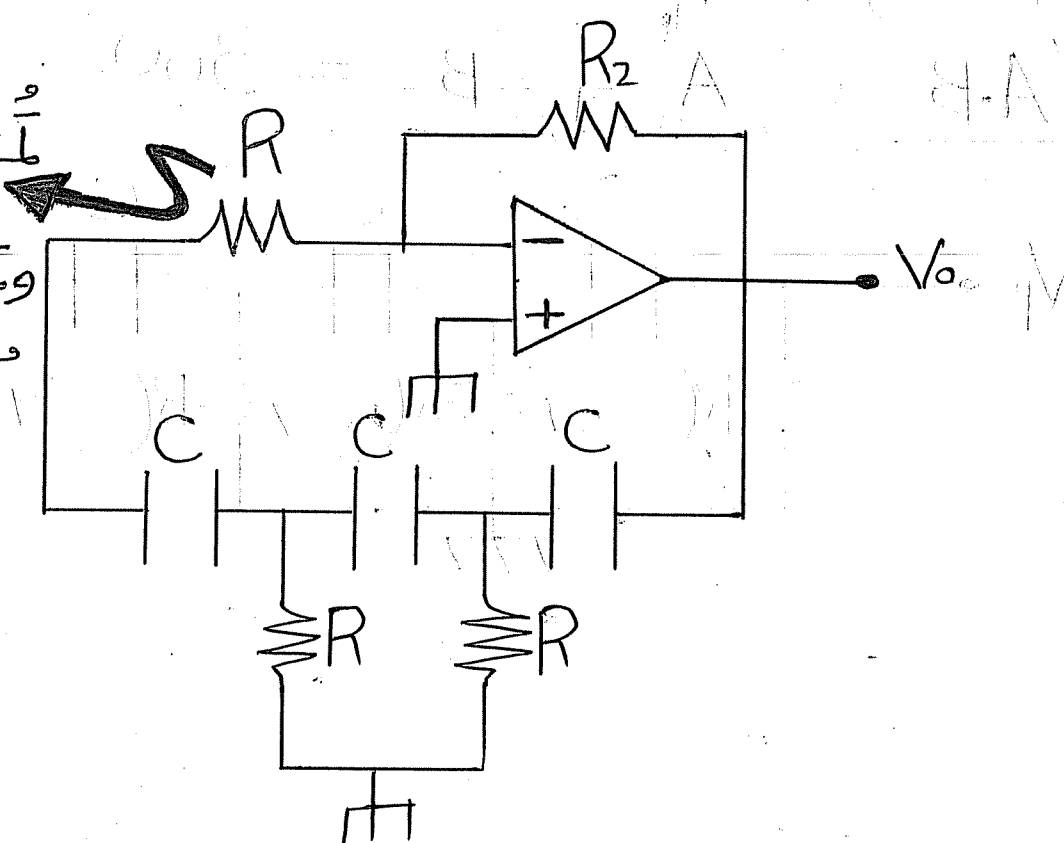Gain Control (R)
Res. (R_1)
وقتيل (R) الاخير
من RC



Exp.: Design a phase-Shift Oscillator to Oscillate at 10 kHz.


$f_o = \frac{1}{2\pi\sqrt{6}RC}$, Choose $C = 0.01 \mu F$.

$R = \frac{1}{2\pi\sqrt{6}f_o C}$
 $= \frac{1}{2\pi\sqrt{6} \times 10^4 \times 0.01 \times 10^{-6}} = \frac{10^4}{15} \approx 650 \Omega$


For this Oscillator:

$A = \frac{R_2}{R_1} = 29$

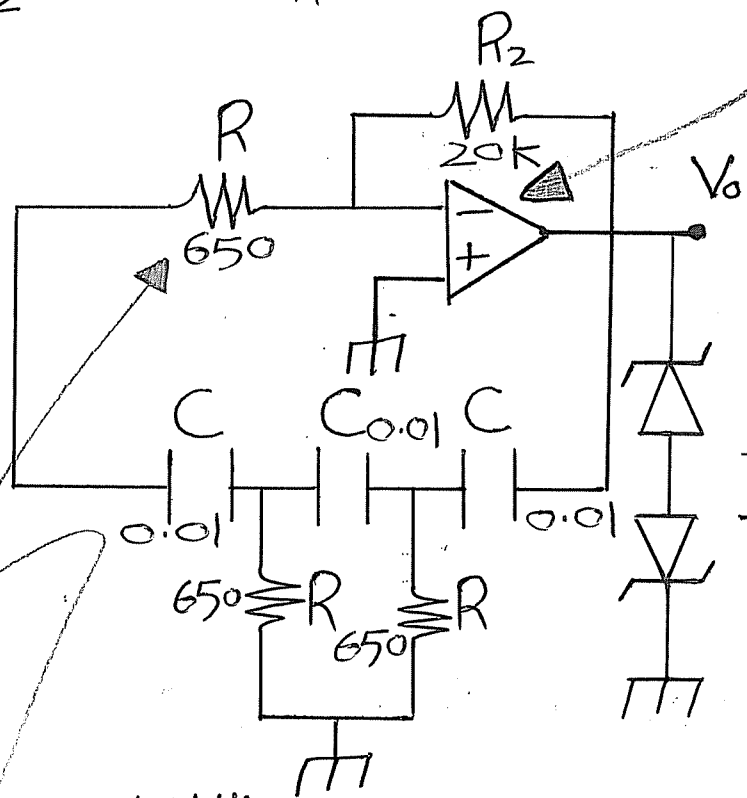$R_2 = 29R_1 = 29 \times 650 = 20k \Omega$



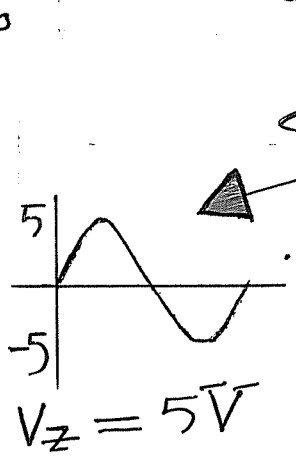Common of Common Emitter or Common Source



Zener diode
 إذا أردنا أن نُحدد 5V
 ربطه مع

إذا استخدمنا CE
 $R_{th} = R_1 // R_2$


LC Oscillator

B \rightarrow LC CCT.

A \rightarrow OP-Amp., BJT, FET.

- 1] Hartley oscillator.
- 2] Colpitts oscillator.
- 3] Crystal oscillator.

Hartley Oscillator :- [2L+1C]

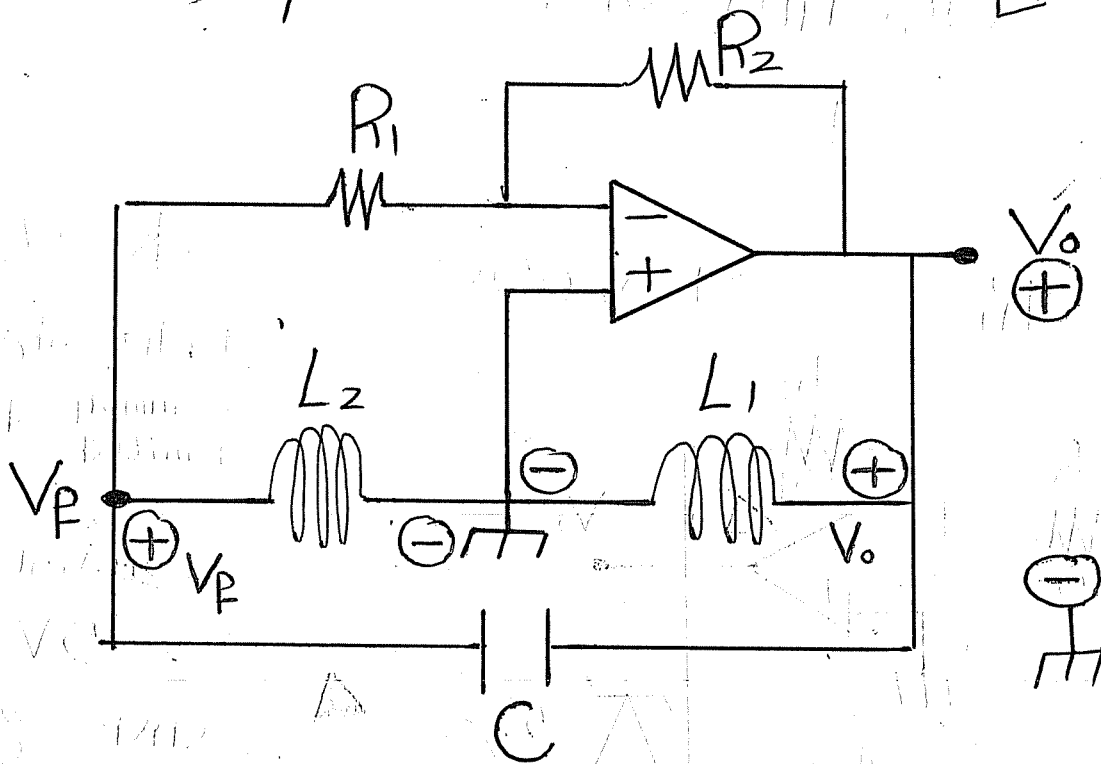

$$\angle A = 180^\circ$$

$$\angle B = 180^\circ \text{ at Resonance.}$$

→ For LC cct. at Resonance :

$$X_L = X_C$$

$$j\omega(L_1 + L_2) = \frac{-1}{j\omega C}$$

$$\omega^2 C(L_1 + L_2) = 1$$

$$\omega_0 = \frac{1}{\sqrt{C(L_1 + L_2)}}$$

$$[j\text{-term} = 0]$$

$$j\omega L + \frac{1}{j\omega C} = 0$$

$$f_0 = \frac{1}{2\pi\sqrt{(L_1 + L_2)C}} \quad ; \text{ Freq. of Oscillation.}$$

$$B = \frac{V_P}{V_0} = \frac{X_{L_2}}{X_{L_1}} = \frac{L_2}{L_1}$$

$$|B| = \frac{L_2}{L_1}$$

$$|A| = \frac{R_2}{R_1}$$

To satisfy $|BA| = 1 \quad \therefore$

$$\boxed{\frac{R_2}{R_1} = \frac{L_1}{L_2}}$$

تُعطى C بالسؤال/ ويظهر ال gain $\frac{R_2}{R_1} \leftarrow$ نستخدم العلاقة $\frac{R_2}{R_1} = \frac{L_2}{L_1}$ لإيجاد


قيمة L_1 و L_2 (نفرض L_1 ونحسب L_2)

أو نجد معادلتين: $L_2 = ?$ $L_1 = ?$

$L_1 + L_2 = \dots$

ثم نحسب قيمة L_1 و L_2

Colpits Oscillator : [2C + 1L]

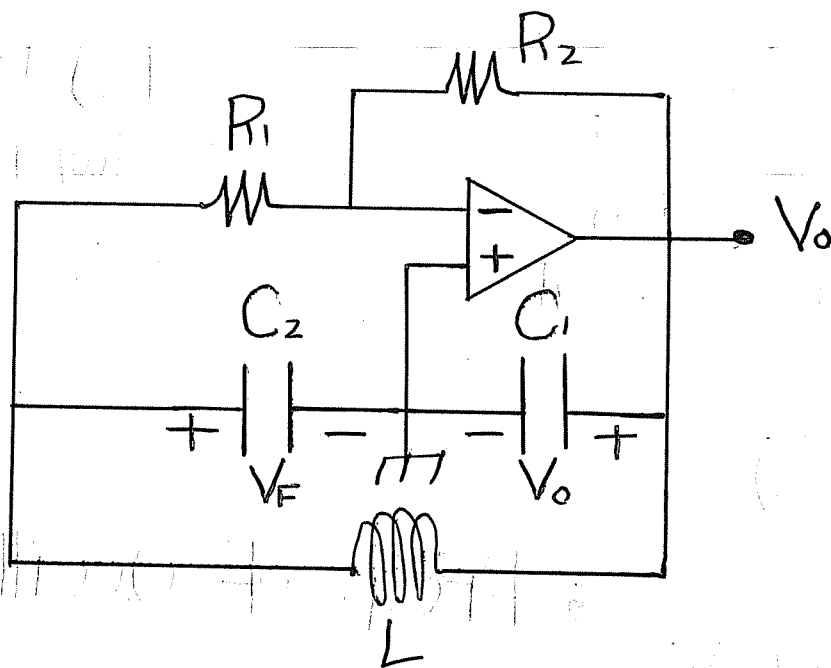

$$\rightarrow \underline{A} \rightarrow 180^\circ$$

$$\rightarrow \underline{B} \rightarrow 180^\circ \text{ at Resonance.}$$

$$X_L + X_C = 0$$

$$j\omega L + \frac{1}{j\omega(C_1 + C_2)} = 0$$

$$j\omega L = \frac{-1}{j\omega(C_1 + C_2)}$$

$$-\omega^2 L = \frac{-1}{(C_1 + C_2)} \rightarrow \omega_0 = \frac{1}{\sqrt{L(C_1 + C_2)}}$$

$$f_0 = \frac{1}{2\pi\sqrt{L(C_1 + C_2)}}, \text{ Freq. of Oscillation.}$$

$$|B| = \frac{V_F}{V_o} = \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1}} = \frac{C_1}{C_2}$$

$$|A| = \frac{R_2}{R_1}$$

To satisfy $|BA| = 1$:

$$\boxed{\frac{R_2}{R_1} = \frac{C_2}{C_1}}$$

hint : gain = $\frac{R_2}{R_1} = 10$ / $C_1 + C_2 =$ نجد معادلة L / $f_o = 10$ نفضل قيمة

نجد معادلة (1) من العلاقة $\frac{R_2}{R_1} = \frac{C_2}{C_1}$ ثم نجد C_1 و C_2

V
V

M

M

M

M

M

M

M


M

→ Freq. Stability = The ability of Oscillator to produce a constant Freq. o/p as long as possible.

For RC and LC, the components R, C, L are varied due to voltage variation, Temp, and aging; So the Freq. stability of RC and LC oscillator are NOT very good.


To Obtain high and stable output Freq we use Crystal Oscillator.

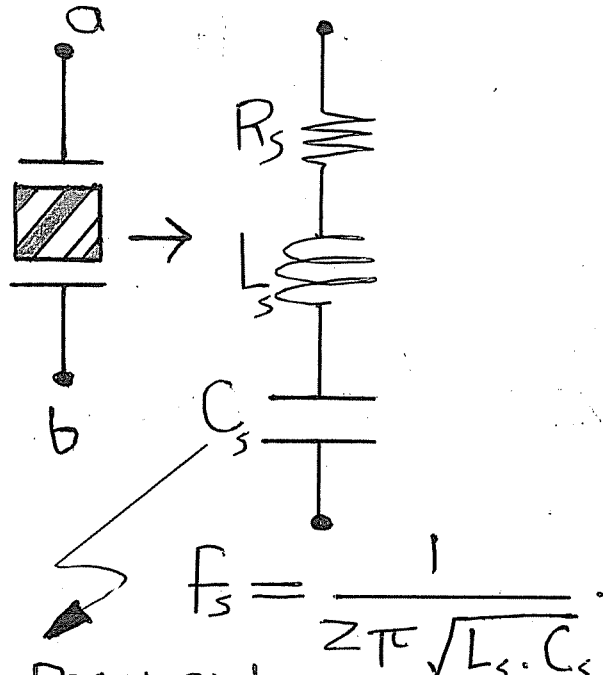→ Crystal Oscillator: It is an Oscillator using quartz crystal as phase shift CCT.




$$f_s = \frac{1}{2\pi \sqrt{L_s \cdot C_s}}$$



Series Resonant CCT.

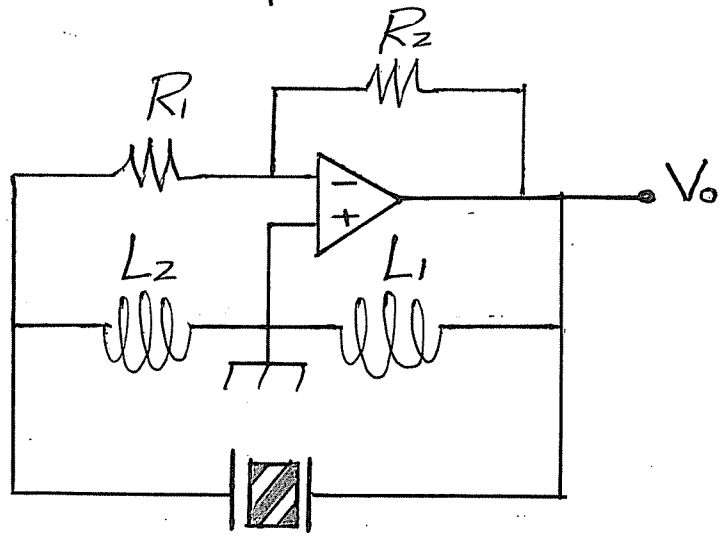

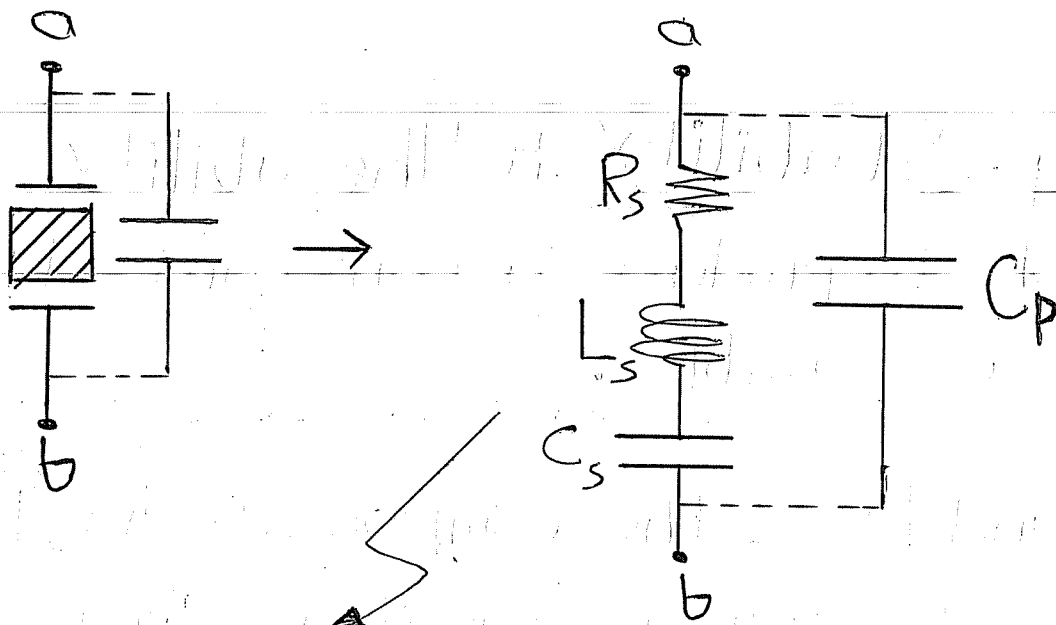local osci. و تحتاج Carrier
 له تردد ثابت




Parallel Resonant
cct.

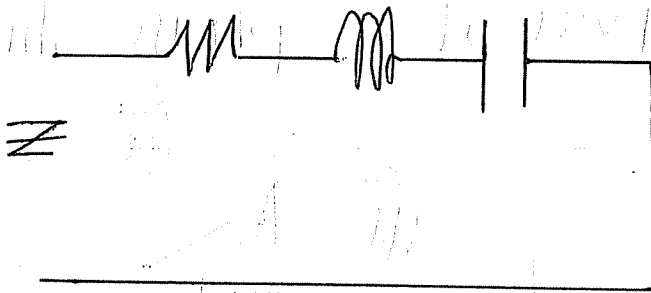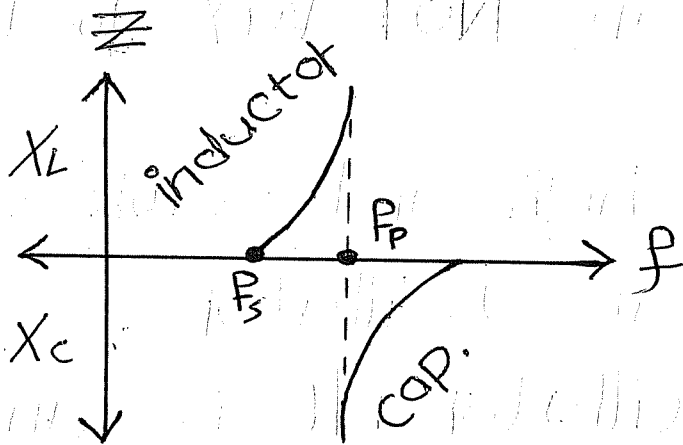

at Resonant:

$$Z = R$$

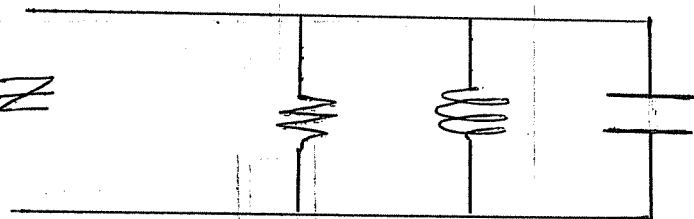

at Resonant:

$$Z = \infty$$

Quartz Crystal is one of pizo electric material which behave as electro-mechanical system when it is subjected to electric field.

Electrically, it is represented by Series RLC cct. and when holder capacitor (C_p) is considered it works as parallel RLC cct.

- If we consider the impedance of the crystal it can work in series mode as a series Resonant cct. with Resonant Freq.:

$$f_s = \frac{1}{2\pi\sqrt{L_s C_s}}, \text{ where } L_s \text{ and } C_s \text{ are parameters of Crystal quartz.}$$

Since C_s , L_s , R_s are not affected by Temp., Voltage variation, aging, So the freq. of Crystal oscillator are very stable. (X-tal oscillator has a very high freq. stability).

Also, the values of L_s, R_s, C_s are very small
 so Freq. of Oscillation is high (MHz) range
 but the value of L_s, R_s, C_s are fixed
 according to X-tal dimensions, so each
 X-tal produce a certain Freq. . .

disadvantage.


- If the crystal works in parallel mode, it
 behaves as parallel tuned cct. with

resonant Freq. : $f_p = \frac{1}{2\pi\sqrt{L_s C_{eq}}}$

$C_{eq} = \frac{C_s \cdot C_p}{C_s + C_p}$

Example : a quartz crystal has $R_s = 100 \Omega$
 $C_s = 0.3 \text{ p.F}$, $L_s = 3 \text{ mH}$, $C_p = 0.6 \text{ p.F}$


Calculate f_s, f_p, Q_s .

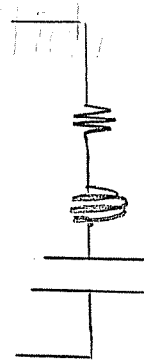

$Q_s = \frac{\omega_s L_s}{R_s}$

$$f_s = \frac{1}{2\pi\sqrt{L_s \cdot C_s}} = \frac{1}{2\pi\sqrt{3 \times 10^{-3} \times 0.3 \times 10^{-12}}} \\ = \frac{10^8}{2\pi \times 3} \approx 5 \text{ MHz}$$
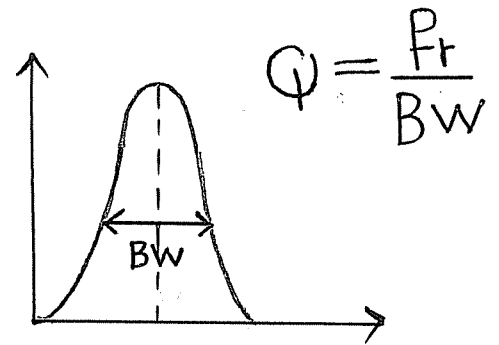
$$Q = \frac{2\pi \times 5 \times 10^6 \times 3 \times 10^{-3}}{100} \\ \approx 999$$



$$C_{eq} = \frac{0.6 \times 0.3}{0.6 + 0.3} = \frac{0.18}{0.9} = 0.2 \text{ p.F.}$$


$$f_p = \frac{1}{2\pi\sqrt{3 \times 10^{-3} \times 0.2 \times 10^{-12}}} = \frac{10^8}{2\pi\sqrt{6}} \\ = 6 \text{ MHz}$$

Non Sinusoidal Oscillator

Relaxation Oscillator

[Charging and discharging of Cap.]

{Multivibrators}

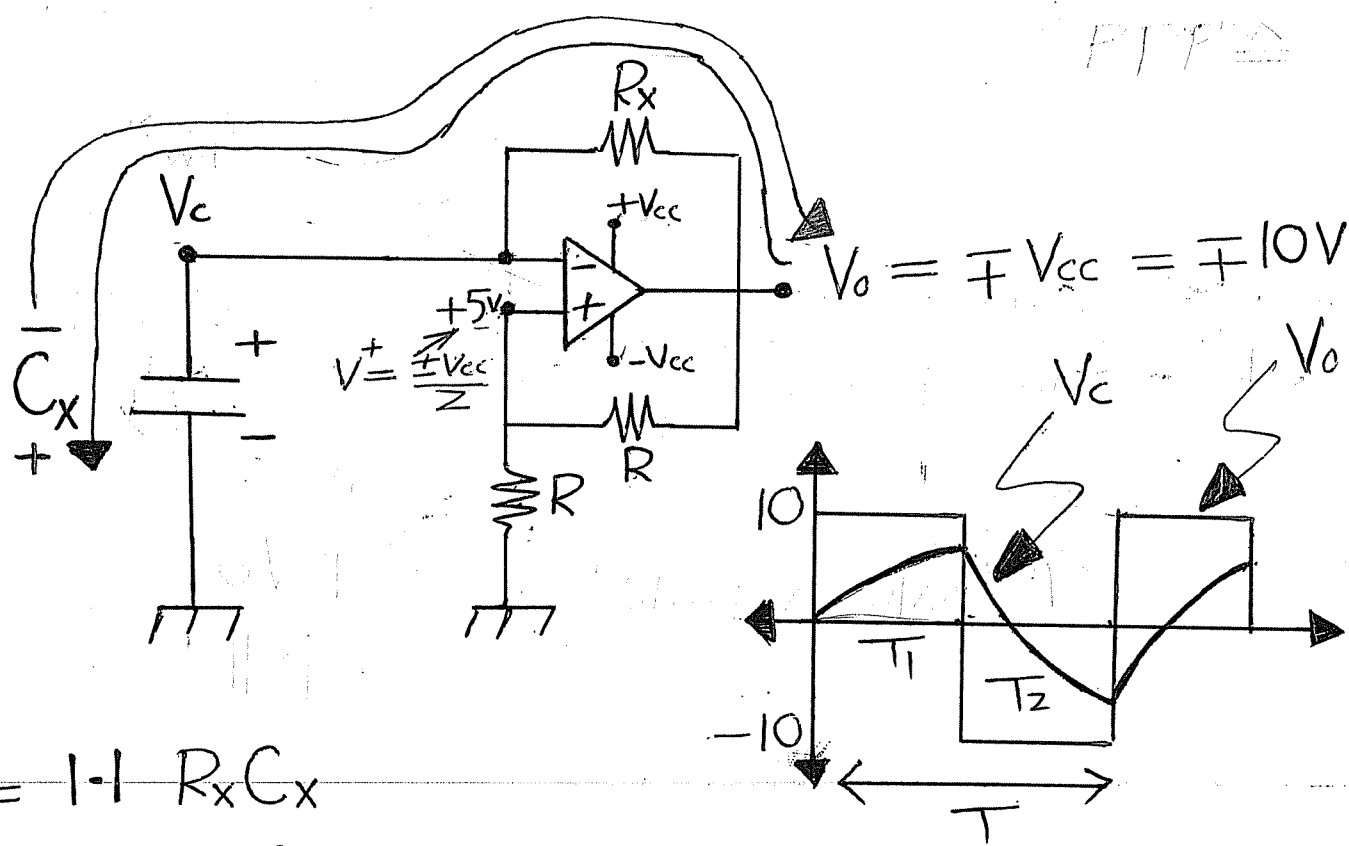


$$T_1 = 1.1 R_x C_x$$

$$T_2 = 1.1 R_x C_x$$


$$T = 2.2 R_x C_x$$

$$f = \frac{1}{2.2 R_x C_x}$$

Astable
multivibrators

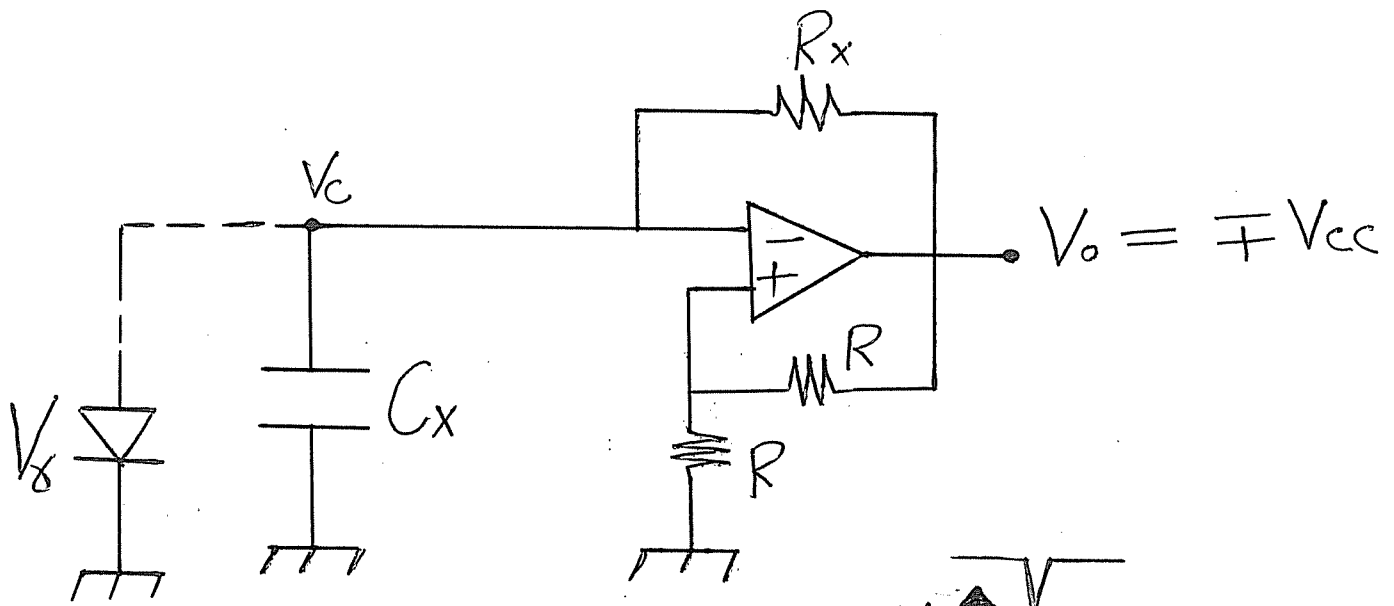

monostable

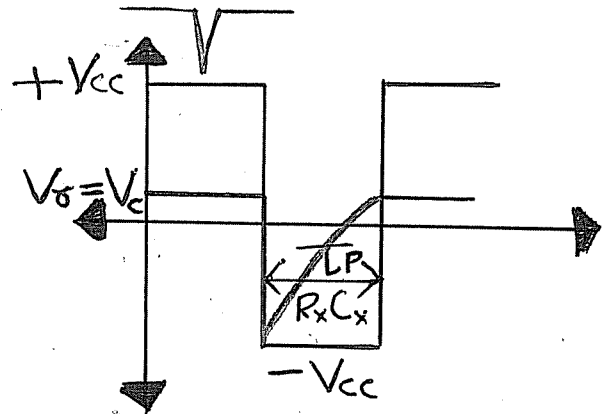


$$T_p = 0.69 R_x C_x$$



Handwritten text at the bottom left, possibly a title or label, including the characters 'x) x) 100'.

power Amplifier - (Large - Signal Amp.)

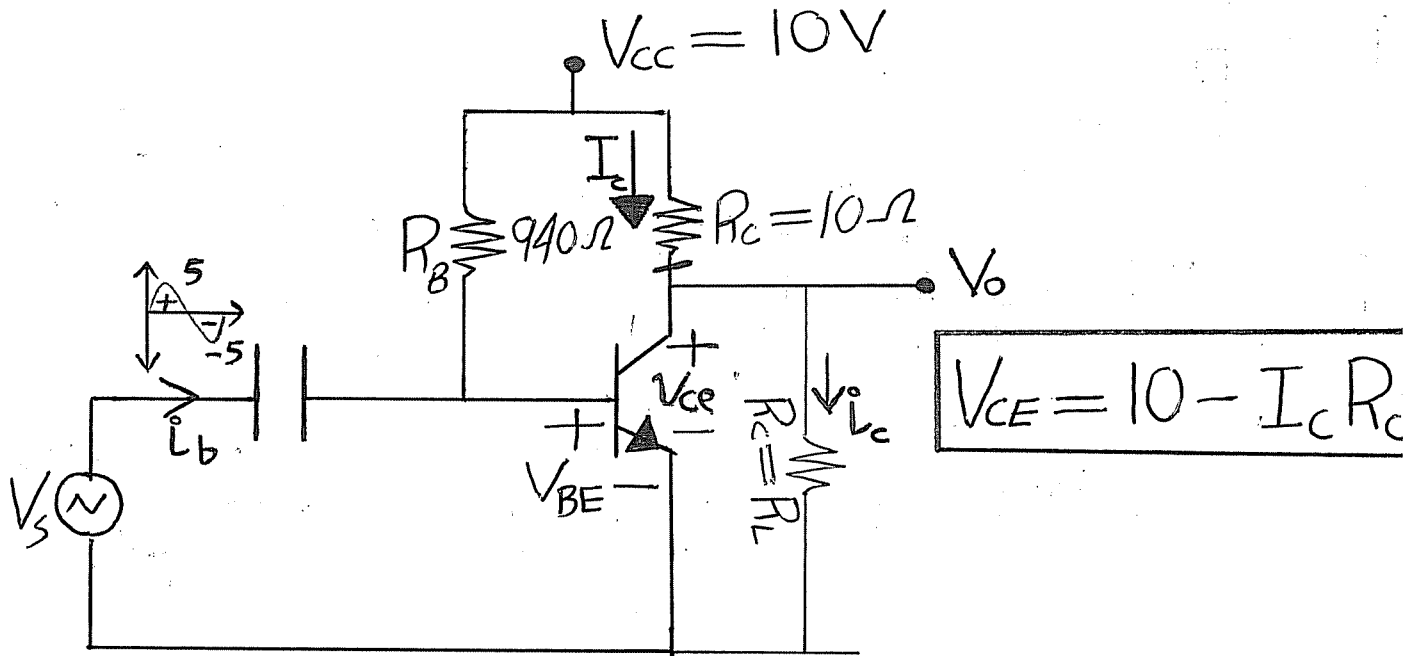

$V_{BE} = 0.6 \text{ V}$
 $\beta = 50$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$


$$= \frac{(10 - 0.6) \text{ V}}{940 \Omega}$$

$$= \frac{9.4}{940} = 10 \text{ mA}$$

$$I_c = \beta I_B = 0.5 \text{ A}$$

$$V_{CE} = 10 - 0.5 * 10 = 5 \text{ V}$$
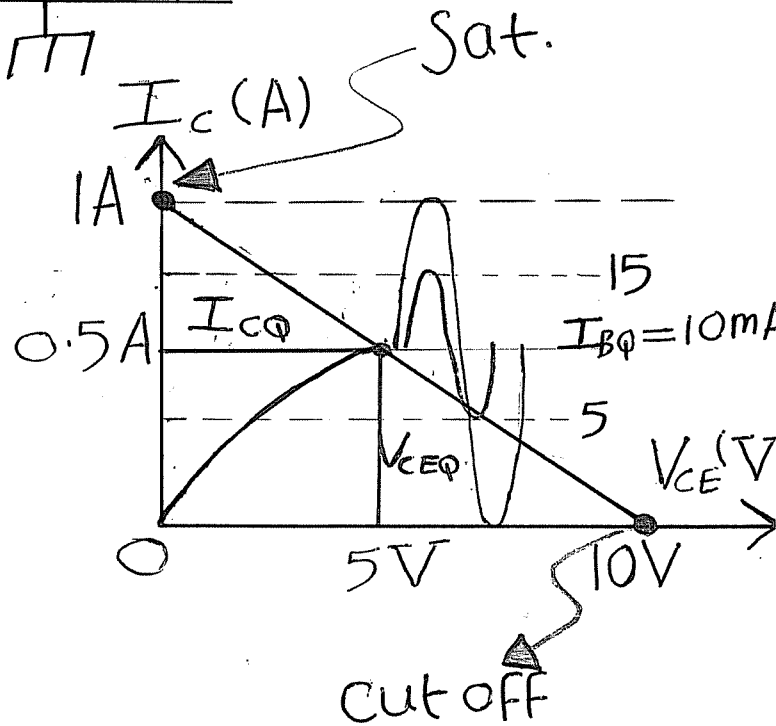
$$Q_{PT} = (5 \text{ V}, 0.5 \text{ A})$$








Power Amp. : dc i/p Power \rightarrow AC o/p Power Signal.

$$\eta = \frac{P_{out}}{P_{in}}$$

$$P_{in} = V_{cc} I_{cq}$$

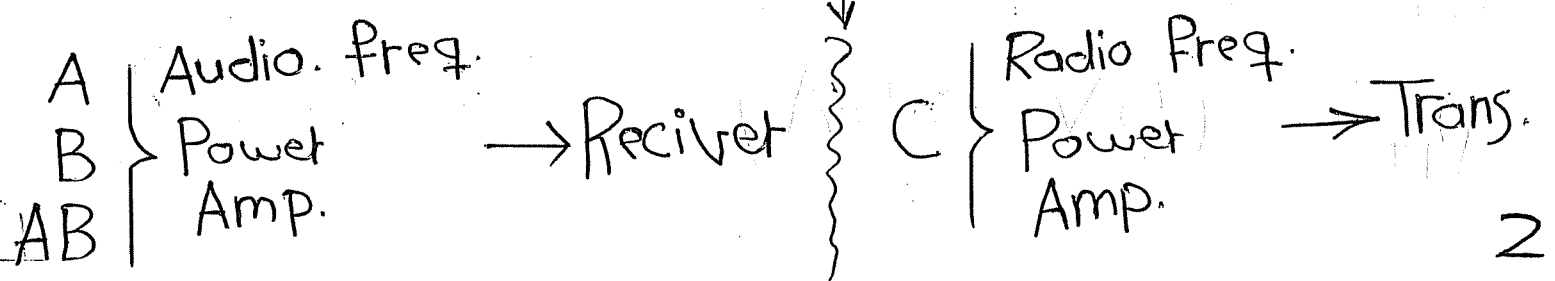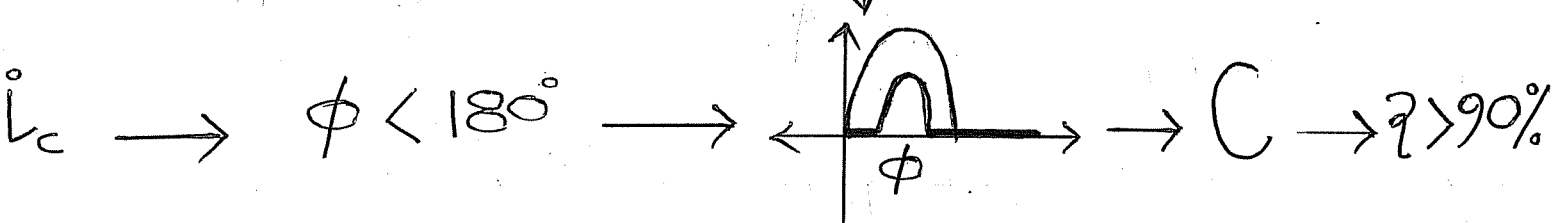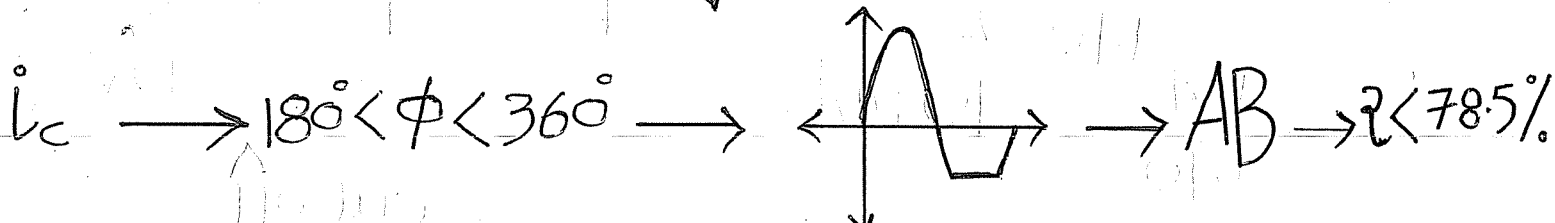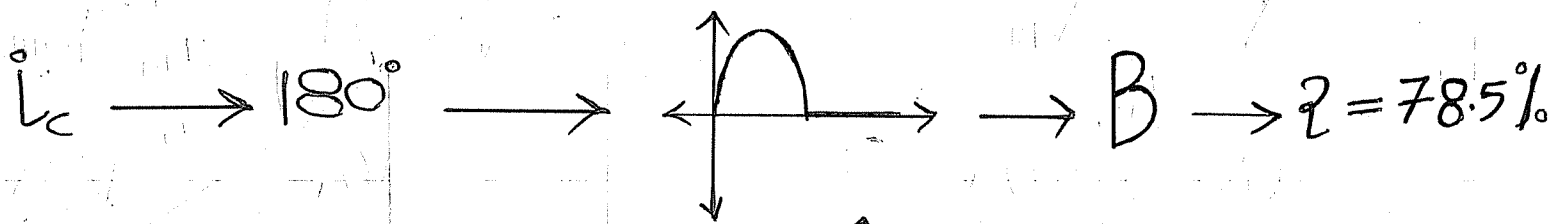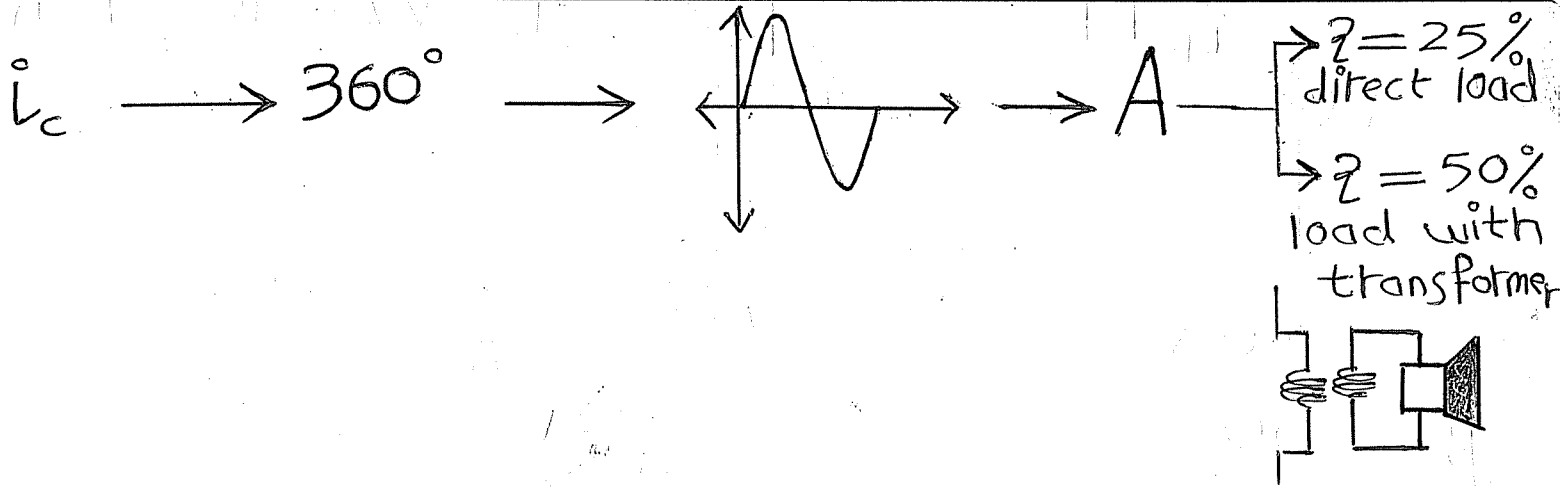
$$P_{out} = V_{ce_{rms}} \cdot i_{c_{rms}} = i_{c_{rms}}^2 R_c = \frac{V_{ce_{rms}}^2}{R_c}$$



Class-A : Q-pt at Center of D.C.I.I


(idealy) . but in general, i_c, V_{ce} are

Complete signals i_c flows for 360° .

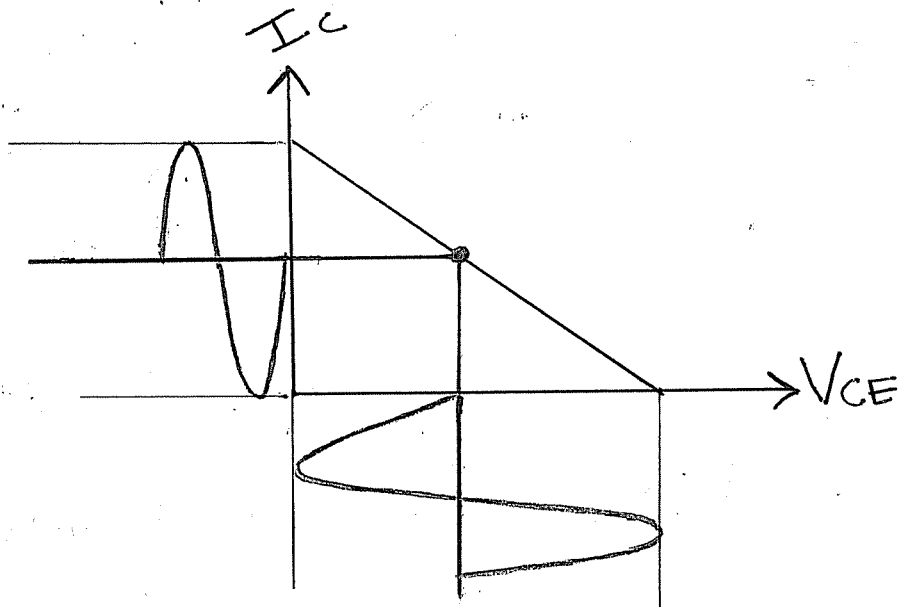


Class-B : idealy, Q-pt at Cut-off $I_{cQ} = 0$

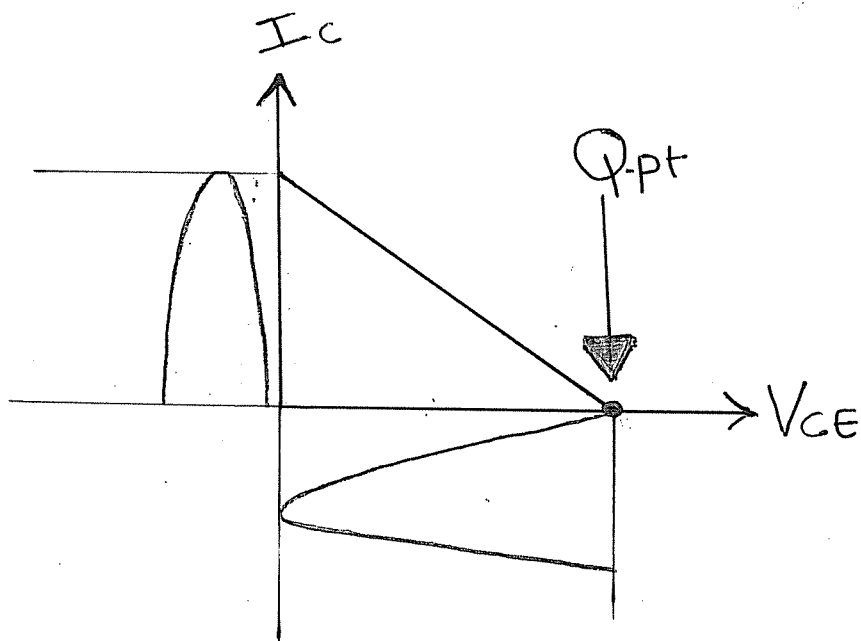but in general, i_c, V_{ce} are half cycle.



$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

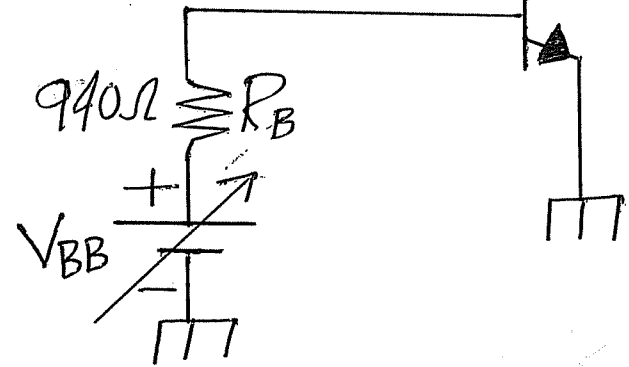


$$V_{CC} = 10V$$

 R_C

in general:


$$V_{CE} = 10 - I_C R_C$$

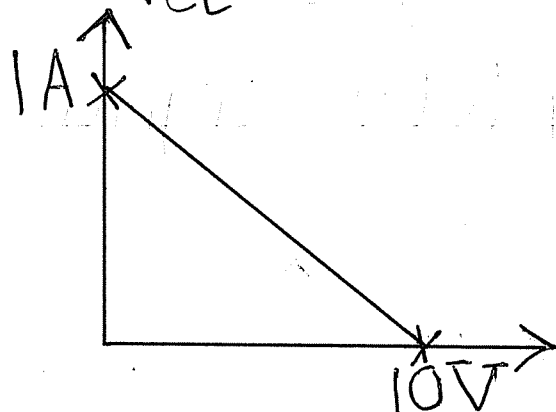

For Class-A : ideally

$$I_C = \frac{1}{2} I_{C_{max}}$$

$$= \frac{1}{2} A$$

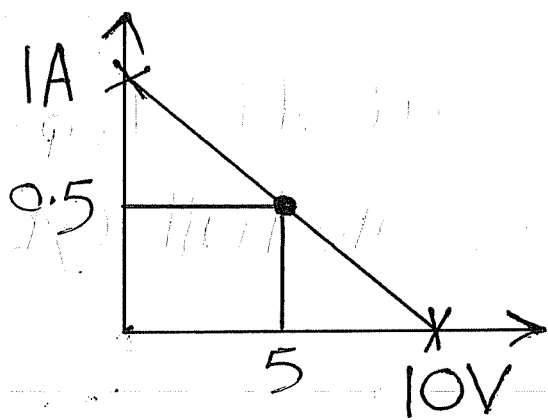

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.5}{50} = 10 \text{ mA}$$

$$I_B = \frac{V_{BB} - 0.6}{R_B}$$



$$V_{BB} = I_B R_B + V_{CE}$$

$$= 10 \times 940 + 0.6$$

$$= 10V \quad \#$$

For Class-B :

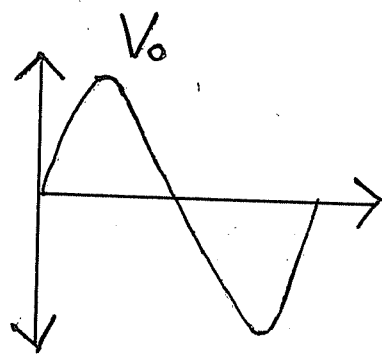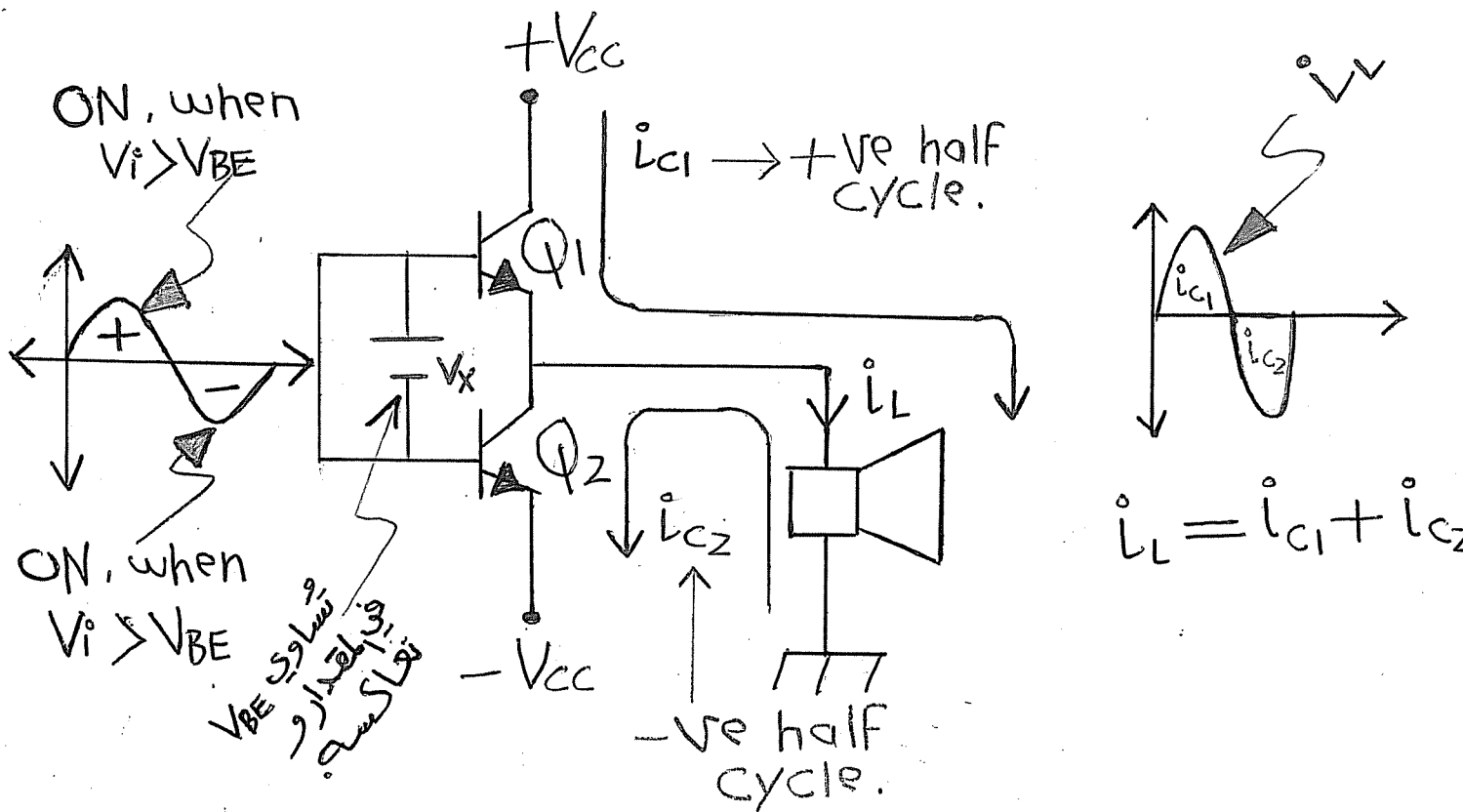
$$I_{CQ} = 0 \rightarrow I_{BQ} = 0 \rightarrow V_{BB} = V_{BE} = 0.6 \text{ V}$$



Class-B Push-Pull Power Amp.

[Using two Complemently Transistor]


Q_{pt} in origin

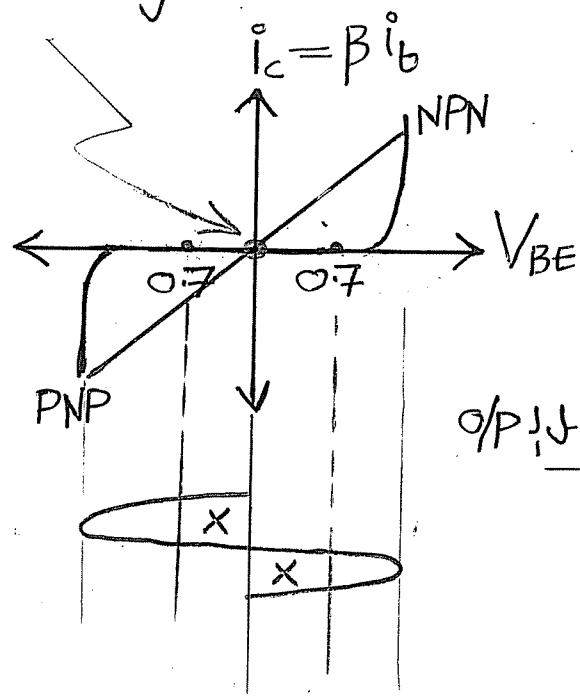

تفاسس نساو و

$$\eta = 78.5\%$$

Class-over distortion

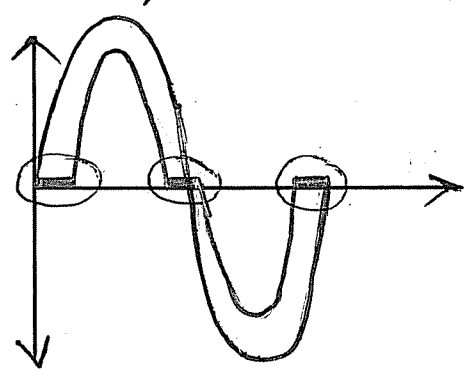

Class-AB:


Q-pt is between A and B,

→ position Choose $I_{CQ} = 0.1 \text{ A}$:

$$I_{BQ} = \frac{0.1}{50} = 2 \text{ mA}$$


$$V_{BB} = I_B R_B + V_{BE}$$
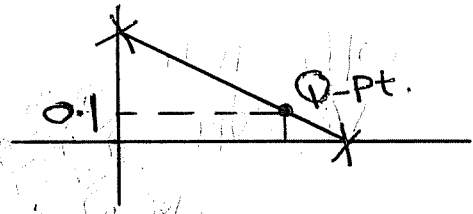
$$= 2 \times 0.94 + 0.6 = 2.48 \text{ V}$$




$$\eta < 78.5\%$$

note :-

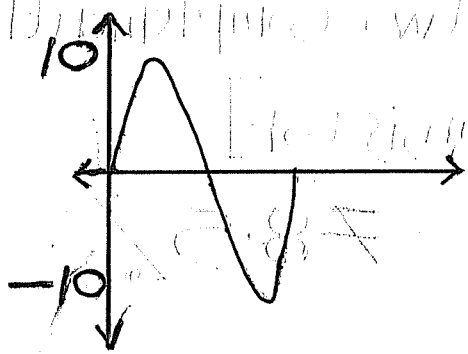
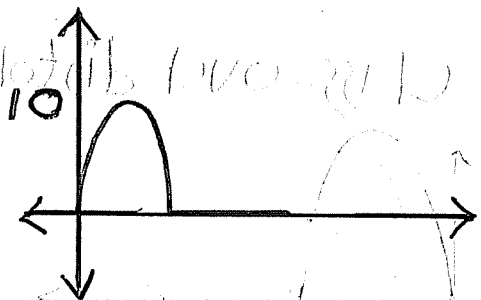
$$R_{ms} = \frac{V_P}{\sqrt{2}} = \frac{10}{\sqrt{2}} \checkmark$$



$$R_{ms} = \frac{V_P}{2} = \frac{10}{2} \checkmark$$





Class-C Power Amp. :-

Q-PT is down the cutoff.

i.e $\phi_c < 180^\circ$ (BJT is ON for $< 180^\circ$).

The BJT will be ON in +ve H.C and only when $V_i > V_{BE}$.


only when $V_i > V_{BE}$.

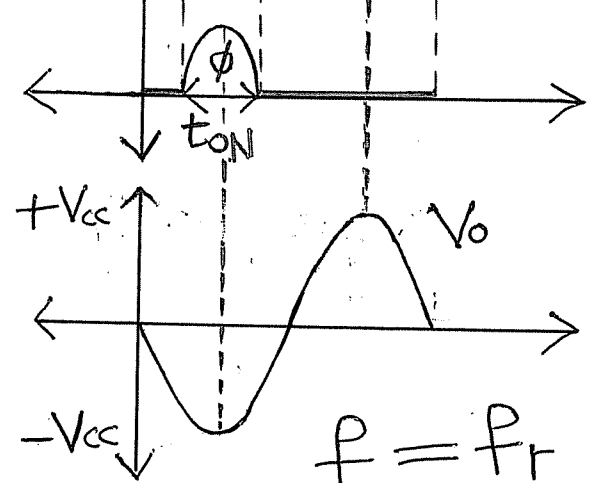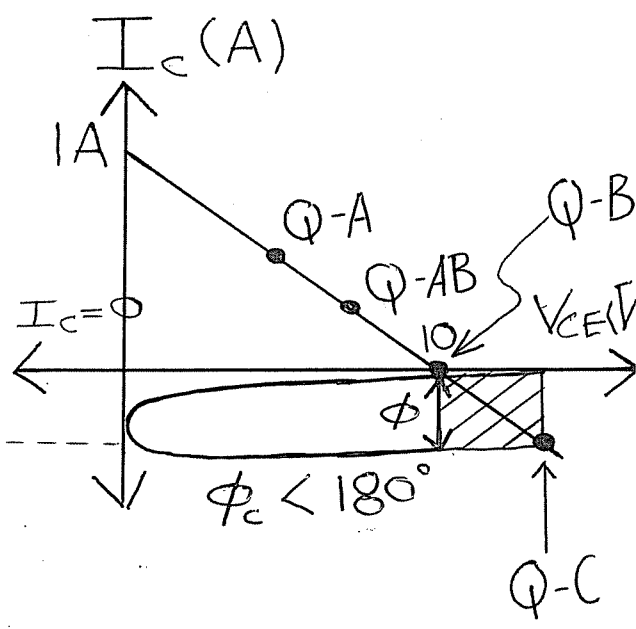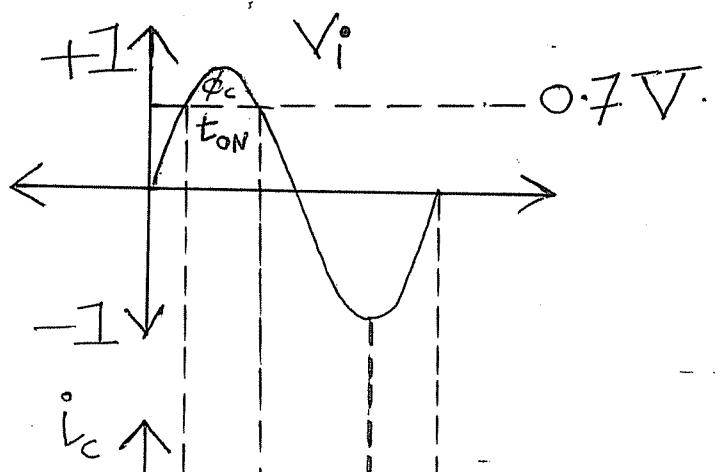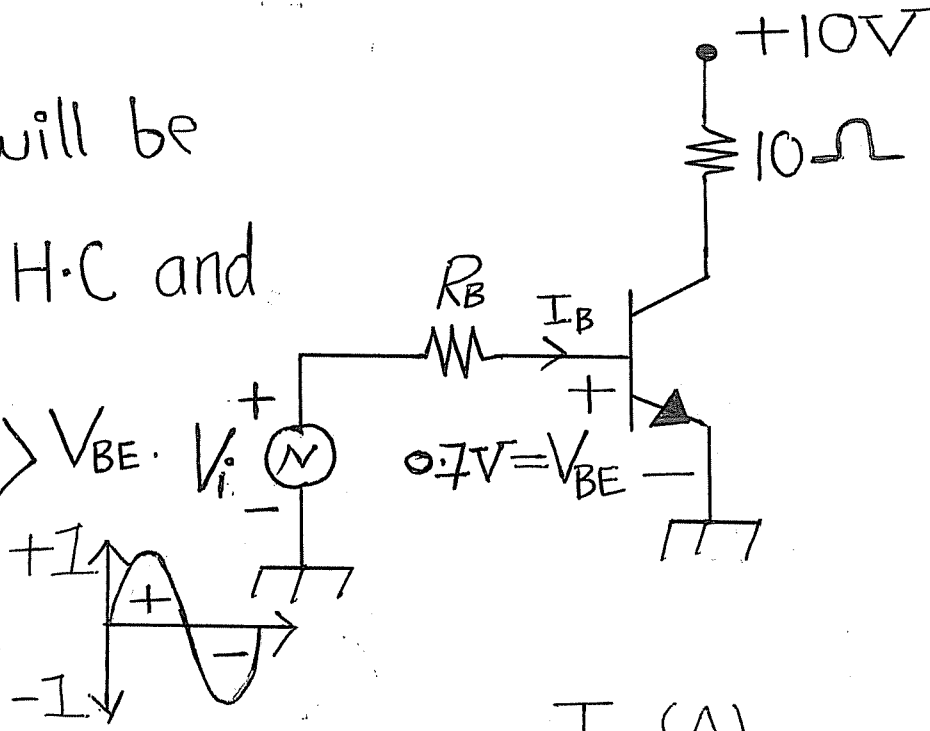

→ Fly wheel effect.


R.F \rightarrow P \uparrow \rightarrow C, L \downarrow (قيمة معتدلة)

\uparrow We use class-C in Radio freq.

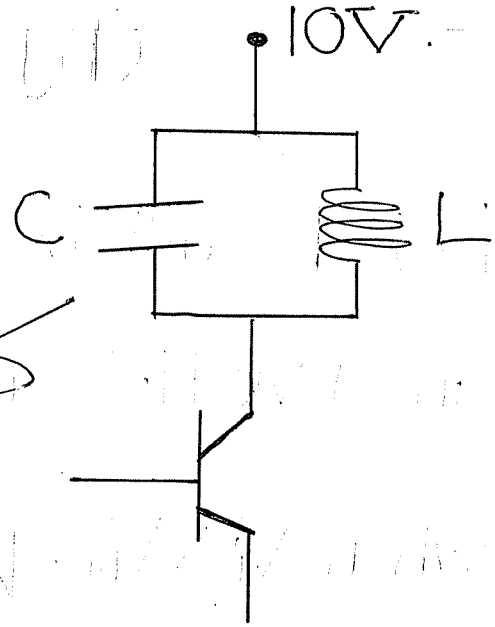


Fund. Power \downarrow تكبير الـ Power
Sig.
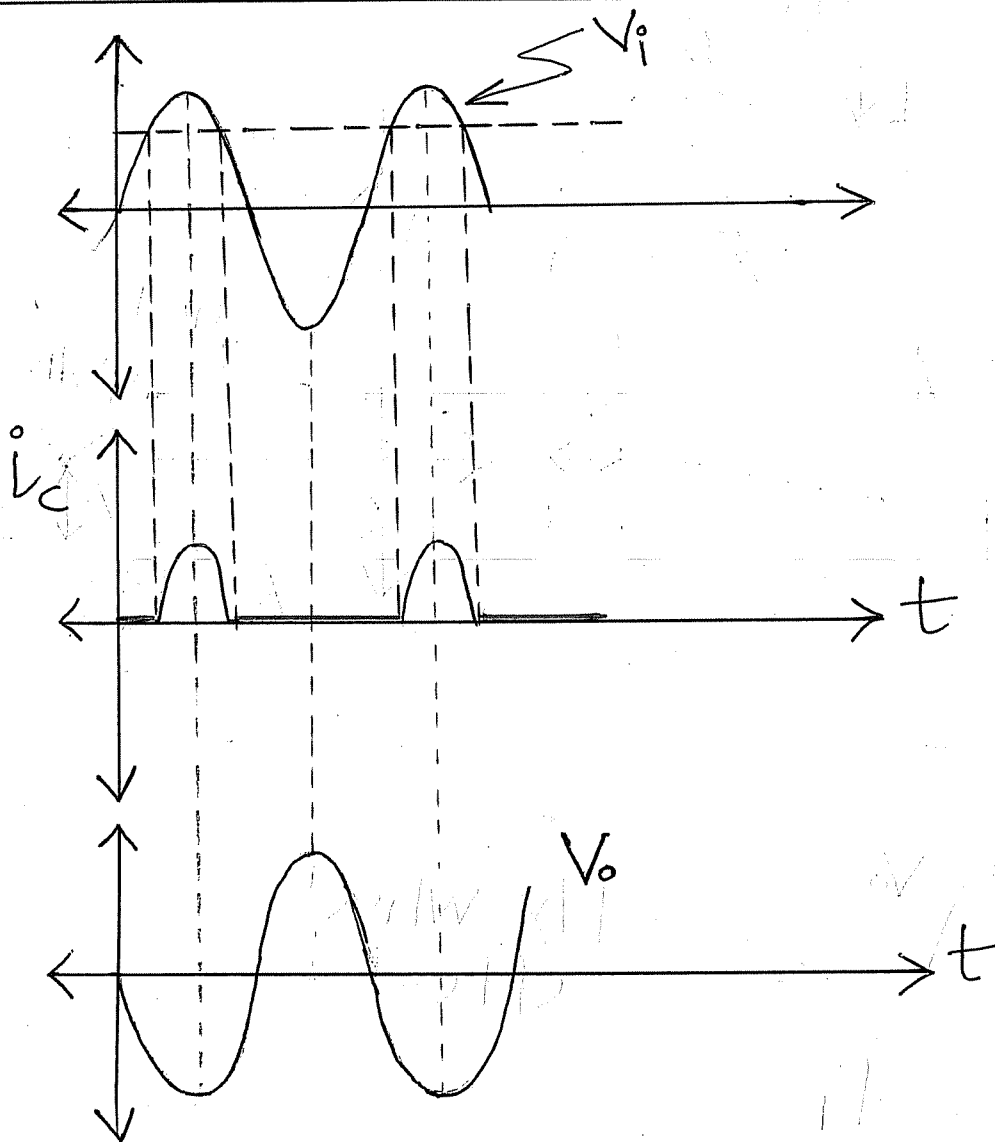
$$f_r = \frac{1}{2\pi\sqrt{LC}} = f_{fund.}$$



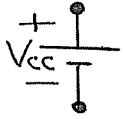2] The shape of i_c is pulse-shape, so i_c will charge the capacitor with $+V_{cc}$ $V_o = -V_{cc}$ (when BJT is ON).




3] When BJT is OFF, the capacitor will charge the inductor with $+V_{cc}$ produce $V_o = +V_{cc}$.
[The Energy will be transferred between C and L].


4] Due to fly wheel effect in tuned LC ckt the o/p will be a complete sinusoidal wave with $V_{pmax} = \pm V_{cc}$ and $f = f_r$

5] In Class-C, the load $= \frac{1}{2\pi\sqrt{LC}}$ is parallel tuned LC ckt.

6] Class-C is used as R.F power amp. in Transmitter.

Power Calculation

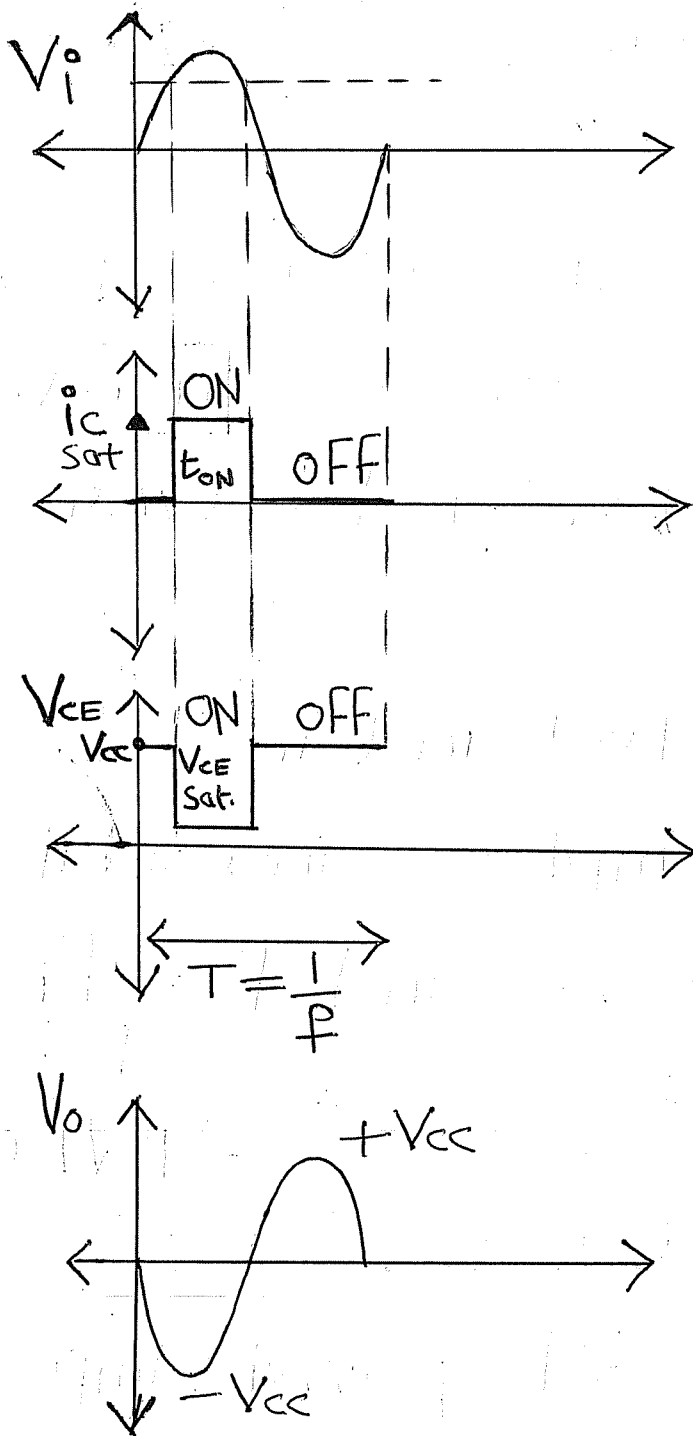

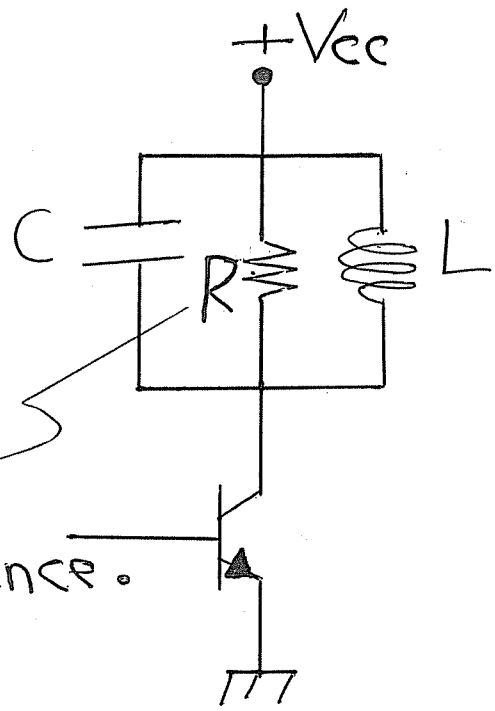

#R: Total effective Resistance.

at Resonant: $X_L = X_C$

• reactance \cancel{X} ←

* Average - load power:

$$\bar{P}_L = \frac{V_o^2(\text{rms})}{R} = \frac{\left(\frac{V_{OP}}{\sqrt{2}}\right)^2}{R} = \frac{V_{CC}^2}{2R} \quad \#.$$

* Average DC power dissipated in BJT:

$$\bar{P}_D = P_D(\text{ON}) \cdot \frac{t_{ON}}{T} = I_C(\text{sat}) \cdot V_{CE}(\text{sat}) \cdot \frac{t_{ON}}{T} \quad \#.$$

$$\boxed{\bar{P}_i(\text{DC}) = \bar{P}_D + \bar{P}_L}$$

Conversion efficiency:-

$$\eta \% = \frac{\text{Average AC load power}}{\text{DC input power drawn from DC source}} * 100\%$$

$$\eta \% = \frac{\bar{P}_L}{P_i(\text{DC})} = \frac{\bar{P}_L}{\bar{P}_D + \bar{P}_L} * 100\%$$

Exa. A Class-C R.F. power Amp. is used to process a signal with ($f = 500 \text{ kHz}$), $V_{cc} = +20 \text{ V}$, and the total effective resistance of the tuned ckt. ($R = 100 \Omega$), and the BJT has $I_{c(\text{sat.})} = 1 \text{ A}$ and ($V_{ce(\text{sat.})} = 0.3 \text{ V}$) and it is (ON) for ($0.4 \mu\text{s}$). Calculate


1) \bar{P}_L , $\bar{P}_i(\text{DC})$, $\eta\%$?

2) Sketch $V_o(t)$.

3) Design the tuned ckt. process the required signal.

Solution :

1)

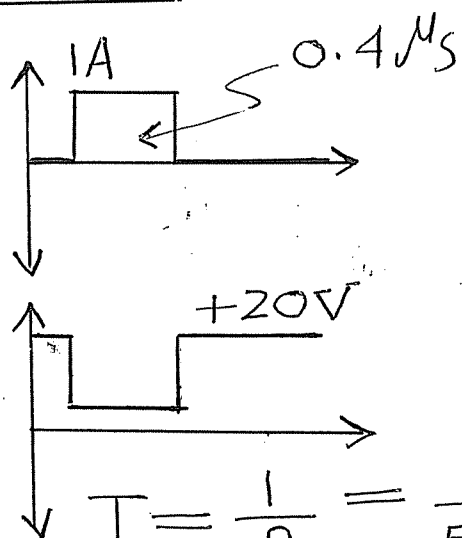

$$T = \frac{1}{f} = \frac{1}{500k} = 2 \mu s.$$


$$\bar{P}_L = \frac{V_{CC}^2}{2R} = \frac{20^2}{2 \times 100} = 2 \text{ W}.$$

$$\begin{aligned} \bar{P}_D(\text{ON}) &= P_D(\text{ON}) \cdot \frac{t_{\text{ON}}}{T} \\ &= I_c(\text{Sat}) \cdot V_{CE}(\text{Sat}) \cdot \frac{t_{\text{ON}}}{T} \\ &= 1 * 0.3 * \frac{0.4 \mu s}{2} = 0.06 \text{ W}. \end{aligned}$$

$$P_i(\text{DC}) = 2 + 0.06 = 2.06 \text{ W}.$$

$$\eta \% = \frac{2}{2.06} * 100\% = 97\%.$$

2)

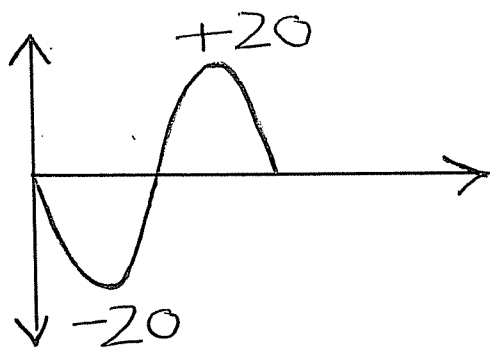

$$f = 500k \text{ Hz}.$$


3) we must Choose $f_r = f = 500 \text{ kHz}$
 $= \frac{1}{2\pi\sqrt{LC}}$

let $C = 0.01 \mu\text{F}$

$$f_r^2 = \frac{1}{2\pi^2 LC}$$


$$L = \frac{1}{4\pi^2 \times 0.01 \mu \times 25 \times 10^{10}}$$

$$= 10 \mu\text{H} \cdot$$

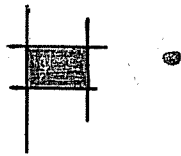


Class - C	Class - A, B, AB
Nonlinear.	linear p. A.
R.F.p.A.	A.F.p.A.
Used in Transmitter	Used in Receiver.

Class - A

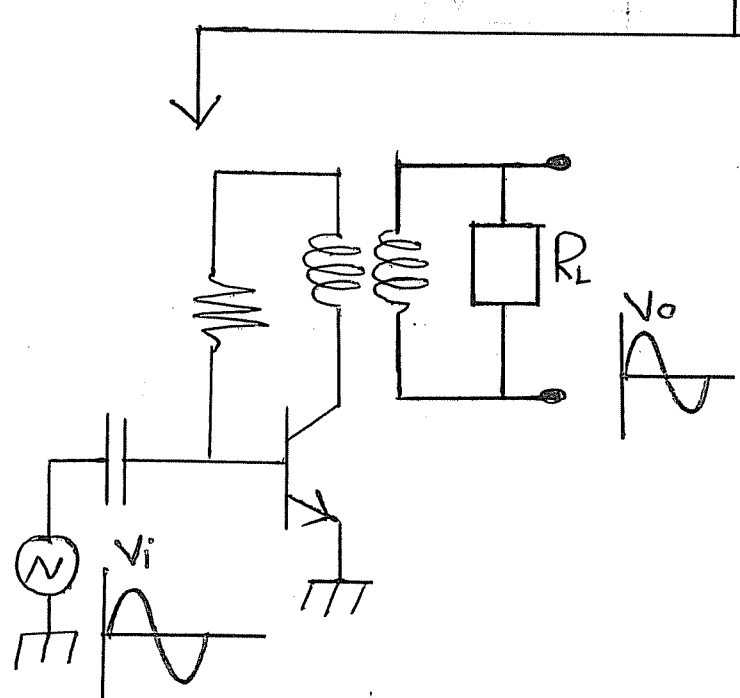

Transformer Coupled
 $\eta_{max} = 50\%$

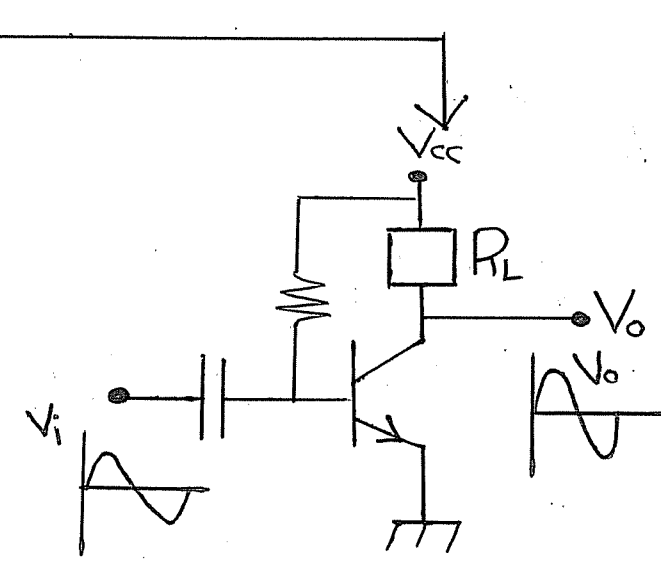


Direct Coupled
 $\eta_{max} = 25\%$


$$\eta = \frac{\bar{P}_L}{P_{i(D.C)}} * 100\%$$

• عند نفس \bar{P}_L و $P_{i(D.C)}$ في direct coupled أكبر من Transformer Coupled.

Class-B push pull power Amp. :-

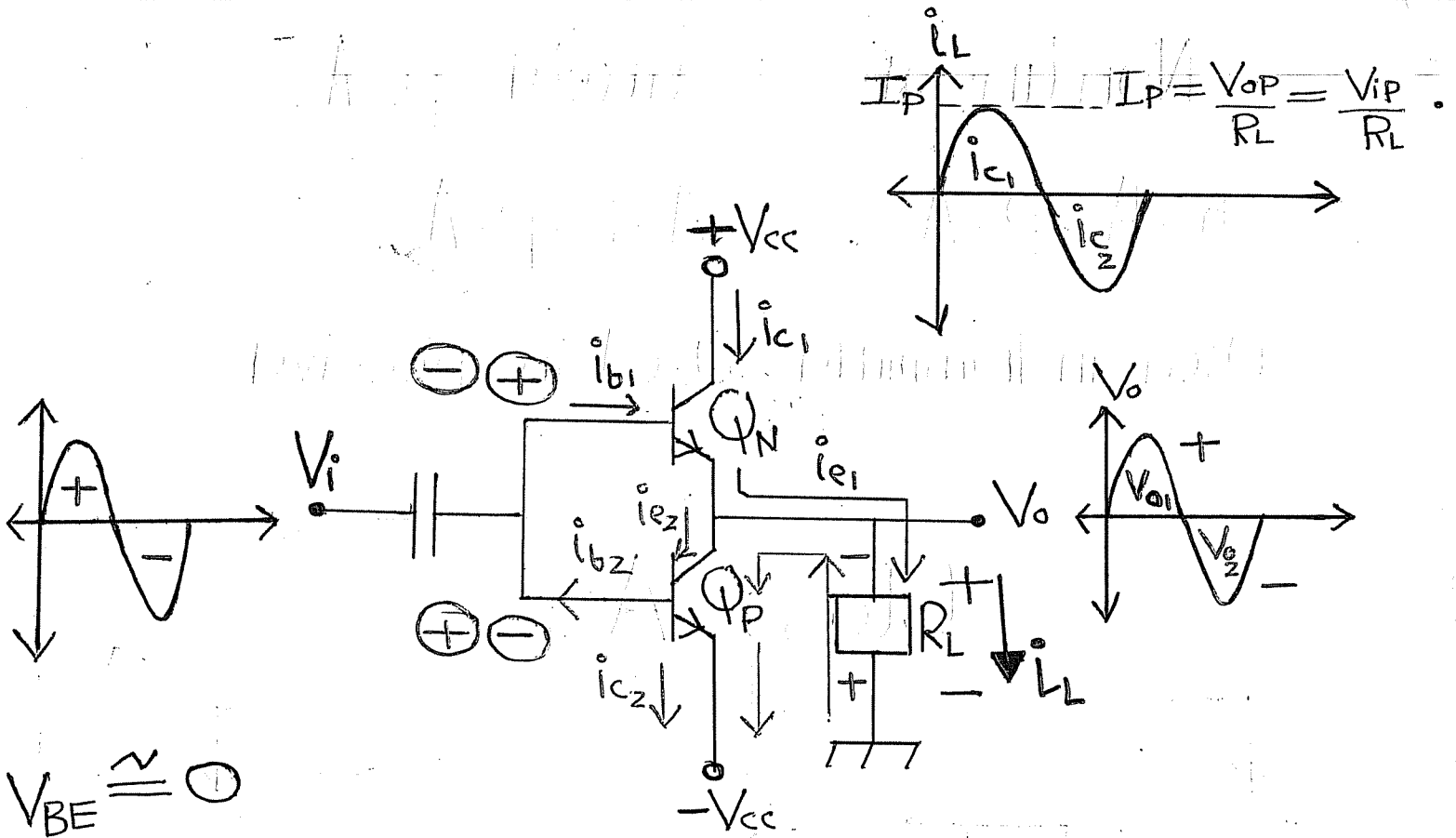

it is Common Collector : [C.C]

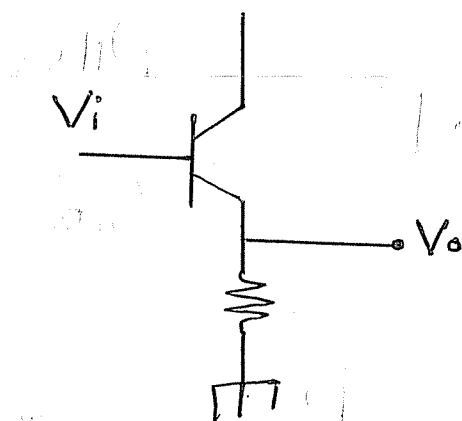

$$A_v \approx 1 \rightarrow V_o = V_i$$

1] without V_i , Q_N and Q_P are off, $V_o = 0$

2] During +ve H.C of V_i , Q_N is ON, Q_P is off

$i_{c1} = i_{e1} = i_L$ will flow in R_L Causing

$$V_o = i_c R_L.$$

3] In -ve H.C of V_i , Q_P is ON, Q_N is off,

$i_{c2} = i_{e2} = i_L$ will flow in R_L Causing

$$V_o = -i_{e2} R_L.$$

$$\bar{P}_L = \frac{V_o^2}{R_L}, i_L^2 R_L, i_L V_L \quad [\text{Rms value}].$$

or:

$$\bar{P}_L = \frac{V_{OP}^2}{Z R_L}, \frac{i_{LP}^2}{Z} R_L, \frac{i_{LP} V_{LP}}{Z}.$$


$$P_{i(DC)} = V_{CC} \cdot I_{DC}$$

$$= P_{DC}^{\oplus} + P_{DC}^{\ominus}$$

1] For +ve H.C :- $\rightarrow Q_N \checkmark$

$$I_{DC} = \frac{I_P}{\pi}$$
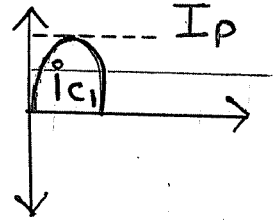
$$P_{DC}^+ = V_{CC} \cdot \frac{I_P}{\pi}$$




2] For -ve H.C :- $\rightarrow Q_P \checkmark$

$$I_{DC} = \frac{-I_P}{\pi}$$

$$P_{DC}^- = -V_{CC} \left(\frac{-I_P}{\pi} \right)$$

$$= V_{CC} \cdot \frac{I_P}{\pi}$$

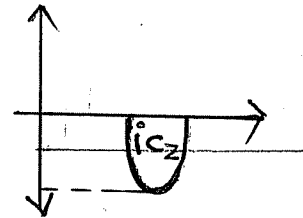

$$\rightarrow \boxed{P_{DC} = 2 \cdot V_{CC} \frac{I_P}{\pi}} \quad \#$$

$$I_P = \frac{V_{OP}}{R_L}$$

Conversion efficiency :-

$$\eta = \frac{\bar{P}_L}{\bar{P}_{D.C.}} * 100\%$$

$$\eta = \frac{\frac{V_{LP} \cdot I_{LP}}{2}}{\frac{2V_{CC} I_{LP}}{\pi}} = \frac{\pi V_{LP}}{4 V_{CC}} * 100\%$$

When $V_{LP} = V_{CC} \rightarrow \eta = \eta_{max}$


$$\eta_{max} = \frac{\pi}{4} 100\% = 78.5\%$$

↳ 22.5% Power dissipated in Transistors.

Power Dissipation in Transistors :-

$$P_D (\text{each}) = \frac{\bar{P}_{i(DC)} - \bar{P}_L}{2}$$

$$V_{CE1} = V_{CC} - I_{C1}R_L$$

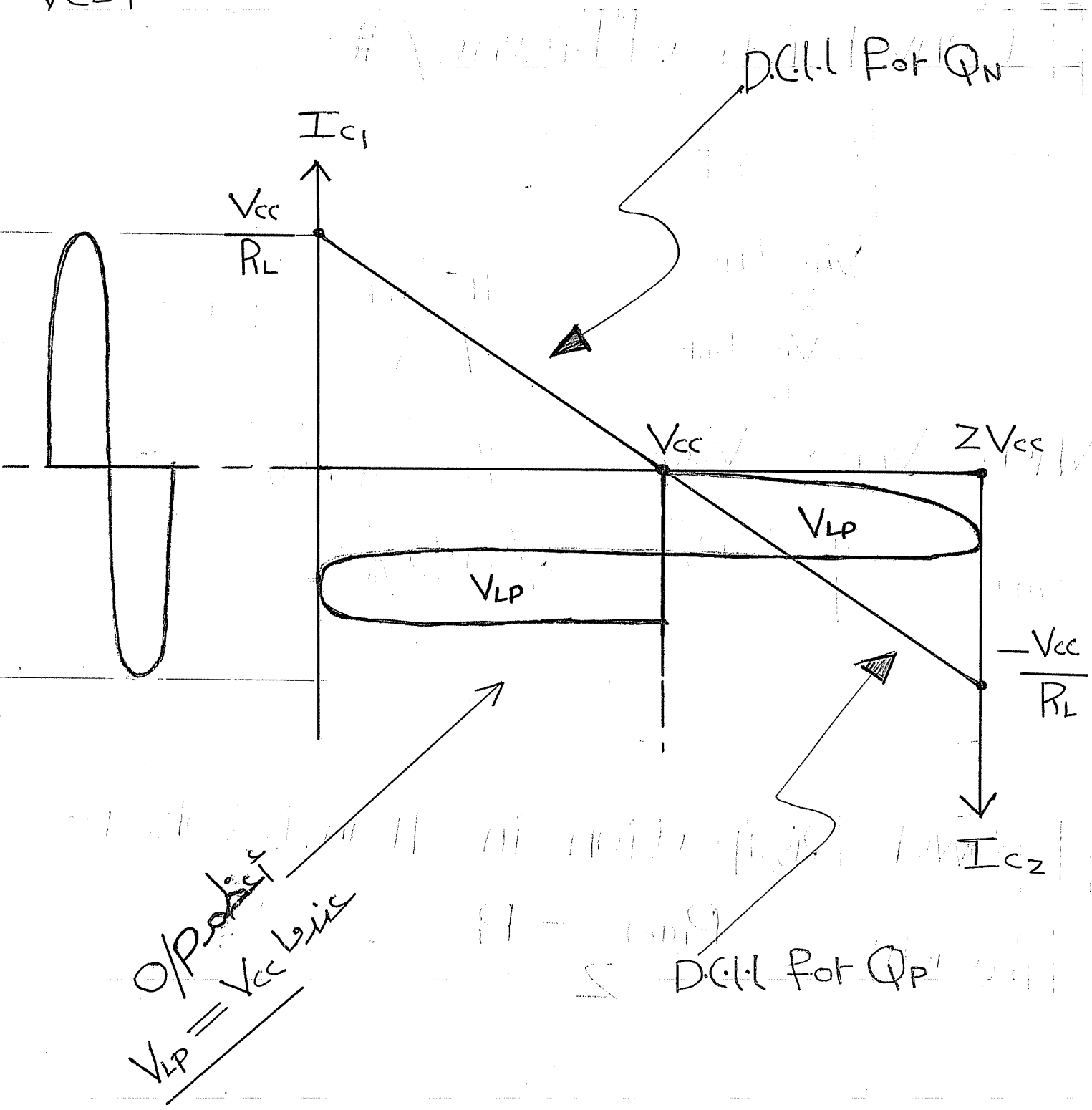

الـ AC و الـ DC منطبتان [نفس الختم].

Exa. A Class-B Push Pull power amp. Using Complementary Trans: has $V_{CC} = \pm 25V$, is used to feed 8Ω Speaker. If the i/p voltage is:

$$V_i = 20 \sin \omega t \text{ V.}$$

1] Calculate: \bar{P}_{DC} , \bar{P}_L , $\eta\%$, P_D (each).


2] Sketch D.C.I.L with o/p voltage and Current Swings.

3] What is the peak i/p voltage required to give max. Conv. efficiency? [assume $V_{BE} \approx 0$].

Sol. Since the cct. is (C.C):

$$V_o = V_i = 20 \sin \omega t \text{ (V).}$$

$$V_o = V_L$$

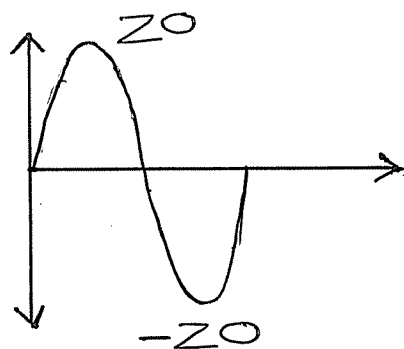

Communication Electronics Sheet 1

Q1: A crystal oscillator has the following parameters:

$$L = 0.33 \text{ H}, C_s = 0.065 \text{ pF}, C_p = 1 \text{ pF}, R_s = 5 \text{ k}\Omega$$

- i) Calculate f_s , f_p and selectivity Q .
- ii) Derive an expression for f_p in terms of f_s , C_p & C_s .

Q2: Does the oscillator shown work?

If yes calculate f_o .

If no modify the ckt. to operate as an oscillator and calculate f_o .

Sketch $V_o(t)$


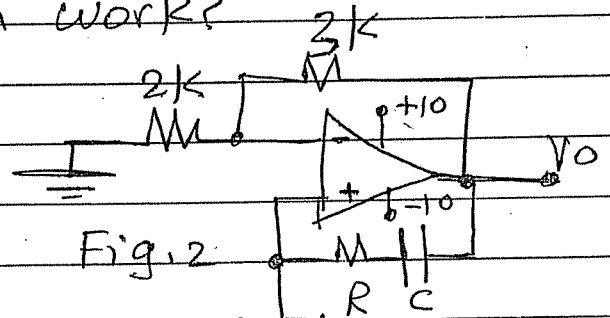


Fig. 2

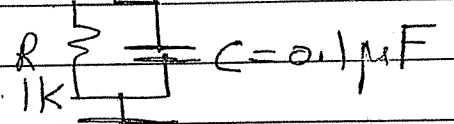

Q3: Name the oscillator shown in Fig. 3 & Calculate the freq. of oscillation and the minimum value for R_D required for oscillation. Assume the JFET is biased such that $g_m = 2 \text{ mA/V}$.

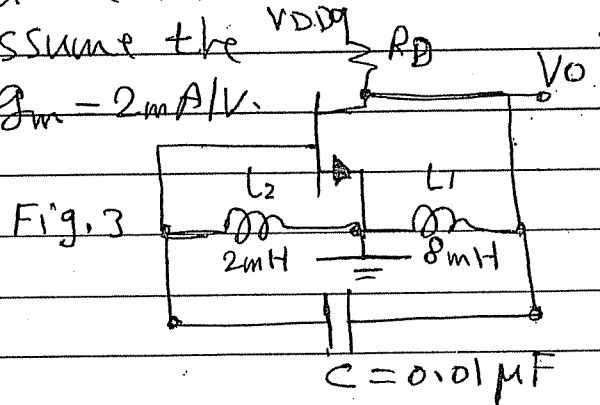


Fig. 3


Q4: Design a Colpitts Oscillator to have $f_o = 50 \text{ kHz}$. Use an op-Amp. with $V_{CC} = \pm 20 \text{ V}$. The gain of the Amplifier must be 10. The available inductor $L = 0.1 \text{ mH}$. Draw the circuit diagram, calculate all the required components value and draw $V_o(t)$.

Q5: For the oscillator ckt. shown.

$$|B| = \frac{V_F}{V_o} = \frac{1}{2g} \text{ at a freq.}$$


$$\text{of } f_o = \frac{1}{2\pi\sqrt{6}RC}$$

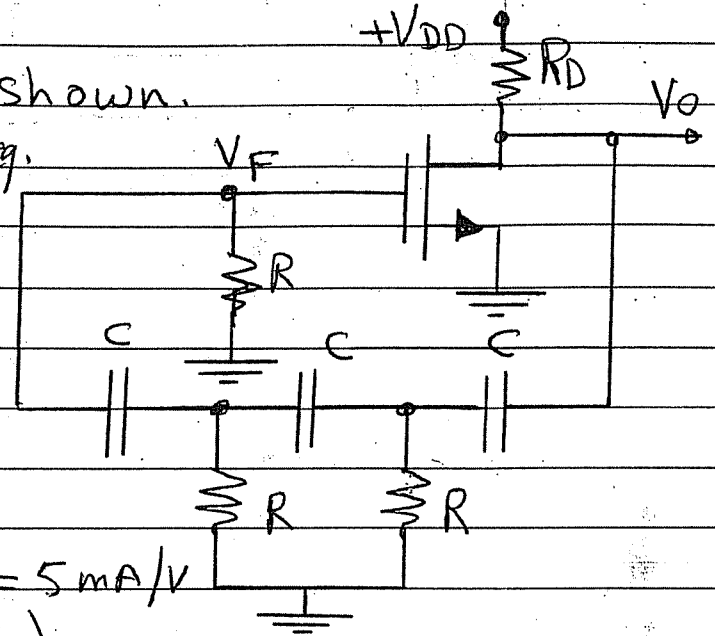*) Design the ckt. to oscillate at 20 kHz
 (choose $C = 0.01 \mu\text{F}$)
 and knowing that $g_m = 5 \text{ mA/V}$
 (Hence determine R & R_D).




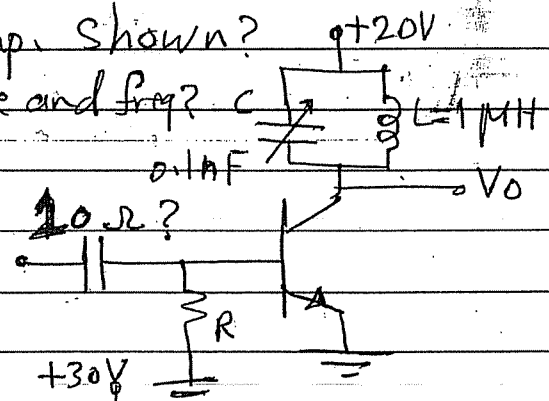Q6: Name the class of the power Amp. shown?


- Draw $V_o(t)$ indicating Amplitude and freq?
- Calculate $P_{o(max)}$ when the total A.C resistance of the tuned ckt. is 10Ω ?



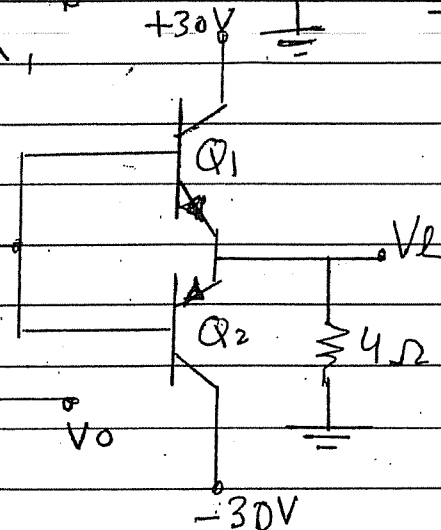Q7: For the Complementary class-B push power Amplifier shown, the input is $V_i = 20 \sin \omega t$ (V)
 Calculate P_L , P_i (D.C)
 $\%$ and power dissipated V_o in each transistor.



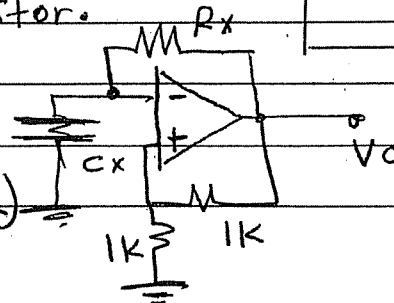Q8) Calculate f_o and draw $V_o(t)$
 ($C_x = 10 \text{ nF}$, $R_x = 1 \text{ k}\Omega$)




Filters :-

Selective ccts allow certain bands of Freq. to pass and reject other bands. It contain freq. dependant elements (C, L and R). In general filters are classified as: (hard wave)

Passive filters
(R, C, L)

Active filters
(R, C, L) + Active element
(BJT, FET, OP-Amp)

<u>Passive filter</u>	<u>Active filter</u>
No gain	Certain gain
No power consumption	<u>DC</u> sources are required (power consumption)
Suffer from loading effect	No loading effect.

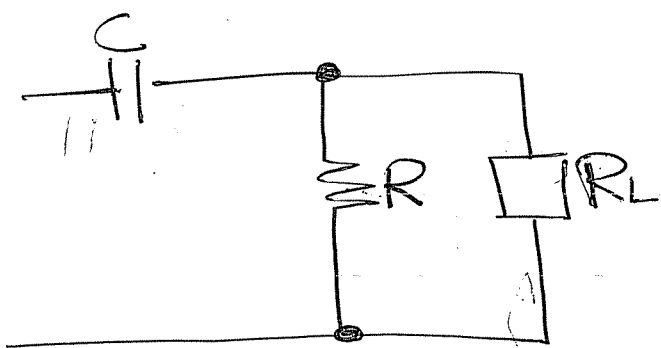

$$f_c = \frac{1}{2\pi RC}$$


load resistor

$$f_c = \frac{1}{2\pi R_{eq} C}$$

↑
(R || RL)

$$f_c = \frac{1}{2\pi RC}$$

بسته به مقاومت بار
در خروجی

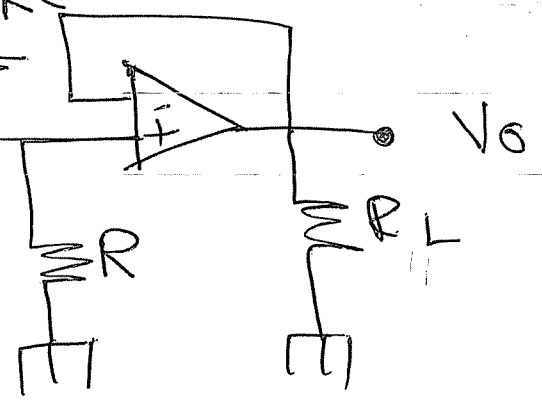


$$R_i = \infty$$

$$R_i || R = R$$

بسته به

According to freq. band, Filters are classified in to :-


① Low pass-filter (LPF) :-

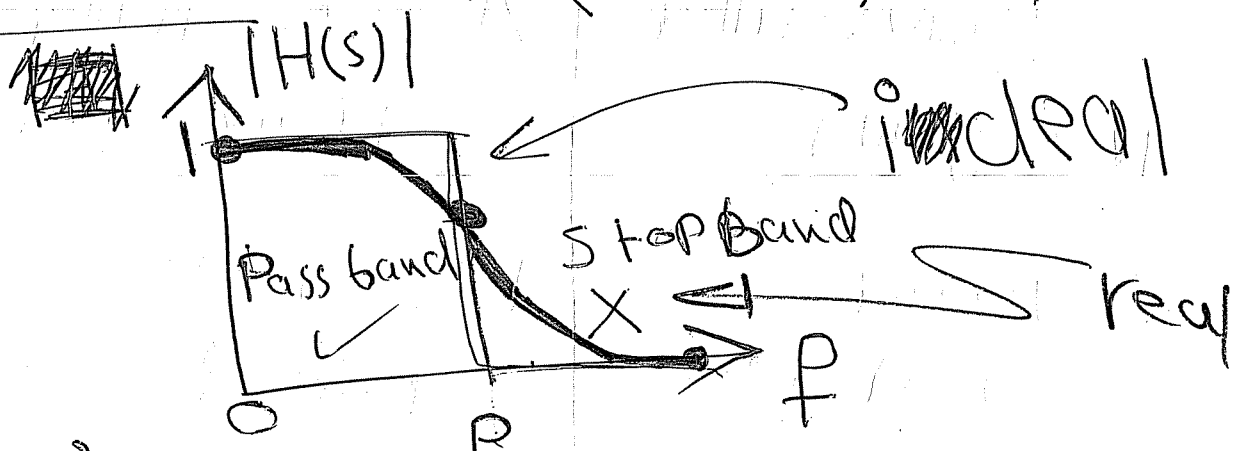

در خروجی

Receiver ,
detector

3KHz

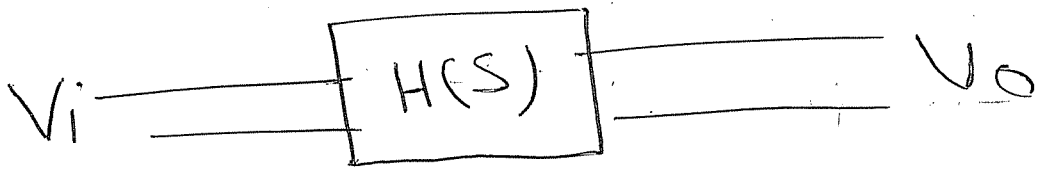


$$H(s) = \frac{V_o}{V_i}$$

active inductor, active

size 25-50u

Passive LPF:

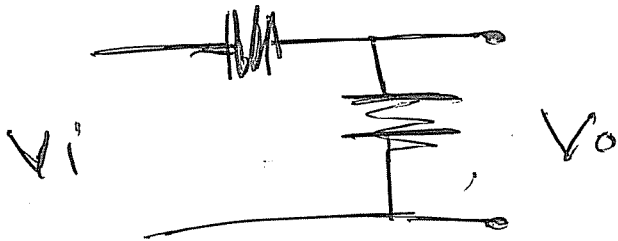

$$f_c = \frac{1}{2\pi RC}$$

$$\frac{V_o}{V_i} = \frac{X_c}{X_c + R} = \frac{1}{1 + \frac{R}{X_c}}$$

$$f = 0 \rightarrow X_c = \infty$$



$$V_o = V_i$$

$$f = \infty \rightarrow X_c = 0$$

$$X_c = \frac{1}{2\pi f C}$$

$$f = 0 \rightarrow \frac{V_o}{V_i} = 1$$
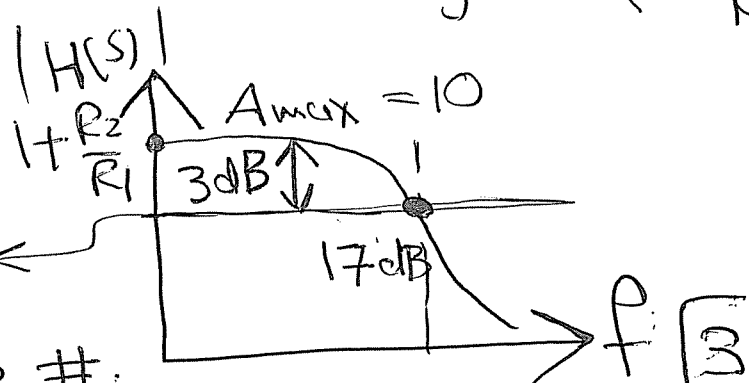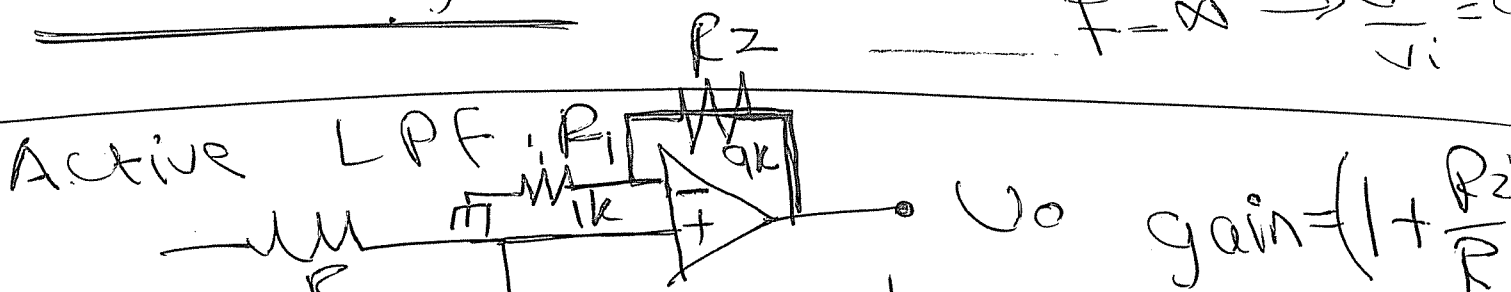
$$f = \infty \rightarrow \frac{V_o}{V_i} = 0$$




$$A(\text{dB}) = 20 \log_{10} A \sqrt{2}$$

$$= 20 \log_{10} 10 = 20 \text{ dB} \#$$


$R_1, R_2 \rightarrow$ ليس لها علاقة بـ f_c

$C, R \rightarrow$ هي التي تحدد f_c

② High-pass Filter (HPF) :-

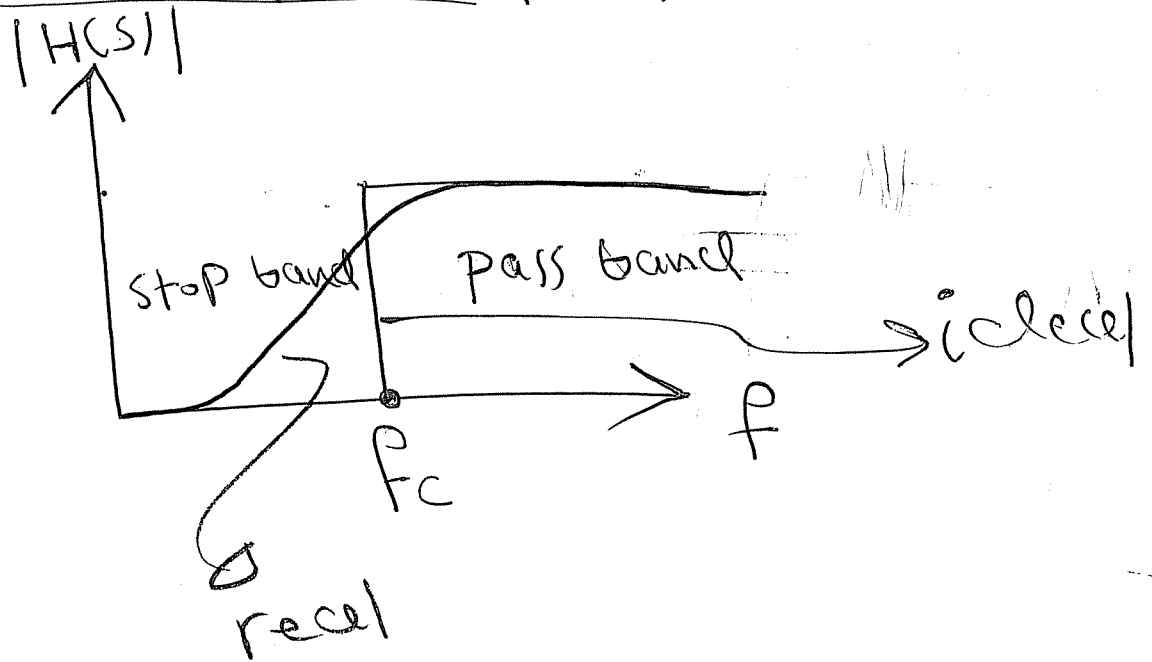

Passive:-

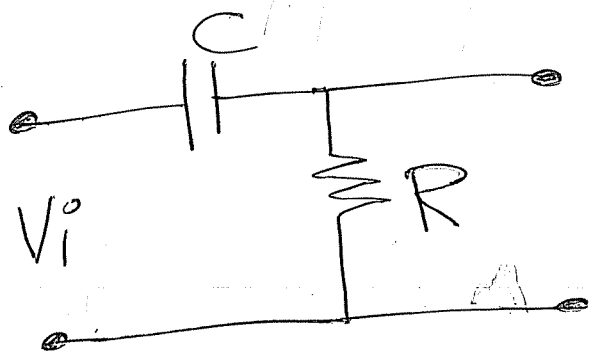

$$\frac{V_o}{V_i} = \frac{R}{R + \frac{1}{j\omega C}}$$


$$= \frac{1}{1 + \frac{1}{j\omega R C}}$$

$\omega = 0 \rightarrow \frac{V_o}{V_i} = 0$
 $V_o = 0$

$\omega = \infty \rightarrow \frac{V_o}{V_i} = 1 \rightarrow V_o = V_i$


$$f_c = \frac{1}{2\pi RC} \sqrt{4}$$

active (HPF) :-

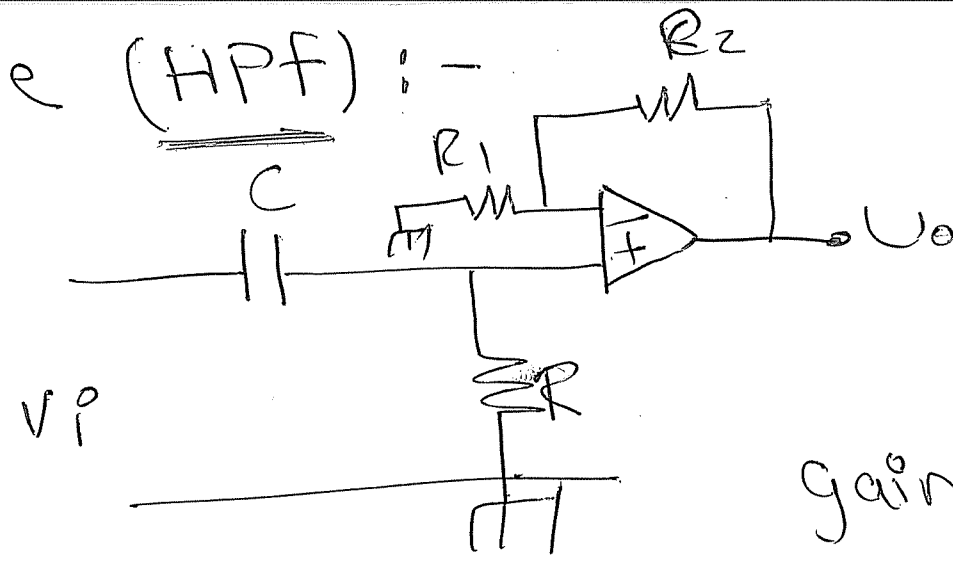

$$\text{gain} = 1 + \frac{R_2}{R_1}$$

$$f_c = \frac{1}{2\pi RC}$$

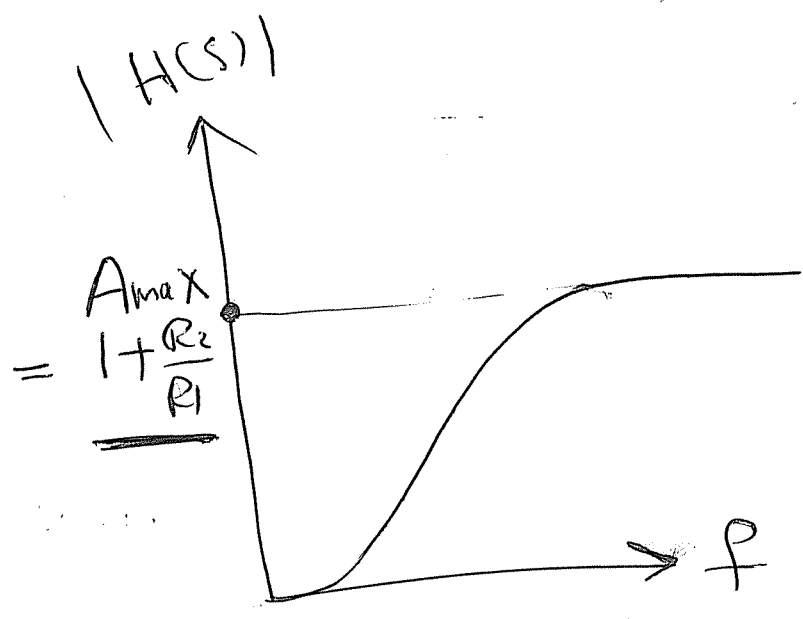

Example: ① Design a HPF to give a gain of 40dB and cutoff freq. of 100kHz.

② sketch Bode Plot of this filter.

$$A(\text{dB}) = 20 \log \left(\frac{V_o}{V_i} \right)$$

$$40 = 20 \log \frac{V_o}{V_i}$$

$$\frac{V_o}{V_i} = 10^{40/20} = 100 \quad \#$$

$$A = 1 + \frac{R_2}{R_1} = 100$$

$$\frac{R_2}{R_1} = 99$$


let $R_1 = \underline{1 \text{ k}\Omega}$, $R_2 = \underline{99 \text{ k}\Omega}$

$$f_c = \frac{1}{2\pi RC} \quad \text{let } C = \underline{1 \text{ nF}}$$


$$R = \frac{1}{2\pi * 10 * 10^{-9} * 10^5} = \frac{10^3}{2\pi}$$
$$\approx 1.7 \text{ k}\Omega$$

varies R up to 10

$\text{k}\Omega$ ← designer

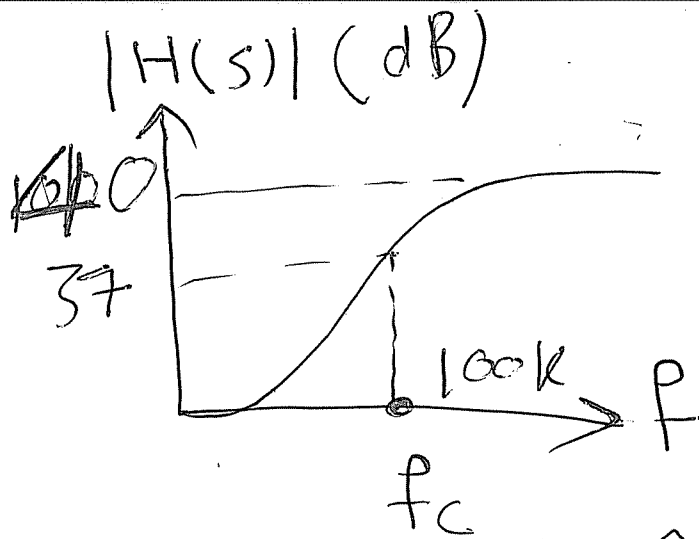

③ Band Pass filter (BPF) :-

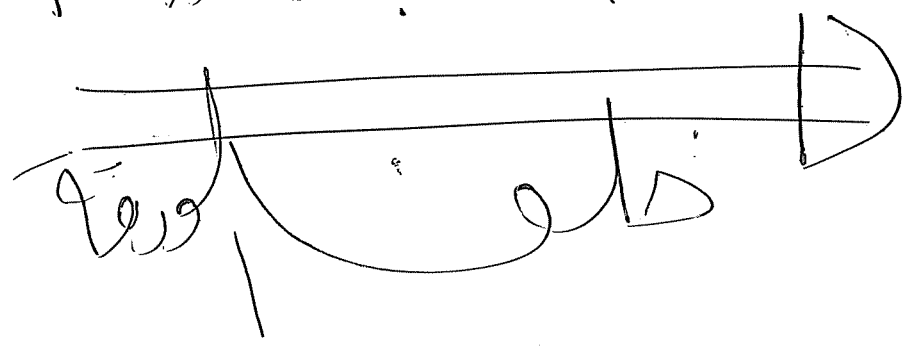

filter order :-

① $\frac{N(s)}{D(s)}$ is $\frac{N(s)}{D(s)}$

Type of filter (LPF, HPF, BPF)

order of filter (C, 1, 2, 3)

$H(s) = \frac{N(s)}{D(s)} = \frac{3}{s+1}$, 1st order LPF

$H(s) = \frac{N(s)}{D(s)} = \frac{s^2}{s^2+s+1}$, 2nd order HPF

$H(s) = \frac{N(s)}{D(s)} = \frac{2s}{s^3+s^2+s+1}$, 3rd order BPF



Legend for N(s):

- constant: LPF (no s)
- s: BPF
- s²: HPF

Legend for D(s):

- 3C
- 7

BPF :-

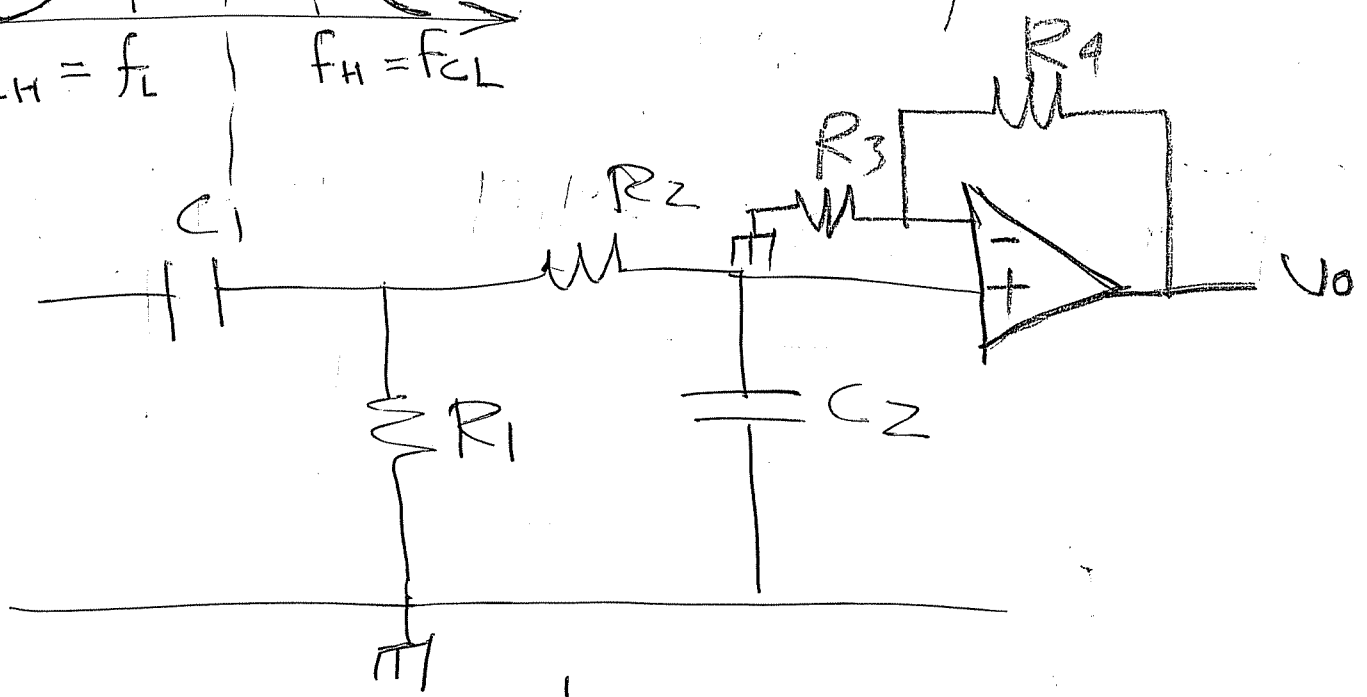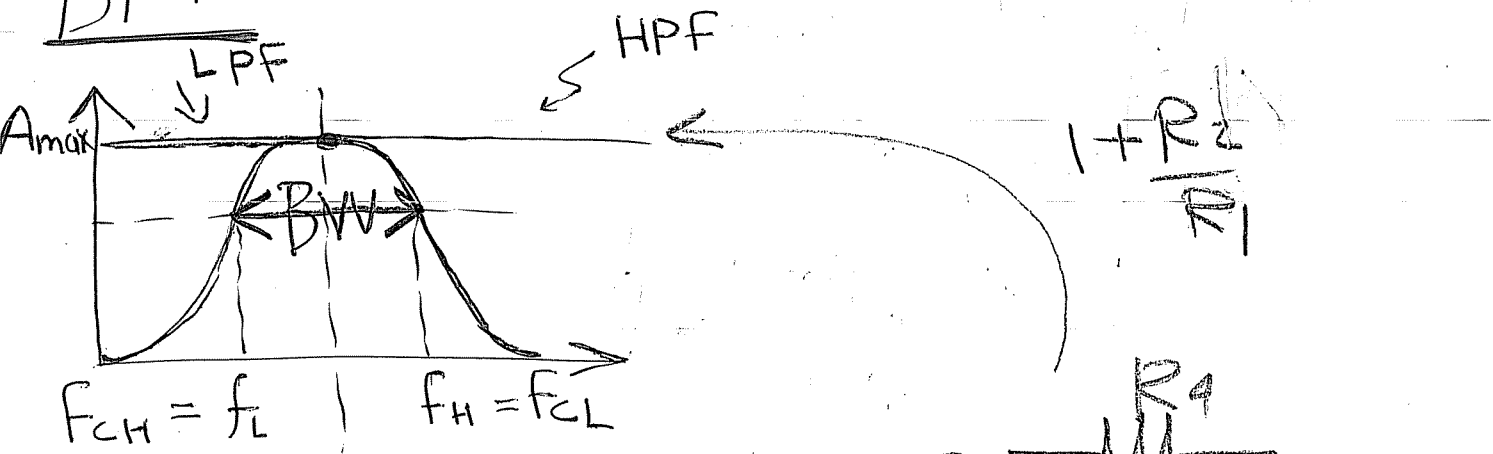


~~Equation~~ $f_{CL} = \frac{1}{2\pi R_2 C_2}$

$f_{CH} = \frac{1}{2\pi R_1 C_1}$


$f_{CL} > f_{CH}$ \leftarrow to obtain band pass filter.
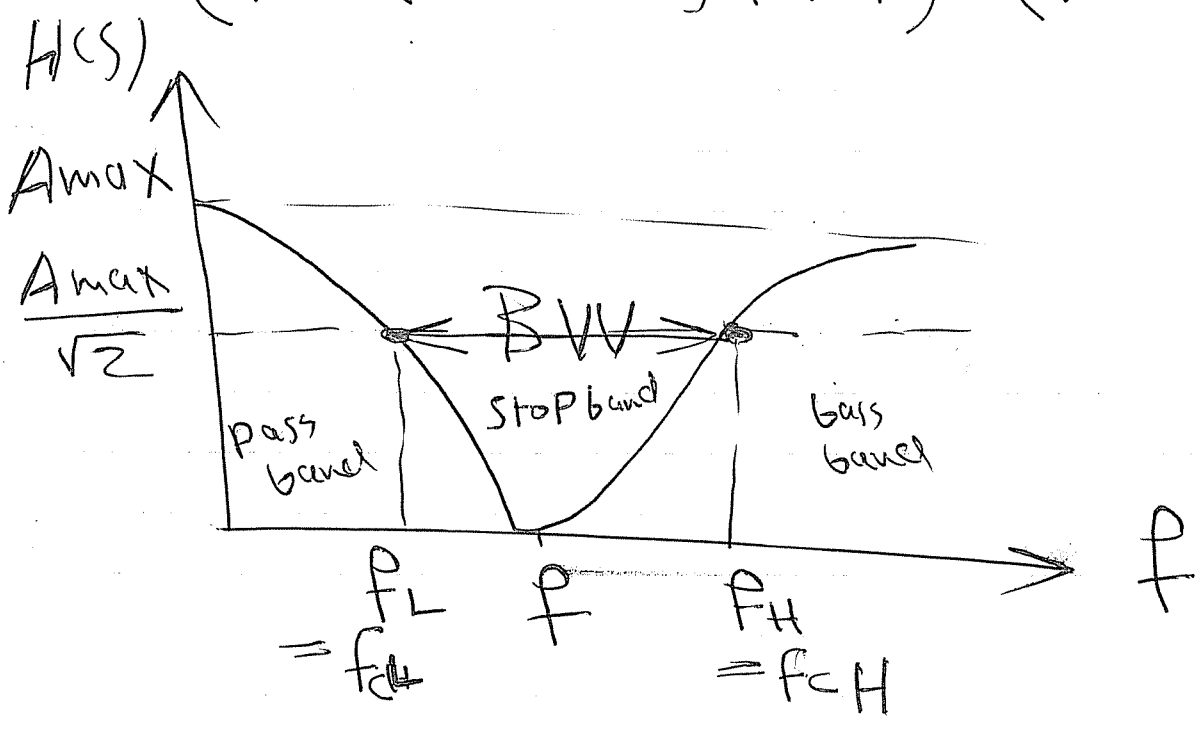
#.

④ Band stop filter :- (BSF)
 (Band Reject) (BRF)
 (notch filter) (NOTCH).



$$f_{CL} < f_{CH}$$

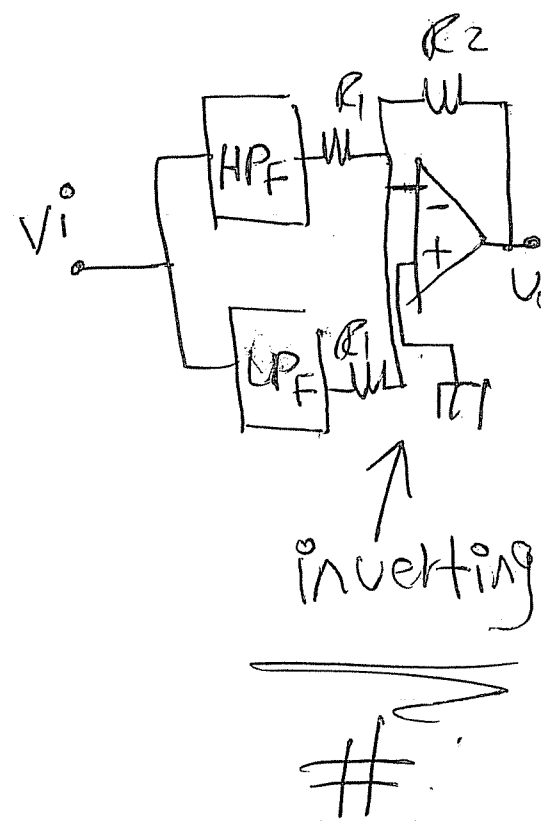


Modulation : Changing Certain Characteristics of Carrier Signal according to amplitude of modulating signal.

FM mod. : Changing freq. Carrier according to Amp. of modulating signal.


PM mod. : Changing the phase of Carrier according to Amp. of modulating signal.

AM :-


$V_c(t) = V_c \sin 2\pi f_c t$

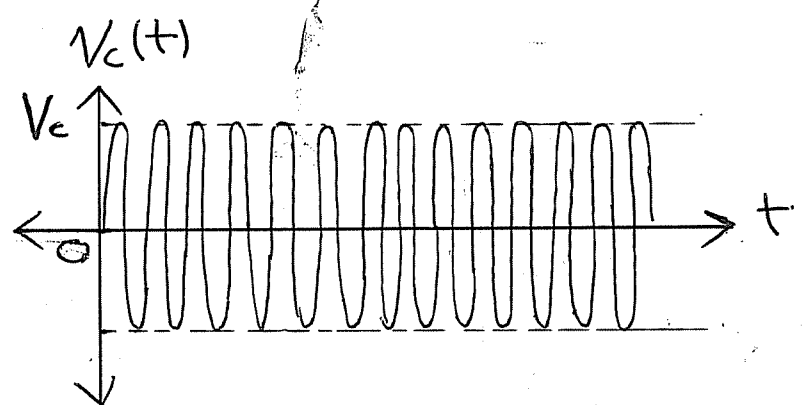

$V_m(t) = V_m \sin 2\pi f_m t$

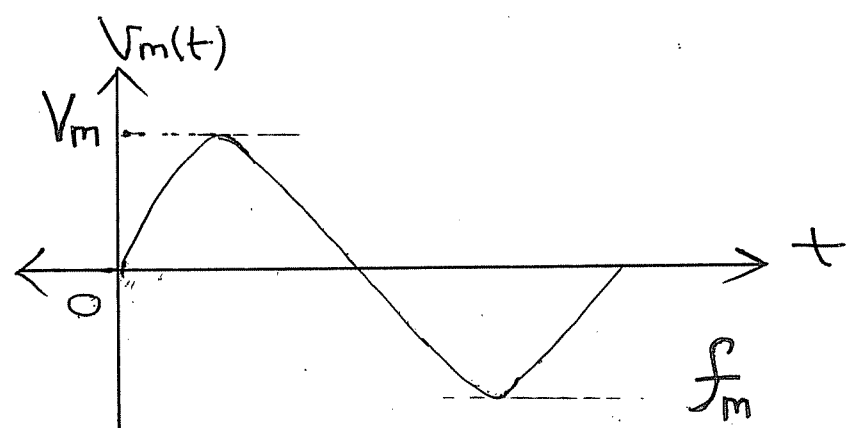

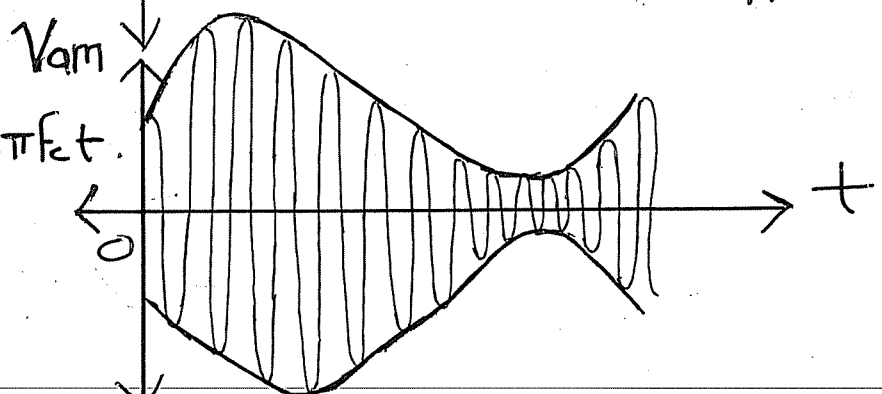$V_{am} = (V_c + V_m \sin 2\pi f_m t) \sin 2\pi f_c t$



$$m = \frac{V_m}{V_c} \longrightarrow V_m = mV_c$$

m : is mod. index.


$$V_{am}(t) = V_c (1 + m \sin 2\pi f_m t) \sin 2\pi f_c t$$

$$V_{am}(t) = 5 (1 + 0.8 \sin 2\pi \times 10^3 t) \sin 2\pi \times 10^6 t$$

$$V_c = 5V, m = 0.8, V_m = 4V, f_m = 10^3 \text{ Hz}, f_c = 10^6 \text{ Hz}$$

In freq. domain:
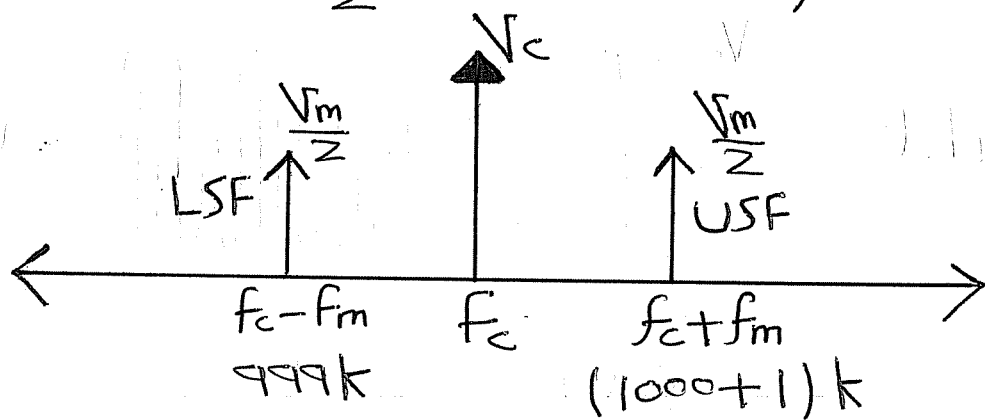
$$V_{am}(f) = V_c \sin 2\pi f_c t + \frac{V_m}{2} \cos(f_c - f_m) - \frac{V_m}{2} \cos(f_c + f_m).$$




When $m=1 \rightarrow V_c = V_m \rightarrow 100\%$ AM modulation.


note: if the modulating signal (V_m) has a single freq. : (Upper side freq., Lower side freq.)

$$\begin{aligned} (BW)_{am} &= USF - LSF = f_c + f_m - (f_c - f_m) \\ &= 2f_m \\ &= 2k \end{aligned}$$


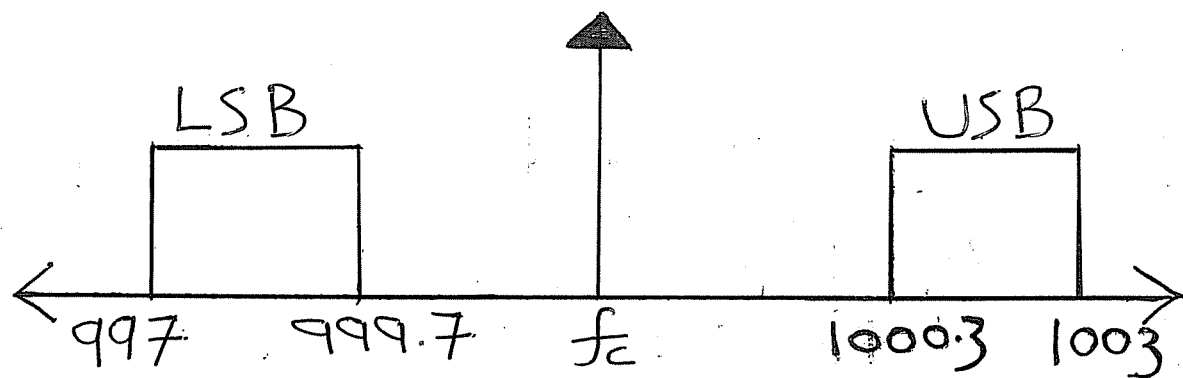
note: if the modulating signal (V_m) has
band $(0.3-3)k$
Voice



f_m : max. freq. of modulating signal.

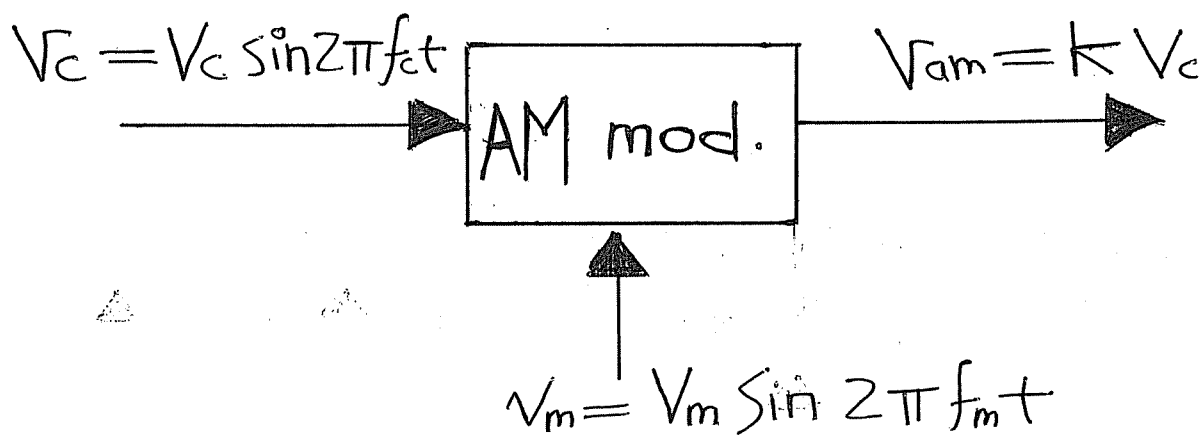

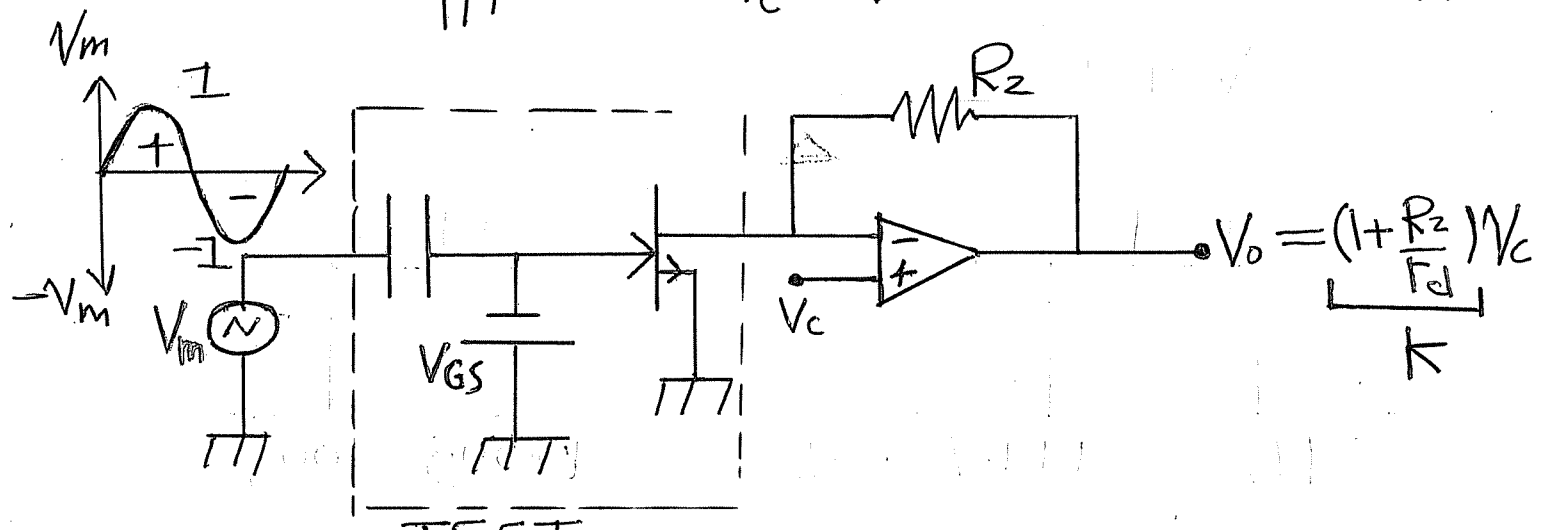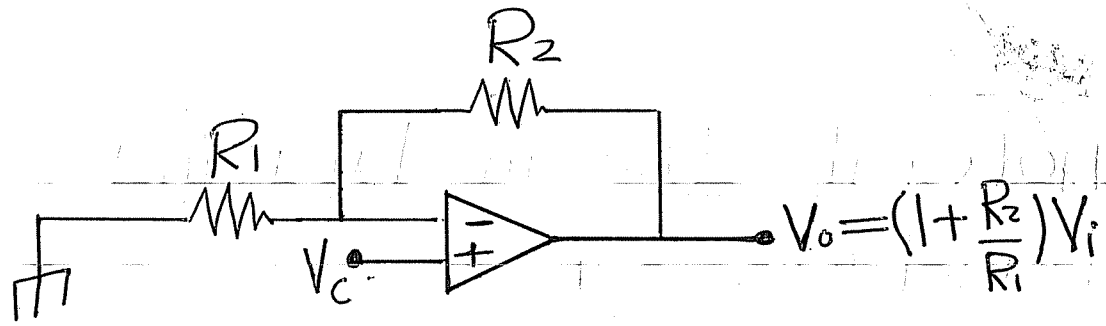k : must be a factor depends on Amp.
of V_m .



JFET
* - نیاز V_{GS} حتی بیشتر


$$r_d = \frac{1}{1 - \frac{V_{GS}}{V_P}}, \quad V_{GS} = V_{GS} + V_{gs}$$

- 1) When V_m increase (During +ve H.C of V_m),
 $V_{GS} = V_{GS}^{DC} + V_{gs}^{AC}$, $r_d \downarrow$, So $K \uparrow$, $V_o \uparrow$,
 i.e Amp. of $V_c \uparrow$.
- 2) When V_m decrease (During -ve H.C),
 $r_d \uparrow$, So $K \downarrow$, $V_o \downarrow$, i.e Amp of $V_c \downarrow$.

In General, the Amp. of Carrier will be \downarrow or \uparrow according to Amp. of mod. signal. This process is AM generation.

AM modulators :-

1) Low level mod. :-

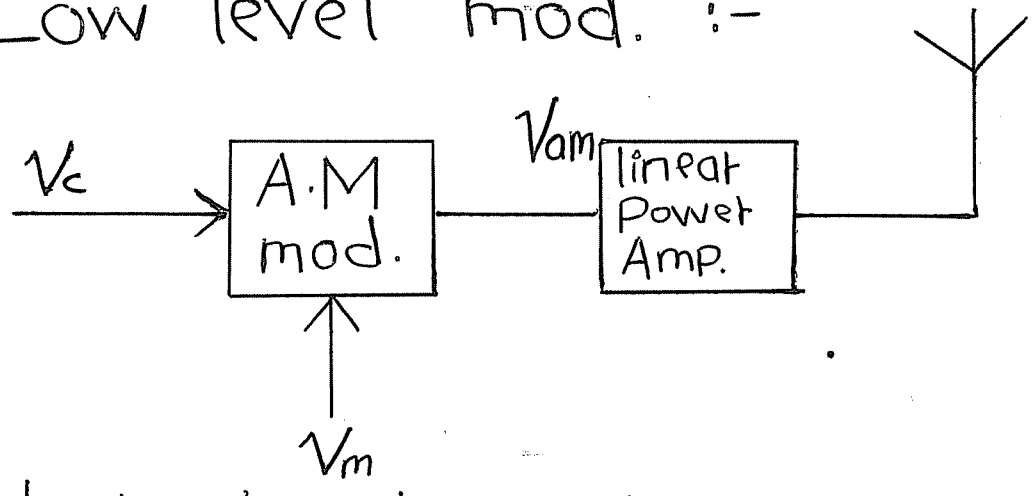


2) High level mod. :-




No Need for linear Power Amp. (The mod is achieved Amp. at Class-C R.F power Amp.).

Low level mod. :-



- 1) Diode Mod.
- 2) Diff. -Amp. mod.
- 3) PIN - Diode Mod.

Diode mod. :-

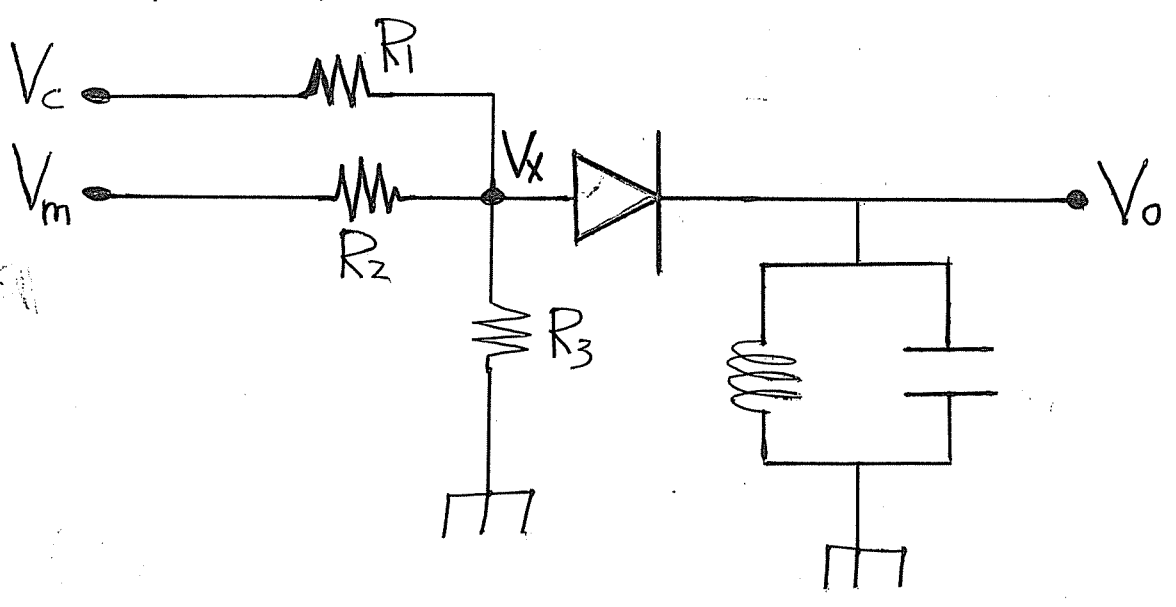

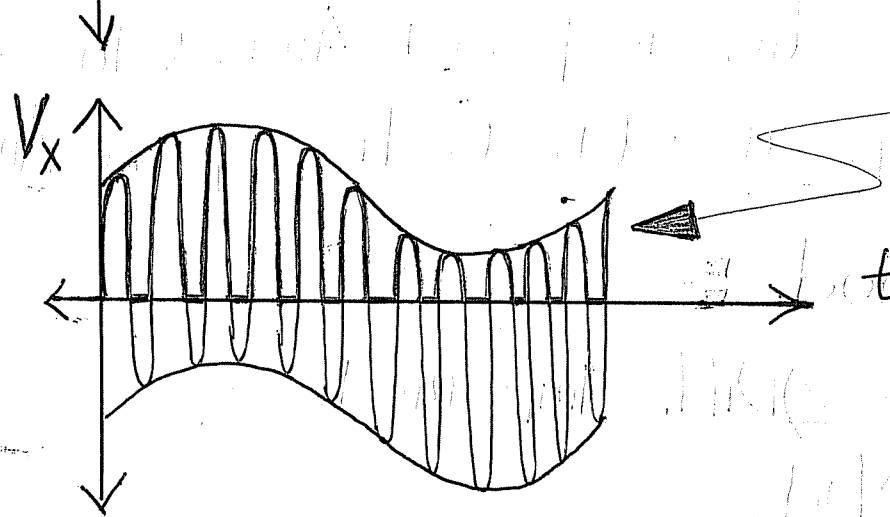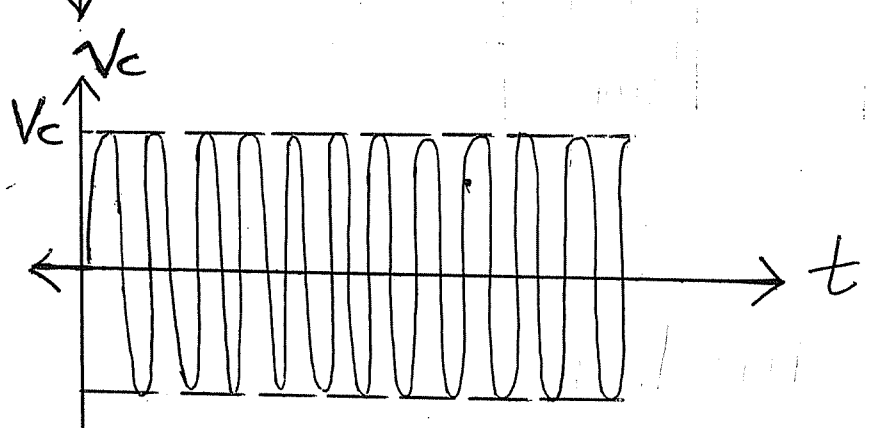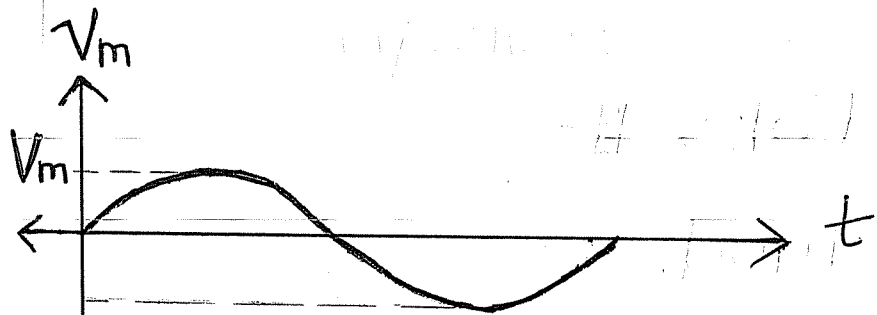

كل شئ فوق
المفرد يتبر.

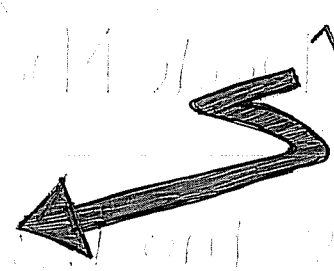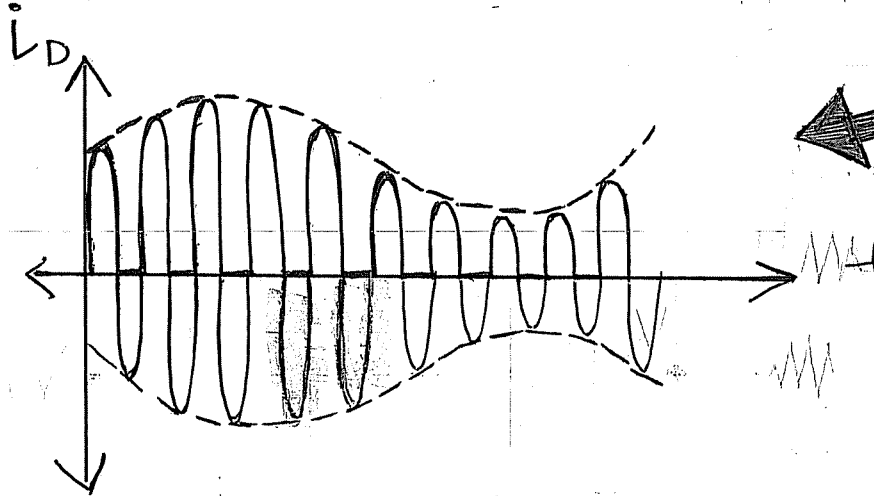

Fly wheel action

إذ حُرَّ تيار بـ Parallel tuned cct. فإنها ستترد عليه بـ V مساوية لها في المقدار وبالعكس الاتجاه.


(كل pulse يرد على pulse)

$$f_r = \frac{1}{2\pi\sqrt{LC}} = f_c$$

$$Q = \frac{f_r}{B.W} \quad \text{selectivity.}$$

$$B.W = \frac{f_r}{Q}$$

Response of LC CCT. :-

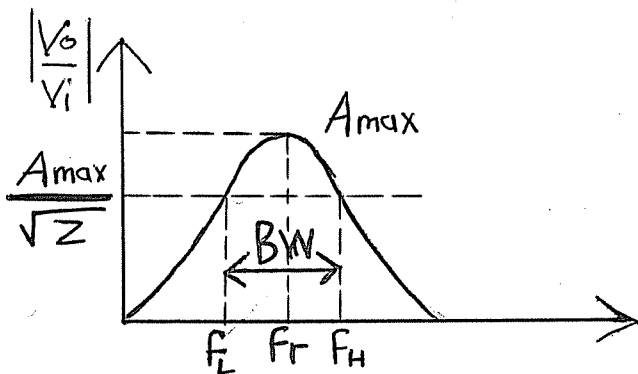

$$Q = \frac{f_r}{B.W}$$

$$B.W = \frac{f_r}{Q} \rightarrow$$

بجیت تشمل، lower و upper

نقار Q بجین (BW > 2fm)

1) The Composite signal $V_x = V_c + V_m$ will be applied to diode, i_D will be a Half-Cycle pulse which excited the tuned CCT.

- 2) Due to fly wheel effect in LC CCT. each pulse of i_D will produce a -ve pulse of amplitude proportional to Amp. of i_D .
- 3) The O/P will be an AM Signal.
- 4) The tuned CCT. must be designed such that $f_r = f_c$ and a selectivity $Q = \frac{f_r}{B.W}$ such that $B.W \geq B.W$ of AM signal ($2f_m$).

← هذه الدارة لا تعطى (gain) [diodes لا يعطي gain].

* in generation of AM using Diode mod.:

المسؤول عن -ve cycle

Parallel tuned CCT.


وخاصية fly wheel effect

• $I_E = \frac{V - V_{BE}}{R_E}$... من الرسمة الأصلية

+ve H.C :

$$I_E = \frac{V_m + V - V_{BE}}{R_E}$$

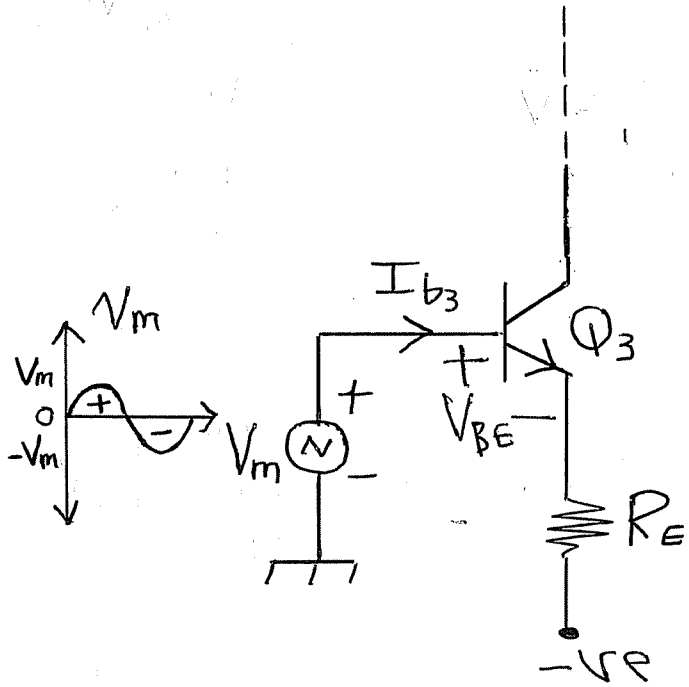$I_E \uparrow$, $A \uparrow$, $V_o \uparrow$.




-ve H.C :

$$I_E = \frac{V - V_m - V_{BE}}{R_E}$$


$I_E \downarrow$, $A \downarrow$, $V_o \downarrow$.

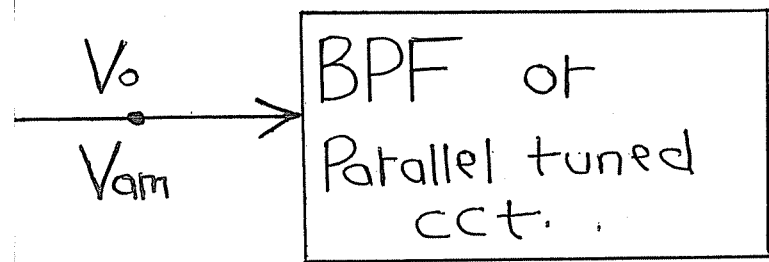- 1) When V_m increase , I_E increase , A increase , V_o increase . (Amp. of Carrier \uparrow).
- 2) When V_m decrease , I_E decrease , A decrease , V_o decrease . (Amp. of Carrier \downarrow).

i.e : Amp. of Carrier will increase and decrease according to Amp. of modulating signal . i.e AM signal is generated.



Response for BPF, PTC :-

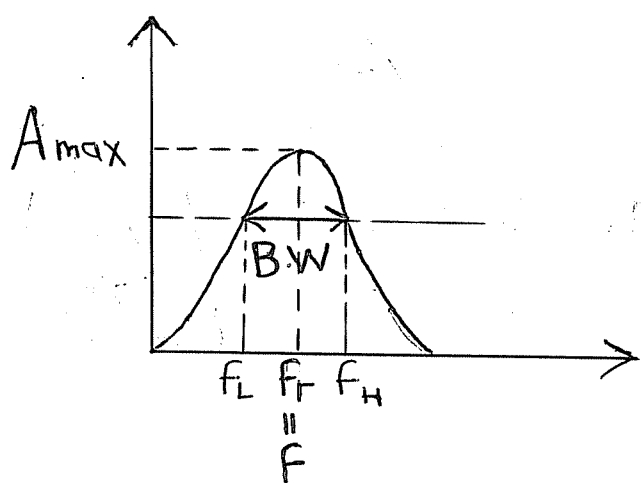

$$Q = \frac{f_r}{\text{B.W.}} = \frac{f_{\text{center}}}{\text{B.W.}}$$

PTC
BPF

$$\text{B.W.} = \frac{f_r}{Q} \geq (\text{B.W.})_{\text{am}}$$


→ To be sure that V_{am} contain USB and LSB and f_c then either a parallel LC cct. is used or BPF, and designed such that :

$$f_r = f_c \text{ (LC cct.)}$$

$$f_{\text{cen}} = f_c \text{ (BPF)}$$

and Q such that :
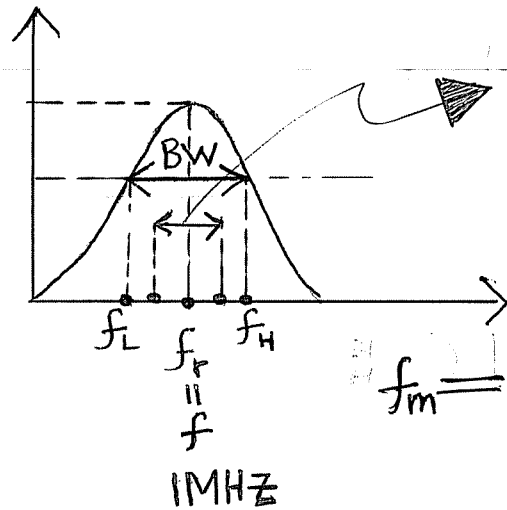
$$\frac{f_c}{Q} \geq (\text{BW})_{\text{am}}$$




$$f_c < (BW)_{am}$$

$$O/P < BW$$

$$f_m = 1 \text{ kHz}$$

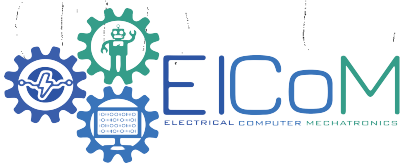distortion of Sig.:
band cutting / band
Limitting







3] PIN-Diode mod. :-

PIN diode : a special diode used at microwave freq. > 100 MHz.

It works as a resistance in F.w biasing,

$$r_f \propto \frac{1}{I_D}$$

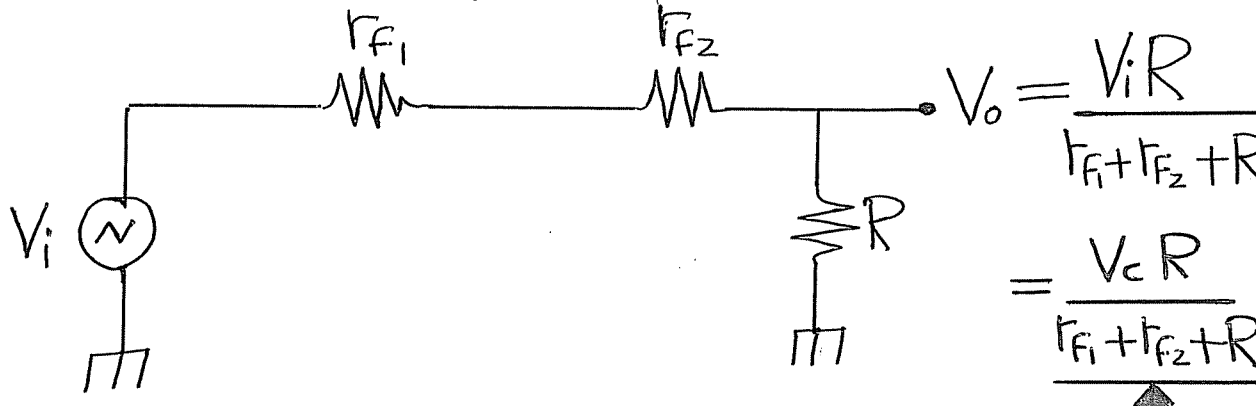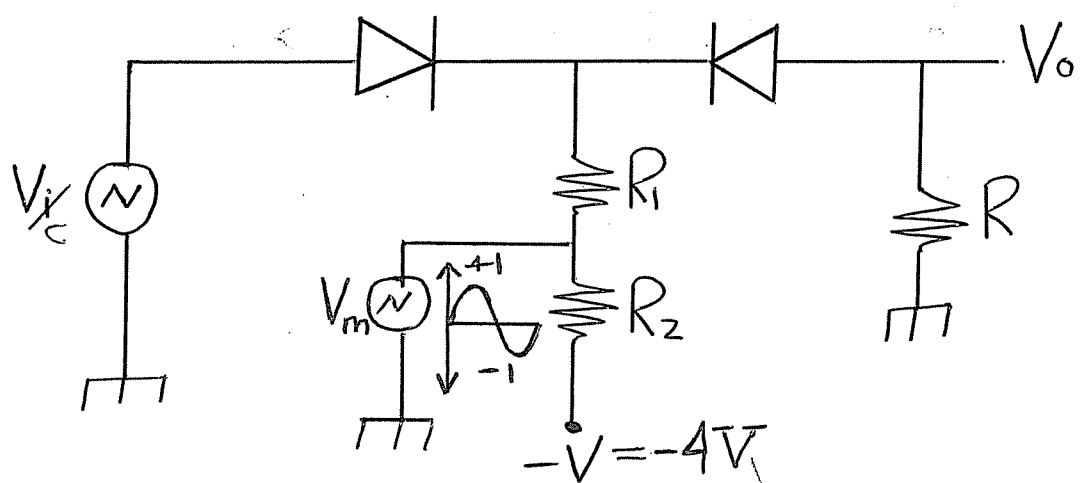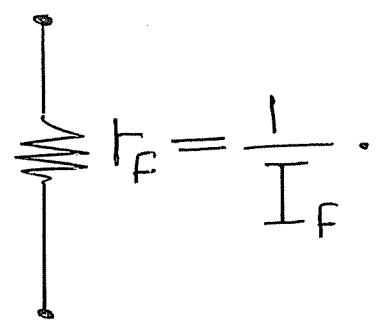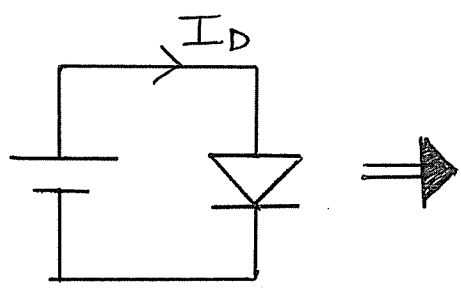

$$V_o = \frac{V_i R}{r_{F1} + r_{F2} + R}$$


$$= \frac{V_c R}{r_{F1} + r_{F2} + R}$$

↑
without modulating signal

This modulator works based ON using PIN diode as variable resistance.

- 1) When V_m increase , $I_D \downarrow$, $r_f \uparrow$, and $V_o \downarrow$.
 - 2) When V_m decrease , $I_D \uparrow$, $r_f \downarrow$, and $V_o \uparrow$.
- i.e V_o increase and decrease according to modulating signal.

note

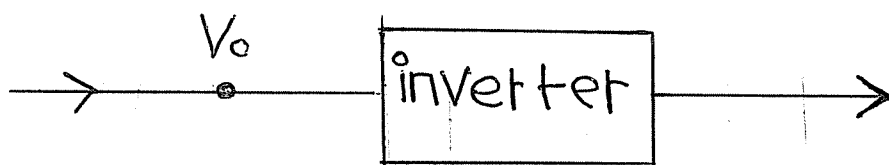

* متن صحیح :

$V_m \uparrow$, $V_o \uparrow$


و


• $V_m \downarrow$, $V_o \downarrow$

High level - AM mod. :-

The mod. is achieved in final Class-C R.F Power Amp. So no need for linear Power Amp. to amplify the AM signal.

Class-C

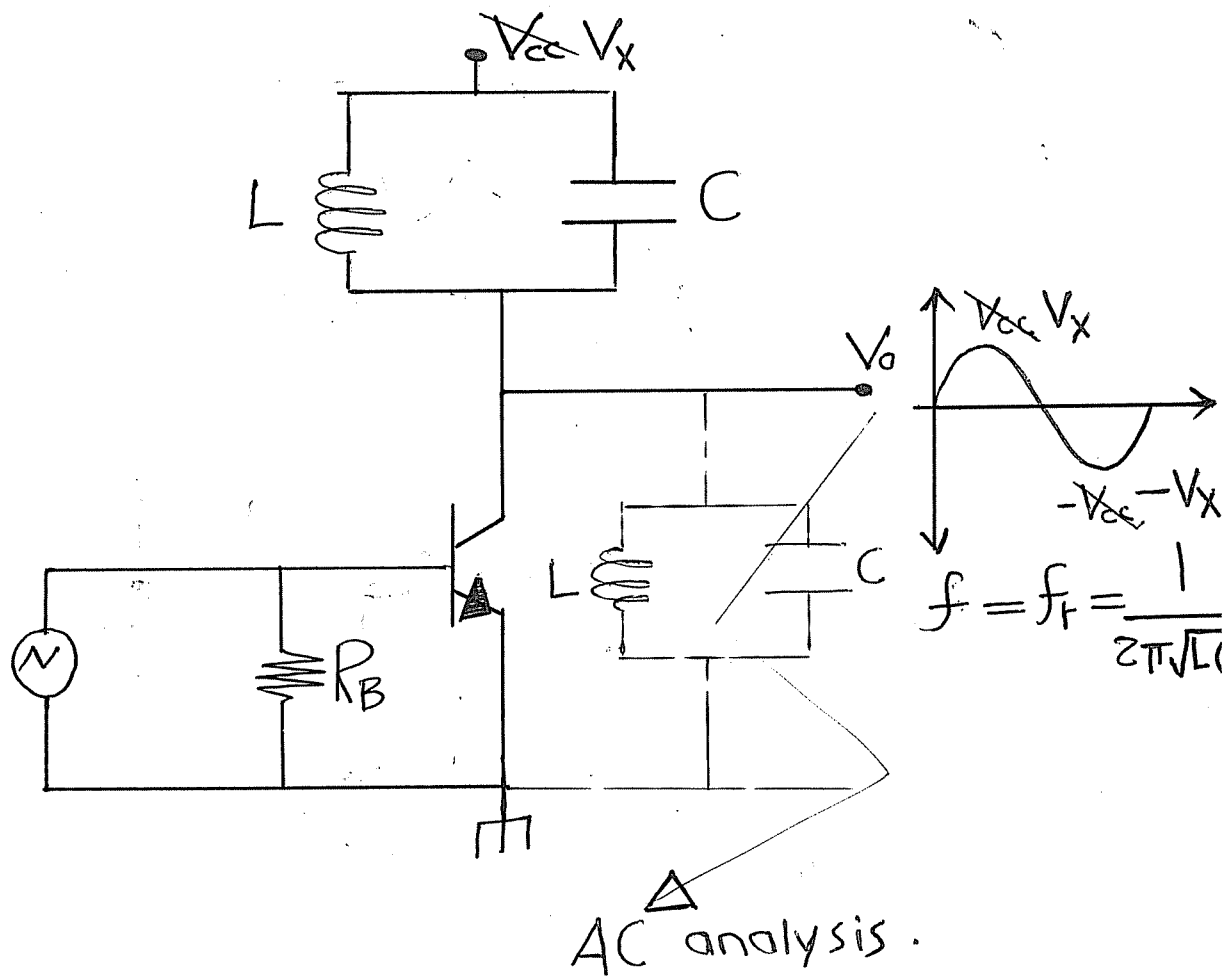

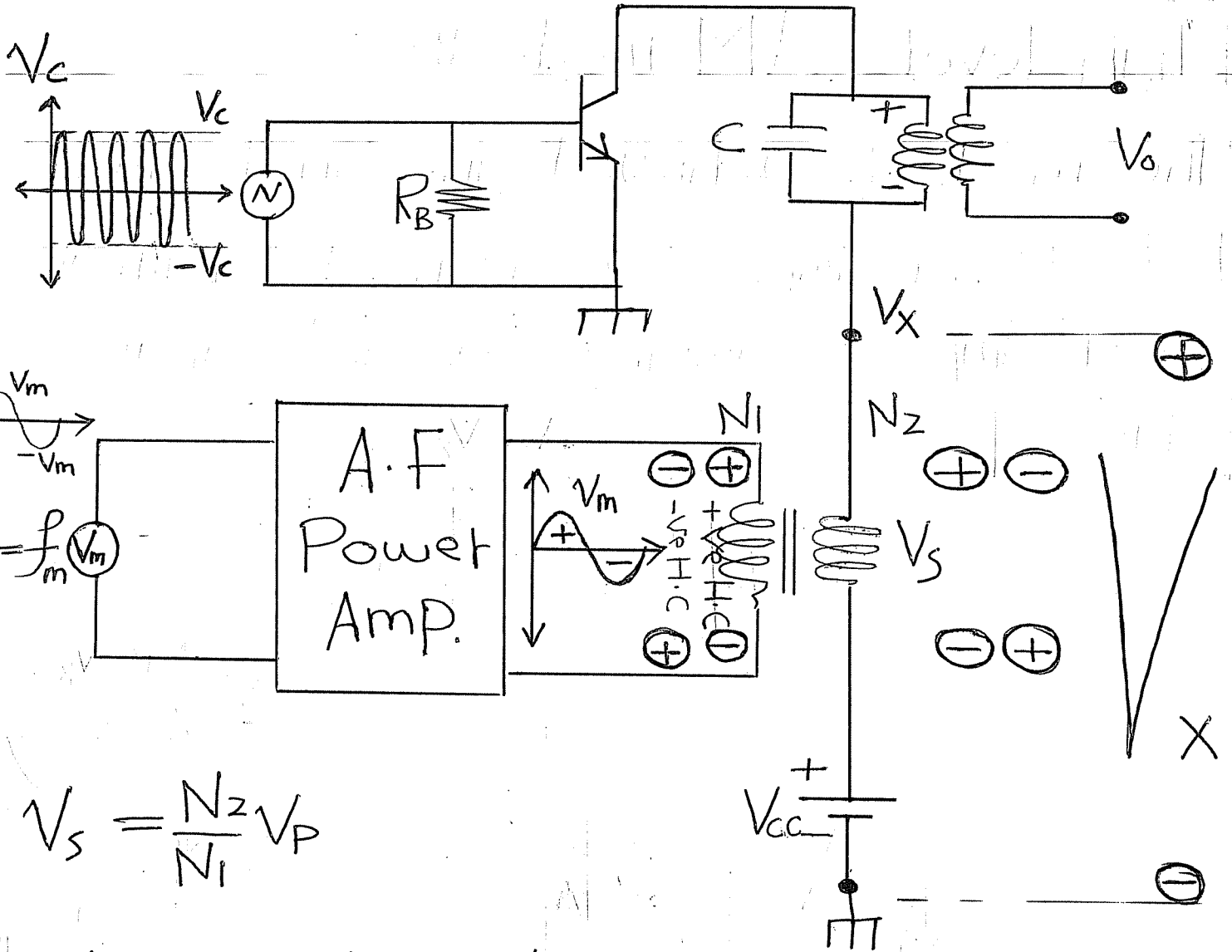


$$V_s = \frac{N_2}{N_1} V_p$$

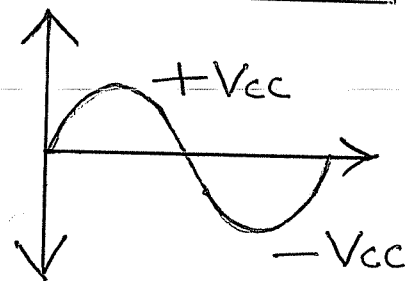1) without V_m ; $V_p = 0 \rightarrow V_s = 0$

$$-V_{cc} - V_s + V_x = 0$$

for $V_m = 0$; $V_s = 0$:- $V_x = V_{cc}$



$$f = f_r = \frac{1}{2\pi\sqrt{LC}}$$

2) During +ve H.C of V_m :


$$-V_{cc} - V_s + V_x = 0$$

$$V_x = V_{cc} + V_s$$

$$V_s = \frac{N_2}{N_1} V_m, \quad \text{for } \frac{N_2}{N_1} = 1 : V_s = V_m$$

∴ $V_x = V_{cc} + V_m$, $V_o \uparrow$, $V_m \uparrow$

تعداد بزرگتره

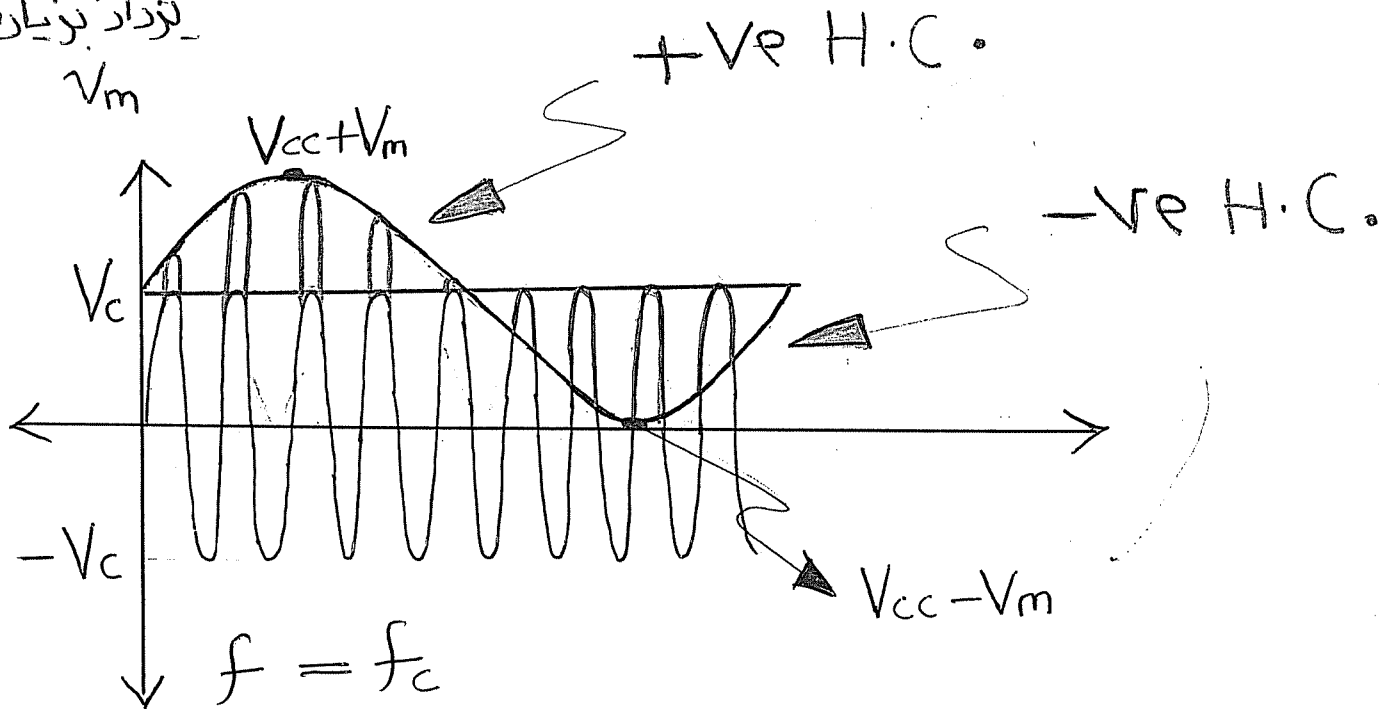

3) During -ve H.C of V_m ,

$$-V_{cc} + V_s + V_x = 0$$


$$V_x = V_{cc} - V_s$$

$$V_s = \frac{N_2}{N_1} V_m, \quad \frac{N_2}{N_1} = 1 : V_s = V_m$$

∴ $V_x = V_{cc} - V_m$, $V_o \downarrow$, $V_m \downarrow$


تعداد بزرگتره

V_m

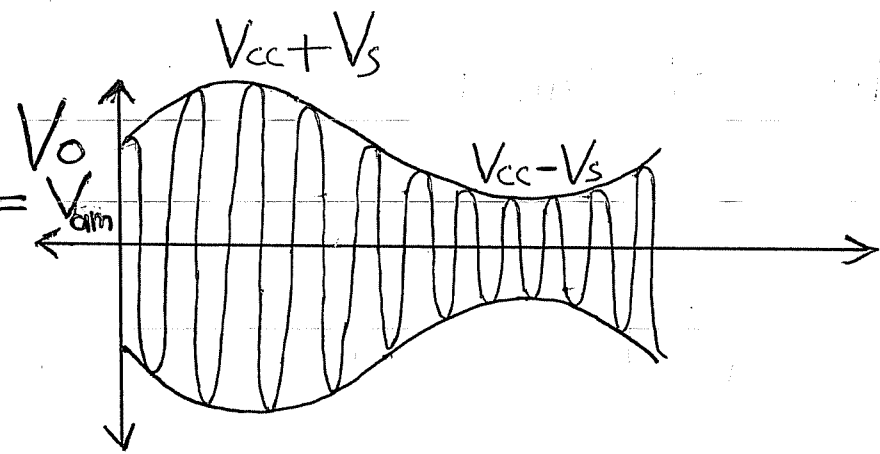


Where $V_s = \frac{N_2}{N_1} V_m$, for $\frac{N_2}{N_1} = 1$:

$$V_s = V_m$$

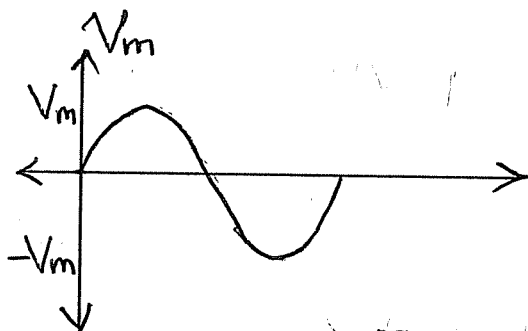

for 100% mod :- $V_s = V_m = V_{cc}$

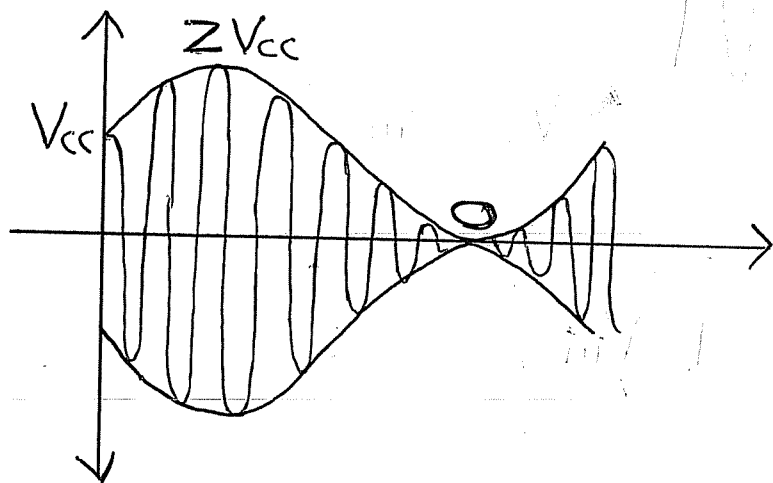


$V_m = 2V$, $V_{cc} = 10$, mod 100%, $\frac{N_2}{N_1} = 1$

$$V_{cc} = V_s$$

$$V_s = \frac{N_2}{N_1} V_m \rightarrow \frac{N_2}{N_1} = \frac{10}{2} = 5 \quad \#$$

AM Receiver Circuits :-

Super heterodyne Rec. Cct.s :-

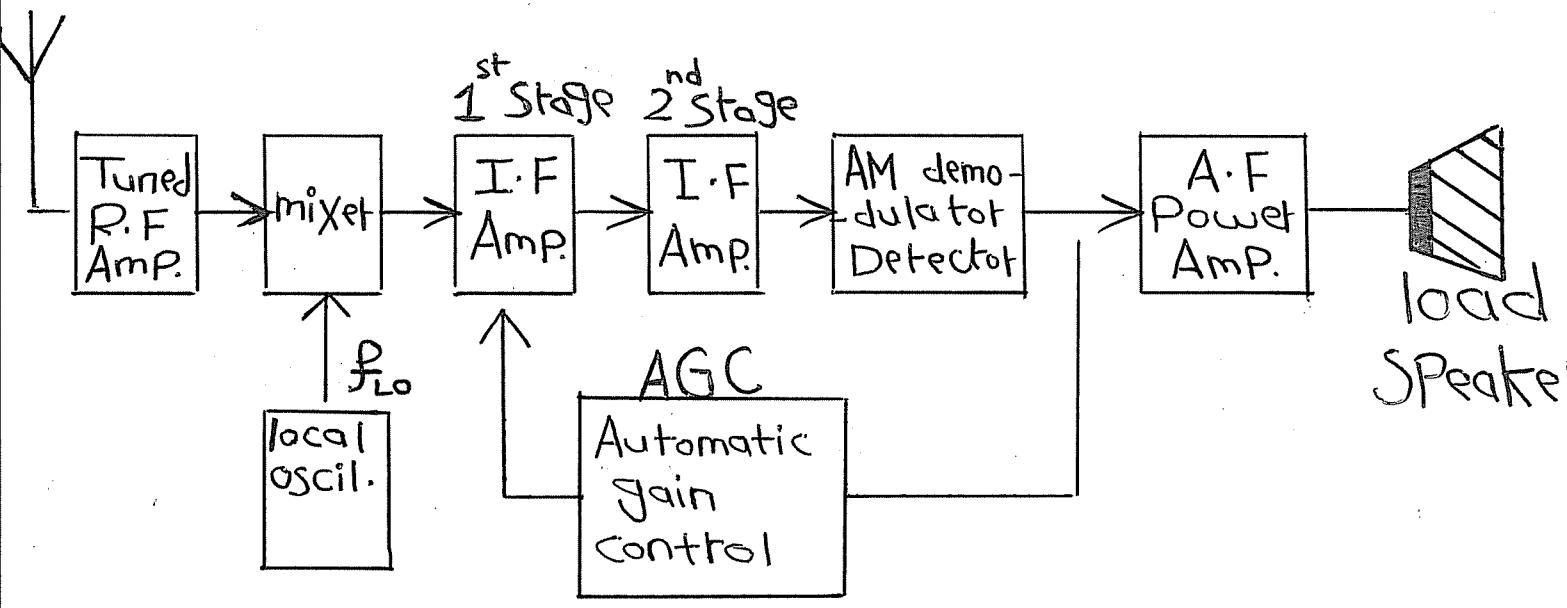

Two important factors in R_x :-

=(Receiver Parameters)=

1) Selectivity : ability of Receiver to select a certain freq. among different frequencies.

depends on selectivity of Tuned R.F. Amp. and I.F. (mainly from T.R.F. Amp.)


. T.R.F. : $\text{جدا بالدرجة الأولى}$
Amp.

2) Sensitivity : The minimum power level for the input signal which can be processed by the Rx.


• gain of the Receiver
 gain = 200
 gain = 100
 $P_{in} \downarrow$

depends on I.F and T.R.F amp. gain (mainly in I.F Amp.).

T.R.F Amp.

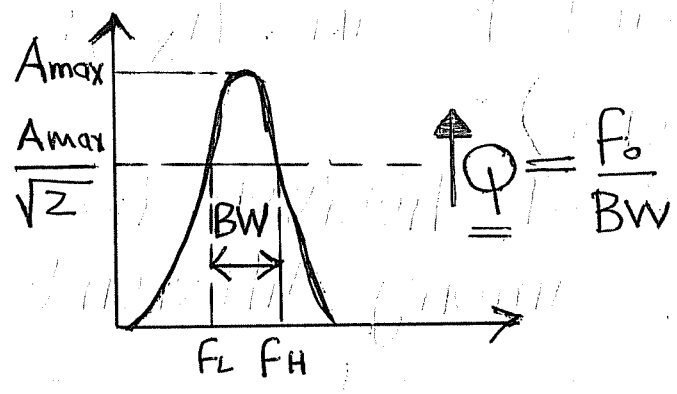


I.F Amp.

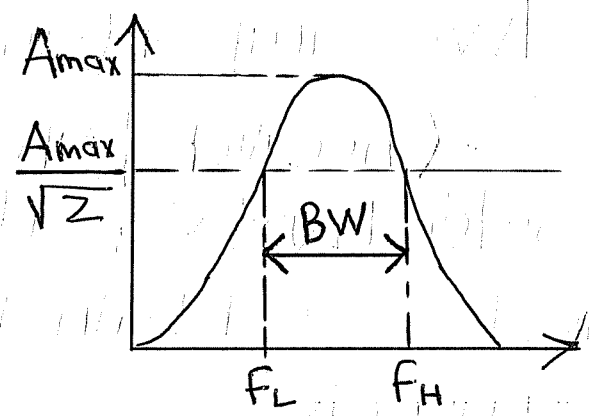

Tuned R.F Amp. :


- 1) Determine and improve R_x Selectivity.
- 2) prevent Reradiation of Lo. Signal (Leak through).

$V_{BE} = 0.6V$
 $\beta = 100$

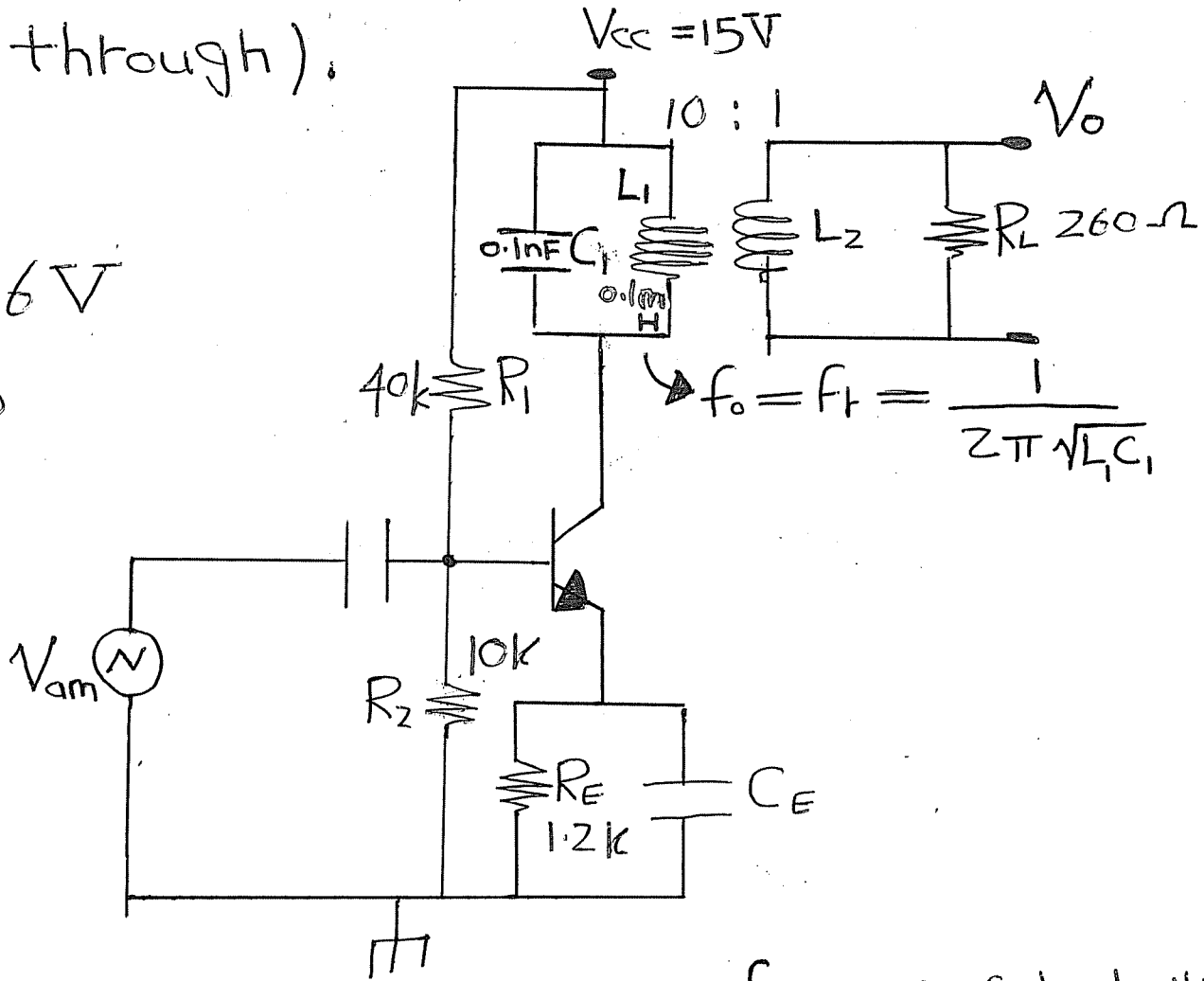

* $Q = \frac{f_0}{B.W}$, is Selectivity

* $f_0 = \frac{1}{2\pi\sqrt{L_1 C_1}}$

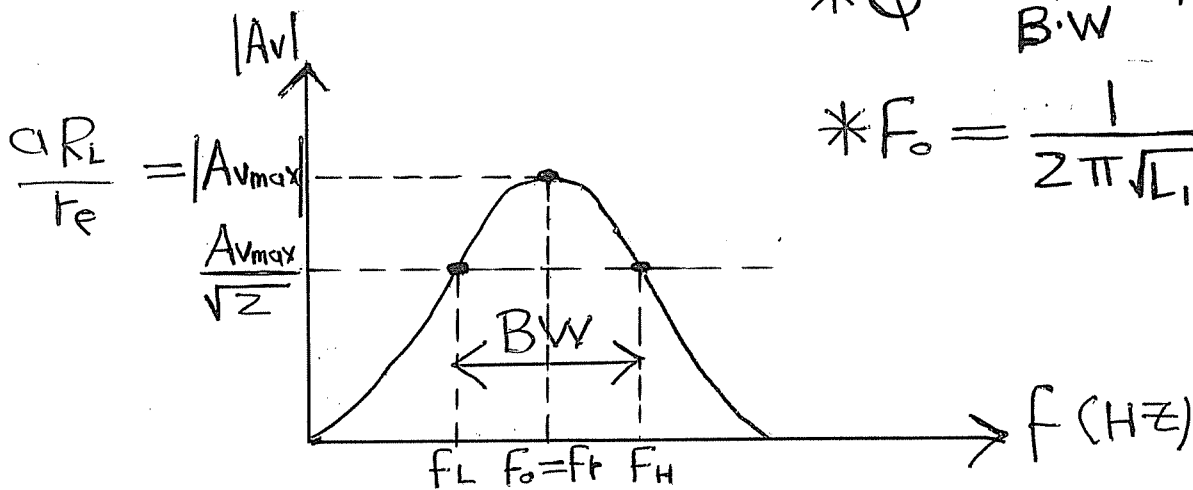

freq. Response.

For the design:

$$1) f_0 = f_r = f_c = \frac{1}{2\pi\sqrt{L_1 C_1}}$$


2) The Selectivity Q must be Chosen Such that $B.W = \frac{f_0}{Q}$, must include USB and LSB of the AM signal, to avoid bandwidth cutting which causes distortion in AM signal.

$$Q = \omega_0 \bar{R}_L C \quad \text{or} \quad Q = \frac{\bar{R}_L}{\omega_0 L}$$


note:- in General, at Resonance:

$$\begin{aligned} \rightarrow Q &= \omega_0 RC \\ &= \frac{\omega R}{\omega_0 L} \end{aligned}$$

$$\rightarrow Q = \frac{\omega_0 L}{R}$$

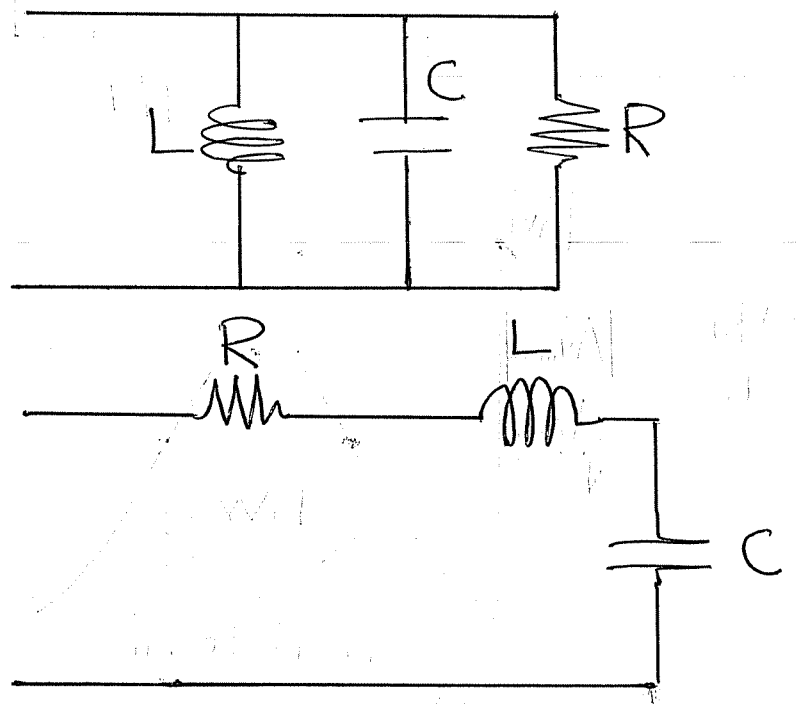

At Resonance :

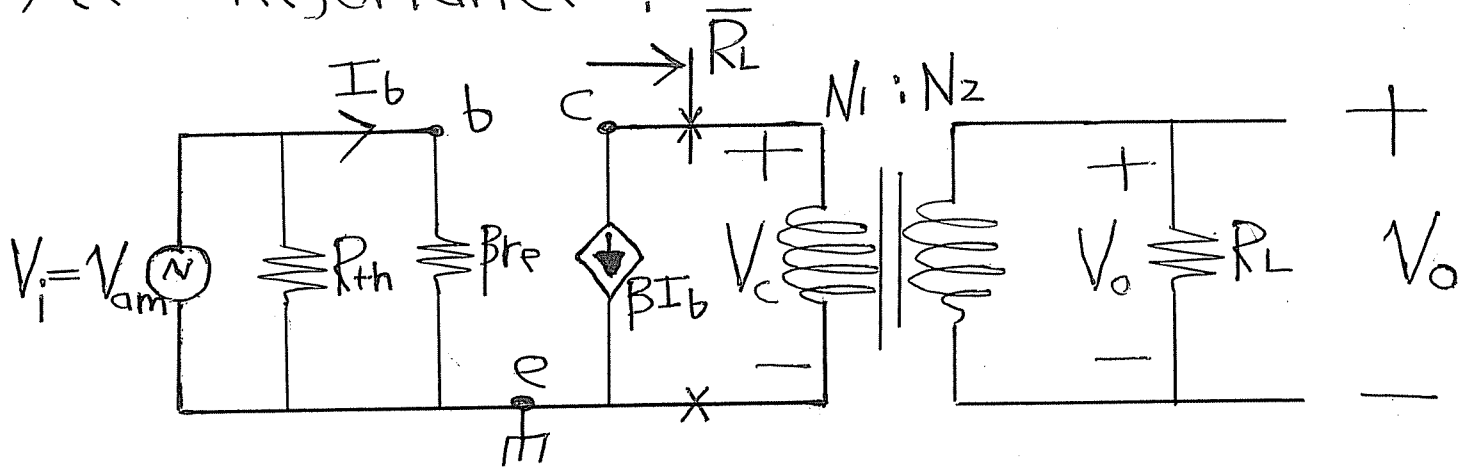

$$A_v = \frac{V_o}{V_i} = \frac{V_c}{V_i} * \frac{V_o}{V_c}$$

$$V_c = -\beta I_b \bar{R}_L, \quad \bar{R}_L = a^2 R_L, \quad a = \frac{N_1}{N_2}$$

\bar{R}_L : AC reflected impedance.

$$\frac{V_c}{V_i} = \frac{-\beta I_b \bar{R}_L}{I_b \cdot \beta r_e} = -\frac{\bar{R}_L}{r_e} = \frac{-a^2 \cdot R_L}{r_e}$$

$$r_e = \frac{V_T}{I_E}, \quad V_T = 26 \text{ mV}$$

$$\frac{V_o}{V_c} = \frac{N_2}{N_1} = \frac{1}{a} \rightarrow A_v = \frac{\bar{R}_L}{r_e} \cdot \frac{1}{a}$$

$$\therefore A_v = \frac{-a R_L}{r_e}$$

$$f_o = f_c = \frac{1}{2\pi \sqrt{L_1 C_1}}, \quad Q = \omega_o \bar{R}_L C$$

Example: ① Calculate $|A_{V_{max}}|$, f_0 , B.W.?

② Sketch freq. Resp.?

③ Can This T.R.F. Process an amod signal of max. freq. of 10 kHz?

Solution:


$$① |A_{V_{max}}| = \frac{\alpha R_L}{r_e}, \quad r_e = \frac{V_T}{I_E}$$

$I_E \rightarrow$ D.C analysis:

$$V_B = \frac{15 * 10}{50} = 3V$$

$$V_E = V_B - V_{BE} = 3 - 0.6 = 2.4V$$
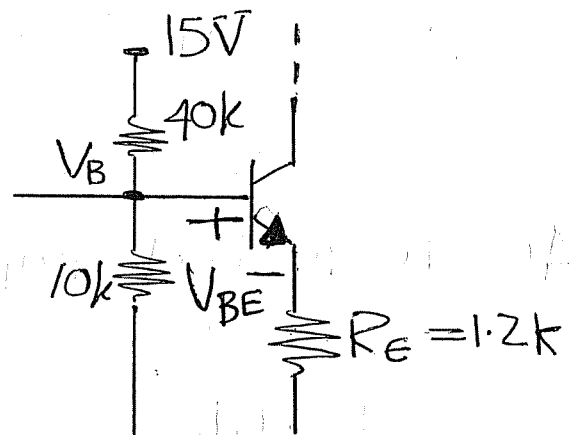
$$I_E = \frac{V_E}{R_E} = \frac{2.4V}{1.2k} = 2mA$$



$$r_e = \frac{26mV}{2mA} = 13\Omega$$

$$\rightarrow |A_{V_{max}}| = \frac{10 * 260}{13} = 200$$

$$f_0 = \frac{1}{2\pi \sqrt{L_1 C_1}} = \frac{1}{2\pi \sqrt{10^{-4} * 10^{-10}}} = \frac{10^7}{2\pi} = 1.6 \text{ MHz}$$

$$\varphi = \omega_0 \bar{R}_L C$$

$$\bar{R}_L = a^2 * R_L = 100 * 260 = 26 \text{ k}\Omega$$


$$\begin{aligned} \rightarrow \varphi &= 2\pi * 10^6 * 1.6 * 26 * 10^3 * 0.1 * 10^{-9} \\ &= 26.13 \end{aligned}$$

$$B.W = \frac{f_0}{\varphi} = \frac{1.6 * 10^6}{26.13} = 61.2 \text{ k}$$

②

$$f_L = f_0 - \frac{B.W}{2} = 1.6 * 10^6 - \frac{61.2 * 10^3}{2} \cong 1.57 \text{ MHz}$$
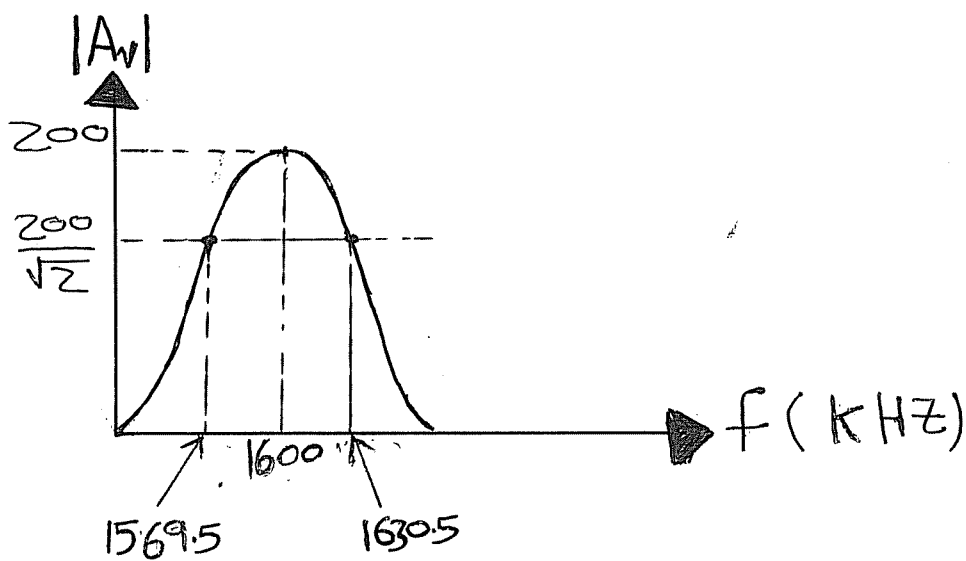
$$f_H = f_0 + \frac{B.W}{2} = 1.6 * 10^6 + \frac{61.2 * 10^3}{2} \cong 1.63 \text{ MHz}$$



$$\textcircled{3} \quad 1600 \text{ k} + 10 \text{ k} = 1610 \text{ k} < 1630.5$$


$$1600 \text{ k} - 10 \text{ k} = 1590 \text{ k} > 1569.5$$

\therefore Yes ... T.R.F Can process a mod. Signal of max. freq. 10 kHz.

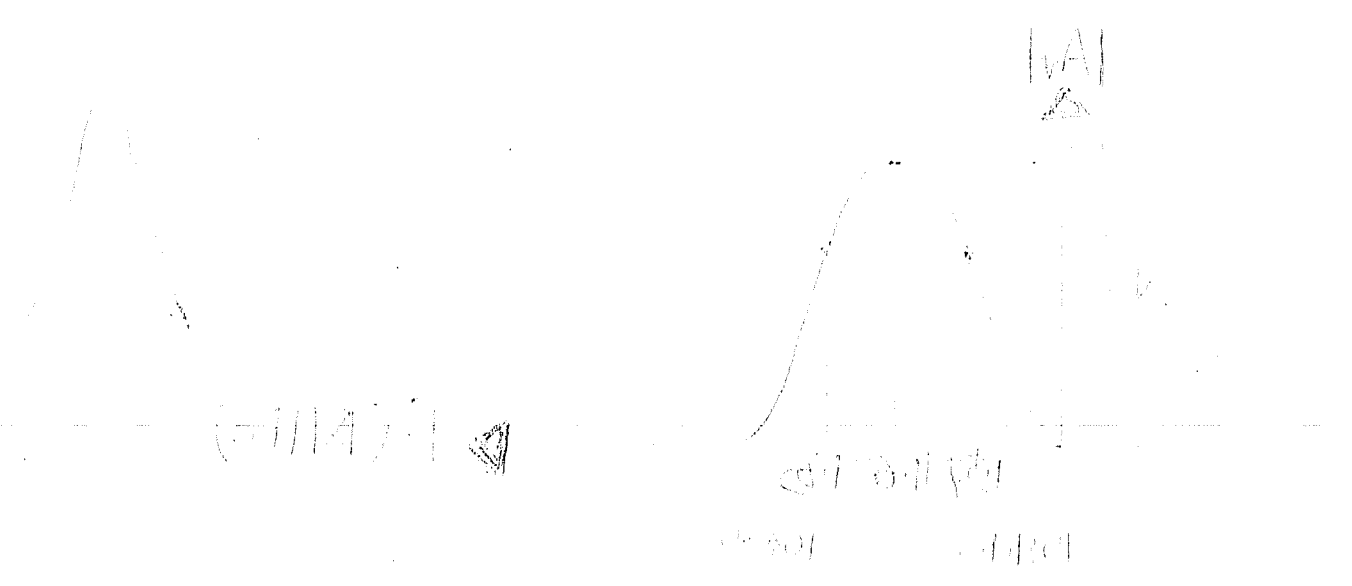1.1.1


Let X_1, X_2, \dots, X_n be independent and identically distributed random variables with probability density function $f(x)$ and cumulative distribution function $F(x)$. The joint probability density function of (X_1, X_2, \dots, X_n) is given by $f(x_1, x_2, \dots, x_n) = \prod_{i=1}^n f(x_i)$.

Let X_1, X_2, \dots, X_n be independent and identically distributed random variables with probability density function $f(x)$ and cumulative distribution function $F(x)$. The joint probability density function of (X_1, X_2, \dots, X_n) is given by $f(x_1, x_2, \dots, x_n) = \prod_{i=1}^n f(x_i)$.



(a) Let X_1, X_2, \dots, X_n be independent and identically distributed random variables with probability density function $f(x)$ and cumulative distribution function $F(x)$. The joint probability density function of (X_1, X_2, \dots, X_n) is given by $f(x_1, x_2, \dots, x_n) = \prod_{i=1}^n f(x_i)$.

Mixer

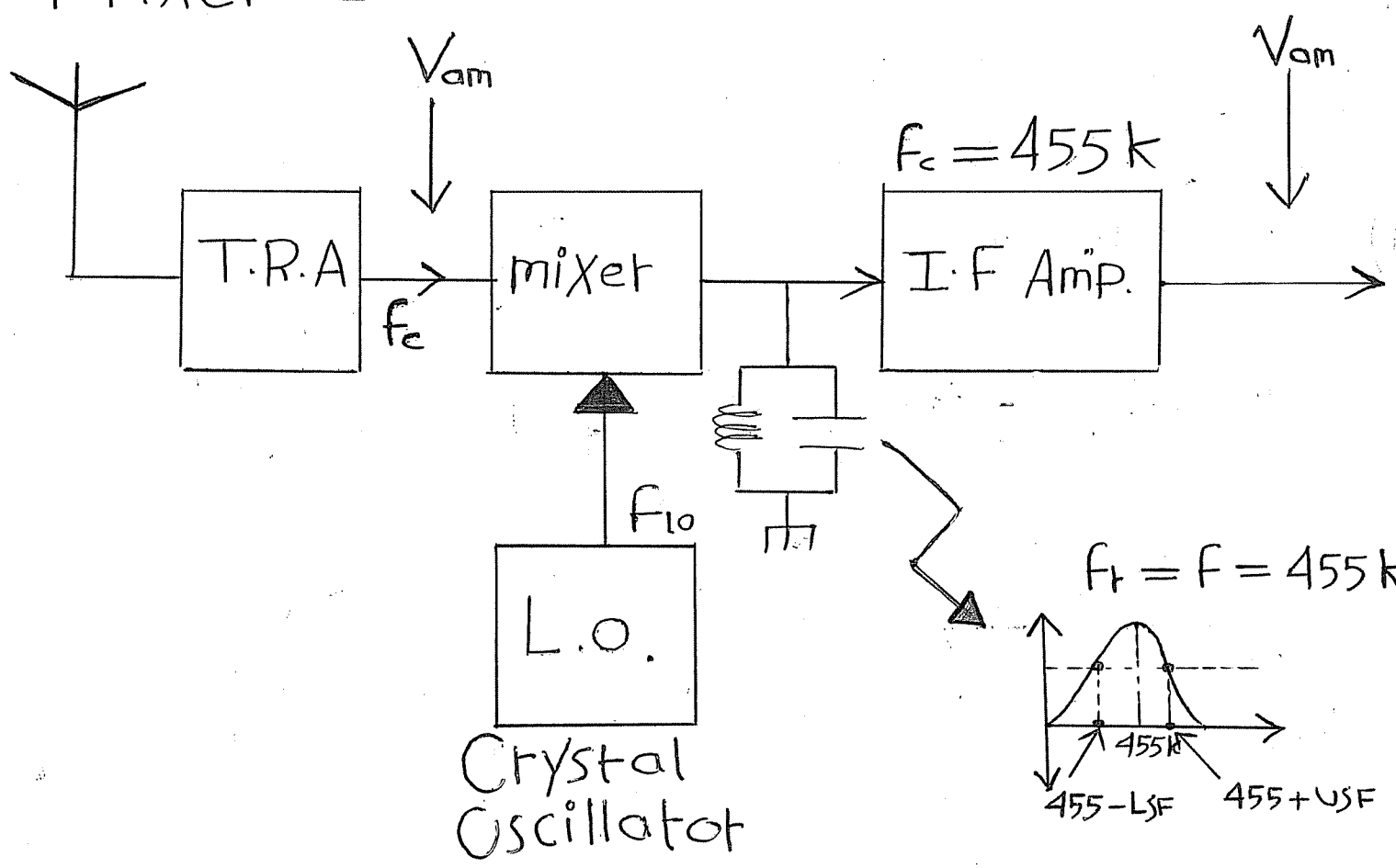

down freq. Converter → كلما قلنا الفreq أكثر كلما كنا قادرين على زيادة R_x gain.

mixer → non linear cct. (diode/BJT/MOSFET).

$$V_i = A \sin 2\pi f_1 t \rightarrow V_o = k V_i^2$$

$$V_2 = B \sin 2\pi f_2 t$$

$$V_o = k (V_1 + V_2)^2$$

$$= k (A \sin 2\pi f_1 t + B \sin 2\pi f_2 t)^2$$

$$= k [A^2 \sin^2 2\pi f_1 t + 2AB \sin 2\pi f_1 t \sin 2\pi f_2 t + B^2 \sin^2 2\pi f_2 t]$$


if $V_o = k e \rightarrow$ infinite # of frequencies. (many harmonics)

$f_1, f_2, 2f_1, 2f_2, f_1 - f_2, f_1 + f_2$

Mixer : is non-linear CCT. used for freq. Conversion. (Mixing \rightarrow multiplication process).

* The following devices can be used as mixer:


1) Diode mixer :-

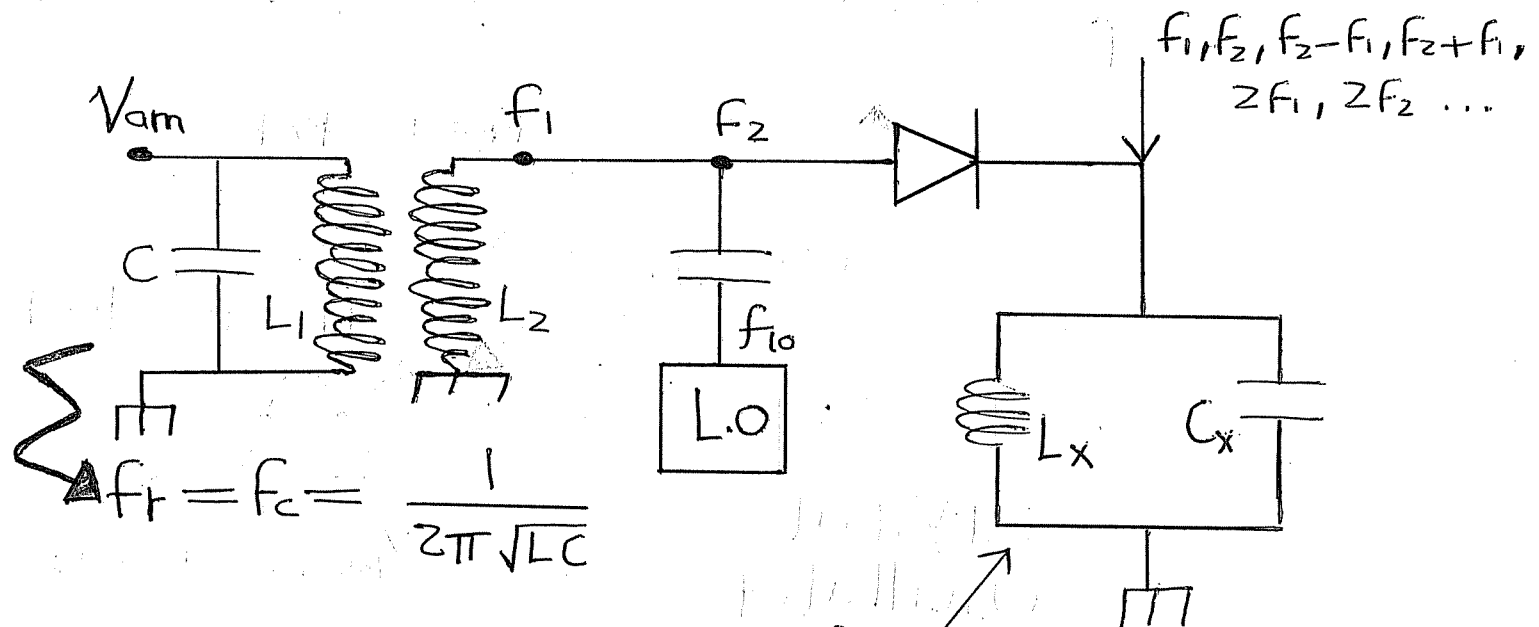

نقارہ بیٹ ٹکڑی Sig. تردد کا
 $f_{IF} = \frac{1}{2\pi\sqrt{L_x C_x}}$


Noisy, No gain, Exponential device.

2) BJT mixer :-

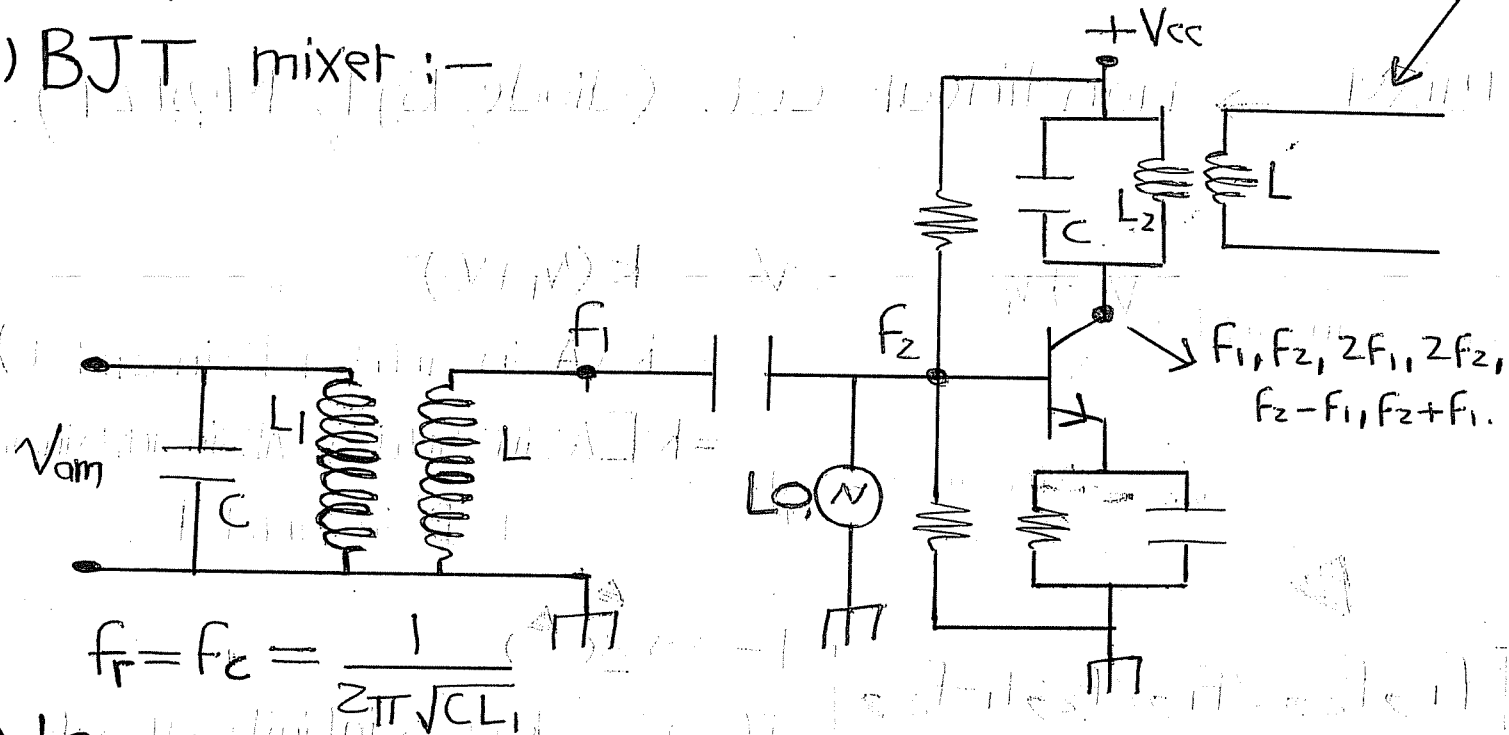

Noisy, Gain, Exponential device.

3) FET Mixer :

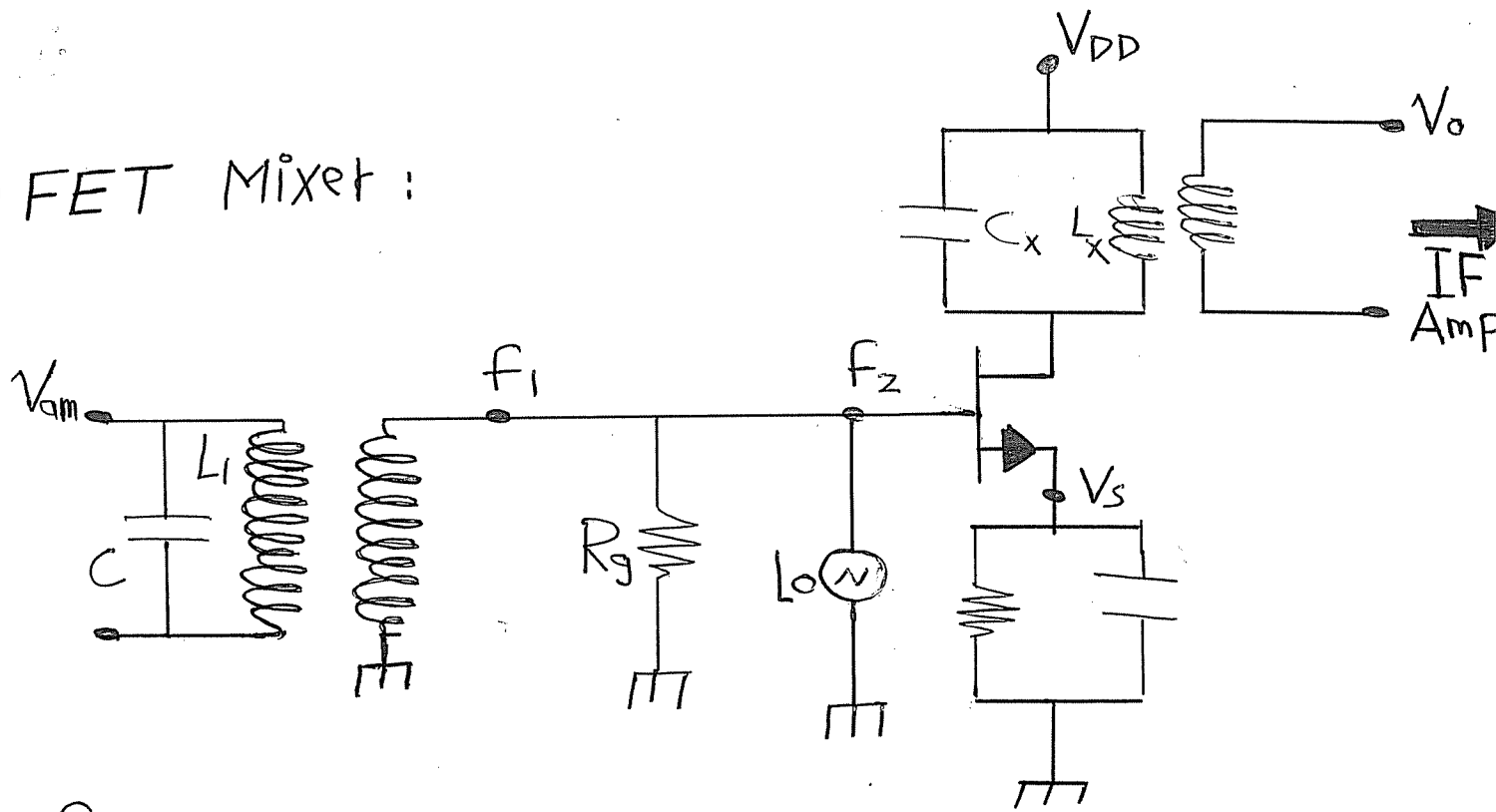

1. Gain.
2. No Noise.
3. maximum Freq. is Second harmonic.
(Square Law device).

• يمكن استبدال الـ LC-CCT بـ BPF


Note:

$$f_{IF} = f_{LO} - f_s = f_s - f_{LO}$$

for high-Side injection : $f_{IF} = f_{LO} - f_s$
 $f_{LO} > f_s$

for low-Side injection : $f_{IF} = f_s - f_{LO}$
 $f_s > f_{LO}$

IF Amp.

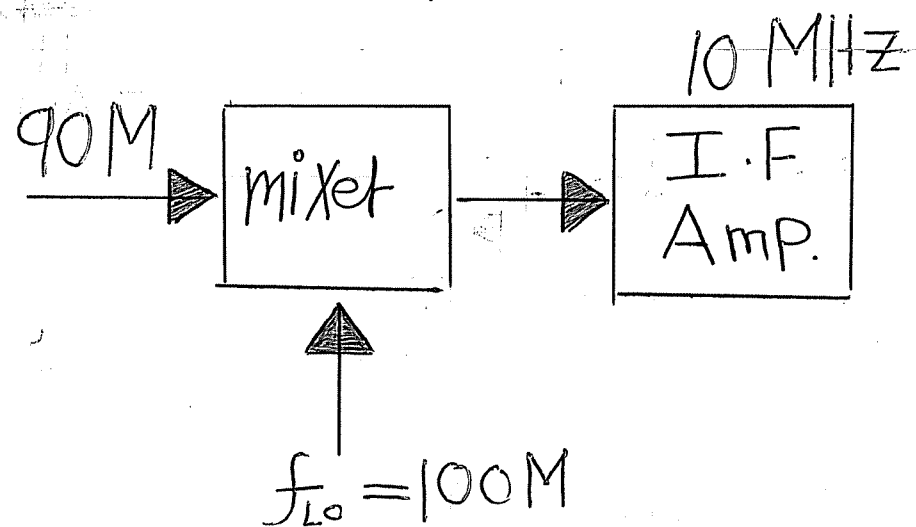


$$f_{\text{image}} = f_s + 2f_{\text{IF}}$$

mixer لا يميز بين 90M و 110M $\underbrace{\text{image}}$ مما يؤدي إلى

• حدوث interference بين الإشارات

نتخلص من ال image بزيادة ال f_{IF} :

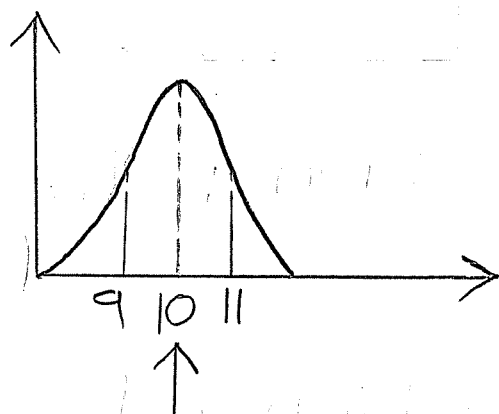

$$Q = \frac{f_0}{\text{B.W.}}$$

$$= \frac{10}{2} = 5 \checkmark$$

* لو اخترنا 50M


B.W. image خارج ال

* The Bulk size of R_x gain is achieved in I.F. Amp.

* In I.F. design, we have to Compromise between high and Stable (Which requires low I.F), and good image rejection (Which requires high I.F).


For AM, 455 kHz was Chosen to give the required gain and image rejection.

For FM, 10.7 MHz was Chosen for I.F.

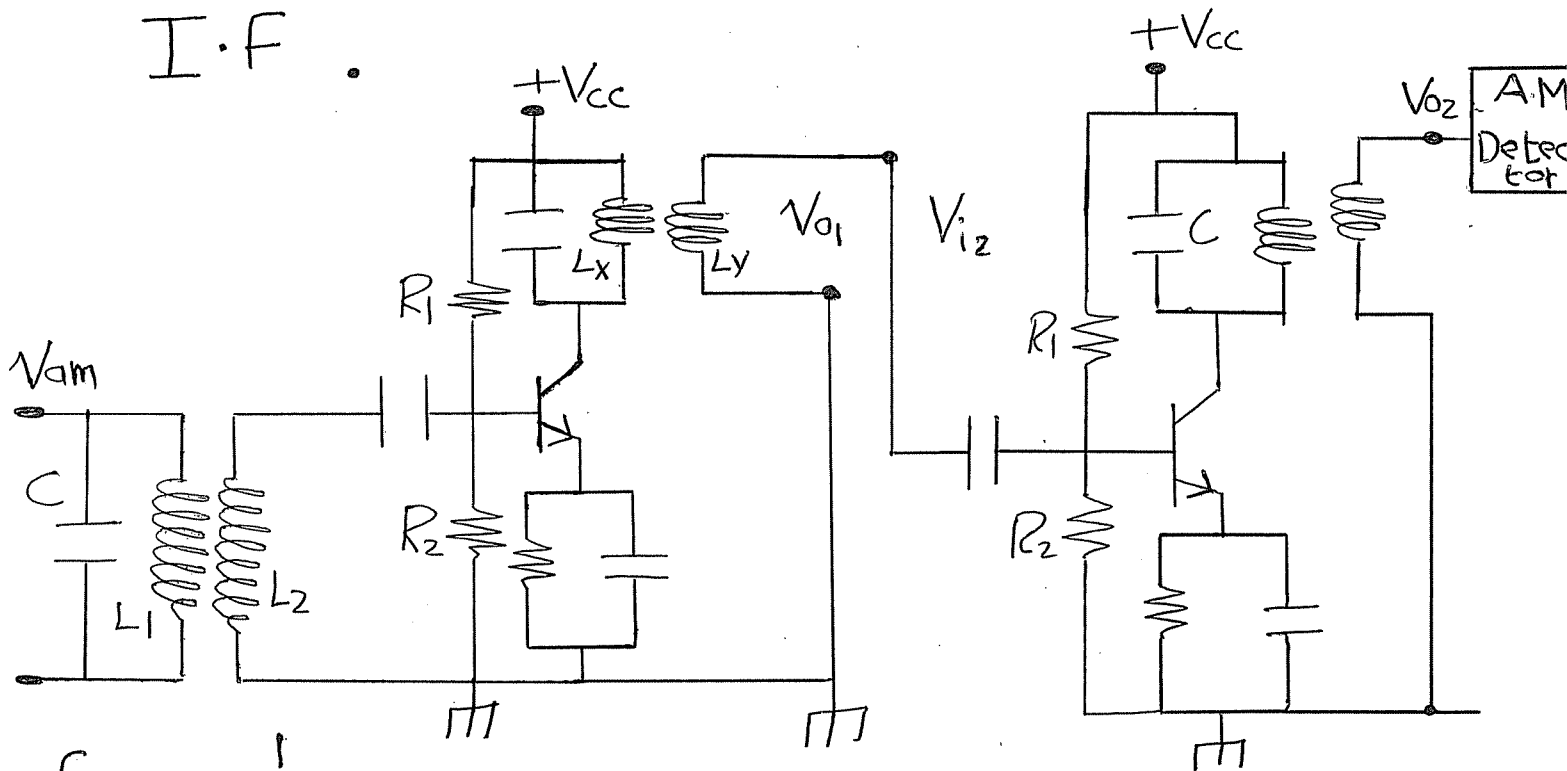

$$f_r = \frac{1}{2\pi\sqrt{L_1 C}} = 455 \text{ kHz}$$




$$\left| \frac{V_o}{V_i} \right|$$

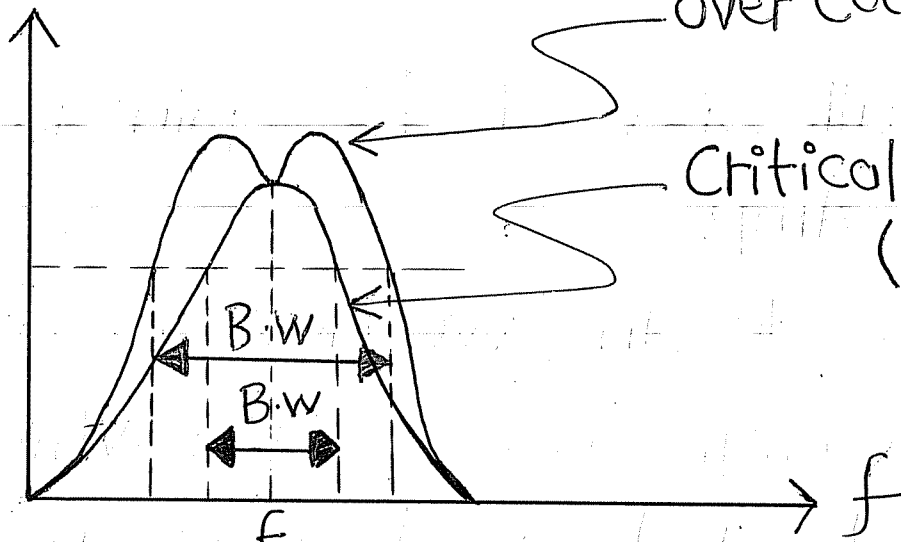


f_0
Center freq.

for high freq. modulating signal,
a wide band Amp. must be used.
(Using over coupling double IF stage).


#AM Demodulator [Diode Detector]

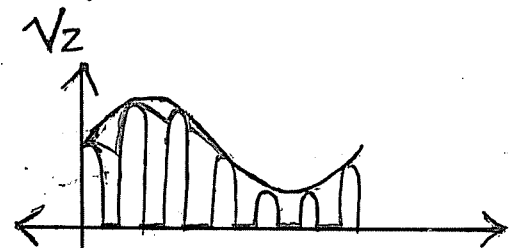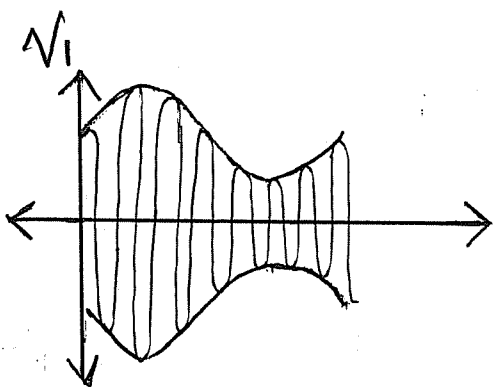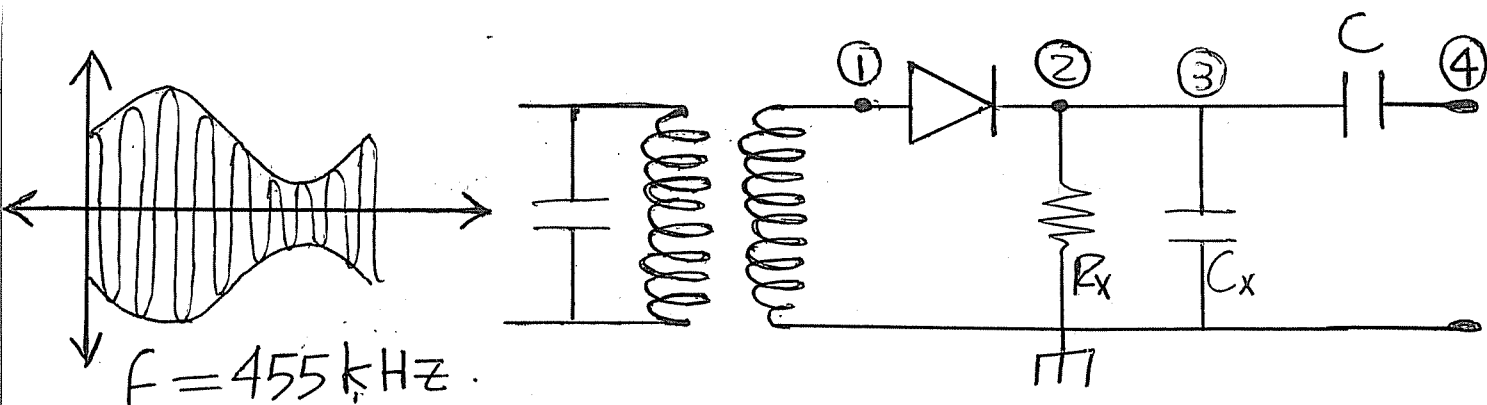

$$V_r = \frac{V_m}{f \cdot C \cdot R}$$

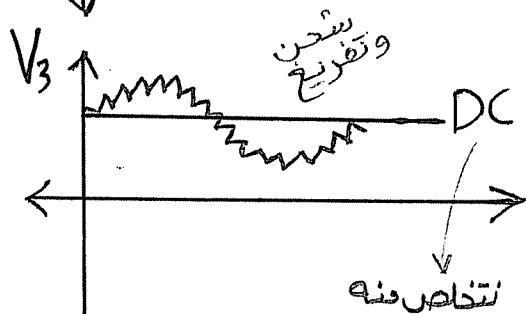


$$X_c = \frac{1}{2\pi f_c}$$

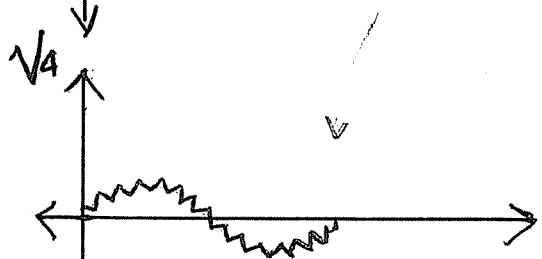


$f = F_m$ (mod. freq. \rightarrow Signal freq.)

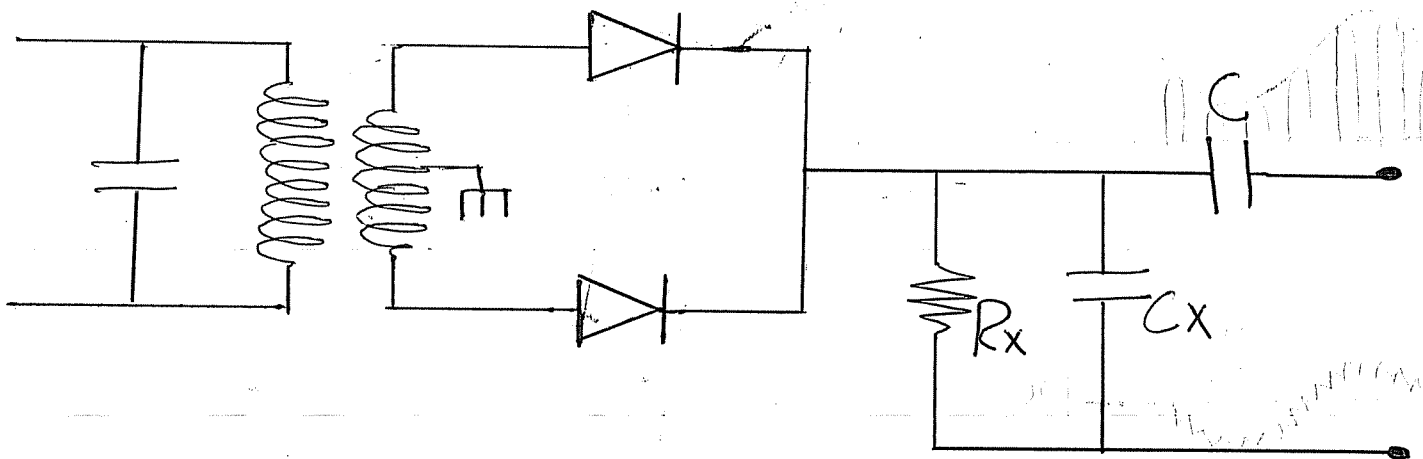- 1] The Diode is Used as Rectifier.
- 2] R_x and C_x used as high pass filter, C_x is chosen such that it gives very low X_c for Carrier (455k).
- 3] C is used as a blocking Capacitor to remove DC component from V_3 .
- 4] we can improve the performance of this modulator (reduce ripple) by using F.W.R with center tap transformer.



$$V_r = \frac{V_m}{2f \cdot C \cdot R}$$

#AGC : Automatic Gain Control :-

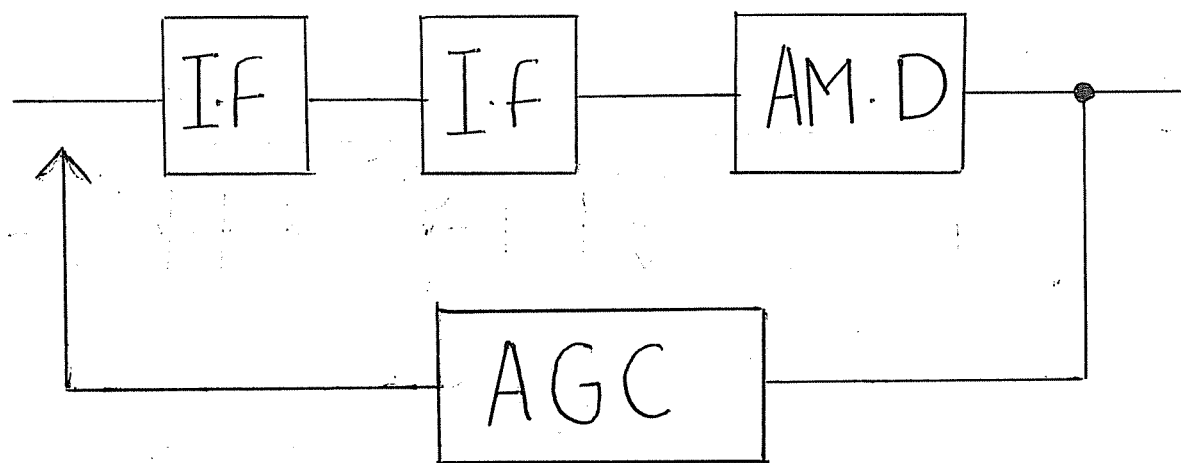

Signal \uparrow : Gain $R_x \downarrow$
Signal \downarrow : Gain $R_x \uparrow$ } at constant Power level.



1] AGC control the power level of the output signal.

2] It is a feedback controlled sys. taking output of AM demodulator and feed it back to I.F. Stage.

من النقطة

③

(فقد لاذ DC)

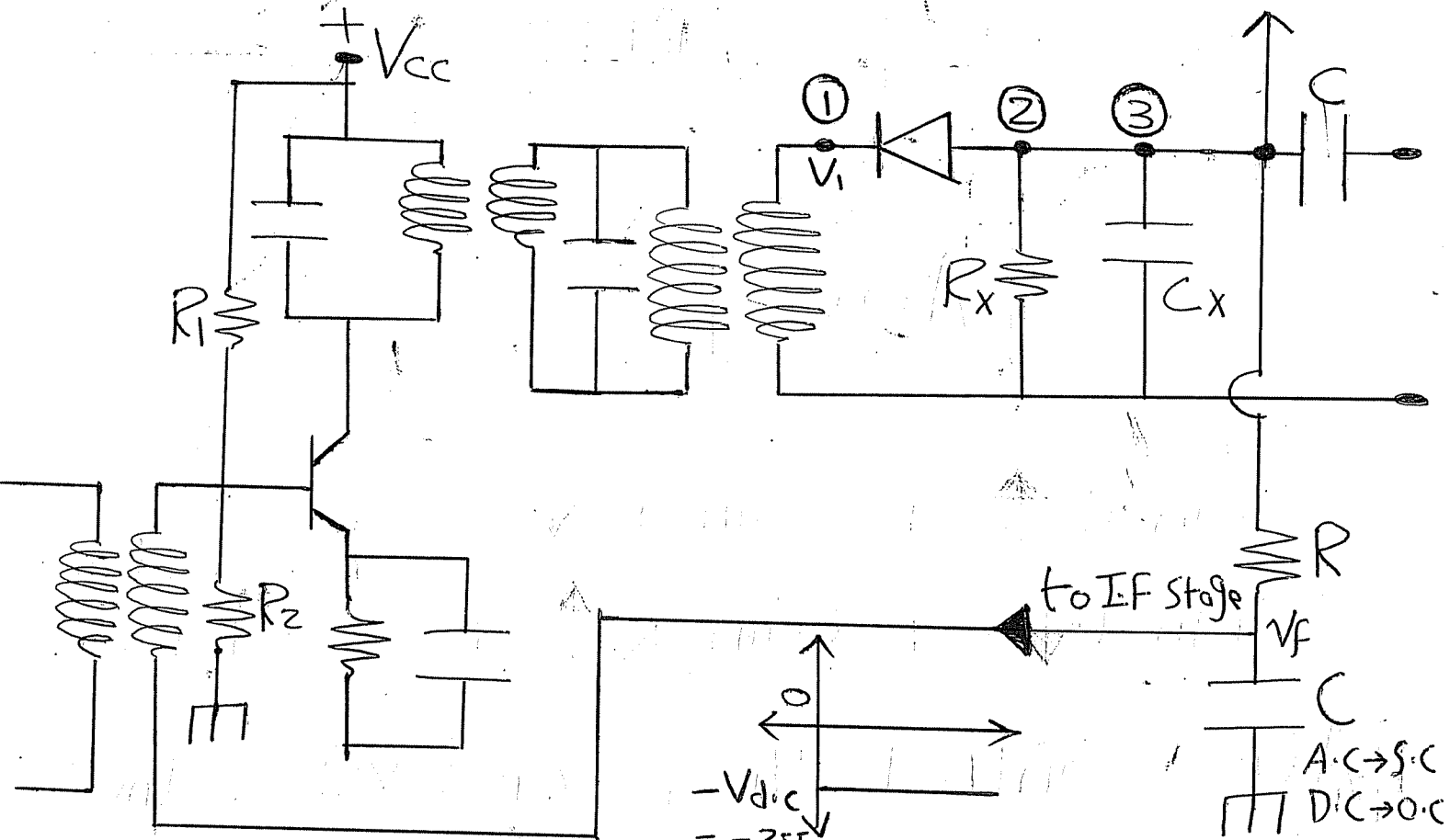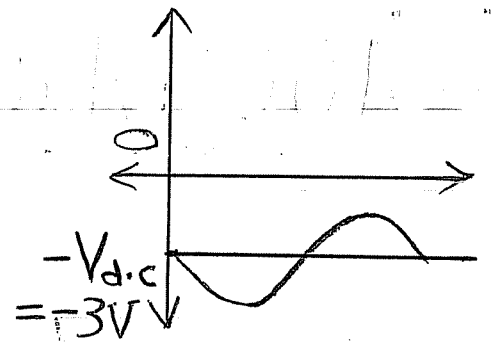

إشارة قوية
 → DC voltage ↑ , I_B ↓ ,
 I_C ↓ , gain ↓ ,
 amplitude V_o ↓ .
 إشارة خفيفة
 → DC voltage ↓ , I_B ↑ ,
 I_C ↑ , gain ↑ ,
 amplitude V_o ↑ .

***note :-**

تظهر DC عالية تظهر DC قليلة



1] For Strong Signal, Large -ve DC Voltage is produced which will reduce I_B , $I_C \downarrow$, $g_m \downarrow$, and Reduce Amp. gain ($A_v = g_m R$) ($g_m = \frac{I_{CQ}}{V_T}$), and Reduce V_o level.

2] The weak Signal produces Small DC voltage $I_B \uparrow$, $I_C \uparrow$, $g_m \uparrow$, $A \uparrow$, $V_o \uparrow$.

→ without -ve F.B :

$$I_B = \frac{2 - 0.6}{16 + 101 * 1} = \frac{1.4}{117k} = 0.012m.$$


$$I_C = 1.2mA.$$

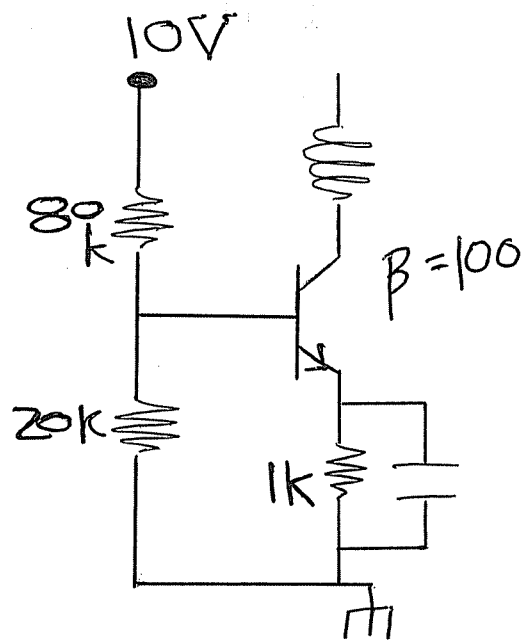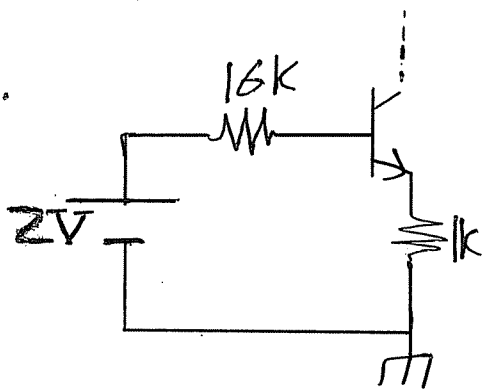

for -ve DC of -1V :
(Strong signal)

$$I_B = \frac{1 - 0.6}{117k}$$


$$I_C = 0.3mA.$$

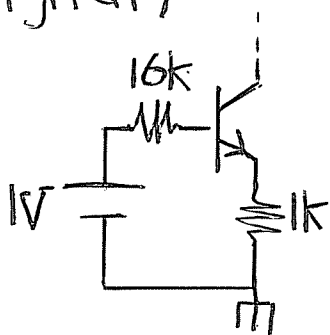


for weak signal :
(Small -ve DC voltage -0.5V)

$$I_B = \frac{1.5 - 0.6}{117k}$$

$$I_C = 0.7mA.$$

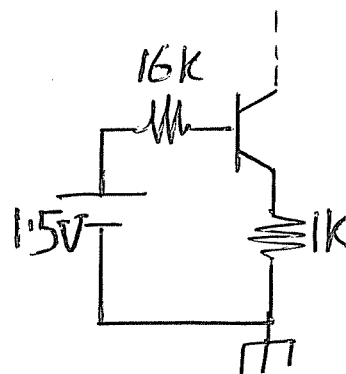


Audio Power Amp. :-

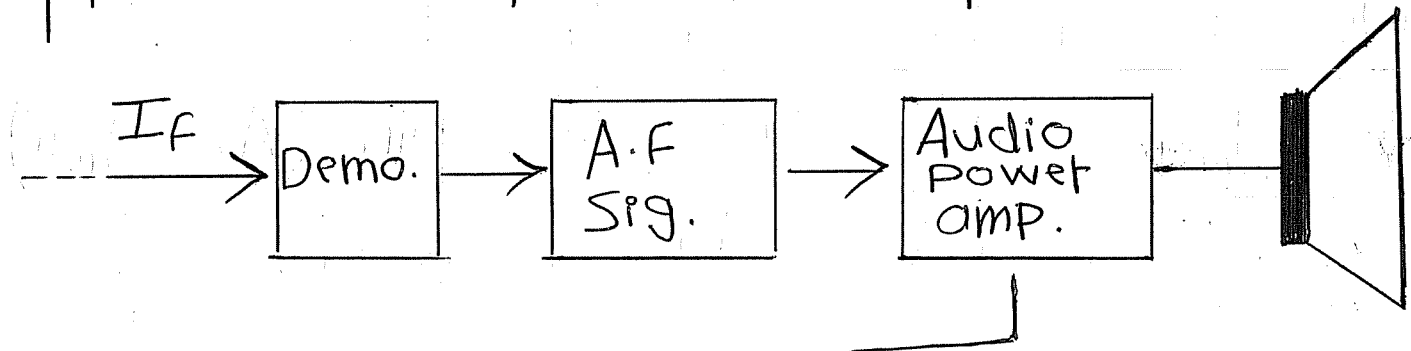

- * It is a linear power Amp. used to increase power level of message signal.
- * It can be Class-A, Class-AB, or Class-B push-pull P.A. #

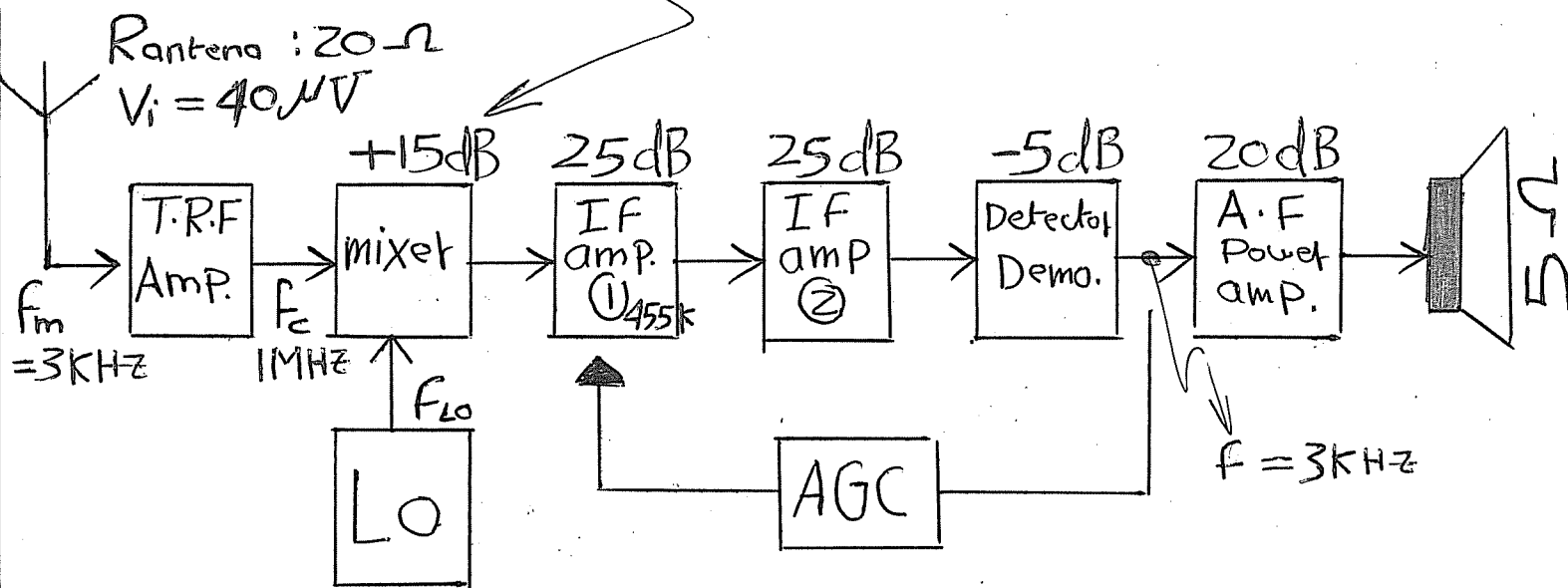Example

-ve \rightarrow Diode mixer.
+ve \rightarrow FET or BJT mixer.



① Calculate R_x power gain.

② Peak output voltage.

③ f_{LO} for HSI.

Solution:

$$\text{① Power gain} = 20 + 15 + 25 + 25 - 5 + 20 = 100 \text{ dB.}$$

$$\text{② } A_P (\text{dB}) = 10 \log \frac{P_o}{P_i}$$

$$100 = 10 \log \frac{P_o}{P_i} \rightarrow \log \frac{P_o}{P_i} = \frac{100}{10}$$

$$P_o = 10^{10} \cdot P_i$$

$$P_i = \frac{V_{i(\text{rms})}^2}{R} = \frac{(40 \cdot 10^{-6})^2}{20} = 80 \cdot 10^{-12} \text{ W.}$$

$$P_o = 10^{10} \cdot 80 \cdot 10^{-12} = 0.8 \text{ W}$$

$$P_o = P_L = \frac{V_o(\text{rms})^2}{R_L} \rightarrow V_o(\text{rms}) = \sqrt{0.8 * 5} = 2V$$

$$V_o(\text{peak}) = 2 * \sqrt{2} = 2.8V$$

③ HSI:

$$f_{LO} - f_c = f_{IF}$$

$$f_{LO} = 1M + 0.455 = 1.455 \text{ MHz}$$

$$f_{\text{Image}} = f_s + 2f_{IF} = 1000 + 910 \\ = 1.910 \text{ MHz}$$

Frequency Modulation :-

$$V_c = V_c \sin 2\pi f_c t \quad (\text{Carrier})$$

$$V_m = V_m \sin 2\pi f_m t \quad (\text{message})$$

$$V_{FM} = V_c \sin (2\pi f_c t + m_f \sin 2\pi f_m t)$$

where m_f : mod. index = $\frac{f_d}{f_m}$,

f_d : frequency deviation.


f_m : message frequency.

Example: $V_{FM} = 5 \sin (2\pi * 10^6 t + 8 \sin 2\pi * 10^3 t)$:


find: V_c , f_c , f_m , m_f , f_d ?

$V_c = 5$, $f_c = 10^6 = 1\text{MHz}$, $f_m = 10^3 = 1\text{kHz}$,

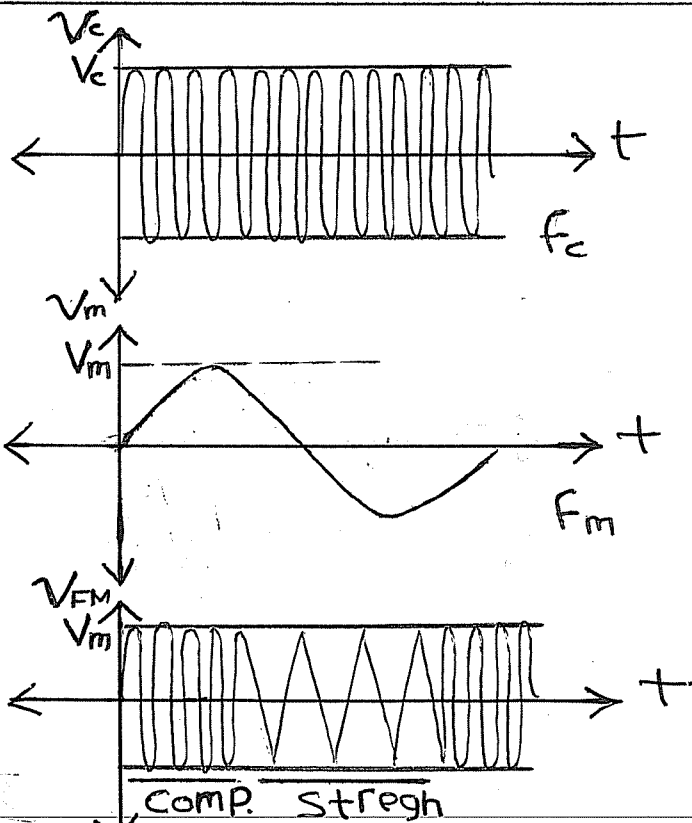$m_f = 8 = \frac{f_d}{f_m}$, $f_d = 8 f_m = 8\text{kHz}$.




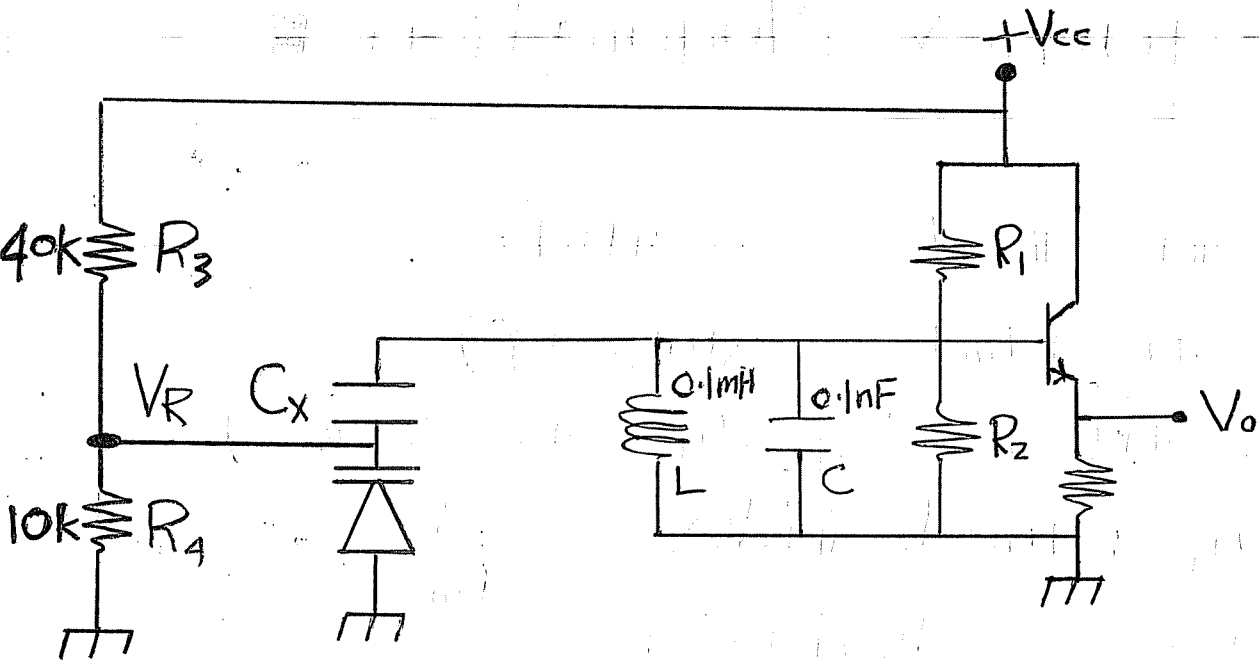FM: Changing freq of carrier according to amplitude of modulating signal.




$$f_c = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10^{-4} * 10^{-10}}} = \frac{10^7}{2\pi} = 1.6 \text{ MHz.}$$


→ C_x is chosen to be very large.

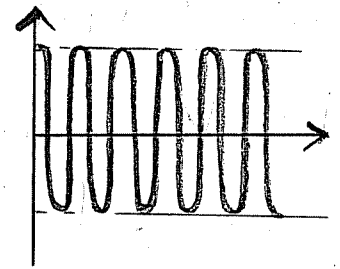

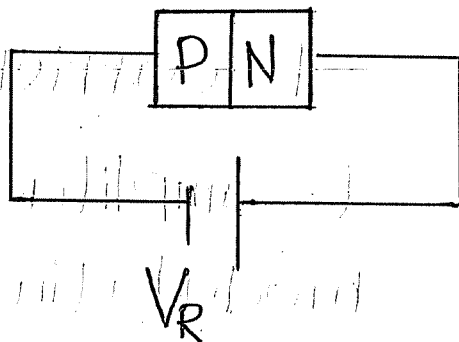* Varactor diode can be used as a Variable Cap.


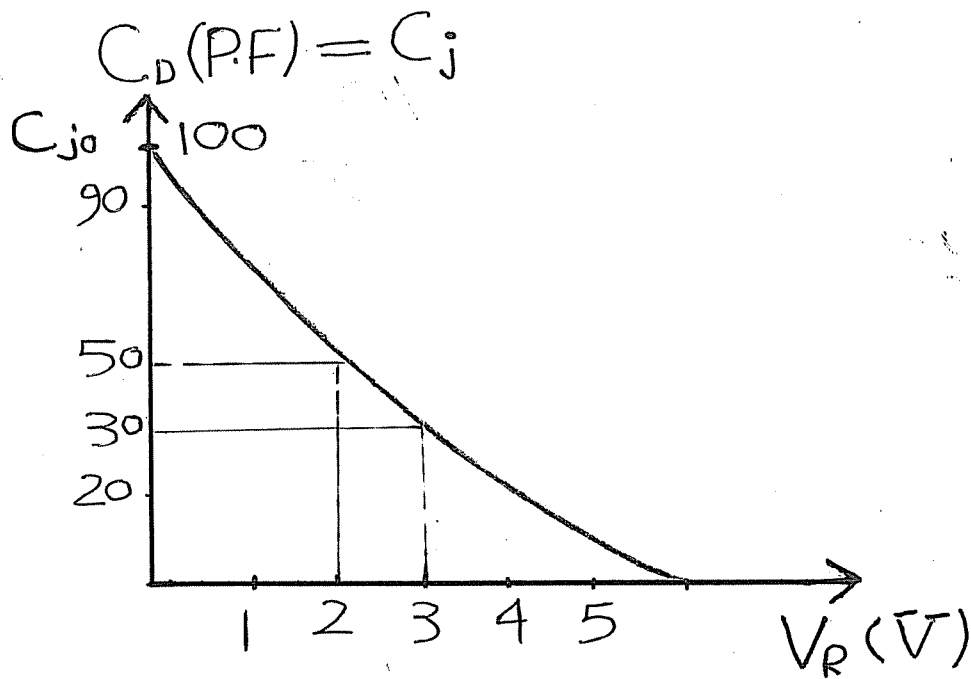
$$C_j = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_{bi}}}}$$




1] without varactor : $f_c = \frac{1}{2\pi\sqrt{LC}} = 1.6 \text{ MHz}$

2] with varactor :

$$f_c = \frac{1}{2\pi\sqrt{LC_{eq}}} \quad , \quad \boxed{C_{eq} = C + C_D}$$

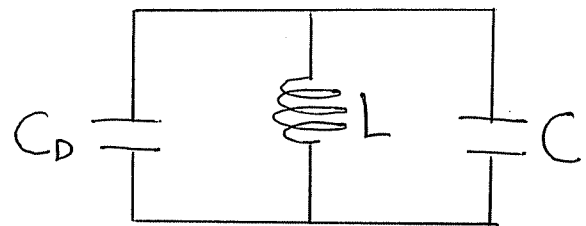Since C_D in series with C_x , and C_x is very large, so $C_D + C_x \approx C_D$.



$$\therefore C_{eq} = C_D + C$$


$$V_R = \frac{10 * 10}{50} = 2 \text{ V}$$

from graph : for $V_R = 2 \text{ V}$. $C_D = 50 \text{ p.F.}$

$$C_{eq} = (50 + 100) \text{ p.F.}$$

$$f_c = \frac{1}{2\pi \sqrt{10^{-4} * 1.5 * 10^{-10}}} = \frac{10^7}{2\pi \sqrt{1.5}} \approx \frac{10^7}{2\pi * 1.2} = \underline{\underline{1.3 \text{ MHz.}}}$$

without V_m .

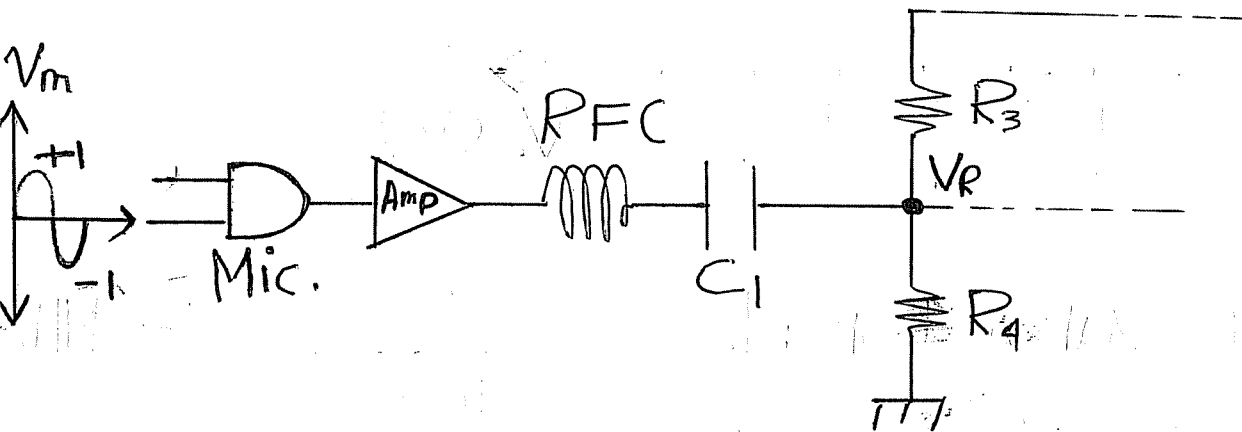


] During +ve HC of V_m :

$$V_R = 2V + V_m = 2 + 1 = 3V$$

$$C_D = 30 \text{ P.F. (From graph)}$$

$$C_{eq.} = 100 + 30 = 130 \text{ P.F.}$$
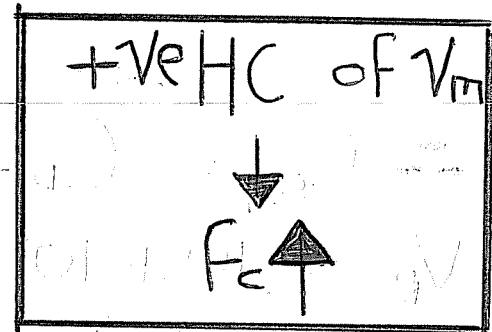
$$f_c^+ = \frac{1}{2\pi \sqrt{10^{-4} * 1.3 * 10^{-10}}} = \frac{10^7}{2\pi \sqrt{1.3}} = \underline{\underline{1.4 \text{ MHz.}}}$$




2] During -ve HC of V_m :

$$V_R = 2 - 1 = 1V$$

$$C_D = 80 \text{ p.F} \rightarrow (\text{from graph})$$

$$C_{eq} = 80 + 100 = 180 \text{ p.F.}$$
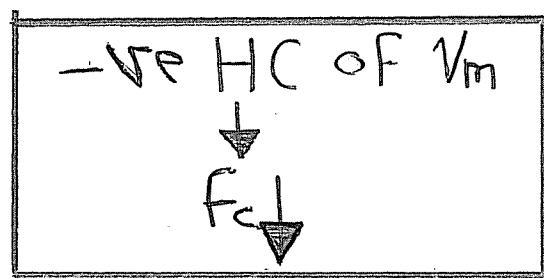
$$f_c^- = \frac{1}{2\pi \sqrt{10^{-9} * 1.8 * 10^{-10}}} = \frac{10^7}{2\pi \sqrt{1.8}} = \underline{\underline{1.18 \text{ MHz.}}}$$



$$m_f = \frac{f_d}{f_m}$$

$$f_d^+ = f_c^+ - f_c = 1.4 - 1.3 = 100 \text{ kHz.}$$

↑
with varactor
and without V_m .

$$\rightarrow m_f = \frac{100}{5} = 20 \checkmark$$

$$f_d^- = f_c^- - f_c = 1.18 - 1.3 = -0.12 \text{ MHz}$$

$$\rightarrow || = 120 \text{ kHz.}$$

$$\rightarrow m_f = \frac{120}{5} = 24 \checkmark$$

* $f_d^+ \neq f_d^-$: because non linear relation between (V_R) and (C_j).

LC-FM Modulator :-

(R_1) and (R_2) \longrightarrow BJT biasing.

(R_3) and (R_4) \longrightarrow Varactor biasing.

C_1 \longrightarrow blocking and Coupling Cap.

RFC : Radio freq. Chock.

$X_L = 2\pi fL$: \rightarrow D.C \rightarrow S.C.
 \rightarrow A.C \rightarrow O.C.

L \rightarrow O.C : For Radio freq.

S.C : Audio Freq.

يمنع ال Carrier من الرجوع الى V_R عن طريق V_m يدخل ويتبع مع V_R .
 \rightarrow because high Impedance.

In This FM mod. :-

1] Varactor is used as Variable Cap. (C_D).

2] As $V_m \uparrow$, $V_R \uparrow$, $C_D \downarrow$, $C_{eq} \downarrow$, $f_c \uparrow$.

3] As $V_m \downarrow$, $V_R \downarrow$, $C_D \uparrow$, $C_{eq} \uparrow$, $f_c \downarrow$.

i.e. the freq. of Carrier (f_c) increase and decrease with increasing and decreasing of amplitude of message signal. (FM signal) is produced 6

• The advantage of this FM mod. is:
Large freq. deviation. ✓

• The disadvantage:

Poor freq. stability. ✓

freq. depends on $R, L, C \rightarrow$ which are affected
by Temp., voltage variation, aging. \rightarrow low stability


Solution: Using Crystal Osc. (high freq. stability)

↩ problem: Small freq. deviation.

↳ Solution: $\omega_0 \rightarrow$


freq. multiplier
*2, *3, ...

Crystal-FM mod.

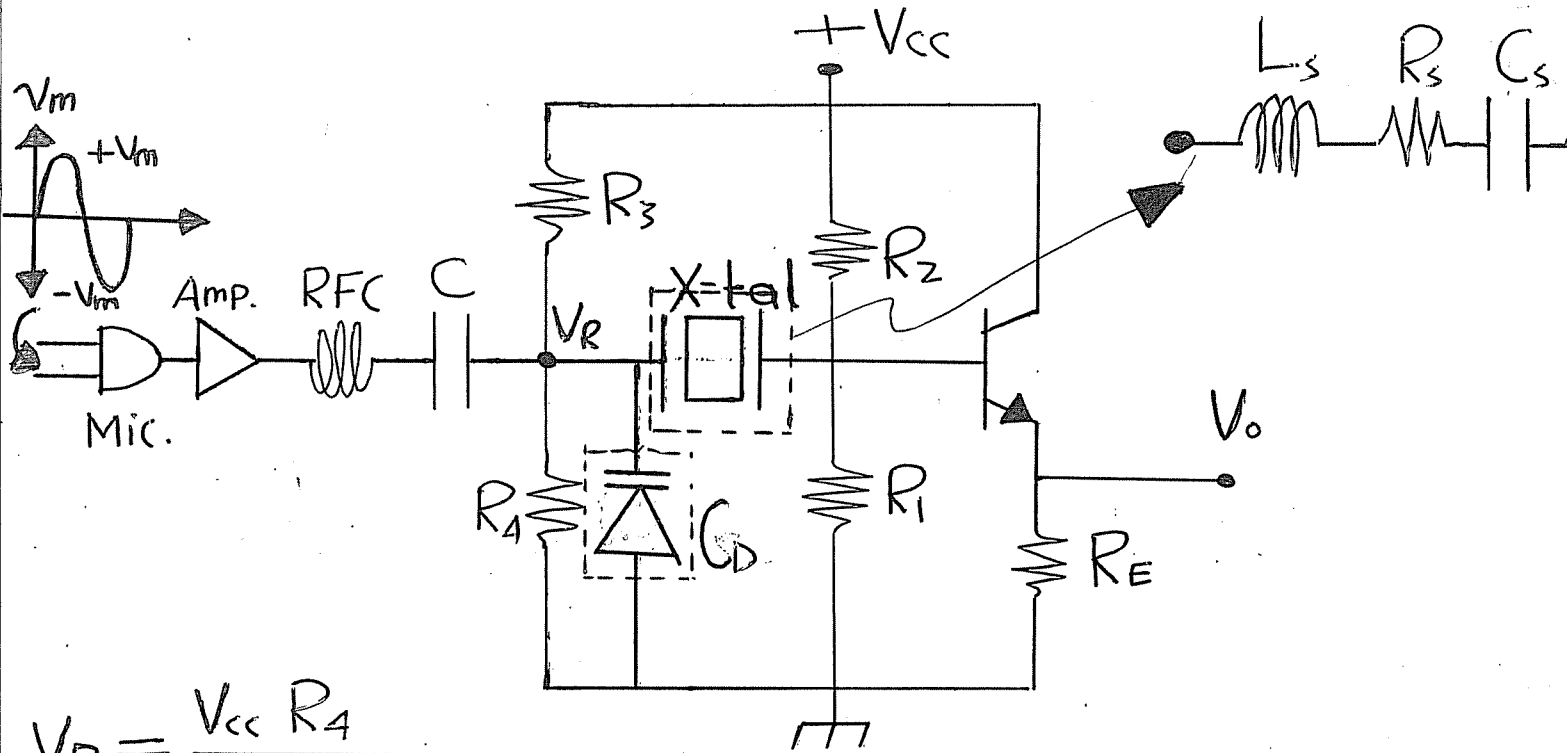

$$V_R = \frac{V_{cc} R_4}{R_3 + R_4}$$
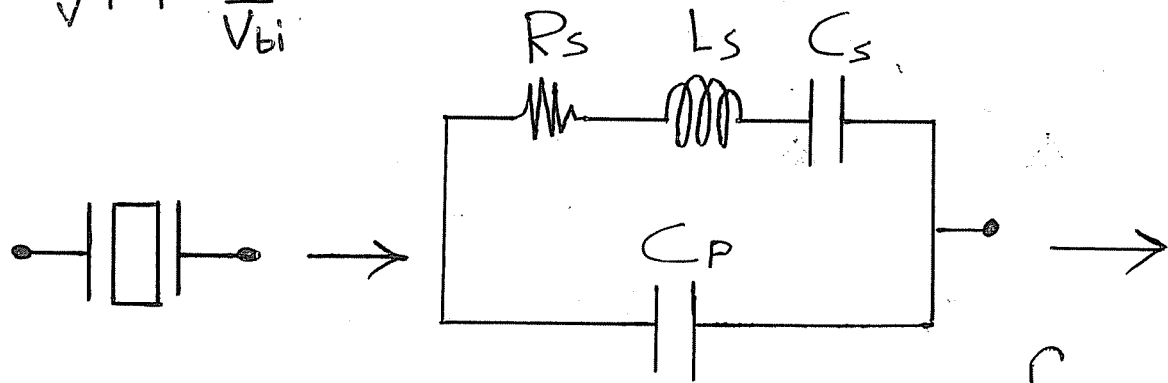
$$C_D = \frac{C_{j_0}}{\sqrt{1 + \frac{V_R}{V_{bi}}}}$$



$$f = \frac{1}{2\pi\sqrt{L_s \cdot C_{eq}}}$$

$$C_{eq} = C_s // C_p$$

Since $C_p \gg C_s$,

$$C_{eq} \approx C_s$$

i] without V_m :-

1] without Varactor :-

$$f_c = \frac{1}{2\pi\sqrt{L_s C_s}}$$

2] with Varactor :-

$$f_c = \frac{1}{2\pi\sqrt{L_s C_{eq}}} \quad , \quad C_{eq} = C_D // C_s .$$

ii] when V_m is applied :-

1] During +ve H.C of V_m :

$$V_R \uparrow , C_D \downarrow , C_{eq} \downarrow , f_c \uparrow .$$

2] During -ve H.C of V_m :

$$V_R \downarrow , C_D \uparrow , C_{eq} \uparrow , f_c \downarrow .$$

i.e : The freq. of Carrier f_c increase with increasing of V_m , and decrease with decreasing of V_m .

[FM is Produced.] .

Advantage : Superior freq. Stability.

Disadvantage : Small freq. deviation (hundred of Hz). (f_d in range of hundred of Hz).


We can increase the freq. deviation by using freq. multiplier.

for example : if the o/p of Crystal FM mod. is : $f_c = 1\text{MHz}$, $f_d = 0.2\text{kHz}$.


→ to make $f_d = 2.4\text{kHz}$, we have to multiply the o/p by 12.

* The available freq. multipliers are

*2 and *3
doubler Triplet

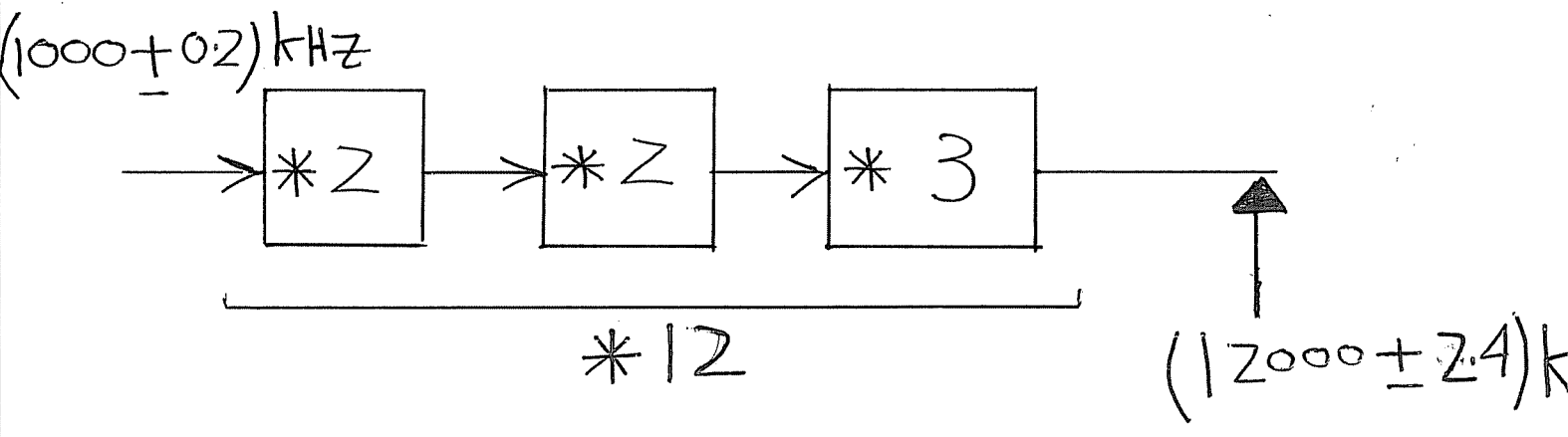

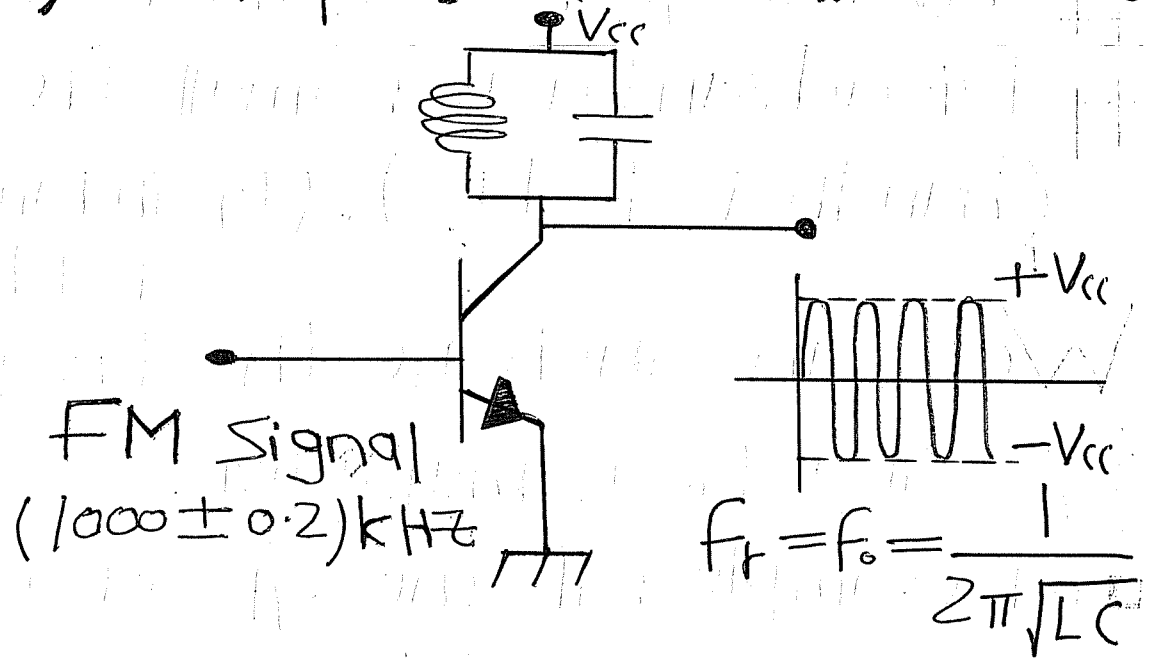practically, multipliers are Class-C amp.




→ To be used as doubler: $f_r = 2f_m$


$$2000 = \frac{1}{2\pi\sqrt{LC}}$$

→ To be used as Tripplet: $f_r = 3f_m$


$$3000 = \frac{1}{2\pi\sqrt{LC}}$$

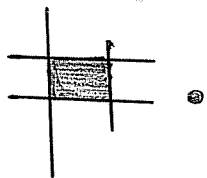

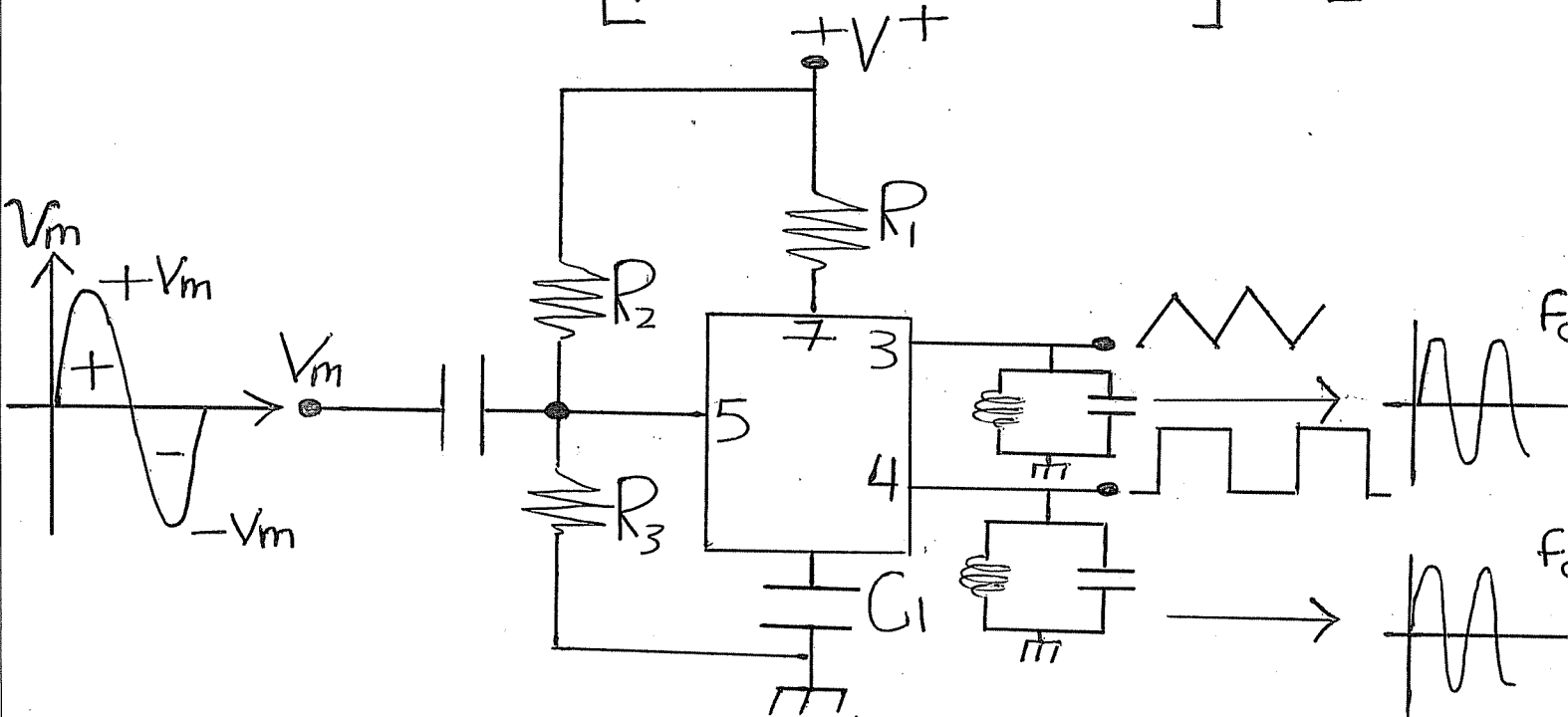Voltage - Controlled Oscillator FM mod. [VCO FM mod.]


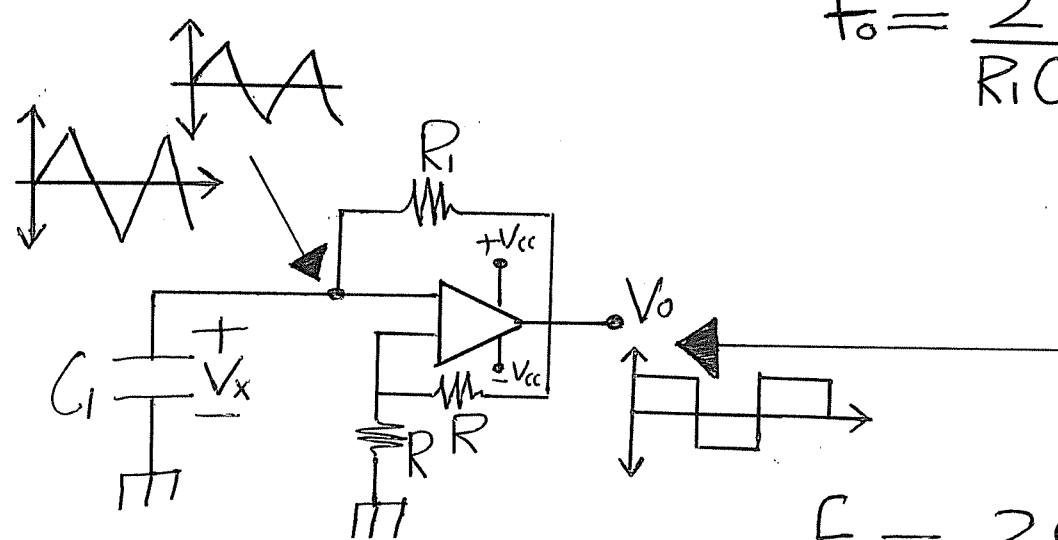
$$f_0 = \frac{2}{R_1 C_1} \text{ (free running freq.)}$$



[without V_c]
[Astable MTV]

$$f_0 = \frac{2(V^+ - V_c)}{R_1 C_1 V^+}$$

[with V_c]
[Voltage Controlled Oscillator].

1] Without V_c , the CGT. will oscillate at free running Mode, with: $f_o = f_c = \frac{2}{R_1 C_1}$

2] With V_c (when R_2 and R_3) are used:

$$f_o = f_c = \frac{2(V^+ - V_c)}{R_1 C_1 V^+}$$

3] When V_m is applied:

i) when $V_m \uparrow$, $V_c \uparrow$, $f \downarrow$.


ii) when $V_m \downarrow$, $V_c \downarrow$, $f \uparrow$.

i.e The freq. of o/p is Changed according to Amp. of mod. signal.

4] To Obtain a Sinusoidal wave (from Square or Triangular), a parallel Tuned CGT. is used.

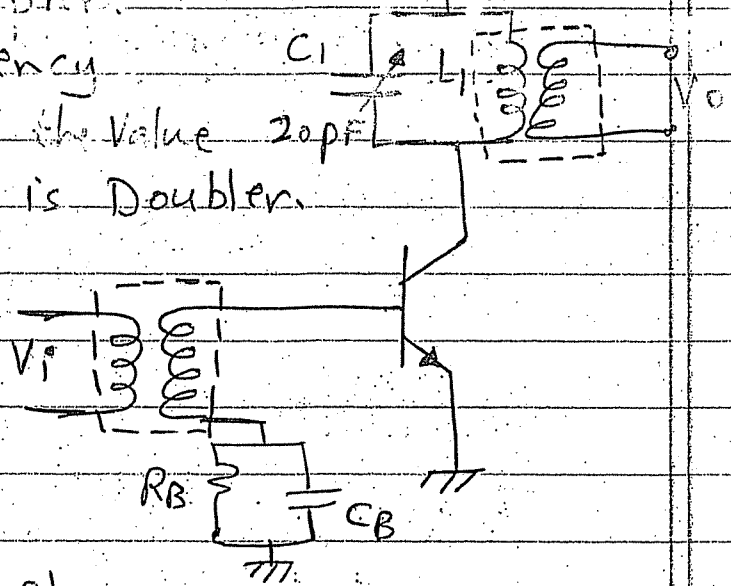
Q1: The freq. multiplier ckt. shown operates as a tripler.

IF the input frequency is 10 MHz. calculate the value of L_1 . Repeat if it is Doubler.



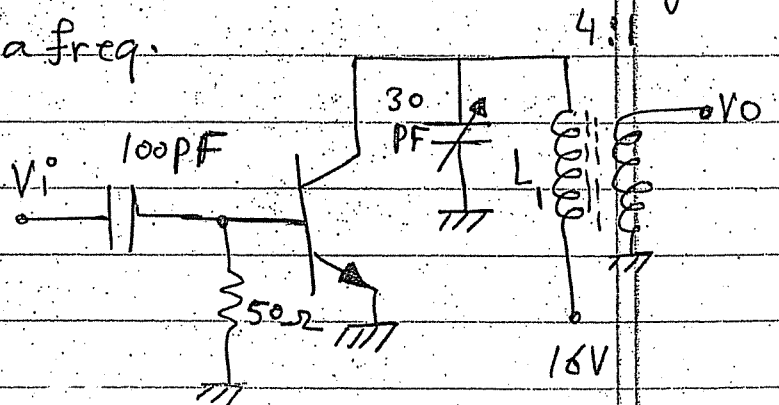Q2: For the power Amp. shown.


- Indicate the class of operation and why?
- Assume ideal Transformer, what is the Max Load Voltage.
- IF the input voltage has a freq. of 15 MHz. calculate L_1 required to tune the ckt. for fundamental.



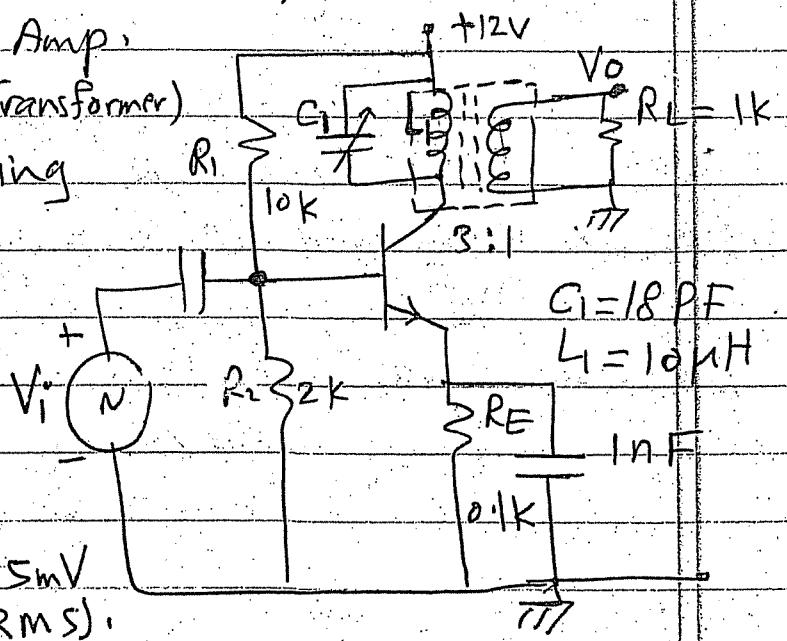Q3: For the tuned RF Amp.

shown (Assume ideal Transformer)

- Calculate the operating frequency.
- Calculate the Max. gain and selectivity and B.W?
- The peak o/p load voltage for $V_i = 2.5mV$ (RMS).




Q4: Sine wave signals with frequencies f_1 10 MHz and f_2 12 MHz are applied to the JFET Mixer shown. (Square Law Mixer)


Find the frequencies (possible) at the o/p?

$$V_a = V_A \sin 2\pi \times 10^7 t$$

$$V_b = V_B \sin 24\pi \times 10^7 t$$

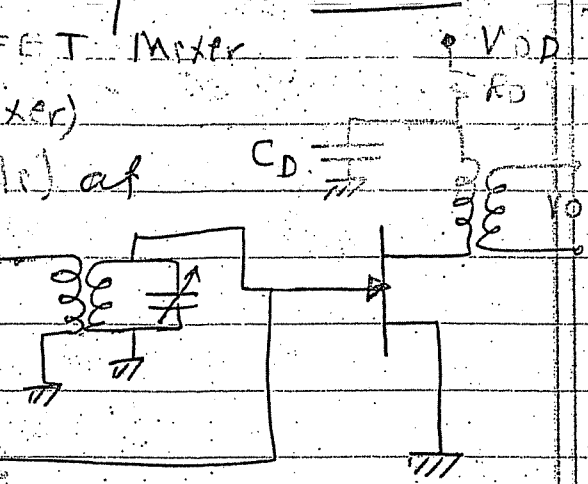


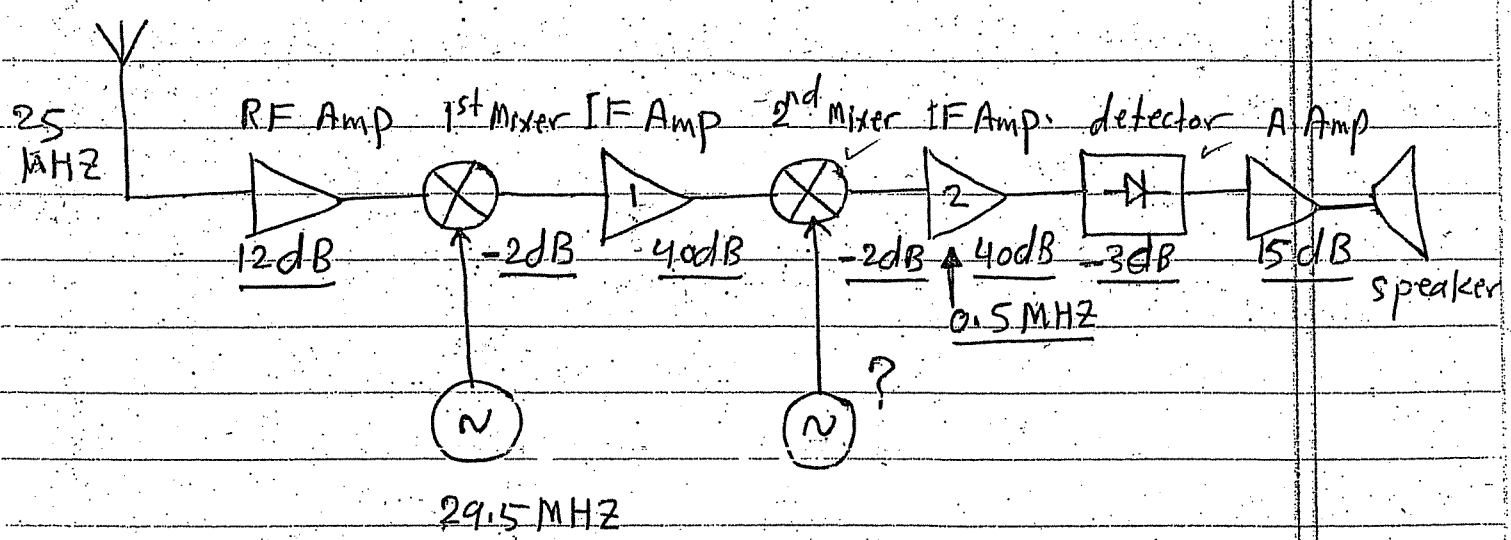Q5: Fig. 5 shows a block diagram for double conversion AM receiver, with max. gain for each stage.



- ① what is the total power gain of the receiver from antenna to speaker.
- ② Calculate the freq of 1st IF Amp & 2nd Local oscillator
- ③ what is the Min. Signal required at antenna in order to get 0.5 W power at speaker. (in μ V) assume 50 Ω impedance antenna.
- ④ Calculate P_o for $V_i = 30 \mu$ V at the antenna.


FM - Receiver :

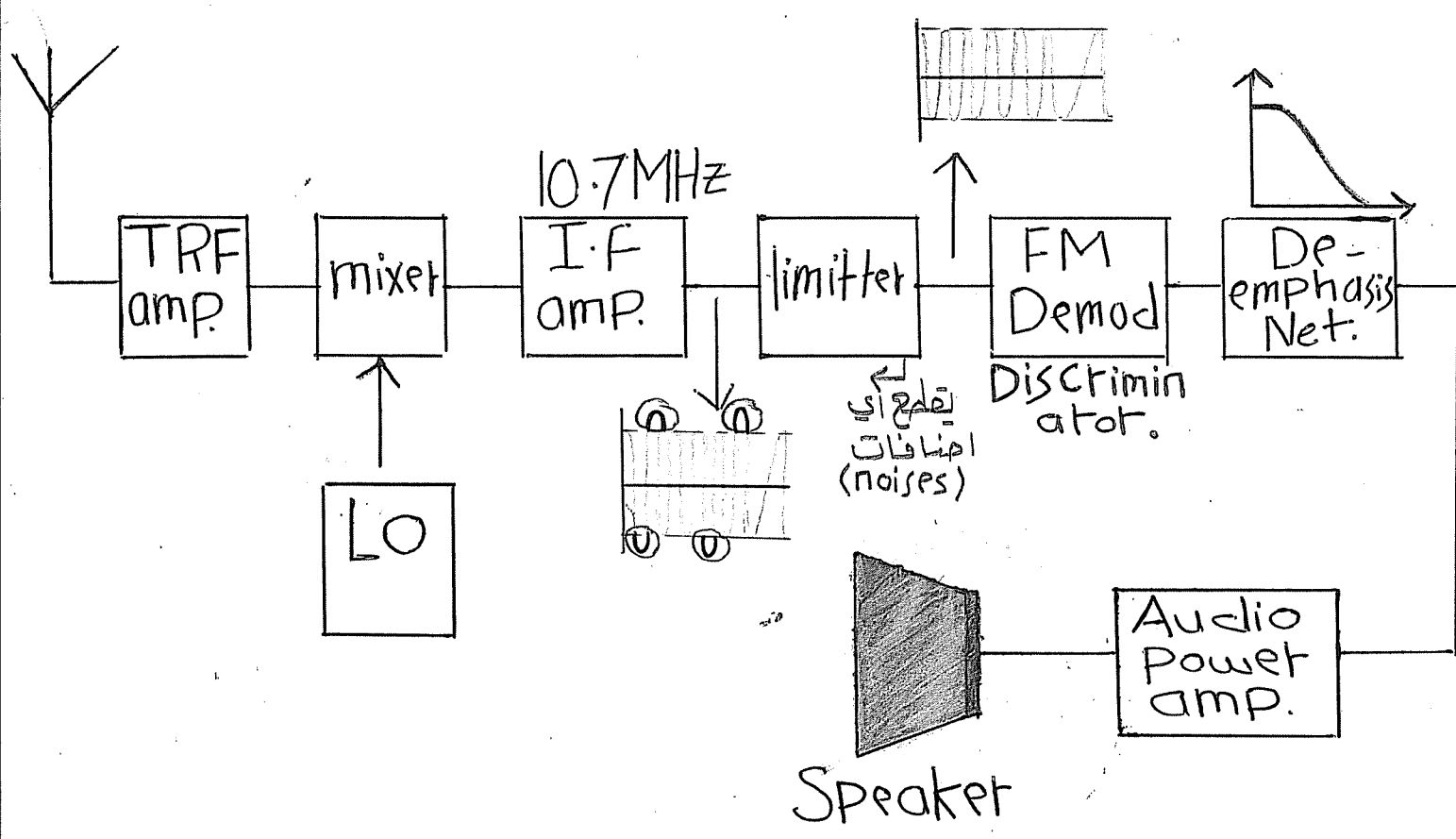

→ @ Transmitter : → Pre-emphasis Net. (HPF)

→ @ Receiver : → De-emphasis Net. (LPF)

--- A ---

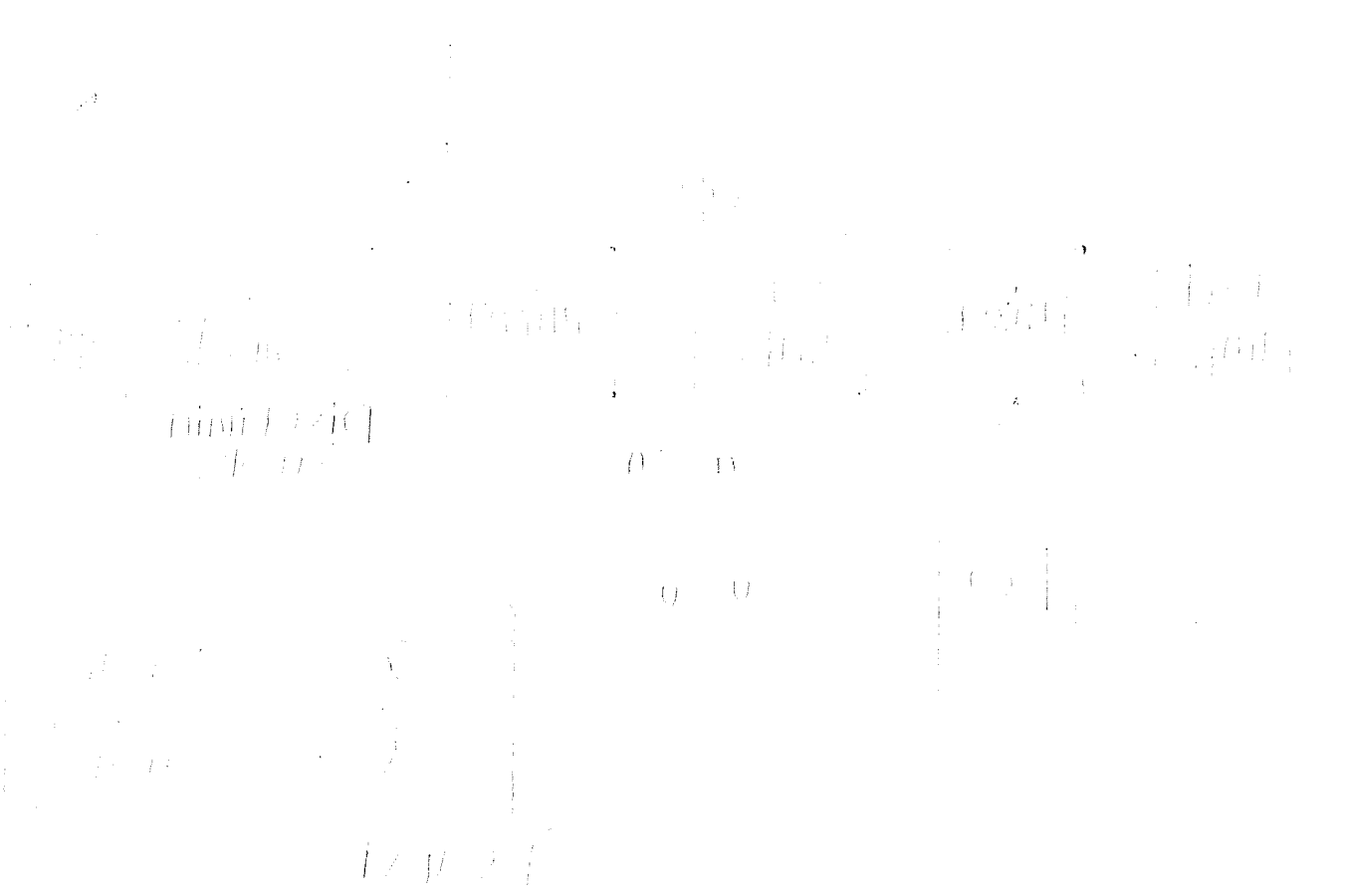

(1111) \leftarrow ... \leftarrow





(1112) \leftarrow ... \leftarrow

FM-Demodulator



1) Slope Detector :-


FM mod :
Voltage to freq
Conversion

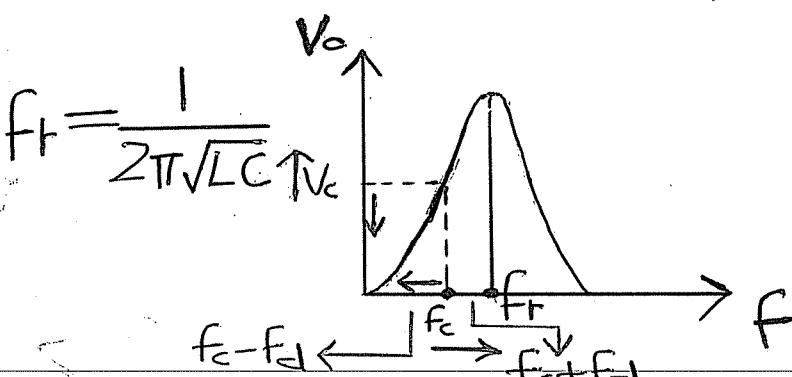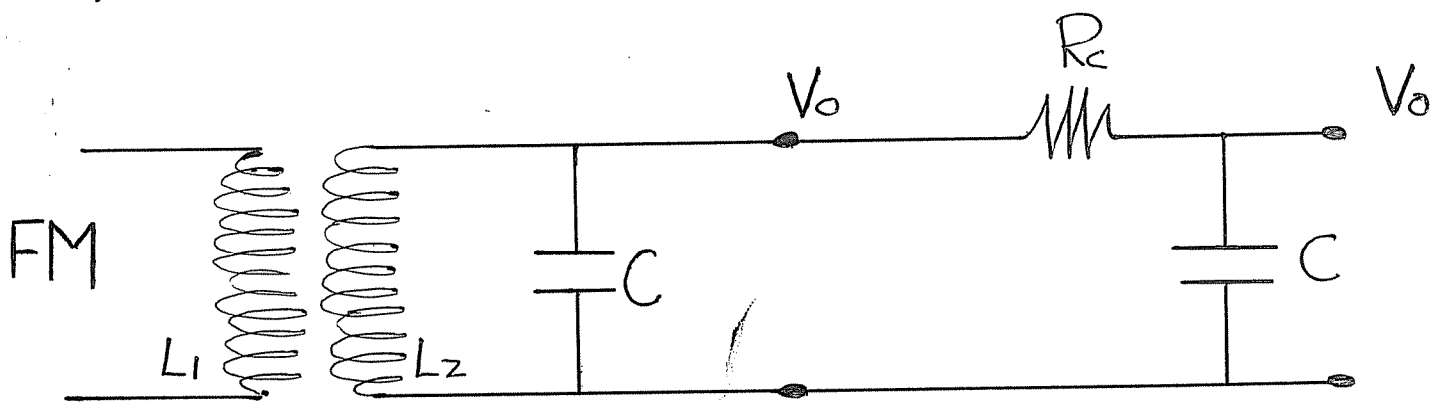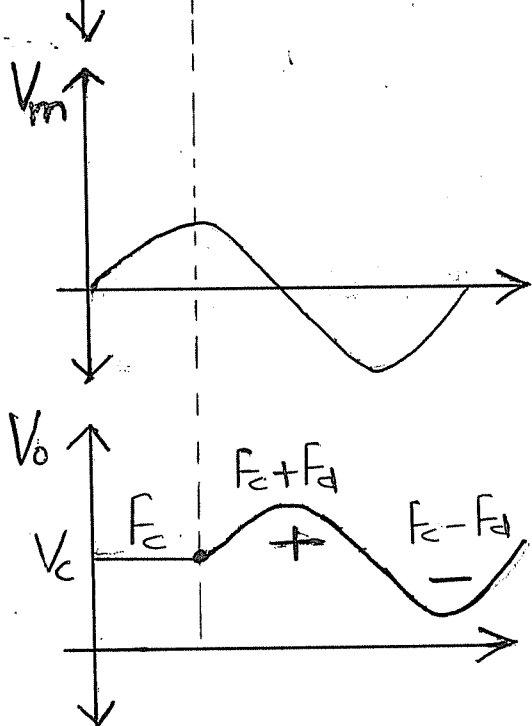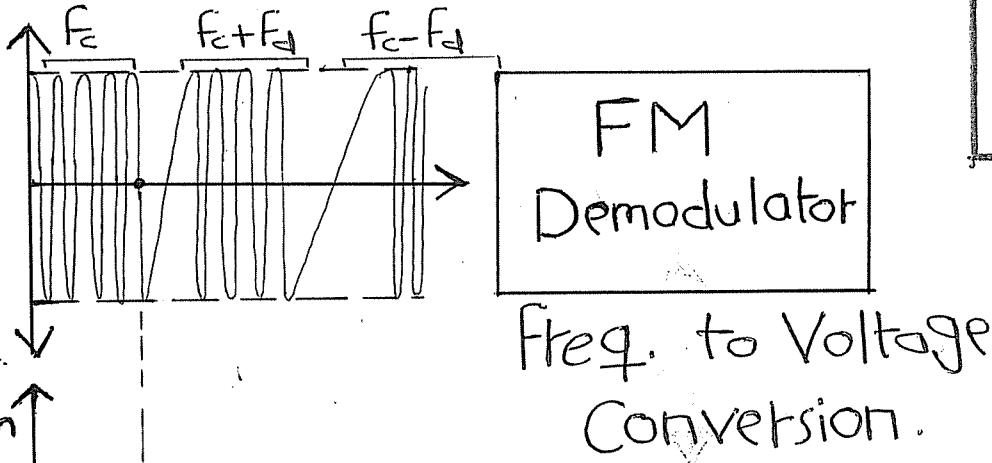


low pass filter
S.C for carrier sig.
O.C for modulating sig.

mod. Sig. جی سیگنل

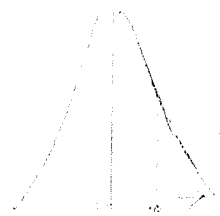- 1) f_r of the tuned CCT must be chosen such that $f_r > f_c$.
- 2) f_c must be in the center of linear part of the response.
- 3) i) when $f = f_c$, $V_o = V_c$.
ii) for $f > f_c$, $V_o \uparrow$.
iii) for $f < f_c$, $V_o \downarrow$.
- 4) This means that o/p of the tuned cct. will be proportional to freq. of the FM input signal.




2) Pulse - averaging FM Demod. :-

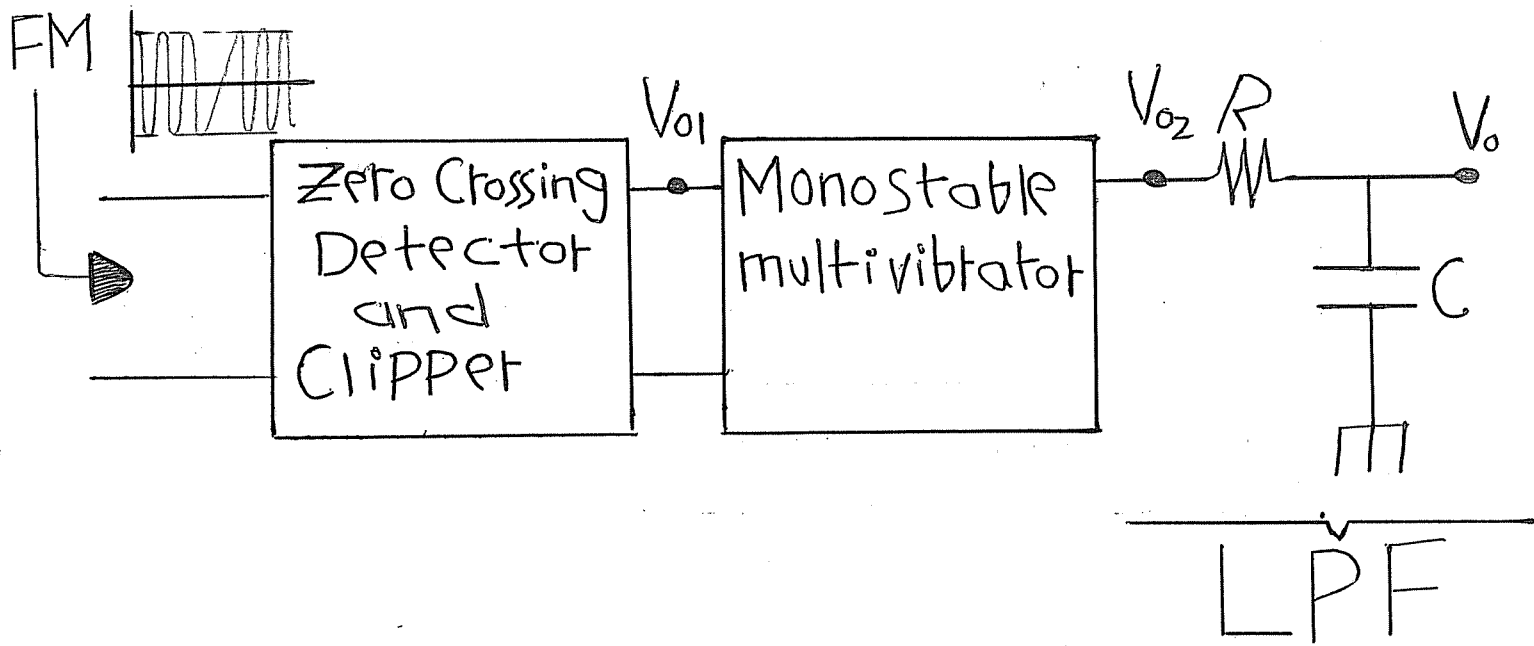

Zero-Crossing Detector :

(Voltage Comparator with $V_{ref} = 0$)

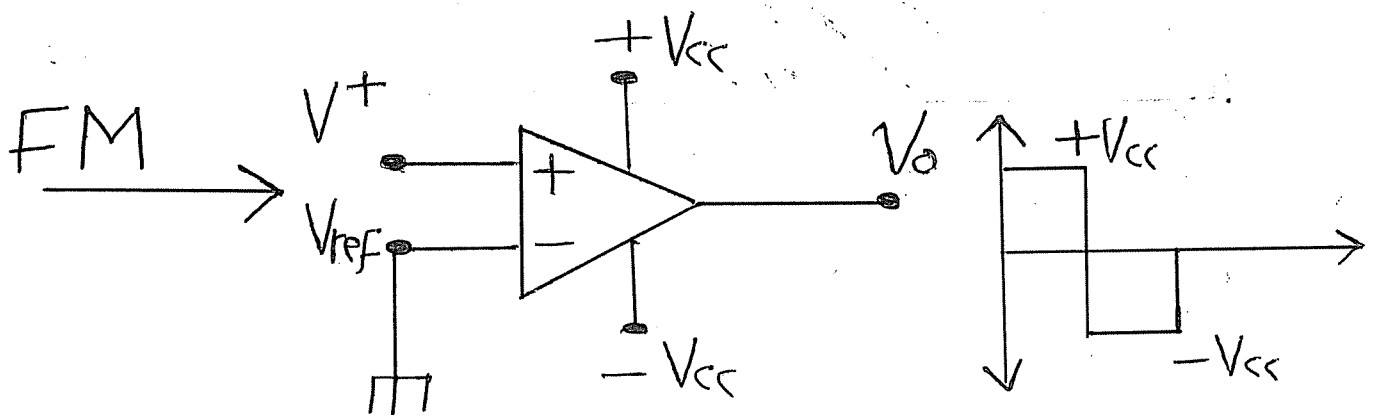

$$V_o = A_{OL} (V^+ - V^-)$$


A_{OL} : Open-loop gain.





$A_{OL} = \infty$ (ideal op-Amp.)

$$V_o = \mp \infty (V^+ - V^-) = \mp \infty \Rightarrow \mp V_{cc}$$

① if $V^+ > V^-$, $V_o = +V_{cc}$.


② if $V^+ < V^-$, $V_o = -V_{cc}$.

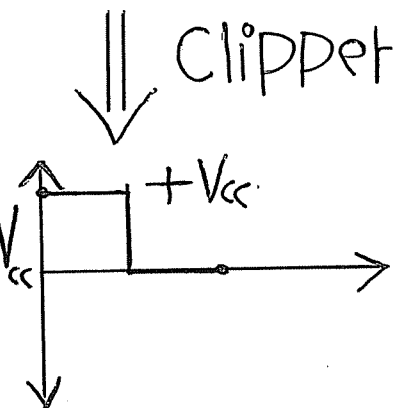

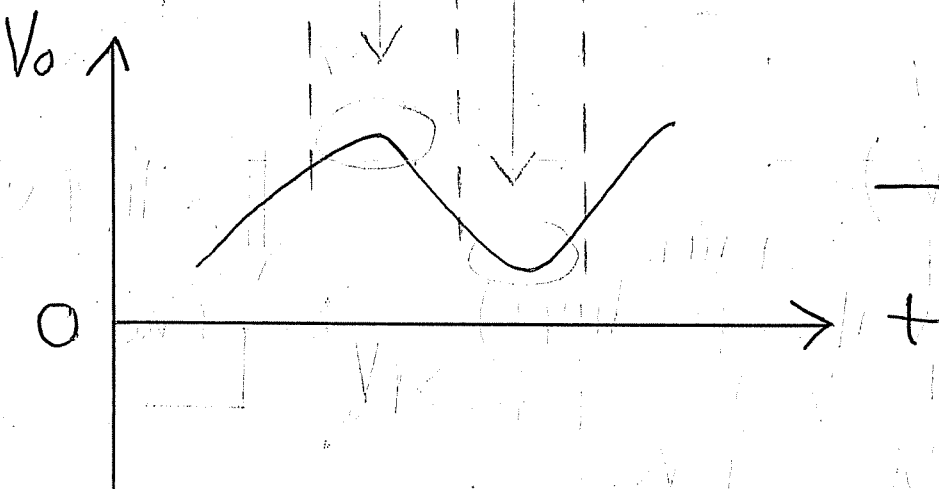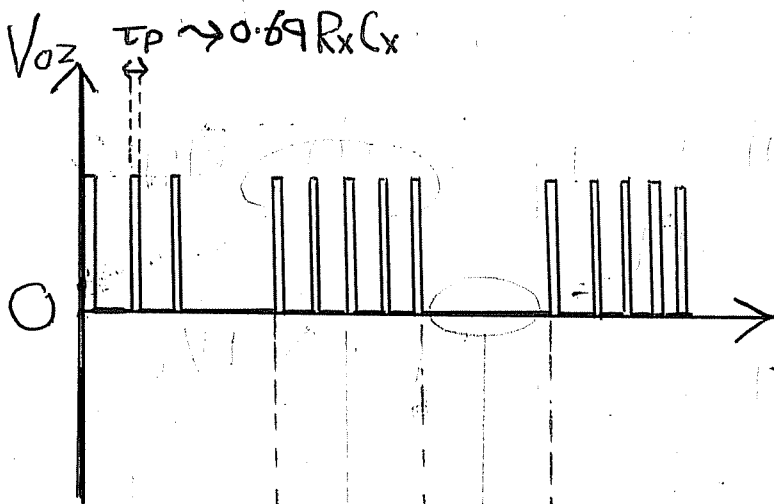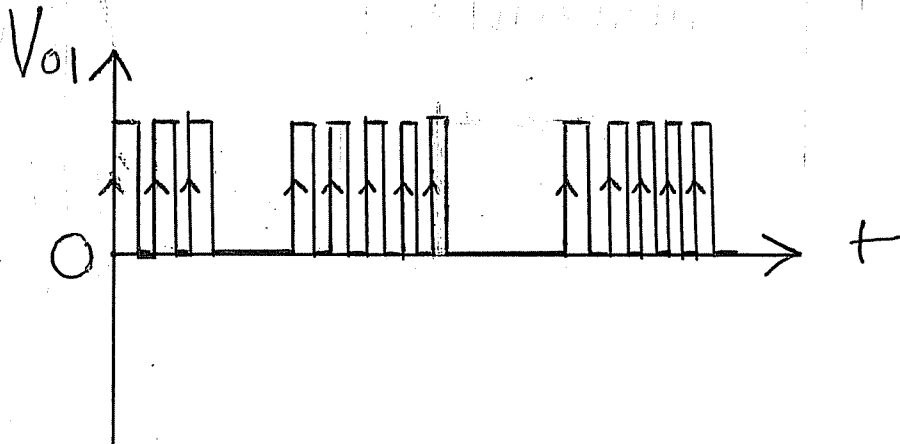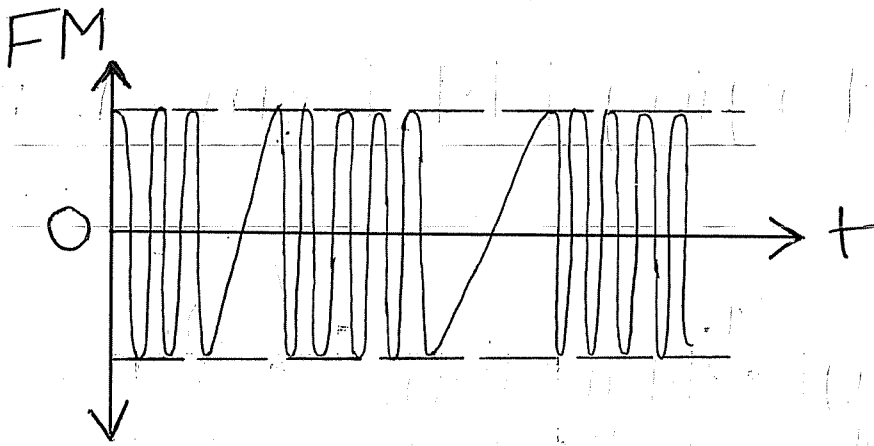

الاختلاف
في duration
فقط

it has a
constant
duration.

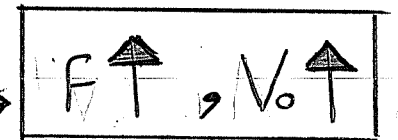



RC must be chosen (design) to have a very large time constant.

$$T = R \cdot C \gg T_{\max}$$

$$T_{\max} = \frac{1}{f_{\max}} \quad \rightarrow \quad f_{\max} : \text{max freq. in FM sig.}$$

$$\rightarrow f_{\max} = f_c + f_d$$

note:-

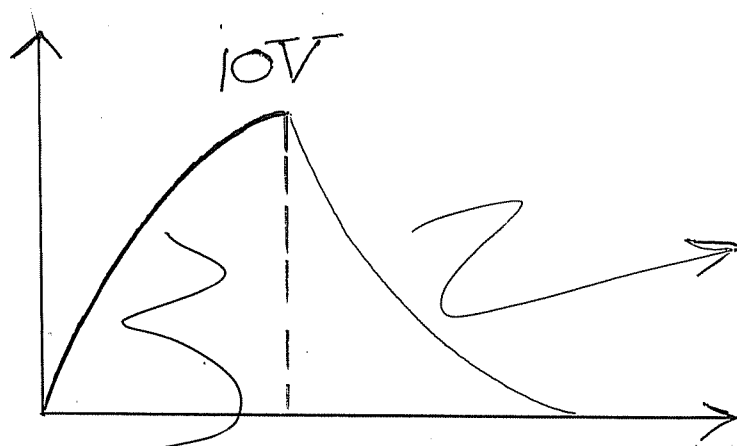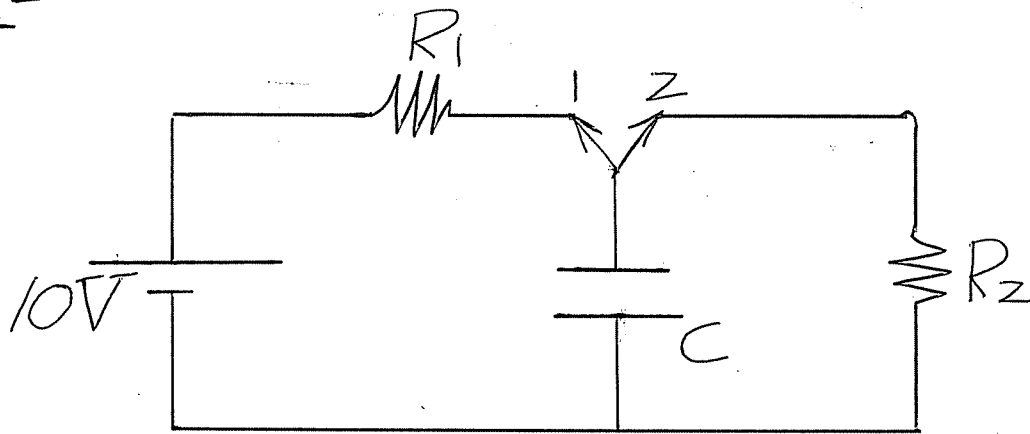


$$\tau = 5R_1C$$

وقت الشحن

$$\tau = 5R_2C$$

وقت التفريغ

3) Foster - Seely Discriminator :-

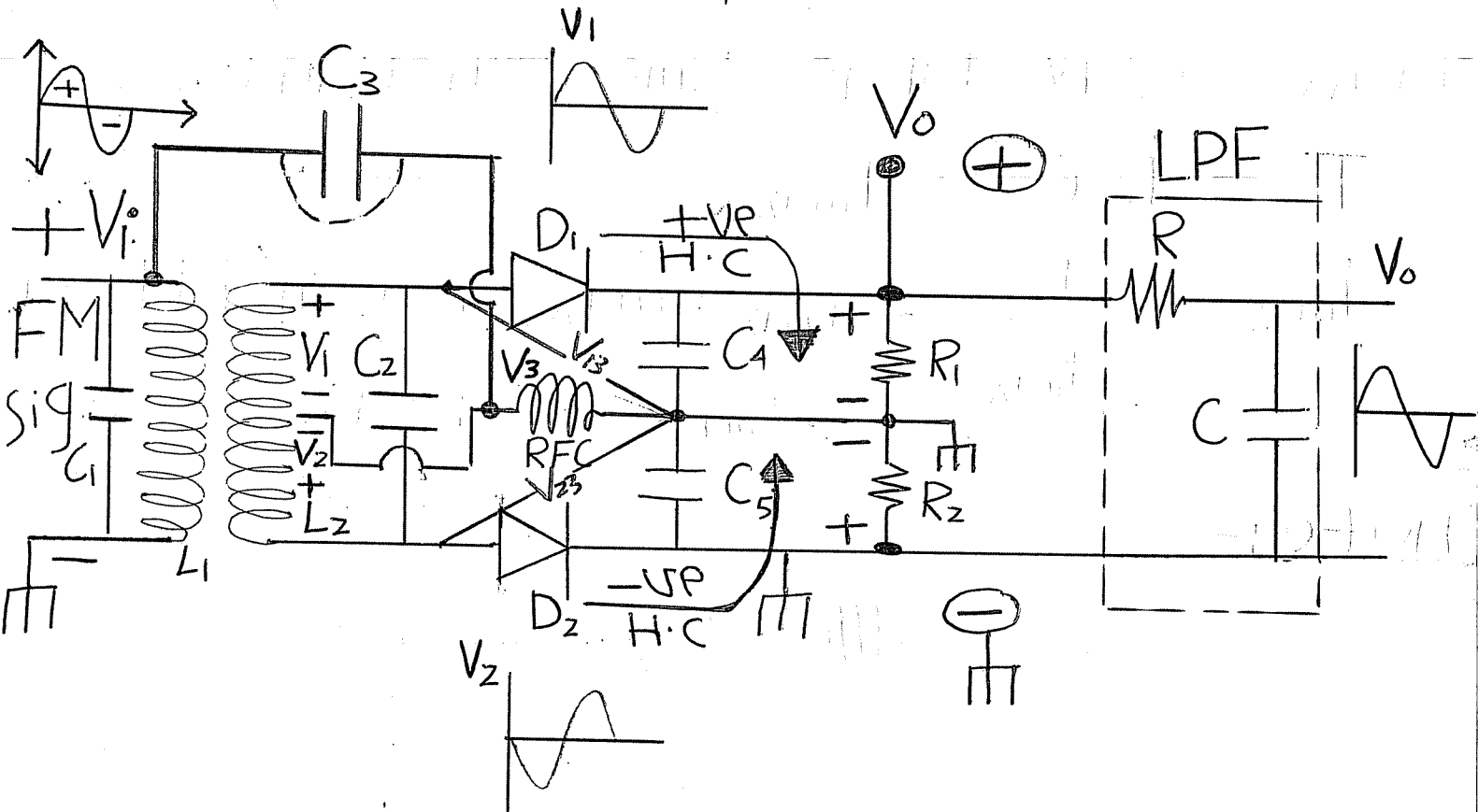

→ C_3 and C_5 are very large, so $V_i = V_3$.

1) For Center Tap Transformer :

V_1 and V_2 are 180° phase shift.

2) For air-core Trans. with Tuned CCT. at primary and secondary, The phase shift between V_i and (V_1 and V_2) is 90°

$$f_c = \frac{1}{2\pi\sqrt{L_1 C_1}} = \frac{1}{2\pi\sqrt{L_2 C_2}}$$

at Resonance :


$(V_1 = V_3)$ is 90° phase Shift with

(V_1) and (V_2) .

1) at $f = f_c$:

$$V_{13} = V_{23}$$


$$\rightarrow V_o = 0$$

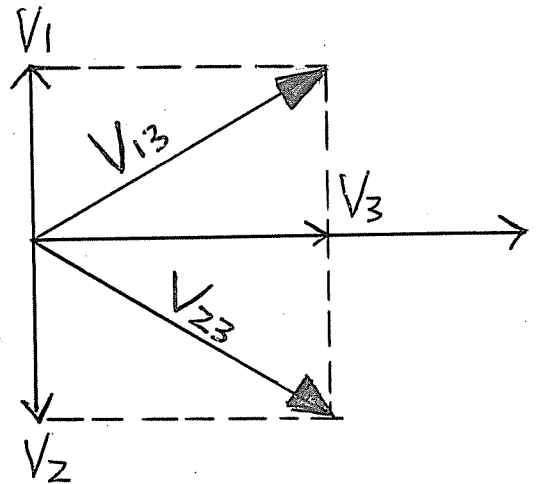

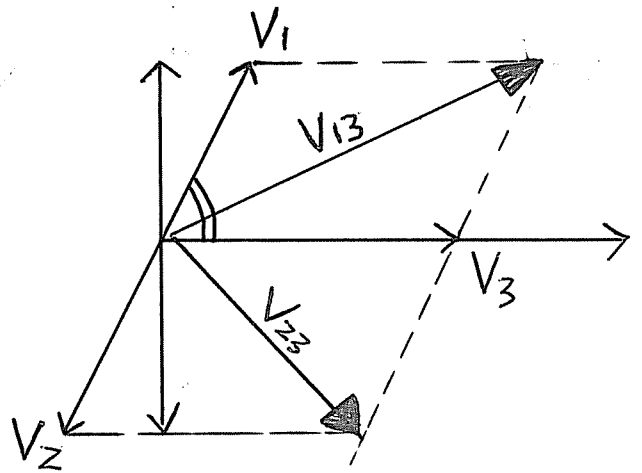2) for $f = f_c + f_d$:

$X_L > X_c$: inductive cct.

V_1 will lead V_3 by less than 90° . (because the Secondary tuned cct. will be inductive)



$$V_{13} > V_{23}$$

So V_o will be +ve.



$$X_L = 2\pi fL$$
$$X_c = \frac{1}{2\pi fC}$$

for $f = f_c - f_d$:

$X_c > X_L$: Capacitive cct.

V_i will lead V_3 by more than 90° .

$V_{23} > V_{13}$
 So V_o will be -ve.

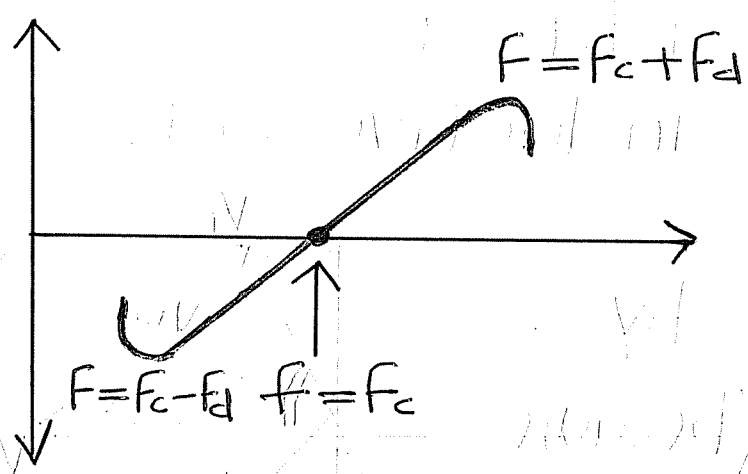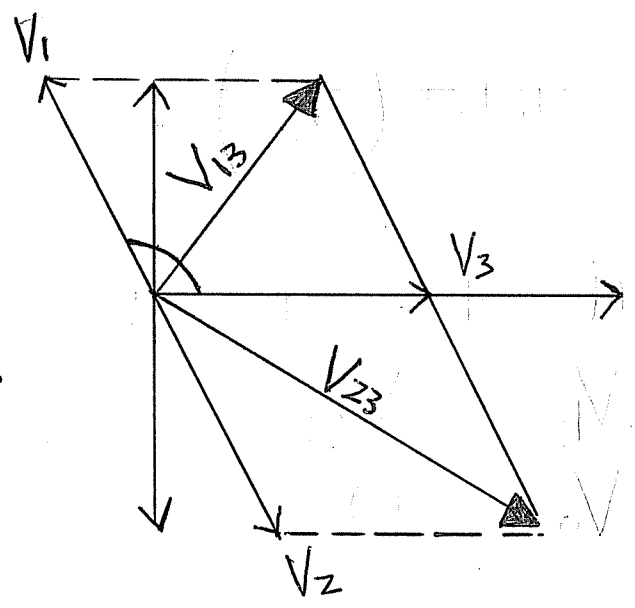

LPF permits only the modulating signal to pass through it

modulating signal فقط LPF

* Foster - Seeley Requires limiter cct. after I.F amp.

* disadvantages : bulky size. - affected by noise.

* not exact o/p
 Preproduced modulating sig.

exact V_m V_o noise FM ← 8

noise : high freq. Component.





↳ interference between

noise and high freq. Component of message signal.

↳ Freq. distortion.

Tx

Rx

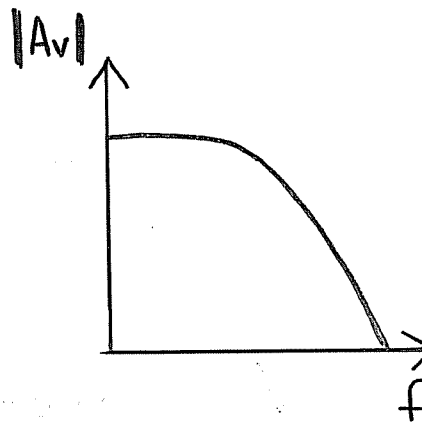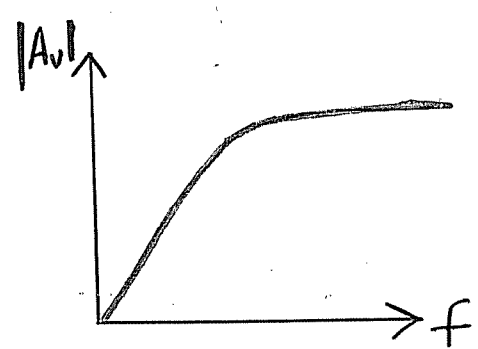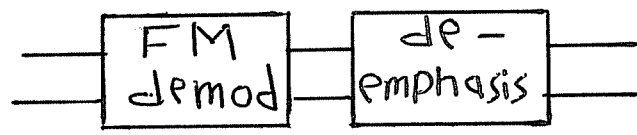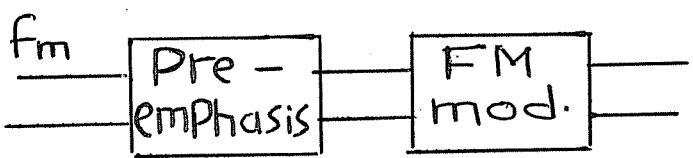


enhancement

offsetting

Pre-emphasis :-

To avoid the effect of Noise (high-freq.) on high freq. Component of message signal and improve $(\frac{S}{N})$ ratio, we use pre-emphasis cct. (Normally HPF) inserted before FM mod. used to enhance high-freq. component and improve $(\frac{S}{N})$ ratio.


The standered cct. :-

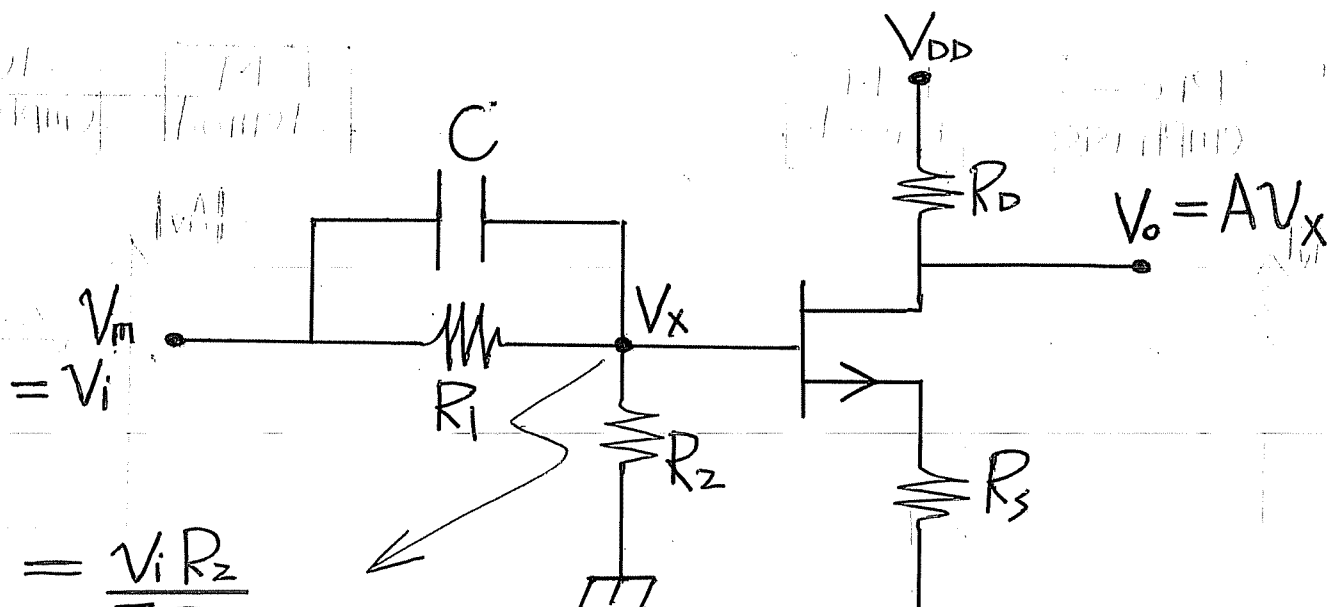

$$* V_x = \frac{V_i R_2}{Z + R_2}$$

$$\rightarrow Z = R_1 \parallel X_c$$

$$* V_o = AV_x$$

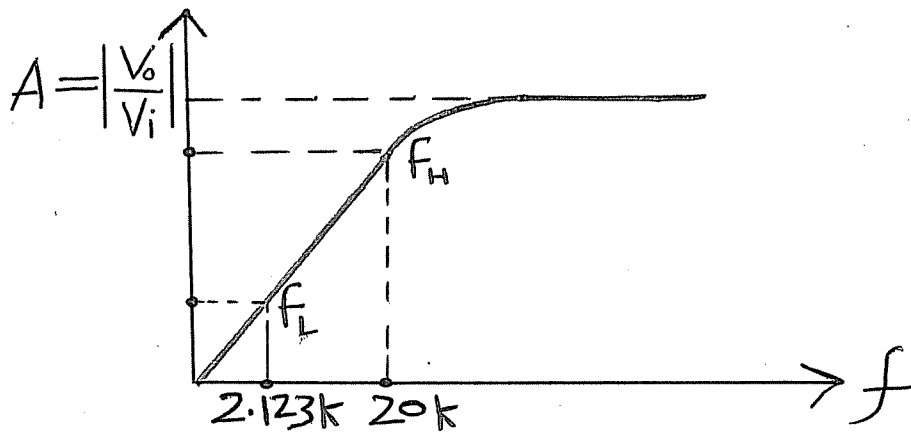

$$f = \infty \rightarrow C \rightarrow \infty \rightarrow \boxed{V_x = V_i}$$

$$\boxed{\frac{V_o}{V_i} = A}$$

$$f_L = \frac{1}{2\pi R_1 C} = 2.123 \text{ kHz} \quad \boxed{R_1 C = \tau = 75 \mu\text{s}}$$


$$f_H = \frac{1}{2\pi R_{eq} C} = 20 \text{ kHz}$$

$$R_{eq} = R_1 \parallel R_2$$

De-emphasis :

To offset the effect of pre-emphasis cct. on message signal and return message - Signal to its Normal level.

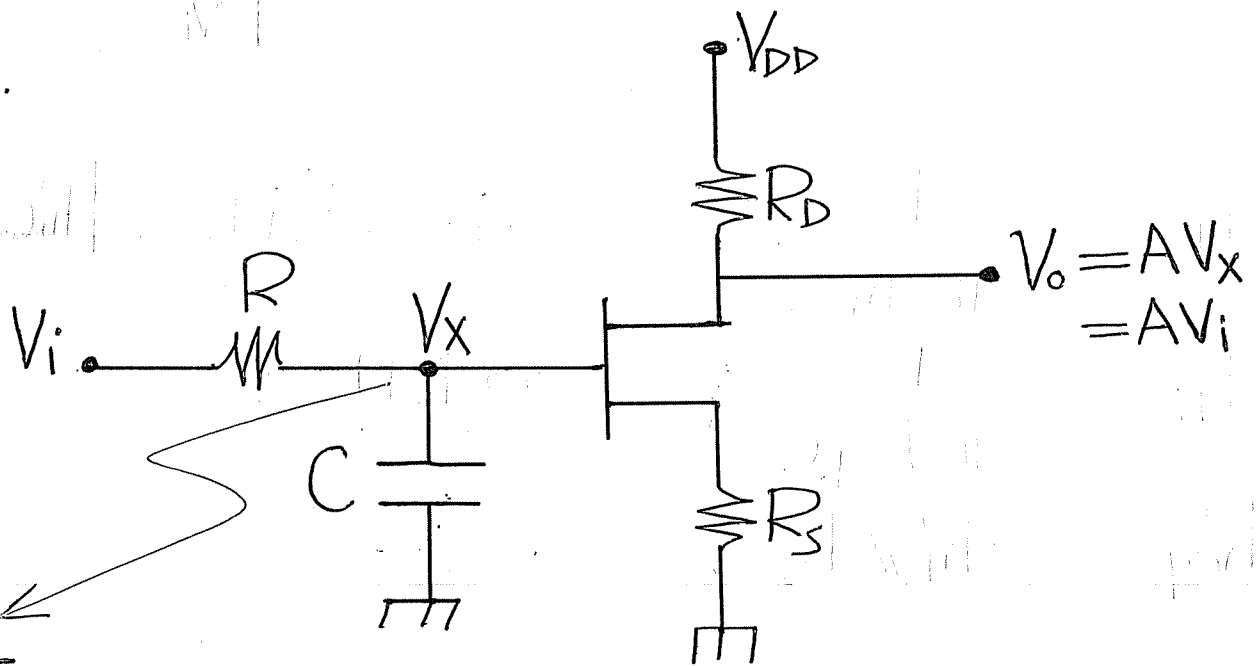
* We use De-emphasis cct. in the R_x and it is a (LPF) Connected in R_x .



$$V_x = \frac{V_i X_c}{R + X_c}$$

$$X_c = \frac{1}{2\pi f C}$$

$$V_x = \frac{V_i}{1 + \frac{R}{X_c}}$$


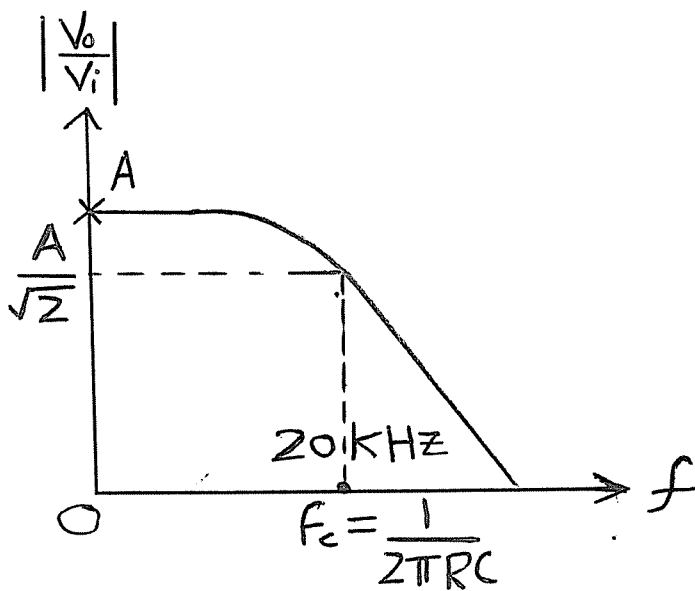


$$\frac{V_o}{V_i} = AV_x = \frac{AV_i X_c}{X_c + R}$$



$$V_x = \frac{A}{\sqrt{1 + \left(\frac{R}{X_c}\right)^2}}$$

$$\hookrightarrow \frac{R}{X_c} = 1 \rightarrow 1 = 2\pi f RC$$


$$f = \frac{1}{2\pi RC}$$

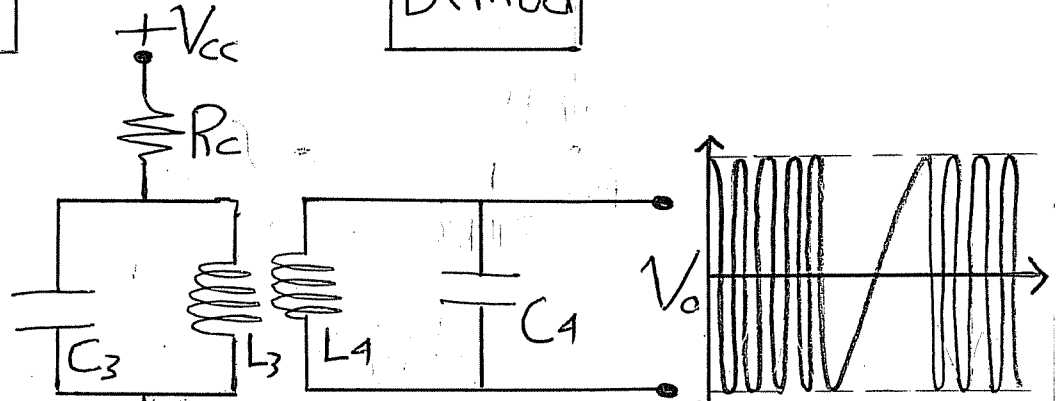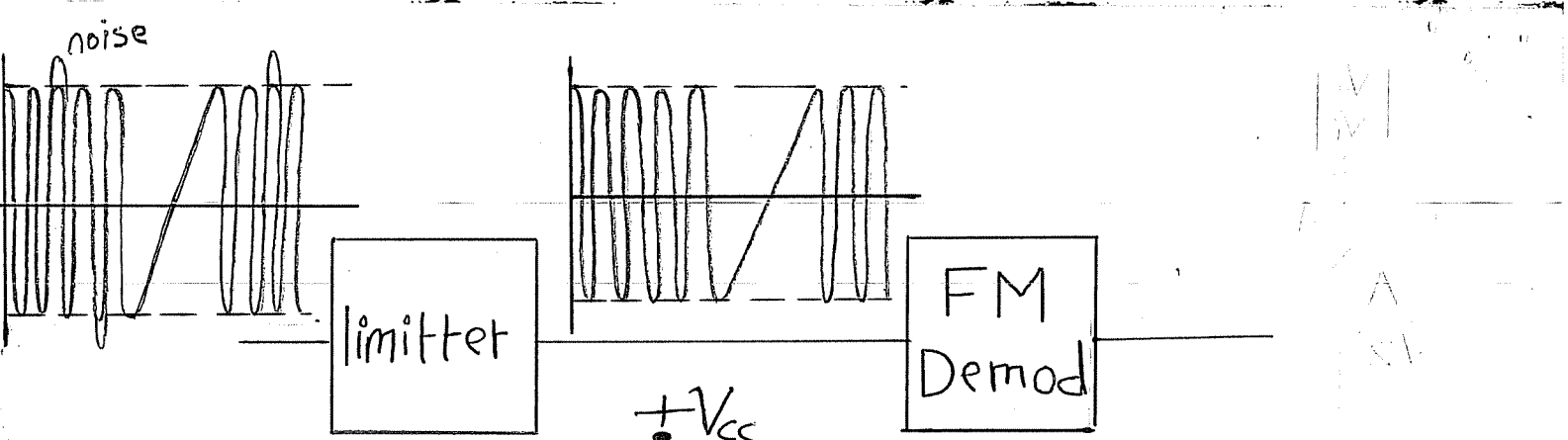

تردوتة على 10.7 MHz.

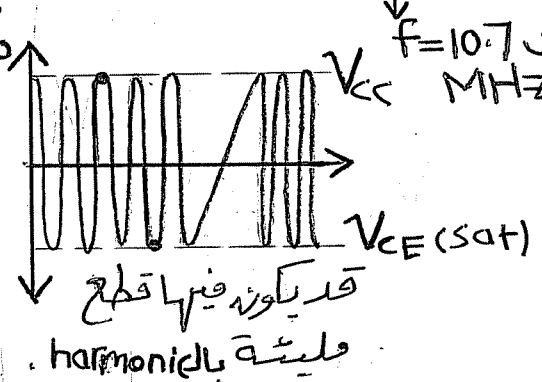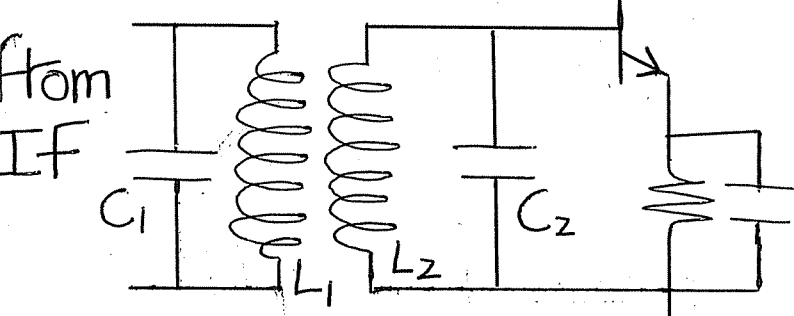
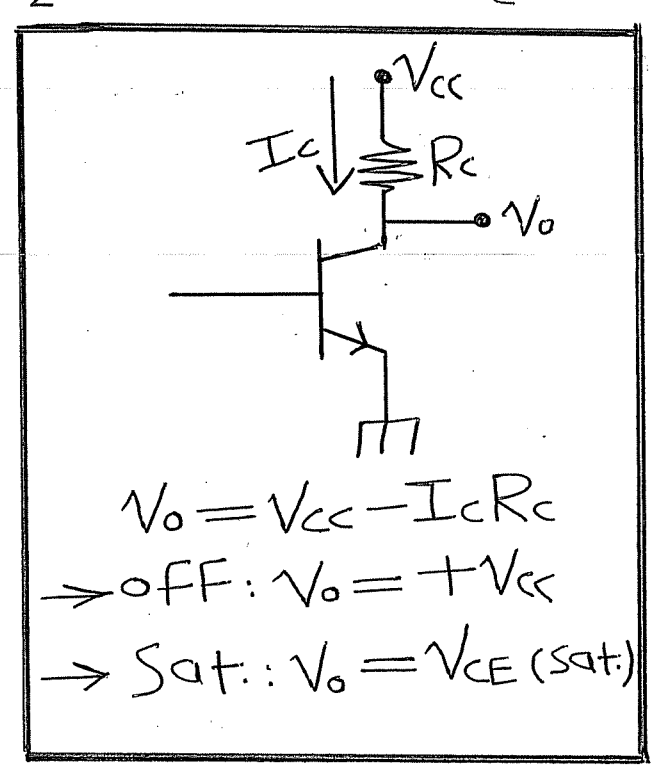
$$f_t = \frac{1}{2\pi\sqrt{L_1 C_1}} = \frac{1}{2\pi\sqrt{L_2 C_2}} = f_{IF} = \underline{\underline{10.7 \text{ MHz}}}$$



$$V_o = V_{cc} - I_c R_c$$

→ off: $V_o = +V_{cc}$

→ Sat.: $V_o = V_{CE(sat)}$

Limiter : a CCT. which gives a Constant amplitude output , Normally it is a Transistor CCT. biased to work a Switch giving $V_o \rightarrow \boxed{V_{CE(sat)} \rightarrow V_{cc}}$. The Output is Taken from parallel Tuned CCT. resonant at :

$$f_r = \frac{1}{2\pi\sqrt{L_3 C_3}} = \frac{1}{2\pi\sqrt{L_4 C_4}} = f_{IF} = 10.7 \text{ MHz}$$

→ Transmitter :

AM → pre-emp. لا يوجد *

FM → pre-emp. يوجد *

→ Receiver :

AM → limiter لا يوجد / De-emp. لا يوجد *

FM → limiter يوجد / De-emp. يوجد *

The first part of the work is devoted to the study of the properties of the function $f(x)$ defined on the interval $[0, 1]$. It is shown that $f(x)$ is continuous and differentiable almost everywhere. The derivative of $f(x)$ is zero almost everywhere, but the function is not constant. This is a classic example of a function that is differentiable almost everywhere but whose derivative is zero almost everywhere.

2. Theorem 1

Let $f(x)$ be a function defined on the interval $[a, b]$. If $f(x)$ is differentiable almost everywhere and $f'(x) = 0$ almost everywhere, then $f(x)$ is constant almost everywhere.



Proof. Let E be the set of points where $f(x)$ is not differentiable. Then E has measure zero. Let F be the set of points where $f'(x) \neq 0$. Then F also has measure zero.

Let G be the set of points where $f(x)$ is not constant. Then G has measure zero.


Let H be the set of points where $f(x)$ is not differentiable and $f'(x) \neq 0$. Then H has measure zero.





Let I be the set of points where $f(x)$ is not constant and $f'(x) = 0$. Then I has measure zero.

Phase Modulator :-

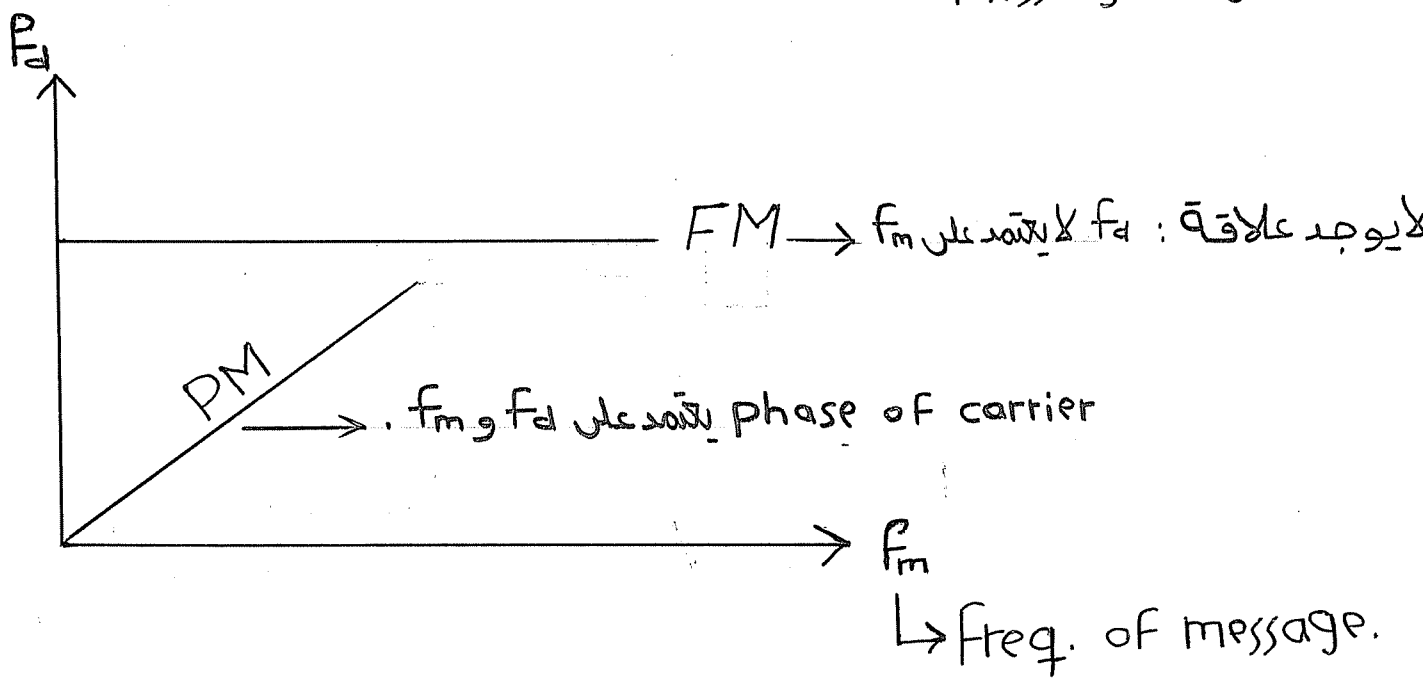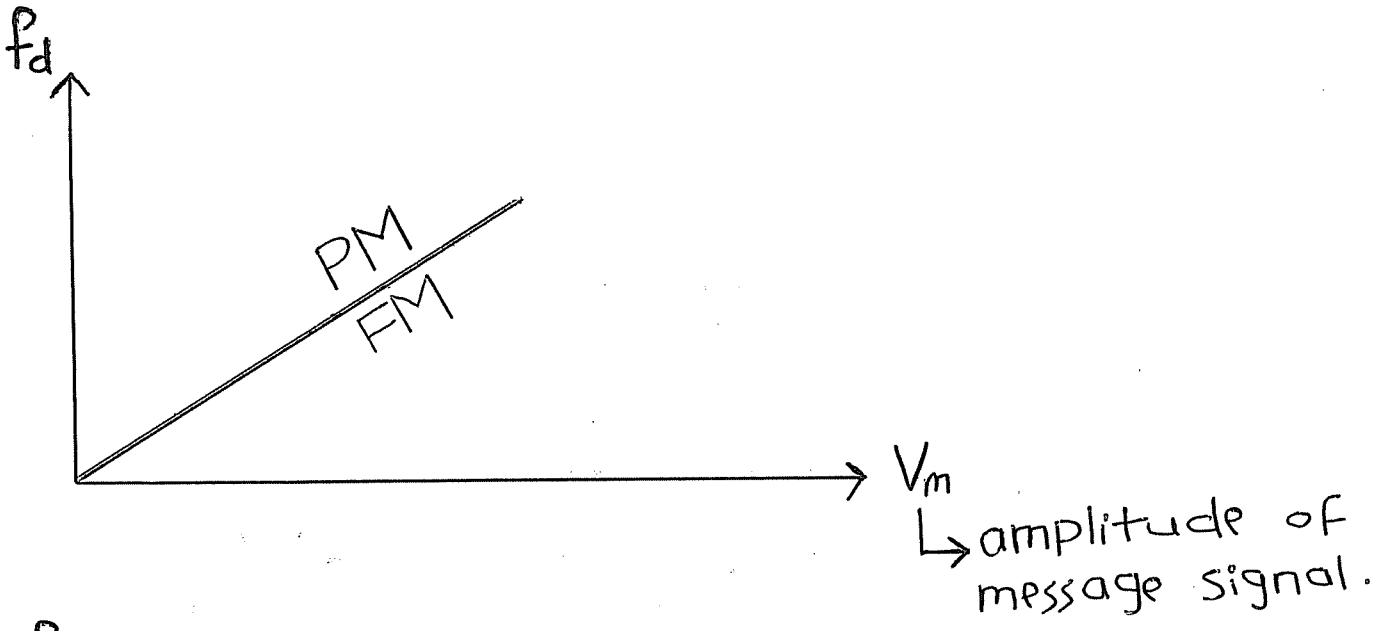

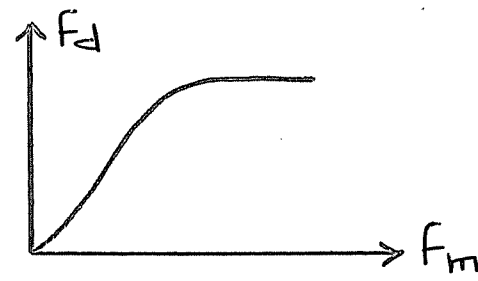high freq. component of modulating signal ; gives $f_d \uparrow$



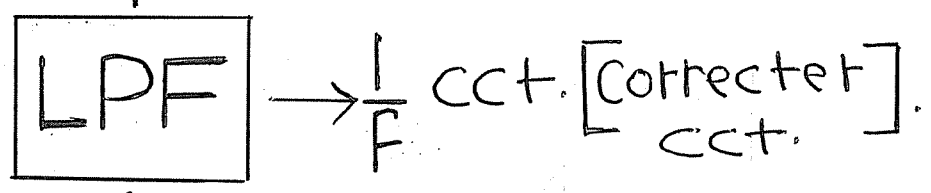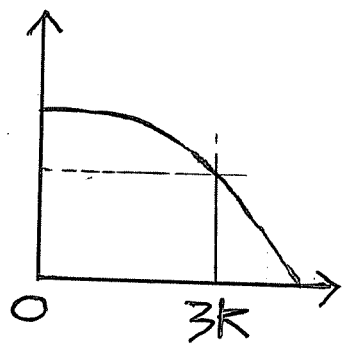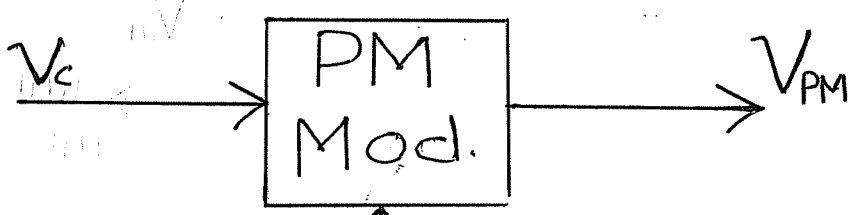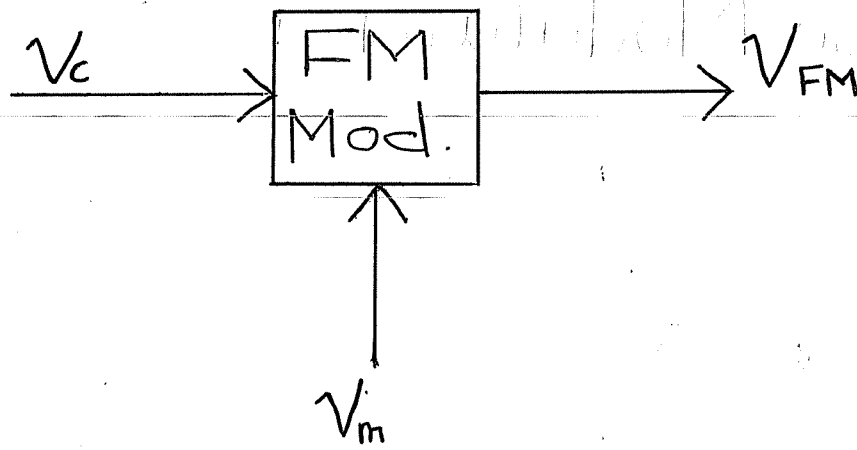


to generate FM from PM, we use

freq. correcting net. #

it is simply a LPF connected between message signal and phase modulator. (indirect generation).

Indirect generation of FM Signal :

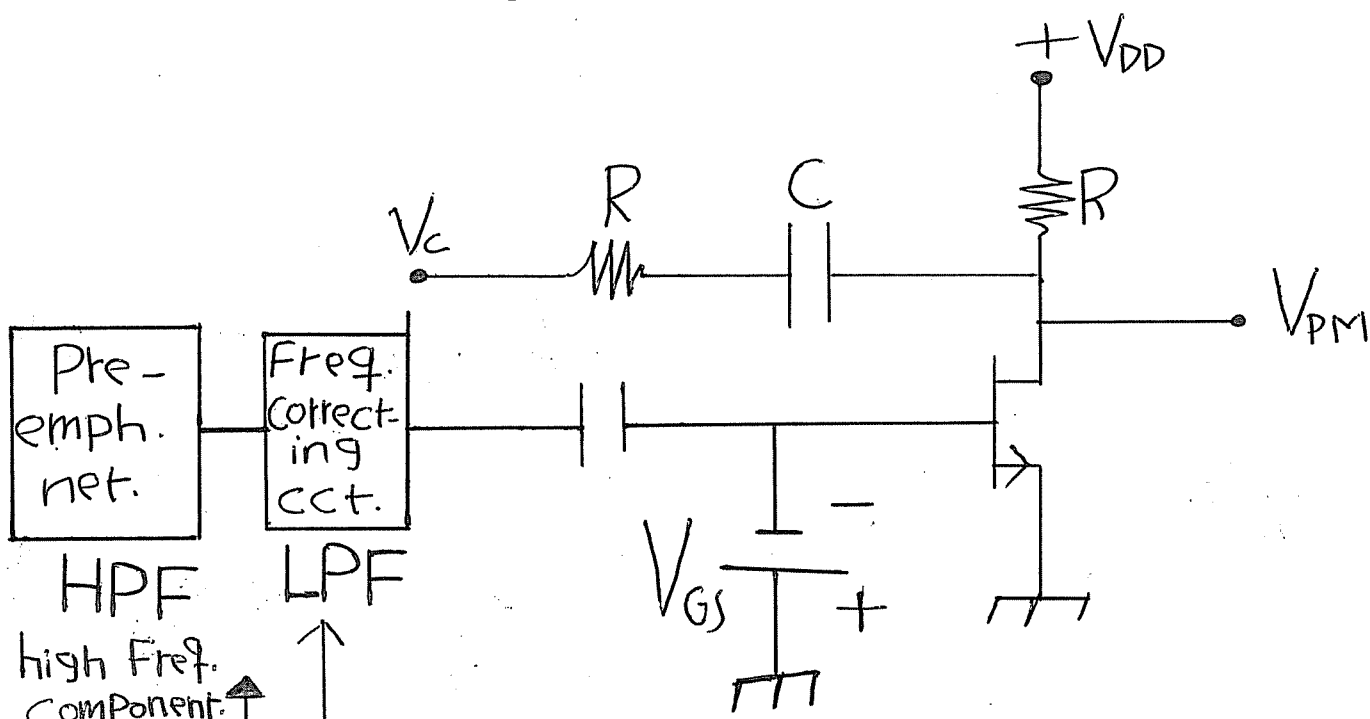


HPF
high Freq.
Component. ↑

LPF
Low freq.
component.
↓
high Freq.
component.


Armstronge
FM generator.

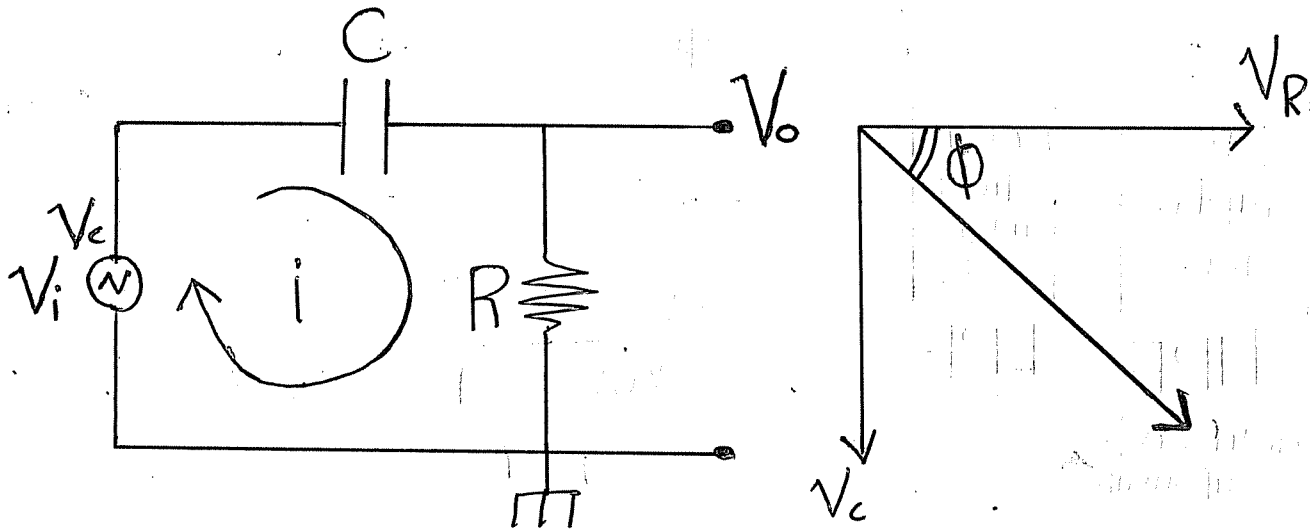Phase Mod :- Changing the phase of Carrier according to amp. of modulating signal.





$$\phi = \tan^{-1} \frac{V_c}{V_R}$$

$$= \tan^{-1} \frac{X_c}{R}$$

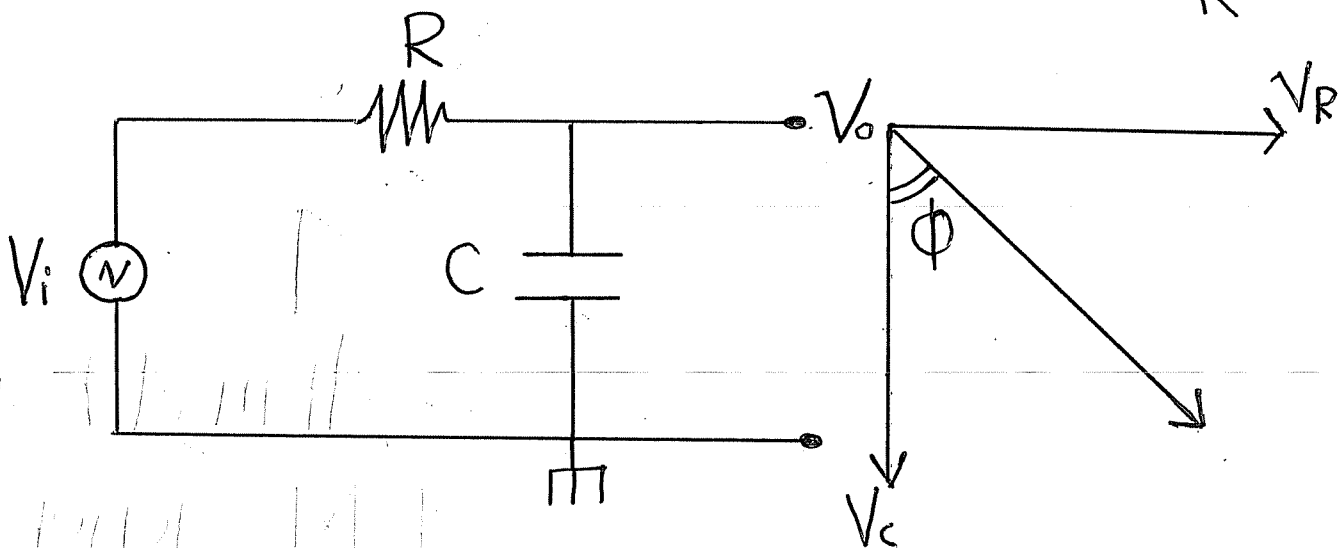


$$\phi = \tan^{-1} \frac{R}{X_c}$$

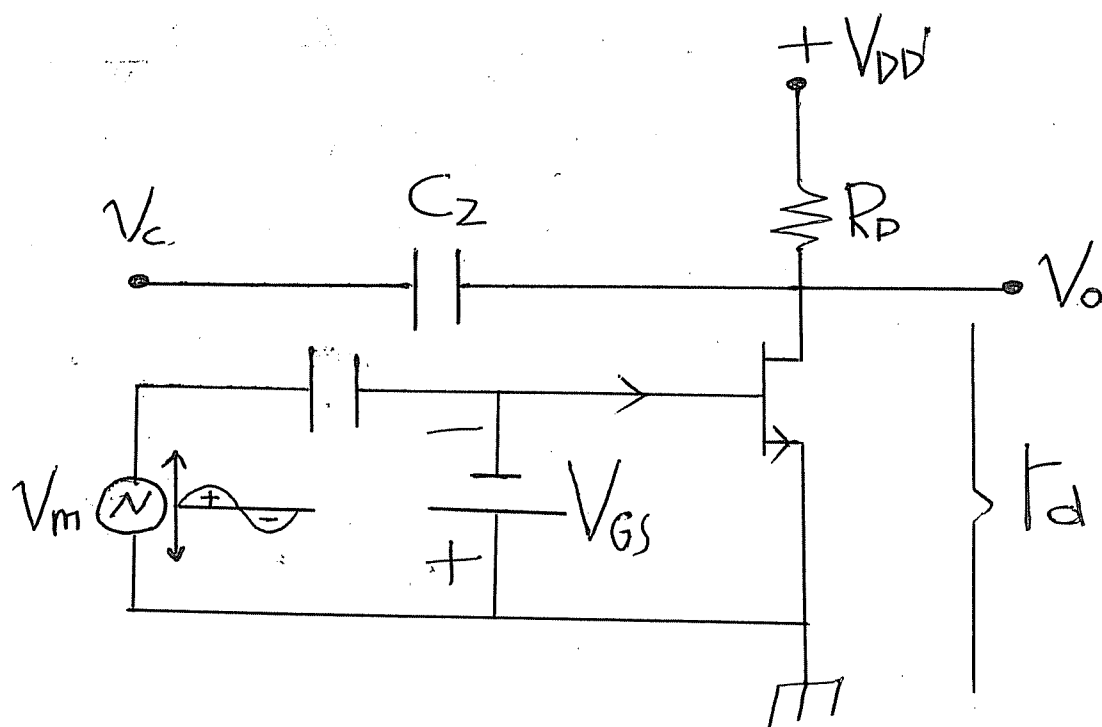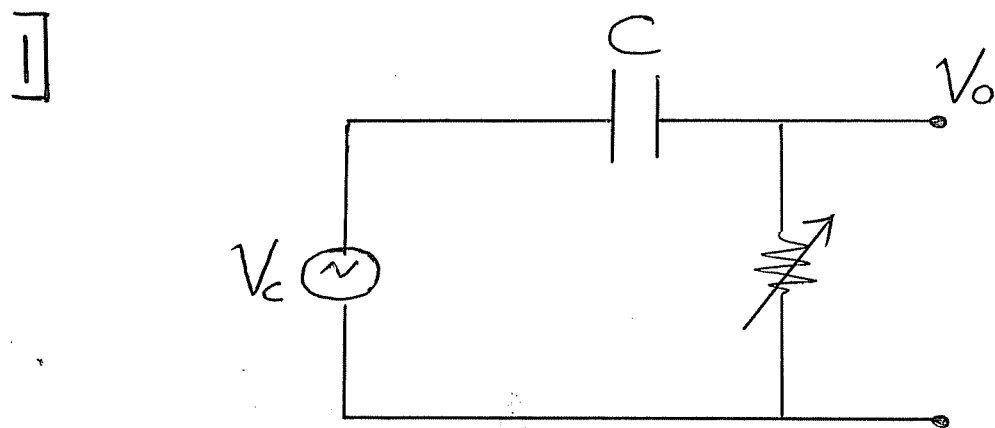To produce PM, ϕ must be changed according to Amp. of message signal.



The J-FET will be biased at linear

Regn. . $r_d \propto \frac{1}{V_{GS}}$.

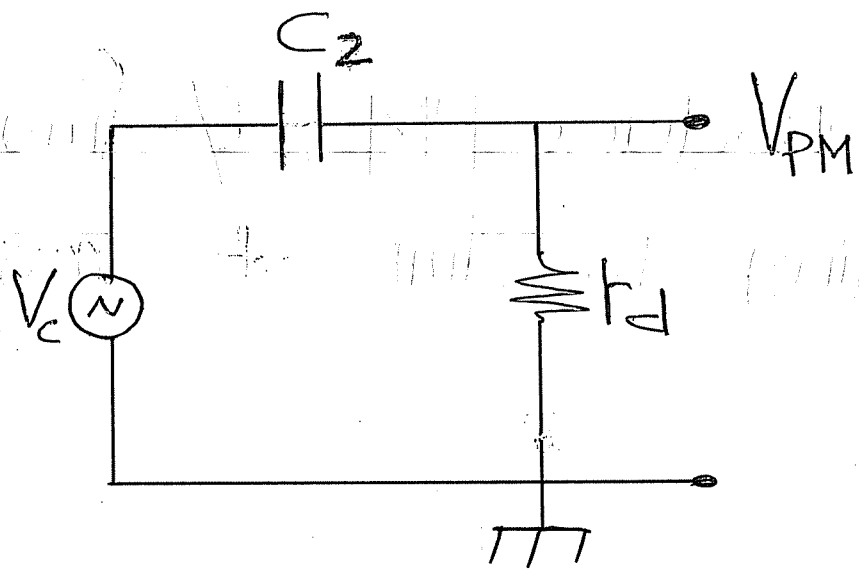

$$\tan^{-1} \frac{X_{C_2}}{r_d}$$

- i. when V_m increase ; $V_{GS} \uparrow$, $r_d \downarrow$, $\phi \uparrow$.
 - ii. when V_m decrease ; $V_{GS} \downarrow$, $r_d \uparrow$, $\phi \downarrow$.
- i.e the phase of carrier increase and decrease according to Amp. of modulating signal. (Producing phase - modulation).

$C_1 \rightarrow$ Coupling and blocking for dc.

\rightarrow Short cct. for Carrier.


$C_2 \rightarrow$ blocking for dc.

\rightarrow Short cct. for modulating signal.


2]

Very high Value (blocking dc)

blocking dc and S.c for carrier (V_c)

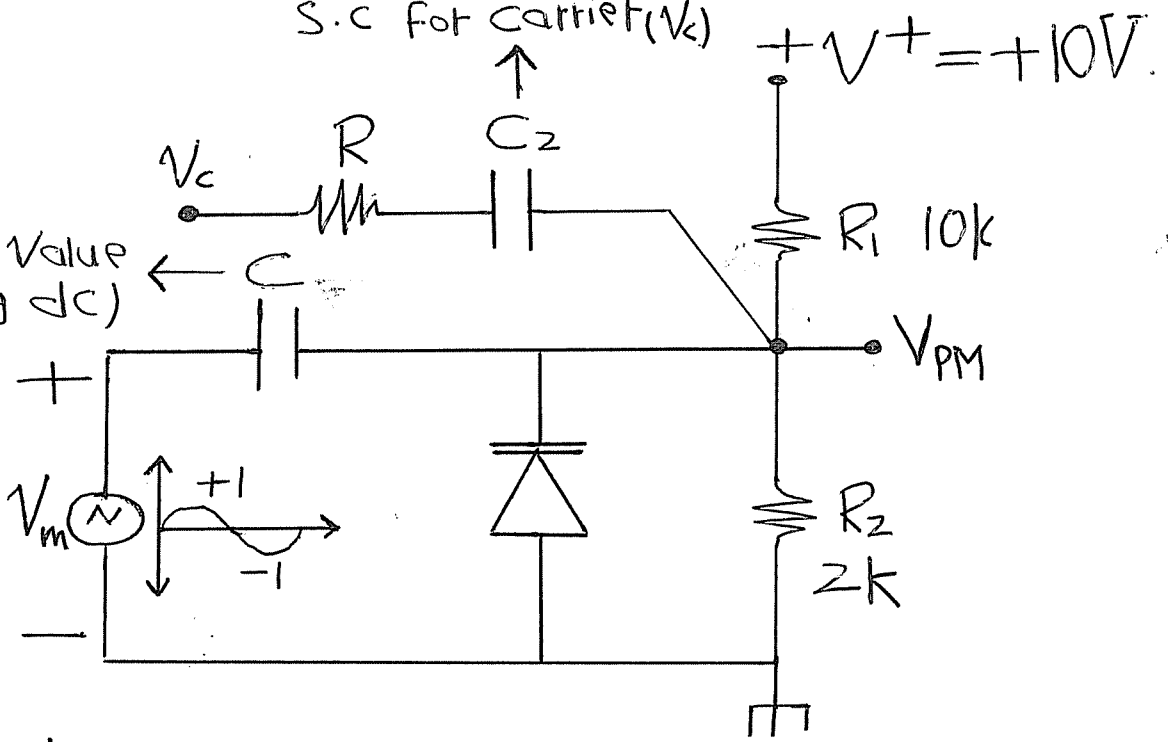

$$C_D = \frac{1}{R}$$

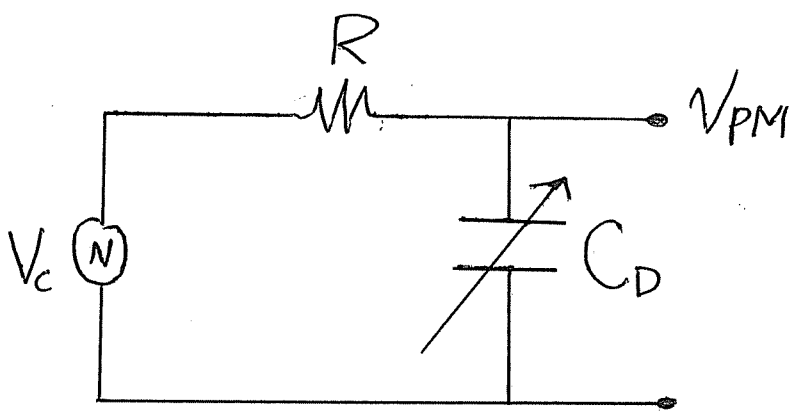

$$\phi = \tan^{-1} \frac{R}{X_{CD}}$$

i) when V_m increase, $V_R \uparrow$, $C_D \downarrow$, $X_{CD} \uparrow$, $\phi \downarrow$.

ii) when V_m decrease, $V_R \downarrow$, $C_D \uparrow$, $X_{CD} \downarrow$, $\phi \uparrow$.

iii) i.e the phase of carrier is Changing

according to Amp. of message Signal Such that

$V_m \uparrow$, $\phi \downarrow$, and $V_m \downarrow$, $\phi \uparrow$.


Q.11) (a) $\phi \uparrow$ with $v_m \uparrow$ and $\phi \downarrow$ with $v_m \downarrow$

To solve this problem and make $\phi \uparrow$ with $v_m \uparrow$ and $\phi \downarrow$ with $v_m \downarrow$, we have to use inverting Amp. with v_m .

- (i) $\phi \downarrow$ with $v_m \downarrow$
- (ii) $\phi \uparrow$ with $v_m \uparrow$
- (iii) $\phi \downarrow$ with $v_m \downarrow$
- (iv) $\phi \uparrow$ with $v_m \uparrow$

Single Side Band Mod. (SSB) :

* Conventional AM :

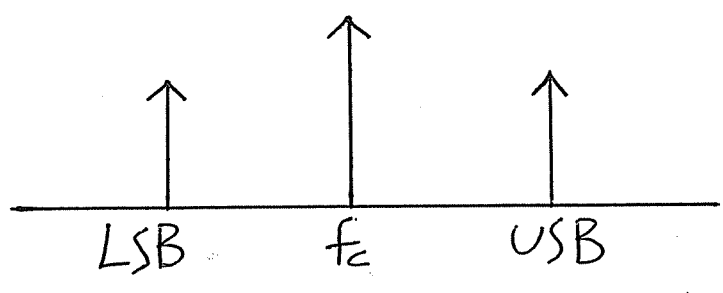

for max. mod. index $m = 1,$

$$P_c = \frac{2}{3}, \quad P_{USB} = P_{LSB} = \frac{1}{6}.$$

$$\therefore P_T = 6W \rightarrow P_c = 4W, \quad P_{USB} = P_{LSB} = 1W.$$

$$(Bw) = 2f_m.$$


Double Side band Sub. Carrier

- 1) filter method.
- 2) Phasing method. (phase shifter 90°).


Single Side band Sub. Carrier.

SSB Generation :-


1) Filter Method :-

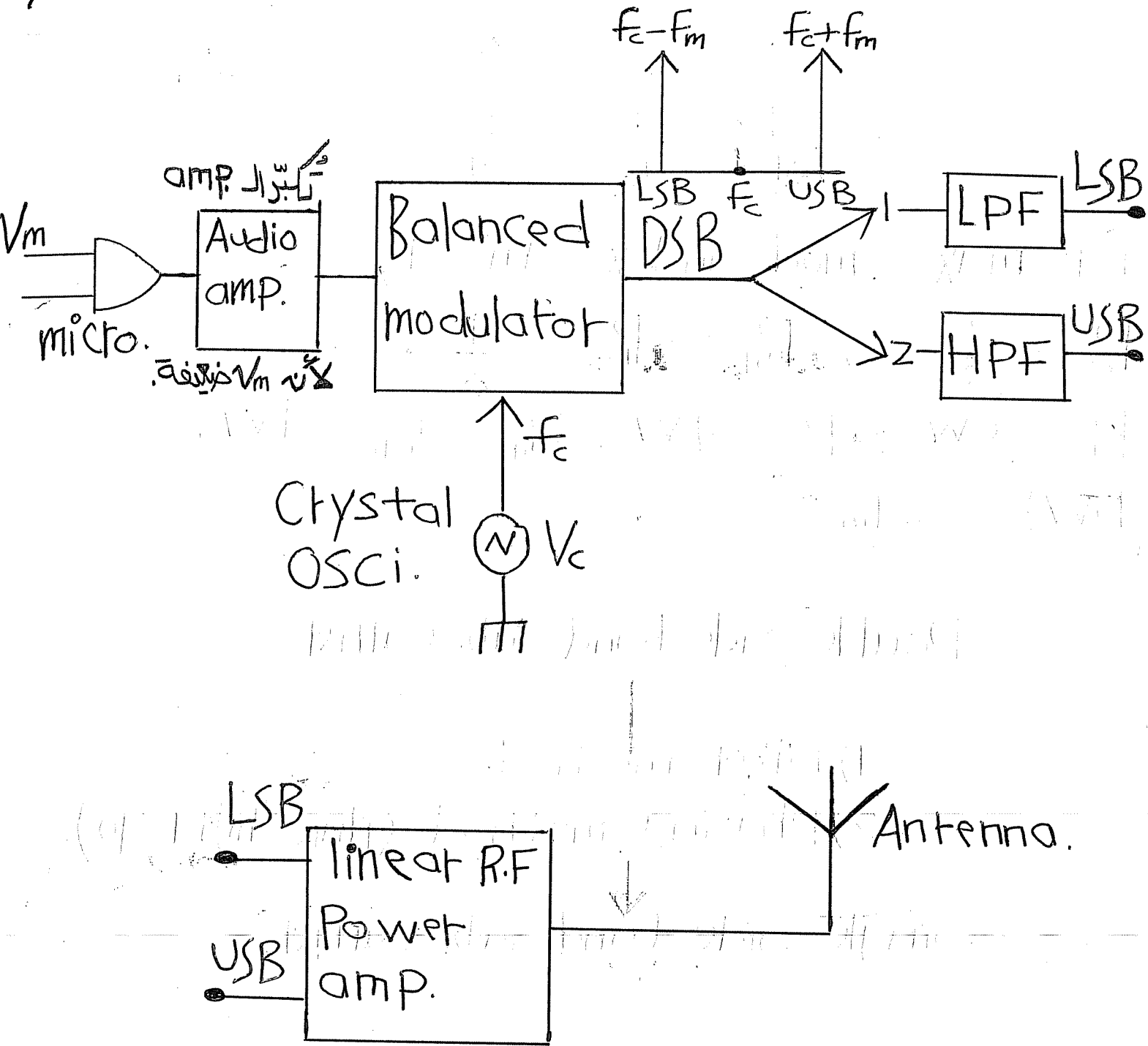

2) Phase - Shift method :-

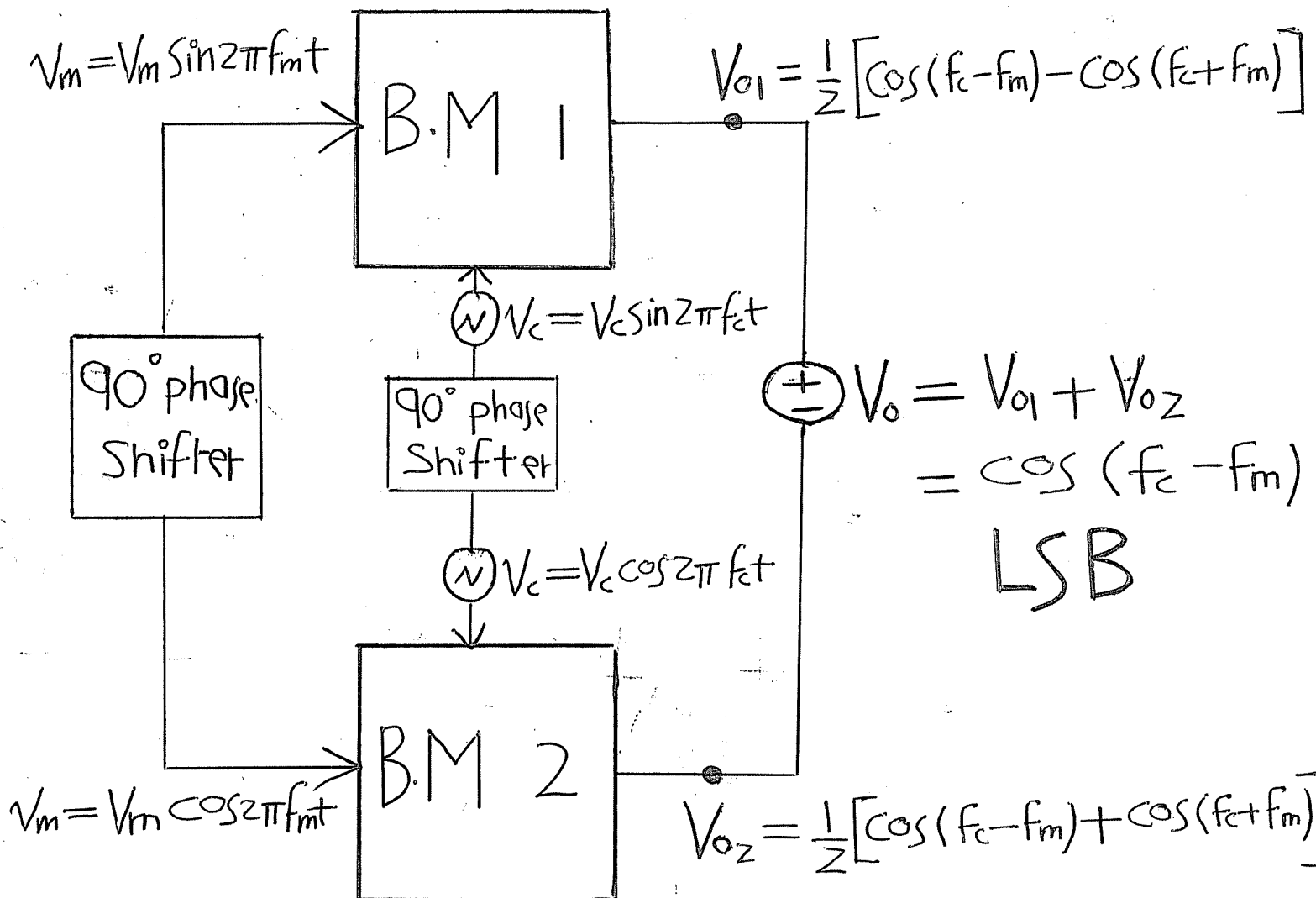

Balanced Mod. :-

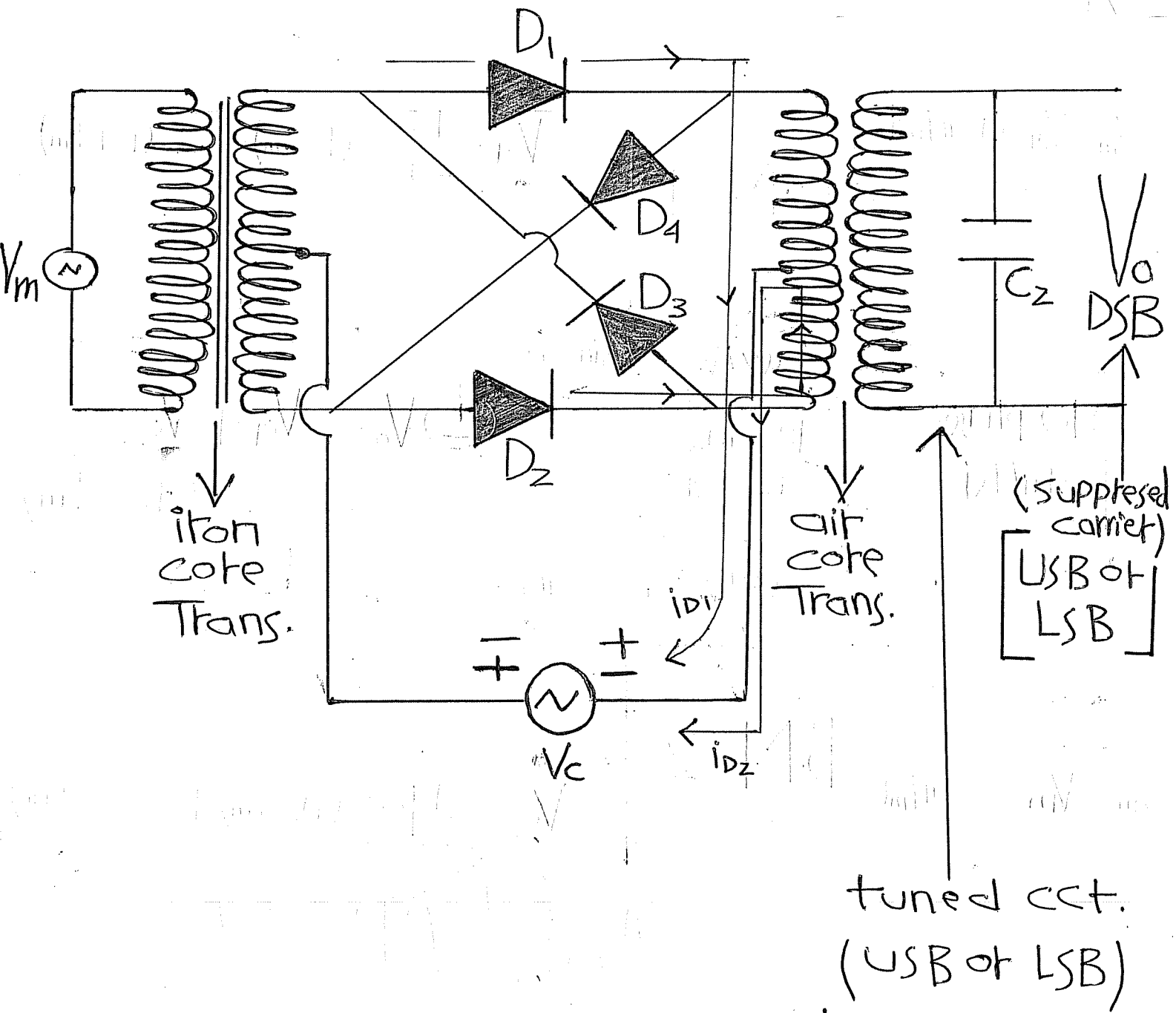

$$f_T = \frac{1}{2\pi\sqrt{L_2 C_2}} \quad \text{: تونیا}$$

$$= \text{USF or LSF.}$$

1) For $V_m = 0$, only V_c is applied.

a) for +ve H.C of V_c :

D_1 and $D_2 \rightarrow$ ON.

D_3 and $D_4 \rightarrow$ OFF.

$i_{D_1} = -i_{D_2}$ will flow in primary of T_2 and

Since i_{D_1} opposes i_{D_2} , So they will

Produce equal and opposite flux, and

the resultant flux = 0, Therefore the

O/P voltage will be zero. (No carrier).

b) for -ve H.C of V_c :

D_1 and $D_2 \rightarrow$ off.

D_3 and $D_4 \rightarrow$ ON.




$i_{D_3} = -i_{D_4}$ will flow in primary of T_2 and

Since i_{D_3} opposes i_{D_4} , So they will produce

equal and opposite flux, and the

resultant flux = 0, Therefore the O/P

voltage will be zero. (No carrier).

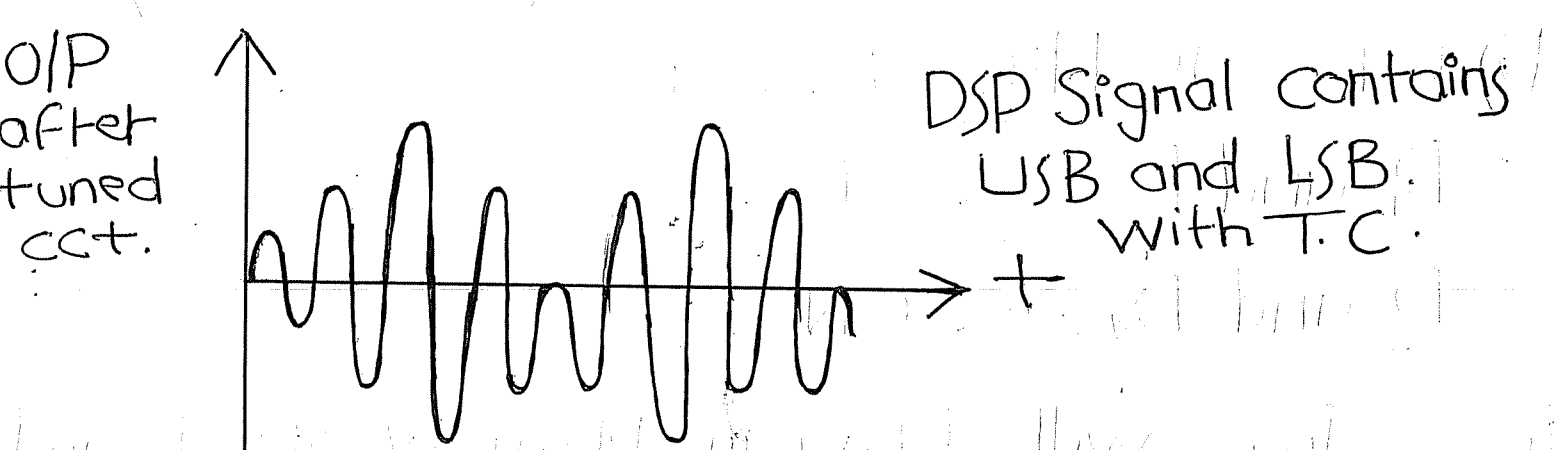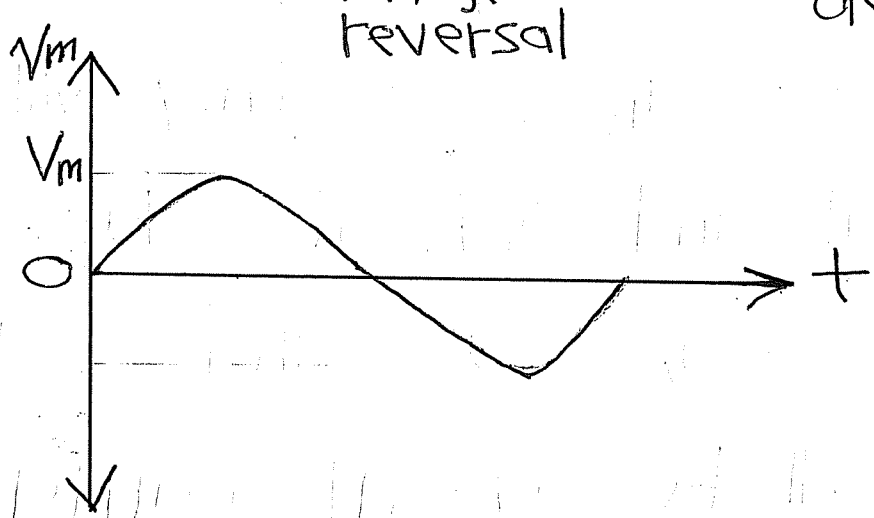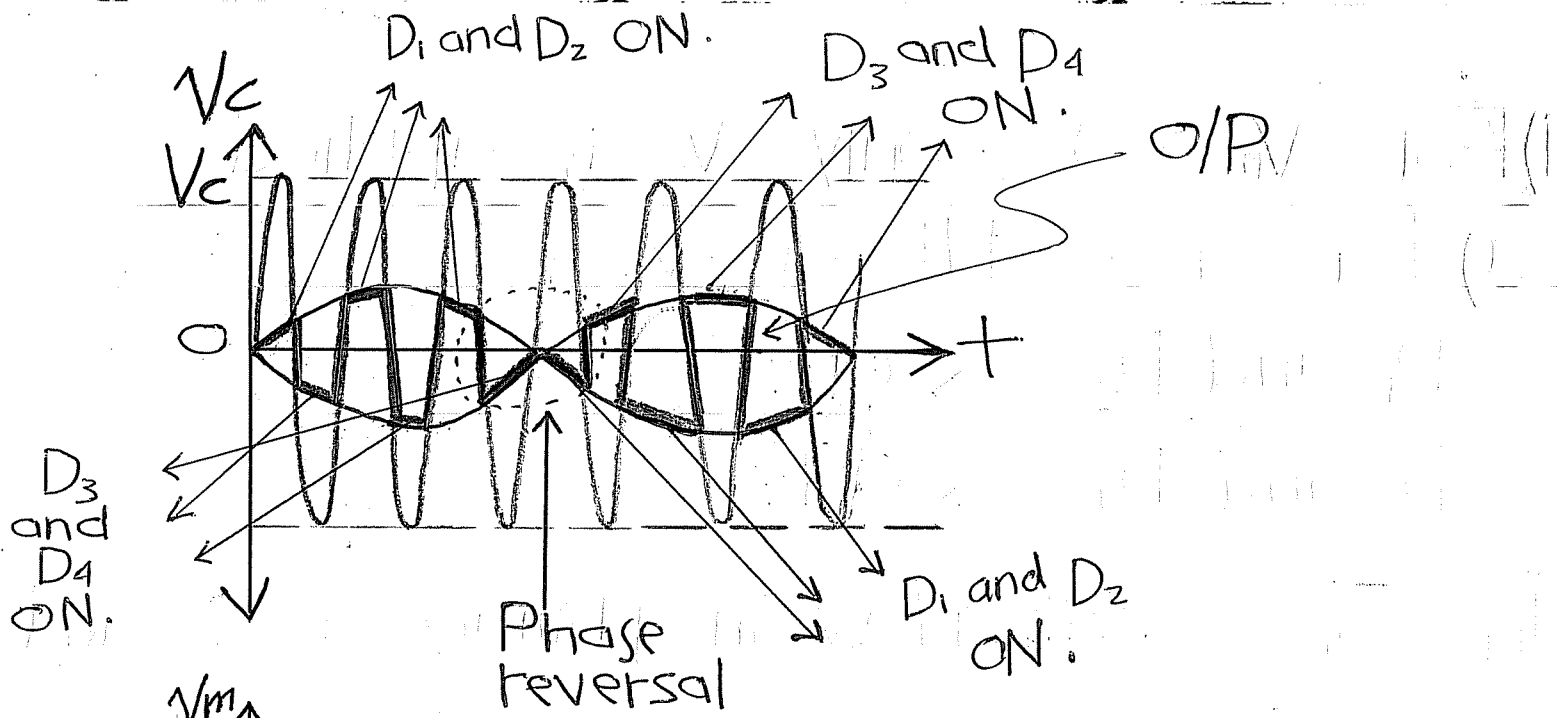

$V * f = f_c \rightarrow$ Carrier controls the speed of diodes.
 (make diodes ON or OFF)

* amplitude = amplitude of modulating signal.

$T_i \rightarrow$ bulk size (iron core) large inductors.

$V_m \rightarrow$ small value.

To improve the performance of this modulator, we can replace the i/p iron core Trans. (T_1) by air core Trans.

and interchange the position of V_m and V_c .



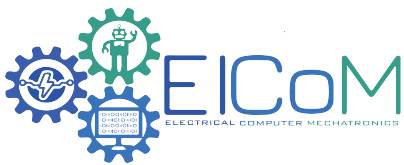


Figure 4-25 Waveforms in the lattice-type balanced modulator. (a) Carrier. (b) Modulating signal. (c) DSB signal—primary T_2 . (d) DSB output.

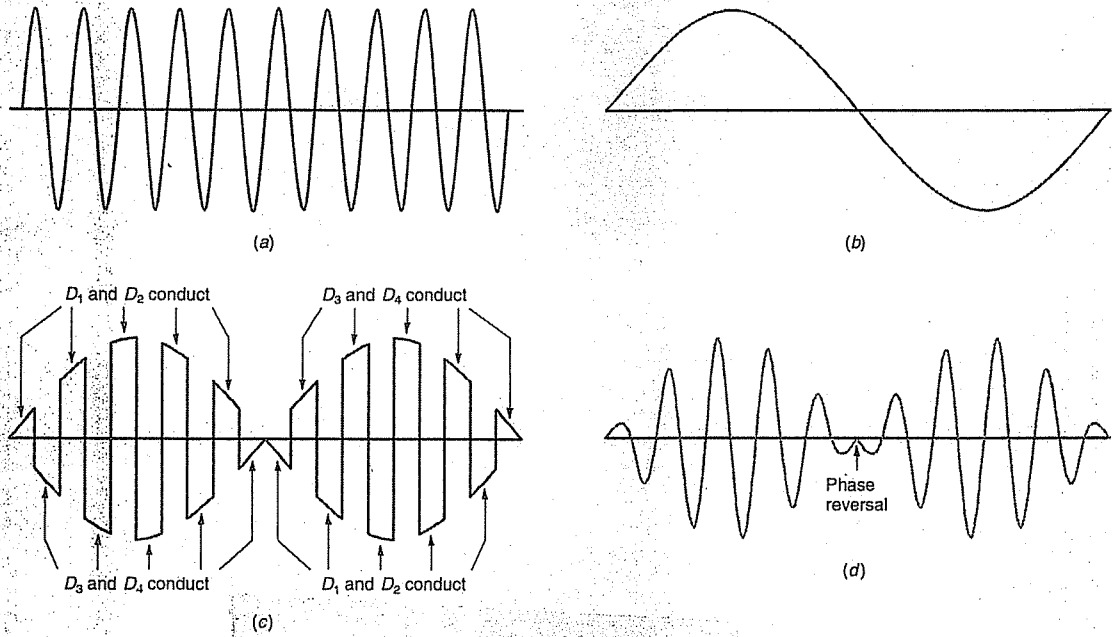


Lattice Balanced modulator

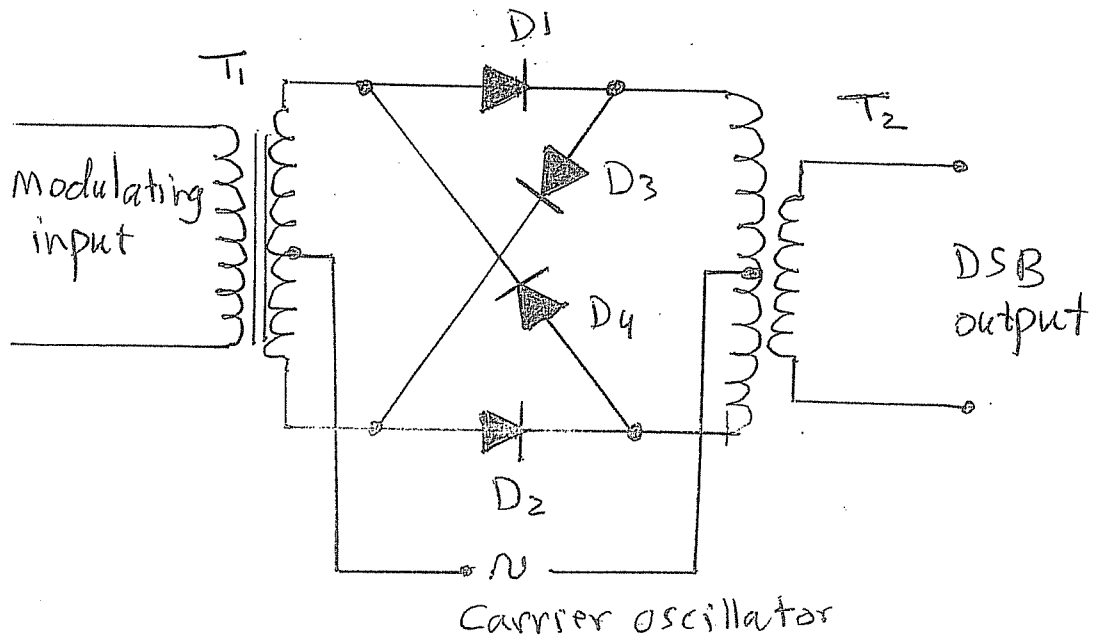


SSB Reception :-

$$f_c = 500 \text{ kHz} \rightarrow f_m = 2 \text{ kHz}$$

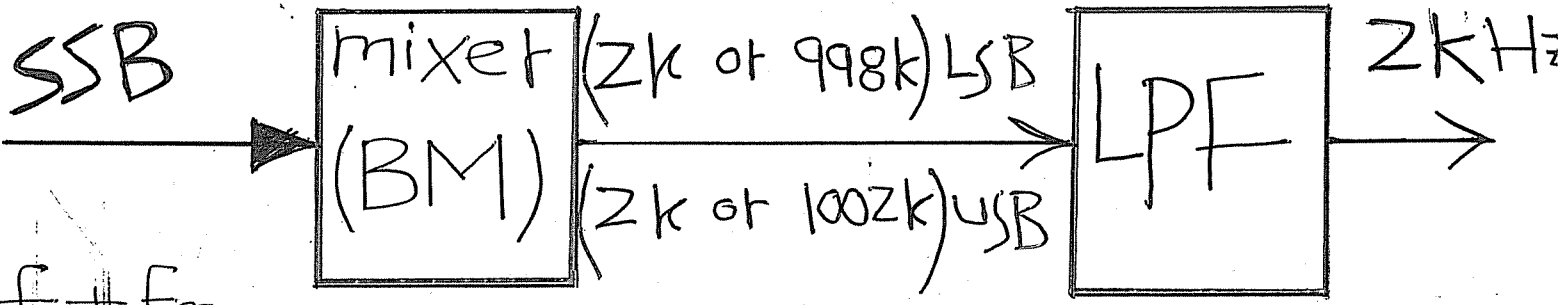
$$f_c - f_m = \underline{498 \text{ kHz}} \text{ LSB}$$


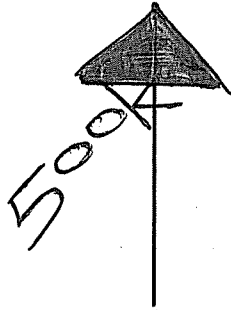
$$f_c + f_m = \underline{502 \text{ kHz}} \text{ USB}$$




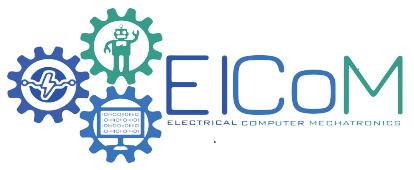freq. تکون Beat
 • f_c نوس Freq. Osc.
 BFO



SSB Receiver :-

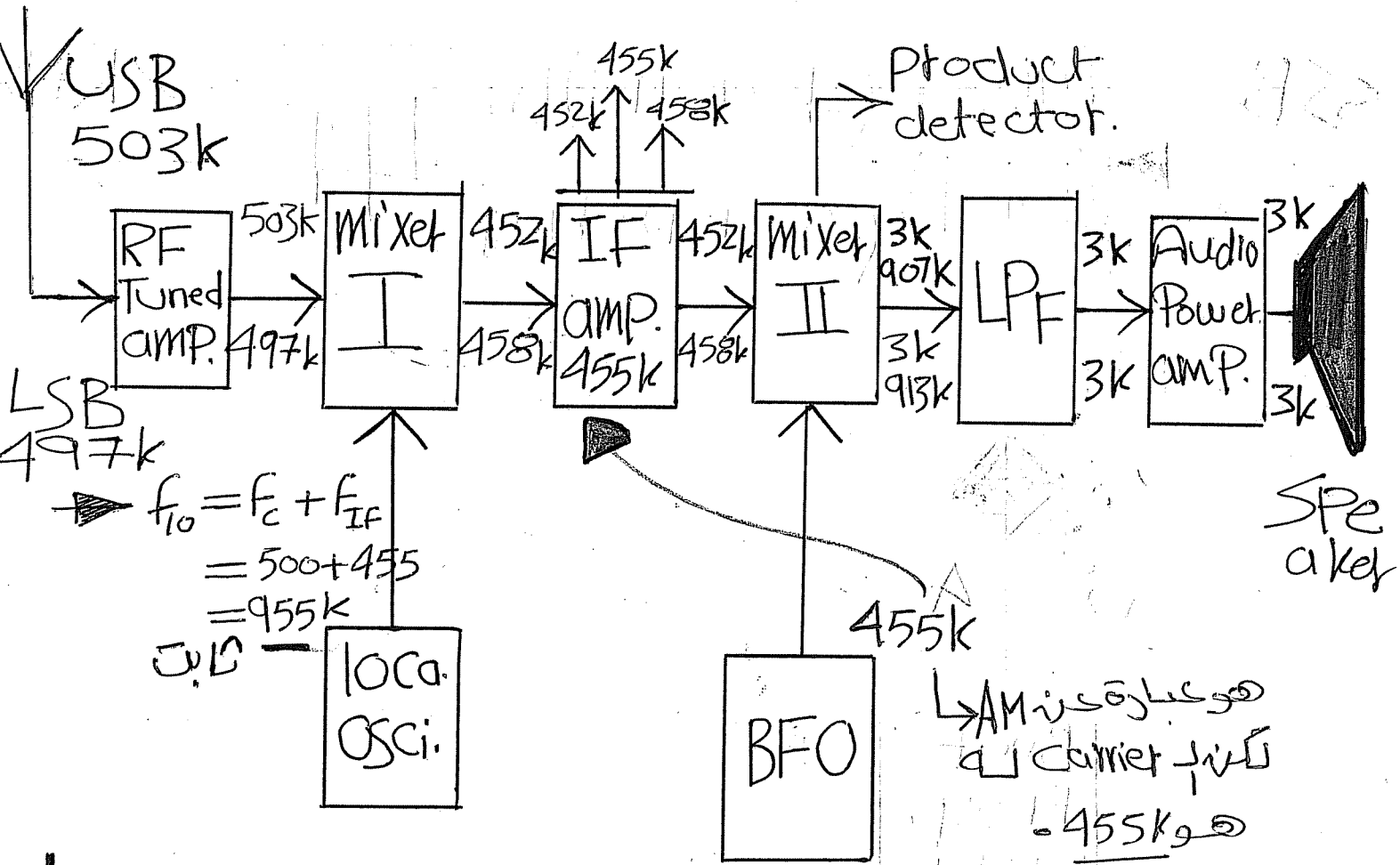$f_c = 500\text{K}$, $f_m = 3\text{KHz}$.



* determine frequencies at the i/p of each stage :-

- (i) when we receive LSB.
- (ii) when we receive HSB.

Comm. Electronics Tutorial Sheet. No. 4.
Dr. Hadi Al-Ithawi


Q1) Name the circuit (X) $C = 7.5 \text{ nF}$

shown in Fig. 1?

explain its function.

and sketch its freq. Resp?

calculate its Cutoff freq?

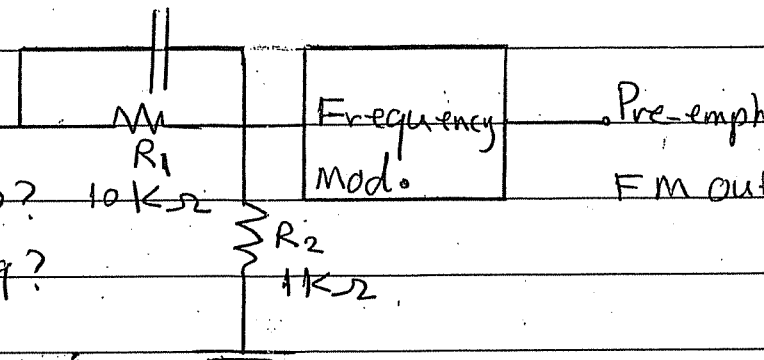

Ans


Q2) Name the circuit (X) ? V (X)

shown in Fig. 2.

explain its function

and sketch its Bode plot?

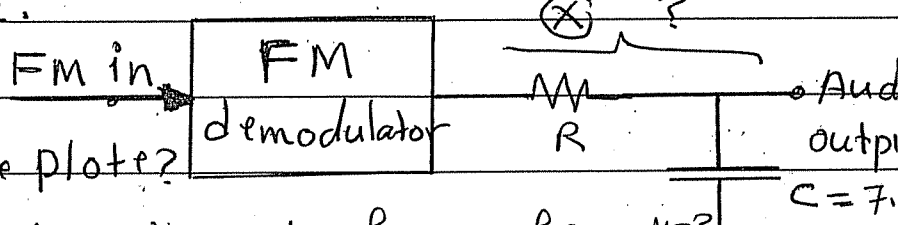calculate R required to give 3dB freq. of 2123 Hz?



Q3) Name the cct.

shown in Fig. 3?

then sketch

$V_i(t), V_c(t)$

and $V_o(t)$ when:

$V_c = 10 \sin 2\pi \times 10^6 t \text{ (V)}$

$V_m = 4 \sin \pi \times 10^3 t \text{ (V)}$

what will be the

output when $V_i(t)$ only is applied or when $V_c(t)$ is applied?

For $L_4 = 1 \mu\text{H}$, what is the value of C required to pass the LSB Frequency?

Redraw the cct. when both transformers are aircore?

