

تقارير مختبر الكترونيات

Electronics Lab

Lab Session 1: Diode Characteristics

19/20

Students Names	ID

Part one:

1. Construct the circuit shown below, measure the forward voltage V_F , V_{R1} , and compute I_F .


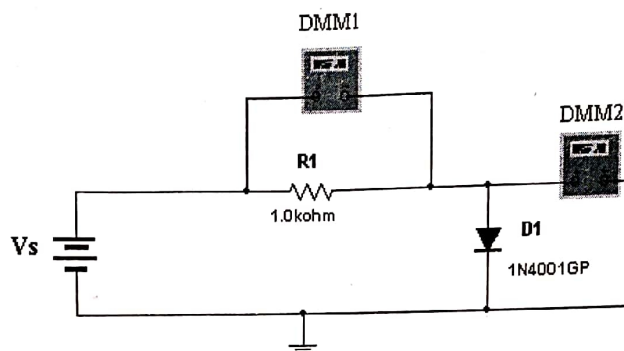


Table2: Diode Forward Currents and Voltages

V_s	V_{R1} Normal	V_D Normal	$I_D = V_R/R$ Normal
0.2	0.58 mv	273.1mv	58 μ V
0.4	36.95mv	431.7mv	36.95 μ V
0.6	206.1mv	507.1mv	206.1 μ V
1.0	486.6mv	547.3mv	486.6 μ V
3.0	2.46v	627.4mv	2460 μ V
5.0	4.45v	657.4mv	4450 μ V

V_s	V_{R1} Zener	V_D Zener	$I_D = V_R/R$ Zener
0.2	0.30 mv	226.1mv	3 μ V
0.4	23.9 mv	435.1mv	23.9 μ V
0.6	99.8 mv	593.3mv	99.8 μ V
1.0	392.7 mv	656.4mv	392.7 μ V
3.0	2.36 v	727.2mv	2360 μ V
5.0	4.39 v	751.4mv	4390 μ V

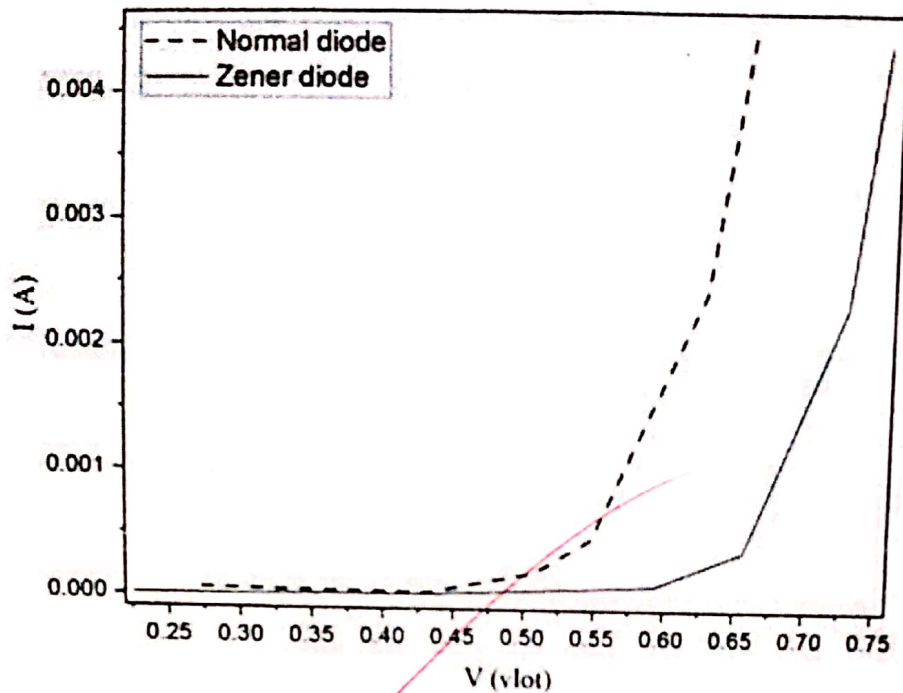2. Use your results from Table 2 to plot the IF versus VF curve for both diodes in the figure below



3. Graphically determine the dynamic resistance of the normal diode at 3.

$$RD = \frac{\Delta V}{\Delta I} = \frac{657.4 \text{ mV} - 547.3 \text{ mV}}{4450 \mu\text{V} - 486.6 \mu\text{V}} = 27.779 \text{ ohm}$$

4. Determine the static resistance of the normal diode at 1.

$$R = \frac{V_d}{I_d} = \frac{547.3 \text{ mV}}{486.6 \mu\text{V}} = 1124.7 \text{ ohm}$$

Part Two :

5. Construct the circuit shown below, Measure the voltage across the zener diode, and record this values


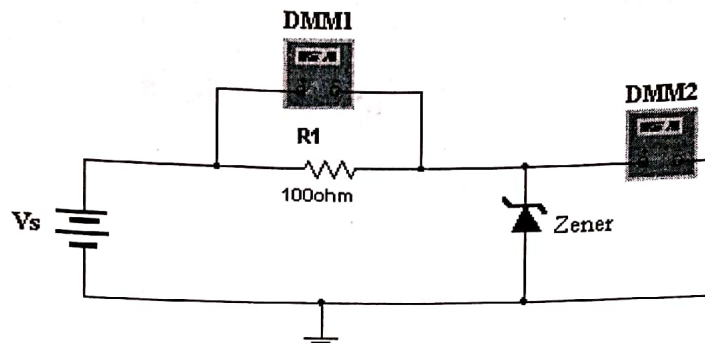


Table.3: Measurement of V_{R1} and V_z

VS (volt)	VR1 (volt)	Vz (volt)	$I_Z = V_{R1} / R1$ (mA)
0.2	0.06mv	217.6 mv	0.0006
0.6	0.22mv	703.7 mv	0.0022
1.0	1.41mv	1040.3 mv	0.0141
3.0	600.5mv	2.497v	6.005
5.0	2.14v	2.98v	21.4
7.0	3.93v	3.233v	39.3
10.0	6.77v	3.46v	67.7
12.0	8.6v	3.56v	86.0
Vz=3v			

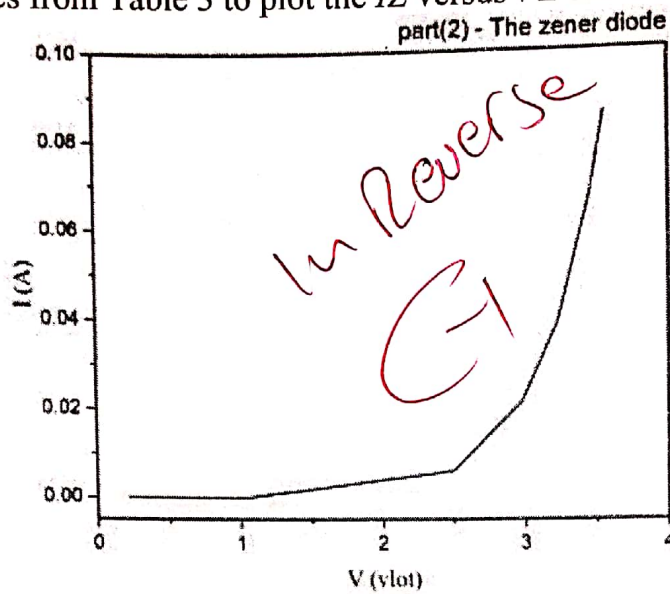6. Use the values from Table 3 to plot the I_Z versus V_Z curve in Figure 3.



Conclusions

- If V_d greater than specific V_a , then the diode is (on), and the voltage on it is equal to battery voltage = V_a .
- If V_d smaller than specific V_a , then the voltage of the diode equal to V_s and the circuit will be open circuit.
- If V_z greater than or equal to specific V_z , so the voltage of the Zener act like a battery with V_z value.
- If V_z smaller than V_z the circuit acts as open circuit and the voltage equal V_s .



Electronics Lab
Lab Session 2: Diode Applications

19.5
26

Student Names	ID#


Part 1: Half-Wave Rectification

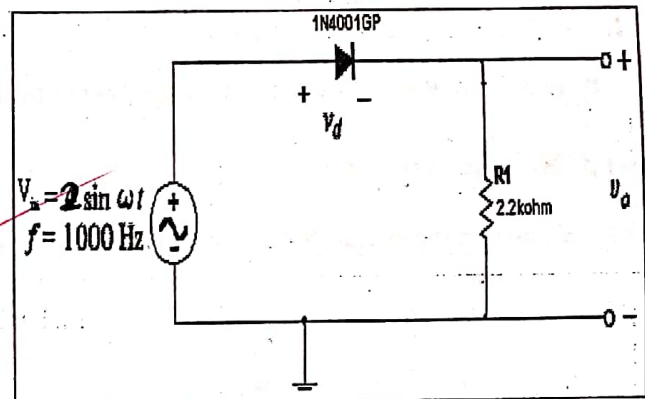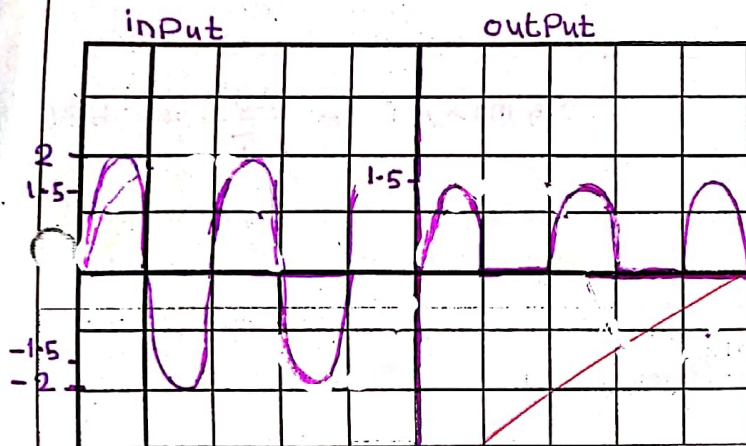- 1) Construct the circuit shown below and draw the input and output signal.



- 2) Measure the DC value of V_o using the DC scale in the DMM. $V_{DC} = \dots\dots\dots 399.2 \text{ mV}$

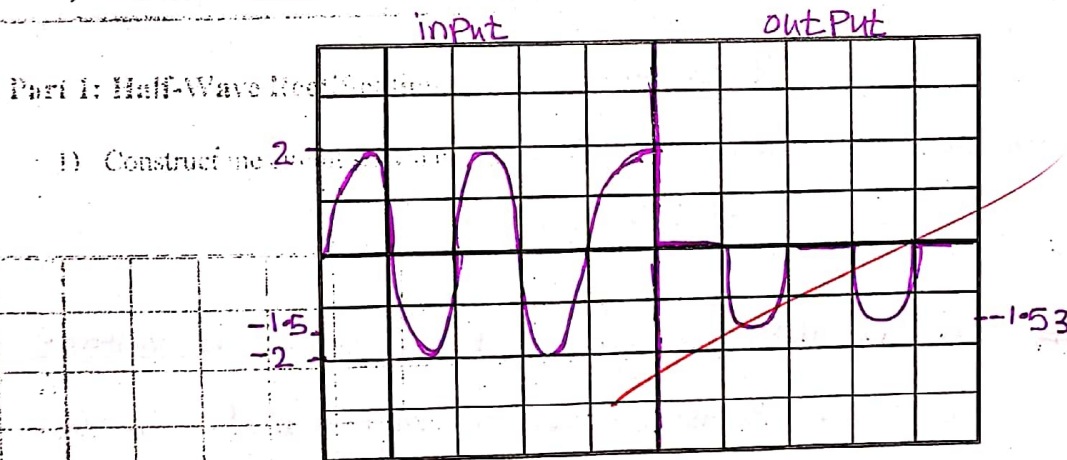- 3) Reverse the diode and draw the input and output signal.



- 4) Measure the DC value of V_o using the DC scale in the DMM. $V_{DC} = \dots\dots\dots -406.8 \text{ mV}$

- 5) For step 1, and 3, Calculate the DC level of the output waveform.



2) Measure the $V_{avg1} = \dots\dots\dots V_m/\pi = 1.5/\pi = 0.477$

3) Reverse the diode $V_{avg4} = \dots\dots\dots V_m/\pi = -1.5/\pi = -0.477$

Part 2: Full-Wave Rectification

- 6) Construct the circuit shown below. Draw the output waveforms. Then, measure the DC load voltage using DMM. $V_{DC} = \dots\dots\dots$


$$0.2142 - (0.2142) = 0.45 \text{ V}$$

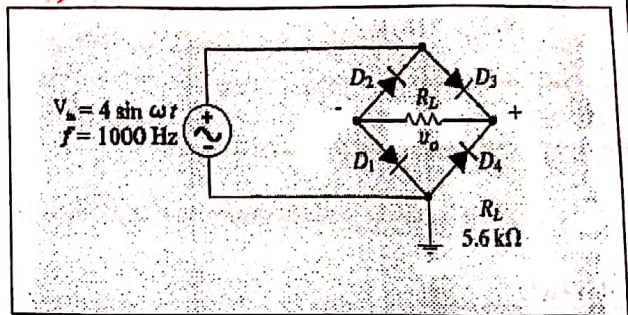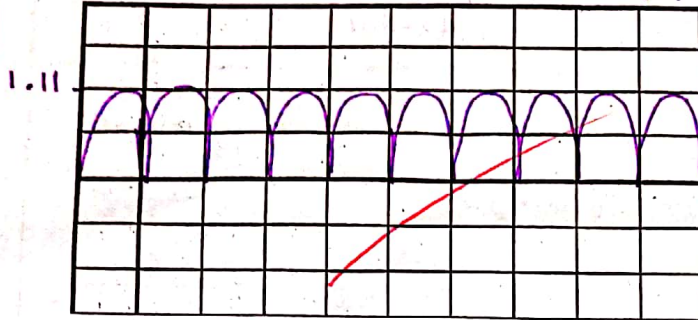

- 7) Calculate the DC level of the output waveform V_o . $V_{avg} = \dots\dots\dots = 0.636$

Part 3: Rectifier Filtering

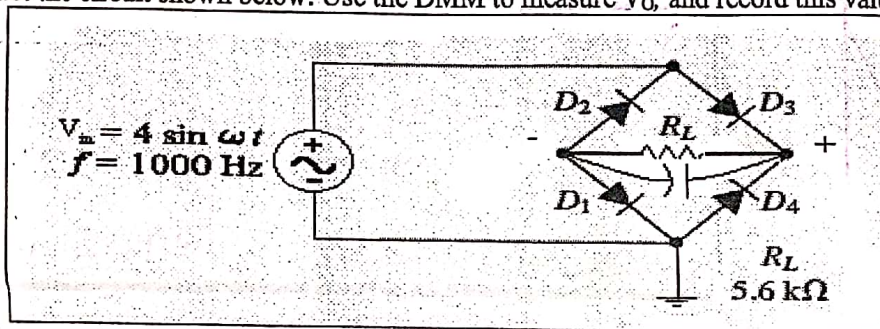- 8) Construct the circuit shown below. Use the DMM to measure V_o , and record this value.



- 9) Use the oscilloscope to observe and measure the ripple voltage using $1 \mu\text{F}$.

$$V_r = \dots\dots\dots 1.464 \text{ mV}$$

- 10) Use the oscilloscope to observe and measure the ripple voltage using $22 \mu\text{F}$.

$$V_r = \dots\dots\dots 61 \text{ mV}$$

Conclusion

the rectifier is used to convert AC voltage to DC, it uses one or more diode in its ckt, which is (H.W or F.W). The Benefits of filter [capacitor with F.W.] is to reduce the ripple in the signals and when the capacitor $\uparrow$ the ripple $\downarrow$.

0.5



Electronics Lab
Lab Session 2.b: Diode Applications

Students Names	ID#
	1


19
26

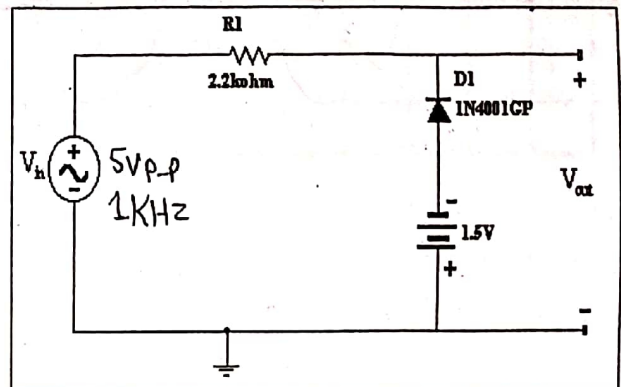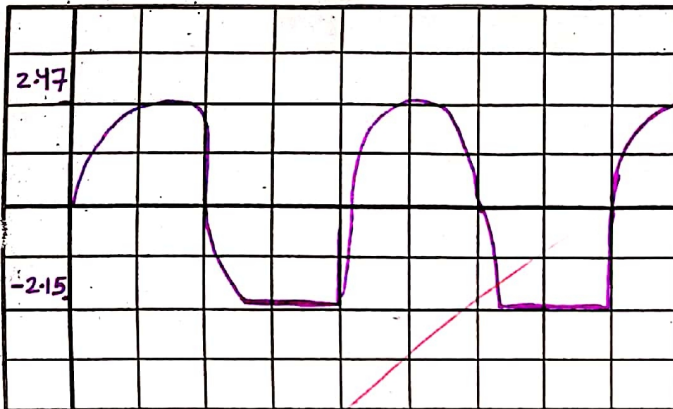Part 1: The Shunt Clipper with a DC Battery

- Construct the circuit shown below. The input signal is $5V_{p-p}$ sine wave at a frequency of 1KHz.
- Draw the output signal.





- Reverse the polarity of the diode and the power supply then draw the output.

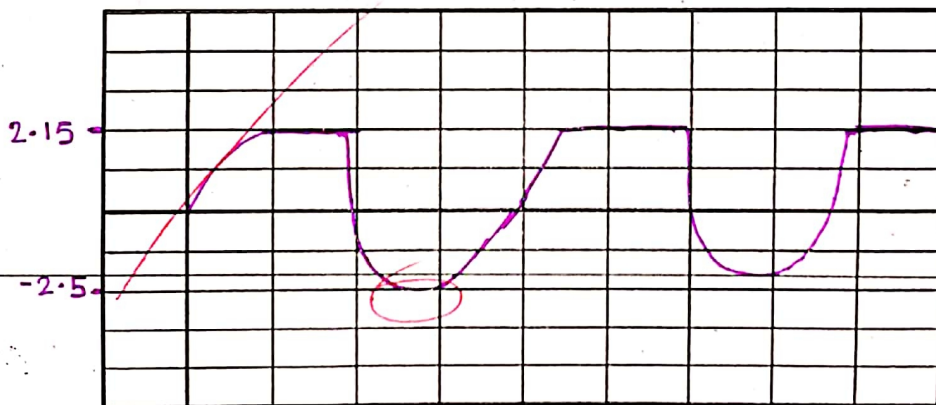


Part 2: The Clamper circuit

- Construct the circuit shown in below. The input signal is $5V_{p-p}$ sine wave at a frequency of 1 KHz.
- Draw the output signal.

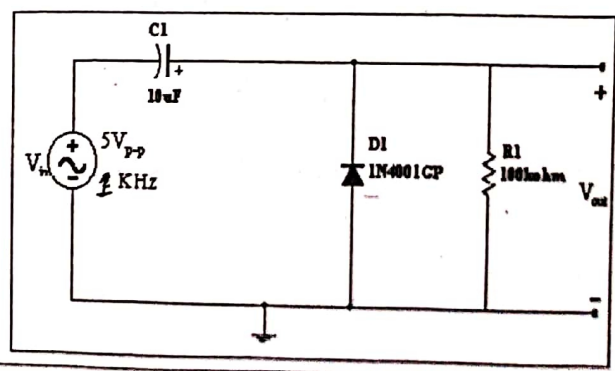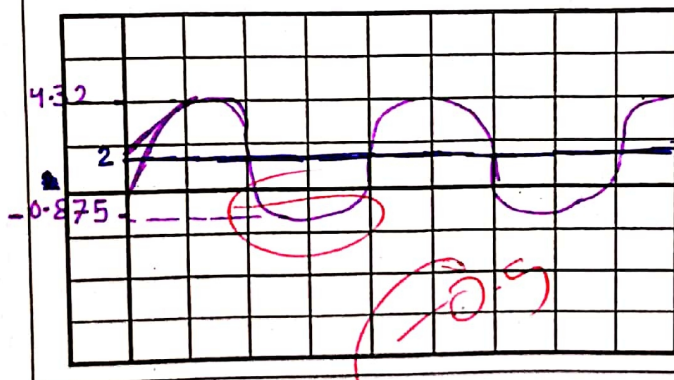

Part 3: the Clamper circuit with DC Battery

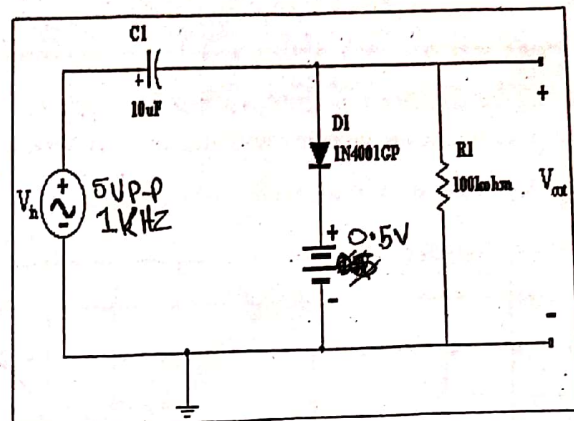6. Construct the circuit shown in the figure and Set the function generator to a 1 KHz, 5V_{p-p} sine wave. Then sketch the output signal



Conclusions

* clipping is a process of cutting a portion of the AC input signal to certain specification level, the ckt which performs clipping is called "clipper" and it contains diodes which represents the main element in the ckt.

* otherwise, the clamper is changing the DC level of the AC input signal to a certain specified level. types of clamping are +ve, -ve, the type of the clamping depends on the diode direction, and the clamping level (D.C level) depends on value and polarity of the DC source connected with diode (if any).


* the difference between clipper and clamper is the capacitor.

Electronics Lab
Lab Session 3: BJT Characteristics and DC Biasing

Students Names	ID#

20
26


Part 1: Checking Transistors

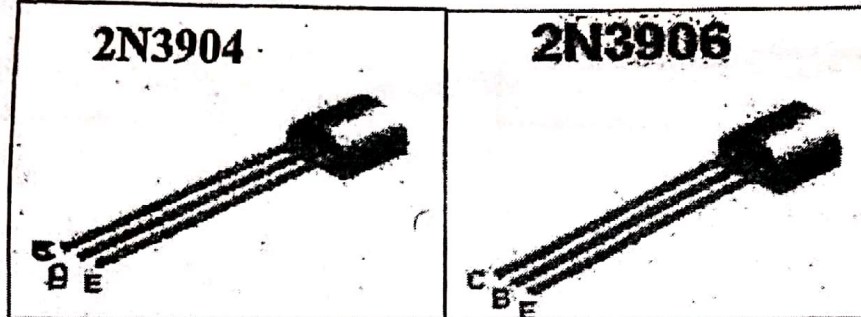


Part 2: Determining Transistor Parameters and the DC Load Line

1. Connect the circuit as shown in Figure 8 in the lab manual using NPN transistor and fill the following table:

Parameter	Measured
V_C	5.895
V_B	4.878
V_E	4.235
V_{CEQ}	1.741
V_{BEQ}	0.6583
I_{BQ}	0.087
I_{CQ}	2.823
I_C	2.736
β	31.44
α	0.969

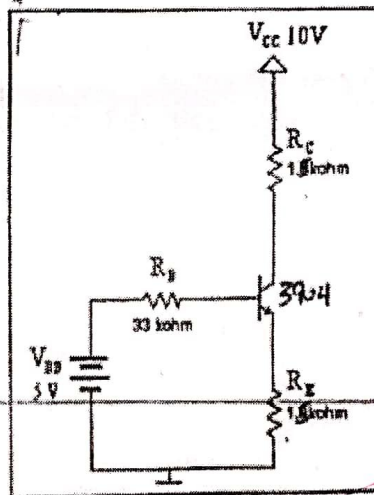

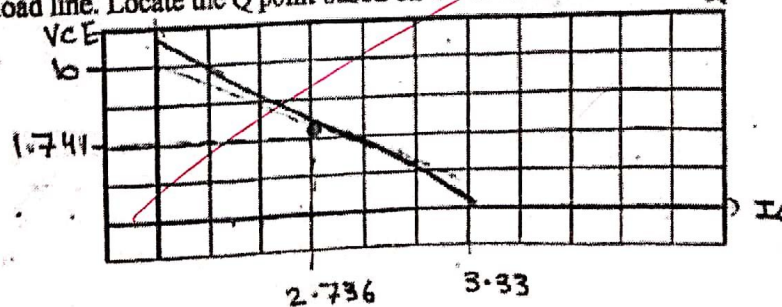
3. Determine the saturation ($I_{C(sat)}$) and cutoff ($V_{CE(off)}$) points on the DC load line for this circuit, then plot the DC load line. Locate the Q point based on the measured values of I_{CQ} and V_{CEQ} .




when $I_C = 0 \rightarrow V_{CE} = 10$
 when $V_{CE} = 0 \rightarrow I_C = \frac{V_{CC}}{R_C + R_E}$
 $= \frac{10}{3}$
 $I_C = 3.33$

4. Connect the circuit as shown in Figure 9 in the lab manual using PNP transistor and fill the following table:

Parameter	Measured
V_c	1.159
V_b	7.226
V_e	8.026
V_{ce}	5.916
V_{ceQ}	5.916
I_{CQ}	1.306
I_{BQ}	0.01
I_{EQ}	1.316
β	130.6
α	0.992

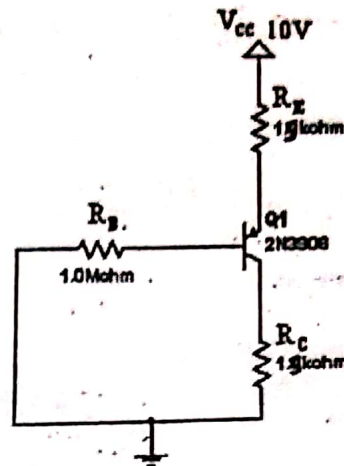

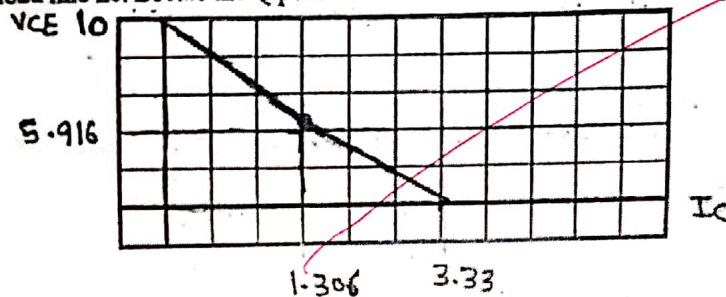5. Determine the saturation ($I_{C(sat)}$) and cutoff ($V_{CE(off)}$) points on the DC load line for this circuit, then plot the DC load line. Locate the Q point based on the measured values of I_{CQ} and V_{CEQ} .



when $I_C = 0 \Rightarrow V_{CE} = V_{CC} = 10$
 $V_{CE} = 10$
 when $V_{CE} = 0 \Rightarrow I_C = \frac{V_{EE}}{R_E + R_C} = \frac{10}{3} = 3.33$
 $I_C = 3.33$

Calculations (PART1 and PART2) calculate All

① $I_C = \frac{V_{CC} - V_C}{R_C} = \frac{10 - 8.695}{1.5} = 2.736$ ② $I_E = \frac{V_{EE} - V_E}{R_E} = \frac{10 - 8.026}{1.5} = 1.316$
 ③ $I_F = \frac{V_E}{R_E} = \frac{4.235}{1.5} = 2.823$ ④ $I_C = \frac{V_C}{R_C} = \frac{1.959}{1.5} = 1.306$
 ⑤ $I_B = I_E - I_C = 2.736 - 1.306 = 1.43$ ⑥ $I_B = I_E - I_C = 1.316 - 1.306 = 0.01$
 ⑦ $\beta = I_C / I_B = 2.736 / 0.01 = 273.6$ ⑧ $\beta = I_C / I_B = 1.306 / 0.01 = 130.6$
 ⑨ $\alpha = \beta / (\beta + 1) = 273.6 / 274.6 = 0.996$ ⑩ $\alpha = \beta / (\beta + 1) = 130.6 / 131.6 = 0.992$


Part (1)

Part (2)

Electronics Lab
Lab Session 4: The Common Emitter Amplifier

Student Names	ID#

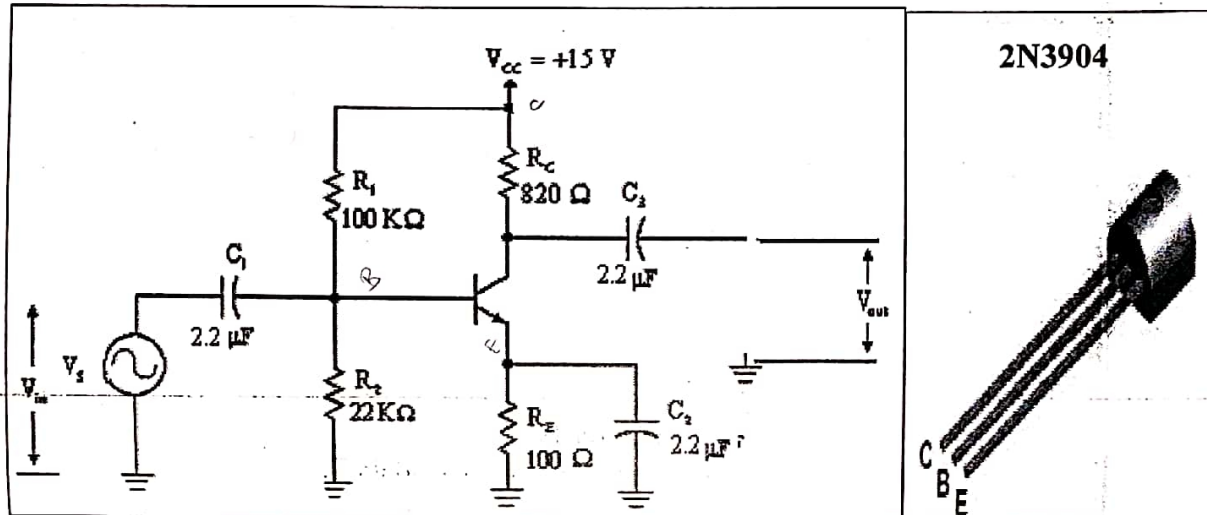1) Construct the circuit shown below and Measure and record the DC voltages listed in Table 1.



DC Parameters	Measured Value
V_B	2 V
V_E	1.36 V
V_C	4.22 V
V_{CE}	2.83 V
V_{BE}	686 mV
I_C	13.14 mA
I_B	0.46 mA
I_E	13.6 mA
β	28.565
α	0.966176

Table.1: DC Parameters of CE Amplifier

Calculations

$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{15 - 4.22}{820} = 13.14 \text{ mA} \quad // \quad I_E = \frac{V_E}{R_E} = \frac{1.36}{100} = 13.6 \text{ mA}$$

$$I_B = I_E - I_C = 0.46 \text{ mA} \quad // \quad \beta = \frac{I_C}{I_B} = 28.565$$

$$\alpha = \frac{\beta}{1 + \beta} = 0.966176$$

2) Connect the AC circuit with $V_s = 150 \text{ mVp-p}$ sine wave at 1.0 kHz. Fill Table2.

$v_b = V_{in}$	150 m Vpp
$r_e = 26\text{mV}/I_E$	1.91176 Ω
$v_c = V_{out}$	3.6 Vpp
$A_v = V_{out}/V_{in}$	24

Table.2: AC Parameters of CE Amplifier

5) Remove C_2 from the circuit and fill Table3.

$v_b = V_{in}$	150 m Vpp
$r_e = 26\text{mV}/I_E$	1.91176 Ω
$v_c = V_{out}$	1.25 Vpp
$A_v = V_{out}/V_{in}$	8.33333

Table3: AC Parameters of CE Amplifier

3) Use $20\text{k}\Omega$ pot. to measurer the R_{in} . $R_{in} = 11.3 \text{ k}\Omega$

4) Use $20\text{k}\Omega$ pot. to measurer the R_{out} . $R_{out} = 300 \Omega$


20
26

Electronics Lab
Lab Session 6: Frequency response

Student Name:
Section No:

Registration No.:
Date:

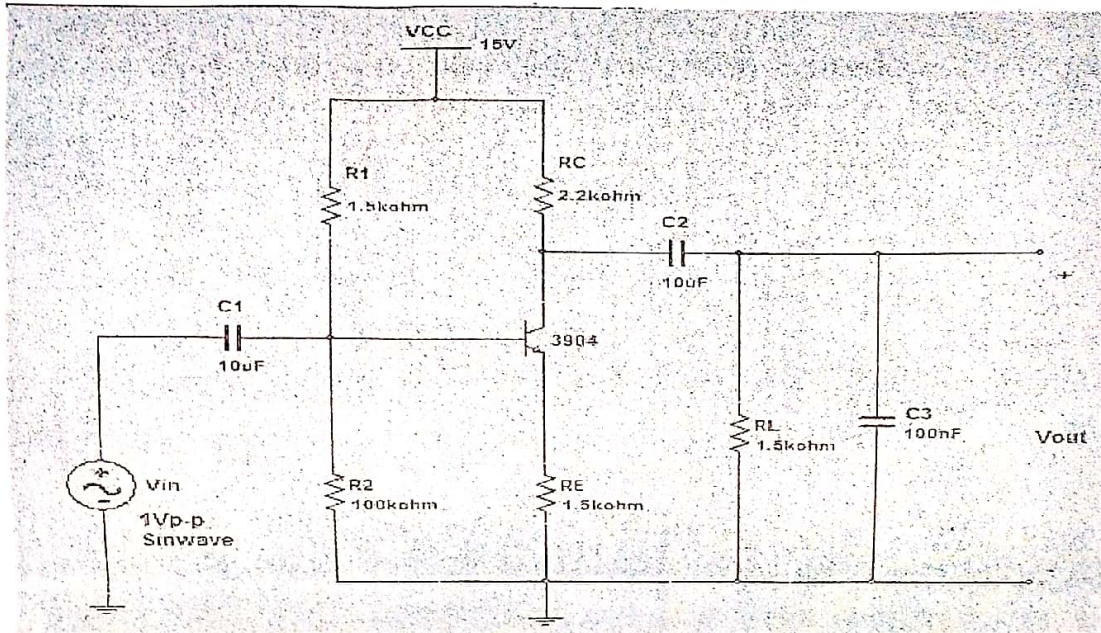a) Assemble the circuit shown in the figure then fill the table below.



mv

F	20	40	50	100	200	1	7	10	50K	100	200	500
	H	H	H	H	H	KH	KH	KH	H	KH	KH	KH
V _{out}	330	589	625	760	812	880	840	820	320	180	120	80
A _v	330	559	625	760	812	880	840	820	320	180	120	80

Note: always check the input voltage

b) Determine the followings.


1. The lower cut off frequency (FL) = $\frac{A_{vm}}{\sqrt{2}} = \frac{880}{\sqrt{2}} = 0.62 \Rightarrow \boxed{50\text{H}}$

2. The upper cut off frequency (FH) = $\boxed{20\text{KH}}$

3. The bandwidth of the amplifier = $20 \times 10^3 - 50 = 20000 - 50 = 19950\text{H}$

4. The midband gain of the amplifier = 880 mV

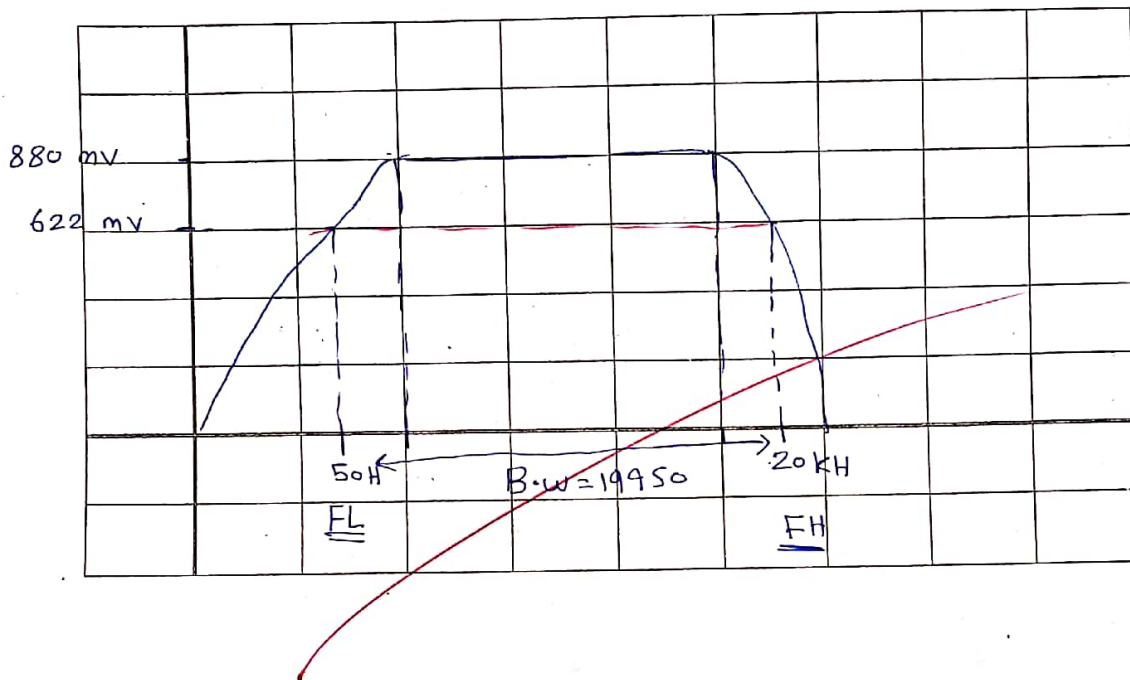5. Plot the resulting frequency response (A_v against F or $A_v(\text{dB})$ against F) showing clearly the results found in 1 through 4.





Electronics Lab
Lab Session 6: Operational Amplifier

Students Names	ID#

18.5
20

Part 1: Inverting Amplifier

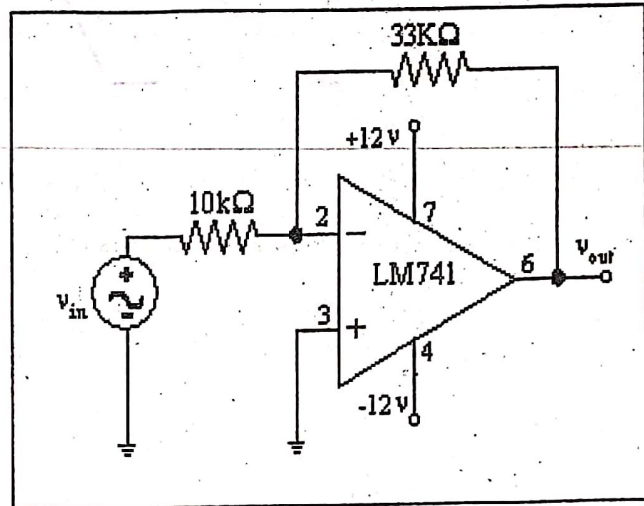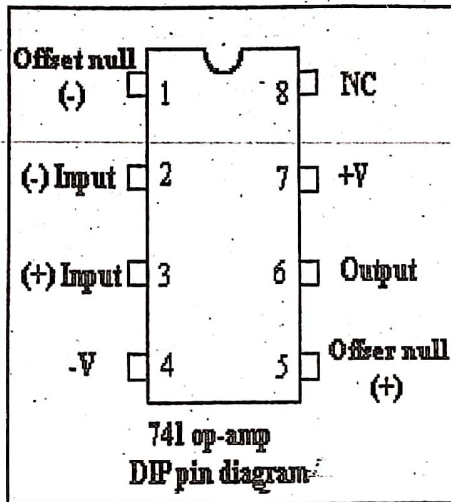
1. Construct the circuit shown Connect a 500 Hz, 1 V_{pp} sine wave.



2. Measure the peak-to-peak values of the input and output Waveforms .

$V_{in} = \dots 1 \dots$ $V_o = \dots 3.38 \dots$ Phase Shift $\dots 180 \dots$ $AV = \dots \frac{V_o}{V_i} = \dots \frac{3.38}{1} = 3.38$

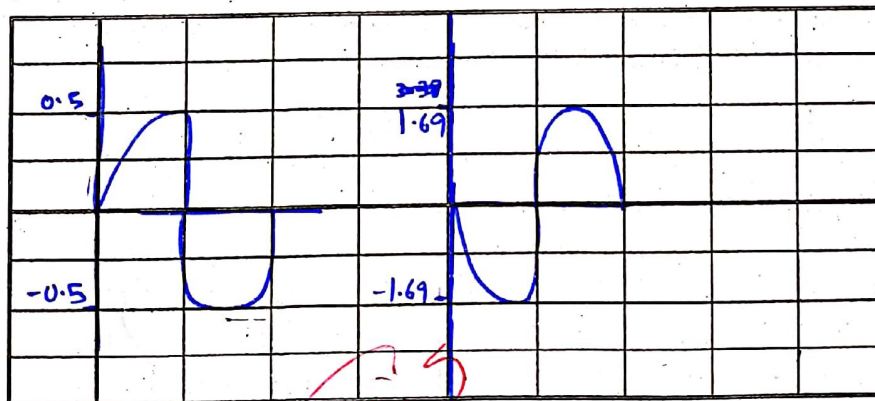3. Sketch V_{out} and V_{in} on the same sheet




الرسمتين لازم يكونوا
مع بعض

4. Increase V_{in} to be 2 V_{p-p} and replace $R_f = 33K\Omega$ with $1M\Omega$, Measure the peak-to-peak values of the input and output. Then, sketch both waveforms.

$V_{in} = \dots 2 \dots$

$V_o = \dots -23.3 \dots$

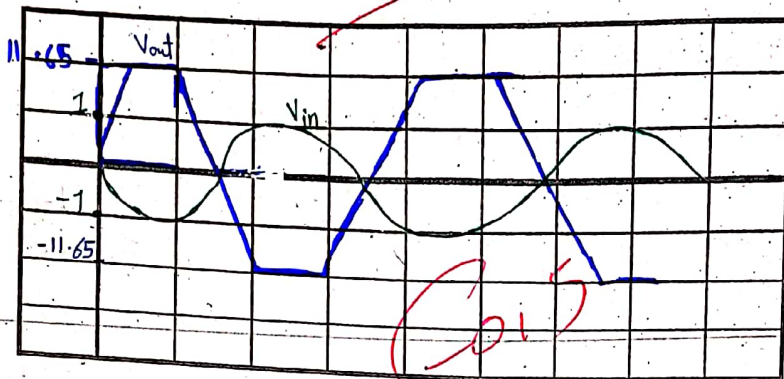
$AV = \dots \frac{V_o}{V_i} = -11.65 \dots$



لا توضح
التيار
التيار
1 و 11.65

Part 2: Non-inverting Amplifier

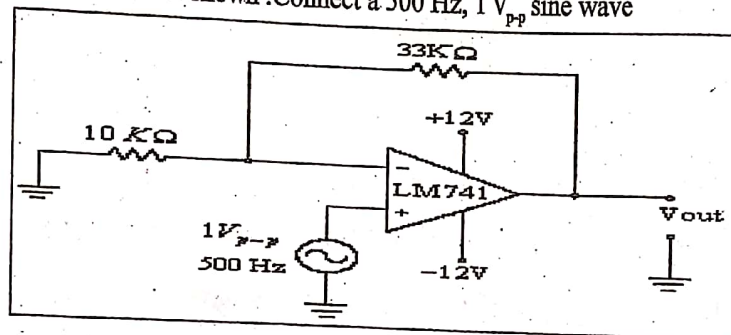1. Construct the circuit shown. Connect a 500 Hz, 1 V_{p-p} sine wave



2. Measure the peak-to-peak values of the input and output waveforms, and record their values. Then, sketch both waveforms.


$V_{in} = \dots 1 \dots$

$V_o = \dots 4.5 \dots$

Phase Shift $\dots 0 \dots$

$AV = \dots 4.5 \dots$

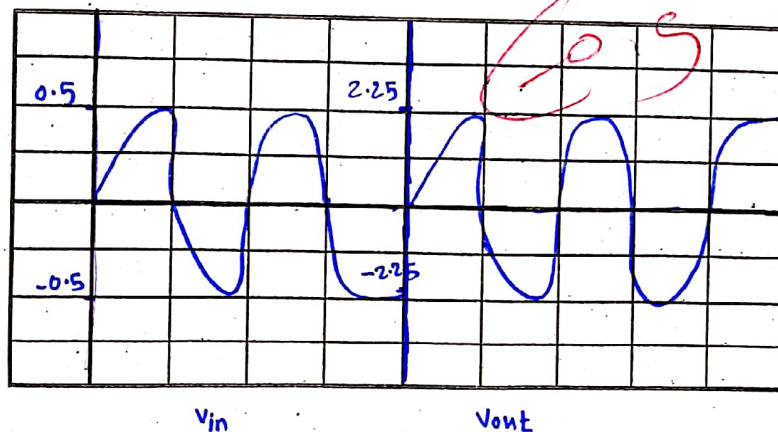3. Sketch V_{out} and V_{in} on the same sheet



التيار
يكون مع بعض

Part 3: Summing Amplifier

تم الحل بالعلي


1. For the circuit shown, calculate V_o

$$V_{in} = 2 \quad [V_{in} \text{ the same for both op Am}]$$

$$V_o = - \left(\frac{R_F}{R_1} V_{in_1} + \frac{R_F}{R_2} V_{in_2} \right)$$

$$= - \left(\frac{10K}{10K} \cdot 2 + \frac{10K}{10K} \cdot 2 \right)$$

$$= -4$$

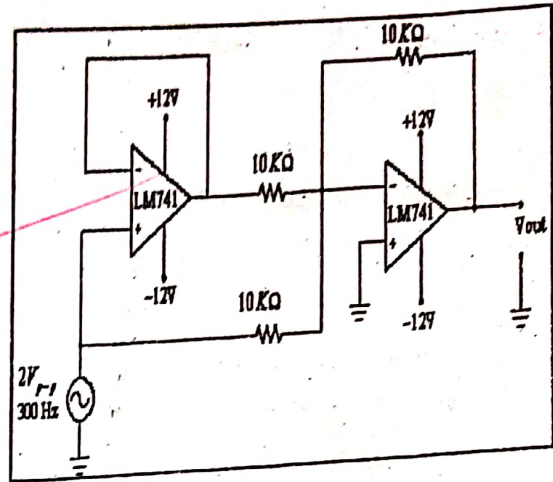


Conclusions

- Regarding the IC, pin (1, 5, 8) $\rightarrow$ we don't connect those pins
- The wires shouldn't be touching, if happen the ckt will be shorted
- The op-Am gives max output $= +V_{cc}, -V_{cc}$
if we connect a circuit that gives output larger than $(+V_{cc}, -V_{cc})$
the output signal is going to be clipped to the max value as I mention before at $(+V_{cc}, -V_{cc})$
- Inverting Amp: have 180° phase shift between the input and the output
- Non-inverting Amp: have zero phase shift between the input and the output
- A_v can be controlled by changing the Resistor values.


Electronics Lab **Lab Session 7: Operational Amplifier**

Students Names	m#

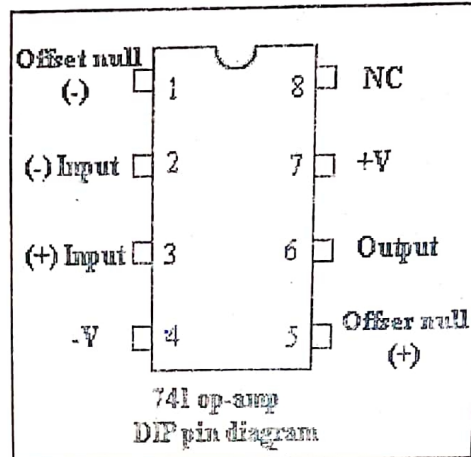

Part I: Comparator with 741 IC Used as a Level Detector

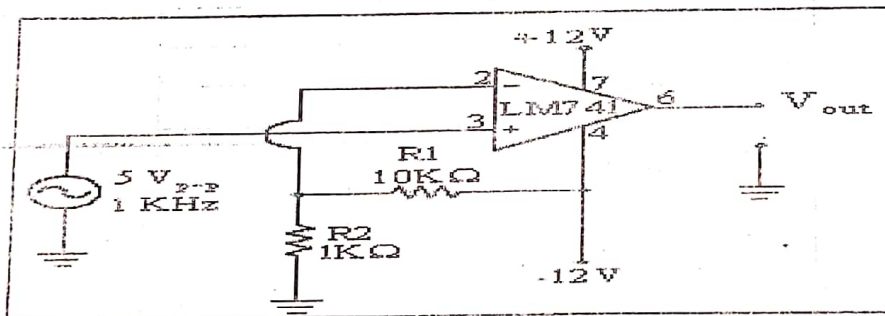
- Construct the circuit shown below, connect a 500 Hz, 5-V_{p-p} to the input. Sketch the input SIGNAL, V_{ref} and the output signal on the same graph,



$$* V_{ref} = \frac{-12 * 1}{1 + 10} = -1.09$$

$$* V_i < V_{ref} \Rightarrow V_o = -12$$

$$* V_i > V_{ref} \Rightarrow V_o = 12$$

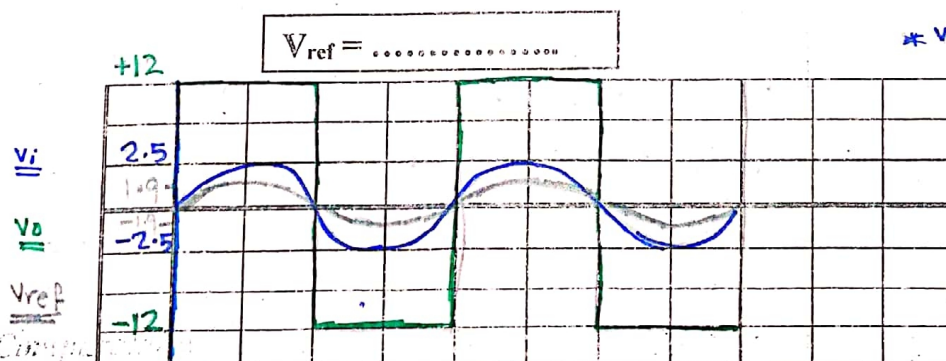

Part I: Comparator



1. Construct the

V_{ref} and the

Part 4: Integrator

- Construct the circuit shown below, apply a $2 V_{p-p}$ of 200Hz sine wave.
- Vary the frequency of V_{in} from 200Hz to 50KHz. Calculate the gain. And record the results in the Table 1, and then plot the gain vs. frequency on semi-log graph paper.

Frequency (Hz)	V_{in} (Volt)	V_{out} (Volt)	A_v
50	2	6.2	3.1
100	2	6	3
200	2	5.5	2.75
400	2	4.6	2.3
1K	2	2.6	1.3
10K	2	900 m	0.45
15K	2		

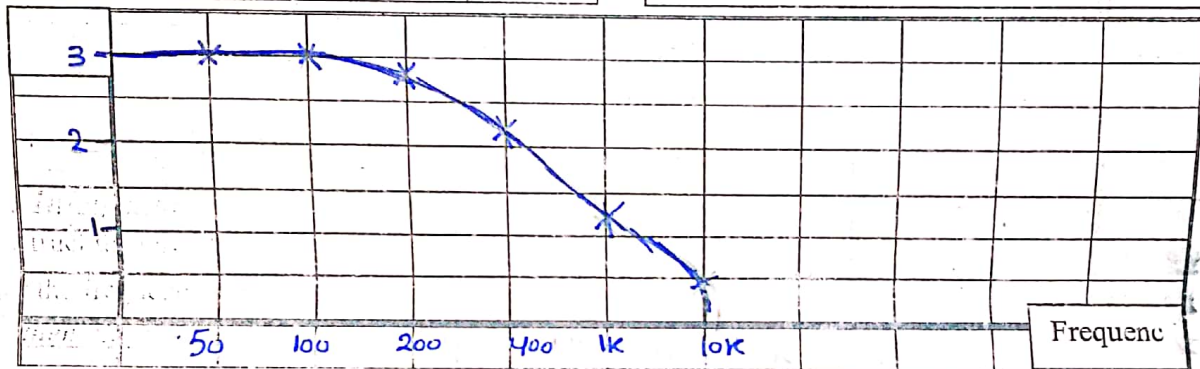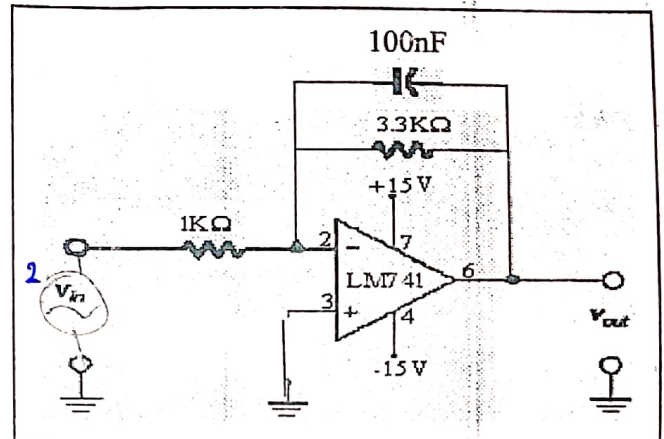



The Break Frequency of the Integrator circuit $FB = \frac{1}{2\pi C_F R_F} = \frac{1}{2\pi \cdot 100 \times 10^{-9} \cdot 3.3 \times 10^3} = 482.53$

Part 5: Differentiator

- Connect the circuit shown. Apply a $2 V_{p-p}$ sine wave at 200 Hz sine wave.
- Vary the frequency of V_{in} as shown in the Table 2 and record the results.
- Calculate the gain and then plot the gain vs. frequency on semi-log graph paper.

Frequency(Hz)	V_{in} (Volt)	V_{out} (Volt)	A_v
200	2	2.85	1.425
1K	2	11.5	5.75
2K	2	15.4	7.45
6K	2	18.4	9.45
8K	2	19.3	9.65

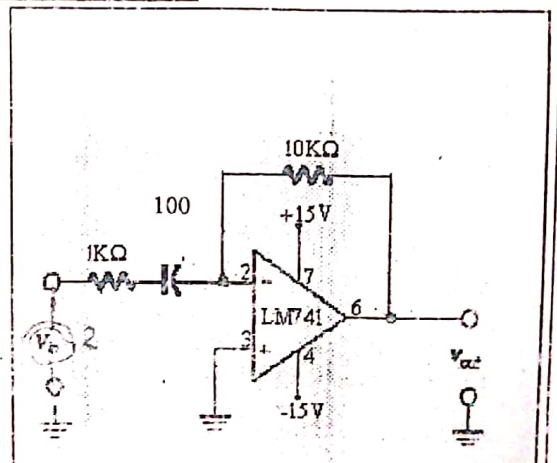

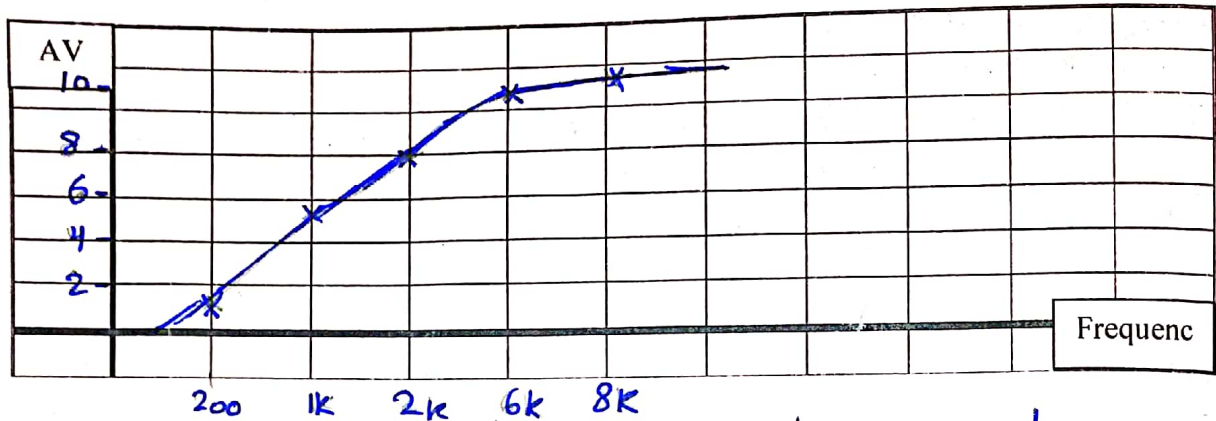

The Break Frequency of the differentiator circuit $f_B = \frac{1}{2\pi CR_1} = \frac{1}{2\pi \cdot 100 \times 10^{-9} \cdot 1 \times 10^3}$

$= 1592.35$

Conclusions

- * We use the comparator to compare between 2 signals (V_{in} and V_{ref}) [between DC signal and ~~sinu~~ sinusoidal signal].
- if $V_{in} > V_{ref} \rightarrow V_{out} = +V_{CC}$
- if $V_{in} < V_{ref} \rightarrow V_{out} = -V_{CC}$, the output is a square wave.
- * the integrator work as a low pass filter $\rightarrow$ pass low frequency at high frequency, which depends on the value of the cutoff frequency.
- * Differentiator work as high pass filter, pass high frequency and atten- low frequency, which depends on the value of the cut off frequency (f_B).
- before (f_B), it works as differentiator.
- after (f_B), it works as inverter with constant gain.
- the gain become constant with increasing the frequency.