

Electronics Lab
Lab Session 1: Diode Characteristics

| | | |
|-----------------------|----------------------------|-------------------------|
| Students Names | Sandy Ghassan fathi | Rami yahia hasan |
| ID | 1834471 | 1838264 |

Part one:

1. Construct the circuit shown below, measure the forward voltage V_F , V_{R1} , and compute I_F .


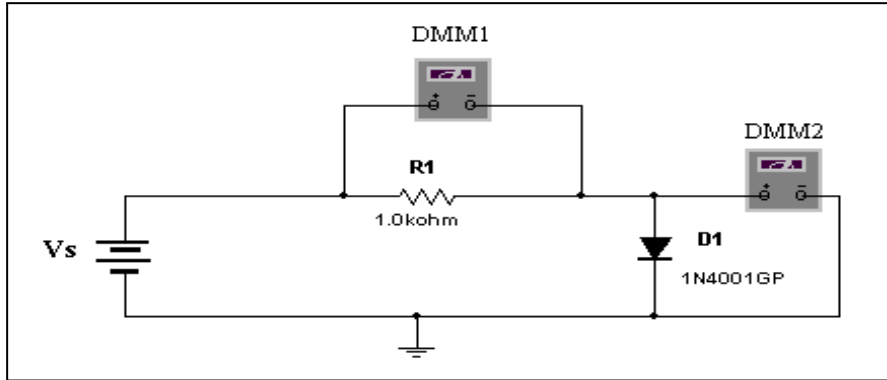


Table2: Diode Forward Currents and Voltages

| V_S | V_{R1} Normal | V_D Normal | $I_D = V_R / R$ Normal |
|-------|--------------------|-----------------|---------------------------|
| 0.2 | 12.97 mV | 187.1 mV | 12.795 uA |
| 0.4 | 92.271 mV | 307.729 mV | 92.271 uA |
| 0.6 | 234.381 mV | 365.619 mV | 234.381 uA |
| 1.0 | 578.147 mV | 421.853 mV | 578.147 uA |
| 3.0 | 2.487 V | 512.901 mV | 2487 uA |
| 5.0 | 4.451 V | 549.281 mV | 4451 uA |

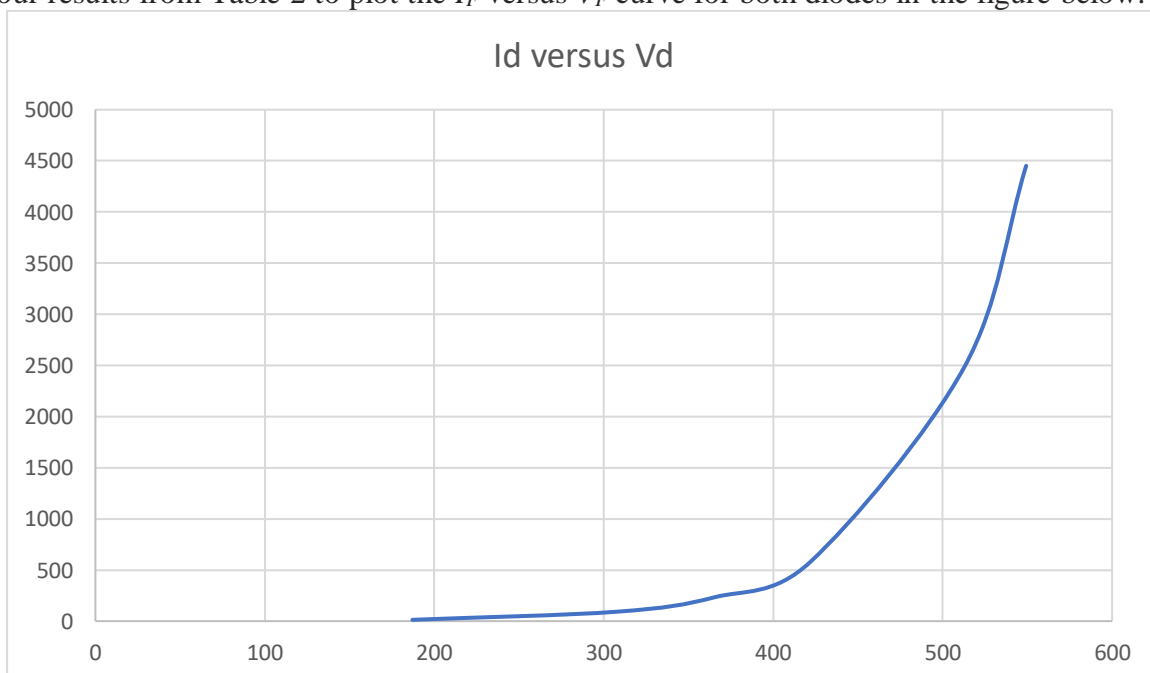2. Use your results from Table 2 to plot the I_F versus V_F curve for both diodes in the figure below.




3. Graphically determine the dynamic resistance of the normal diode at 3.



$$R_d = \Delta V \setminus \Delta I = (549.281 \text{ mV} - 421.853 \text{ mV}) \setminus (4451 \text{ uA} - 578.147 \text{ uA}) = 33.21 \text{ ohm}$$

4. Determine the static resistance of the normal diode at 1.

$$R = V_D \setminus I_D = 421.853 \text{ mV} \setminus 578.147 \text{ uA} = 729.66 \text{ ohm}$$

There are some of results in multsim:

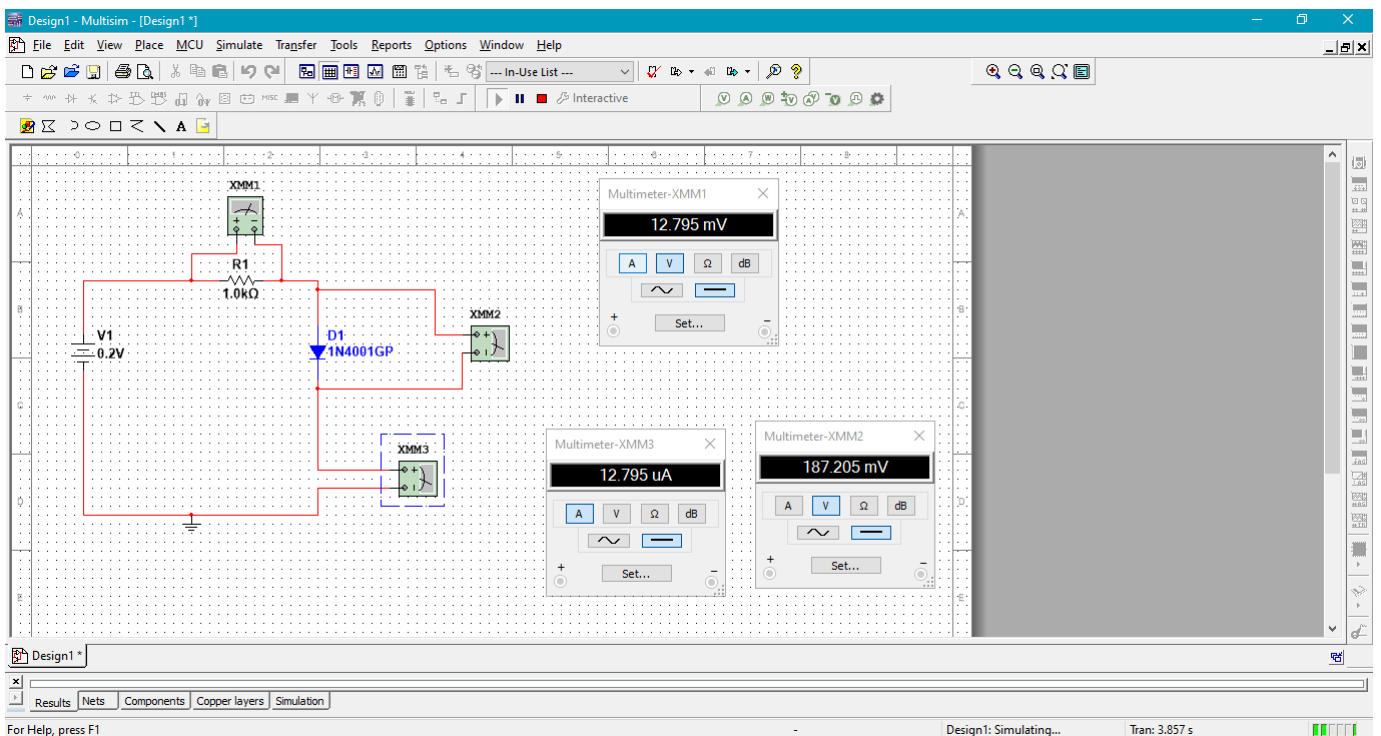

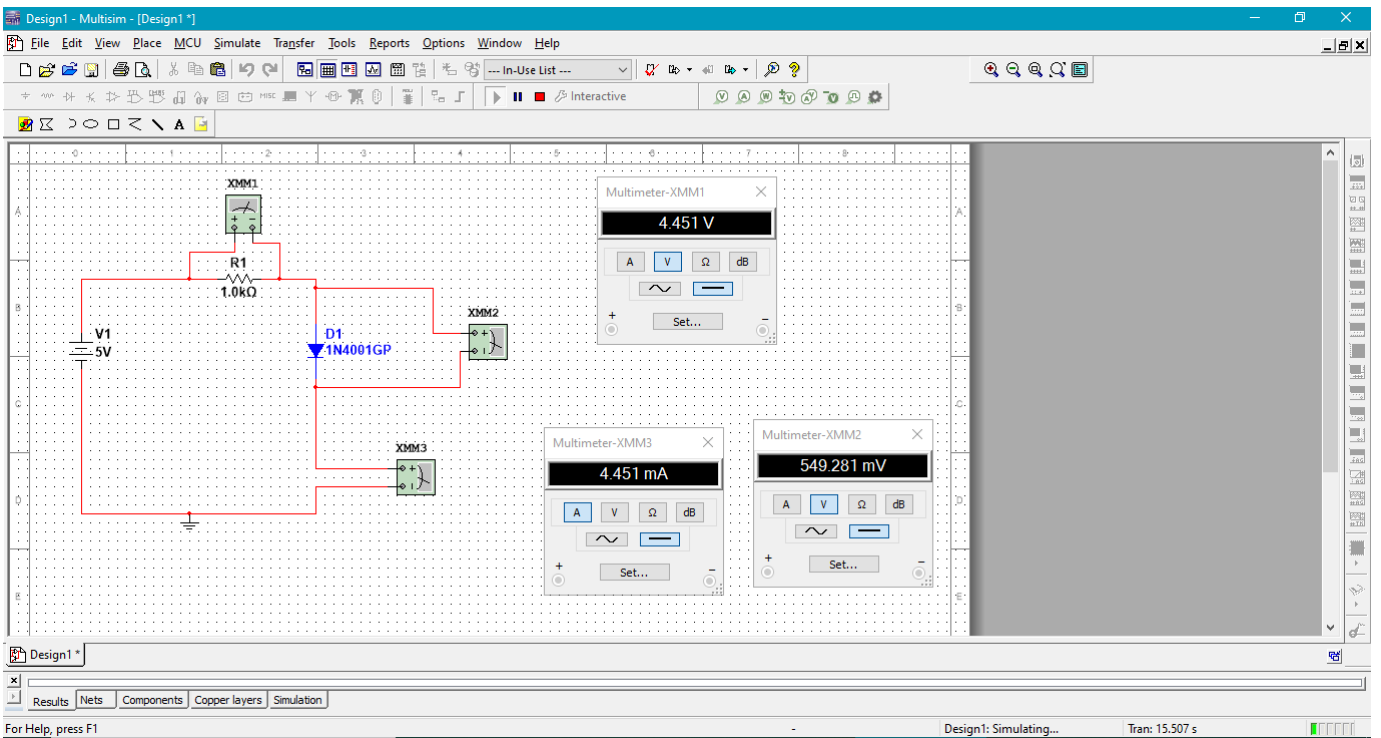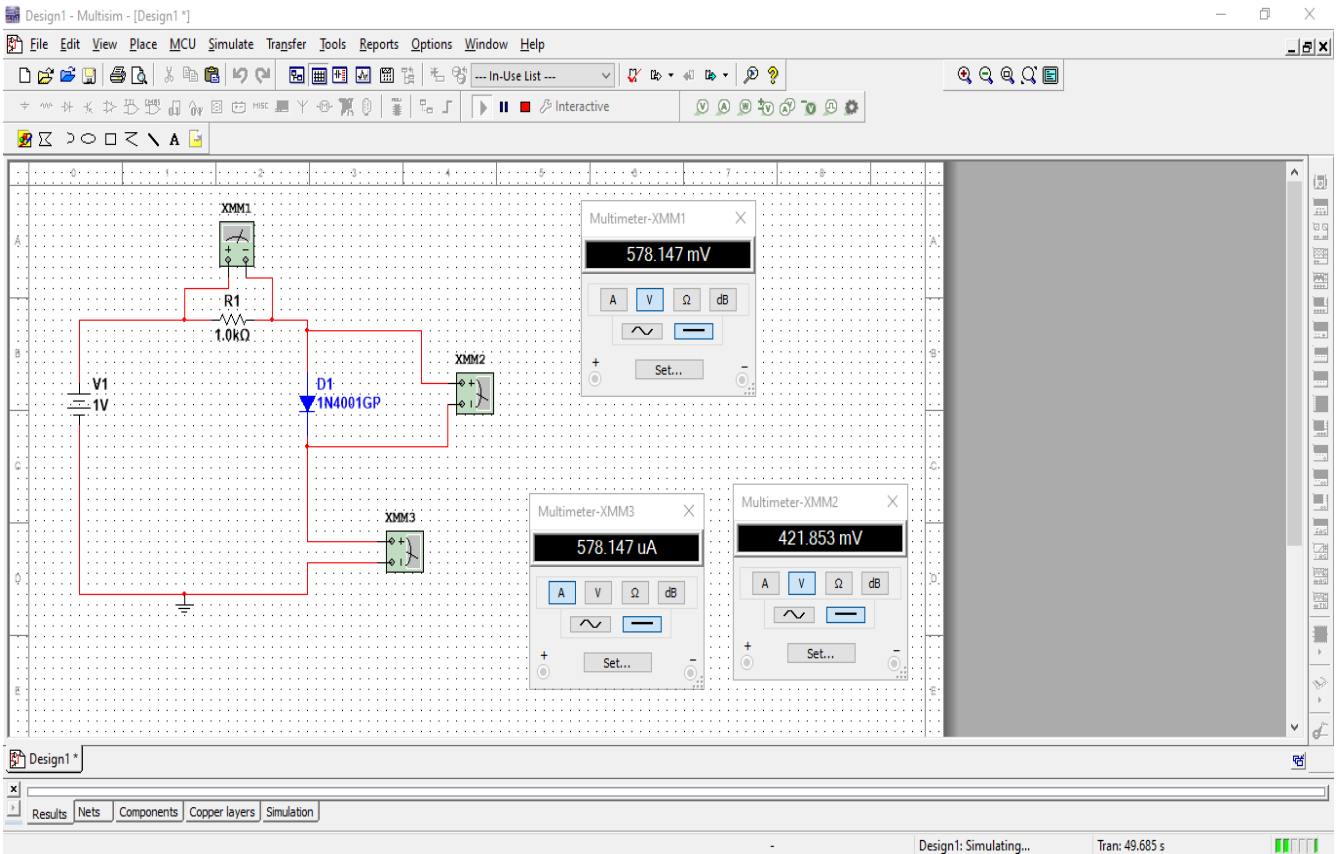

Part Two :

5. Construct the circuit shown below, Measure the voltage across the zener diode, and record this values.


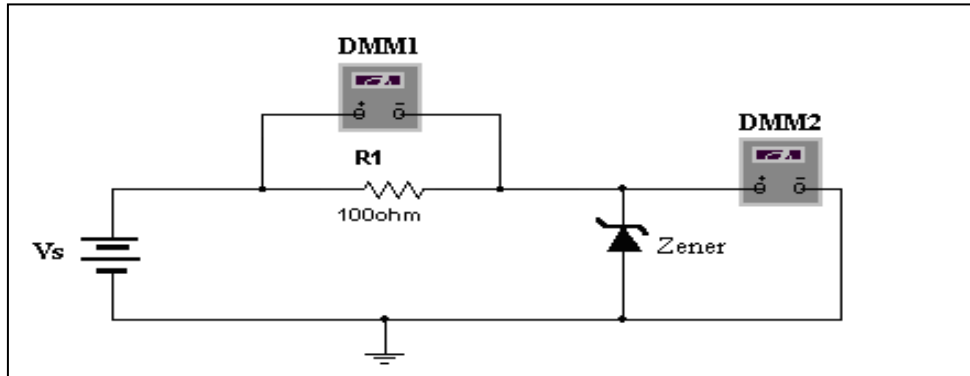


Table.3: Measurement of V_{R1} and V_Z

| V_S (volt) | V_{R1} (volt) | V_Z (volt) | $I_Z = V_{R1} / R_1$ (mA) |
|--|-----------------|--------------|---------------------------|
| 0.2 | 6.687 uV | 199.993 | 66.865 nA |
| 0.6 | 20.059 uV | 599.98 mV | 200.594 nA |
| 1.0 | 33.432 uV | 999.967 mV | 334.323 nA |
| 3.0 | 67.735mV | 2.932 V | 677.35 uA |
| 5.0 | 2v | 3 v | 20 mA |
| 7.0 | 3.986 v | 3.014 v | 39.862 mA |
| 10.0 | 6.975 v | 3.025 v | 69.75 mA |
| 12.0 | 8.97 v | 3.03 v | 89.7mA |
| $V_Z = \dots\dots 3 \text{ v}$ | | | |

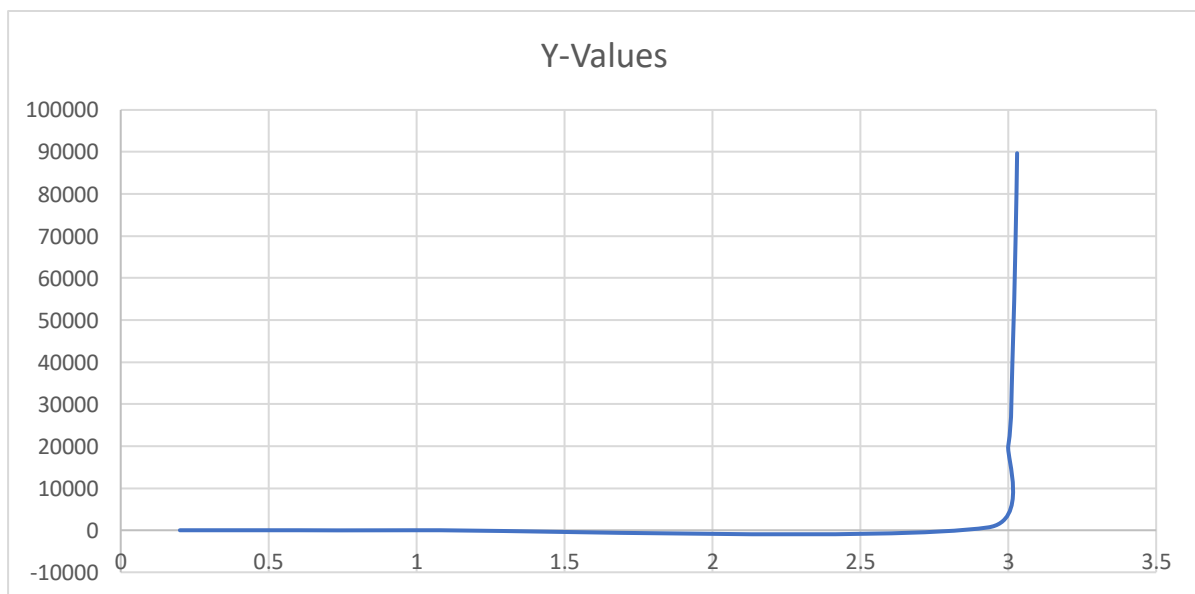6. Use the values from Table 3 to plot the I_Z versus V_Z curve in Figure 3.



There are some of results in multsim:

