



# Electronics Lab

## Lab Session 2: Diode Applications

Students Names	Sandy Ghassan fathi	Rami yahia hasan
ID	1834471	1838264

### Part 1: Half-Wave Rectification

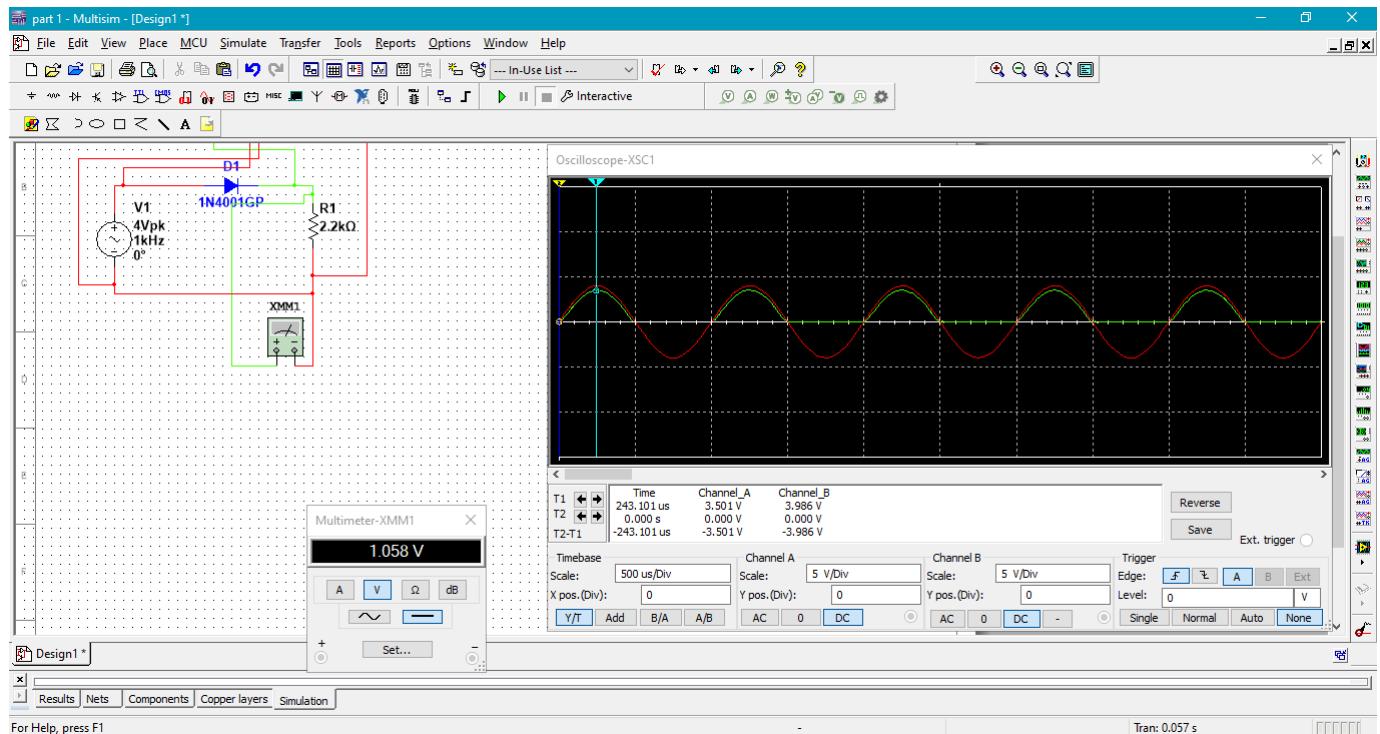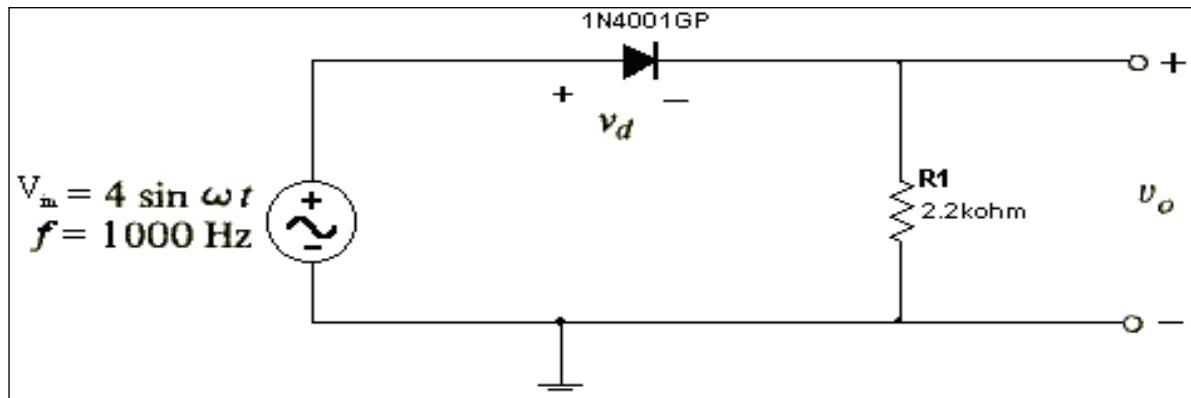- 1) Construct the circuit shown below and draw the input and output signal.





- 2) Measure the DC value of  $V_o$  using the DC scale in the DMM.  $V_{oDC}=1.058\text{ v}.....$

- 3) For step 1, calculate the DC level of the output waveform.

$$V_{avg1} = .....(3.501) \setminus \pi = 1.114\text{ v}.....$$

## Part 2: Full-Wave Rectification

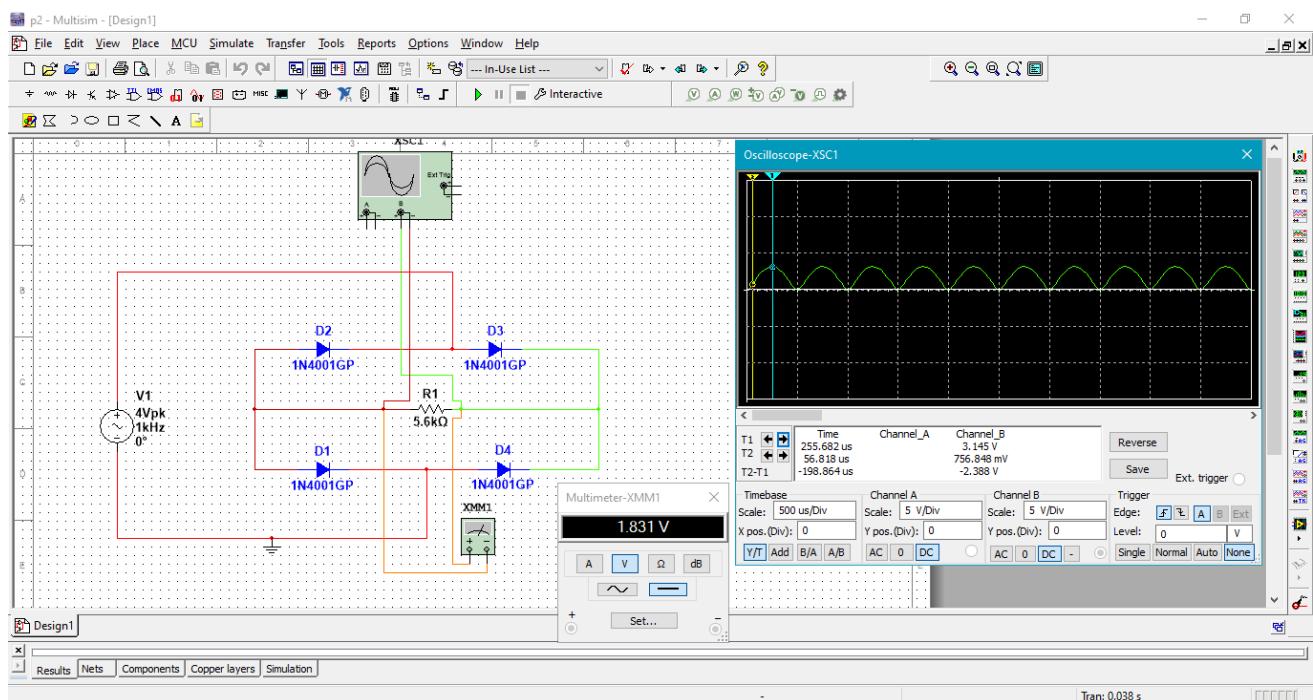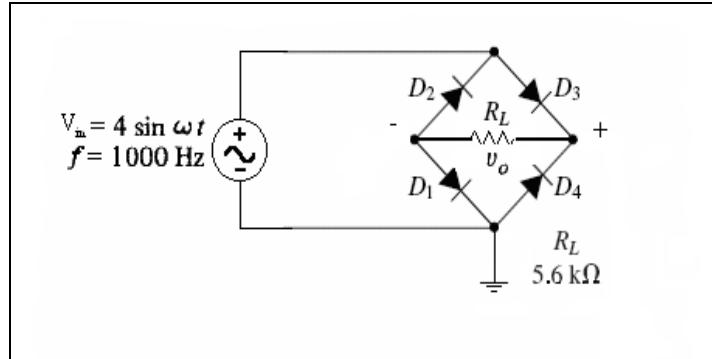
- 4) Construct the circuit shown below. Draw the output waveforms. Then,  
 5) Measure the DC load voltage using DMM.  $V_{ODC} = \dots \dots \dots \text{1.831 v} \dots \dots \dots$



- 6) Calculate the DC level of the output waveform  $V_o$ .  
 $V_{avg} = \dots \dots \dots 2(3.145) / \pi = 2.002 \text{ v} \dots \dots \dots$


### Part 3: Rectifier Filtering

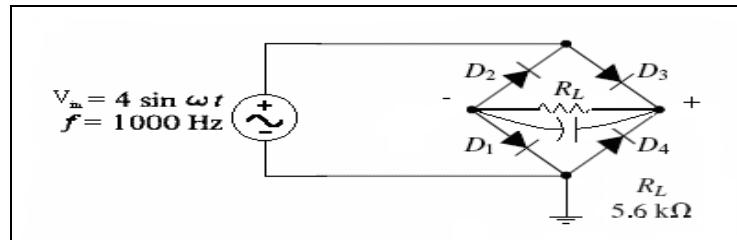- 8) Construct the circuit shown below. Use the DMM to measure  $V_o$ , and record this value.



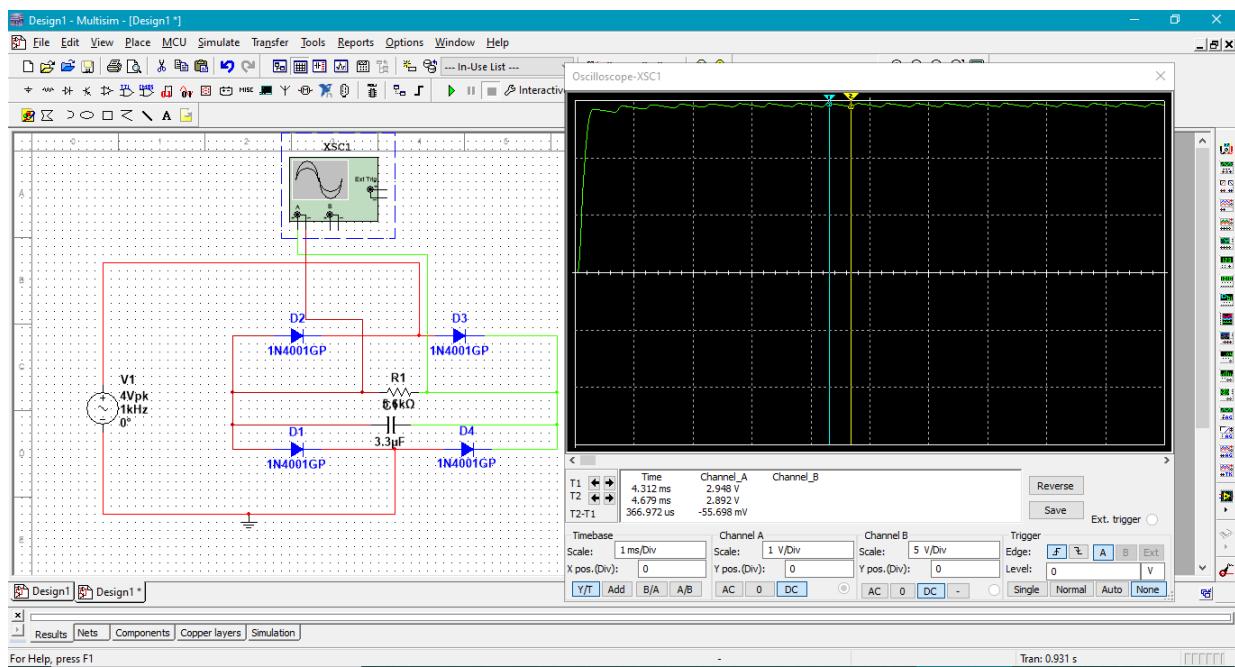
- 9) Use the oscilloscope to observe and measure the ripple voltage using  $3.3 \mu\text{F}$ .

$$V_r = \dots \dots \dots 2.948 - 2.892 = 0.056 \text{ v} \dots \dots \dots$$




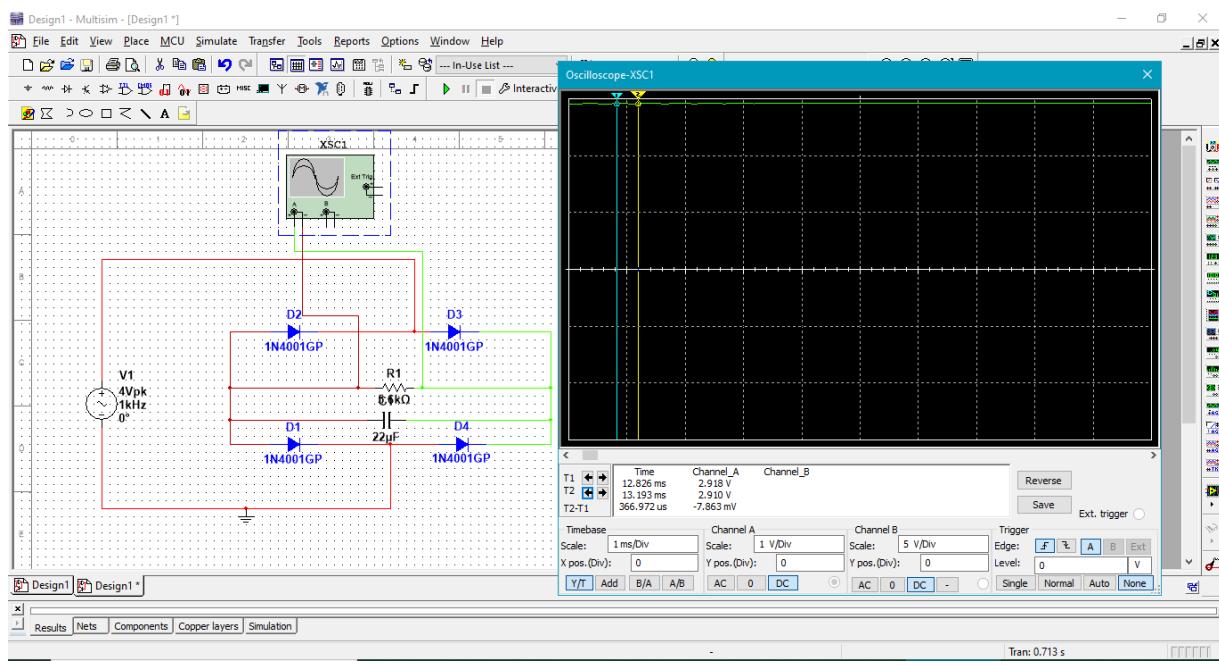
- 10) Use the oscilloscope to observe and measure the ripple voltage using  $22 \mu\text{F}$ .

$$V_r = \dots \dots \dots 2.918 - 2.910 = 0.008 \text{ v} \dots \dots \dots$$



## Part4: The Shunt Clipper with a DC Battery

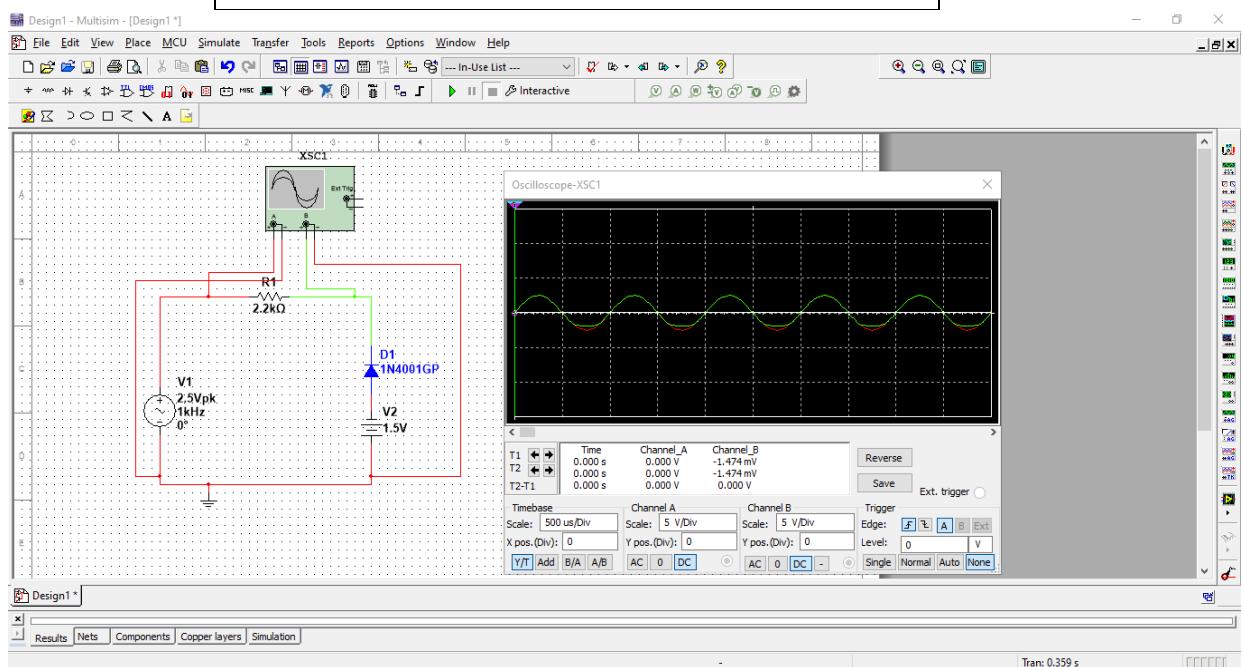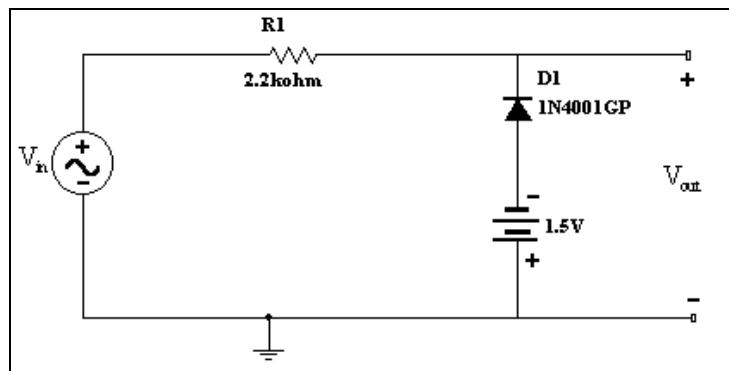1. Construct the circuit shown below. The input signal is  $5 \text{ V}_{\text{p-p}}$  sine wave at a frequency of 1KHz.
2. Draw the input and output signal.



## Part 5: the Clamper circuit with DC Battery

1. Construct the circuit shown in the figure and Set the function generator to a 1 KHz, 5-V<sub>P-P</sub> sine wave. Then sketch the output signal

