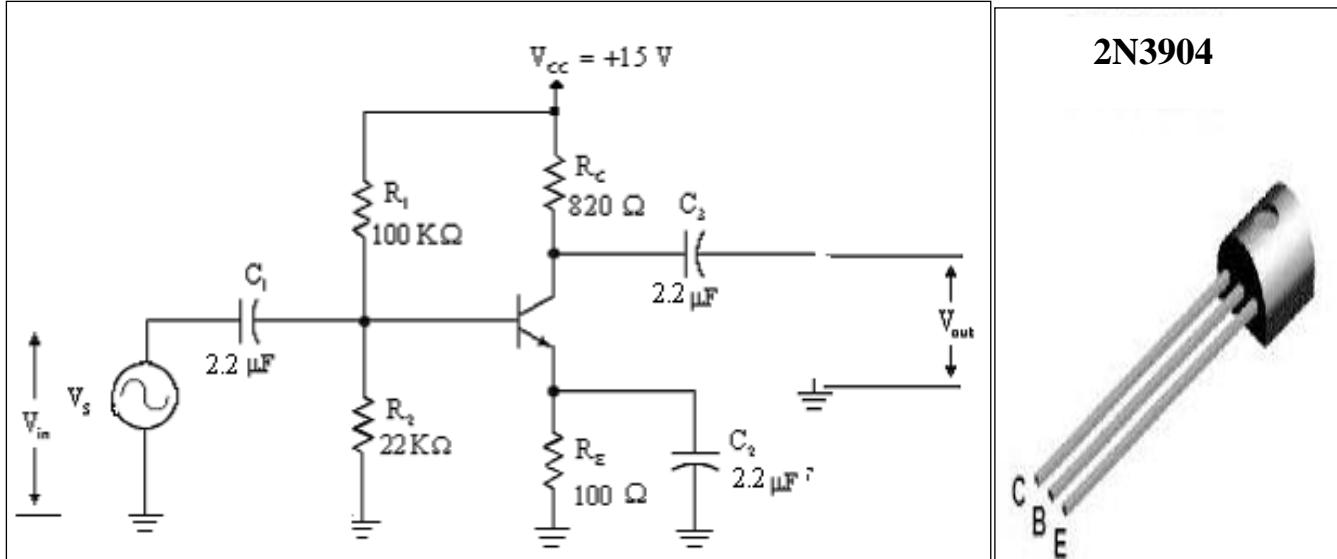


Electronics Lab
Lab Session 4: The Common Emitter Amplifier

<i>Students Names</i>	<i>Sandy ghassan fathi</i>	<i>Rami yahia hasan</i>
<i>ID</i>	<i>1834471</i>	<i>1838264</i>

- 1) Construct the circuit shown below and Measure and record the DC voltages listed in Table 1.



DC Parameter	Measured Value
\$V_B\$	1.693v
\$V_E\$	0.967v
\$V_C\$	7.118v
\$V_{CE}\$	6.151v
\$V_{BE}\$	0.725v
\$I_C\$	9.597mA
\$I_B\$	0.056mA
\$I_E\$	9.652mA
\$\beta\$	171.375
\$\alpha\$	0.99419

Table 1: DC Parameters of CE Amplifier

Calculations

$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{15 - 7.118}{820} = 9.61\text{ mA}$$



$$I_E = \frac{V_E}{R_E} = \frac{0.967}{100} = 9.67\text{ mA}$$

$$V_{th} = \frac{R_{th} * V_{CC}}{R_2} = 2.7049\text{ V}$$

$$R_{th} = \frac{R_2 * R_1}{R_1 + R_2} = 18.03\text{ K}$$

$$I_B = \frac{V_{th} - V_B}{R_{th}} = \frac{2.7049 - 1.693}{18.03} = 0.056\text{ mA}$$

DC -values

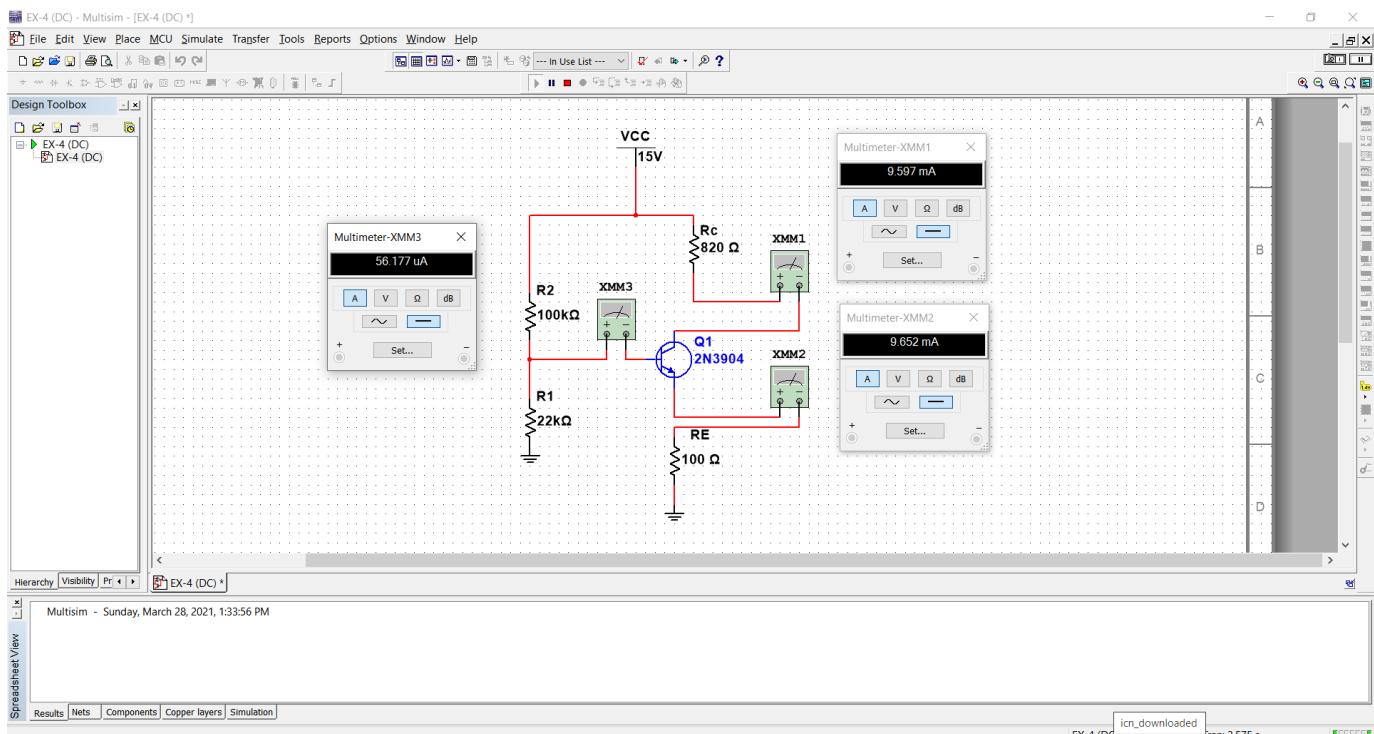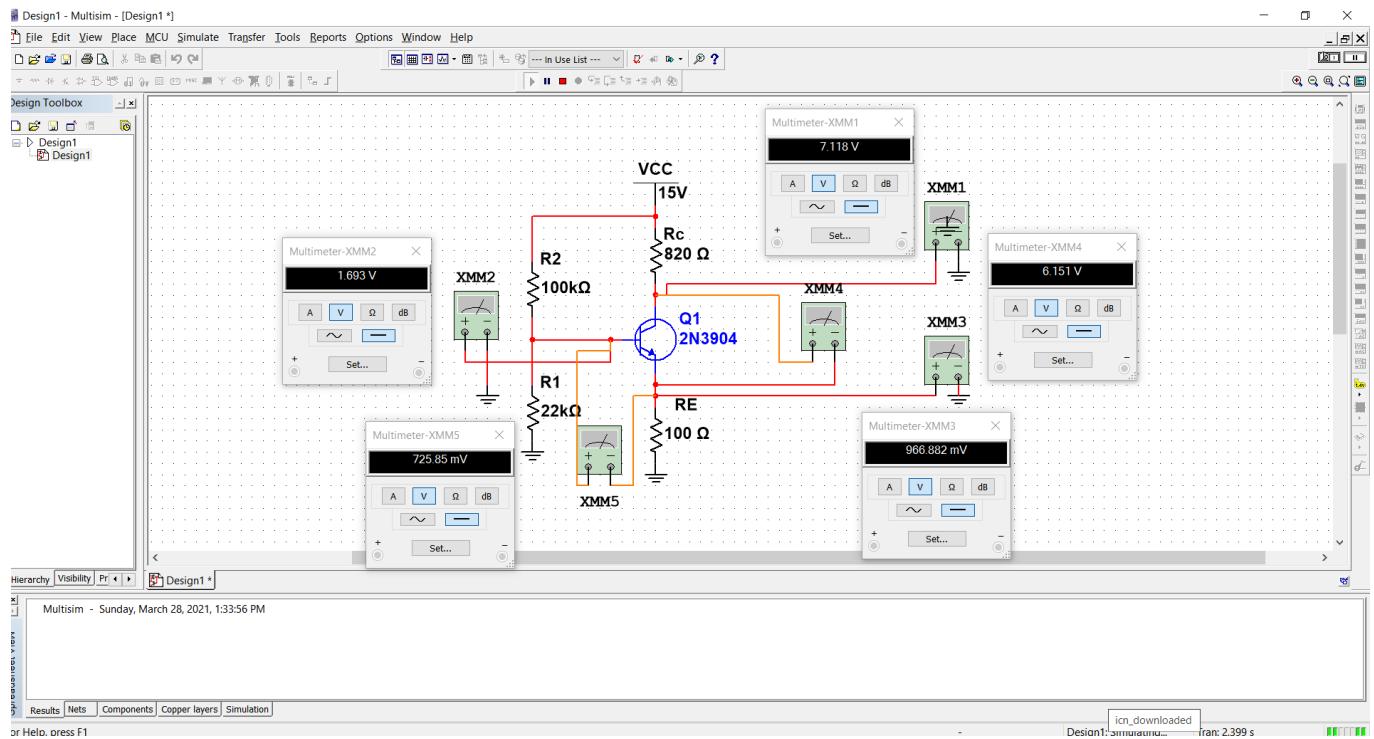

2) Connect the AC circuit with $V_s = 500 \text{ mVp-p}$ sine wave at 1.0 kHz. Fill Table2.

AC Parameter	R _E bypass
V _b = V _{in}	499.33mVP-P
r _e = 26mv/I _E	2.6887Ω
V _C = V _{out}	6.660 Vp-p
A _v = V _{out} /V _{in}	13.3226


Table.2: AC Parameters of CE Amplifier

5) Remove C_2 from the circuit and fill Table3.


AC Parameter	R _E unbypass
V _b = V _{in}	499.41 mVp-p
r _e = 26mV/I _E	2.6887Ω
V _C = V _{out}	3.935 Vp-p
A _V = V _{out} /V _{in}	7.88577

Table3: AC Parameters of CE Amplifier


Plotting of Vi with bypass

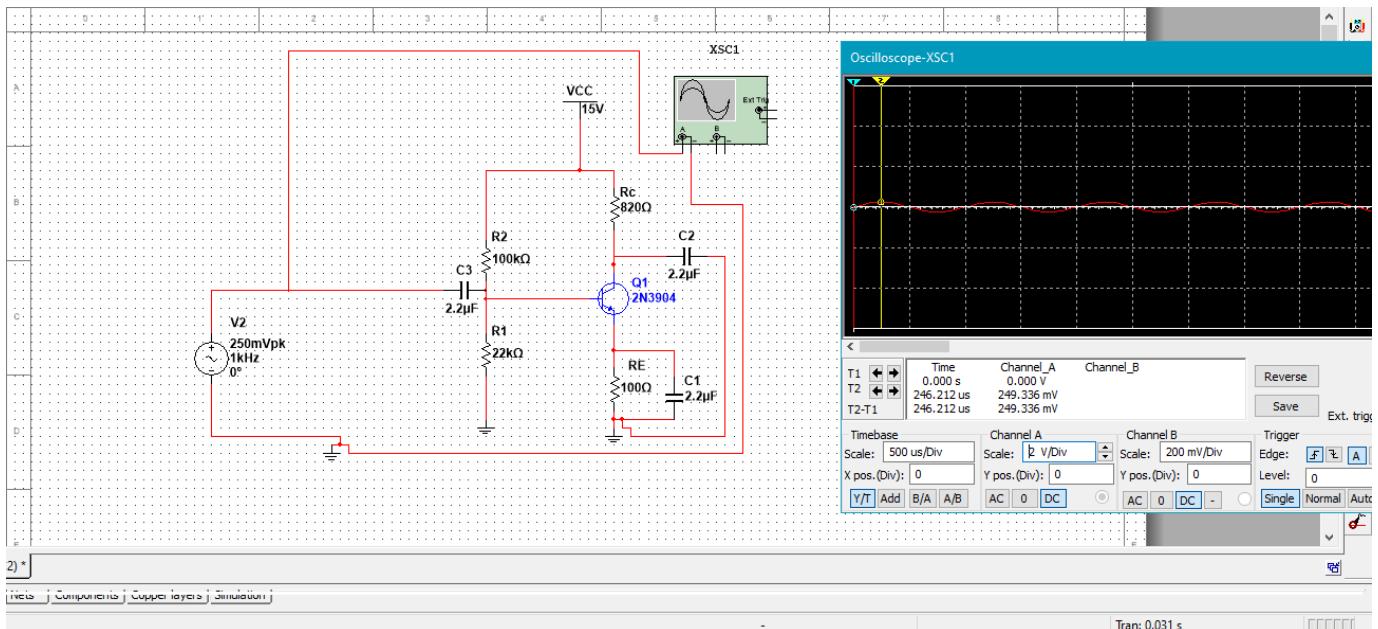


Plotting of V_i & V_o with bypass

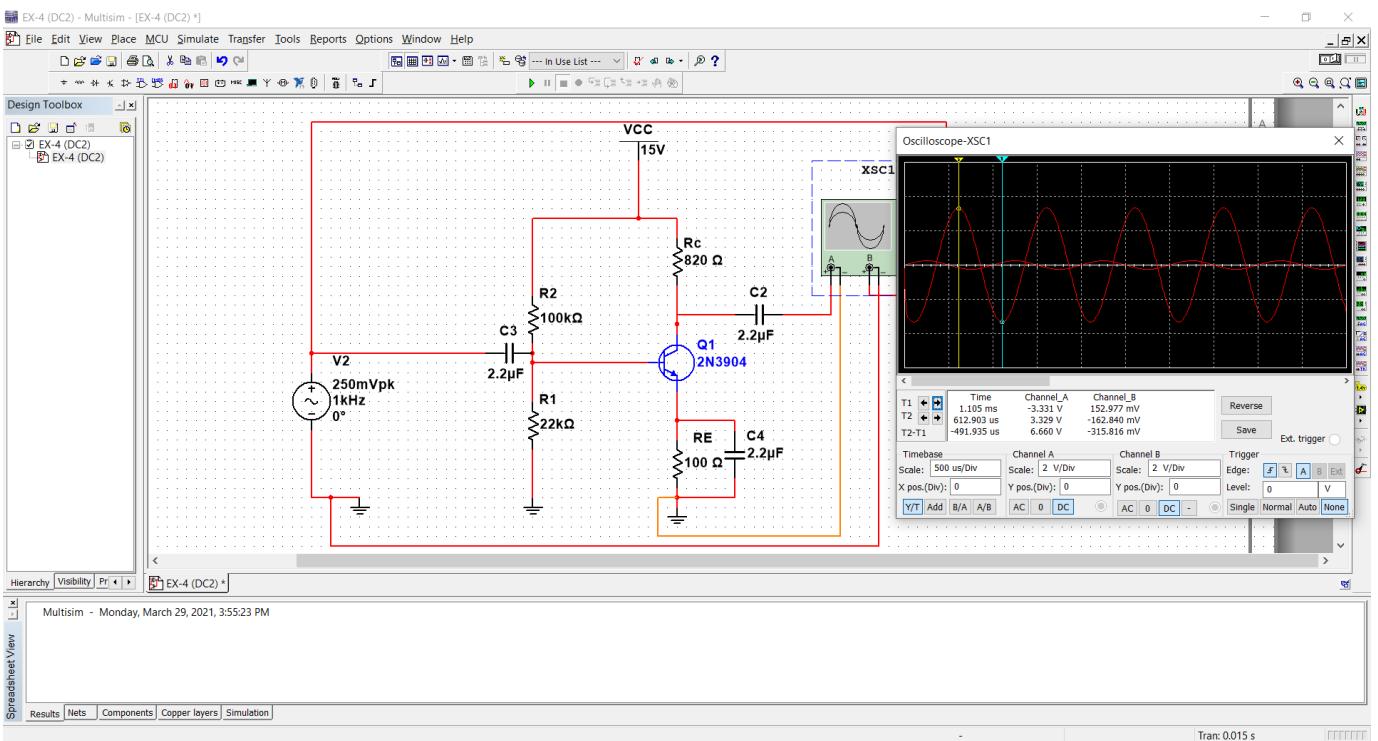


Plotting of Vi without bypass

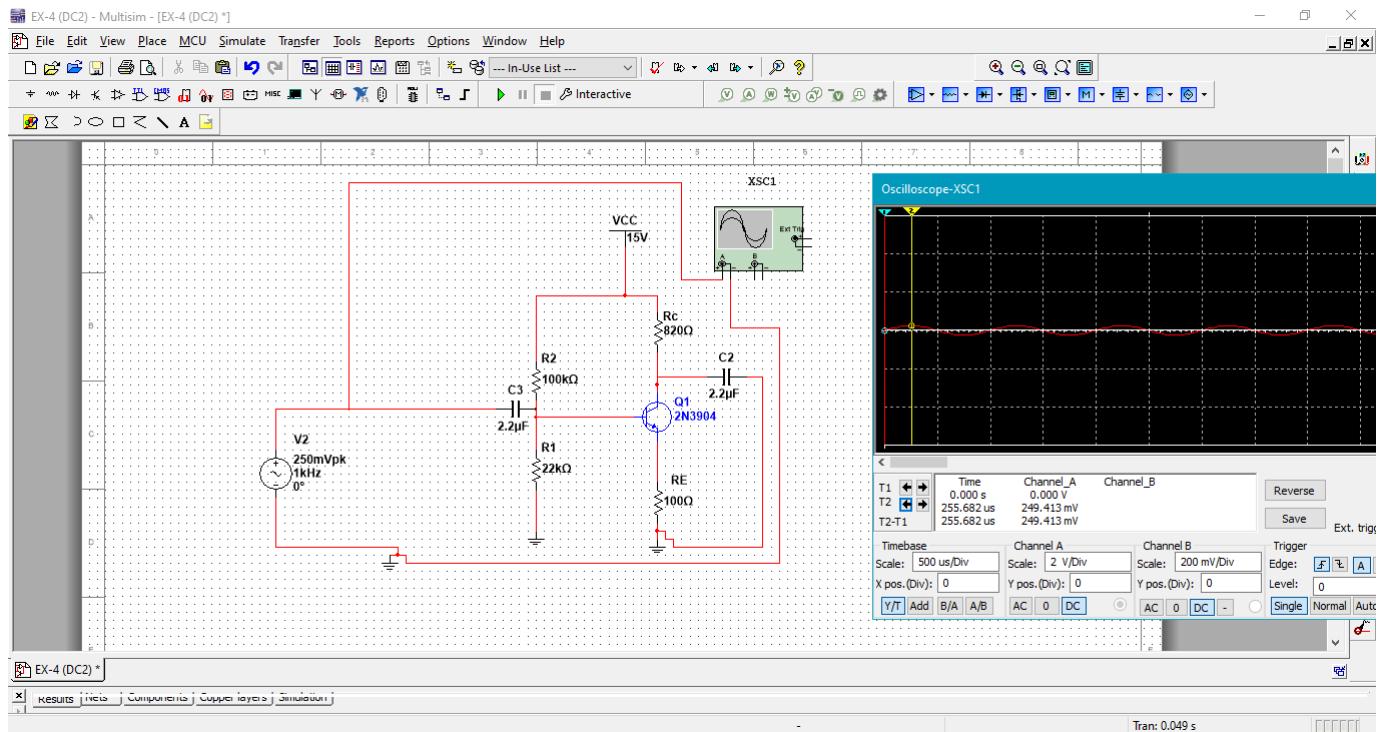


Plotting of Vi & Vo without bypass

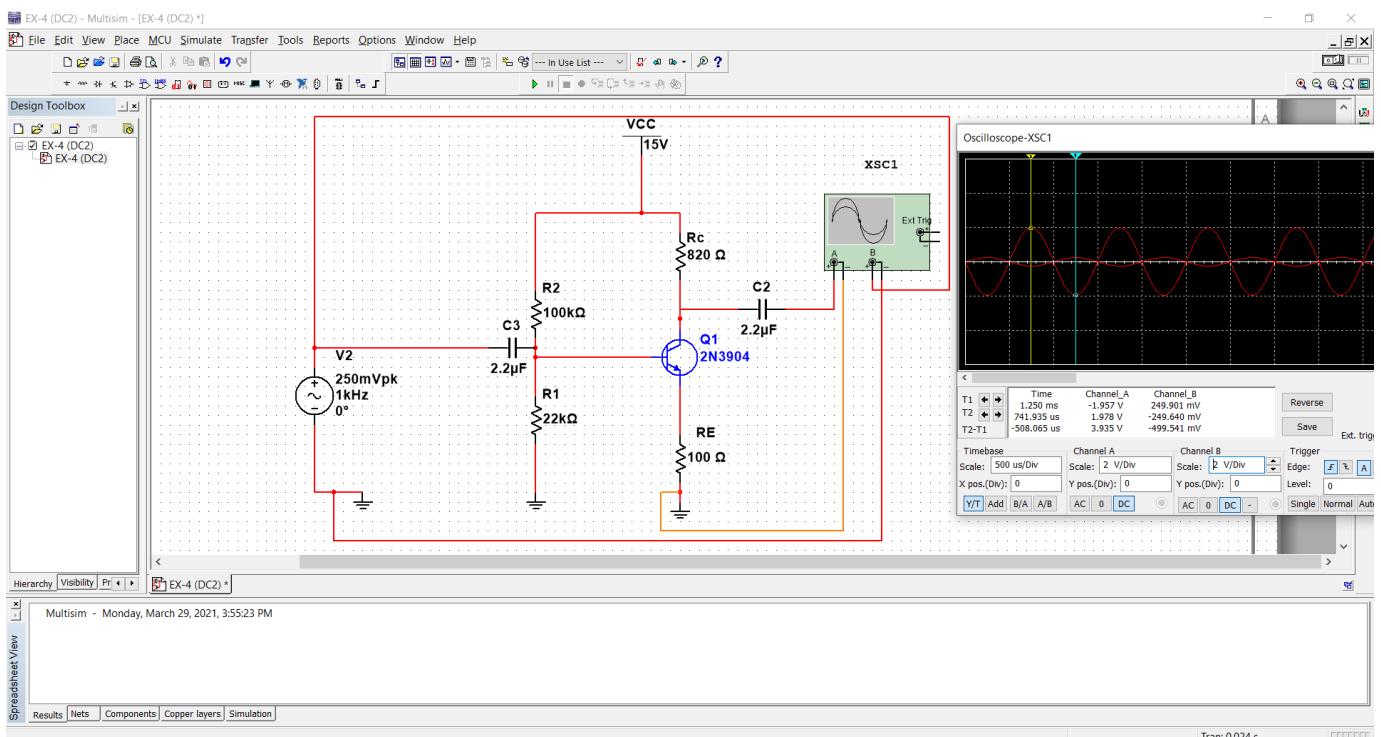

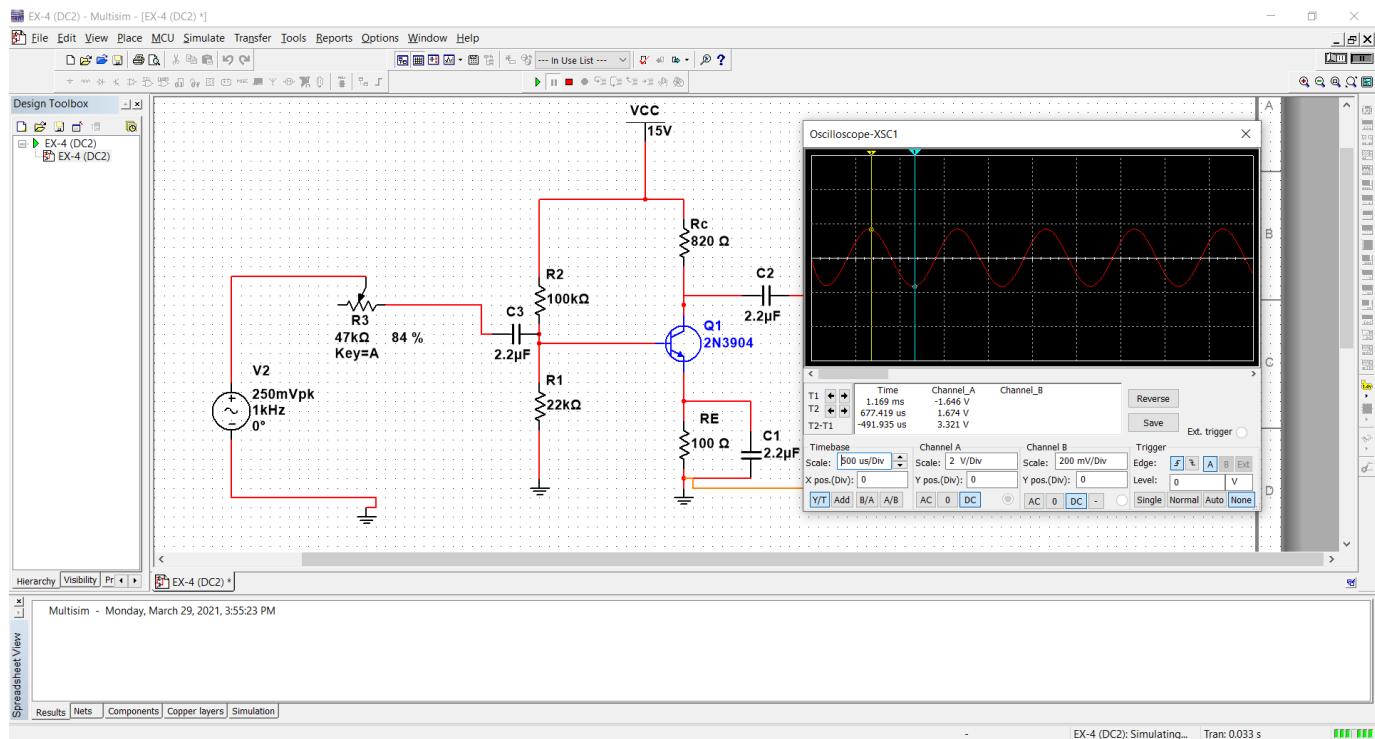
Plotting of Vo with potentiometer (input)



R INPUT VALUE

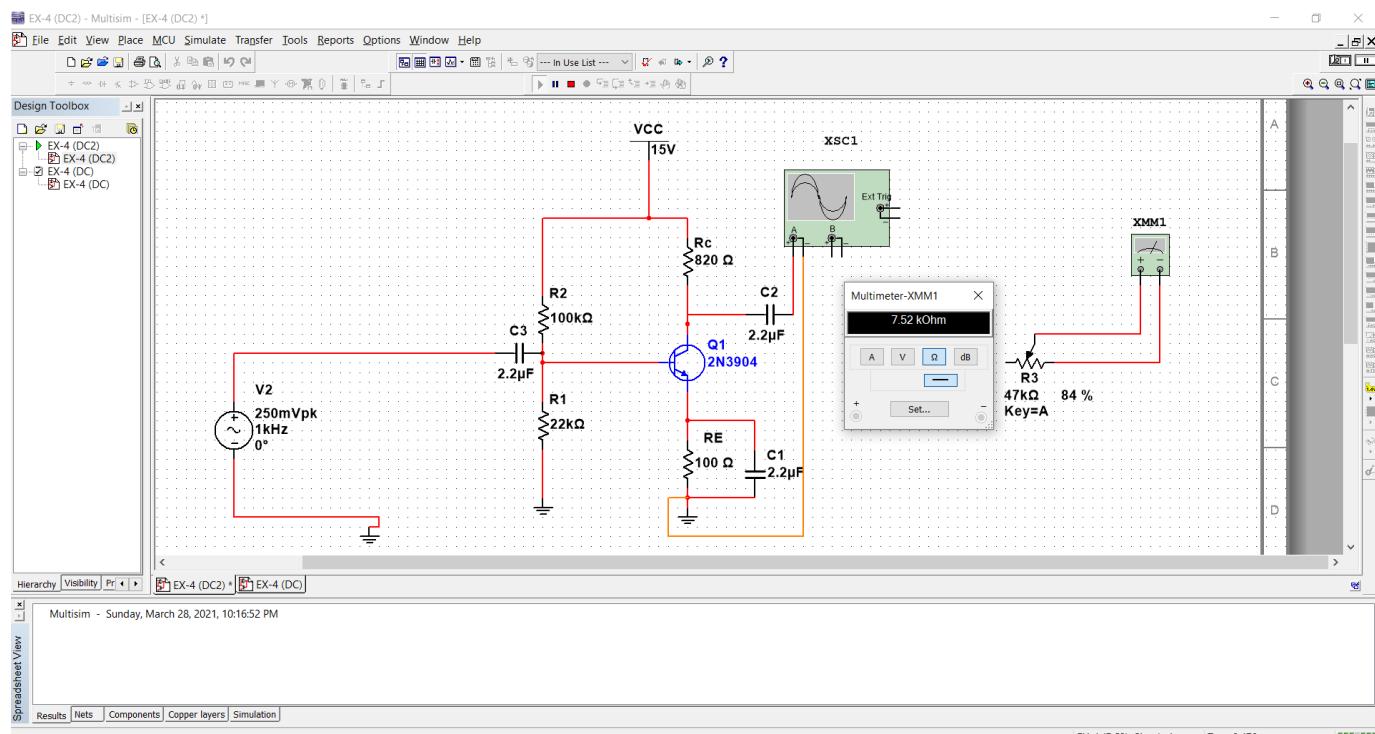

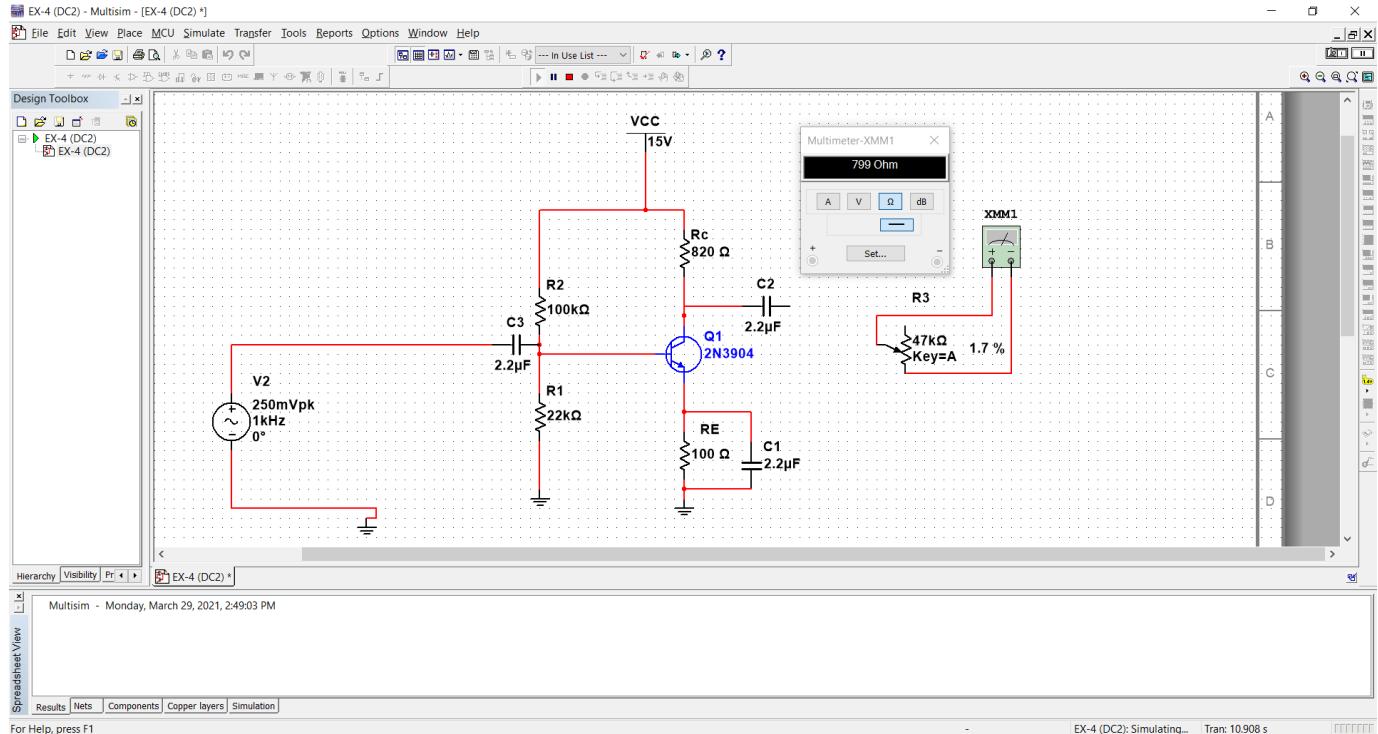Plotting of Vo with potentiometer (output)



R OUTPUT VALUE

