

Feedback sheet


17

Q₁ For the F.B amplifier shown the amplifier has:

$R_i = 1k, R_o = 5k, f_L = 500Hz$

$f_H = 50kHz, A = 50$ with:

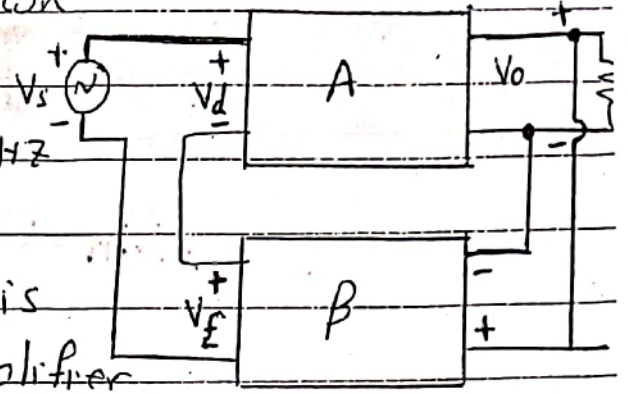No. F.B. If 8% -ve F.B is applied, recalculate the Amplifier parameters? sketch the freq. response with and without F.B?



Q₂ A current amplifier has $A_I = 40$ dB, $R_i = 2k\Omega$, $R_o = 1k\Omega$. If it is required to make $R_i = 200\Omega$


- (i) What type of -ve F.B is required, draw block diagram
- (ii) Recalculate A_I, R_o and find the required β ?
- (iii) Suggest a F.B network to realize this β ?

Q₃ For the cct. shown in Fig.

(i) What type and Topology of the F.B?

(ii) How does this F.B affect the input & output impedances.

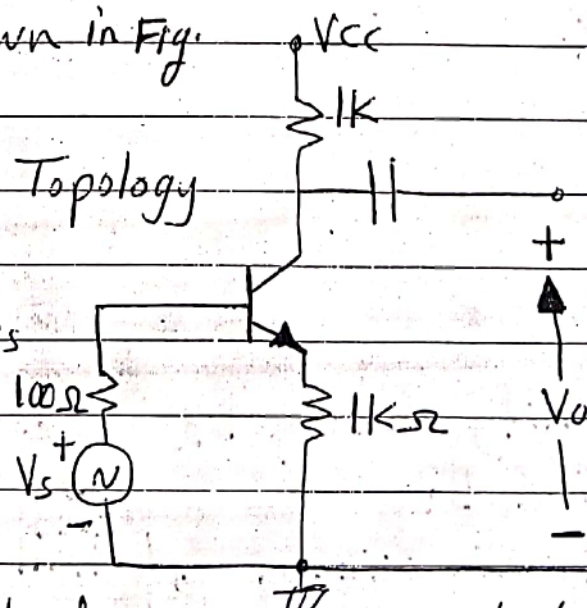(iii) Draw the block diagram representation for the above F.B.




P.T.O →

Q4

Given: $g_m = 4.5 \text{ mS}$

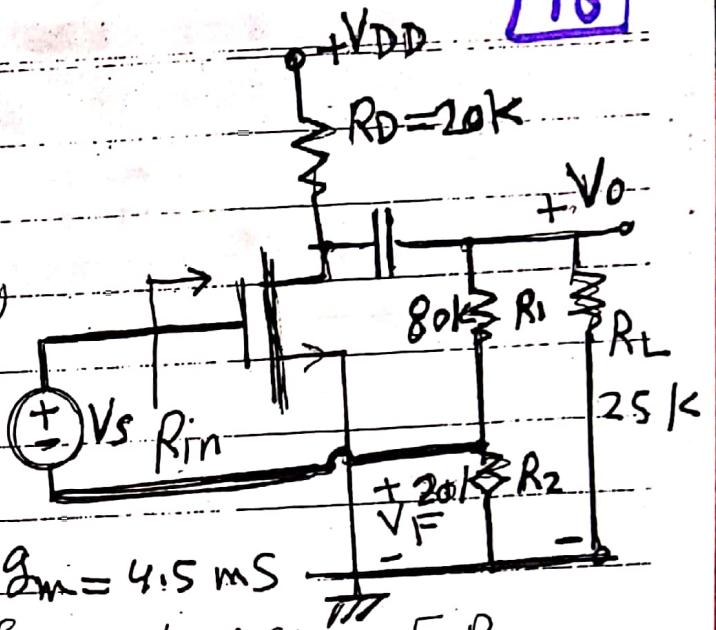- 1) Identify F.B Topology
- 2) Find A_v, R_o, β
 $A_{vF}, R_{oF}, R_{in}, R_{inF}$
- 3) If $f_L = 500 \text{ Hz}$
 $f_H = 500 \text{ kHz}$




Draw Freq. Response before and After F.B.

Q5: Consider the circuit shown in Fig.

- 1) Identify type and topology of this F.B.

- 2) Indicate X_s, X_p, X_d, X_o

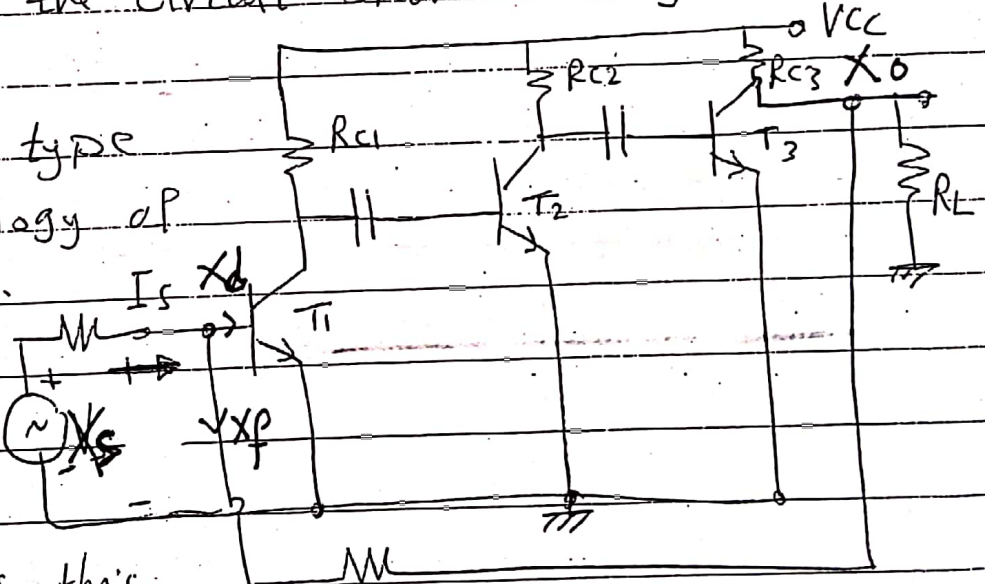


- 3) How does this F.B affect Z_i & Z_o .

- 4) Name this Amp, and indicate A type & units, β value & unit.

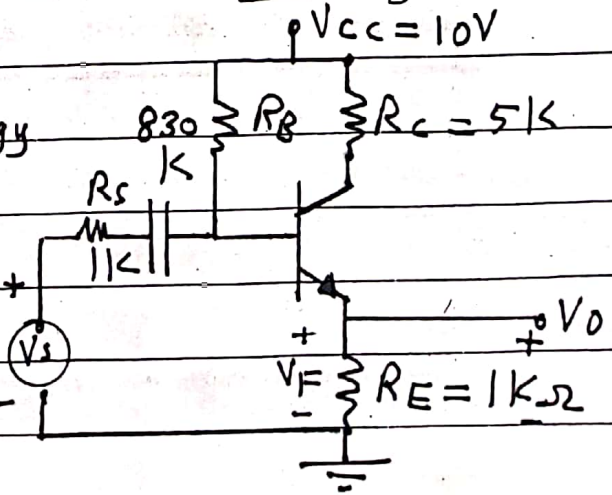
Q6: Identify the topology and find β ?

- Estimate R_{in} without F.B and with F.B?
- Sketch Block diagram.



Q₄: The F.B is through R₁ & R₂ where V_F is across R₂. Since they form a voltage divider
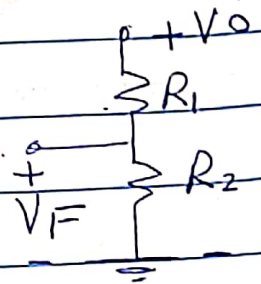
$$V_F = \frac{V_o \cdot R_2}{R_1 + R_2} \Rightarrow B = \frac{V_F}{V_o} = \frac{R_2}{R_1 + R_2} \quad \underline{\underline{VDR}}$$




i.e. $V_F \propto V_o \Rightarrow$ If $V_o = 0, V_F = 0$, No F.B"

So it is voltage from o/p, V_F is mixed in series with V_s \Rightarrow So it is "Voltage-Series" and used with "Voltage-Amplifier"

① Without F.B:
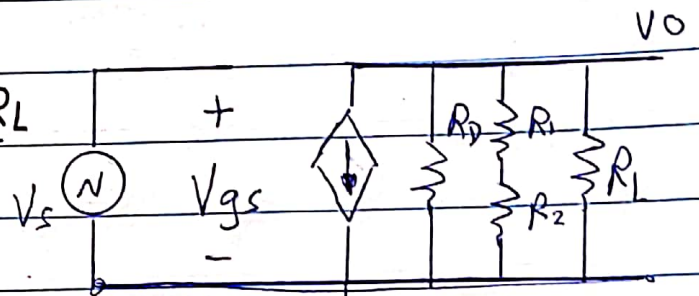
$$A_v = \frac{V_o}{V_s} = \frac{-g_m V_{gs} (R_D \parallel (R_1 + R_2) \parallel R_L)}{V_{gs}}$$



$$\infty |A_v| = g_m (R_D \parallel (R_1 + R_2) \parallel R_L)$$

$$= 4.5 (20 \parallel (100) \parallel 25) = 10 \text{K}\Omega \quad g_m = 4.5 \text{mS}$$

$$\infty |A_v| = 45$$

$$4.5 \text{mS} \quad R_D = 20 \text{K}, R_L = 25 \text{K}$$

$$R_{in} = \infty, R_o = R_D \parallel (R_1 + R_2)$$

$$R_1 = 80 \text{K}, R_2 = 20 \text{K}$$

$$= 16.666 \text{K}\Omega$$

$$f_L = 500 \text{Hz}, f_H = 500 \text{KHz}$$

with F.B: $B = \frac{V_F}{V_o} = \frac{R_2}{R_1 + R_2} = \frac{20}{100} = 0.2$


$$A_{vF} = \frac{A_v}{1 + B A_v} = \frac{45}{1 + 0.2 \times 45} = 4.5$$

$$R_{inF} = R_{in} (1 + B A_v) = \infty (10) = \infty$$

$$R_{oF} = R_o / (1 + B A) = 16.666 / 10 = 1.666 \text{K}\Omega$$

$$f_{LF} = f_L / (1 + B A) = 500 / 10 = 50 \text{Hz}$$
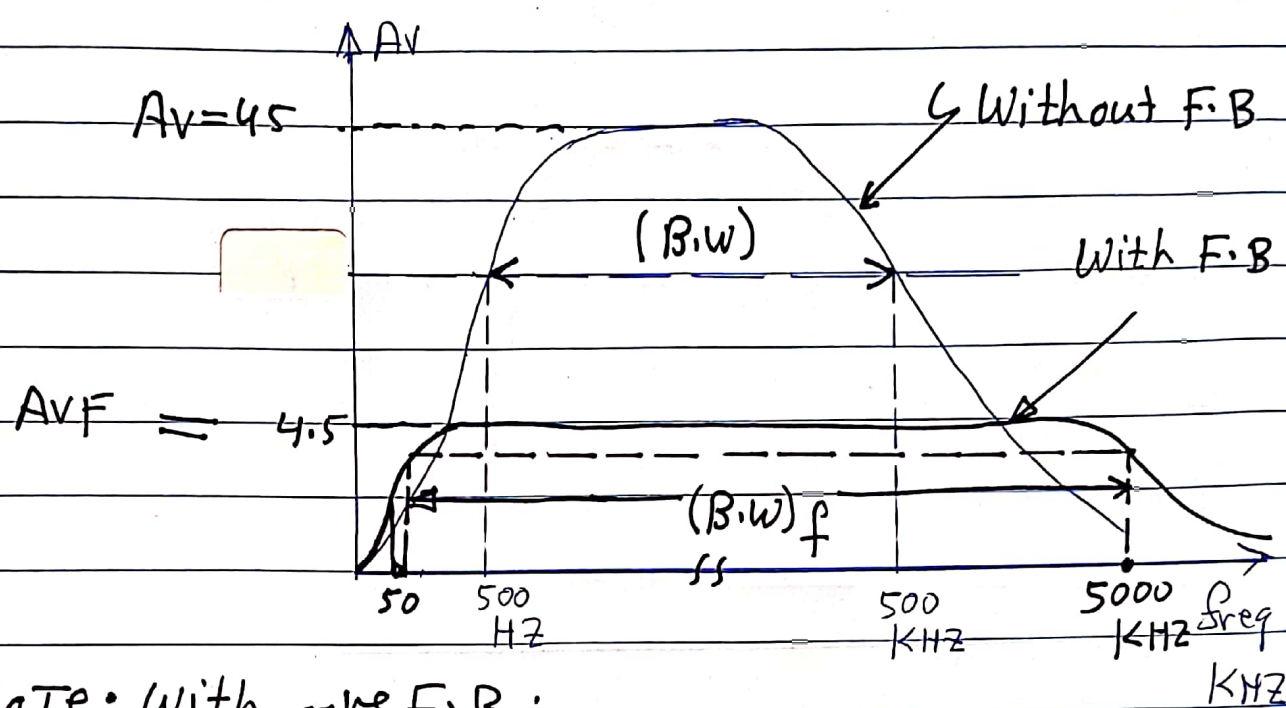
$$f_{HF} = f_H (1 + B A) = 500 \text{K} \times 10 = 5000 \text{KHz} = 5 \text{MHz}$$



Note: With -ve F.B :-

$A_v \rightarrow$ decreases

(B.W) \rightarrow extends (Increases).

* This is True Since Gain \times B.W \approx Constant.

Q5: The topology is "Voltage-Shunt"

We Sample from Node \Rightarrow Voltage

\Rightarrow Mix Current \Rightarrow Shunt.

$Z_{in f} = Z_{in} / (1 + BA)$, $Z_{o f} = Z_o / (1 + BA)$

Amp: \rightarrow Transresistance Amp.

$A = \frac{V_o}{I_s} = R(\Omega)$, $B = \frac{I_f}{V_o} \approx \frac{1}{R_f} (\Omega^{-1})$

$X_o \rightarrow V_o$

$X_f \rightarrow I_f$

$X_s \rightarrow I_s$

$X_d \rightarrow I_d$

$R_{in f}, R_{o f}$

Q6: Topology \rightarrow Voltage-Series because $V_f \propto V_o$ and

If $V_o = 0$, $V_f = 0$. $B = \frac{V_f}{V_o}$ and Since $V_f = V_o$, $B = 1$

* Without F.B. $R_{in} = R_B \parallel V_{\pi}$ (No R_E), $R_E \neq 0$

* with F.B $R_{in f} = R_B \parallel (V_{\pi} + (B+1)R_E)$

Since R_E is present and causes -ve F.B, Series \Rightarrow I/P