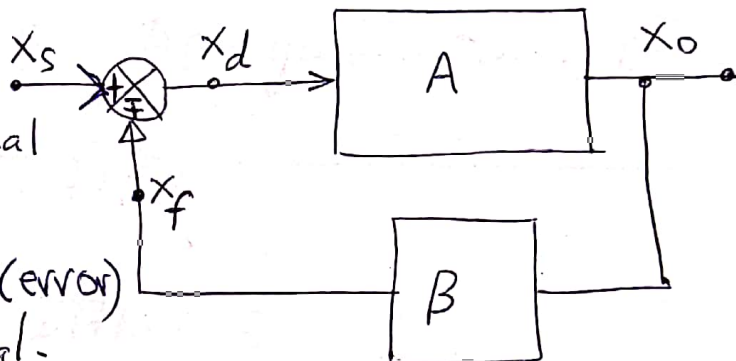


Feedback Amplifiers

F.B is a process by which a portion of the o/p is returned back to the input.

Consider the F.B System

shown in Fig. where:



$X_s \rightarrow$ is the external signal

$X_f \rightarrow$ = = feedback =

$X_d \rightarrow$ = = difference = (error)

$X_o \rightarrow$ = = output signal.

$A \rightarrow$ = = open-loop gain (gain without F.B) = $\frac{X_o}{X_d}$

$B \rightarrow$ = = Feedback ratio. $\rightarrow B = \frac{X_f}{X_o}$

Types of Feedback: According to the relation between

X_f and X_o , there are two types of F.B:

(i) If X_f opposes X_s (antiphase) this is called negative feedback and then $X_d = X_s - X_f$.
(reduces X_d)


(ii) If X_f aids X_s (inphase) this is called positive feedback and then $X_d = X_s + X_f$.
(increases X_d)

Negative Feedback (-ve F.B)

In -ve F.B, the following relations are applied:

$X_o = A X_d$, $X_d = X_s - X_f$

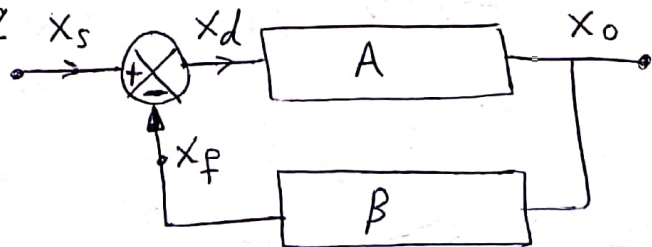$X_f = B X_o$, $A_f = \frac{X_o}{X_s}$ where : -ve F.B system.



A_f = Amplifier gain with feedback.

Effect of -ve F.B on Amplifier

(2)

The -ve F.B has the following effects:

(a) Reduce the gain: $A_f = \frac{A}{1 + \beta A}$

where:

A = gain without F.B, A_f = gain with F.B
 β = F.B factor.

(b) Extend the Bandwidth:

$$(B.W)_f = B.W (1 + \beta A)$$

where: $(B.W)_f$ = B.W with F.B

hence -ve F.B decrease f_L and increase f_H

$$f_{L_f} = f_L / (1 + \beta A), \quad f_{H_f} = f_H (1 + \beta A)$$

$f_L \Rightarrow$ low cutoff freq, $f_H \Rightarrow$ high cutoff freq.

(c) Increase Amplifier gain stability

$$\frac{dA_f}{A_f} = \frac{(dA/A)}{1 + \beta A} \text{ where}$$

(dA/A) : fractional change in gain without F.B

(dA_f/A_f) : = = = = with F.B

(d) Reduce Internal noise and nonlinear distortion.

$$X_{nf} = \frac{X_n}{1 + \beta A}, \quad D_f = \frac{D}{1 + \beta A} \text{ where}$$

X_n = Internal noise without F.B

X_{nf} = = = with =

D = nonlinear distortion without F.B

D_f = = = with =

(e) Decrease or Increase Amplifier impedances:


This effect depends on the type of -ve F.B (Topology) i.e. Connection of F.B network to the Amplifier at input and output.

Types of -ve F.B (TOPOLOGY) (Connection) 3

According to the types of signals x_s and x_o , there are four types of -ve F.B to be applied with the four types of Amplifiers.

① Voltage-Series: This topology is used with Voltage-Amplifier in which $x_s = V_s$ and $x_o = V_o$, $A = A_v = \frac{V_o}{V_s}$ and the block diagram is shown in Fig.

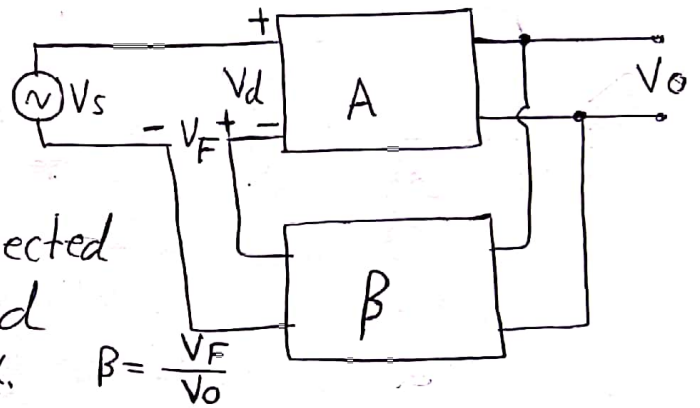This connection increase Z_i and decrease Z_o because the F.B network is connected in series with input and in parallel with output.



$$Z_{if} = Z_i(1 + \beta A), \quad Z_{of} = \frac{Z_o}{1 + \beta A}, \quad A_{vf} = \frac{A_v}{1 + \beta A}$$

② Voltage-Shunt: This type is used with (Transimpedance Amplifier) in which $x_s = I_s$, $x_o = V_o$. So the gain $A = \frac{V_o}{I_s} (\Omega)$. the block diagram is shown:


This topology Decrease both Z_i and Z_o where:

$$Z_{if} = \frac{Z_i}{1 + \beta A}$$

$$Z_{of} = \frac{Z_o}{1 + \beta A}$$

$$A = \frac{V_o}{I_s} = R_m (\Omega)$$

$$R_{mf} = \frac{R_m}{1 + \beta A}$$

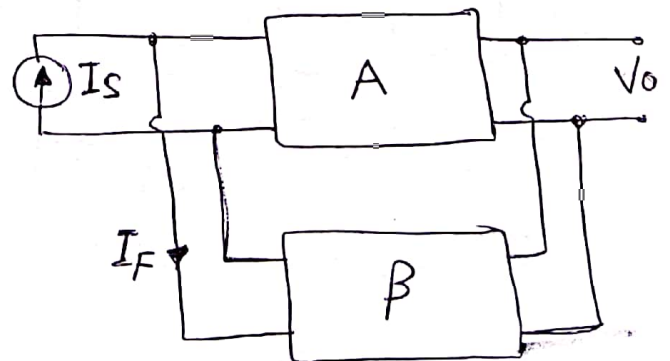


$$\beta = \frac{I_f}{V_o} \quad \Omega^{-1}$$

③ ^{o/p} Current-Shunt: This type is used with ^{i/p} (Current-Amplifier) in which $x_s = I_s$, $x_o = I_o$ so the gain $A = \frac{I_o}{I_s}$, the block diagram is shown: (4)

This topology decrease Z_i and increase Z_o

$$Z_{i_f} = \frac{Z_i}{1+\beta A}, \quad Z_{o_f} = Z_o(1+\beta A)$$
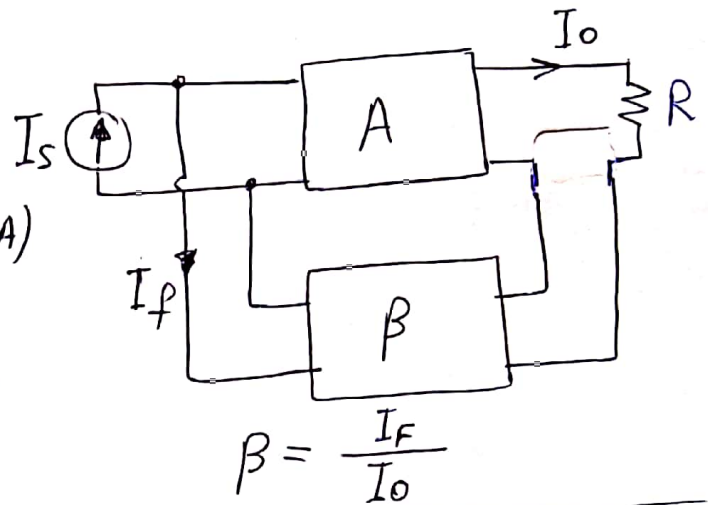
$$A = A_I = \frac{I_o}{I_s}, \quad A_{I_f} = \frac{A_I}{1+\beta A}$$




④ ^{o/p} Current-Series: This topology is used with ^{i/p} (Transconductance-Amplifier) where $x_s = V_s$, $x_o = I_o$ so its gain is $A = \frac{I_o}{V_s} = G_m(-v)$. The block-diagram is shown:

This topology Increases both input and output impedances.

$$Z_{i_f} = Z_i(1+\beta A)$$

$$Z_{o_f} = Z_o(1+\beta A)$$
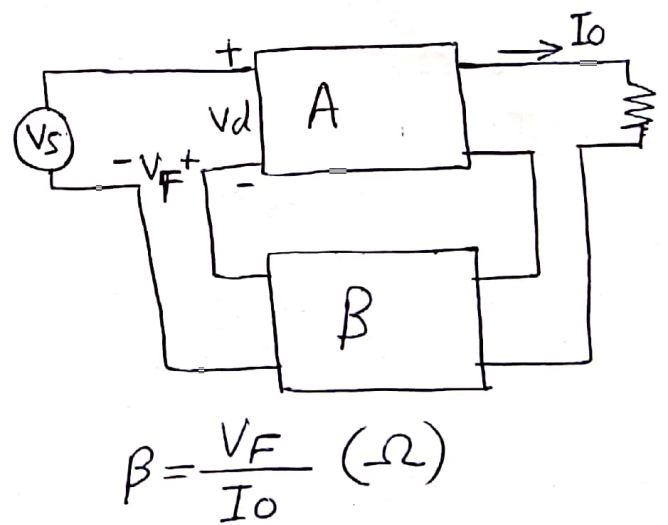
$$A_f = G_{m_f} = \frac{G_m}{1+\beta A}$$



*NOTES

- i - The product (βA) is always unitless.
- ii - Z_i, Z_o refer to impedances without F.B
- iii - $Z_{i_f}, Z_{o_f} = = =$ with -ve F.B

① Voltage-Series or (Shunt-Series) Topology


This topology is used with (Voltage-Amp.) in which $x_s = V_s$

and $x_o = V_o$

and has a transfer gain

$$A = \frac{x_o}{x_s} = \frac{V_o}{V_s} \text{ (unitless)}$$

In this topology;

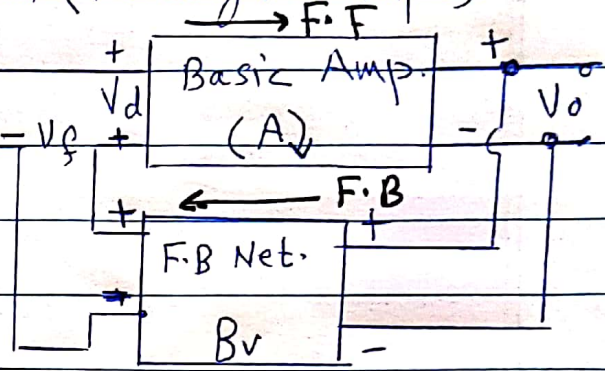

* We Sample (take) voltage (V_o) from o/p and mixe voltage with V_s .

* A : gain of basic Amp. ($A = \frac{V_o}{V_d}$)

V_d : error or difference voltage ($V_d = V_s - V_f$).

V_f : feedback voltage ($V_f = B V_o$), where

$$B = \frac{V_f}{V_o} \text{ (F.B Factor or F.B ratio)}$$

F.B net- is passive cct and has a attenuation ($B < 1$). To derive an expression for the gain with F.B (A_f) then:

① Voltage-gain $A_{vf} = \frac{V_o}{V_s}$

$$V_o = A_v V_d, \quad V_d = V_s - V_f, \quad V_f = B V_o$$

$$V_o = A_v (V_s - V_f) = A_v (V_s - B V_o) = A_v V_s + A B V_o$$

$$V_o + B A V_o = A_v V_s \rightarrow V_o (1 + B A) = A_v V_s$$

$$\frac{V_o}{V_s} = \boxed{A_{vf} = \frac{A_v}{1 + B A_v}} \text{ where}$$

A_v : gain of basic Amp. (without F.B)

A_{vf} : gain of F.F.B Amp.

$$B: \text{ F.B ratio} = \frac{V_f}{V_o}$$

* In this topology: A_v, B_v, A_{vf} have no unit i.e (unitless)

② Input Resistance: R_{in}

$$V_s = V_d + V_f = V_d + B_v V_o$$

$$V_o = A_v V_d$$

$$V_s = V_d + B_v A_v V_d$$


$$= V_d (1 + B_v A_v)$$

but $R_{in} = \frac{V_d}{I_i}$ divide by I_i

$$\frac{V_s}{I_i} = \left(\frac{V_d}{I_i} \right) (1 + B_v A_v)$$

$$R_{in} = R_{in} (1 + B_v A_v)$$

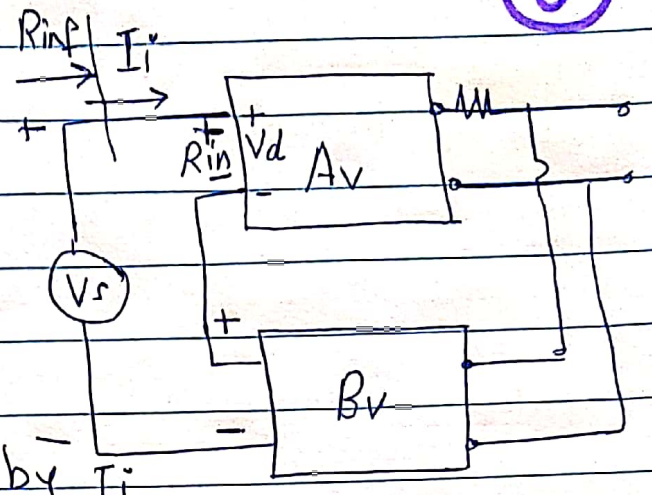i.e this connection (Series Connection) increase R_{in} .



③ Output Resistance R_{oF}

$$R_{oF} = \frac{V_x}{I_x} \quad V_s = 0$$

$$I_x = \frac{V_x - V_o}{R_o}$$

$$V_o = A_v V_d$$

$$V_d = V_s - V_f, \quad V_f = B_v V_x$$


when $V_s = 0, V_d = -V_f = -B_v V_x$

$$\therefore I_x = \frac{V_x + B_v V_x A_v}{R_o} \quad (\text{because } V_o = A_v V_d = -B_v V_x A_v)$$

$$\therefore I_x = \frac{V_x (1 + B_v A_v)}{R_o} \rightarrow \frac{I_x}{V_x} = \frac{1}{R_{oF}} = \frac{1 + B_v A_v}{R_o}$$

$$\therefore R_{oF} = \frac{R_o}{1 + B_v A_v} \quad [\text{i.e Shunt Connection Reduces } R_o]$$

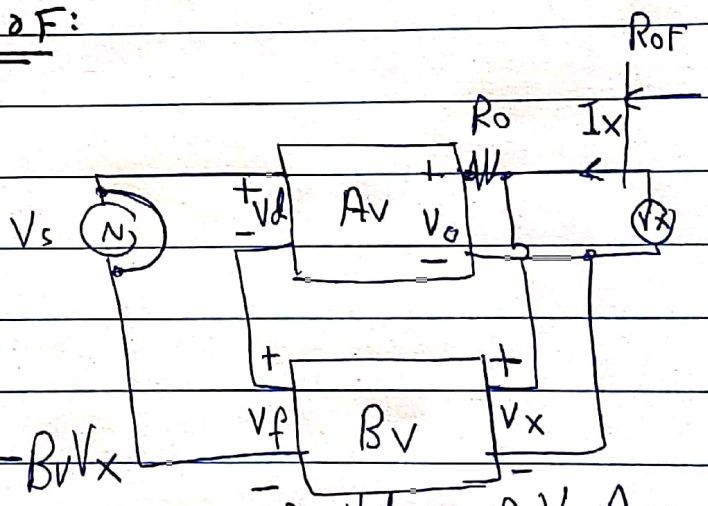This means: Series Connection increase R_i or R_o and Shunt Connection decreases R_i or R_o .
Where ever it is at input or output.



EXA: a voltage Amp. has: $A_v = 1000$, $R_{in} = 1k\Omega$, $R_o = 2k\Omega$
 $B.W = 500kHz$ and distortion $D = 100dB$. with F.B
 * If it is subjected to -ve. F.B with voltage-Series
 topology. Recalculate its parameters when the F.B
 ratio $\beta_v = 0.04$ or 4% ?

$$A_{vF} = \frac{A_v}{1 + \beta_v A_v} = \frac{1000}{1 + 0.04 \times 1000} = \frac{1000}{5} = 200$$

$$R_{inF} = R_{in} (1 + \beta_v A_v) = 1k (1 + 0.04 \times 1000) = 5k\Omega$$

$$R_o = \frac{R_o}{1 + \beta_v A_v} = \frac{2k}{1 + 0.04 \times 1000} = 400\Omega$$

$$(B.W)_F = B.W (1 + \beta_v A_v) = 500 \times 5 = 2500kHz$$

$$D_F = \frac{D}{1 + \beta_v A_v} = \frac{100}{1 + 0.04 \times 1000} = 20dB$$


Voltage-Series in Electronics cct.

In this cct. we sample
 voltage (V_o) and Mix Voltage

(V_F) so the topology

* is from o/p
 voltage \rightarrow Shunt V_s

* For input

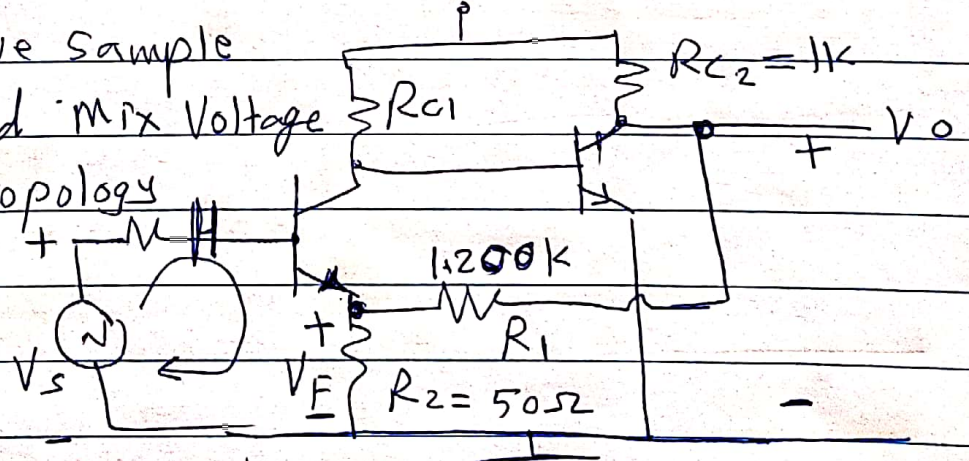


We Mix voltage (V_F) as Topology is

[Voltage-Series]

$$\beta = \frac{V_F}{V_o} = \frac{R_2}{R_1 + R_2}$$

(Voltage-divider)

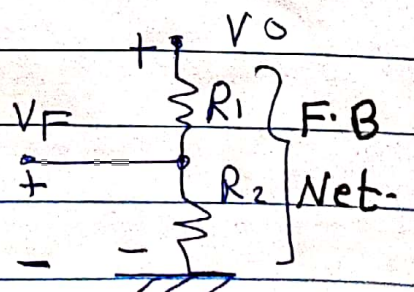

EXA: Given the Amp. has $A_v = 100$, $R_{in} = 5k\Omega$, $R_o = 1k\Omega$, $A_I = -1000$, $B.W = 100kHz$.

Recalculate A_v , R_{in} , R_o and $B.W$ after applying the F.B shown. (what is the type of Amp).

$$B_v = \frac{R_2}{R_1 + R_2} = \frac{50}{1200 + 50} = 0.04$$

Since the topology is Voltage-Series, then:

$$A_{vF} = \frac{A_v}{1 + B_v A_v} = \frac{-200}{1 + 0.04 \times 100} = \frac{-200}{5} = -40$$

$1 + B_v A_v = 1 + 0.04 \times 100$

$$A_{IF} = \frac{A_I}{1 + B_v A_v} = \frac{-1000}{1 + 0.04 \times 100} = -200 = 5$$

$$R_{inF} = R_{in}(1 + B_v A_v) = 5(5) = 25k\Omega$$


$$R_{oF} = \frac{R_o}{1 + B_v A_v} = \frac{1k\Omega}{5} = 200\Omega$$

$$(B.W)_F = B.W(1 + B_v A_v) = 100 \times 5 = 500kHz$$

The type of Amp. is Voltage-Amp.

* H.W: Identify the topology and Find: B_v , R_{vF} . assume $A_o = 1000$.

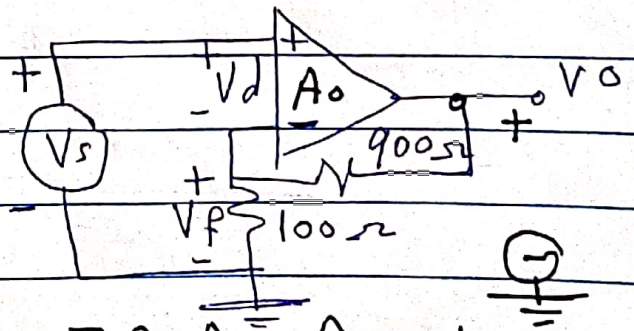* Since we sample Voltage V_o and mix. Voltage V_f so it is Voltage-Series



$$B = \frac{V_f}{V_o} = \frac{100}{100 + 900} = 0.1$$

$$A_{vF} = \frac{A_v}{1 + B A_v}, \text{ without F.B } A_v = A_o = 1000$$

$$\therefore A_{vF} = \frac{1000}{1 + 0.1 \times 1000} = 9.09$$

* For Non-Inverting Amp

$$A_v = 1 + \frac{R_2}{R_1} = 1 + \frac{900}{100} = 10$$

② Current-shunt Topology:

[Series-shunt]


* $I_o \rightarrow I_o$

$x_f \rightarrow I_f$

$x_s \rightarrow I_s$

$x_d = I_d = I_s - I_f$

* Used with Current Amp.

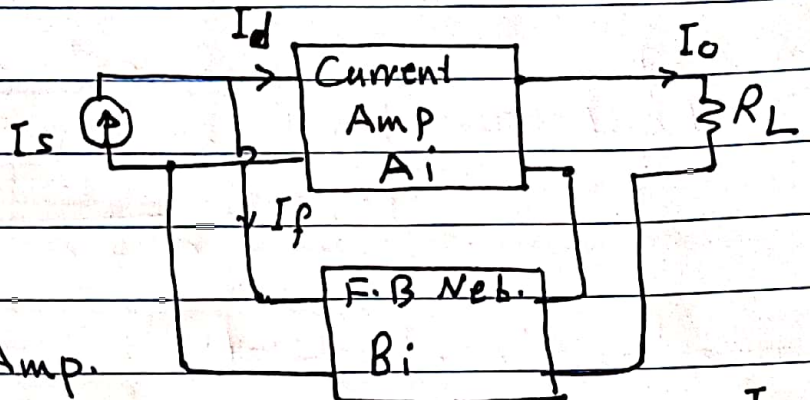

Transfer gain: $A = A_i \Rightarrow$ Current gain (unitless) = $\frac{I_o}{I_d}$

F.B factor: $B = B_i = \frac{I_f}{I_o}$ (unitless)

EXAMPLE:

A current Amp. has the following parameters before F.B: $A_i = 10^3$, $R_{in} = 10k\Omega$, $R_o = 20k\Omega$, $B.W = 200kHz$.

It is required to make $R_{in} = 1k\Omega$. Identify the required Topology and calculate Amp. parameters with F.B? Find A_{if} , R_{of} , $(B.W)_f$.

* The required topology is Current-shunt.

$$R_{inf} = \frac{R_{in}}{1 + B_i A_i} \rightarrow 1k\Omega = \frac{10k}{1 + B_i A_i} \rightarrow 1 + B_i A_i = 10$$

$$\therefore B_i = \frac{9}{A_i} = \frac{9}{1000} = 0.009$$

$$R_{of} = (1 + B_i A_i) R_o = 10 \times 20 = 200k\Omega$$

$$A_{if} = \frac{A_i}{1 + B_i A_i} = \frac{1000}{10} = 100$$

$$(B.W)_f = (1 + B_i A_i) (B.W) = 10 \times 200 = 2000kHz = 2MHz.$$

* If the gain is changed by 20% before F.B calculate the percentage change in gain after F.B


$$\frac{dA_f}{A_f} = \frac{(dA/A)}{1 + B_i A_i} = \frac{20\%}{10} = 2\%$$

Circuit diagram:

* A portion of I_o (I_f) is returned to input

The F.B factor:

$$\beta_i = \frac{I_f}{I_o}$$

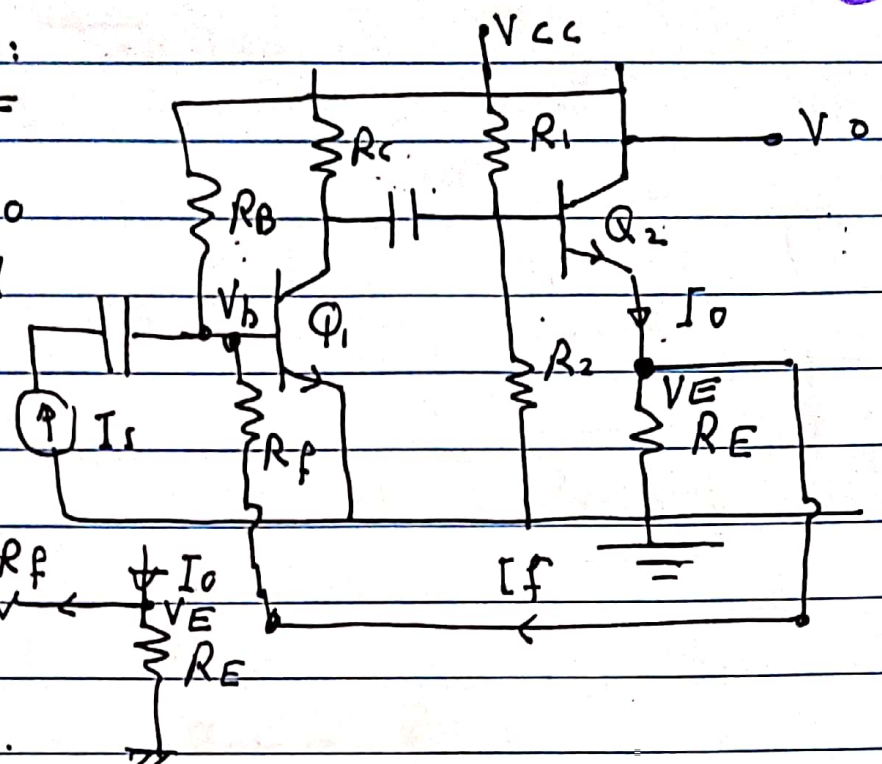

Since $V_E \gg V_b$ (Amplification).

V_b can be considered ground compared to V_E .

i.e R_E and R_F can be considered in parallel

So Current division rule is applied:

$$I_f = \frac{I_o \cdot R_E}{R_E + R_F} \Rightarrow \frac{I_f}{I_o} = \beta_i = \frac{R_E}{R_E + R_F}$$

* The above amp. has $R_i = 1k\Omega$, $R_o = 100\Omega$ and a gain $A_i = 100$, $B.W = 150kHz$. a negative F.B is applied with (R_E & R_F). calculate Amp. parameters when $R_E = 1k\Omega$, $R_F = 99k\Omega$.

Solution: $\beta_i = \frac{R_E}{R_E + R_F} = \frac{1}{1 + 99} = 0.01$

$$1 + \beta_i A_i = 1 + 0.01 \times 100 = 2$$

$$A_{if} = \frac{A_i}{(1 + \beta_i A_i)} = \frac{100}{2} = 50$$

$$R_{if} = \frac{R_i}{(1 + \beta_i A_i)} = \frac{1}{2} = 0.5k\Omega$$

$$R_{of} = R_o (1 + \beta_i A_i) = 100 \times 2 = 200\Omega$$

$$(B.W)_f = (B.W)(1 + \beta_i A_i) = 150 \times 2 = 300kHz$$

③ Voltage-shunt Topology:

We Sample Voltage and Mix \rightarrow Current:


$$x_o = V_o, x_s = I_s$$

$$x_d = I_d, x_f = I_f$$

$$A = \frac{V_o}{I_s} = A_z = \Omega$$

Transresistance Amp.
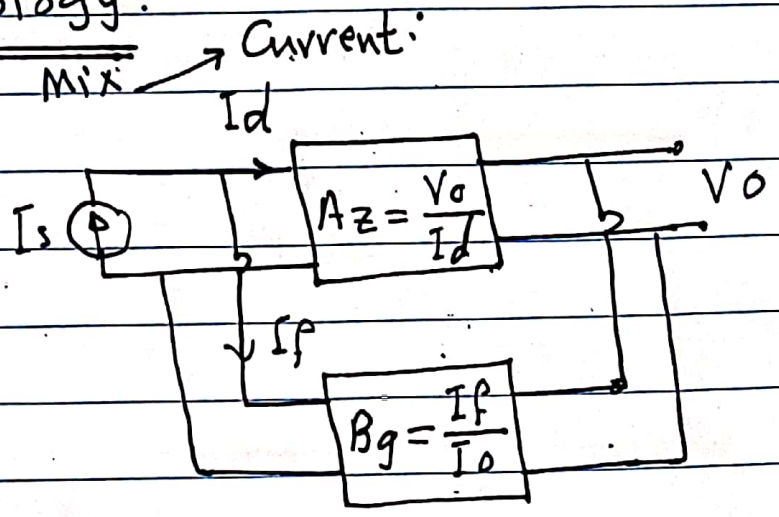
$$B = \frac{I_f}{V_o} = B_g (\Omega^{-1})$$



B is connected with A... shunt i/p, shunt o/p.

$$So \quad Z_{if} = \frac{Z_i}{1+BA}, \quad Z_{of} = \frac{Z_o}{1+BA}$$

$$(A_z)_f = \frac{A_z}{1+A_z B_g}$$

EXAMPLE: A transresistance Amp. has $A_z = 1000$

$R_{in} = 5000 \Omega, R_o = 2000 \Omega, (BW) = 20 \text{ KHz}$.

* If a F.B with $B_g = 0.009 \text{ semins } (\Omega^{-1})$. Calculate Amp. parameters with F.B.

Solution:

$$(A_z)_f = \frac{A_z}{1+BA} = \frac{1000}{1+0.009 \times 1000} = 100 \Omega$$

$$(B.W)_f = (B.W)(1+BA) = 20 \times 10 = 200 \text{ KHz}$$

$$Z_{of} = \frac{Z_o}{1+BA} = \frac{2000}{10} = 200 \Omega$$

$$Z_{if} = \frac{Z_i}{1+BA} = \frac{5000}{10} = 500 \Omega$$

* If the Amp. has a distortion of 80 dB after F.B what is the Distortion before F.B? $D_f = D/(1+BA) \Rightarrow D = D_f(1+BA) = 800 \text{ dB}$


Circuit diagram: (Example).

$V_o \gg V_b$ (Amplifier)

$$I_f = \frac{V_o - V_b}{R_f} \Rightarrow I_f \approx \frac{V_o}{R_f}$$

$$B = \frac{x_f}{x_o} = \frac{I_f}{V_o} = \frac{1}{R_f} (\Omega^{-1})$$
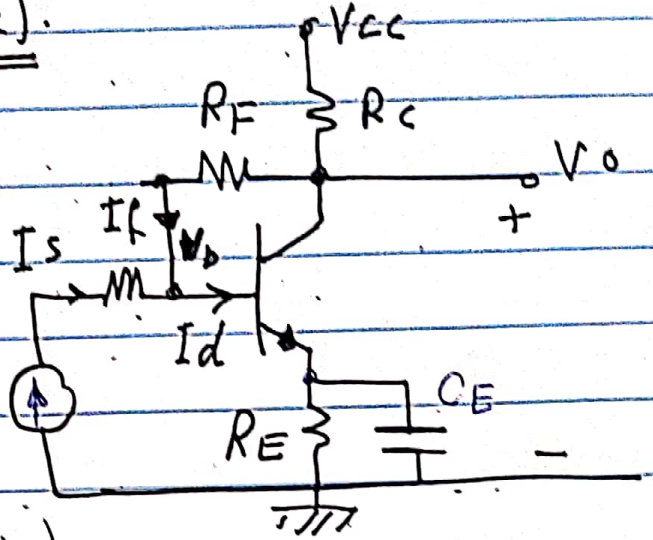
$$A = \frac{V_o}{I_s} = A_z \text{ (Transfer gain)}$$



EXA: For the above ckt. the Amp. has a transfer gain $A_z = \frac{V_o}{I_s} = 1000 \Omega$, $R_{in} = 2k\Omega$, $R_o = 1k\Omega$
 Distortion $D = 50dB$, noise $X_n = 10mV$.
 Recalculate Amp. parameter when $R_f = 250\Omega$.

$$B_g = \frac{1}{R_f} = 1/250 = 0.004 \Omega^{-1}$$

$$1 + BA = 1 + 0.004 \times 1000 = 5$$

$$(A_z)_f = 1000/5 = 200 \Omega$$

$$R_{if} = R_{in}/(1 + BA) = 2k/5 = 400 \Omega$$

$$R_{of} = R_o/(1 + BA) = 1k/5 = 200 \Omega$$

$$D_f = D/(1 + BA) = 50/5 = 10dB$$

$$X_{nf} = X_n/(1 + BA) = 10mV/5 = 2mV$$

* Recalculate A_z , R_{if} , R_{of} , $(B.W)_f$, D_f & X_{nf}

When $R_f = 2.5 \Omega$? $B_z = 1/R_f = 0.4$, $1 + BA = 401$


$$A_{zf} = A_z / (1 + B_g A_z) = \frac{1000}{1 + 0.4 \times 1000} = 2.493 \Omega \approx 2.5 \Omega$$

Since $BA \gg 1 \Rightarrow A_f = \frac{1}{B} \approx 2.5 \Omega$

$R_{if} =$, $R_{of} =$, $(B.W)_f =$

$D_f =$, $X_{nf} =$

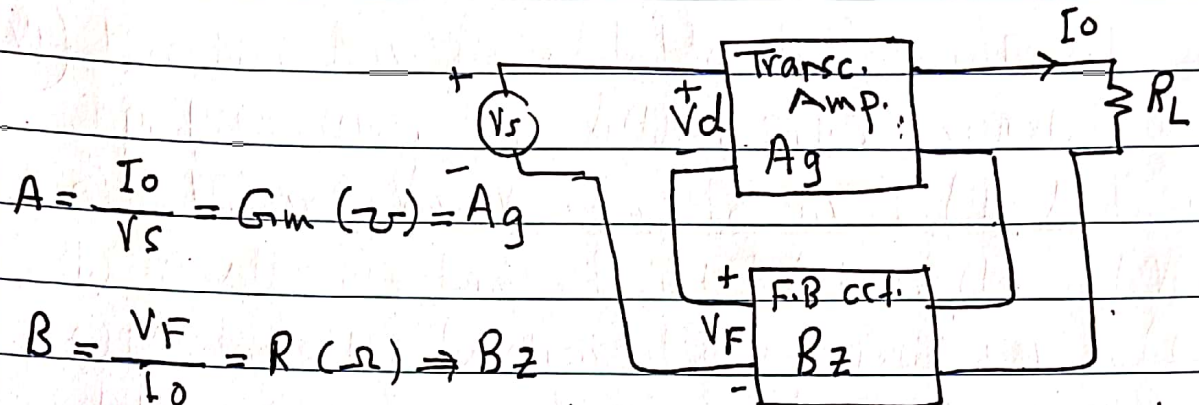④ Current-Series or Series-Series Topology.



$$A = \frac{I_o}{V_s} = G_m (\Omega) = A_g$$

$$B = \frac{V_f}{I_o} = R (\Omega) \Rightarrow B_z$$

* This topology is used with Transconductance Amp.

$$A_{gf} = \frac{A_g}{1 + B_z A_g} (\Omega) \text{ Transconductance}$$

* Both Rin and Ro will be increased because F.B. ckt. is connected in series with Basic Amp. from both side input & output. So:

$$R_{if} = R_{in}(1 + B_z A_g), R_{of} = R_o(1 + B_z A_g)$$

* $B_z A_g$ has no unit (unitless).

EXAMPLE: A transconductance Amp. has a transfer gain $A_g = 400 \text{ Sem.}(\Omega)$, $R_{in} = 1k\Omega$, $R_o = 2k\Omega$, $B.W = 200kHz$ and distortion $D = 100dB$. If a -ve F.B with Current-Series topology is applied with $B_z = 0.01 \Omega$.

* Recalculate Amp. parameter After F.B:

Solution:


$$A_{gf} = \frac{A_g}{1 + B_z A_g}, B_z A_g = 0.01 \times 400 = 4, (1 + B_z A_g) = 5$$

$$\therefore A_{gf} = 400 / 5 = 80 \Omega, (B.W)_f = 200 \times 5 = 1MHz$$

$$R_{if} = R_i(1 + B_z A_g) = 1 \times 5 = 5k\Omega, D_f = 100 / 5 = 20dB$$

$$R_{of} = R_o(1 + B_z A_g) = 2 \times 5 = 10k\Omega$$

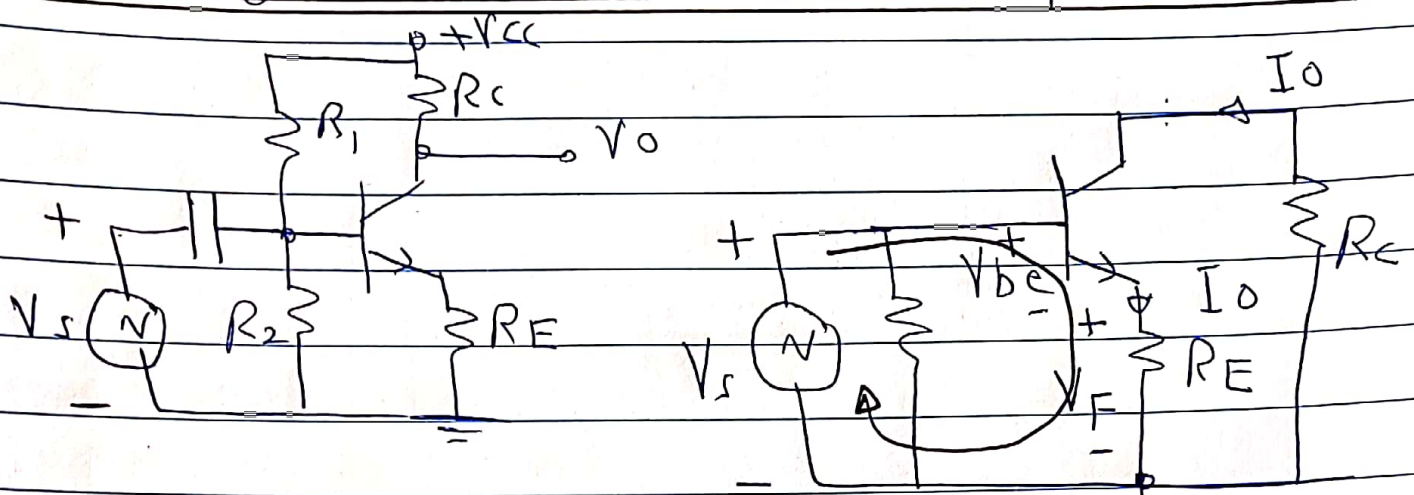Cct. diagram with "Series-Series" Topology:



* There is a F.B in RE which is VF, this VF opposes Vs, where $-V_s + V_{be} + V_F = 0$

∴ $V_{be} = V_s - V_F$ so -ve F.B.

$V_F = I_o \cdot R_E$ i.e $V_F \propto I_o$ which is the Current in o/p loop.

* So from o/p we sample a Current and from input we Mix. a Voltage so the topology is "Current-Series".

$$B = \frac{x_F}{x_o} = \frac{V_F}{I_o} = \frac{I_o \cdot R_E}{I_o} = R_E (\Omega).$$

$$A = \frac{I_o}{V_s} = g_m.$$

EXAMPLE: The above Amp. has $A_g = \frac{I_o}{V_s} = 100 \text{ S}$
 $R_i = 10 \text{ k}\Omega, R_o = 1 \text{ k}\Omega, \text{BW} = 100 \text{ kHz}$

* Recalculate Amp. parameters when $R_E = 25 \Omega$.

$$A_{gf} = A_g / (1 + B A_g), \quad 1 + B A_g = 1 + 100 \times \frac{1}{25} = 5$$

$$\therefore A_{gf} = 100 / 5 = 20, \quad (\text{BW})_f = 100 \times 5 = 500 \text{ kHz}$$

$$R_{if} = R_i (1 + B A) = 10 \times 5 = 50 \text{ k}\Omega$$

$$R_{of} = R_o (1 + B A) = 1 \times 5 = 5 \text{ k}\Omega.$$

ExA: 2 Given $\beta, R_1, R_2, R_c, R_E$


Calculate A_v, R_{in}

When C_E :


1) exists \checkmark

2) Removed

and Comment.

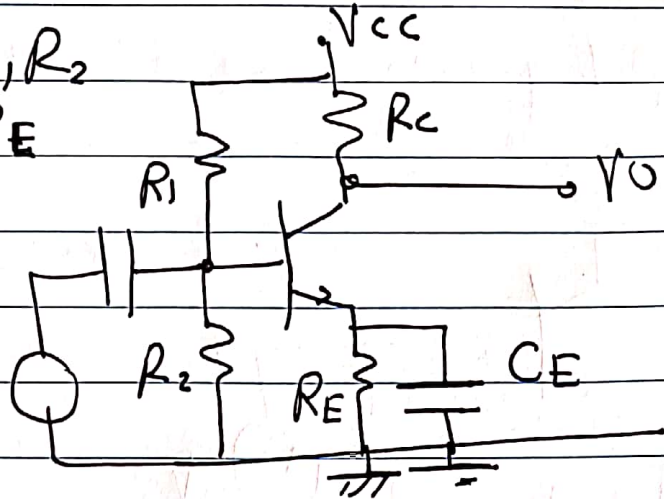

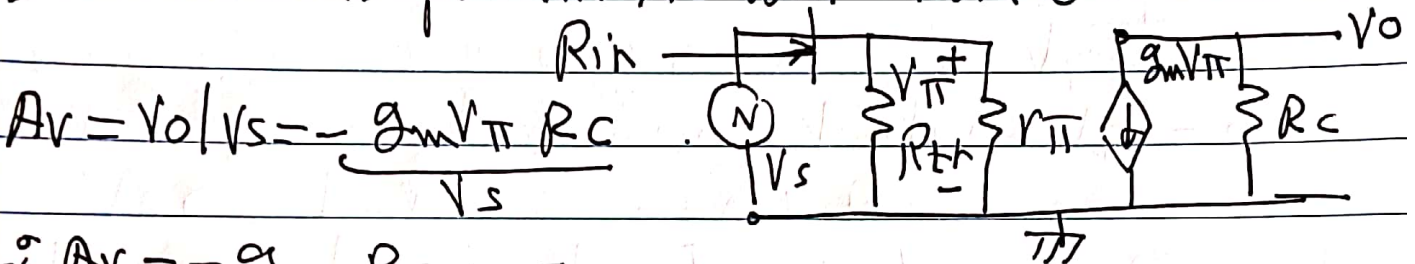1) When C_E is present, it will short out R_E




$$A_v = V_o / V_s = - \frac{g_m V_{\pi} R_c}{V_s}$$

$$\therefore A_v = -g_m R_c \checkmark$$

$$R_{in} = R_{th} \parallel r_{\pi} \checkmark \text{ (No -ve F.B)}$$

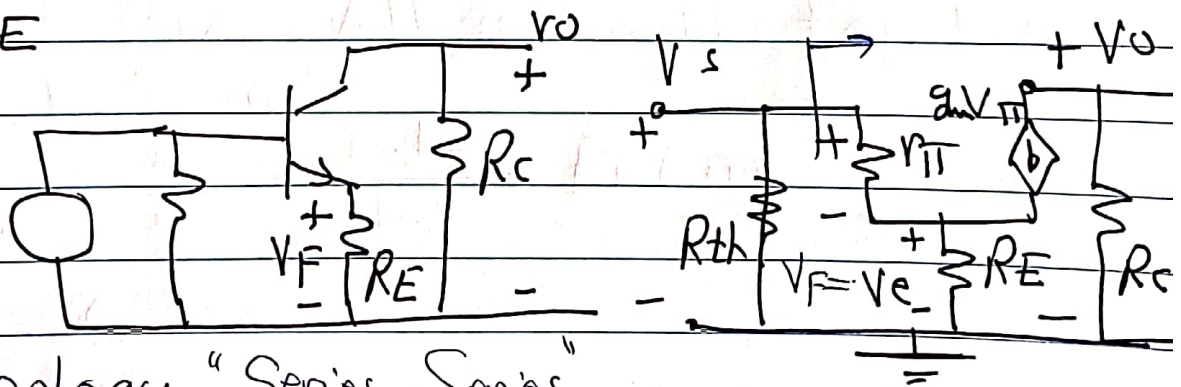2) When C_E is removed a -ve F.B will be ON R_E



With topology "Series-Series"

$$A_{VF} = V_o / V_s = -g_m V_{\pi} R_c / (V_{\pi} + (\beta+1) I_b R_E)$$

$$A_{VF} = (-g_m V_{\pi} R_c) / (V_{\pi} + (\beta+1) \frac{V_{\pi}}{r_{\pi}} R_E)$$

$$A_{VF} = \frac{-g_m R_c}{(1 + (\beta+1) \frac{R_E}{r_{\pi}})} \Rightarrow A_v \rightarrow \text{reduces}$$

$$R_{inF} = \left[r_{\pi} + (\beta+1) R_E \right] \parallel R_{th} \quad R_{in} \rightarrow \text{Increases}$$


So this F.B decrease A_v and Increase R_{in}

$$A_g = \frac{I_o}{V_s} = \frac{g_m V_{\pi}}{V_{\pi} + (\beta+1) I_b R_E} = \frac{g_m V_{\pi}}{V_{\pi} + (\beta+1) \frac{V_{\pi}}{r_{\pi}} R_E} = \frac{g_m}{1 + \frac{R_E}{r_{\pi}} (\beta+1)}$$

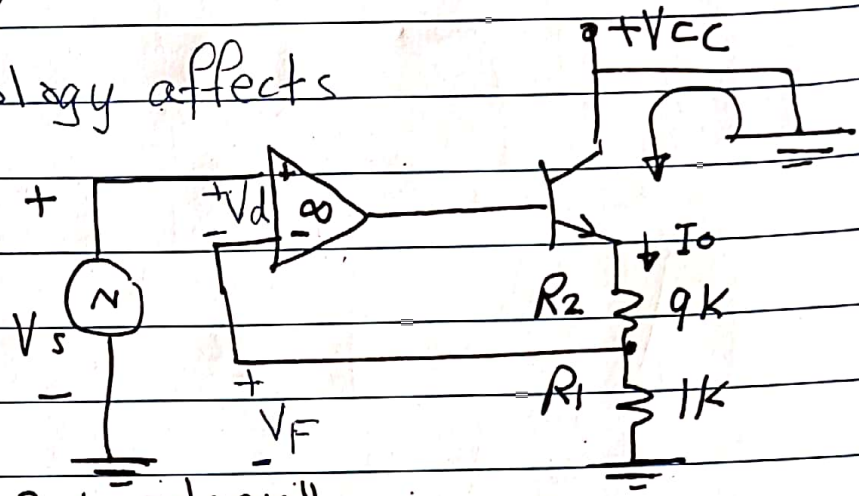Examples:

① For the system shown. Identify the topology and determine B??

How does this topology affects A_v, R_{in}, R_o



"Summary of -ve F.B topology".

In all topology: $A_f = \frac{A}{1+BA}$, $(B.W)_f = (1+BA)B.W$, $D_f = \frac{D}{1+BA}$

Topology	Amp Type	X_s	X_o	X_f	A	B	R_{in_f}	R_{o_f}
Voltage-Series "Shunt-Series"	Voltage Amp.	V_s	V_o	V_f	A_v	B_v	$R_{in}(1+BA)$	$\frac{R_o}{(1+BA)}$
Current-Shunt "Series-Shunt"	Current Amp.	I_s	I_o	I_f	A_i	B_i	$\frac{R_{in}}{1+BA}$	$R_o(1+BA)$
Voltage-Shunt "Shunt-Shunt"	Transconductance Amp	I_s	V_o	I_f	R_{Ω} <u>A_z</u>	B_g	$\frac{R_{in}}{1+BA}$	$\frac{R_o}{1+BA}$
Current-Series "Series-Series"	Transconductance Amp.	V_s	I_o	V_f	A_g	B_z	$R_{in}(1+BA)$	$R_o(1+BA)$

* In all Topology: $AB \rightarrow$ No unit (unitless)

Feedback sheet


17

Q₁ For the F.B amplifier shown the amplifier has:

$R_i = 1k, R_o = 5k, f_L = 500Hz$

$f_H = 50kHz, A = 50$ with:

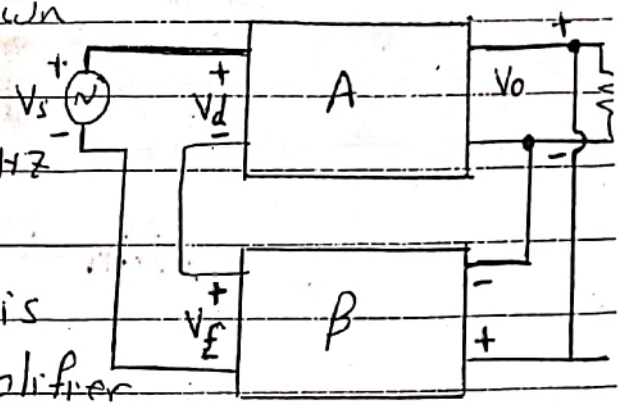No. F.B. If 8% -ve F.B is applied, recalculate the Amplifier parameters? sketch the freq. response with and without F.B?



Q₂ A current amplifier has $A_I = 40$ dB, $R_i = 2k\Omega$, $R_o = 1k\Omega$. If it is required to make $R_i = 200\Omega$


- (i) What type of -ve F.B is required, draw block diagram
- (ii) Recalculate A_I, R_o and find the required β ?
- (iii) Suggest a F.B network to realize this β ?

Q₃ For the cct. shown in Fig.

(i) What type and Topology of the F.B?

(ii) How does this F.B affect the input & output impedances.

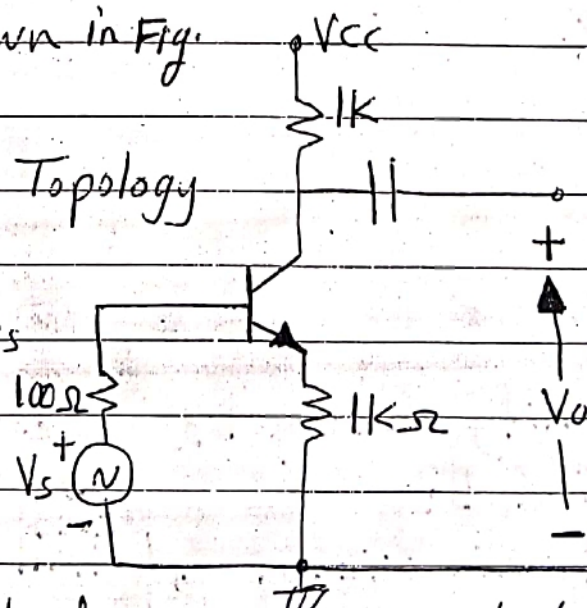(iii) Draw the block diagram representation for the above F.B.




P.T.O →

Q4

Given: $g_m = 4.5 \text{ mS}$

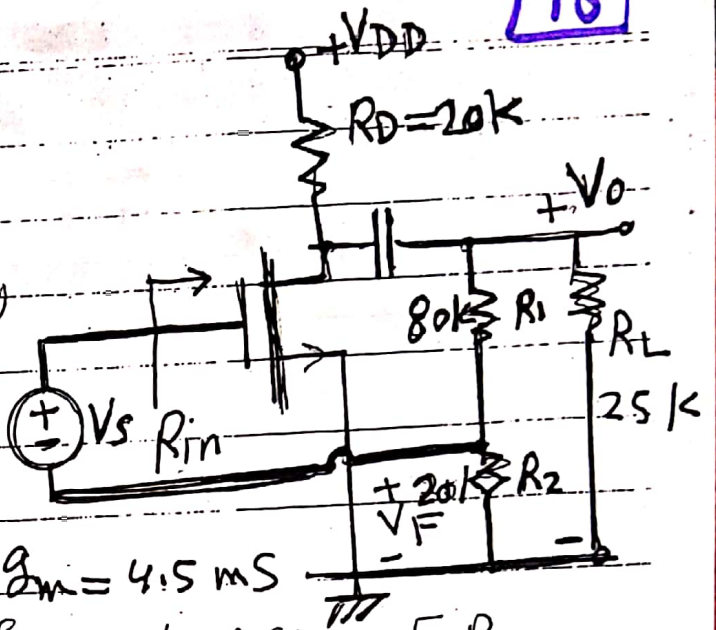- 1) Identify F.B Topology
- 2) Find A_v, R_o, β
 $A_{vF}, R_{oF}, R_{in}, R_{inF}$
- 3) If $f_L = 500 \text{ Hz}$
 $f_H = 500 \text{ kHz}$




Draw Freq. Response before and After F.B.

Q5: Consider the circuit shown in Fig.

- 1) Identify type and topology of this F.B.

- 2) Indicate X_s, X_p, X_d, X_o

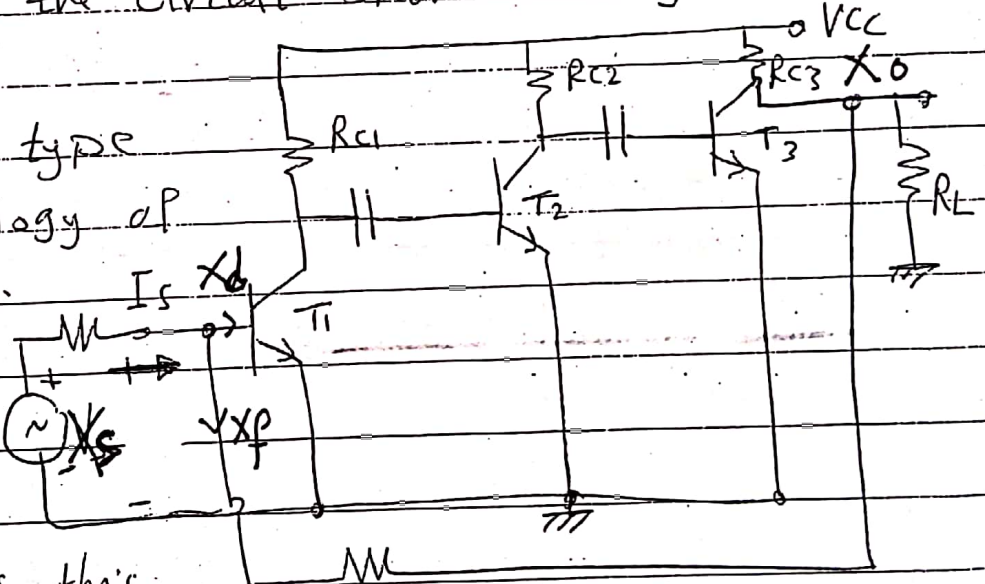


- 3) How does this F.B affect Z_i & Z_o .

- 4) Name this Amp, and indicate A type & units, β value & unit.

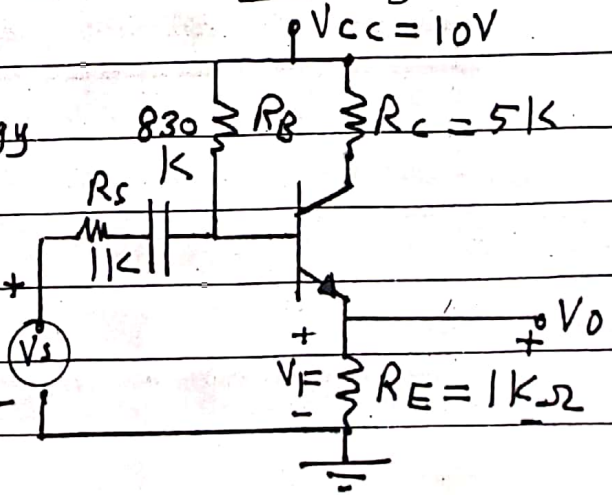
Q6: Identify the topology and find β ?

- Estimate R_{in} without F.B and with F.B?
- Sketch Block diagram.



Q₄: The F.B is through R₁ & R₂ where V_F is across R₂. Since they form a voltage divider
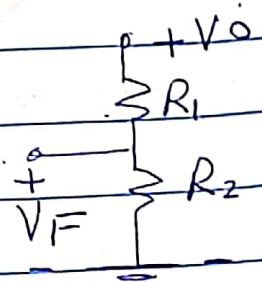
$$V_F = \frac{V_o \cdot R_2}{R_1 + R_2} \Rightarrow B = \frac{V_F}{V_o} = \frac{R_2}{R_1 + R_2} \equiv \underline{\underline{VDR}}$$




i.e. $V_F \propto V_o \Rightarrow$ If $V_o = 0, V_F = 0$, No F.B"

So it is voltage from o/p, V_F is mixed in series with V_s \Rightarrow So it is "Voltage-Series" and used with "Voltage-Amplifier"

① Without F.B:
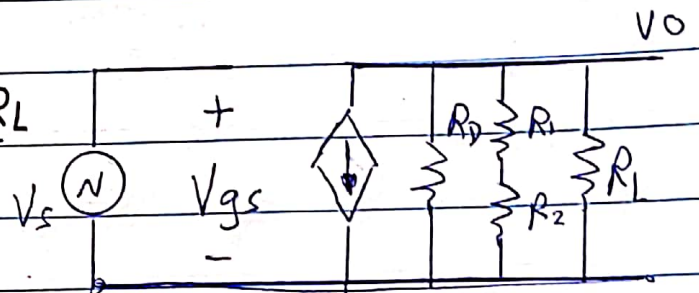
$$A_v = \frac{V_o}{V_s} = \frac{-g_m V_{gs} (R_D \parallel (R_1 + R_2) \parallel R_L)}{V_{gs}}$$



$$\infty |A_v| = g_m (R_D \parallel (R_1 + R_2) \parallel R_L)$$

$$= 4.5 (20 \parallel (100) \parallel 25) = 10 \text{K}\Omega \quad g_m = 4.5 \text{mS}$$

$$\infty |A_v| = 45$$

$$4.5 \text{mS} \quad R_D = 20 \text{K}, R_L = 25 \text{K}$$

$$R_{in} = \infty, R_o = R_D \parallel (R_1 + R_2)$$

$$R_1 = 80 \text{K}, R_2 = 20 \text{K}$$

$$= 16.666 \text{K}\Omega$$

$$f_L = 500 \text{Hz}, f_H = 500 \text{KHz}$$

with F.B: $B = \frac{V_F}{V_o} = \frac{R_2}{R_1 + R_2} = \frac{20}{100} = 0.2$


$$A_{vF} = \frac{A_v}{1 + B A_v} = \frac{45}{1 + 0.2 \times 45} = 4.5$$

$$R_{inF} = R_{in} (1 + B A_v) = \infty (10) = \infty$$

$$R_{oF} = R_o / (1 + B A) = 16.666 / 10 = 1.666 \text{K}\Omega$$

$$f_{LF} = f_L / (1 + B A) = 500 / 10 = 50 \text{Hz}$$
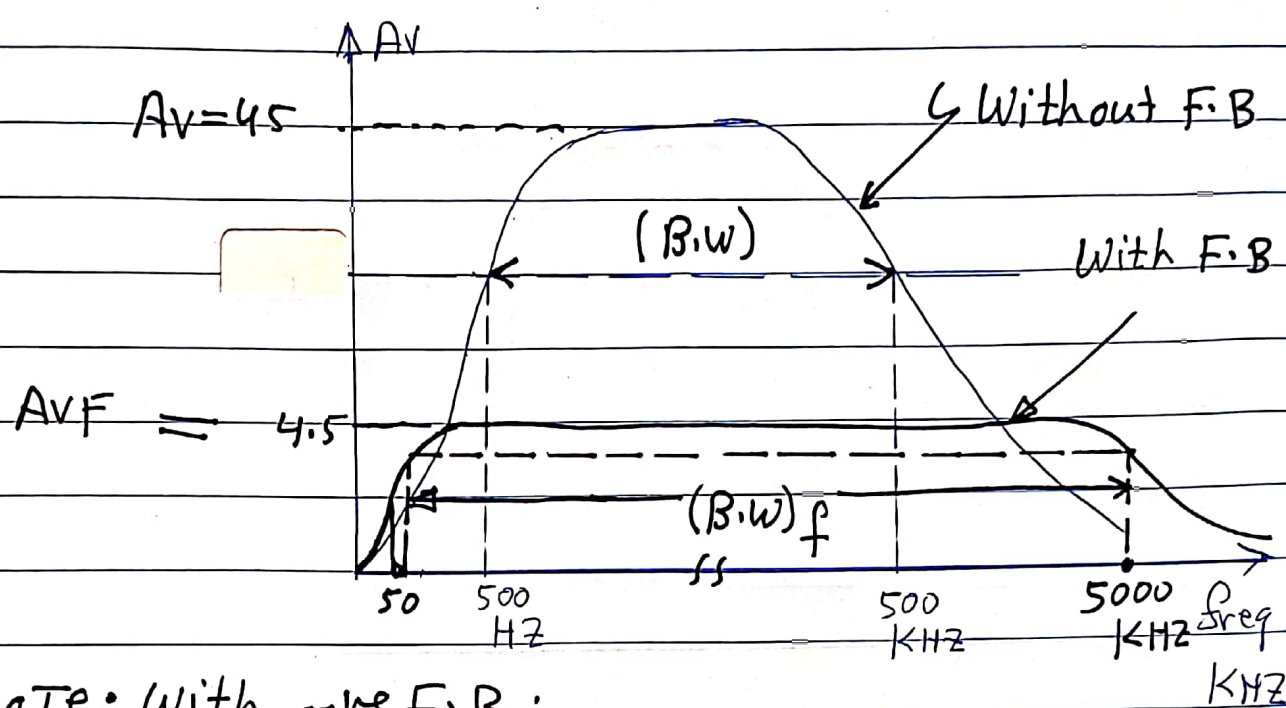
$$f_{HF} = f_H (1 + B A) = 500 \text{K} \times 10 = 5000 \text{KHz} = 5 \text{MHz}$$



Note: With -ve F.B :-

$A_v \rightarrow$ decreases

(B.W) \rightarrow extends (Increases).

* This is True Since Gain \times B.W \approx Constant.

Q5: The topology is "Voltage-Shunt"

We Sample from Node \Rightarrow Voltage

\Rightarrow Mix Current \Rightarrow Shunt.

$Z_{in f} = Z_{in} / (1 + BA)$, $Z_{o f} = Z_o / (1 + BA)$

Amp: \rightarrow Transresistance Amp.

$A = \frac{V_o}{I_s} = R(\Omega)$, $B = \frac{I_f}{V_o} \approx \frac{1}{R_f} (\Omega^{-1})$

$X_o \rightarrow V_o$

$X_f \rightarrow I_f$

$X_s \rightarrow I_s$

$X_d \rightarrow I_d$

$R_{in f}, R_{o f} \downarrow$

Q6: Topology \rightarrow Voltage-Series because $V_f \propto V_o$ and

If $V_o = 0$, $V_f = 0$. $B = \frac{V_f}{V_o}$ and Since $V_f = V_o$, $B = 1$

* Without F.B. $R_{in} = R_B \parallel r_{\pi}$ (No R_E), $R_E \neq 0$

* with F.B $R_{in f} = R_B \parallel (r_{\pi} + (\beta + 1)R_E)$

Since R_E is present and causes -ve F.B, Series \Rightarrow I/P

Oscillators "Signal Generators"

21

Oscillator: Feedback Amplifier with +ve F.B produces a periodical A.C output signal with a certain amplitude and a certain freq. without any A.C input signal.

* only D.C voltage is required to bias the Active device in a proper mode.

They can be classified into:

- 1) Sinusoidal Oscillators \rightarrow produce Sine waves
- 2) non-Sinusoidal Oscillators which include Triangulare-wave, Square-wave - Sawtooth wave.

Sinusoidal Oscillators

F.B Amplifiers contain:

* Amplifier: which contains an Active device

Such as: BJT, FET

or op-Amp.


* F.B ckt.: which must be freq. dependant ckt. Such as LC, RC, RL passive ckt.

* principle of oscillation: Consider the F.B Amp. with +ve F.B.

$$X_o = A(j\omega) \cdot X_d, \quad X_d = X_s + X_f \quad (+ve. F.B)$$

$$X_f = B(j\omega) X_o. \quad \text{So: } X_o = A(j\omega) [X_s + B(j\omega) X_o]$$
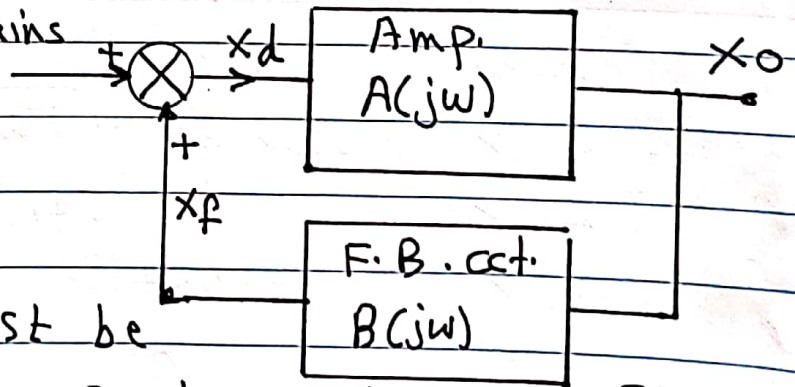
$$\therefore X_o = A(j\omega) X_s + A(j\omega) B(j\omega) X_o$$



$$X_o (1 - A(j\omega) B(j\omega)) = A(j\omega) X_s$$

$$\therefore \frac{X_o}{X_s} = A_f = \frac{A(j\omega)}{1 - A(j\omega) B(j\omega)}$$

Now: IF $A(j\omega) B(j\omega) = 1$, then

$$\frac{X_o}{X_s} = A_f = \infty, \text{ this means}$$

either $X_o = \infty$ which is impossible since X_o is a certain value

OR $X_s = 0$ which means No input !!!

i.e there is an o/p but No input. which means the system will start giving an o/p but No input i.e Generate an o/p signal

* This happens when $A(j\omega) B(j\omega) = 1$

Since Both are complex function. i.e real + imaginary $A(j\omega) = A \angle \phi$, $B(j\omega) = B \angle \theta$

So $A(j\omega) B(j\omega) = 1$ means

$$|AB| = 1, \angle A + \angle B = 0 \text{ or } 360$$

which are oscillation conditions or

" Barkhausen Condition "

1) $|BA| = 1$ (magnitude condition.

i.e when $|A| = 10$, then $|B| = \frac{1}{10}$ to satisfy

$$|BA| = 1. \text{ Where } A: \text{ Amp. gain}$$

B : Attenuation of F.B ckt.

2) phase condition: $\angle A + \angle B = 0, 360$

where $\angle A$ phase produced by Amp.

$$\angle B = \text{---} = \text{---} = \text{---} = \text{F.B ckt -}$$


The phase condition can be satisfied when:

- i) either both Amp. and B-Net. \rightarrow Inverting
 So A gives 180° and B gives 180° So the total phase $\angle A + \angle B = 180^\circ + 180^\circ = 360^\circ$
- ii) OR both of them are non-inverting i.e. giving zero phase: $\angle A + \angle B \Rightarrow 0^\circ + 0^\circ = 0^\circ$


Consider the following cases: For $|BA|$

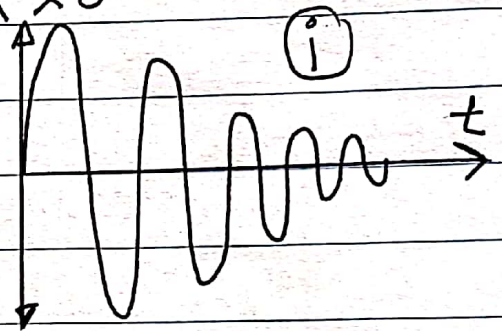- i) when $BA < 1$, the oscillation x_o


will start but will die out because $A < \frac{1}{B}$ i.e. the signal will lose energy more than gain, as shown in Fig. i



- ii) when $BA \gg 1$, the oscillation will start and continue increasing till the ckt. will be out of control because $|BA| \gg 1 \rightarrow$ means the signal will gain more than loss and continue increasing. See Fig. ii

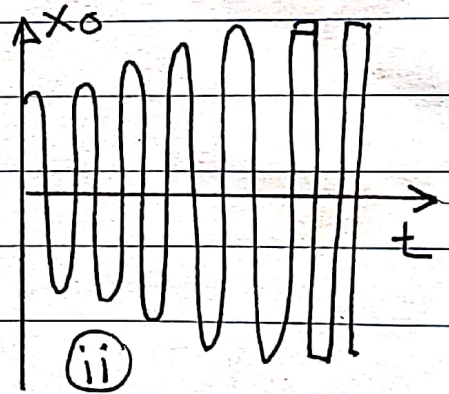

- iii) when $|BA| = 1$, this is the required condition, here the signal will be maintained oscillating between A and B gain energy from A and loss energy in B by the same amount, giving steady-state

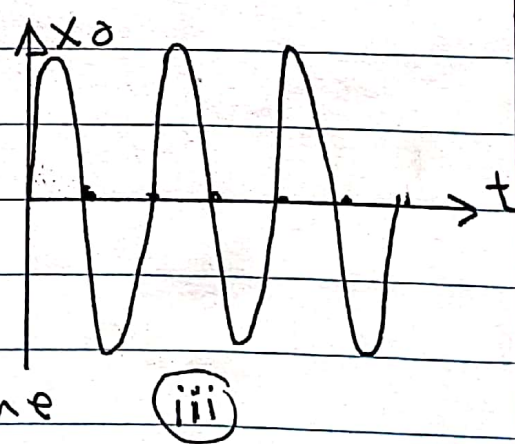

output sinusoidal signal with a certain frequency and a certain amplitude. See Fig. iii


RC-Oscillators

24

Oscillators in which F.B cct. contain R & C element and Amp. can be BJT Amp, FET Amp, Op-Amp.

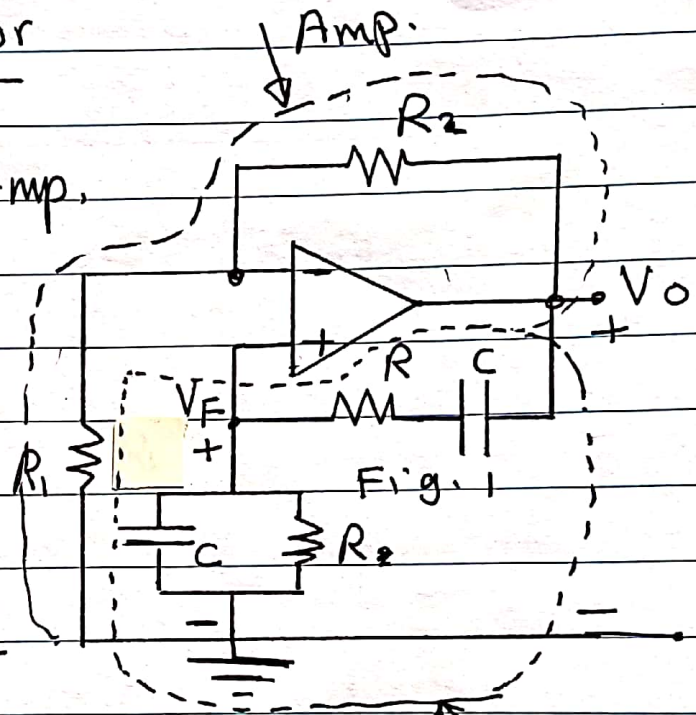1) WIEN-Bridge Oscillator

In this oscillator Amp is non-inverting Amp, which gives $\phi = 0^\circ$ at certain $\omega \rightarrow \omega_0$. F.B cct. must give $\phi = 0^\circ$ at the same value of ω also at $\omega = \omega_0$.



How to derive freq. of oscillations " $\omega_0 \rightarrow f_0$ "

* We have to extract F.B cct. and indicate V_o & V_F then find $B = \frac{V_F}{V_o}$.

Consider the cct. in Fig. 2 which is the F.B cct.

Using VDR: $\frac{V_F}{V_o} = B = \frac{Z_p}{Z_p + Z_s}$

Where

$$Z_p = R \parallel \frac{1}{j\omega C} = \frac{R}{R + \frac{1}{j\omega C}}$$

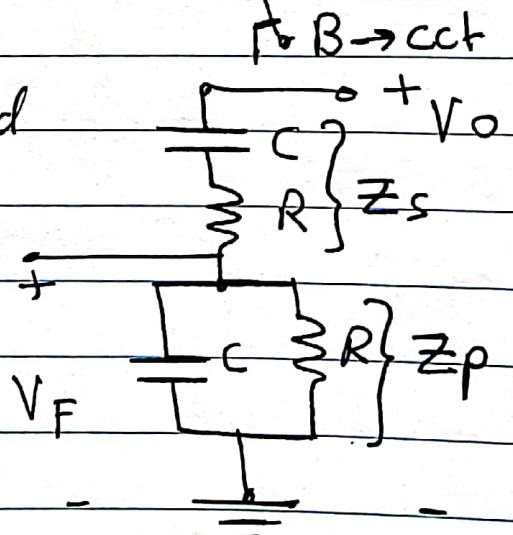


Fig. 2

$$Z_p = \frac{R}{1 + j\omega CR}, \quad Z_s = R + \frac{1}{j\omega C}$$

$$\therefore B = \frac{R/(1 + j\omega CR)}{R/(1 + j\omega CR) + R + \frac{1}{j\omega C}} \quad (\text{multiply by } 1 + j\omega CR)$$

$$B = \frac{R}{R + (1 + j\omega CR)(R + \frac{1}{j\omega C})}$$

$$B = \frac{R}{R + R + \frac{1}{j\omega C} + j\omega CR^2 + R} = \frac{R}{3R + j(\omega CR^2 - \frac{1}{\omega C})}$$

consider eqn. (x) For B

The F.B ckt. will give zero phase when j-term i.e equal zero (i.e $j(\omega CR^2 - \frac{1}{\omega C}) = 0$)
i.e when $\omega = \frac{1}{RC}$ which is called the

freq. at which phase condition is satisfied.

$$\angle A + \angle B = 0^\circ + 0^\circ = 0^\circ$$

i.e $f = \frac{1}{2\pi RC}$ this is called frequency of oscillation

* Now what about magnitude condition??

* At this freq. i.e when j-term = 0

$$B = \frac{R}{3R} = \frac{1}{3} \quad (\text{i.e } |B| = \frac{1}{3} \text{ and } \angle B = 0^\circ)$$

$$\text{To satisfy } |BA| = 1 \quad \therefore |A|_{\min} = \frac{1}{|B|} = 3$$

We know that for

non-inverting Amp:


$$A = 1 + \frac{R_2}{R_1}$$

$$\therefore \left(1 + \frac{R_2}{R_1}\right)_{\min} = 3$$

$$\therefore \left(\frac{R_2}{R_1}\right)_{\min} = 2 \Rightarrow \boxed{R_2 = 2R_1}$$

So to satisfy $|BA| = 1$, we must choose
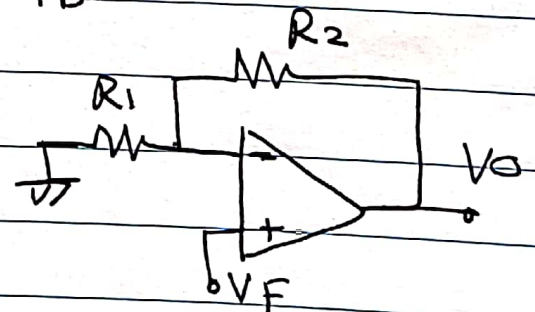
$$\left(\frac{R_2}{R_1}\right)_{\min} = 2$$



Example: Design a WIEN-Bridge Oscillator to oscillate at $f_0 = 50\text{ KHz}$. The available capacitors are: $0.01\mu\text{F}$

Solution:


$$f_0 = \frac{1}{2\pi RC} \Rightarrow R = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi \times 50 \times 10^3 \times 1 \times 10^{-8}}$$

$$\therefore R = \frac{10^3}{\pi} = 318.3\Omega$$

$$\left(\frac{R_2}{R_1}\right)_{\text{min}} = 2, R_2 = 2R_1$$

Choose $R_1 = 1\text{K}\Omega$

$$\therefore R_2 = 2\text{K}\Omega$$

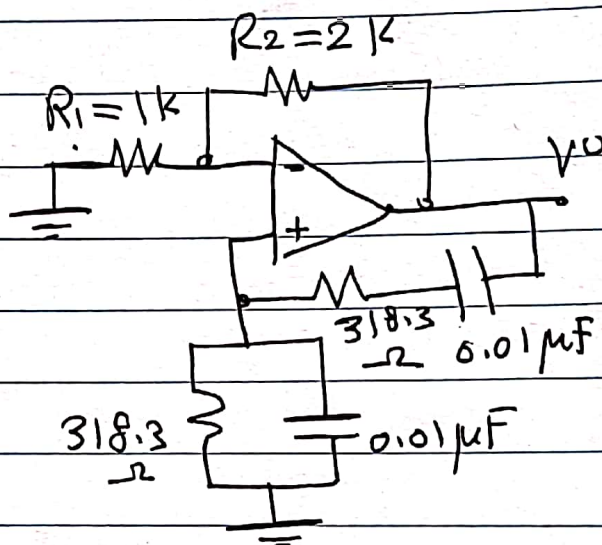

* If we want to replace the Non-inverting Amp. by BJT Amp.

* We must use C.B Amplifier with $A_v = 3$ [Since C.B gives 0° and A_v]

* If we want to use FET Amp.


We must use C.G Amplifier with $A_v = 3$ Since it gives 0° and $A_v > 1$

* Can we use C.C or C.D and why?

* Can this ckt. oscillate?

* If yes calculate f_0


* If No explain why?

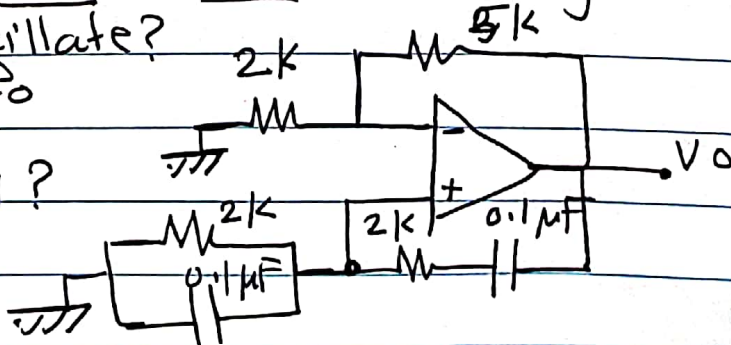

phase-shift oscillator

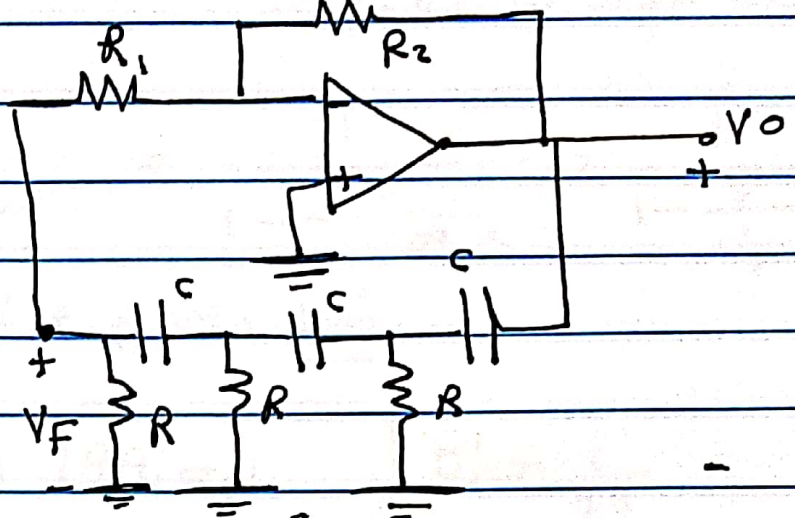(27)

In this oscillator, the Amp. is inverting Amp. and gives 180° and the F.B ckt.




is three-identical RC Section. at certain freq. (ω) each Section gives 60° i.e the total

phase-shift of F.B ckt is 180° .

So the total phase-shift around the loop will be 360° .

Frequency of oscillation.

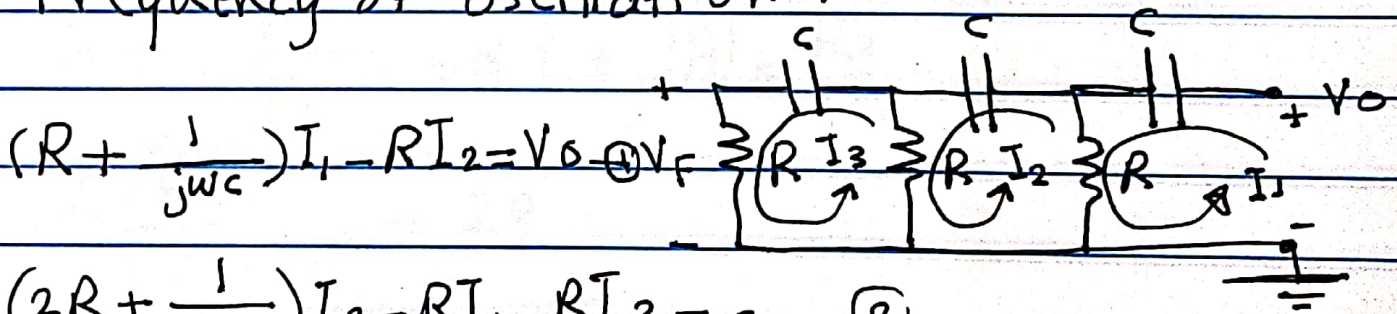

$$(R + \frac{1}{j\omega C})I_1 - RI_2 = V_0 - V_F$$

$$(2R + \frac{1}{j\omega C})I_2 - RI_1 - RI_3 = 0 \quad \text{--- (2)}$$

$$(2R + \frac{1}{j\omega C})I_3 - RI_2 = 0 \quad \text{--- (3)}$$

$$V_F = I_3 R \quad \text{--- (4)}$$

Solve the above eqns to find $B = \frac{V_F}{V_0}$

$$B = \frac{j\omega^3 C^3 R^3}{(6R^2 C^2 \omega^2 - 1) + j(\omega^3 C^3 R^3 - 5\omega RC)} = \frac{V_F}{V_0}$$

When Real term = 0, $6R^2 C^2 \omega^2 = 1$

$$\omega^2 = \frac{1}{6R^2C^2}$$

$$\therefore \omega = \frac{1}{\sqrt{6}RC} = \omega_0 \Rightarrow f_0 = \frac{1}{2\pi\sqrt{6}RC}$$

at this freq. freq. of oscillation.

$$B = \frac{\omega^3 R^3 C^3}{\omega^3 R^3 C^3 - 5\omega RC} = \frac{1}{1 - \frac{5}{\omega^2 R^2 C^2}} = \frac{1}{1 - \frac{5}{\frac{1}{6}}}$$

$$\therefore B = -\frac{1}{29} \text{ i.e gives } 180^\circ$$

Now to satisfy $|BA| = 1$
 $|A_{min}| = 29$

$$|B| = \frac{1}{29}$$

$$\angle B = 180^\circ$$

For Inverting Amp.


$$A = -\frac{R_2}{R_1} \rightarrow \text{i.e } |A| = \frac{R_2}{R_1}$$

$$\therefore \left(\frac{R_2}{R_1}\right)_{min} = 29$$

$$\text{i.e } R_2 = 29 R_1$$

*The last R in RC section is in parallel with R_1 due to virtual ground concept in op Amp.

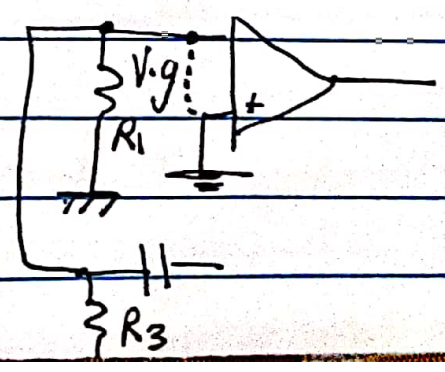So this will affect the symmetry of RC section, so we have to make $(R \parallel R_1) = R$.




OR We use only R (ONE Resistance) to be as last element in RC-section and work as R_1 and therefore minimize No of Resistance

EXA: Design a phase-shift Oscillator to produce 20kHz A.C signal.

"Draw the required Comp. Values and draw $v_o(t)$?"

* The cct. is shown in Fig.

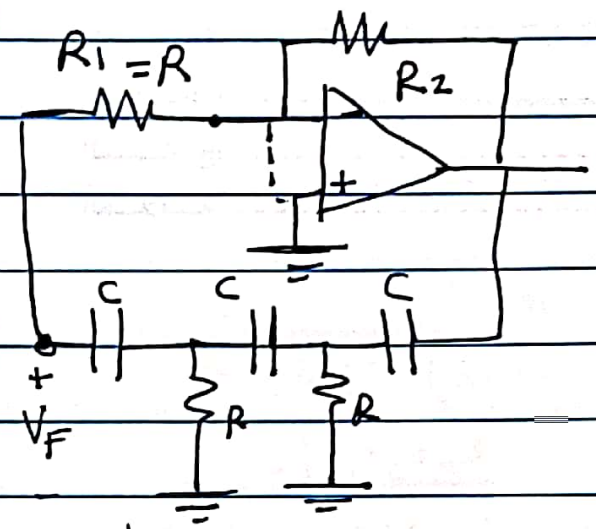

* For this oscillator $f_0 = \frac{1}{2\pi\sqrt{6}RC}$ and $|A|_{min} = 29$


let $C = 0.01\mu F \Rightarrow R = \frac{1}{2\pi\sqrt{6}f_0 C} =$

$$R = \frac{1}{2\pi\sqrt{6} \times 10^{-8} \times 2 \times 10^4} = 0.325 k\Omega$$

$$R = R_1 = 0.325 k\Omega$$

$$|A| = 29 = \frac{R_2}{R_1} \Rightarrow R_2 = 29R_1 = 29 \times 0.325 = 9.425 k\Omega$$

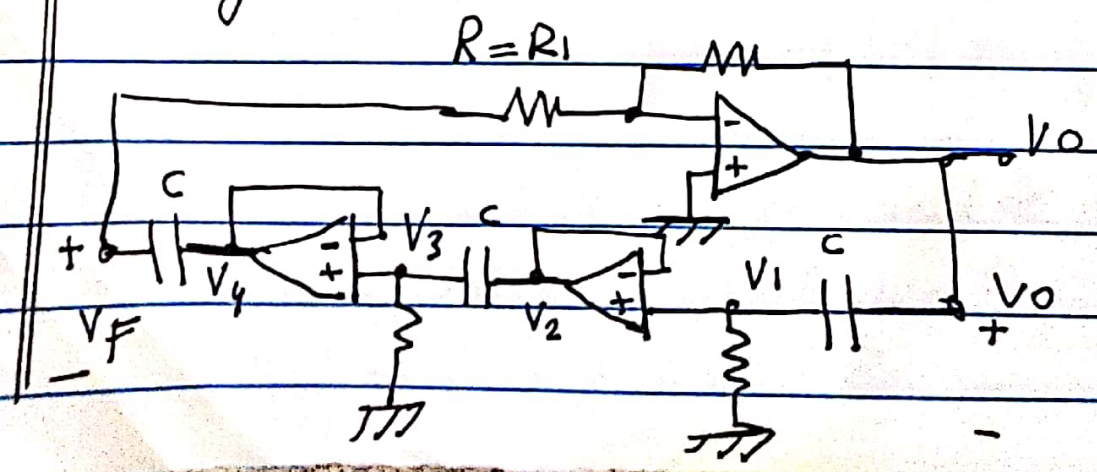* In the previous cct. each RC section loaded the other, to cancel loading effect, a buffer "Voltage follower" can be used as shown.



For this cct.

$$\frac{V_F}{V_0} = \beta = \frac{V_F}{V_4} \times \frac{V_4}{V_3} \times \frac{V_3}{V_2} \times \frac{V_2}{V_1} \times \frac{V_1}{V_0}$$

$$\text{but } \frac{V_2}{V_1} = \frac{V_4}{V_3} = 1$$

$$\frac{V_1}{V_0} = \frac{V_3}{V_2} \times \frac{V_F}{V_4} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$\text{So } \frac{V_F}{V_0} = \left(\frac{R}{R + \frac{1}{j\omega C}} \right) (1) \left(\frac{R}{R + \frac{1}{j\omega C}} \right) (1) \left(\frac{R}{R + \frac{1}{j\omega C}} \right) = \left(\frac{R}{R + \frac{1}{j\omega C}} \right)^3$$

$$\therefore \frac{V_F}{V_0} = \beta = \frac{R^3}{\left(R + \frac{1}{j\omega C} \right) \left(R + \frac{1}{j\omega C} \right)^2} = \frac{-j\omega^3 C^3 R^3}{(1 + j\omega CR)(1 + j\omega CR)^2}$$

$$\beta = \frac{-j\omega^3 R^3 C^3}{(1 - 3\omega^2 C^2 R^2) + j\omega CR(3 - \omega^2 C^2 R^2)}$$

This will give zero phase-shift when real term = 0

i.e. when $1 - 3\omega^2 C^2 R^2 = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{3} RC}$

$\therefore f_0 = \frac{1}{2\pi \sqrt{3} RC}$ Freq. of oscillation

At this freq. $\beta = \frac{-\omega^2 C^2 R^2}{3 - \omega^2 C^2 R^2}$ Since $\omega_0^2 = \frac{1}{3R^2 C^2}$

$$\therefore \beta = \frac{-\frac{1}{3R^2 C^2} C^2 R^2}{3 - \frac{1}{3R^2 C^2} C^2 R^2} = \frac{-\frac{1}{3}}{3 - \frac{1}{3}}$$

$$\beta = \frac{-1}{9-1} = -\frac{1}{8} \Rightarrow |\beta| = \frac{1}{8}$$

i.e. F.B cct will give 180° and $\beta = \frac{1}{8}$

\therefore To satisfy $|\beta A| = 1 \Rightarrow |A|_{\min} = 8$

i.e. $\left| \frac{R_2}{R_1} \right| = 8 \Rightarrow R_2 = 8R_1$


EXA: Design a phase-shift Oscillator to give 30KHZ signal. Draw the cct. diagram and calculate the required component value.

"Without loading effect" "Three op-Amp. cct"

* For this cct. $f_0 = \frac{1}{2\pi\sqrt{3}RC}$, $|A|_{min} = 8$

let $C = 0.01\mu F$

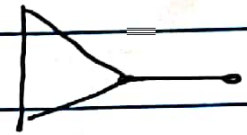$R = \frac{1}{2\pi\sqrt{3} \times 30 \times 10^3 \times 10^{-8}} = \frac{10^4}{6\pi\sqrt{3}} = 0.3k$



$\left|\frac{R_2}{R_1}\right| = 8 \Rightarrow R_2 = 8R_1 = 2.4u8k\Omega$

* We can replace the Inverting Amp. by:

- ① C.E cct in BJT Amp.
- ② C.S in C.S. Amplifier.

EXA: Calculate f_0, R_g, R_D

When the MOSFET has $g_m = 5mA/V$


$f_0 \approx 65KHZ$

$R_g = R = 1k\Omega$

$|A_v| = 29$

$|g_m R_D| = 29$

$R_D = \frac{29}{5} = 5.8k\Omega$

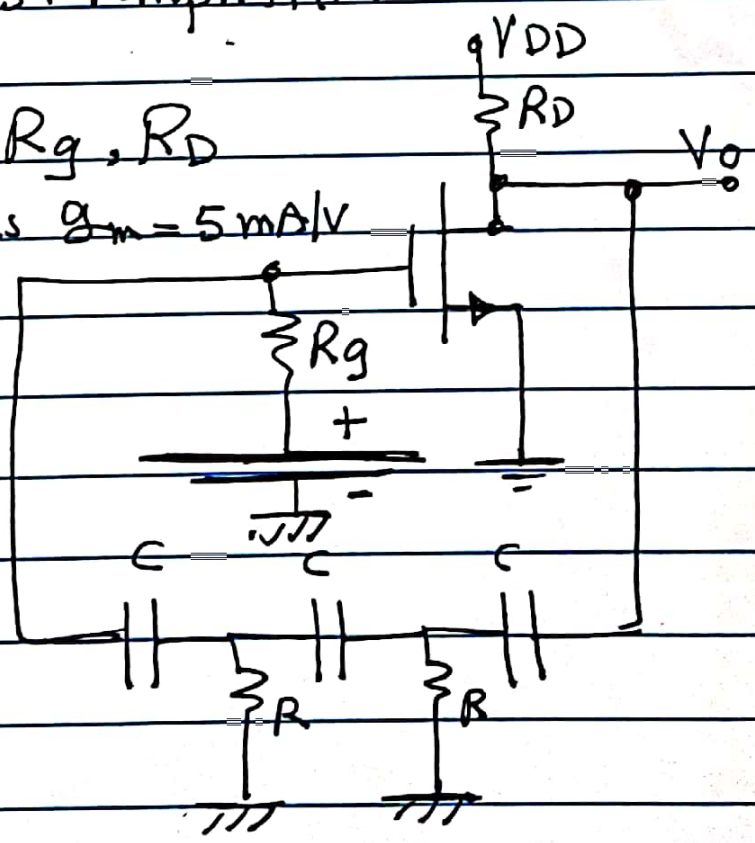

* $f_0 = \frac{1}{2\pi\sqrt{6}RC}$

$C = 1nF, R = 1k\Omega$

" " " " " "


LC-Oscillators OR Tuned-Cct. Oscillators

These oscillators have LC or RL ccts. as F.B ccts. which produce the required phase-shift at resonance and an amp., which can be BJT, FET or Op-Amp amplifier. that give the required gain and phase.

* For LC-Oscillators, there are two main types

1) Hartley Oscillator: This contains two inductors and one Capacitor to form the F.B cct. and Amp. to give the required gain: The cct. is shown in Fig.

* The Amp. is inverting which gives $\phi = 180^\circ$ and gain $|A| = \frac{R_2}{R_1}$

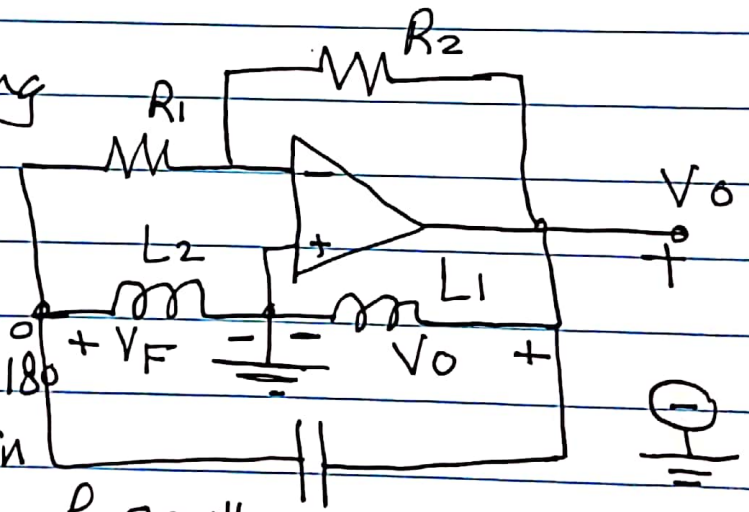

* The F.B cct. gives $\phi = 180^\circ$ at resonance. and certain attenuation $|B|$. The freq. of Oscilln: C

Can be derived as show: $\therefore f_0 = \frac{1}{2\pi\sqrt{C(L_1+L_2)}}$

At resonance the j-term = 0

$$j(\omega L_1 + \omega L_2) + \frac{1}{j\omega C} = 0 \Rightarrow j(\omega L_1 + \omega L_2) = \frac{1}{j\omega C}$$

$$\therefore \omega(L_1 + L_2) = \frac{1}{\omega C} \Rightarrow \omega^2(L_1 + L_2)C = 1$$

$$\therefore \omega_0 = \frac{1}{\sqrt{(L_1 + L_2)C}} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{C(L_1 + L_2)}}$$

$$B = \frac{VF}{V_0} = \frac{j\omega L_2}{j\omega L_1} = \frac{L_2}{L_1} \quad (\text{VDR})$$

To satisfy $|B| = 1 \Rightarrow A = \frac{1}{B} = \frac{L_1}{L_2}$

But $|A| = \frac{R_2}{R_1} \Rightarrow \frac{L_1}{L_2} = \frac{R_2}{R_1}$

EXA: Design a Hartley oscillator to have $f_0 = 100 \text{ kHz}$, the minimum gain of the Amp. NOT less than 9? the available Cap. is 1 nF ?

$$f_0 = \frac{1}{2\pi \sqrt{(L_1 + L_2)C}} \Rightarrow (L_1 + L_2) = \frac{1}{4\pi^2 f_0^2 C}$$

$$(L_1 + L_2) = \frac{1}{4(3.14)^2 \times 10^6 \times 10^{-9}} = \frac{1}{40 \times 10^9 \times 10^0} = \frac{1}{400} \text{ H} = 2.5 \text{ mH}$$

but $\frac{L_1}{L_2} = 9 \text{ (gain)} \Rightarrow L_1 = 9L_2$

$$9L_2 + L_2 = 2.5 \Rightarrow L_2 = \frac{2.5}{10} = 0.25 \text{ mH}$$


$$L_1 = 2.25 \text{ mH}$$

R_1 & R_2 ? Since $A = \frac{L_1}{L_2} = 9 = \frac{R_2}{R_1}$

$$R_2 = 9R_1$$

let $R_1 = 1 \text{ k}\Omega$

$$R_2 = 9 \text{ k}\Omega$$

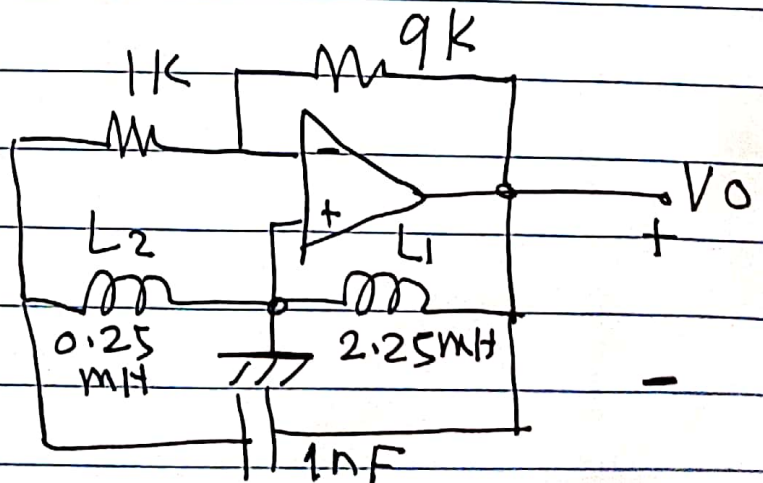


2) Colpitts Oscillator: This contains two caps. and one inductor to form the F.B ckt. as shown in Fig. The Amp. is inverting which gives 180° and the F.B ckt. will give 180° at Resonance.

Consider the LC-ckt

which has

$$Z = j\omega L + \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}$$

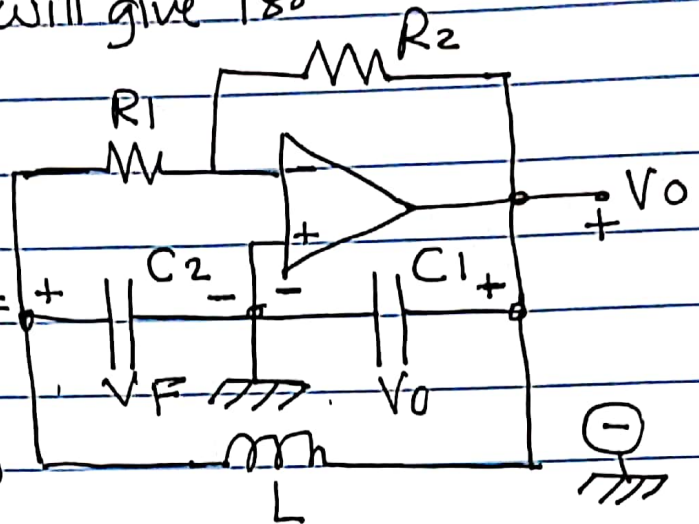At Resonance j -term = 0
i.e. $j(\omega L - \frac{1}{\omega C_1} - \frac{1}{\omega C_2}) = 0$



$$\omega L = \frac{1}{\omega C_1} + \frac{1}{\omega C_2}$$

$$\omega^2 = \frac{1}{L} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \Rightarrow \omega_0^2 = \frac{1}{L C_{eq}}$$

$$\text{where } C_{eq} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

$$f_0 = \frac{1}{2\pi \sqrt{L \cdot C_{eq}}} \Rightarrow f_0 = \frac{1}{2\pi \sqrt{L C_{eq}}}$$

$$B = \frac{V_F}{V_0} = \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1}} = \frac{C_1}{C_2}$$

$$\text{To satisfy } |BA| = 1 \Rightarrow |A| = \frac{C_2}{C_1}$$

$$\text{but For Inverting Amp. } |A| = \frac{R_2}{R_1}$$

$$\therefore \text{ we must choose } \left(\frac{R_2}{R_1} \right)_{\min} = \frac{C_2}{C_1}$$

EXA 2: Design Colpitts Oscillator to give sinusoidal signal at 80KHZ. The gain must NOT exceed 4? The available inductor is 1 μH? draw cct. diagram and o/p signal?

$$f_0 = \frac{1}{2\pi \sqrt{L C_{eq}}}$$

$$C_{eq} = \frac{1}{4\pi^2 L f_0^2} = \frac{1}{40 \times 64 \times 10^8 \times 1 \times 10^{-6}} = 3.9 \mu F$$

but $A = 4 = \frac{C_2}{C_1} \Rightarrow C_2 = 4C_1$

$$3.9 = \frac{C_1 \cdot C_2}{C_1 + C_2} = \frac{4C_1^2}{5C_1} = 0.8C_1$$



$$\therefore C_1 = \frac{3.9}{0.8} = 4.875 \mu F$$

$$C_2 = 19.5 \mu F$$

R₂ & R₁?

Since $|A| = \frac{R_2}{R_1} = 4 \therefore R_2 = 4R_1$

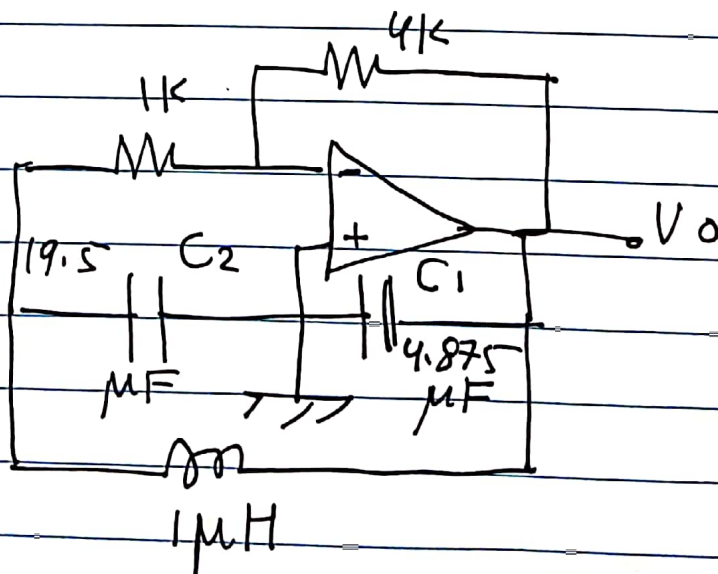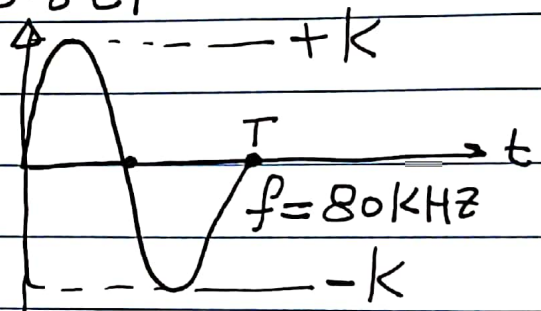let $R_1 = 1k\Omega \Rightarrow R_2 = 4 \times 1 = 4k\Omega$



"Frequency Stability"

36

Freq. Stability = $\frac{\Delta f}{f_0}$ where Δf : change in Freq. due to temperature and ageing effect on device and components values.

f_0 : designed freq.

* In RC and LC oscillator, the components (R, C, L) values are changed according to temp. and ageing and since freq. of oscillation depends on these values (i.e. in RC-oscillator) $\rightarrow f_0 = \frac{1}{2\pi RC}$ i.e. $f_0 \propto \frac{1}{RC}$ and in LC $f_0 \propto \frac{1}{\sqrt{LC}}$ or $f_0 \propto \frac{1}{\sqrt{LC}}$ as Temp. or ageing affect the \sqrt{LC} values of R, C, L the freq. of oscillation will be changed.

* For example, If we design an RC oscillator today with $f_0 = 50\text{KHz}$, after one year we may find $f_0 = 45\text{KHz}$. (due to change in R, C values)

$$\text{So } f.s = \frac{\Delta f}{f_0} = \frac{50 - 45}{50} = \frac{5}{50} = 10\%$$

* But in some applications (especially medical applic) we require an oscillator with stable f_0 ,

so we have to use Crystal Oscillator.


which has a very good or Superior freq. Stability compared to RC, LC or RL oscillator.

This will be discussed in the following section.

Crystal Oscillator

37

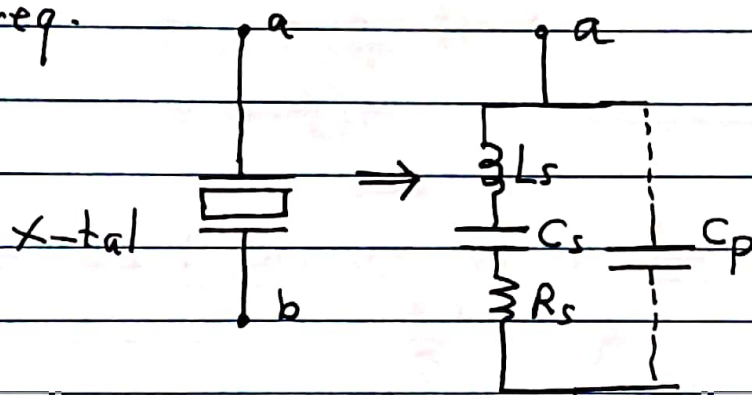This oscillator is characterized by superior freq. stability compared to RC and LC oscillator. Also it has high freq. of oscillation. It is using quartz crystal which is a piezoelectric material. These materials when subjected to an electric field, it will behave as a series-resonance ckt. and oscillate at the resonant freq.



L_s, C_s, R_s are parameters of series-resonance ckt. and depend on dimension of quartz-crystal and polarization.

C_p : Crystal holder cap. (Stray Cap. between electrode).

* This will oscillate at series-resonance freq.

$$f_s = \frac{1}{2\pi\sqrt{L_s \cdot C_s}} \quad (\text{series-mode})$$

* With quality factor $Q = \frac{\omega_s \cdot L_s}{R_s}$

* When C_p is considered it will work



in parallel mode $f_p = \frac{1}{2\pi\sqrt{L_s \cdot C_{eq}}}$

$$C_{eq} = \frac{C_s \cdot C_p}{C_s + C_p}$$


Since the impedance $Z = \sqrt{R_s^2 + j(\omega L - \frac{1}{\omega C})}$ of LRS ckt.

So x-tal can work as inductive or Capacitor

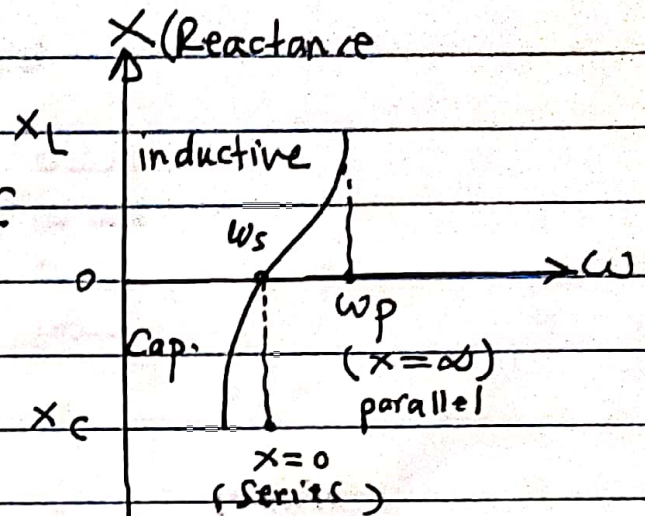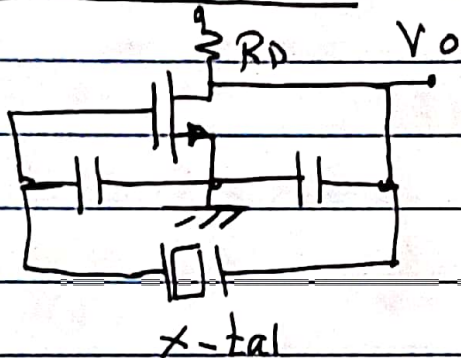* It can replace the inductor in Colpitts oscillator



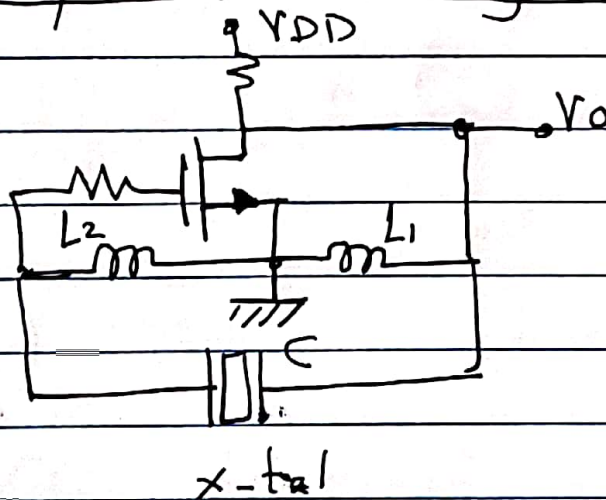or R: as Capacitor in Hartley Oscillator.



In these oscillators the freq. of oscillation depends on Crystal dimension. (C_s, L_s)

* L_s, C_s do not affected by Temp. and aging
So f_0 is not affected by Temp. and aging and
there for they are very stable oscillators.

EXA: a. X-tal Quartz has the following parameters

$L_s = 2\mu H$, $C_s = 0.01 pF$ and $R_s = 1000\Omega$

1) Calculate f_s and Q ?

2) If the crystal has $C_p = 1 pF$. Calculate f_p ?

Solution:

$$1) f_0 = \frac{1}{2\pi\sqrt{L_s \cdot C_s}} = \frac{1}{2\pi\sqrt{2 \times 10^{-6} \times 0.01 \times 10^{-12}}} = \frac{1}{2\pi \times 2 \times 10^{-9}} = \frac{10^7}{4\pi}$$

$\therefore f_0 = 795.774 \text{ KHz}$

$$Q = \frac{\omega_s \cdot L}{R_s} = \frac{2\pi \times 795.774 \times 10^3}{1000} = 5000$$

2) When C_p is considered, then $f_p = \frac{1}{2\pi\sqrt{L C_{eq}}}$

$$C_{eq} = \frac{C_s \cdot C_p}{C_s + C_p} = \frac{0.01 \times 1}{1 + 0.01} = 9.9 \times 10^{-15} \text{ F}$$

$$f_p = \frac{1}{2\pi\sqrt{4 \times 9.9 \times 10^{-15}}} = \frac{1}{2\pi\sqrt{3.96}} = 799.783 \text{ KHz}$$


i.e $f_p > f_s$

* Since C_s, L_s, R_s depends on Crystal dimension.

So: ~~For~~ each Crystal-oscillator, has a Certain-Fixed freq. i.e "It is a Fixed-freq. device" and this is an disadvantages

Advantages: Very high freq. stability & high freq. of oscillation "KHz \rightarrow MHz" range

* Disadvantages: Fixed-Freq. device

Fragile () "handle with care?"

"NON-Sinusoidal Oscillator" → "Relaxation Oscillators"

These oscillators produces, Square-Wave, Triangular-Wave Sawtooth wave and it is based on charging and discharging of capacitor, so the frequency of oscillation depends on charging and discharging time-Constant of a Capacitor in the ckt.

- 1) Multivibrators: These produces Square-Wave o/p and they include:
 - i) Astable MTV: "has No Stable-State" "Free-Running"
 - ii) Monostable MTV: "has one Stable-State" "ONE shot"
 - iii) Bistable MTV: "has two stable States"

Astable Multivibrator "AMTV"

This can be realized using:

- i) op-Amp. as a Comparator
- ii) 555 Timer.

This is based on using the Op-Amp. as a Comparator giving $V_o = \pm V_{cc}$

- When $V^+ > V^- \Rightarrow V_o = +V_{cc}$
- When $V^+ < V^- \Rightarrow V_o = -V_{cc}$



Comparator:

$$V_o = A_o(V^+ - V^-)$$

For ideal Op-Amp.

$$A_o = \infty, \text{ So:}$$

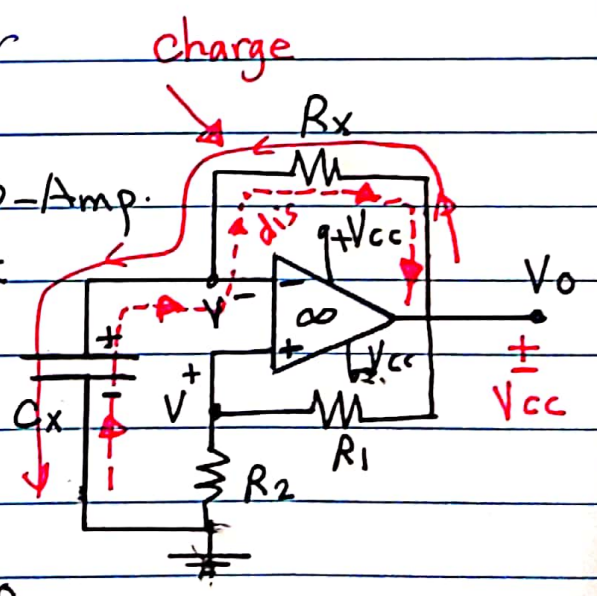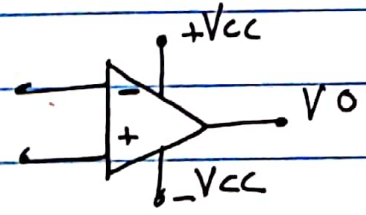When $V^+ > V^- \Rightarrow V_o = +V_{cc}$, when $V^- > V^+ \Rightarrow V_o = -V_{cc}$.



Operation: When we switch-on D.C power supply
The o/p will be either $+V_{CC}$ or $-V_{CC}$.

let us assume $V_0 = +V_{CC}$, then $V_F = V^+ = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$

For $R_1 = R_2$, $V^+ = \frac{1}{2} V_{CC}$

The Cap. C_x will charge with time constant $\tau_x = R \times C_x$

When C_x try to exceed $\frac{V_{CC}}{2}$, the Comparator will change the state and give $V_0 = -V_{CC}$

Now $V^- = \frac{-V_{CC} \cdot R_2}{R_1 + R_2}$ and when $R_1 = R_2$, $V^- = -\frac{V_{CC}}{2}$.

The Capacitor C_x will start discharging aiming $-V_{CC}$ through R_x .

but when C_x try to exceed $-\frac{V_{CC}}{2}$, the Comparator will change the state and give $V_0 = +V_{CC}$, i.e back to the first state - and the cycle will be repeated

Frequency of oscillation

$$T = t_{ch} + t_{dis}$$

Starting from expression

of Cap. Voltage during

charging or discharging

$$V_c(t) = V_{Final} + (V_{initial} - V_{final}) e^{-\frac{t}{\tau}}$$


$V_c(t)$: Cap. Voltage at any time

V_f : final Voltage which Cap. aim to reach

$$"V_f = \pm V_{CC}"$$

$V_{initial}$: initial Cap. Voltage $\mp \frac{V_{CC}}{2}$ (which C_x start charge or discharge -)

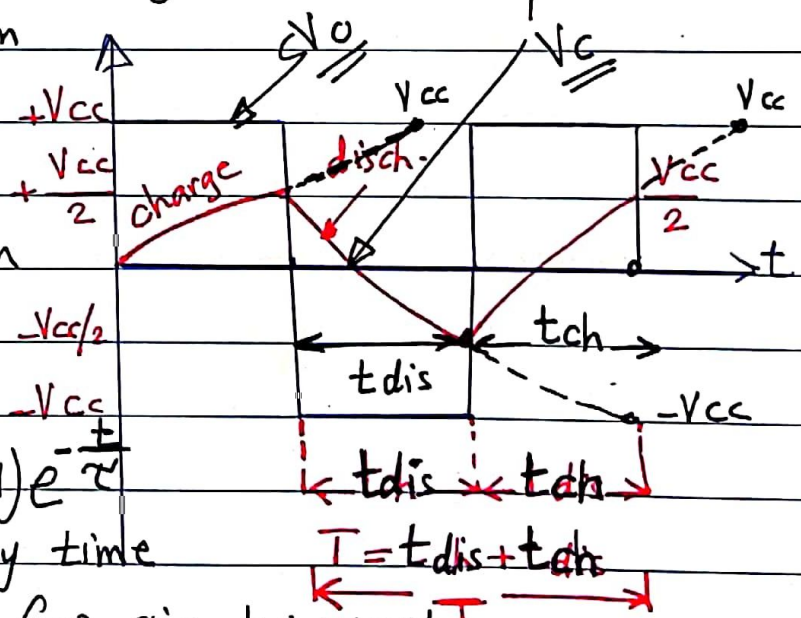τ : time constant, $\tau = R \times C_x$.



Charging time.

$$V_c(t) = V_{cc} + \left(\frac{-V_{cc}}{2} - V_{cc} \right) e^{-\frac{t}{\tau}}$$

at $t = t_{ch}$, $V_c(t) = \frac{V_{cc}}{2}$

$$\therefore \frac{V_{cc}}{2} = V_{cc} + \left(\frac{-V_{cc}}{2} - V_{cc} \right) e^{-\frac{t_{ch}}{\tau}}$$

$$\frac{V_{cc}}{2} = \frac{3}{2} V_{cc} e^{-\frac{t_{ch}}{\tau}}$$

$$\text{or } 1 = 3 e^{-\frac{t_{ch}}{\tau}} \Rightarrow e^{\frac{t_{ch}}{\tau}} = \frac{1}{3} \Rightarrow t_{ch} = \tau \ln 3$$

$$\therefore t_{ch} = 1.1 \tau = 1.1 R_x C_x$$

by symmetry $t_{ch} = t_{dis} = 1.1 R_x C_x$

$$T = t_{ch} + t_{dis} = 2.2 R_x C_x$$

$$\therefore f_0 = \frac{1}{2.2 R_x C_x}$$

* The o/p will be symmetrical square-wave o/p.

EXAMPLE: For $V_{cc} = \pm 10V$, $R_x = 1K\Omega$, $C_x = 0.01\mu F$
 $R_1 = R_2 = 1K\Omega$. Calculate f_0 & draw $V_o(t)$?


$$f_0 = \frac{1}{2.2 \times 10^3 \times 1 \times 10^{-8}} = \frac{10^5}{2.2} = 45.454 \text{ KHz}$$

EXA: Design an Astable MTV

to produce V_o with amplitude

$\pm 15V$ and $f_{req} = 40 \text{ KHz}$.

* Use ideal Op-Amp.?

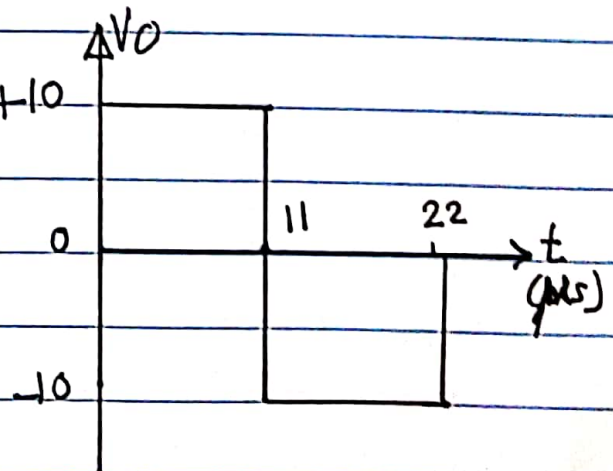

$$T = \frac{1}{f} =$$

To obtain assymetrical Square-Wave o/p, i.e

" +ve t.h.c > -ve t.h.c "




* We have to change charging or discharging time constant -

- To make $t_{dis} > t_{ch}$

* We can connect diode with Series resistance

$R < R_x$

$t_{ch} < 1/1 R_x C_x$

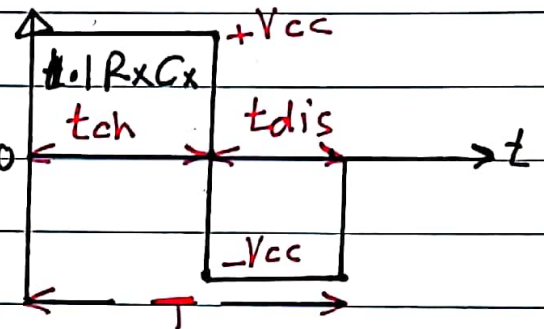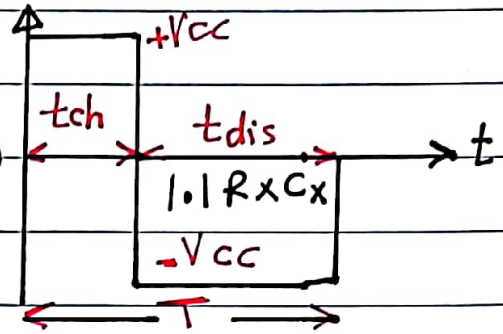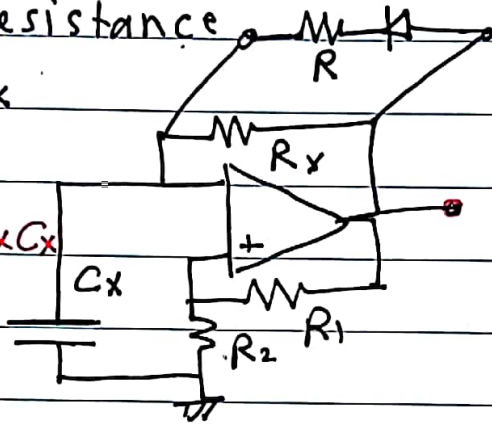


Assymetrical Squar wave

* To make $t_{ch} > t_{dis}$

We can change the direction of diode

$R < R_x$

$t_{dis} < 1/1 R_x C_x$

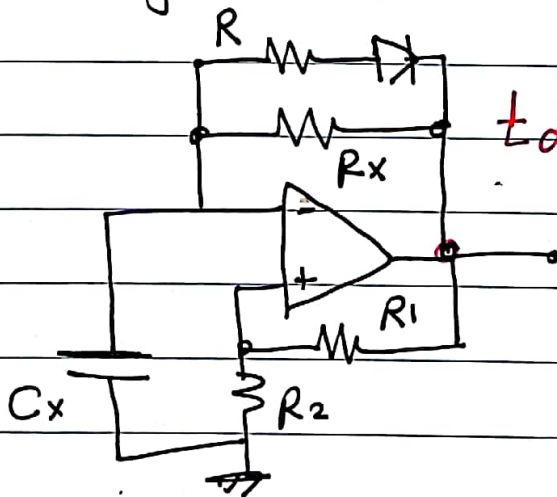

In both cases when Diode is "ON" => "Short"

So $R // R_x \Rightarrow < R_x$ which will make t_{ch} or $t_{dis} < 1/1 R_x C_x$; When Diode is OFF t_{ch} or $t_{dis} = 1/1 R_x C_x$

Monostable Multivibrator MMTV

"ONE-Shot" cct.

This cct. has one stable-state

"When $V_o = +V_{cc}, V_c = V^- = V_{\gamma}$ "


- Assume that, when we

switch-on, power supply

$V_o = +V_{cc}$, so $V^+ = \frac{V_{cc}R_2}{R_1+R_2}$

For $R_1 = R_2 = R$

$\therefore V^+ = \frac{1}{2} V_{cc}$

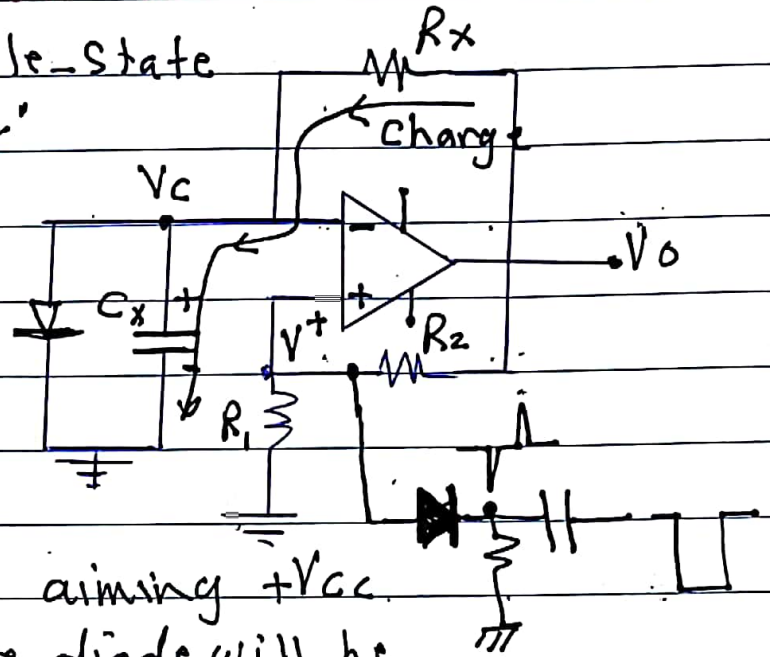


- The Cap. C_x will charge aiming $+V_{cc}$

but when $V_c = V_{\gamma}$, the diode will be

on. Fixing $V_c = V^- = V_{\gamma}$ and the cct. will be in steady-state. [$V_o = +V_{cc}, V^+ = \frac{1}{2} V_{cc}, V^- = V_{\gamma} < V^+$]

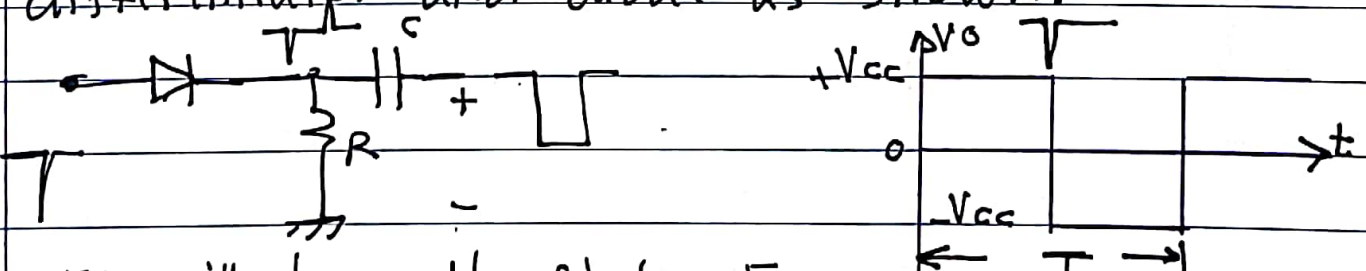- Now to change the state of comparator, we have to make $V^+ < V^-$, this can be, by applying a -ve pulse at \oplus terminal or through differentiator and diode as shown.



- This will change the state of

the comparator because $V^- > V^+$


and $V_o = -V_{cc}, V^+ = -V_{cc}/2$

- The Cap. C_x will start discharge

aiming $-V_{cc}$ but when C_x try

to exceed $-V_{cc}/2$, it will change the state, back

to steady state.

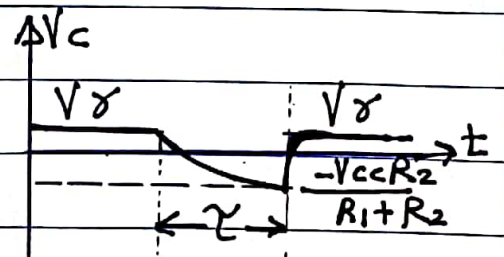

So For Full-cycle of output, we requires one pulse "Trigger" i.e we need "one shot" to obtain Full-cycle

The duration of the o/p pulse is controlled via R_x, C_x and pulse duration can be calculated as follow:

$$V_c(t) = V_f + (V_f - V_{initial}) e^{-\frac{t}{\tau}}$$

Consider the "ausg - state" [discharge]

$$\frac{V_{cc}}{2} = -V_{cc} + (V_x - (-V_{cc})) e^{-\frac{t_p}{R_x C_x}}$$

$$t_p = \tau \ln \left[\frac{1 + (V_x/V_{cc})}{1 - B} \right]$$

$$B = \frac{R_2}{R_1 + R_2}$$

For $R_1 = R_2 = R, V_x = 0$

$$t_p = R_x C_x \ln 2$$

$$0.5 V_{cc} = (V_x + V_{cc}) e^{-\frac{t_p}{\tau}}$$

$$0.5 = \left(1 + \frac{V_x}{V_{cc}}\right) e^{-\frac{t_p}{\tau}}$$

For $V_x \ll V_{cc}$

$$-0.5 = e^{-\frac{t_p}{\tau}} \Rightarrow t_p = \tau \ln 2 = 0.69 R_x C_x$$


$$t_p = 0.69 R_x C_x \text{ "Pulse duration"}$$

ExA: Design a MMTV to give a puls duration of $2 \mu s$ and a freq. of $100 kHz$. Draw $V_o(t)$, let $V_{cc} = \pm 10V$?

$$t_p = 0.69 R_x C_x = 2 \mu s$$


Assume: $C_x = 1 \mu F$ $\therefore R_x = \frac{2 \times 10^{-6}}{0.69 \times 10^{-6}}$

$$R_x = 2.898 k \Omega$$

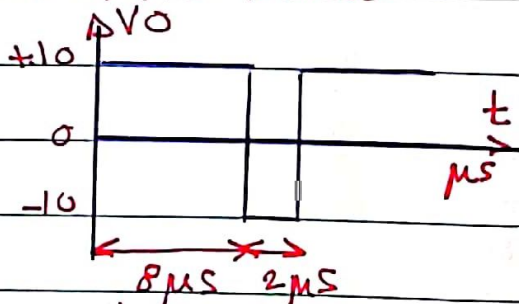

* The Freq. of Trigger must be = $100 kHz$

let $R_1 = R_2 = 1k \Omega$

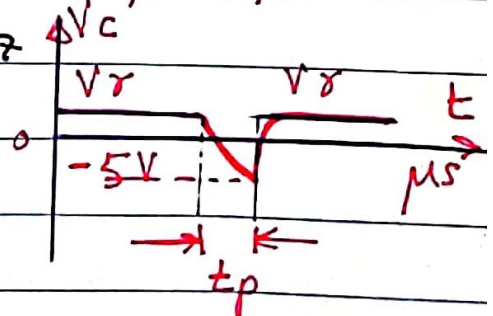


Tutorial Sheet ② Oscillator

Q₁ Given: $K_n = 2 \text{ mA/V}^2$, $V_{TN} = 2 \text{ V}$

Design the ckt. shown to

oscillate at $f_0 = 10 \text{ kHz}$

choose $C = 10 \text{ nF}$

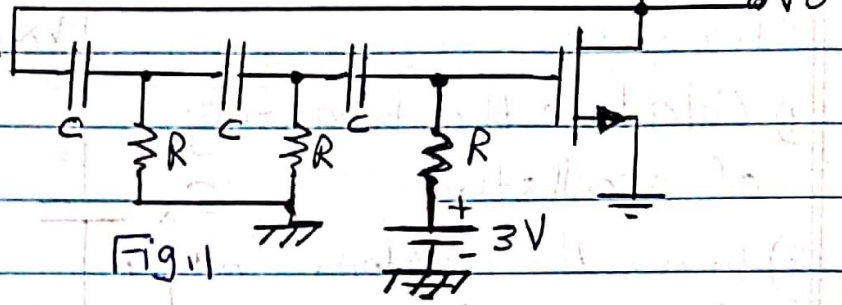

① 'Find R & R_D '?

② Draw $V_o(t)$?

③ Redraw this oscillator using op-Amp.

Q₂ Name the oscillator ckt.

Shown in Fig. 2 and


1) Calculate freq. of oscillation and minimum Amp. gain?

2) Calculate R_2 & R_1 ?

3) Draw $V_o(t)$?

4) what happen when $R_2 = 10R_1$?

Fig. 2

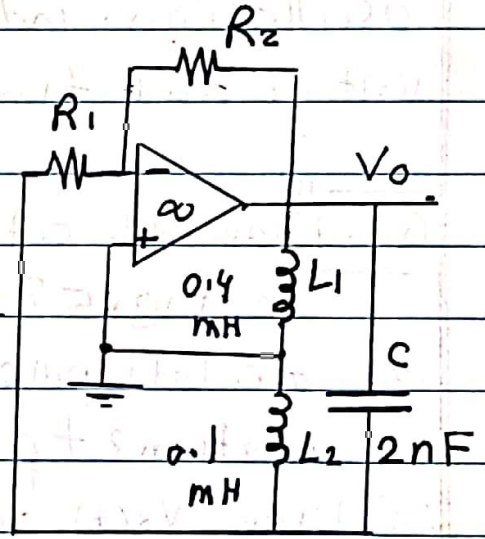

Q₃ Name the ckt. shown in Fig. 3 and:


1) Calculate freq. of oscillation.

2) The minimum gain required by the Amp. to start oscillation?

3) Calculate R_1 & R_2 ?

4) Redraw the ckt. using MOSFET Amplifier?


5) Draw $V_o(t)$ For two cycles?

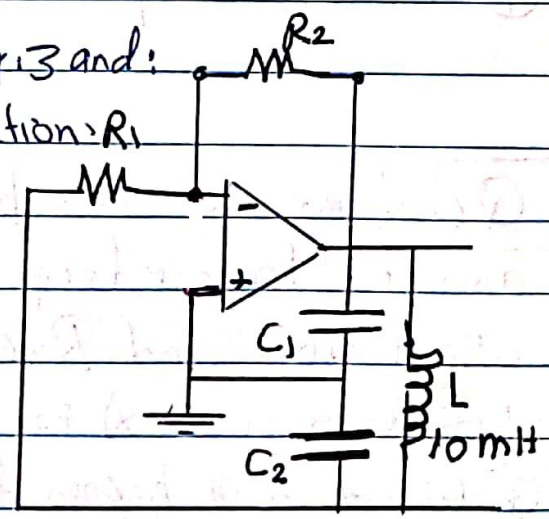

$C_2 = 800 \text{ pF}$, $C_1 = 20 \text{ pF}$

Q4


For the oscillator circuit shown:

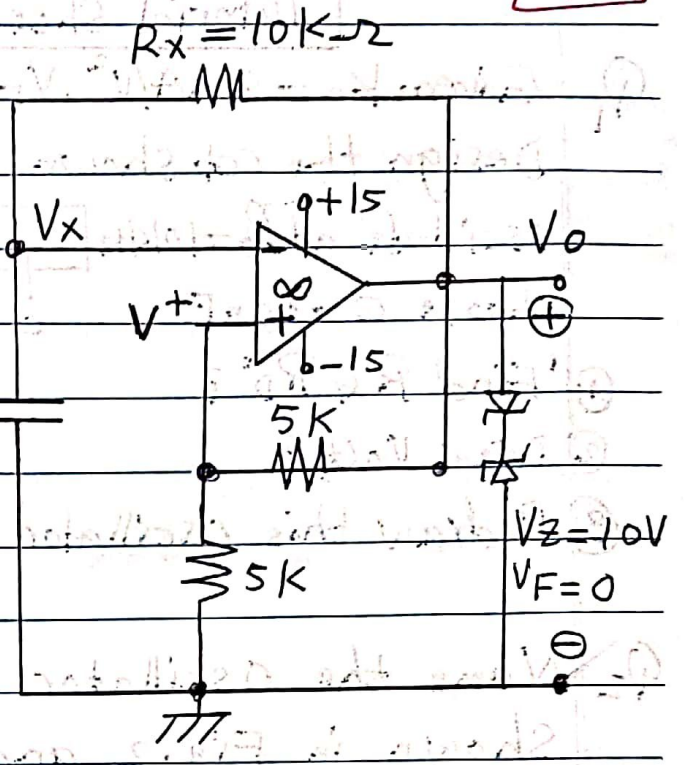

- 1) Calculate the frequency of oscillation.
- 2) Draw the waveform of $V_o(t)$ and $V_x(t)$ for two periods of oscillation, indicating voltage and time levels.

Q5


Name the cct. shown in Fig. 5?

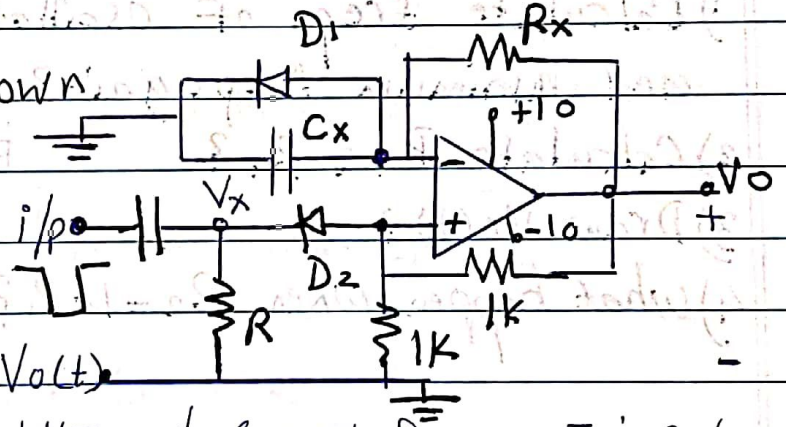

- 1) Calculate pulse duration? t_p ?
- 2) Draw $V_x(t)$ and $V_o(t)$.
- 3) To have $f_{req} = 20\text{kHz}$, what must f_{in} of input pulse?

Q6

Name the cct. shown

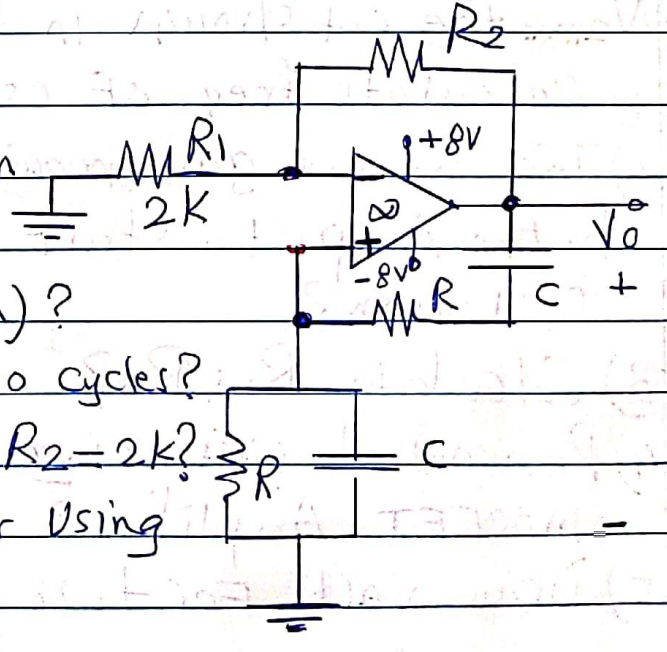

- 1) Calculate f_{req} of oscillation? and R_2 (min)?
- 2) Sketch $V_o(\text{max})$ for two cycles?
- 3) What will happen for $R_2 = 2\text{k}$?
- 4) Redraw the oscillator using BJT Amp?

Power Amplifiers
Large-Signal Amps

→ delivered to Load P_L

Convert some of the D.C power drawn from D.C sources into A.C power

* Compared to Small-Signal Amps. power Amps have the following characteristics:

- 1) Deal with Large Voltage and Current signals.
- 2) Large Size active devices due to high power rating, heat sink may be required.
- 3) Usually, Located as final stages in electronics system such as Radio receiver (before speaker).
- 4) Amplify power of the A.C input signal.
- 5) The most important parameter is the conversion efficiency $\eta = \frac{\text{Average A.C Power delivered to load}}{\text{Average D.C power drawn from D.C Source}}$

Graphical technique is used to calculate the performance. (P_L), P_S , $\eta\%$


Classification of power Amplifiers

They are classified according to the angle by which the output current and voltage are present of the full input cycle "Conduction angle of the active device".

* The input is Full-Cycle:


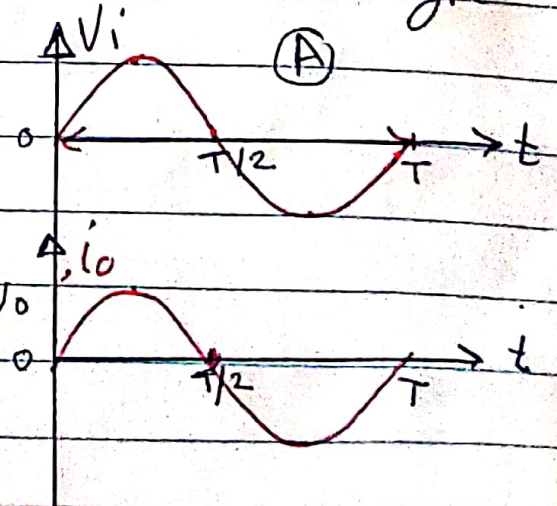
1) Class-A power Amp:

The o/p current flows for a complete cycle, V_o is present for 360° full-cycle.



Class-AB:

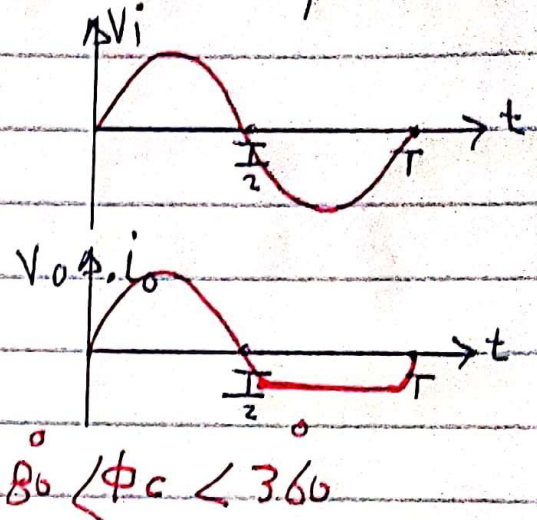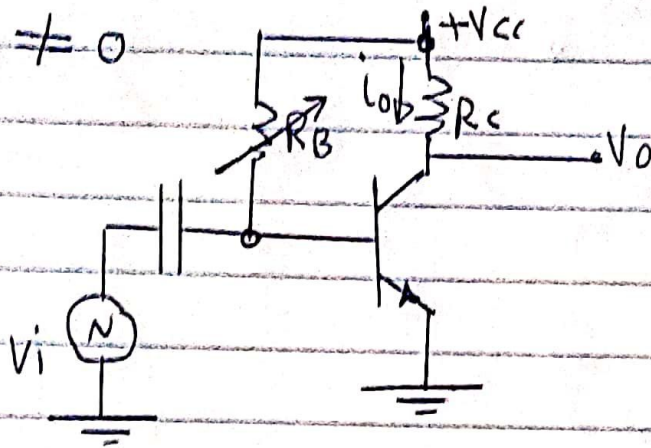The o/p is present and the o/p Current flows for more than half-cycle and less than Full cycle $180^\circ < \phi_c < 360^\circ$. The Q-pt is present (Located) Some where between class-A and class-B position $I_{CQ} \neq 0$



* Normally class-AB is more close to class-B than class-A, practically class-AB is a remedy to a problem happened in class-B push-pull which is called "crossover-distortion", solved by biasing Amp. more than cut-off $I_{CQ} \neq 0$, which makes the Amp. works as class-AB.

Class-C Power Amp.


The o/p is present for a small conduction Angle $\phi_c < 180^\circ$

The Q-pt is located ~~to~~ down

the cut-off. $I_{CQ} < 0$

It has an application as RF Amp. in Communication Transmitters.

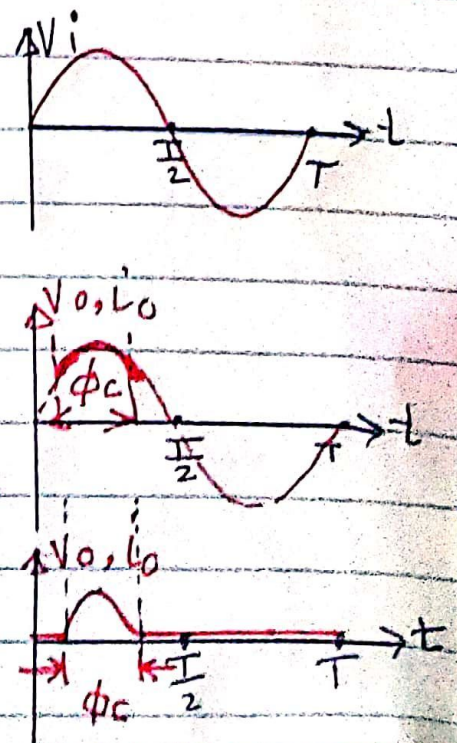* This class widely used as RF power amp. with high Conversion efficiency.





The o/p signal shape depends on the position of the Q-point. For class-A, the optimum position for class-A Q-pt. is at the center of D.C. Load line.

* The Amp. draws D.c power with or without i/p signal because $I_{CQ} \neq 0$


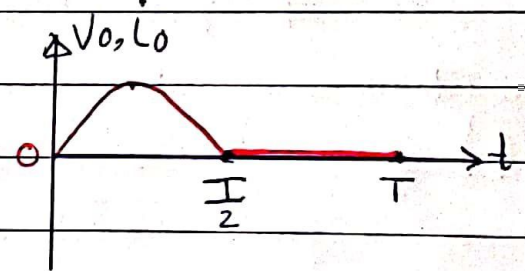
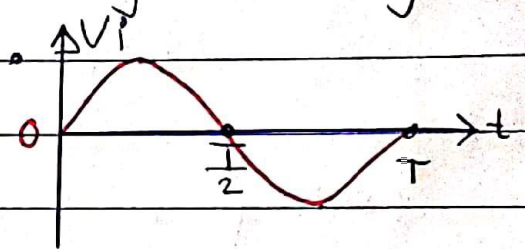
2) Class-B power Amp.

The o/p current flows for a half-cycle and the o/p is present for 180° i.e half-cycle. ideally the Q-pt at cut-off ($I_{CQ} = 0$).




* The Amp. will NOT draw D.c power from V_{CC} for No A.c input signal because $I_{CQ} = 0$ So the D.c power drawn from D.c Source $P_S = I_{CQ} \cdot V_{CC} = 0$



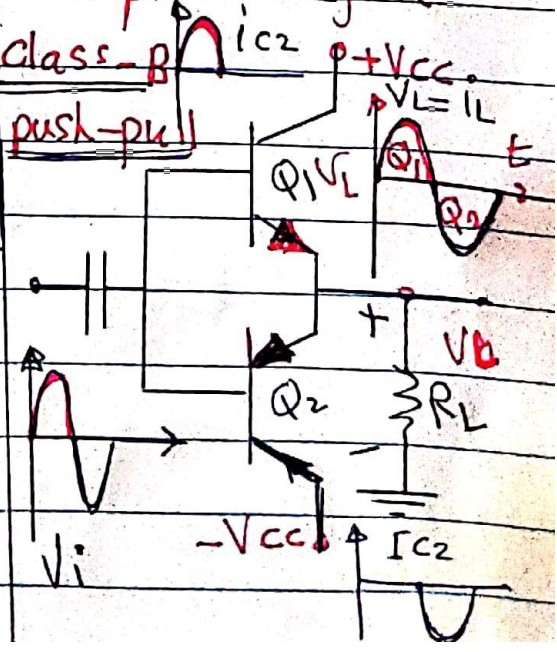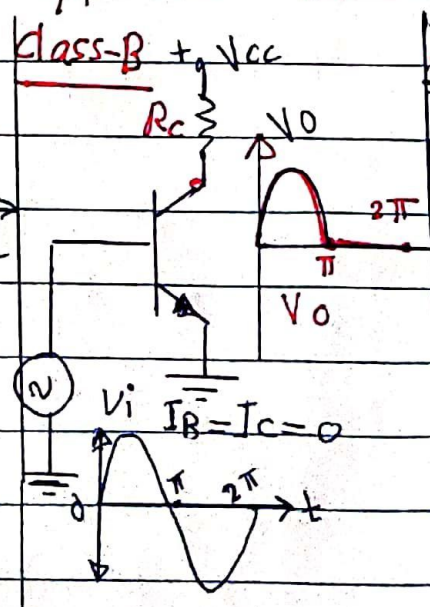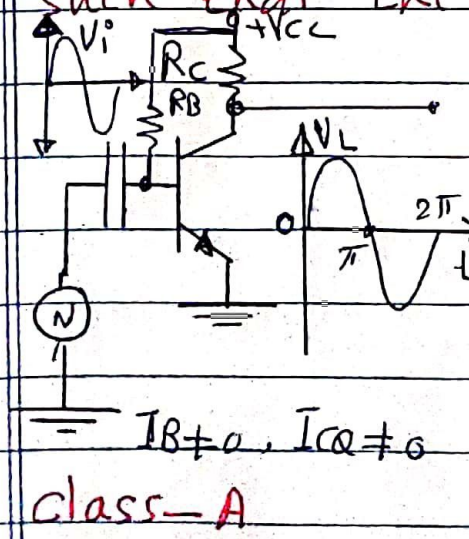* Normally class-B is used in "push-pull arrangement" two transistors are used, one process +ve H.c of V_i and the other to process the -ve half-cycle of V_i such that the o/p will be a complete cycle.



o/p Voltage and Current for classer

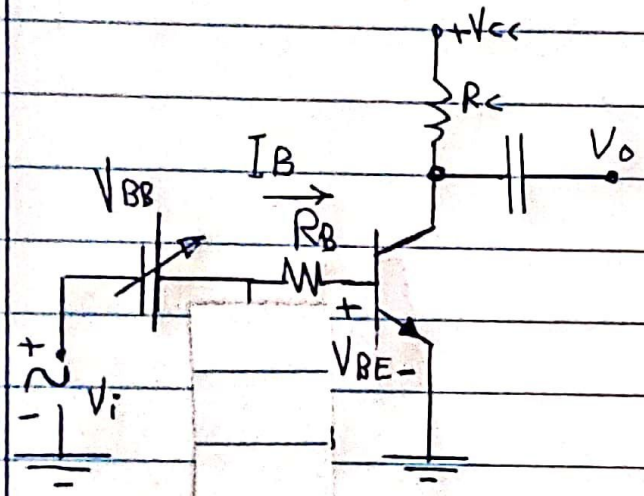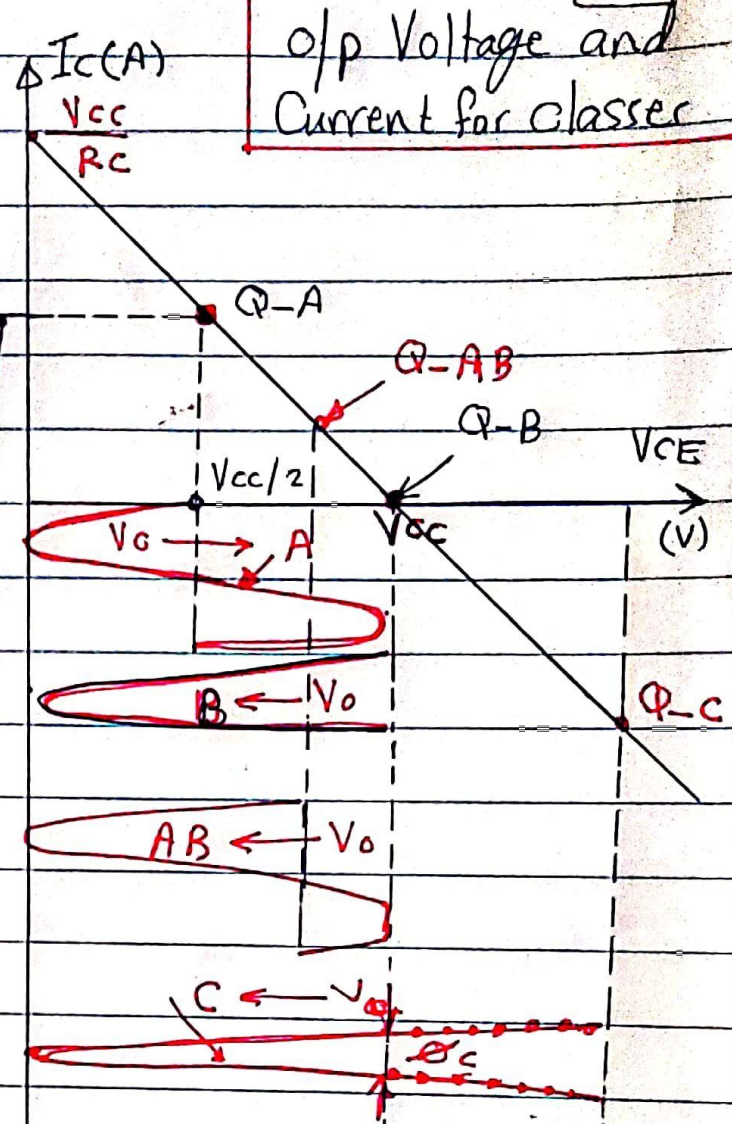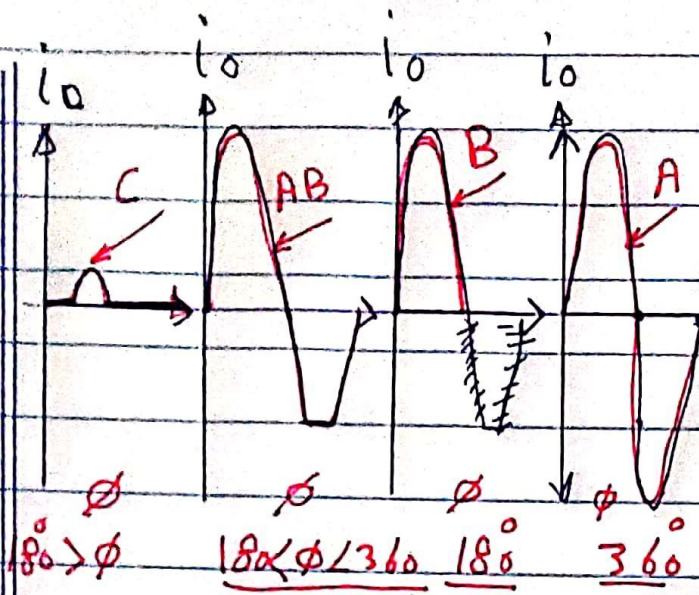

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

① When $V_{BB} > V_{BE}$, the BJT will be in F.A.M, $I_C = \beta I_B$
 * The BJT can be biased as class-A or AB
 * When $V_{BB} = V_{BE}$, $I_B = 0$
 $I_C = 0 \rightarrow$ Cut-off.
 * When $V_{BB} = 0$ or $V_{BB} < 0$ the BJT will be as class-C mode. Down the cut-off mode
 In A, B, AB V_i can be zero

* ~~No~~ No current flows until V_i is applied.
 * In class-C, the BJT will be on only in +ve H.C of V_i and only when $V_i > V_{BE}$, which makes $I_B > 0$. So I_B will be > 0 and $I_C > 0$ which will flow for $< 180^\circ$. For small conduction angle $\phi_c < 180^\circ$.
 * by varying V_{BB} , the ckt. can be biased as class-A, B, AB or C.

Let $V_{CC} = 10V$, $R_C = 10\Omega$, $\beta = 25$, $V_{BE} = 0.6V$

$$R_B = 10k\Omega$$

$$V_{CE} = V_{CC} - I_C R_C, I_B = \frac{I_C - V_{BE}}{R_B}, V_{BB} = V_{BE} + I_B R_B$$

* For $V_{CE} = 0$, $I_C = \frac{10}{10} = 1A$

* For $I_C = 0$, $V_{CE} = 10V$

* ∴ D.C. L.L points: $(10V, 0)$, $(0V, 1A)$.

① For ideal class-A: Q pt \rightarrow Center of D.C. L.L
i.e. $I_{CQ} = 1/2 = 0.5A$, $V_{CEQ} = \frac{1}{2} V_{CC} = 5V$.

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.5}{25} = 0.02A \rightarrow 20mA$$

$$\therefore V_{BB} = V_{BE} + I_{BQ} R_B = 0.6 + 0.02 \times 10^3 = 20.6V$$

② For class-B, $I_{CQ} = 0$, $I_{BQ} = 0 \rightarrow V_{BB} = 0.6V$

$$\therefore V_{BB} = V_{BE} = 0.6V$$

③ For class-AB, $[0 < I_B < 0.02A]$

let $I_B = 0.01A$

$$\therefore V_{BB} = 0.6 + 0.01 \times 10^3 = 10.6V$$

④ Class-C, $V_{BE} = 0$ or $-ve$

let $V_{BB} = 0$, $I_B = \frac{V_i - V_{BE}}{R_B}$

only when $V_i > 0.6V$

$$I_B > 0, I_C > 0$$

Class-A power Amp.

The o/p is full-cycle, i.e. i_c flows for 360° and V_L is present for full-cycle. There are two types of Class-A depending on the position of the Load R_L .

(i) Direct-coupled (Series-Fed) type.

The load is directly connected between V_{CC} and Collector, as shown in Fig.

In this class, ideally

Q-point at Center of D.C.L.L



$$\text{i.e. } V_{CEQ} = \frac{V_{CC}}{2}$$

$$I_{CQ} = \frac{V_{CC}}{2R_L}$$

* For Max. output

$$V_{CEP} = V_{CC}/2$$

$$i_{CP} = \frac{V_{CC}}{2R_L}$$

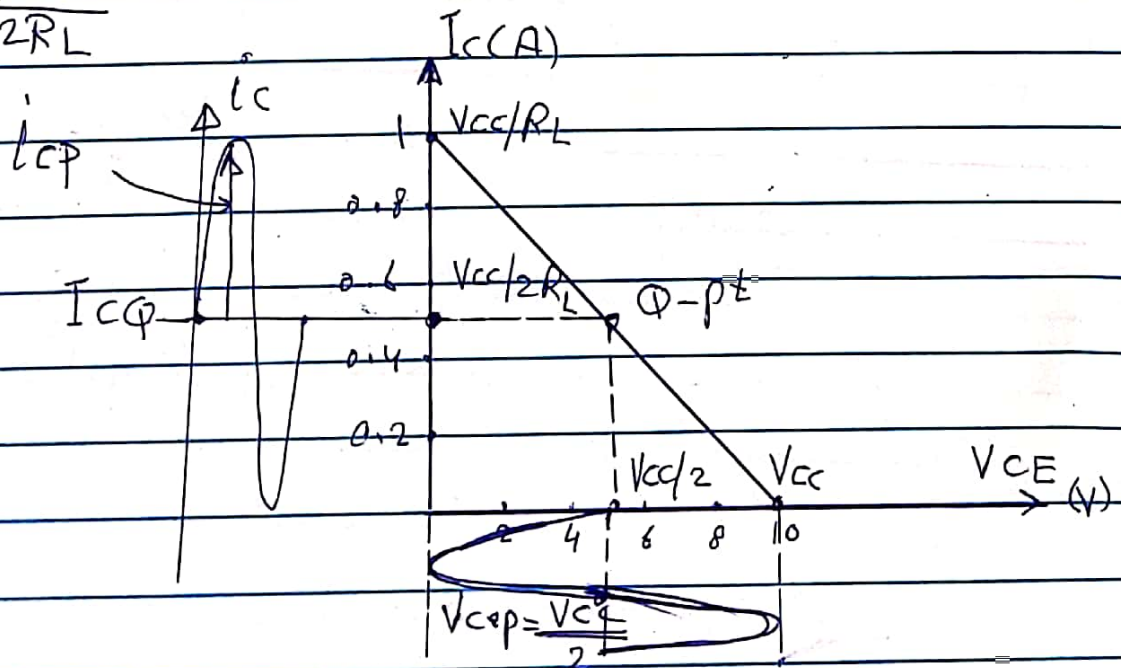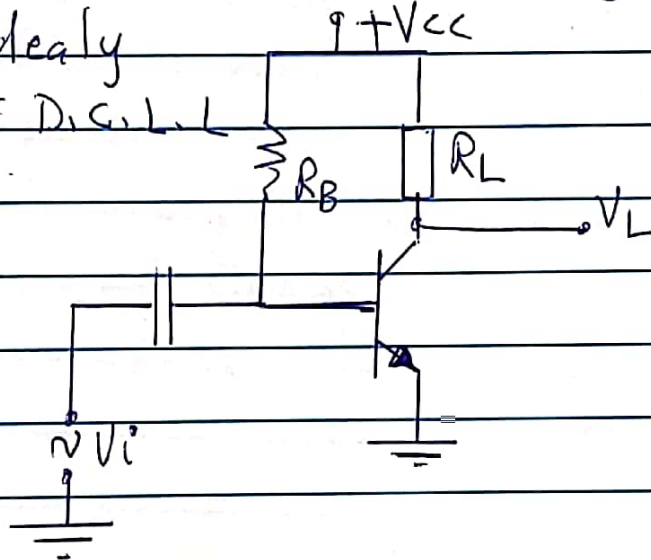

Average D.C. input power drawn from V_{CC}

$$\bar{P}_S = V_{CC} \cdot I_{CQ}$$


where I_{CQ} is from D.C. Analysis.

and can be obtained as follows:

$$V_{CC} + I_B R_B + V_{BE} = 0$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B} - I_{BQ}$$

$$I_{CQ} = \beta I_{BQ}$$

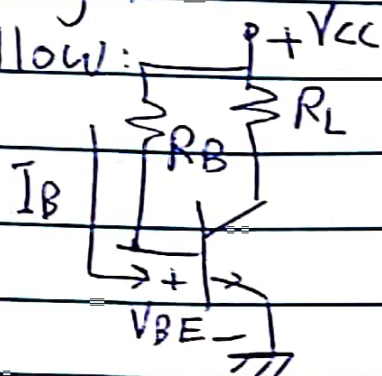

The average A.C. power delivered to load R_L is obtained when an A.C. input signal is applied which will produce A.C. base current i_b which will produce A.C. collector current $i_c = \beta i_b$ and causes A.C. voltage on the load $V_L = i_c \cdot R_L$
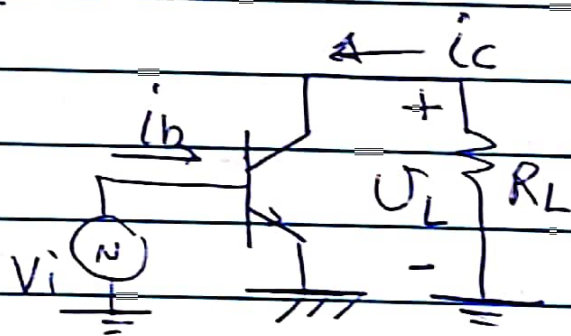
$$\begin{aligned} \bar{P}_L &= I_L(\text{rms}) \cdot V_L(\text{rms}) \\ &= \frac{I_L(\text{rms})^2 \cdot R_L}{V_L(\text{rms})} \end{aligned}$$



In terms of R_L peak or peak-peak value

$$I_L(\text{rms}) = i_{LP} / \sqrt{2} \quad \Rightarrow \quad V_L(\text{rms}) = V_{LP} / \sqrt{2}$$

$$\text{So } \bar{P}_L = \frac{(i_{LP}^2 R_L)}{2} \quad \text{or } \bar{P}_L = \frac{V_{LP}^2}{2 R_L}$$

$$\text{OR } \bar{P}_L = \frac{V_{LP} \cdot I_{LP}}{2}$$

$$\text{The Conversion efficiency} = \frac{\bar{P}_L}{\bar{P}_S} \times 100\%$$

The difference between \bar{P}_s and \bar{P}_L is the power dissipated in the transistor and R_L which is in the form of heat.

In R_L : $P_D = I_{CQ}^2 R_L$.

In transistor: $\bar{P}_D(\text{trans}) = \bar{P}_s - P_L - I_{CQ}^2 R_L$

Maximum Conversion efficiency:

This happens when Q-pt. at center of D.C. L.L, $V_{CEQ} = V_{CC}/2$, $I_{CQ} = V_{CC}/2R_L$

$\bar{P}_s = V_{CC} \cdot I_{CQ}$.

$V_{CEQ} = V_{CC}/2$, $I_{CQ} = V_{CC}/2R_L$

$P_L = \frac{V_{CEQ} \cdot I_{CQ}}{2} = \frac{V_{CC} \cdot V_{CC}}{8R_L} = \frac{V_{CC}^2}{8R_L}$

$\bar{P}_s = V_{CC} \cdot I_{CQ} \Rightarrow \text{but } I_{CQ} = \frac{V_{CC}}{2R_L}$


$\bar{P}_s = \frac{V_{CC}^2}{2R_L}$

$\eta = \frac{P_L}{\bar{P}_s} \times 100\% = \frac{\frac{V_{CC}^2}{8R_L}}{\frac{V_{CC}^2}{2R_L}} \times 100\%$

$\eta = \frac{V_{CC}^2}{8R_L} \times \frac{2R_L}{V_{CC}^2} \times 100\% = 25\% = \eta_{\text{max}}$

EXA: Given $V_{BE} = 0.7V$, $\beta = 25$

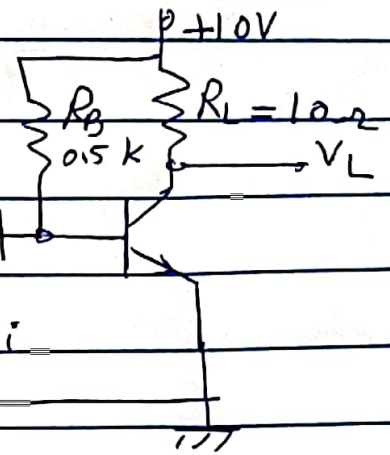- 1) Calculate I_{BQ} , I_{CQ} , $P_D(\text{tran})$, $P_D(R_L)$ and \bar{P}_S . (without I/p signal)



- 2) If an A.c i/p is applied and cause a peak base current of $i_{bp} = 16mA$. Calculate \bar{P}_S , \bar{P}_L , $\xi\%$ and $P_D(R_L)$ and $P_D(\text{tran})$.

- 3) Sketch D.C.L.L and A.C.L.L, indicate Q-pt and Collector Current and V_{CE} Swings.

- 4) What is i_{bp} which gives max $\xi\%$?

$$10 - I_B R_B + V_{BE} = 0$$

$$\therefore I_B = \frac{10 - 0.6}{0.5} = 18.8 \text{ mA}$$

$$I_{CQ} = \beta I_B = 25 \times 18.8 = 470 \text{ mA} = 0.47 \text{ A}$$

$$V_{CE} = 10 - I_C R_C = 10 - 0.47 \times 10 = 5.3 \text{ V}$$

$$\bar{P}_S = V_{CC} \cdot I_{CQ} = 10 \times 0.47 = 4.7 \text{ Watt}$$

$$P_D(R_L) = I_C^2 R_L = (0.47)^2 \cdot 10 = 2.209 \text{ W}$$

$$P_D(\text{tra}) = I_{CQ} \cdot V_{CEQ} = 0.47 \times 5.3 = 2.491 \text{ W}$$

*All \bar{P}_S is dissipated in R_L and tran. (In the form of heat)

$$2) \bar{P}_S = I_{CQ} \cdot V_{CC} = 0.47 \times 10 = 4.7 \text{ W}$$

$$\bar{P}_L = i_c^2(\text{rms}) R_L = i_{cp}^2 \times R_L$$

$$i_{cp} = \beta i_{bp} = 25 \times 16 \text{ mA} = 0.4 \text{ A}$$

$$\therefore \bar{P}_L = \frac{(0.4)^2}{2} \times 10 = 0.8 \text{ W}$$

$$\xi = \frac{\bar{P}_L}{\bar{P}_S} \times 100\% = \frac{0.8}{4.7} \times 100\% = 17\%$$

$$P_D(R_L) = I_{CQ}^2 R_L = (0.47)^2 \times 10 = \underline{2.209 \text{ Watt}}$$



i.e $P_D(R_L) \rightarrow$ does NOT change.

$$P_D(\text{tran}) = P_S - P_D(R_L) - \bar{P}_L = 4.7 - 2.209 - 0.8$$

$$P_D(\text{tran}) = 1.691 \text{ Watt}$$

$\&$ $P_D(\text{tran})$ is reduced from 2.491 \rightarrow 1.691 Watt by the amount of \bar{P}_L which is 0.8W

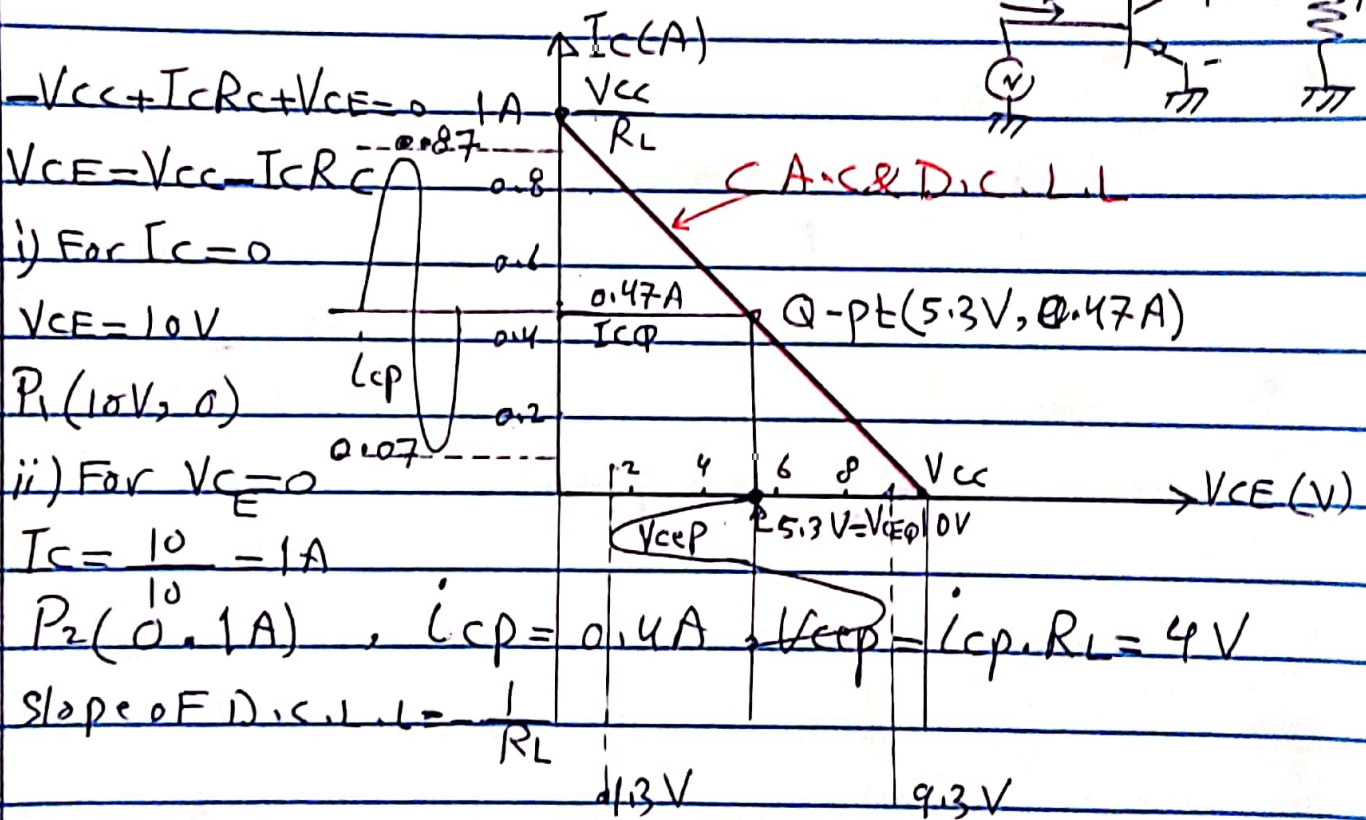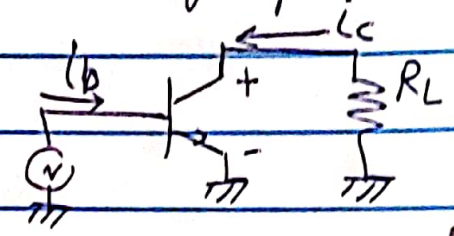i.e when A.C signal is applied: Some of $P_D(\text{tran})$ is converted to an A.C average power delivered to Load



A.C.L.L.: $V_{ce} = -i_c R_L \rightarrow$ slope = $-\frac{1}{R_L}$
 D.C.L.L & A.C.L.L have the same slope = $-\frac{1}{R_L}$

4) For I_{max} , $I_{cp} = \frac{1}{2} I_{Cmax} = \frac{1}{2} \times 0.94 = 0.47A$
 (Q-pt. must be at center of D.C.L.L & $I_{cp} = \frac{1}{2} \frac{V_{CC}}{R_L}$)
 $I_{bp} = I_{cp} / \beta = 0.47 / 25 = 18.8mA$

ii) Class-A transformer coupled P.A:

In this type, the load is connected at the secondary of a transformer, so for the same P_s there is no $I_{CQ}^2 R_L$ i.e \bar{P}_L will increase or less \bar{P}_s is required for the same \bar{P}_L "Compared to direct-coupled type" which means higher conversion efficiency?


The cct-diagram is shown in Fig.

* For given $V_{CC}, R_1, R_2, V_{BE}, \beta$

D.C. Analysis gives:

Assume ideal primary coil with series-resistance $R_s = 0$
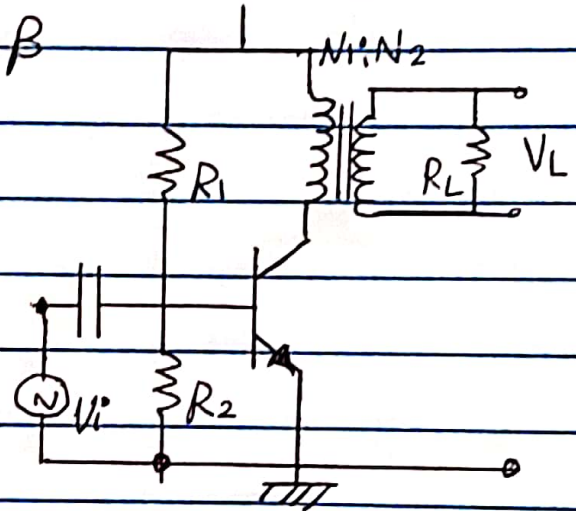
$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2} \quad , \quad R_{th} = R_1 // R_2$$



$$I_B = \frac{V_{th} - V_{BE}}{R_{th}} \quad , \quad I_C = \beta I_B = I_{CQ}$$

$$V_{CE} = V_{CC}$$


$$P_s = V_{CC} \cdot I_{CQ} = P_D(\text{trans})$$

For A.C Analysis:

\bar{P}_L can be calculated from primary side or from secondary side.

* From secondary side

Use R_L, I_L, V_L

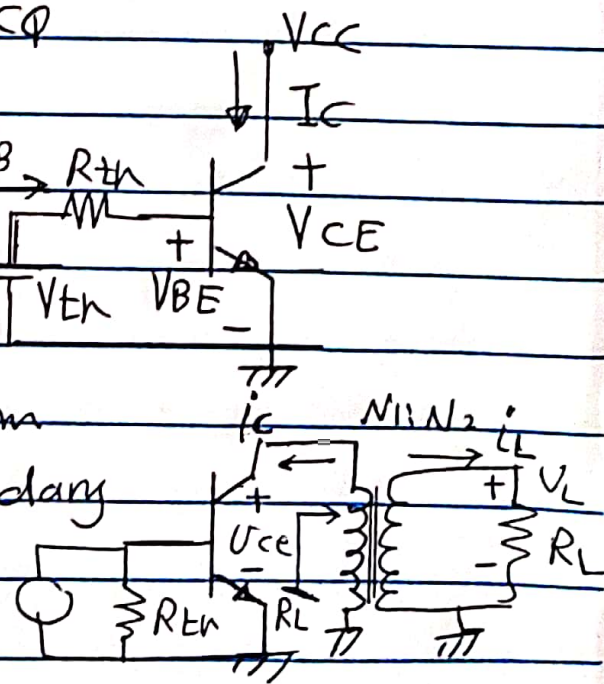

$$\bar{P}_L = I_L(rms) \cdot V_L(rms) = \frac{I_{LP}}{\sqrt{2}} \times \frac{V_{LP}}{\sqrt{2}} = \frac{V_{LP} \cdot I_{LP}}{2}$$

$$\text{OR } \bar{P}_L = I_L^2(rms) R_L = \frac{I_{LP}^2}{2} R_L$$

$$\text{OR } \bar{P}_L = \frac{V_{LP}^2}{R_L} = \frac{V_{LP}^2}{2R_L}$$


* From primary side: Use I_c, V_{ce}, \bar{R}_L
 where \bar{R}_L is A.C reflected resistance seen from primary $\bar{R}_L = \left(\frac{N_1}{N_2}\right)^2 R_L = a^2 R_L$

where $\left(\frac{N_1}{N_2}\right)$: transformer turn-ratio


$$\bar{P}_L = I_c(rms) \cdot V_{ce}(rms) = \frac{I_{cP}}{\sqrt{2}} \frac{V_{ceP}}{\sqrt{2}} = \frac{I_{cP} \cdot V_{ceP}}{2}$$

$$\text{OR } \bar{P}_L = I_c^2(rms) \bar{R}_L = \frac{I_{cP}^2}{2} \bar{R}_L$$
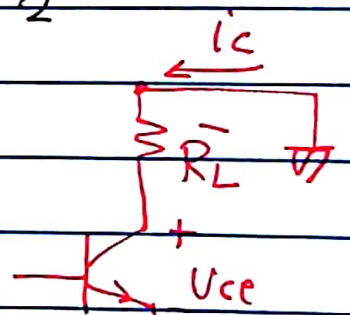
$$\text{OR } \bar{P}_L = \frac{V_{ceP}^2(rms)}{\bar{R}_L} = \frac{V_{ceP}^2}{2\bar{R}_L}$$




D.C. & A.C. LL

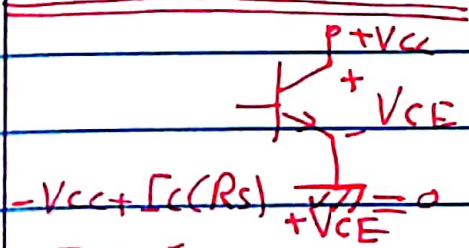

$-V_{CC} + I_c(R_s) + V_{BE} = 0$
 For $I_c = 0$
 $V_{CE} = V_{CC}$
 For $V_{CE} = 0$
 $I_c = \frac{V_{CC} - V_{BE}}{R_s} = \frac{V_{CC} - V_{BE}}{R_s}$

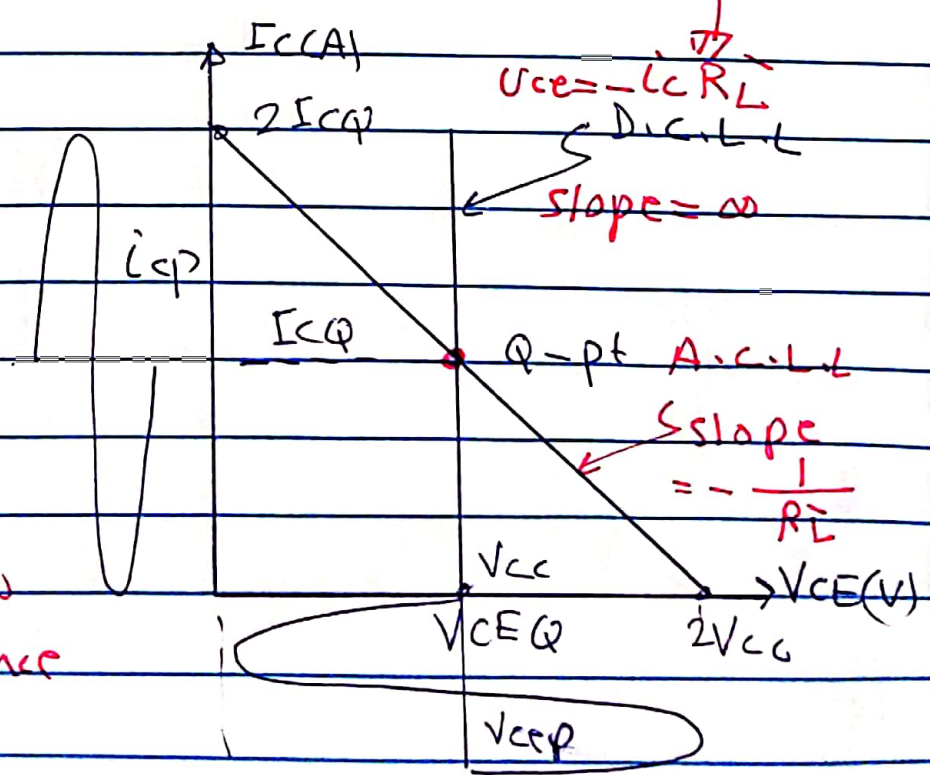" R_s = Series resistance of primary coil"



At Q-pt. A.c & D.c L.L are intersected, So it satisfied both A.c & D.c lines. At Q-pt.

$$V_{CEQ} - V_{CC} = I_{CQ} \cdot R_L, \quad I_{CQ} = \frac{V_{CC}}{R_L}, \quad R_L = \frac{V_{CC}}{I_{CQ}}$$

To Find Intersections of A.c L.L on

I_C & V_{CE} axis: (For V_{CE} axis) --

$$V_{CE} = V_{CEQ} + \Delta V_{CE}$$

$$\text{slope of A.c L.L} = \frac{1}{R_L} = \frac{\Delta I_C}{\Delta V_{CE}}, \quad \Delta V_{CE} = \Delta I_C R_L$$

$$\text{but } \Delta I_C = I_{CQ} \Rightarrow \Delta V_{CE} = I_{CQ} R_L \text{ and}$$

$$I_{CQ} R_L = V_{CC} \Rightarrow V_{CE} = V_{CC} + V_{CC} = 2V_{CC}$$

(For I_C axis): $I_C = I_{CQ} + \Delta I_C$

$$\frac{\Delta I_C}{R_L} = \frac{V_{CC}}{R_L} = I_{CQ}$$

$$\therefore I_C = I_{CQ} + I_{CQ} = 2I_{CQ}$$

Max intersections are: $2V_{CC}$ & $2I_{CQ}$.

Max. Conversion efficiency ζ_{max} ?

$$\zeta = \frac{P_L}{P_S} \times 100\% \quad , \quad P_L = \frac{V_{LP}^2}{2R_L}$$

P_L will be Max. when $V_{LP} = V_{LP(max)} = V_{CC}$ ("See A.c L.L.")

$$\therefore P_{L(max)} = \frac{V_{CC}^2}{2R_L}$$

$$\text{and } P_S = V_{CC} \cdot I_{CQ} = \frac{V_{CC} \cdot V_{CC}}{R_L} = \frac{V_{CC}^2}{R_L}$$

$$\therefore \zeta_{max} = \frac{P_{L(max)} \times 100\%}{P_S} = \frac{(V_{CC}^2 / 2R_L) \times 100\%}{V_{CC}^2 / R_L} = 50\%$$

$$\therefore \zeta_{max} = 50\% \quad \text{[When } V_{CEQ} = V_{CC}, V_{CEP} = V_{CC}]$$

EXA: A class-A transformer-coupled power Amp. deliver a Max. Load power of 4W to 8Ω load. If the BJT has $\beta = 20$, $V_{BE} = 0.6V$ and $V_{CC} = 20V$.

- 1) Calculate $(\frac{N_1}{N_2})$ of the transformer.
- 2) The value of R_B .
- 3) Transistor ratings (I_{Cmax} , V_{CEmax} , P_{Dmax}).
- 4) Sketch D.c. & A.c. L.L with i_C & V_{CE} swings.

For max. operation: $\xi_{max} = 50\% = \frac{P_L}{P_S}$

~~$$P_S = \xi_{max} P_{Dmax} = 0.5 P_{Dmax}$$~~

$$\bar{P}_S = \frac{P_{L(max)}}{\xi_{max}} = \frac{4W}{0.5} = 8W$$

$$\bar{P}_S = V_{CC} \cdot I_{CQ} \Rightarrow I_{CQ} = \frac{\bar{P}_S}{V_{CC}} = \frac{8}{20} = 0.4A$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.4}{20} = 0.02A$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{20 - 0.6}{0.02} = \frac{19.4V}{0.02} = 970\Omega$$

$$\left(\frac{N_1}{N_2}\right) = a = \sqrt{\frac{R_L}{R_L}} \quad (R_L = a^2 R_L)$$

$$R_L = \frac{V_{CC}}{I_{CQ}} = \frac{20V}{0.4} = 50\Omega$$


$$a = \frac{N_1}{N_2} = \sqrt{\frac{50}{8}} = 2.5$$

$$I_{Cmax} = 2I_{CQ} = 0.8A, \quad V_{CEmax} = 2V_{CC} = 40V$$

$$P_{D(max)} = \bar{P}_S - P_L = 8 - 4 = 4W$$

For No A.c signal $P_L = \bar{P}_S = 8W$.

(Worst Case P_D on BJT).

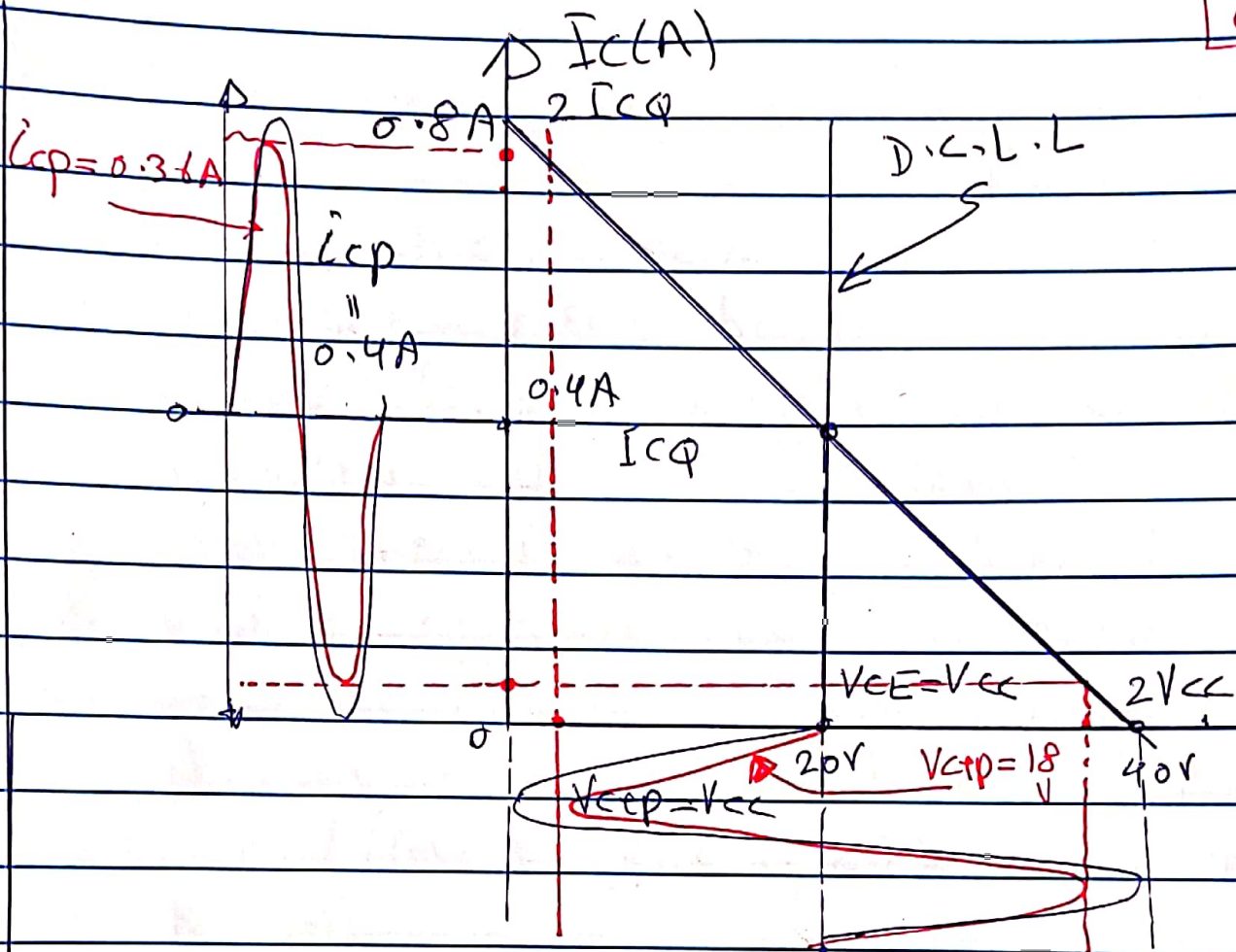

EXA 2: For the same R_B (From previous example) calculate \bar{P}_L , $\%$, P_D when the input signal causes a peak collector current of $0.36A$? [Sketch i_c & V_{ce}]

* For the same ($R_B = 970\Omega$, $I_B = 20\mu A$, $I_{cQ} = 0.4A$)

$$\text{So } \bar{P}_S = 0.4 \times 20 = 8W$$

$$\bar{P}_L = \frac{i_{cp}^2}{2} R_L = \frac{(0.36)^2}{2} \times 50 = 3.24W$$

$$\% = \frac{3.24 \times 100}{8} = 40.5\%$$

$$P_D (\text{trans}) = \bar{P}_S - \bar{P}_L = 8 - 3.24 = 4.76W$$

$$V_{cep} = i_{cp} \cdot R_L = 0.36 \times 50 = 18V$$


Class-B push-pull power Amplifier

In this p.A, two transistors are used. ONE For processing +ve H.c of the A.c input and the other to process the -ve H.c. because the Q-pt is at cut-off ($I_{CQ} = 0$) i.e. No \bar{P}_S For No V_S . The transistor will draw \bar{P}_S From D.c Source only when there is an A.c i/p signal. i.e. compared to class-A, less \bar{P}_S is required for the same \bar{P}_L , So the Conversion efficiency is high. The transistors can be of the same type or different types (PNP & NPN) or (n-channel & p channel).

"Transformer-coupled, class-B push-pull power Amp"

* "Using Same type of transistor"

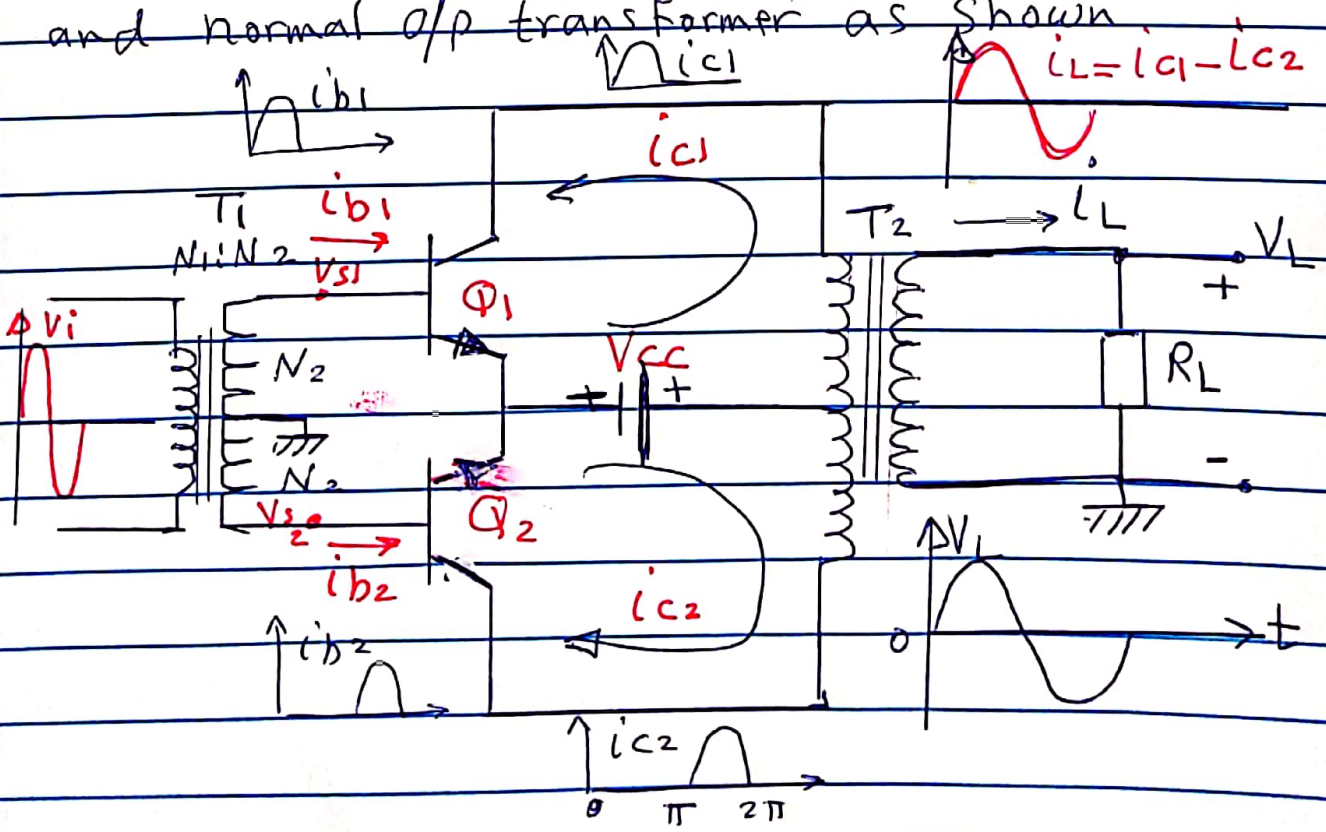* This type must use i/p Center-tapped Trans. and normal o/p transformer as shown"




Class-B push-pull power Amplifier

In this p.A, two transistors are used. ONE For processing +ve H.c of the A.c input and the other to process the -ve H.c. because the Q-pt is at cut-off ($I_{CQ} = 0$) i.e. No \bar{P}_S For No V_S . The transistor will draw \bar{P}_S From D.c Source only when there is an A.c i/p signal. i.e. compared to class-A, less \bar{P}_S is required for the same \bar{P}_L , So the Conversion efficiency is high. The transistors can be of the same type or different types (PNP & NPN) or (n-channel & p channel).

"Transformer-coupled, class-B push-pull power Amp"

* "Using Same type of transistor"

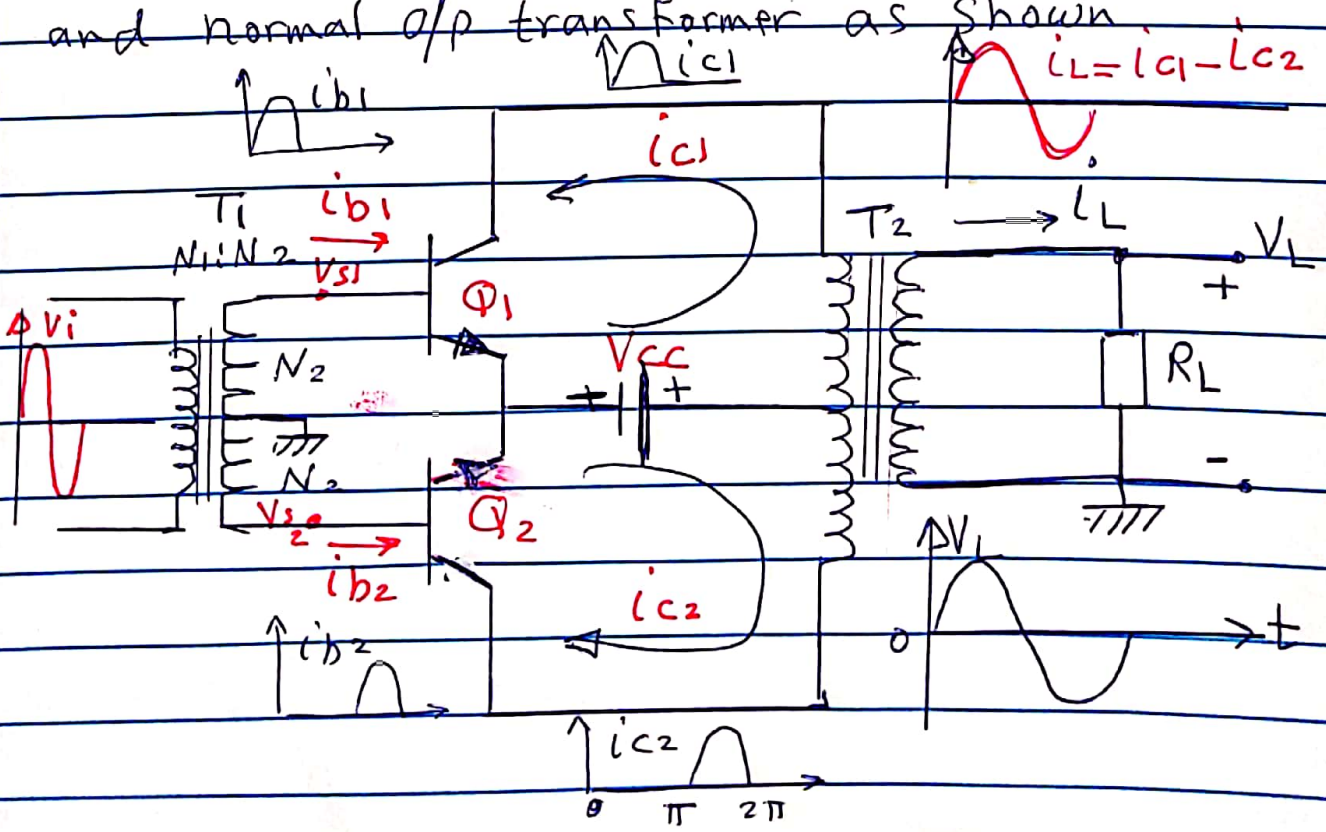* This type must use i/p Center-tapped Trans. and normal o/p transformer as shown"



The waveforms of V_i, i_{c1}, i_{c2}
 i_L and V_L are shown-








$$I_{cp1} = I_{cp2} = \frac{V_{cp}}{R_L}$$

where $R_L = a^2 R_L$

R_L : A.c reflected Resistance

* Due to the presence of center-taped transformer
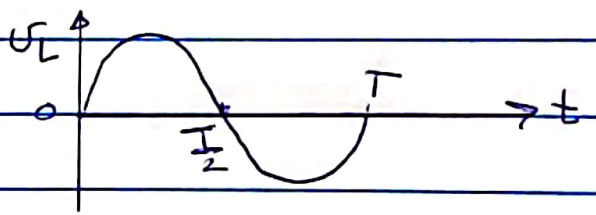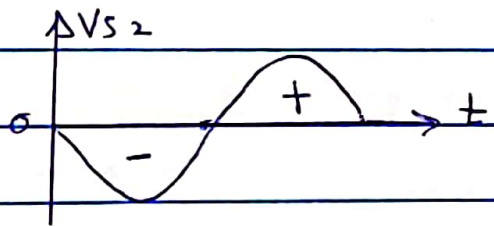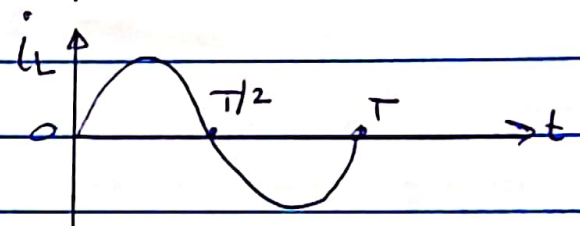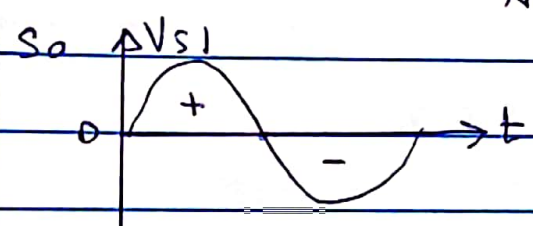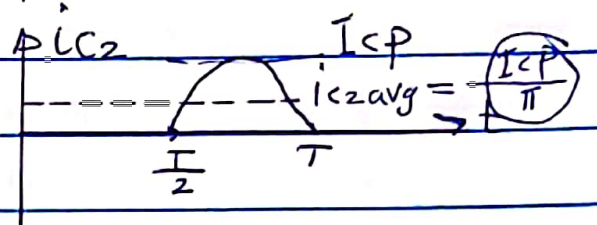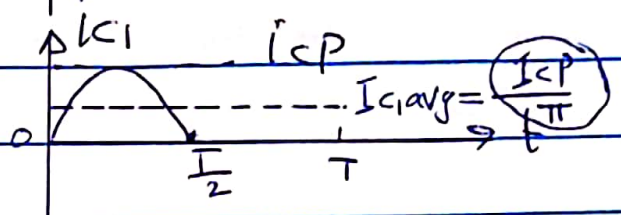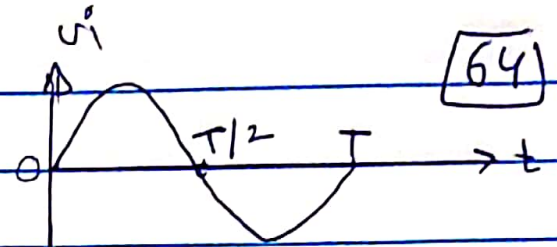
$$T_1:2 \quad V_{s2} = -V_{s1} = \frac{N_2}{N_1} V_i$$



① During +ve H.c of V_i , V_{s1} is +ve, Q_1 is ON, $Q_2 \rightarrow$ OFF (V_{s2} is -ve). i_{c1} will flow in through + V_{cc} and Q_1 , $\bar{P}_{s1} = V_{cc} \cdot I_{c1 avg}$


where $I_{cp} = \frac{V_{cp}}{R_L}$, $I_{c1 avg} = \frac{I_{cp}}{\pi}$

$$\bar{P}_{s1} = V_{cc} \cdot \frac{I_{cp}}{\pi}$$

② During -ve H.c of V_i , $V_{s1} \rightarrow$ -ve, $V_{s2} \rightarrow$ +ve
 So $Q_1 \rightarrow$ OFF, $Q_2 \rightarrow$ ON, i_{c2} will flow in V_{cc} and Q_2 . $\bar{P}_{s2} = V_{cc} \cdot I_{c2 avg} = \frac{I_{cp}}{\pi} V_{cc}$

③ During a Full-Cycle of V_i , \bar{P}_s average drawn from V_{cc} is: $\bar{P}_s = \bar{P}_{s1} + \bar{P}_{s2} = 2V_{cc} \cdot \frac{I_{cp}}{\pi}$

D.C. & A.C. Load line:

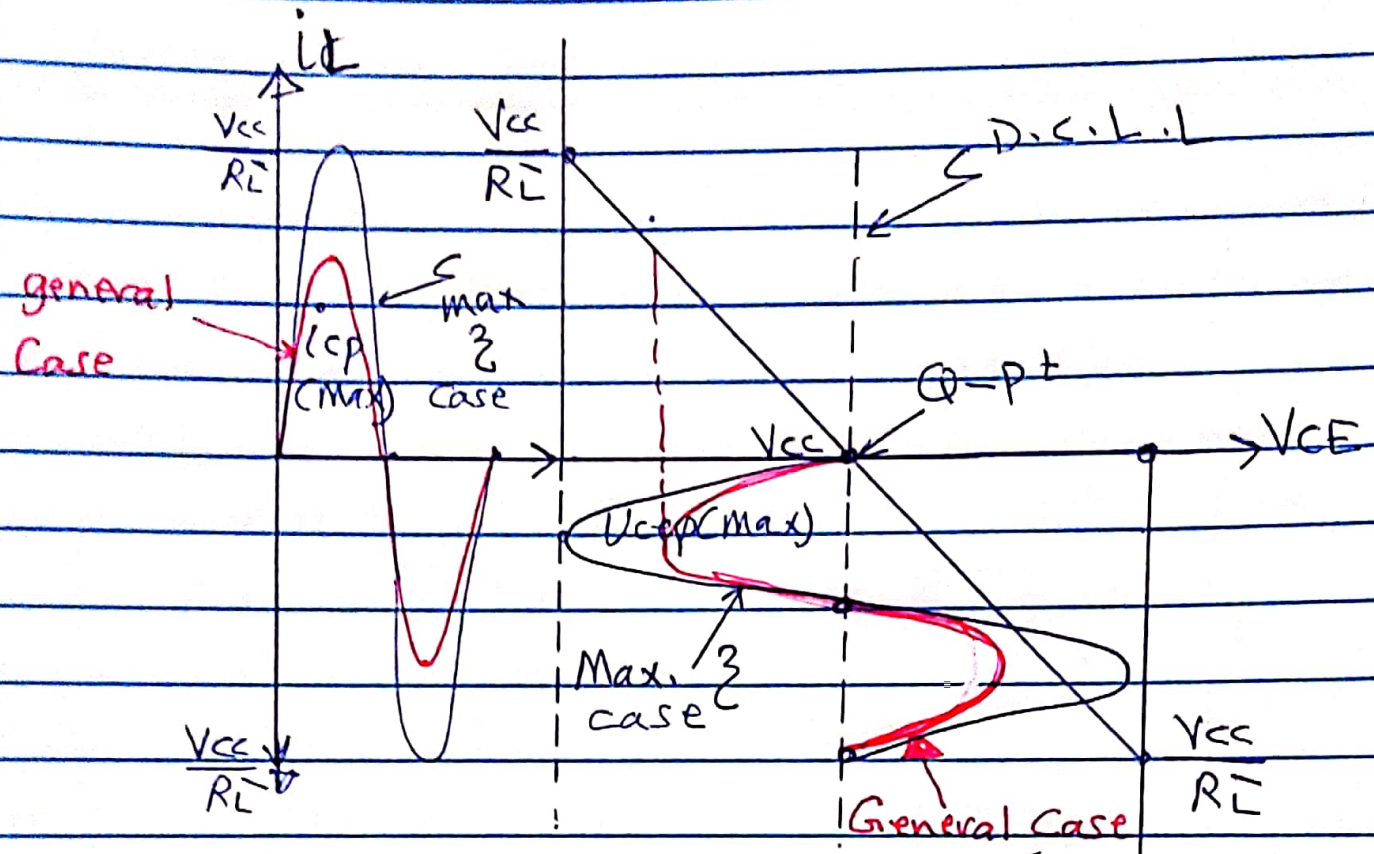

For Max. ζ , $V_{cep} = V_{cc} \Rightarrow \bar{P}_s = 2V_{cc} \frac{I_{cP}}{\pi}$

$I_{cP} = \frac{V_{cc}}{R_L} \Rightarrow \bar{P}_s = \frac{2V_{cc}^2}{R_L \pi}$

$\bar{P}_L = \frac{V_{cep}^2}{2R_L} = \frac{V_{cc}^2}{2R_L} \Rightarrow \bar{P}_L(max) = \frac{V_{cc}^2}{2R_L}$

$\zeta_{max} = \frac{P_L(max)}{\bar{P}_s} = \frac{\frac{V_{cc}^2}{2R_L} \times \pi R_L}{2V_{cc}^2} = \frac{\pi}{4} \times 100\%$

$\zeta_{max} = 78.5\% \text{ [when } V_{cep} = V_{cc}]$

$P_D \text{ For each transistor} = \frac{\bar{P}_s - \bar{P}_L}{2}$

$P_D \approx 0.2 \bar{P}_L(max) \text{ For each transistor.}$

Complementary class B push-pull power Amp.

Both input and o/p transformers can be eliminated using complementary transistors (PNP & NPN) or (n-channel & P-channel). The ckt. is shown in in Fig.

① For +ve H.c of V_i , $Q_1 \rightarrow ON$, $Q_2 \rightarrow OFF$


i_{cn} flow in R_L (assume $i_c \approx i_e$)

$V_L = i_{cn} R_L$ with polarity $+V_L -$



② For -ve H.c of V_i

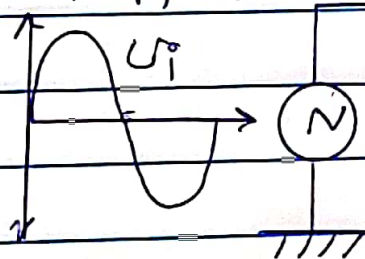
$Q_1 \rightarrow OFF$, $Q_2 \rightarrow ON$



i_{cp} will flow in R_L causing V_L with polarity $V_L +$

③ For a full cycle of V_i , $i_L = i_{cn} + (-i_{cp})$

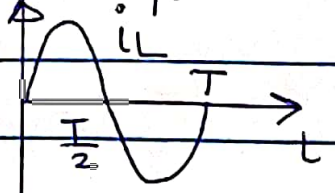
$\therefore i_L = i_{cn} - i_{cp}$ will be of the form



V_L will be of the same form

of i_L i.e. V_L and i_L are in phase

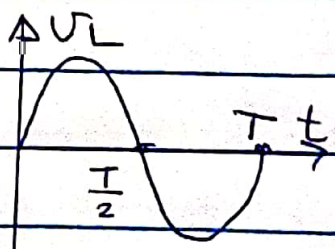* Note that V_L & V_i are in phase because the ckt. is Common Collector



$V_o \approx V_i = V_L$

* When Q_1 is ON, $P_s \oplus = V_{cc} \cdot I_{cn}(\text{avg})$

$$I_{cn}(\text{avg}) = \frac{I_{cp}}{\pi}, \quad I_{cp} = I_{ep} = \frac{V_{LP}}{R_L}$$

* When Qp is on, we draw $\bar{P}_S \ominus = -V_{CC} (I_{CP(avg)})$


$$I_{CP(avg)} = \frac{I_{CP(peak)}}{\pi} \Rightarrow I_{CP(peak)} = \frac{V_{LP}}{R_L}$$

$$\text{So } \bar{P}_S \ominus = +V_{CC} \frac{I_{CP(peak)}}{\pi}$$

For Full cycle of V_i : $\bar{P}_S = \bar{P}_S + +\bar{P}_S \ominus = \frac{2I_{CP(peak)} V_{CC}}{\pi}$

Since V_L is a complete cycle.
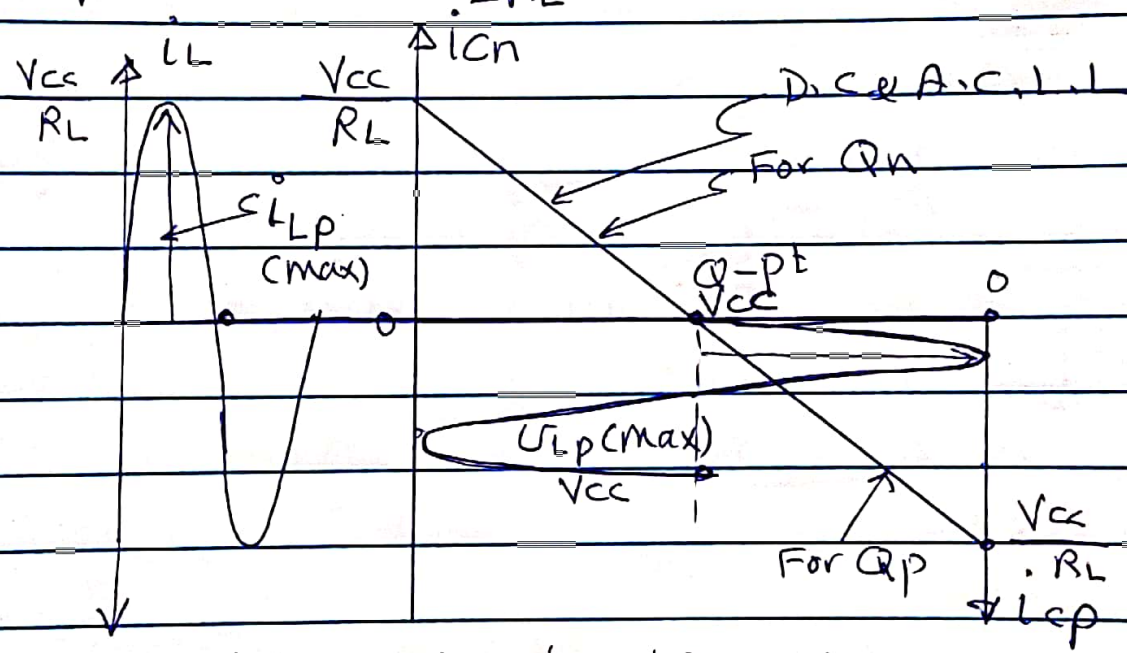
$$\bar{P}_L = \frac{(V_{L(peak)})^2}{R_L} = \frac{V_{L(peak)}^2}{2R_L}$$



$\bar{P}_L(max)$ is obtained when $V_{LP} = V_{CC}$

$$\text{or } \bar{P}_L(max) = \frac{V_{CC}^2}{2R_L}$$

and since $\bar{P}_S = \frac{2V_{CC} I_{CP(peak)}}{\pi}$, $I_{CP(peak)} = \frac{V_{CC}}{R_L}$

$$\text{or } \bar{P}_S = \frac{2V_{CC} V_{CC}}{\pi R_L} = \frac{2V_{CC}^2}{\pi R_L}$$

$$\text{or } \zeta_{max} = \frac{\bar{P}_L(max)}{\bar{P}_S} = \frac{V_{CC}^2}{2R_L} \times \frac{\pi R_L}{2V_{CC}^2} = \frac{\pi}{4} \times 100\%$$

$$\text{or } \zeta_{max} = 78.5\% \quad [\text{When } V_{LP} = V_{CC} \text{ and } V_{ip} = V_{LP} = V_{CC}]$$

In general $\zeta = \frac{V_{LP}}{V_{CC}} \times \frac{\pi}{4} \% \quad [\text{Valid For both type}]$

When $V_{LP} = V_{CC} \rightarrow \xi = \xi_{max} = \frac{\pi}{4} \times 100\% = 78.5\%$

*NOTE: This ckt. is emitter follower, so

$V_L = V_i$ ***

68

EXA: A class-B output stage with complementary transistors is biased with $V_{CC} = \pm 6V$ and deliver 3W to 4Ω load. calculate:

- 1) peak input voltage, \bar{P}_s , ξ , P_D (each tr.)
- 2) sketch D.C. & A.C. L.L. with V_{CE} & i_C swings.
- 3) What is the peak input voltage required to give ξ_{max}

① $\bar{P}_L = \frac{V_{LP}^2}{2R_L}$

$V_{LP} = \sqrt{2\bar{P}_L R_L} = \sqrt{2 \times 3 \times 4}$

$V_{LP} = 4.9V$

and since $A_v \approx 1$ (c.c.), $V_i \approx V_{LP} = 4.9V$


$\bar{P}_s = \frac{2\bar{I}_{CP}}{\pi} \times V_{CC}$, $\bar{I}_{CP} = I_{LP} = \frac{V_{LP}}{R_L} = \frac{4.9}{4} = 1.225A$

$\bar{P}_s = \frac{2 \times 1.225}{\pi} \times 6 = 4.68W$

$\xi = \frac{\bar{P}_L}{\bar{P}_s} \times 100\% = \frac{3}{4.68} \times 100\% = 64.1\%$


$P_D(\text{each}) = \frac{\bar{P}_s - \bar{P}_L}{2} = \frac{4.68 - 3}{2} = 0.84W$

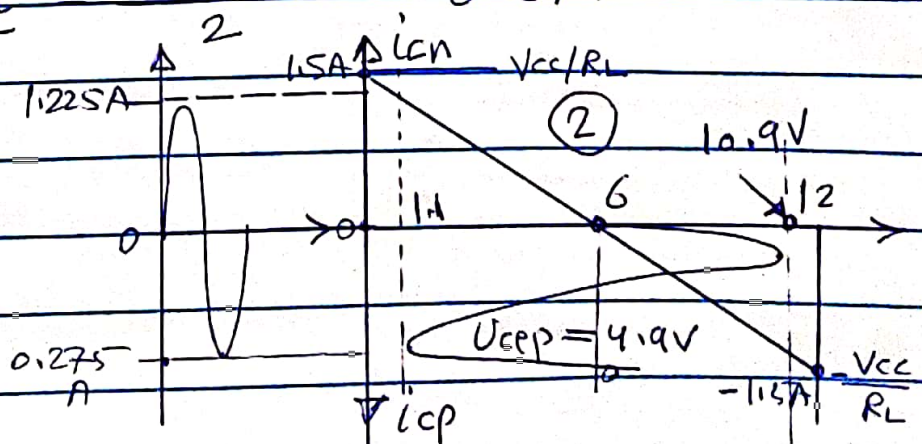- ③ For ξ_{max}
 $V_{LP} = V_{CC} = 6V$
 but $V_{ip} = 2V_{LP}$
 $\therefore V_{ip} = 6V$




Distortion in power Amplifiers

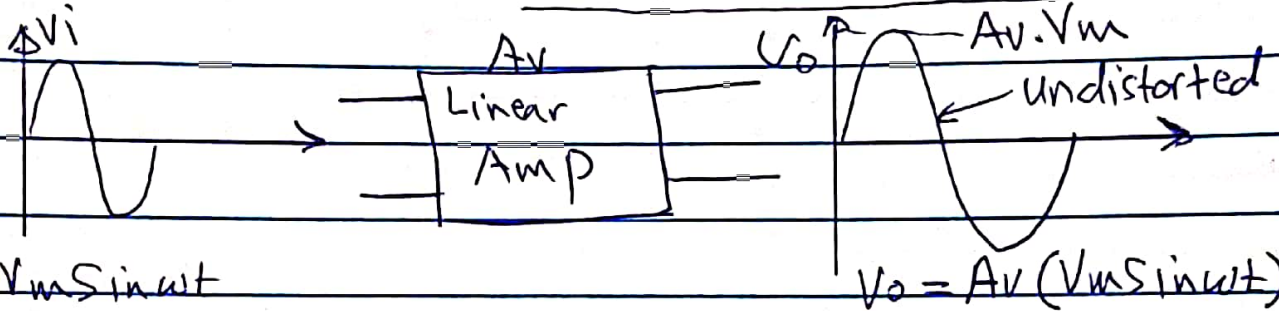Distortion: Deformation in the signal due to nonlinear characteristics of the transistor and this is called nonlinear distortion.



$V_i = V_m \sin \omega t$

$V_o = A_v (V_m \sin \omega t)$

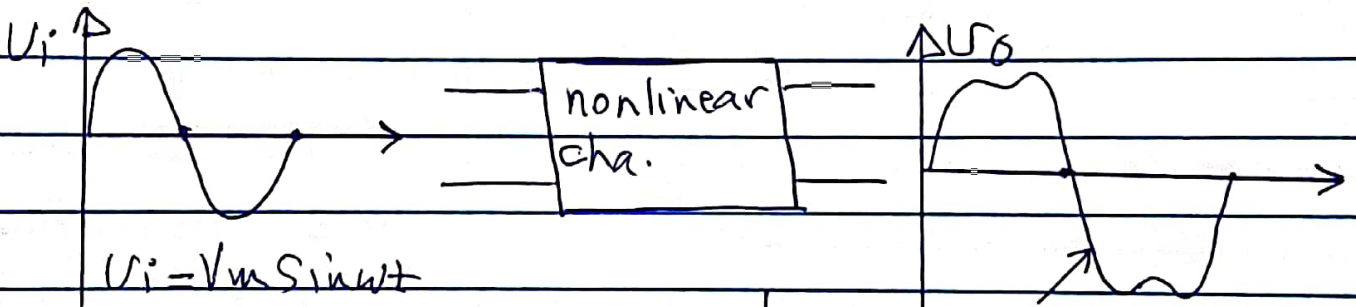

$V_i = V_m \sin \omega t$

distorted signal

For the distorted signal:

$V_o(t) = B_0 + B_1 \sin \omega t$

B_0 : D.C component $f=0$

B_1 : Amplitude of fundamental frequency (ω)

$+ B_2 \sin 2\omega t$ (marked with a red X)

$+ B_3 \sin 3\omega t$ (marked with a red X and 'eqn.')

$+ B_n \sin n\omega t$

B_2 : Amp. of 2nd Harmonics (2ω)

B_3 : = = 3rd Harmonic (3ω)


B_n : = = nth Harmonics ($n\omega$)

$D_2 = \frac{B_2}{B_1}$ (2nd Harmonics distortion)

$D_3 = \frac{B_3}{B_1}$ (3rd = =)

$$D_n = \frac{B_n}{B_1} \text{ (n}^{th} \text{ harmonic distortion)}$$
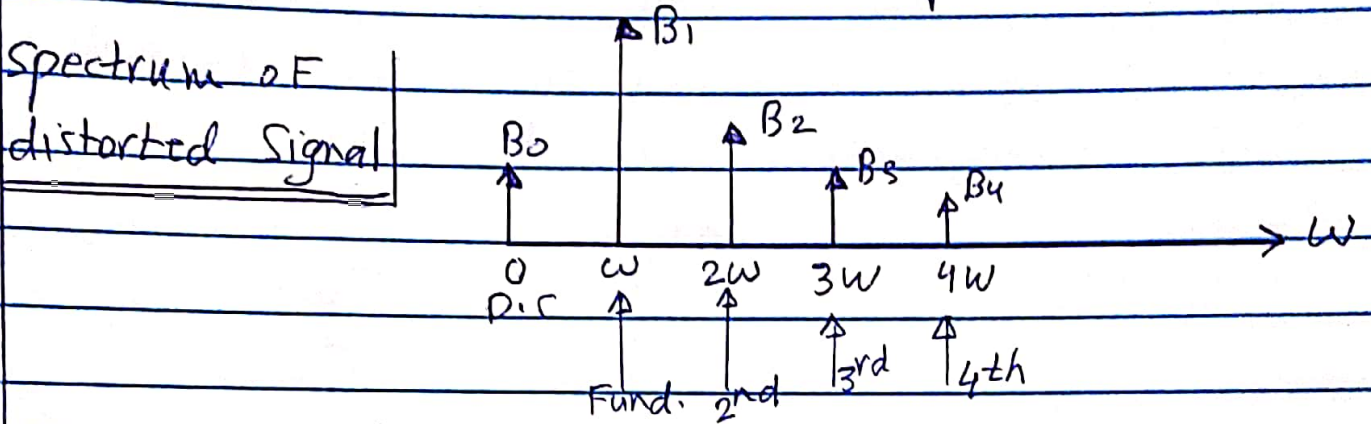
$$\text{Total Harmonic distortion T.H.D} = \sqrt{D_2^2 + D_3^2 + \dots + D_n^2}$$



EXA: The a/p voltage of a certain power is given by:

$$V_o(t) = 2 + 8\sin 2\pi \times 10^3 t + 6\sin 4\pi \times 10^3 t + 2\sin 6\pi \times 10^3 t$$

- 1) calculate 2nd and 3rd Harmonic and T.H.D (V)
- 2) Sketch the Spectrum of V_o .

Compared to eqn. x [general eqn. For distorted signal]


$$B_0 = 2V \text{ (d.c.)}, B_1 = 8V \text{ (Fundamental)}$$

$$B_2 = 6V \text{ (2nd Harmonic)}, B_3 = 2V \text{ (3rd Harmonic)}$$

$$\text{So: } D_2 = \frac{B_2}{B_1} = \frac{6}{8} \times 100\% = 75\%$$


$$D_3 = \frac{B_3}{B_1} = \frac{2}{8} \times 100\% = 25\%$$
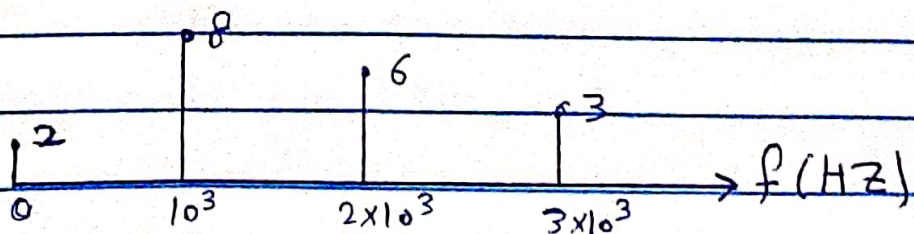
$$\text{T.H.D} = \sqrt{(0.75)^2 + (0.25)^2} = \sqrt{0.625} = 79\%$$



Crossover distortion

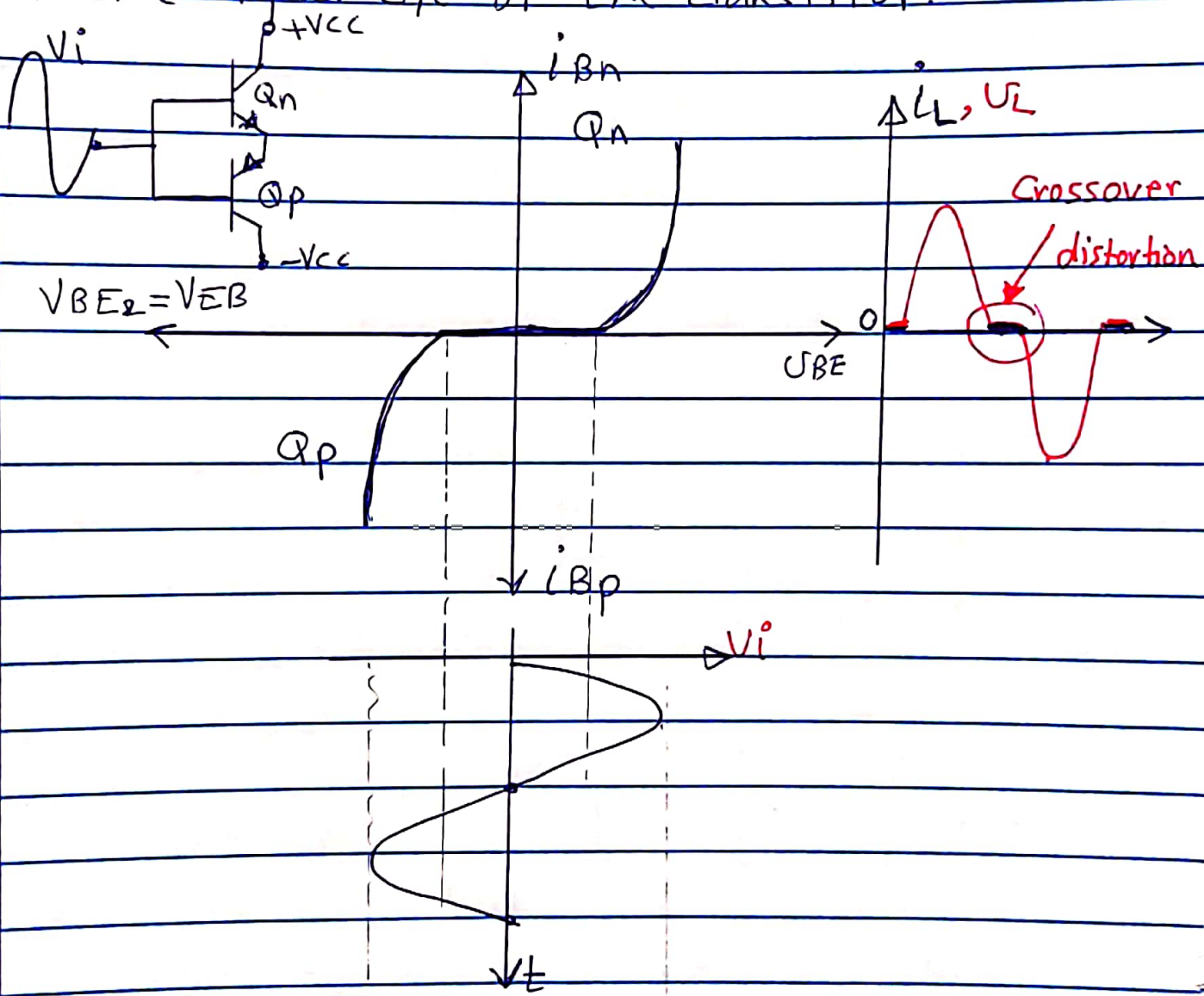This type of distortion happens only in class-B power Amp. because its Q-pt is at Cutoff. It is due to finite voltage V_{BE} of the transistor and causes dead zone on the input c/c of the transistor.



This distortion can be eliminated by cancelling the effect of V_{BE} . This can be achieved by applying a D.C voltage on the bases of transistor equal and opposite to V_{BE} .

This makes ~~class~~ the Amp. biased at $I_{CQ} > 0$

i.e. class AB. practically either using Diode sources or using diode of the same type of the transistors as shown in Figs.


When Q_n is ON in the H.C of V_i

$$V_i - \frac{V_{BB}}{2}, V_{BE_n} + V_o = 0$$

$$V_o = V_i + \frac{V_{BB}}{2} - V_{BE_n}$$

If $\frac{V_{BB}}{2} = V_{BE_n}$, then
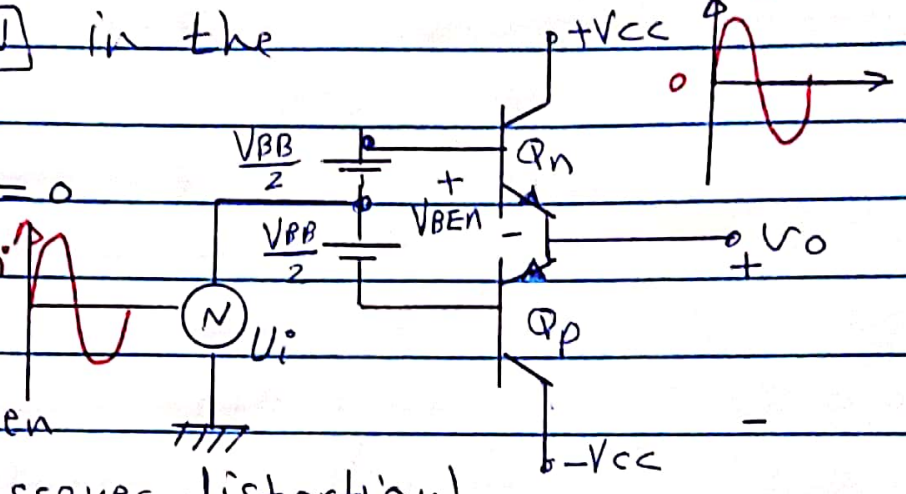
$$V_o = V_i \text{ (No Crossover distortion)}$$



* D_1 & D_2 must be matched

With transistors

$$V_{D1} = V_{D2} = V_{BE_n} = V_{BE_p}$$

* In this modification


$$I_B > 0, I_C > 0$$

i.e. the cct. is

NOT class-B.


It is class-AB but it is

very close to class-B than class-A.

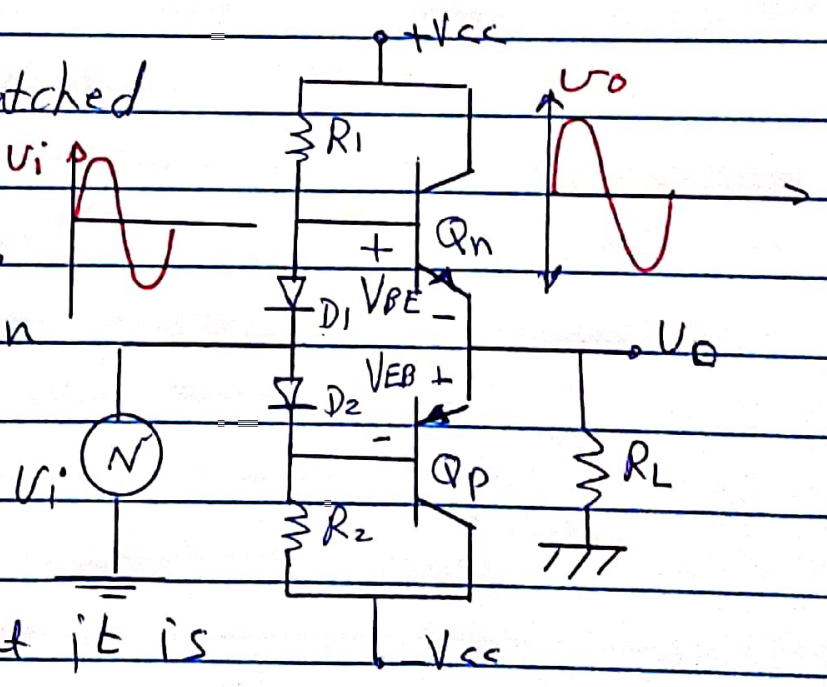


Class-C power Amplifier

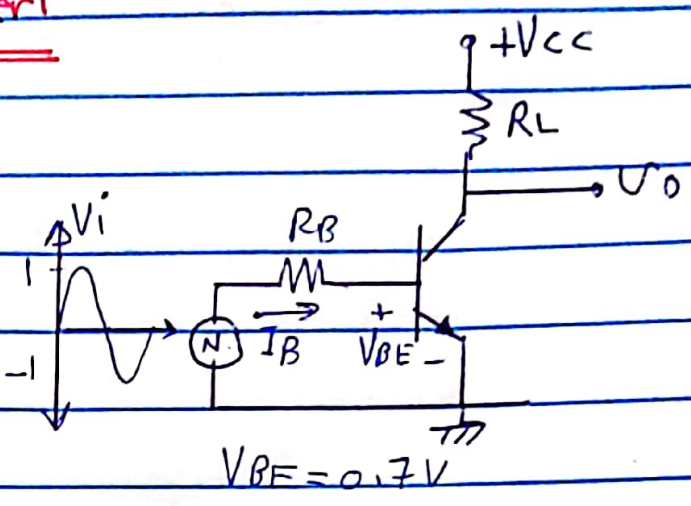1) The Q-pt. is down the Cutoff, i.e. the transistor conducts for $< 180^\circ$ (Small conduction angle normally $< 90^\circ$).







The BJT will be FW in the H.C and $I_B = \frac{V_i - V_{BE}}{R_B}$. I_B is ON when $V_i > V_{BE}$.

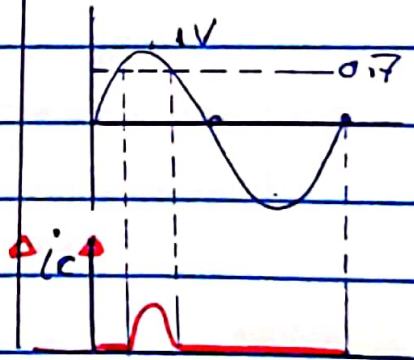2) The o/p current is less than half cycle, i.e. it is distorted signal which is full of harmonics.
 3) practically the load is a parallel tuned ckt. its resonance freq. is the fundamental frequency of the input signal.



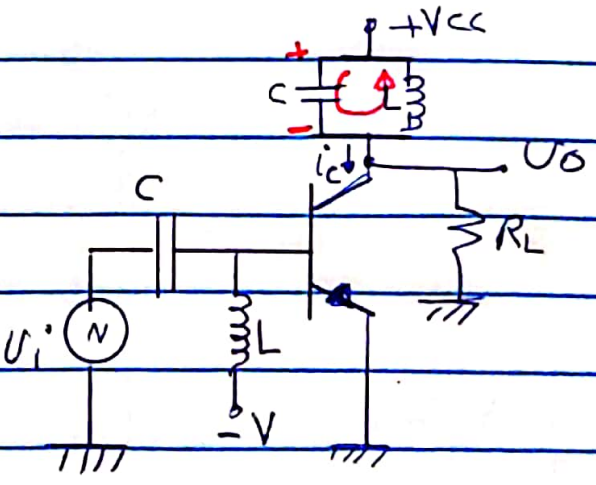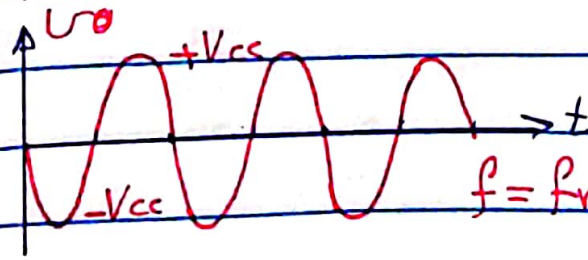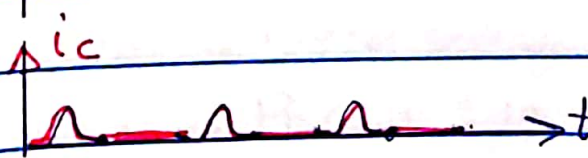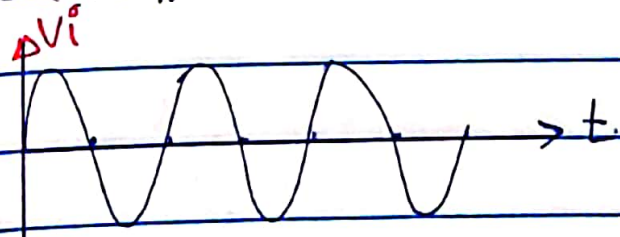* For a periodical V_i , i_c will have the form



$$f = f_r = \frac{1}{2\pi\sqrt{LC}}$$

When the form of i_c is a pulse form, the parallel tuned cct. has a characteristic called "flywheel effect" which is when it is excited by a pulse current, it will oscillate and give a sinusoidal o/p signal at resonant freq $f_r = \frac{1}{2\pi\sqrt{LC}}$ with amplitude $\approx V_{cc}$. "due to charging and discharging of the capacitor).

For a certain load, the average load power \bar{P}_L is given by $\bar{P}_L = \frac{V_{cc}^2}{2R_{eff}}$

where R_{eff} : parallel combination of R_L and parallel tuned cct resistance.

* In class C, the transistor works as switch "ON & OFF" (Saturation & Cutoff)

when it is ON: (Saturation: $I_c = I_c(sat)$
 $V_{CE} = V_{CE}(sat)$)

when it is OFF [$I_c = 0, V_{CE} = V_{cc}$]


When transistor is in Sat.

$$P_{D(ON)} = I_c(sat) V_{CE}(sat)$$

$$P_{D(avg)} = P_{D(ON)} \frac{t_{on}}{T}$$


$$\bar{P}_s = \bar{P}_L + P_{D(avg)}$$
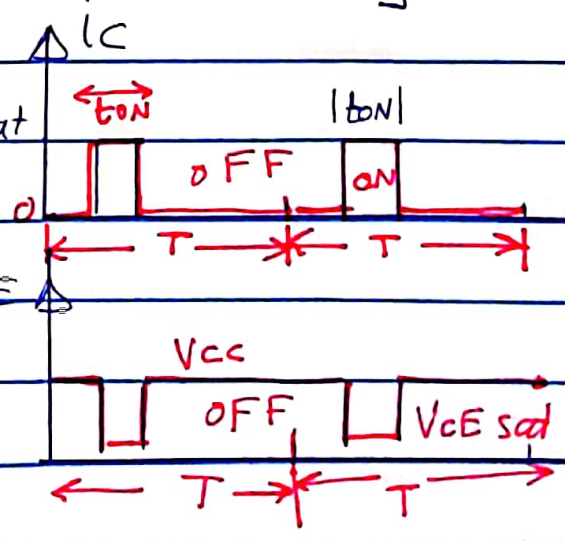
$$\eta = \frac{\bar{P}_L}{\bar{P}_s} \times 100\%$$



EXA: A class-C power Amplifier has an input of $f = 100\text{kHz}$, the BJT has $V_{CE(sat)} = 0.3\text{V}$ and $I_C(sat) = 0.2\text{A}$ and its on For $\approx 2\mu\text{s}$. If $V_{CC} = 20\text{V}$, the effective Resistance is 50Ω

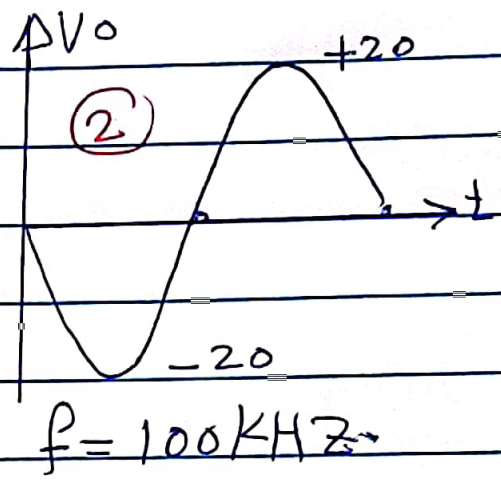- 1) calculate \bar{P}_L , \bar{P}_S and $\eta\%$.
- 2) Sketch $V_o(t)$.
- 3) Calculate L, C required (Give design the tuned cct. required to process the input signal).



$$\textcircled{1} \quad \bar{P}_L = \frac{V_{CC}^2}{2R_{EFF}} = \frac{400}{2 \times 50} = 4\text{W}$$

$$\bar{P}_S = \bar{P}_L + P_{D(avg)}$$

$$P_{D(avg)} = P_{D(on)} \frac{t_{on}}{T} = I_C(sat) \cdot V_{CE(sat)} \frac{t_{on}}{T}$$

$$T = \frac{1}{f} = \frac{1}{10^5} = 10\mu\text{s}$$

$$P_{D(avg)} = 0.2 \times 0.3 \frac{2}{10} = 0.012\text{W}$$

$$\bar{P}_S = 4 + 0.012 = 4.012\text{W}$$

$$\eta = \frac{4}{4.012} \times 100\% = 99.7\%$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

let $C = 1\text{pF}$

$$L = \frac{1}{4\pi^2 f_r^2 C}$$


$$= \frac{1}{4 \times 10 \times 10^{10} \times 10^{-12}}$$

$$= 2.5\text{H}$$

Active Filters:

Filter: It is a selective circuit allows a certain band of frequency to pass and this band is called passband and reject other band which is called stopband or reject band.

It must contain freq.

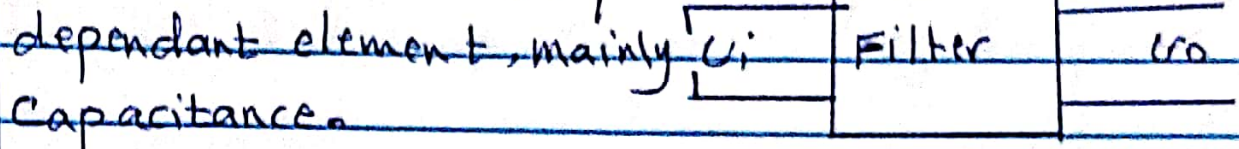


Filters are classified into: passive Filters and Active Filters. A comparison between them is presented in the following table

<u>Passive Filter</u>	<u>Active Filter</u>
1) Contains only passive elements (R, C, L)	1) Contain passive and active element (R, C, L) + BJT, MOSFET or Op-Amp
2) No power supply is needed (No P _D on device) "No power consumption"	2) D.C power supply is required to bias the active devices, power consumption happen.
3) No Amplification "No gain is achieved"	3) Gain is achievable due to Active device
4) Can't be integrable So it is NOT compatible with modern electronics systems.	4) Can be made as an IC "Integrated cct" So it can be compatible with modern electronic system.

Filter Classification According to passband:

They are classified into:

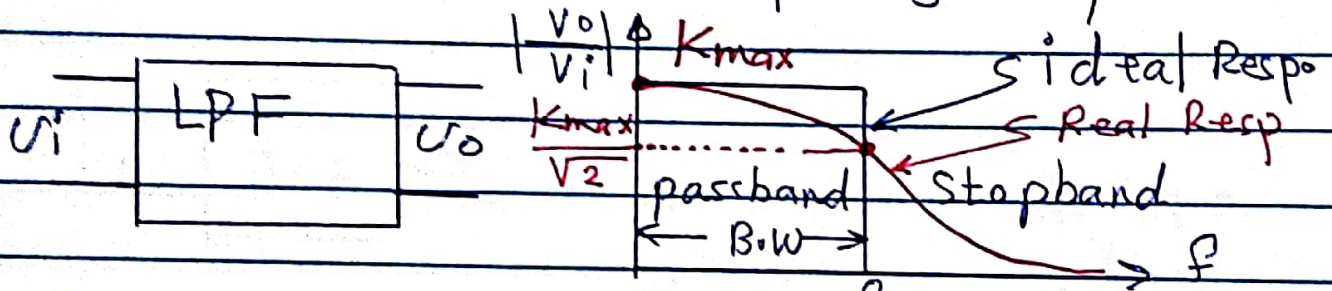1) Low pass Filter (LPF): This type allows low freq. band to pass [its bandwidth extends from $(0 \rightarrow f_c)$ where f_c is called Cutoff freq and rejects frequencies above f_c as show in its frequency Response




* For passive Filters, $K_{max} = 1$

* Active $\leftarrow K_{max} > 1 \rightarrow$


* f_c : Cutoff frequency: the frequency at which the value of $|V_o/V_i|$ drops to $0.707 K_{max} = \frac{K_{max}}{\sqrt{2}}$

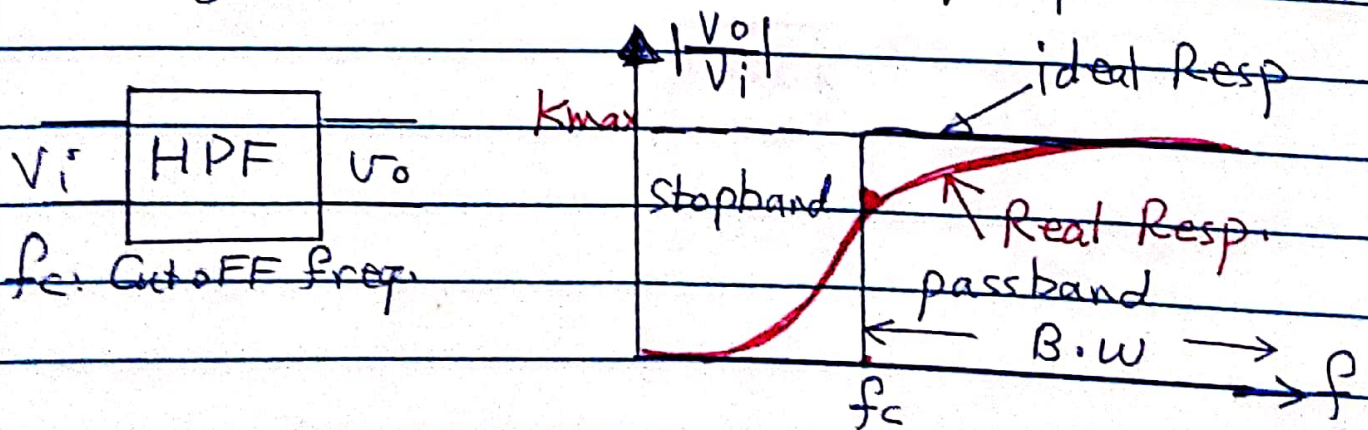2) High-pass Filters (HPF). This type allows high freq. band to pass [its bandwidth extends from $(f_c \rightarrow \infty)$ where f_c is called Cutoff freq] and rejects other bands. its freq. Resp is shown



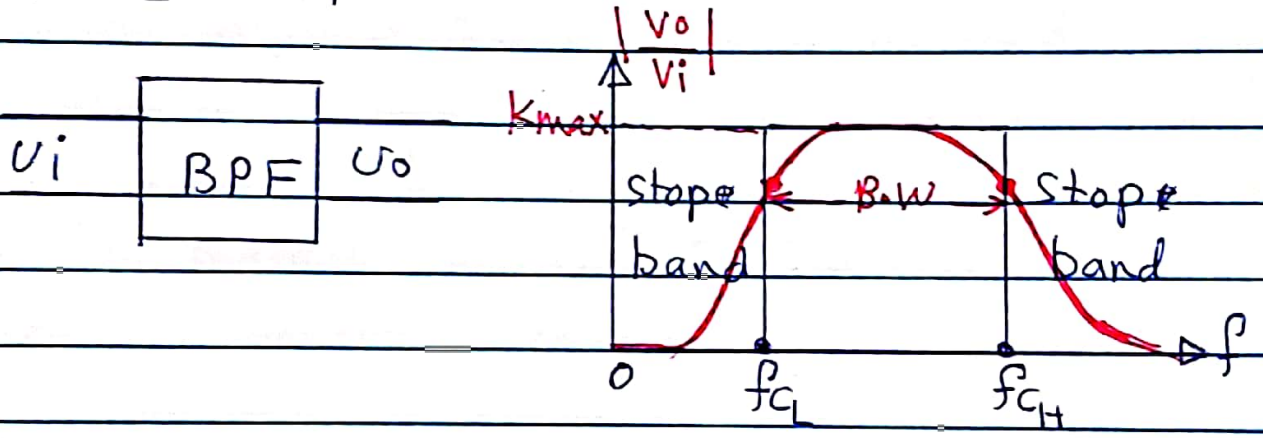
3) Bandpass Filter (BPF)

This type allows a certain band of freq to pass extending from $(f_{CL} \rightarrow \text{to } f_{CH})$ over a bandwidth of $B.W = f_{CH} - f_{CL}$ where $f_{CL} \rightarrow$ low cutoff freq and $f_{CH} \rightarrow$ high cutoff freq. and reject frequencies band $(0 \rightarrow f_{CL})$ and $f_{CH} \rightarrow \infty$ as shown in the frequency response shown.



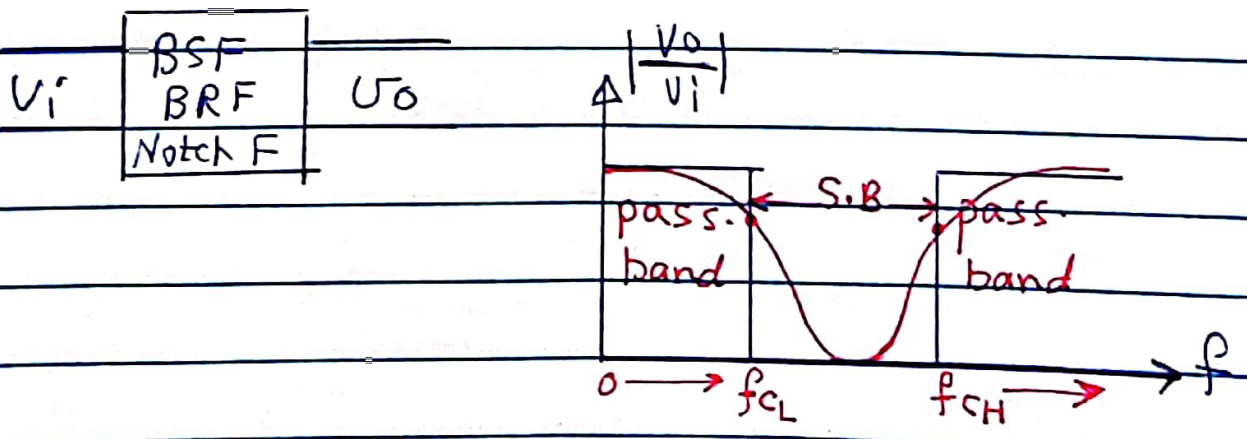4) Bandstop or Bandreject Filter "BSF" or "BRF"

This type rejects a certain bands of frequency $(f_{CL} \rightarrow f_{CH})$ and allows $(0 \rightarrow f_{CL})$ and $(f_{CH} \rightarrow \infty)$ over a bandwidth (from $0 \rightarrow f_{CL}$ and $f_{CH} \rightarrow \infty$) This also called "Notch Filter"



Filter Transfer Function:

It represents the ratio of $\frac{V_o(s)}{V_i(s)} = H(s) = \frac{N(s)}{D(s)}$

Filter Order: : The highest power of (s) in the denominator $D(s)$, i.e. $D(s)$ indicate Filter order.

* If the highest power is ① Such as $H(s) = \frac{5}{s+2}$ it is 1st order.

* If the highest power is ② Such that: $H(s) = \frac{5}{s^2+2s+1}$ it is 2nd order.

* If the highest power is ③ Such that: $H(s) = \frac{4}{s^3+2s^2+0.5s+1}$ it is 3rd order

* If it is: $H(s) = \frac{k}{s^n + s^{n-1} + s^{n-2} + \dots + 1}$ it is nth order

* $N(s)$ indicate type of Filter:

1) If $N(s) = \text{Constant } (k_0) \rightarrow N(s) = 5 \rightarrow$ LPF

2) $= k \cdot s \rightarrow 4s \rightarrow N(s) = 5s \rightarrow$ BPF

3) $= k_1 s^2 + k_2 \rightarrow N(s) = 2s^2 + 3 \rightarrow$ BSF

4) $= k s^2 \rightarrow N(s) = 4s^2 \rightarrow$ HPP

Ex: Name type and order of the following T.F

1) $H(s) = \frac{2}{s+3} \rightarrow$ 1st order LPF

2) $H(s) = \frac{4s}{s^2+2s+1} \rightarrow$ 2nd order BPF

3) $H(s) = \frac{2s^2}{s^2+2s+1} \rightarrow$ 2nd order HPF

4) $H(s) = \frac{5s^2+3}{s^3+2s^2+s+1} \rightarrow$ 3rd order BSF

First Order Filters




These Filters have one (S) in the D(s) of the transfer function and since each (S) represent single Capacitor ($X_C = \frac{1}{j\omega C} = \frac{1}{sC}$). they contain single Capacitor

1) Passive Filter representation:

They are consisting of (R and C) and as follow:

a) Low-pass filter:

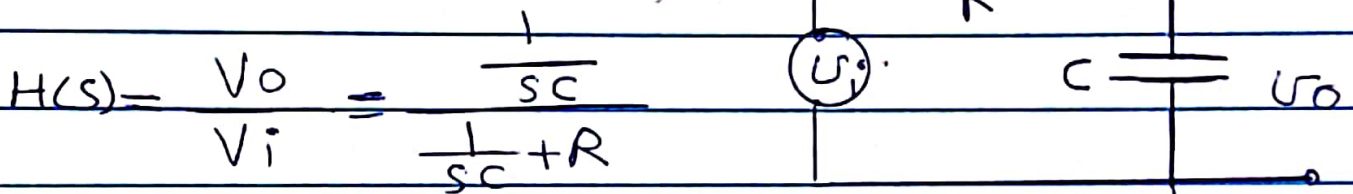

$$H(s) = \frac{V_o}{V_i} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R}$$

$$H(s) = \frac{1}{1 + sRC} \rightarrow |H(s)| = \frac{1}{1 + (\omega RC)}$$


Compare to: $H(s) = \frac{K_{max}}{1 + |sRC|}$ to find f_c , then

$$K_{max} |H(s)| = \frac{|V_o|}{|V_i|} = \frac{K_{max}}{\sqrt{2}}$$

this will happen when, $|sRC| = 1$

$$\text{or } |\omega_c RC| = 1 \Rightarrow |2\pi f_c RC| = 1$$
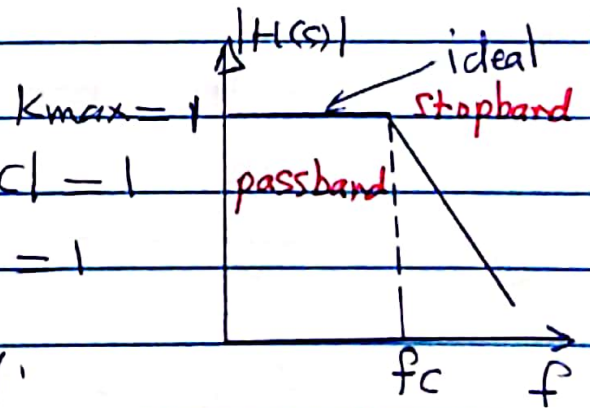
$$\text{or } \left[f_c = \frac{1}{2\pi RC} \right] \text{ Cutoff freq.}$$




b) high-pass filter:

to obtain high-pass Filter

Use $C \rightarrow R$ and $R \rightarrow C$

transformation the ckt.

is shown in Fig.

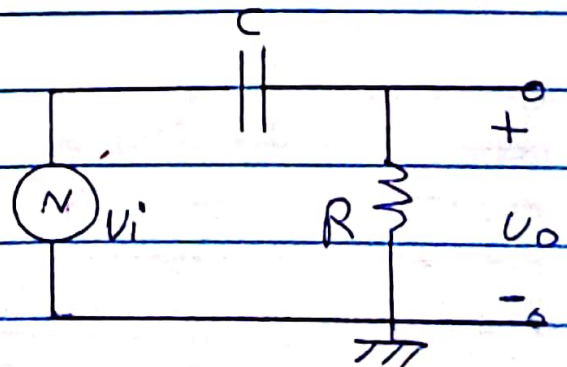


$$H(s) = \frac{V_o}{V_i} = \frac{R}{R + \frac{1}{sC}} = \frac{1}{1 + \frac{1}{sRC}} = \frac{1}{1 + \frac{1}{j\omega RC}}$$

$$H(s) = \frac{K_{max}}{1 + \frac{1}{j\omega RC}}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{K_{max}}{1 + \left| \frac{1}{\omega RC} \right|}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{K_{max}}{\sqrt{2}} \text{ when } \frac{1}{\omega RC} = 1$$

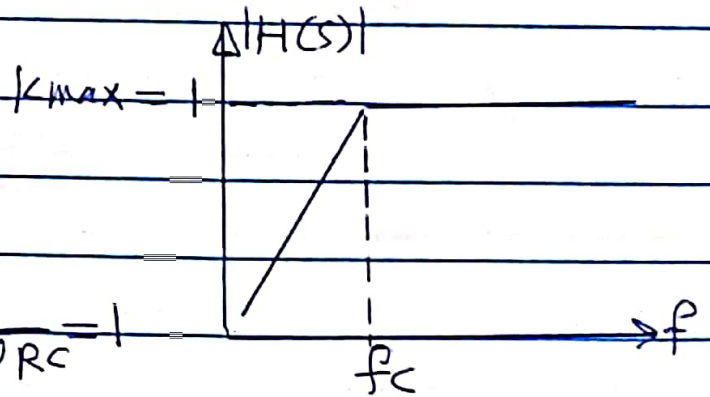

i.e. when $\omega = \frac{1}{RC} \Rightarrow \omega_c$

$$\therefore f_c = \frac{1}{2\pi RC} \text{ (Cutoff Freq.)}$$


2) Active Filter Representation.

a) Low-pass Filter

$$f_c = \frac{1}{2\pi RC}$$

and $K_{max} = 1$

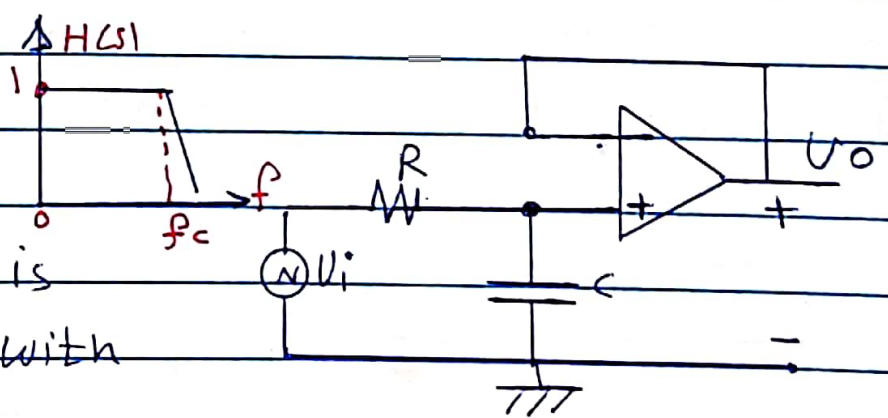because the ckt. is voltage follower with $A_v = 1$




To have a gain, we can use the op Amp. as noninverting Amp. as shown


$$\text{in this case } H(s) = \frac{\left(1 + \frac{R_2}{R_1}\right)}{1 + j\omega RC}$$

$$f_c = \frac{1}{2\pi RC}$$

$$K_{max} = 1 + \frac{R_2}{R_1}$$

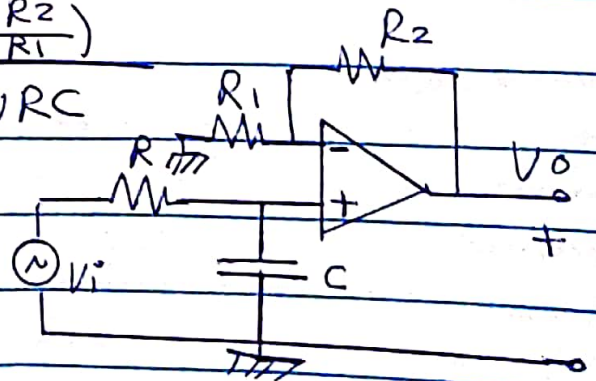

In this case the Response will be:

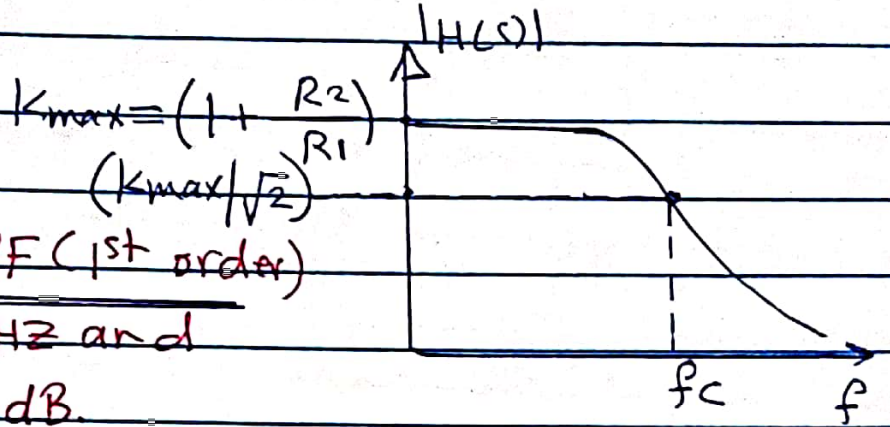

Ex A1 Design a LPF (1st order)

to have $f_c = 2\text{KHz}$ and

a Max. gain = 20dB.

1) Calculate R_1, R_2, R, C . 2) Sketch the Bode Plots.

$$f_c = \frac{1}{2\pi RC} = 2\text{KHz}, \text{ choose } C = 0.1\mu\text{F}$$

$$\therefore R = \frac{1}{2\pi C f_c} = \frac{1}{2\pi \times 1 \times 10^{-7} \times 2 \times 10^3} = \frac{10^4}{4\pi}$$


$$\therefore R = 795.8 \Omega$$

$$k_{max} = 20\text{dB} = 20 \log \left| \frac{V_o}{V_i} \right| \Rightarrow \log \left| \frac{V_o}{V_i} \right| = \frac{20}{20} = 1$$

$$\therefore \left| \frac{V_o}{V_i} \right| = 10^1 = 10 = 1 + \frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = 9$$

$$\therefore R_2 = 9R_1 \Rightarrow \text{let } R_1 = 1\text{K}\Omega$$
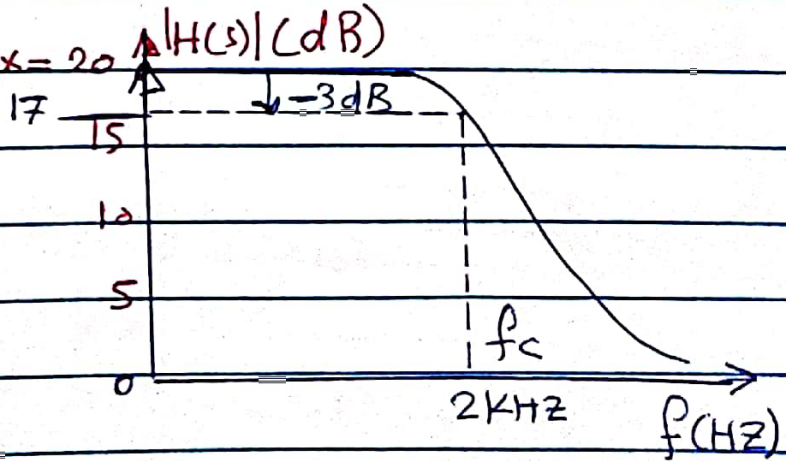
$$\therefore R_2 = 9\text{K}\Omega \quad k_{max} = 20$$




Bode Plots or "Frequency Response"

b) High-pass filters

$$f_c = \frac{1}{2\pi RC}$$

$$K_{max} = 1$$

Since $A_v = 1$

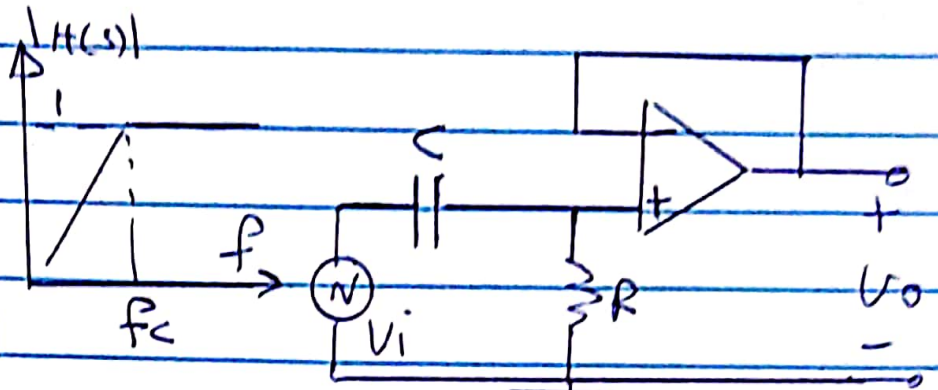

* To have a gain, we must use the Op-Amp. as Noninverting Amp. as shown



where: $f_c = \frac{1}{2\pi RC}$

but the max. gain

will be $K_{max} = (1 + \frac{R_2}{R_1})$

and the transfer function
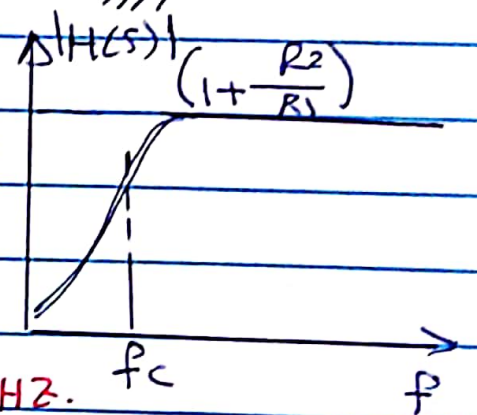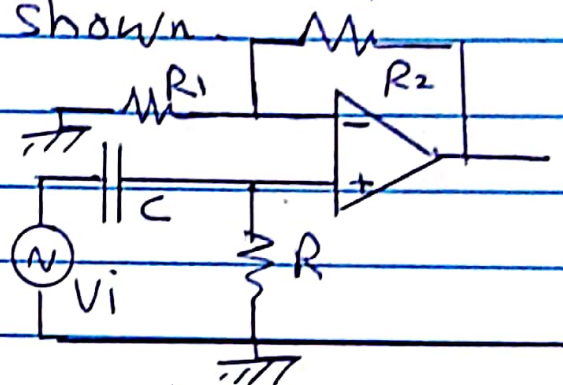
$$H(s) = \frac{(1 + \frac{R_2}{R_1})}{1 + \frac{1}{sRC}}$$



EXA: Design a 1st order HPF

to have $A_v = |H(s)| = 20, f_c = 5\text{KHz}$.

~~R/A~~ $f_c = \frac{1}{2\pi RC} = 5\text{KHz}$, let $C = 0.01\mu\text{F}$

$$\therefore R = \frac{1}{2\pi C f_c} = \frac{1}{2\pi \times 10^{-8} \times 5 \times 10^3} = \frac{10^4}{\pi}$$


$$\therefore R = 3.183\text{K}\Omega$$

$$|H(s)| = 20 = 1 + \frac{R_2}{R_1}, \frac{R_2}{R_1} = 19$$

let $R_1 = 1\text{K}\Omega$ $\therefore R_2 = 19\text{K}\Omega$

2nd Order Filters

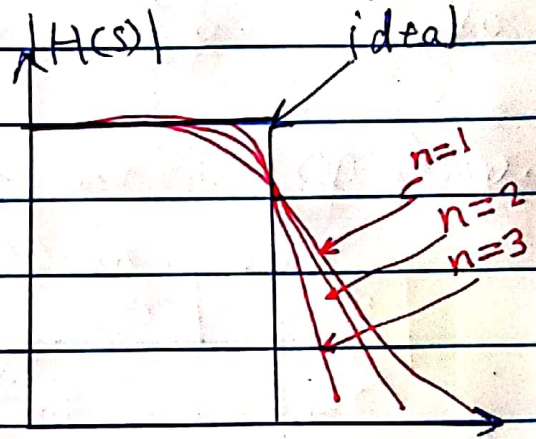These filters have a sharper (steep sided) response compared to 1st order. In general as filter order increase, the response will be sharper. For example, look the response shown for a LPF with different order.



* As filter order increase the response will be closer to ideal response.


* n : Filter order.

* The basic building block is the 2nd order filter.


* High-order active filters can be obtained:

(i) by cascading 2nd order filters and 1st order filters where:

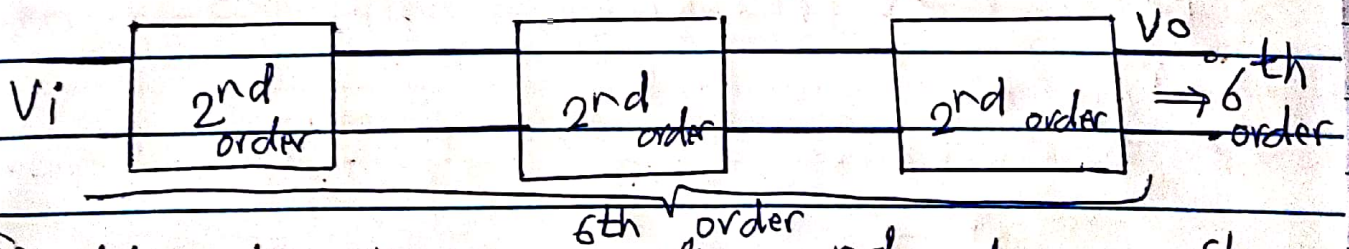(i) Even-order filters: by cascading 2nd order only. For example 6th order, using three 2nd order filter in cascade.



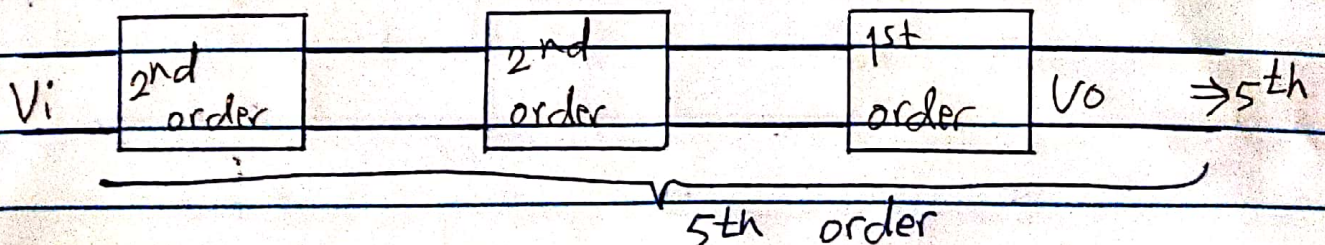(ii) odd order filters: cascading 2nd order and 1st order. For example: 5th order



* In cascading, we require many (Large No of) op-Amp.


② Using different well-known configurations such as:

- (i) Multiple-loop -ve FFB configuration: MLNFB.
- (ii) Follow the leader configuration: "FL"
- (iii) Leap-Froge configuration.

* In this technique, we require less No of passive and Active elements.

* For example to realize 2nd order LPF with a certain gain:


: Using cascading technique.

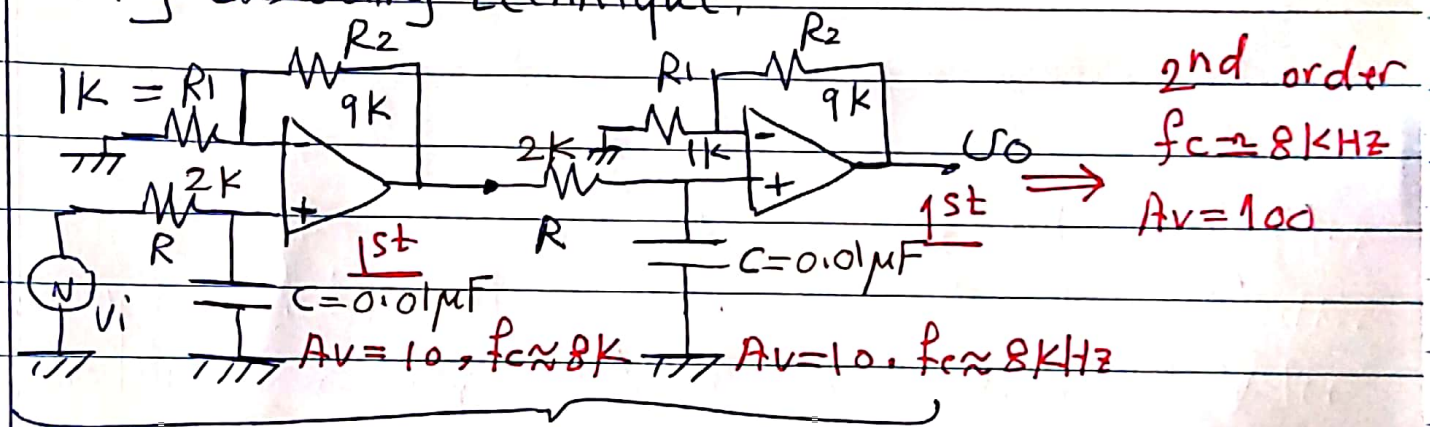

* It is required to use: 2-op-Amp, 2 Cap, 6 Resistors

2nd order using Multiple-loop configuration

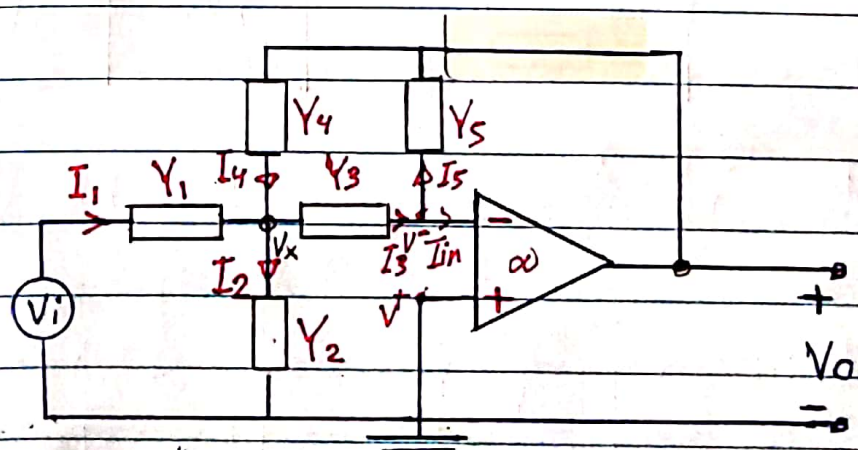General 2nd Filter using MLNFB configurations



* This ckt. can realize 2nd order LPF, HPF or BPF by the proper choice of the Components "Y"

"ideal Op-Amp" $A_o = \infty$, $I_{in} = 0$, $V^+ = V^- = 0$

We can derive an expression for the transfer function $H(s) = \frac{V_o}{V_i}$ by writing KCL at node \oplus

$$I_1 + I_4 = I_2 + I_3$$

$$(V_i - V_x)Y_1 + (V_o - V_x)Y_4 = V_x Y_2 + (V_x - V^-)Y_3 \quad \text{--- (1)}$$

at node \ominus KCL yields:

$$I_3 = I_{in} + I_5 \quad \text{--- (2)} \Rightarrow Y_3(V_x - V^-) = I_{in} + (V^- - V_o)Y_5$$

but $I_{in} = 0, V^- = V^+ = 0$ (ideal op-amp).

$$V_i Y_1 - V_x(Y_1 + Y_2 + Y_3 + Y_4) + V_o Y_4 = 0 \quad \text{--- (1)}$$

$$Y_3 V_x = -V_o Y_5 \quad \text{--- (2)}$$

$$\therefore V_x = \frac{-V_o Y_5}{Y_3} \quad \text{--- (3)}$$

Sub. (3) in (1) yields:

$$V_i Y_1 + \left[\frac{Y_5}{Y_3} (Y_1 + Y_2 + Y_3 + Y_4) + Y_4 \right] V_o = 0$$

$$V_o \left[\frac{Y_5}{Y_3} (Y_1 + Y_2 + Y_3 + Y_4) + Y_4 \right] = -Y_1 Y_3 V_i$$

$$\therefore \frac{V_o}{V_i} = H(s) = \frac{-Y_1 Y_3}{Y_5 (Y_1 + Y_2 + Y_3 + Y_4) + Y_3 Y_4} \quad \text{--- (X)}$$

① To realize 2nd order LPF $H(s) = \frac{K}{s^2 + s + C}$

we must choose Y_1 and $Y_3 \rightarrow$ Resistance $\rightarrow G_1 \& G_3$
 $Y_5 \rightarrow$ Capacitor $\rightarrow C_5, Y_4 \rightarrow$ Resistor $\rightarrow G_4$
 and $Y_2 \rightarrow$ Capacitor $\rightarrow C_2$, then sC_2

$$H(s) = \frac{(-G_1 G_3)}{s^2 C_5 C_2 + s C_5 (G_1 + G_3 + G_4) + G_3 G_4} \quad \text{--- (4)}$$

To make the above in the form $H(s) = \frac{K_0}{s^2 + K_1 s + K_2}$

Divide numerator N(s) and denominator D(s) by C₂C₅ and sub: $G = \frac{1}{R_1}$

$$H(s) = \frac{1}{R_1 R_3 C_2 C_5} \left(\frac{1}{s^2 + s \frac{1}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4} \right) + \frac{1}{R_3 R_4 C_2 C_5}} \right) \quad (5)$$

Compare the above eqn. with standard 2nd order system equation:

$$H(s) = \frac{1}{s^2 + \frac{\omega_0 z}{Qz} + \omega_0 z^2}$$

$$s^2 + \frac{\omega_0 p}{Qp} + \omega_0 p^2$$

where $\omega_0 z$ and $\frac{Qp}{z}$ → Frequency and quality factor of zero.

$\omega_0 p$ and Qp → freq. and quality factor of poles.

Consider eqn. (5) it is 2nd order LPF with cutoff frequency:


$$\omega_c = \omega_0 = \frac{1}{\sqrt{R_3 R_4 C_2 C_5}} \quad \text{cutoff freq.}$$

* To Find Max. gain: $K_{max} = \left| \frac{V_o}{V_i} \right|$ when $s=0$

So when we subst.

$s=0$ in eqn. (5)

$$|H(s)| = \frac{R_3 R_4 C_2 C_5}{R_1 R_3 C_2 C_5} = \frac{R_4}{R_1}$$

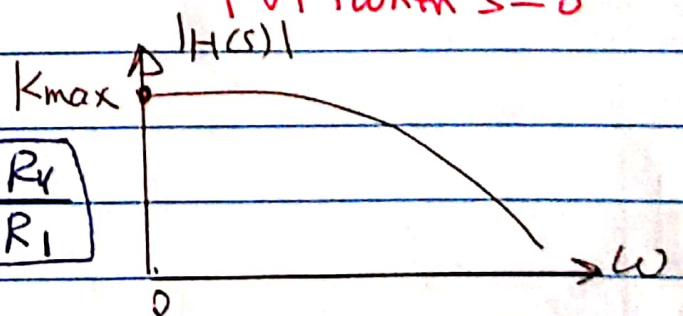


∴ This 2nd order LPF

$$\text{has: } f_c = \frac{1}{2\pi \sqrt{R_3 R_4 C_2 C_5}}, \quad K_{max} = \frac{R_4}{R_1}$$

For equal cap. design, $C_2 = C_5 = C$

$$f_c = \frac{1}{2\pi C \sqrt{R_3 R_4}}$$

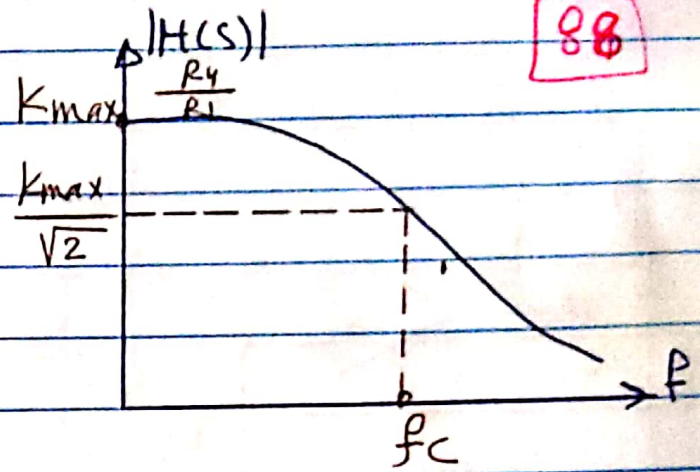and its response is shown in Fig.
Notice the Max. gain is $\frac{R_4}{R_1}$



EXA: Design a 2nd order LPF with a Max. gain = 40 dB and Cutoff freq = 2 kHz.

$$K_{max} = 40 \text{ dB} = 20 \log \frac{V_o}{V_i} \Rightarrow \log \frac{V_o}{V_i} = 2$$

$$\therefore \left| \frac{V_o}{V_i} \right| = 10^2 = 100 = K_{max}$$

$$K_{max} = \frac{R_4}{R_1}, \text{ assume } R_1 = 2 \text{ k}\Omega, R_4 = 50 \text{ k}\Omega$$

$$\therefore R_1 = 2 \text{ k}\Omega, R_4 = 50 \text{ k}\Omega$$

* Assume Equal-Cap. design and choose $C_2 = C_5 = C$
choose $C = 0.01 \mu\text{F}$.

From f_c expression: $R_3 R_4 = \frac{1}{4\pi^2 C^2 f_c^2}$

$$\therefore R_3 R_4 = \frac{1}{4 \times (3.14)^2 \times 10^{-6} \times 4 \times 10^6} = \frac{1}{4 \times 10 \times 10^{-6} \times 4 \times 10^6}$$


$$\therefore R_3 R_4 = \frac{10^9}{16} = 62.5 \times 10^6 \Omega$$

but $R_4 = 50 \text{ k}\Omega$


$$\therefore R_3 = \frac{62.5 \times 10^6}{5 \times 10^4} = 1.25 \text{ k}\Omega$$

$\therefore R_1 = 2 \text{ k}\Omega, R_4 = 50 \text{ k}\Omega$

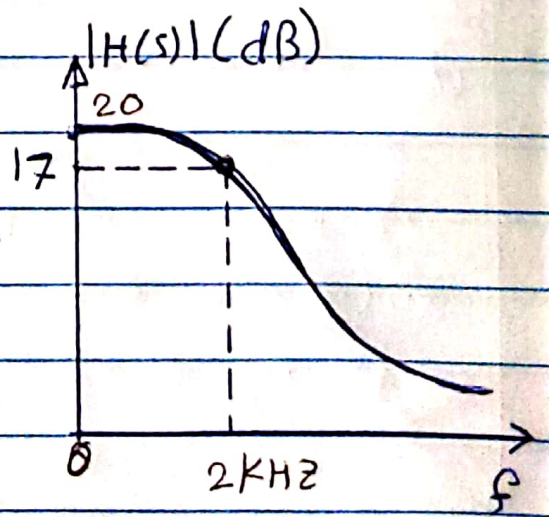$R_3 = 1.25 \text{ k}\Omega, C_2 = C_5 = 0.01 \mu\text{F}$



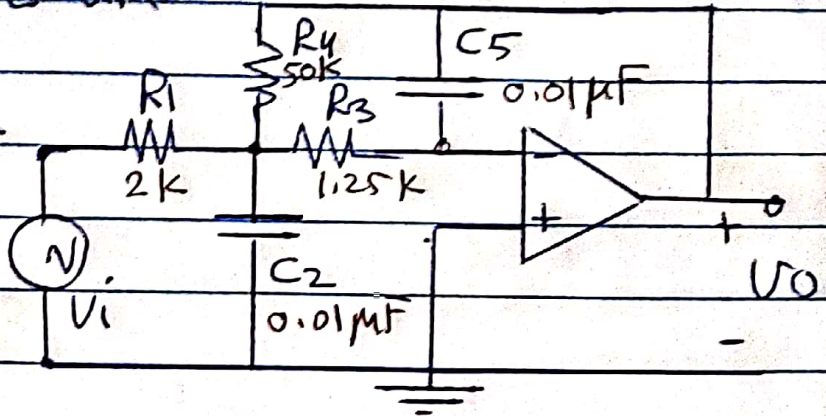all Resistor values are in K Ω range which is desirable for design.



2) Realization of HPF

This filter can be obtained by C \rightarrow R and R \rightarrow C transformation OR looking at eqn. (4) and choose the components Y such that the H(s) will have a form $H(s) = \frac{s^2}{s^2 + s + 1}$

which means Y1 & Y3 must be capacitors to give $sC1, sC3 \rightarrow s^2 C1 C3$, Y4 \rightarrow capacitor $sC4$, Y2 and Y5 \rightarrow resistors $G2$ and $G5$

then:

$$H(s) = \frac{-s^2 C1 C3}{s^2 C3 C4 + G5(C1 + C3 + C4)s + G5 G2 - (C1/C4)s^2}$$


$$= \frac{s^2 + \frac{G5(C1 + C3 + C4)s}{C3 C4} + \frac{G5 G2}{C3 C4}}{1}$$

Compare to standard 2nd order system eqn.

$$H(s) = \frac{s^2 + (w_0 z / Q_z)s + w_0^2 z}{s^2 + \frac{w_0 p}{Q_p} s + w_0^2 p}$$

$$o/s \quad w_0^2 = \frac{1}{R5 R2 C3 C4} \rightarrow f_c = \frac{1}{2\pi \sqrt{C3 C4 R2 R5}}$$

$K_{max} = \left| \frac{V_o}{V_i} \right|_{s=\infty}$. divide $N(s)$ & $D(s)$ by s^2

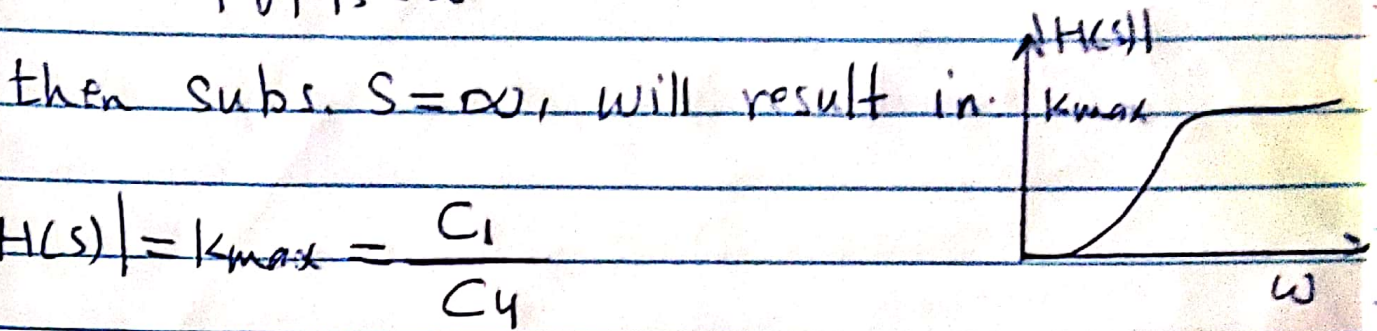

$|H(s)| = K_{max} = \frac{C_1}{C_4}$

∴ For this 2nd order HPF:

$f_c = \frac{1}{2\pi\sqrt{R_2 R_5 C_3 C_4}}$ (Cutoff Freq)

and Max. gain $K_{max} = \frac{C_1}{C_4}$


and the cct. is

EXA2: Design a 2nd order HPF to have:

$f_c = 20\text{KHz}$, and

a Max. gain $K_{max} = 10$.

• Sketch freq. response.

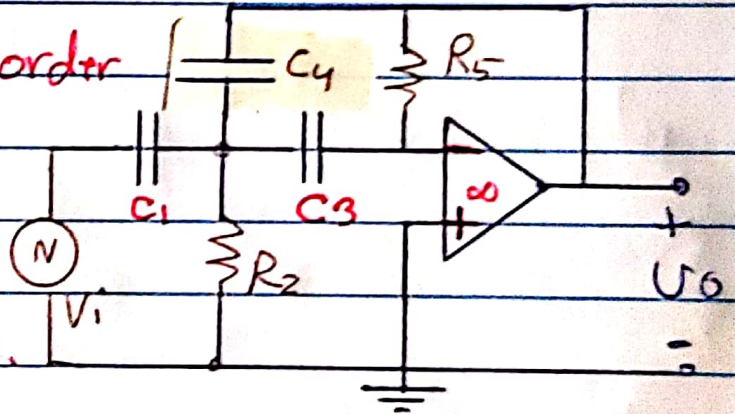

Since $K_{max} = C_1/C_4 = 10$

∴ $C_1 = 10C_4$, let $C_4 = 0.1\mu\text{F}$

∴ $C_1 = 10 \times 0.1 = 1\mu\text{F}$.

$f_c = 1/2\pi\sqrt{R_2 R_5 C_3 C_4} \Rightarrow$ For equal Resistors design $R_2 = R_5 = R$

$f_c = \frac{1}{2\pi R\sqrt{C_3 C_4}}$, let $R = 1\text{k}\Omega = R_2 = R_5 = 1\text{k}$

$C_3 C_4 = \frac{1}{4\pi^2 R^2 f_c^2} \Rightarrow C_3 = \frac{1}{4\pi^2 R^2 f_c^2 C_4}$

but $C_4 = 0.1 \mu\text{F}$

91


$$C_3 = \frac{10^{-8}}{4 \times 10 \times (10^3)^2 \times (2 \times 10^4)^2 \times 10^{-7}} = \frac{10^{-8}}{16} = 0.625 \text{ nF}$$

So the designed components values:

$$R_2 = R_5 = 1 \text{ k}\Omega$$

$$C_1 = 1 \mu\text{F}, C_4 = 0.1 \mu\text{F}, C_3 = 0.625 \text{ nF}$$

and the response is shown in Fig.

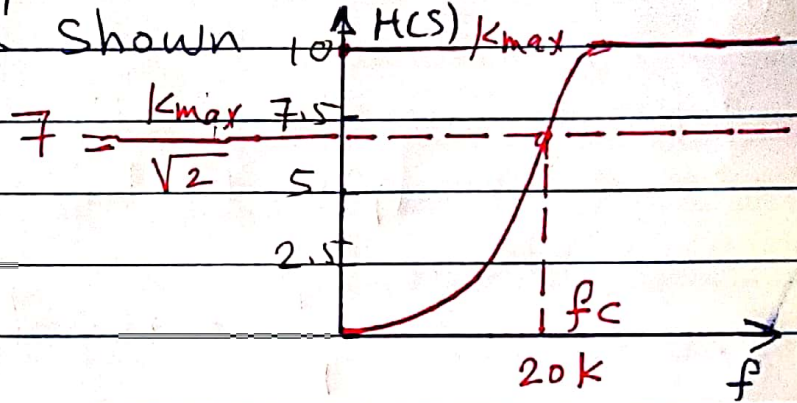

3 Realization of 2nd order BPF

Consider equation (x), to realize BPF, it must have a transfer function of the form $H(s) = \frac{s}{s^2 + s + c}$

So we have to choose Y_1 and Y_2 of different type such that $Y_1 Y_3 \rightarrow$ contain s

either $Y_1 \rightarrow G_1$ & $Y_3 \rightarrow sC_3$ OR $Y_1 \rightarrow sC_1$ & $Y_3 \rightarrow G_3$

let $Y_1 \rightarrow G_1$, $Y_3 \rightarrow sC_3$, so $Y_5 \rightarrow G_5$, $Y_2 \rightarrow G_2$

and $Y_4 \rightarrow G_4$: this choice will result in:

$$H(s) = \frac{-G_1 C_3 s}{C_3 C_4 s^2 + G_5 (C_3 + C_4) s + G_5 (G_1 + G_2)}$$

Divide $N(s)$ & $D(s)$ by $C_3 C_4$ will result in:

$$H(s) = \frac{(-G_1 / C_4) s}{s^2 + G_5 \left(\frac{C_3 + C_4}{C_3 C_4} \right) s + G_5 \left(\frac{G_1 + G_2}{C_3 C_4} \right)} \quad (7)$$

Compare eqn. (7) with standard 2nd order system eqn.

$$H(s) = \frac{s^2 + \frac{\omega_0 z}{Q_z} s + \omega_0 z^2}{s^2 + \frac{\omega_0 p}{Q_p} s + \omega_0 p^2}$$

The center freq ω_0 is: $\omega_0 = \sqrt{C_3 C_4 R_5 R_{eq}}$

where $R_{eq} = R_1 // R_2$

Using equal-cap. design $C_3 = C_4 = C$


∴ $f_0 = \frac{1}{2\pi C \sqrt{R_5 R_{eq}}}$

The Max. Gain K_{max} , can be derived as

$K_{max} = \left| \frac{V_o}{V_i} \right|_{s = \omega_0 = \omega}$

From eqn. (7) s^2 will cancel ω_0^2

$|H(s)| = \left[\frac{G_1}{C_4} \right] / \left[\frac{C_3 + C_4}{C_3 C_4} G_5 \right]$

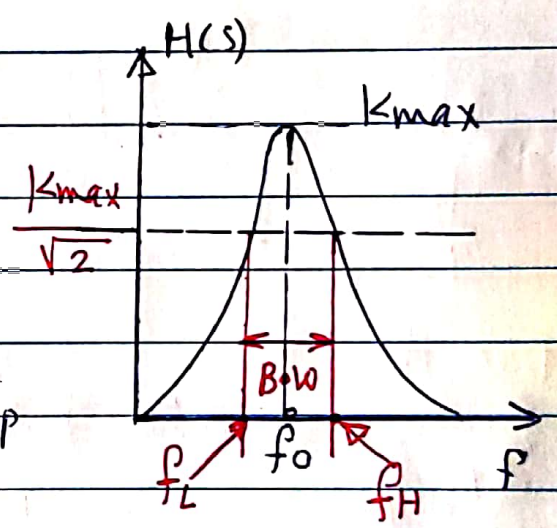

$|H(s)| = \frac{G_1}{C_4} \times \frac{C_3 C_4}{G_5 (G_4 + G_3)} = \frac{G_1 C_3}{G_5 (C_3 + C_4)}$ passband gain

For equal cap. design $C_3 = C_4 = C$

∴ Max. gain = $\frac{R_5 \cdot C}{R_1 \cdot 2C} = \frac{R_5}{2R_1}$

the selectivity $Q = \frac{f_0}{B.W}$ can be derived as follow:

From eqn. (7) $\frac{\omega_0 p}{Q_p} = \frac{G_5 (C_3 + C_4)}{C_3 C_4} = \frac{2G_5 \cdot C}{C}$

$B.W = \frac{2}{R_5 C}$

Using the idea: $Q = \frac{Q}{\omega_0} \cdot \omega_0$

where $\omega_0 = \frac{1}{C\sqrt{R_5 R_{eq}}}$ ~~or~~ $\omega_0 = \sqrt{\frac{G_5(G_1+G_2)}{C_3 C_4}}$

and $\frac{\omega_0}{Q} = \frac{G_5(C_3+C_4)}{C_3 C_4}$

∴ $Q = \frac{C_3 C_4}{G_5(C_3+C_4)} \cdot \sqrt{\frac{G_5(G_1+G_2)}{C_3 C_4}}$

For $C_3 = C_4 = C \rightarrow Q = \frac{1}{2} \sqrt{\frac{G_1+G_2}{G_5}} = \frac{1}{2} \sqrt{\frac{R_5}{R_{eq}}}$

∴ For BPF realization: ($R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$)


① $f_0 = \frac{1}{2\pi C \sqrt{R_5 R_{eq}}}$ center freq.

② $\frac{\omega_0}{Q} = \frac{2}{R_5 \cdot C}$


③ Max. gain = passband gain $K_{max} = \frac{R_5}{2R_1}$

④ Selectivity $Q = \frac{1}{2} \sqrt{\frac{R_5}{R_{eq}}}$

and the circuit is as shown in Fig.

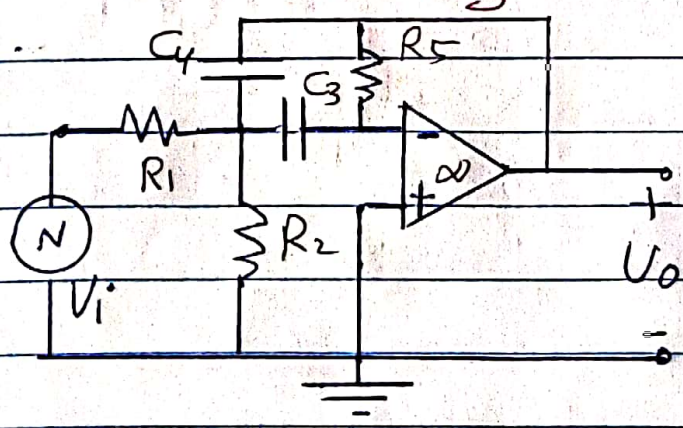

cct. diagram

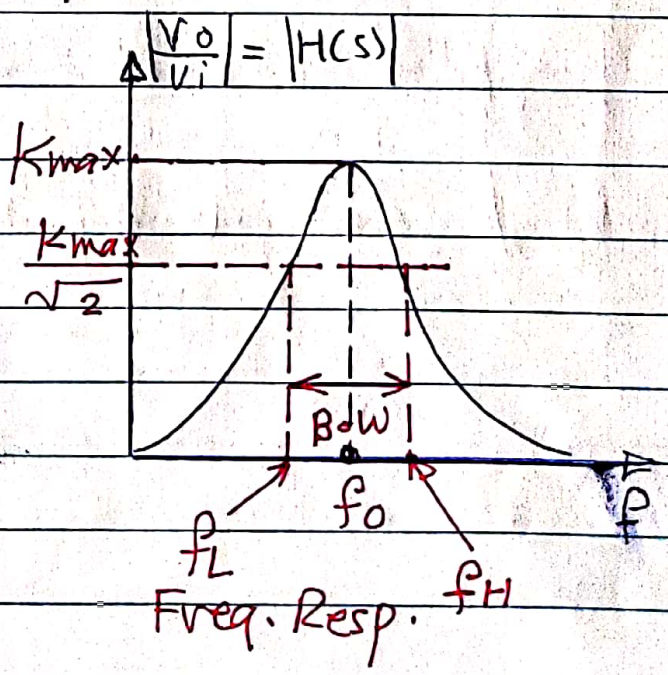

EXA: Design a 2nd order BPF Filter to have a passband gain = 10, Center freq = 20 kHz and selectivity $Q = 10$. Sketch the freq. response. "The available cap. is 1 nF". 94

From eqn: $\frac{\omega_0}{Q} = \frac{2}{R_5 \cdot C} \Rightarrow R_5 = \frac{2Q}{\omega_0 \cdot C} = \frac{2 \times 10}{2\pi \times 2 \times 10^4 \times 10^{-9}}$

$R_5 = \frac{2 \times 10}{2\pi \times 2 \times 10^4 \times 10^{-9}} = \frac{2 \times 10}{4\pi \times 10^5} = 159.155 \text{ k}\Omega$

$K_{max} = \frac{R_5}{2R_1} \Rightarrow R_1 = \frac{R_5}{2K_{max}} = \frac{159.155}{2 \times 10}$

$R_1 = 7.957 \text{ k}\Omega$

$f_0 = \frac{1}{2\pi C \sqrt{R_5 R_{eq}}} \Rightarrow R_{eq} = R_1 \parallel R_2 = \frac{1}{4\pi^2 C^2 R_5}$

OR From Q expr. $Q = \frac{1}{2} \sqrt{\frac{R_5}{R_{eq}}}$


$R_{eq} = \frac{R_5}{4Q^2} = \frac{159.155}{4 \times 100} = 0.397 \text{ k}\Omega = \frac{R_1 R_2}{R_1 + R_2}$

∴ $R_2 = \frac{R_1 \cdot R_{eq}}{R_1 - R_{eq}} = \frac{7.957 \times 0.397}{7.957 - 0.397} = 0.412 \text{ k}\Omega$


$B.W = \frac{f_0}{Q} = \frac{20}{10} = 2 \text{ kHz}$ $K_{max} = 10$

$f_L = f_0 - \frac{B.W}{2} = 20 - \frac{2}{2} = 19 \text{ kHz}$

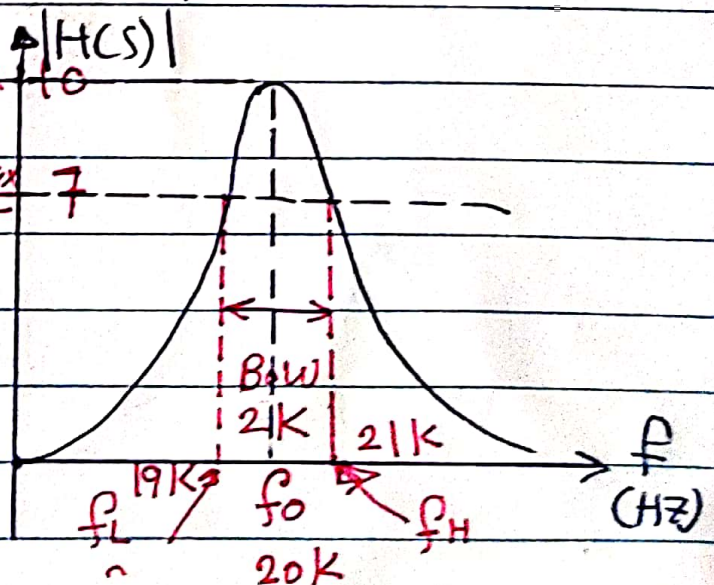$f_H = f_0 + \frac{B.W}{2} = 20 + \frac{2}{2} = 21 \text{ kHz}$



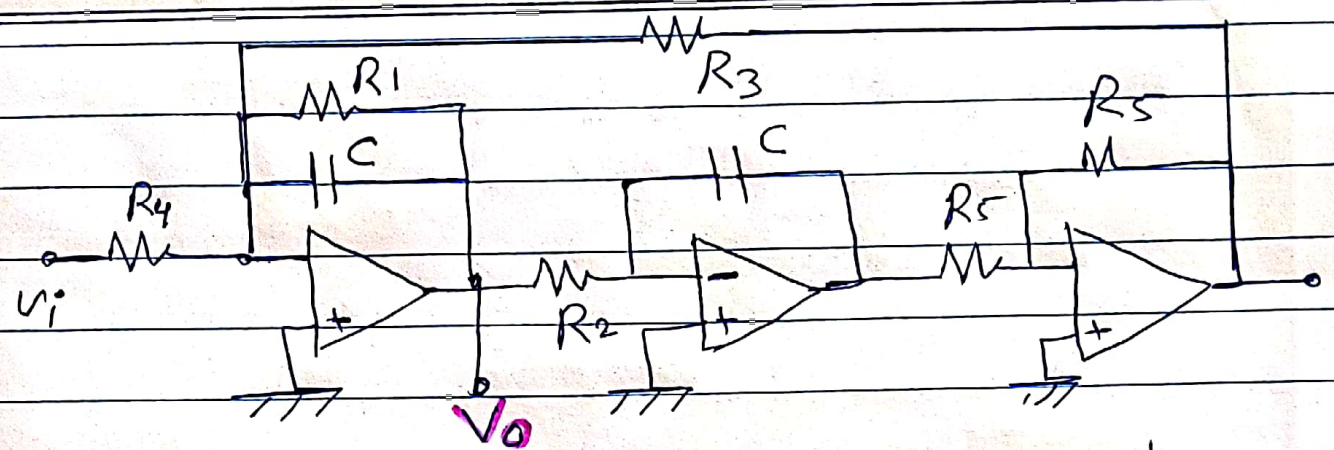Tow-Thomas Biquad "BP/IP" 2nd order Filter



The transfer function $H(s) = \frac{V_o}{V_i} = \frac{-\frac{1}{CR_4} s}{s^2 + \frac{1}{R_1 C} s + \frac{1}{R_2 R_3 C^2}}$

So it is a 2nd order BP Filter for the output indicated.

For $R_2 = R_3 = R$, then: $H(s) = \frac{-\frac{1}{R_4 C} s}{s^2 + \frac{1}{R_1 C} s + \frac{1}{R^2 C^2}}$

Compare to Standard 2nd order system eqn.

$D(s) = s^2 + \frac{\omega_0}{Q} s + \omega_0^2$


∴ $\omega_0 = \frac{1}{RC} \Rightarrow f_0 = \frac{1}{2\pi CR}$

Max. Gain $|A_{V(max)}| = |H(s)|_{s=\omega_0} = \frac{1}{R_4 C} \times \frac{R_1 C}{1}$
 ∴ $|A_{V(max)}| = \frac{R_1}{R_4}$

$Q = \frac{Q}{\omega_0} \times \omega_0 = \frac{R_1 C}{1} \times \frac{1}{RC} = \frac{R_1}{R}$

$f_H = f_0 + \frac{B.W}{2}$

$f_L = f_0 - \frac{B.W}{2}$

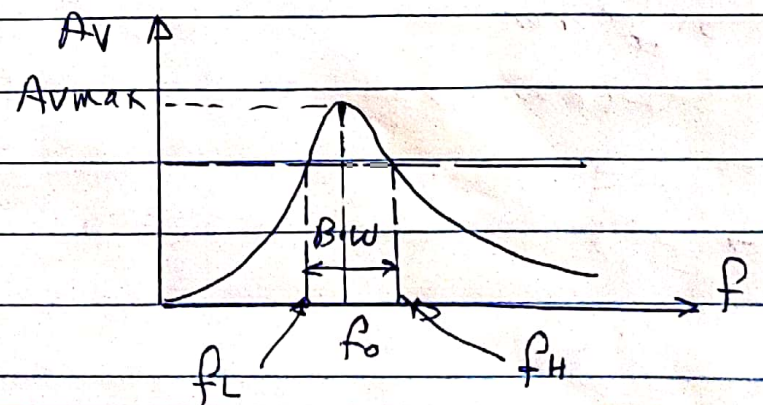

EXA: Design a 2nd order BPF to have
 $f_0 = 10 \text{ KHz}$, $Q = 50$ and $A_{v(\text{max})} = 100$
 sketch freq. Response. (Use $C = 0.01 \mu\text{F}$).

$$f_0 = \frac{1}{2\pi RC} \Rightarrow R = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi \times 10^4 \times 10^{-8}}$$

$$\therefore R = \frac{10^4}{2\pi} = 1.592 \text{ K}\Omega = R_2 = R_3$$

$$Q = \frac{R_1}{R} \Rightarrow R_1 = Q \cdot R = 50 \times 1.592 = 79.577 \text{ K}\Omega$$

$$A_{v(\text{max})} = \frac{R_1}{R_4} \Rightarrow R_4 = \frac{R_1}{A_{v(\text{max})}} = \frac{79.577 \text{ K}}{100}$$

$$\therefore R_4 = 0.79577 \text{ K}\Omega.$$

