

تقدم لجنة EiCoM الاكاديمية

تلخيص لمادة:

الات كهربائية

جزيل الشكر للطالب:

تولين هبرة



** In rotary machines, speed is measured in (radian per second [r/s])
or (revolution per minute [rpm])*

$$1[\text{rpm}] = \frac{\pi}{30} [\text{r/s}]$$

Where [r/s] < [rpm]

** In all motors and generators, electric power is measured in Watts [W]*

*On the other hand, mechanical power is measured either in watts [W]
or in Horsepower [hp]*

$$1[\text{hp}] = 746[\text{W}]$$

Where [hp] < [W]

** It should be noted that the mechanical power can be computed
from the torque and speed as:*

$$\text{Power [W]} = \text{Torque [N.m]} \times \text{speed [r/s]}$$

** Electrical power can be computed as:*

$$\text{—DC Machines} \rightarrow \text{Power [W]} = \text{current [A]} \times \text{voltage [V]}$$

$$\text{—AC Machines — } 1\theta^{(\text{one phase})} \rightarrow$$

$$\text{Active power [W]} = \text{current [A]} \times \text{voltage [V]} \times \cos\theta$$

$$\text{—AC Machines — } 3\theta \rightarrow$$

$$\text{Active power [W]} = \sqrt{3} \times \text{line current [A]} \times \text{line voltage [V]} \times \cos\theta$$

$$\text{Active power [W]} = 3 \times \text{phase current [A]} \times \text{phase voltage [V]} \times \cos\theta$$

Magnetic field

* The total flux in the core due to the current i in the winding is

$\Phi = BA = \mu \frac{NiA}{L_c}$, $N \rightarrow$ Num of turns, $i \rightarrow$ the current in the coil, $A \rightarrow$ the cross-sectional area of the magnetic field, $L_c \rightarrow$ the average path in which the mag field flows, $\mu \rightarrow$ permeability

Where Φ (magnetic field) in Webers [Web], B (magnetic field density) in Webers per square meter [Web/m²]

known as Tesla [T]

**right hand rule:-four fingers in the direction of the current*

-the thumb in the direction of the magnetic field

-palm of the hand in the direction of the force

In the magnetic circuit:

* The reluctance of a magnetic circuit is the counterpart of electrical resistance, and its units are ampere – turns per weber

$\Phi = BA = \mu HA$ $\mathcal{F} \rightarrow$ magnetomotive force of circuit

$\Phi = \mu \left(\frac{Ni}{L_c} \right) A = Ni \left(\frac{\mu A}{L_c} \right)$ $\Phi \rightarrow$ flux of circuit, $\mathcal{R} \rightarrow$ reluctance

$\Phi = \mathcal{F} \left(\frac{\mu A}{L_c} \right) = \frac{\mathcal{F}}{\mathcal{R}}$ $H \rightarrow$ magnetic field intensity

$B = \mu H$

Linear DC Machine

* the equation for the force on a wire in the presence of a magnetic field:

$F = i(L \times B) \rightarrow F = iLB \sin \theta$

where $F \rightarrow$ force on wire, $i \rightarrow$ magnitude of current in wire, $B \rightarrow$ magnetic flux density vector
 $L \rightarrow$ length of wire. with direction of L defined to be in the direction of current flow

* the equation for the voltage induced on a wire moving in a magnetic field:

$$e_{ind} = (v \times B) \cdot L \rightarrow e_{ind} = (VB \sin \theta_1) L \cos \theta_2$$

where $e_{ind} \rightarrow$ voltage induced in wire, $v \rightarrow$ velocity of the wire, $B \rightarrow$ magnetic flux density vector, $L \rightarrow$ length of conductor in the magnetic field

* Kirchoff's voltage law for this machine


$$V_B - iR - e_{ind} = 0 \rightarrow V_B = e_{ind} + iR = 0$$

*Newton's law for the bar across the tracks:

$$F_{net} = ma$$

Linear DC Machine cases:

First case: (Ideal motor)

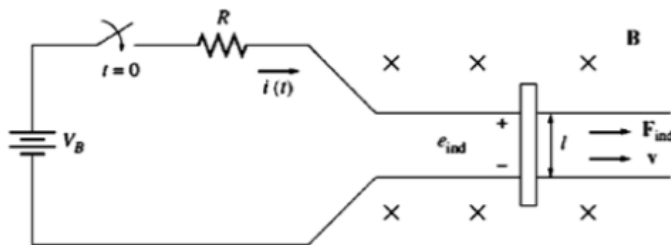

1. closing the switch produces a current flow $i = \frac{V_B}{R}$ (starting current)

2. the current flow produces an induced force on the bar given be

$$F_{ind} = iLB$$

3. The bar accelerates due to the induced force as $a = \frac{F_{ind}}{m} = \frac{\Delta v}{\Delta t}$


4. The bar moves to the right, producing an induced voltage $e_{ind} = vBL$ as it speeds up

5. This induced voltage reduces the current flow $i = (v_B - e_{ind} \uparrow)/R$

6. The induced force is thus decreased $F_{ind} = i \downarrow LB$ until eventually $F_{ind} = 0$ At that point. $e_{ind} = V_B$, $i = 0$, and the bar moves at a constant no – load speed

$v_{ss} = V_B/BL$ where $a = 0$ (note that $F_{ind} = 0$)

Second case: (real case of DC motor)

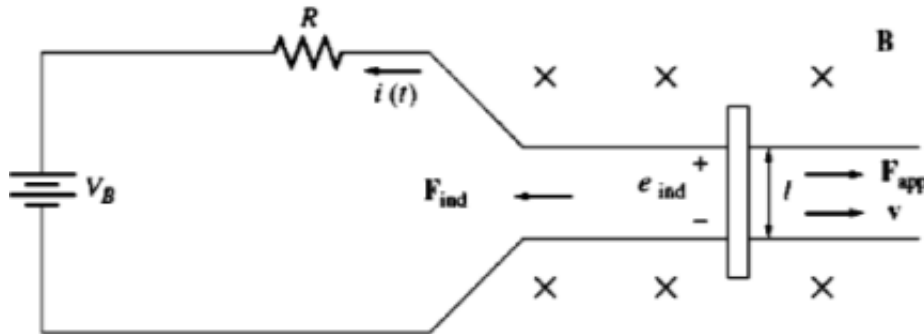

** if a force F_{load} is applied to the bar in OPPOSITE direction of motion hence the net force is $F_{net} = -F_{load}$ and the following events occur:*

1. The bar decelerates due to the load force as $a = F_{net}/m = \Delta v/\Delta t$ since $F_{net} < 0$
note that $F_{load} < F_{ind}$


2. The effect of this net force will reduce $e_{ind} = v \downarrow BL$ as the bar slows down

3. This induced voltage increases the current flow $i = (V_B - e_{ind} \downarrow)/R$

4. The induced force is thus increased $F = i \uparrow LB$ until $|F_{ind}| = |F_{load}|$ at a lower speed v

5. An amount of electric power equal to $e_{ind}i$ is now being converted to mechanical power equal to $F_{ind}v$, and the machine is acting as a motor.

Third case:

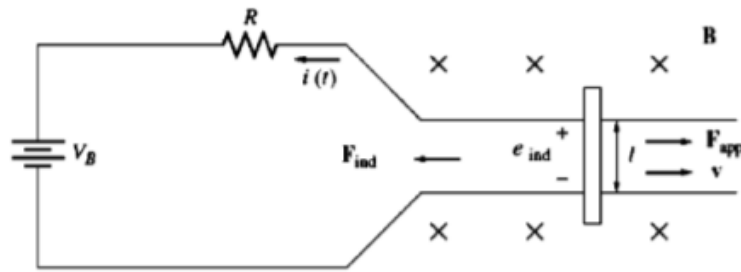


* If a force F_{app} is applied to the bar in the SAME direction of motion, hence the net force is $F_{net} = F_{app}$ and the following events occur:

1. The bar accelerates due to the load force as $a = F_{net}/m = \Delta v/\Delta t$ since $F_{net} > 0$
2. The effect of this net force will increase $e_{ind} = v \uparrow BL$ as the bar speeds up
3. This induced voltage reverses the direction of the current flow $i = (V_B - e_{ind})/R$ since $(V_B < e_{ind})$
4. The induced force is thus reverses its direction due to the reversed current $-F_{ind} = -iLB$ until $|F_{ind}| = |F_{app}|$. Note that $F_{net} = F_{app} - F_{ind}$ in this case
5. An amount of mechanical power equal to $F_{app}v$ is now being converted To electric power equal to $e_{ind}i$, and the machine is acting as a generator.

DC Machines-simple rotating loop

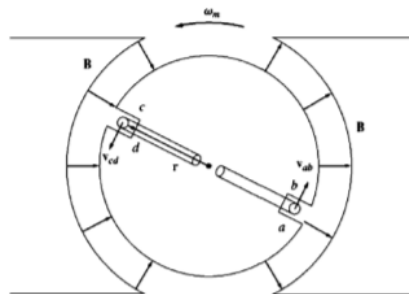- * If the rotor of this machine is rotated, a voltage will be induced in the wire loop.
- * To determine the total voltage e_{tot} on the loop, we need to examine each segment of the loop separately and sum all the resulting voltages. The voltage on each segment is given by



$$e_{ba} = (v \times B).L = \begin{cases} vBL & \text{positive into page under the pole face} \\ 0 & \text{beyond the pole edges} \end{cases} \dots(1)$$

$$e_{cb} = 0, \text{ because of thetas in sin and cos } \dots(2)$$


$$e_{dc} = (v \times B).L = \begin{cases} vBL & \text{positive out of page under the pole face} \\ 0 & \text{beyond the pole edges} \end{cases} \dots(3)$$

$$e_{ad} = 0, \text{ because of thetas in sin and cos } \dots(4)$$

The total induced voltage on the loop e_{ind} is given by:

$$e_{ind} = e_{ba} + e_{cb} + e_{dc} + e_{ad}$$
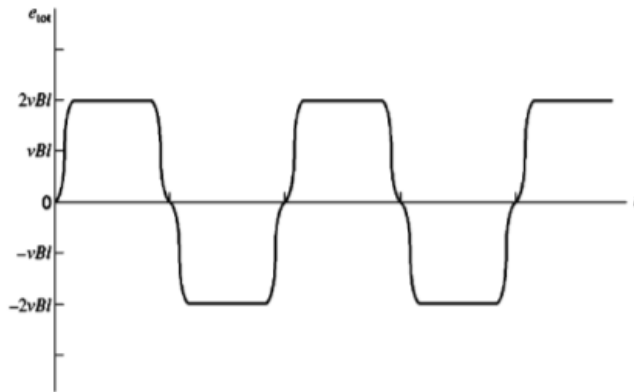
$$e_{ind} = \begin{cases} 2vBL & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \dots(5)$$



Given $v = r\omega$, $\Phi = A_p B$, and pole surface area of $A_p = \pi rL$, an alternative expression can be obtained.


$$e_{ind} = \begin{cases} 2r\omega BL & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases}$$

$$e_{ind} = \begin{cases} \frac{2}{\pi} A_p B \omega & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases}$$

$$e_{ind} = \begin{cases} \frac{2}{\pi} \Phi \omega & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \dots(6)$$

-This is for single loop (speed of rotor $\omega = \frac{V_B}{2rLB}$ when $V_B = e_{ind}$)

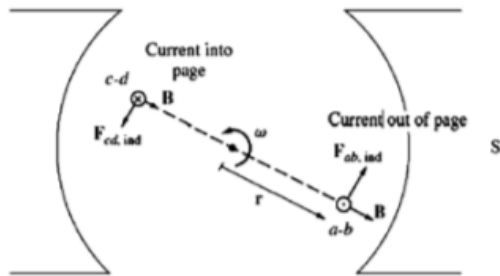* Suppose a battery is connected to the machine how the torque is developed inside it.(P11 in slides)



$$F_{ab} = i(L \times B) = iLB \text{ (tangent to direction of motion)...(7)}$$

The torque on the rotor caused by this force is

$$\tau_{ab} = rF \sin\theta = r(iLB) \sin 90^\circ = riLB \text{ CCW....(8)}$$

$$F_{bc} = i(L \times B) = 0 \text{ since } L \text{ is parallel to } B \text{....(9)}$$

$$\text{Therefore } \tau_{bc} = 0 \text{ (10)}$$

$$F_{cd} = i(L \times B) = iLB \text{ (tangent to direction of motion)(11)}$$

The torque on the rotor caused by this force is

$$\tau_{cd} = rF \sin\theta = r(iLB) \sin 90^\circ = riLB \text{ CCW....(12)}$$

$$F_{da} = i(L \times B) = 0 \text{ since } L \text{ is parallel to } B \text{....(13)}$$

$$\text{Therefore } \tau_{da} = 0 \text{ (14)}$$

* the resulting total induced torque on the loop is given by

$$\tau_{ind} = \tau_{ab} + \tau_{bc} + \tau_{cd} + \tau_{da}$$

$$\tau_{ind} = \begin{cases} 2riLB & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \text{....(15)}$$

By using $A_p \approx \pi rL$ and $\phi = A_p B$

$$\tau_{ind} = \begin{cases} \frac{2}{\pi} \phi i & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \text{....(16), } P = \tau \omega$$

this is in single loop if it's more than this $\frac{2}{\pi}$ will be represented as another constant(K)

Power flow and losses

* the copper losses for the armature and field windings are given by:

$$\text{Armature loss: } P_A = I_A^2 R_A$$

Where $P_A \rightarrow$ armature loss, $I_A \rightarrow$ armature current, $R_A \rightarrow$ armature resistance

$$\text{Field loss: } P_F = I_F^2 R_F$$


Where $P_F \rightarrow$ field circuit loss, $I_F \rightarrow$ field current, $R_F \rightarrow$ field resistance

* the brush losses it is given by the equation:

$$P_{BD} = V_{BD} I_A$$

where $P_{BD} \rightarrow$ brush drop loss, $V_{BD} \rightarrow$ brush voltage drop, $I_A \rightarrow$ armature current

Page(42 in slides)

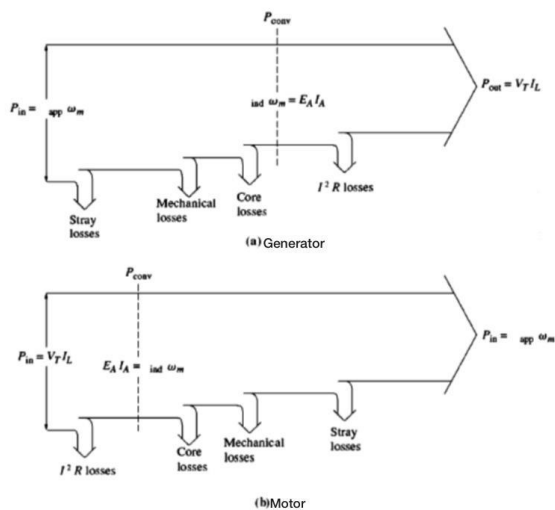

$$P_{conv} = \tau_{ind} \omega_m$$

$$P_{conv} = E_A I_A$$

* The efficiency of a DC machine is defined by the equation

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

$$\eta = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$$


DC Machines-Motors

* *the speed regulation (SR) of a motor is defined by*

$$SR = \frac{\omega_{nl} - \omega_{fl}}{\omega_{fl}} \times 100\% \quad (nl \rightarrow \text{no load}, fl \rightarrow \text{full load})$$

$$SR = \frac{n_{nl} - n_{fl}}{n_{fl}} \times 100\%$$

Separately Excited and Shunt DC Motors

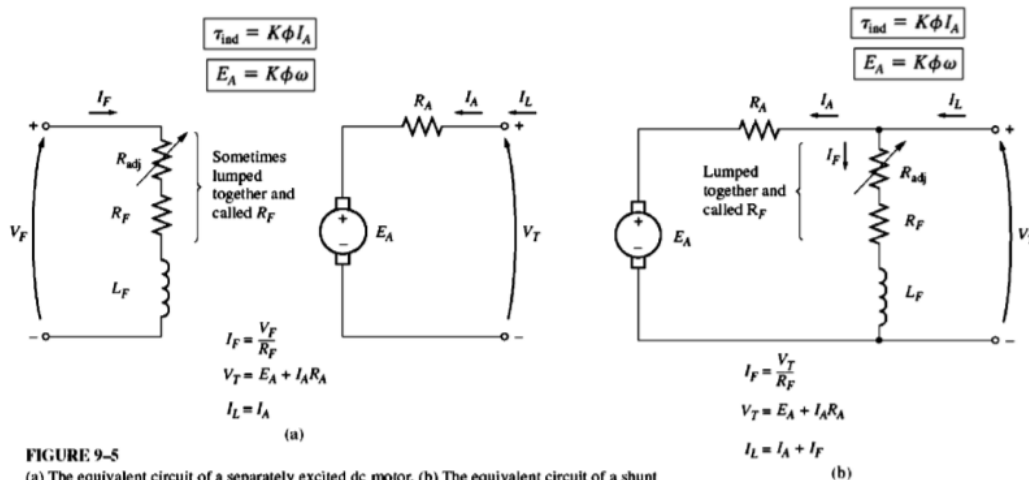

* *Speed of the motor* $\rightarrow \frac{E_A}{E_{A0}} = \frac{n}{n_0}$

#Changing the Field Resistor Control Method:

1. *Increasing R_F causes $I_F = (V_F/R_F \uparrow)$ to decrease.*
2. *Decreasing I_F decreases ϕ*
3. *Decreasing ϕ lowers $E_A = (K\phi \downarrow \omega)$.*
4. *Decreasing E_A increases $I_A = ((V_T - E_A \downarrow)/R_A)$*
5. *Increasing I_A increase $\tau_{ind} = (K\phi \downarrow I_A \uparrow)$, with the change in I_A dominant over the change in flux.*
6. *Increasing τ_{ind} makes $\tau_{ind} > \tau_{load}$, and the speed ω increases*
7. *Increasing ω increases $E_A = (K\phi\omega \uparrow)$ again.*

8. Increasing E_A decreases I_A

9. Decreasing I_A decreases τ_{ind} until $\tau_{ind} = \tau_{load}$ at a higher speed ω

#Changing the Armature Voltage Control Method

1. Increasing V_T increases $I_A = ((V_T \uparrow - E_A)/R_A)$

2. Increasing I_A increases $\tau_{ind} = (K\phi I_A \uparrow)$

3. Increasing τ_{ind} , makes $\tau_{ind} > \tau_{load}$ and the speed ω increases

4. Increasing ω increases $E_A = (K\phi\omega \uparrow)$

5. Increasing E_A decreases $I_A = ((V_T - E_A \uparrow)/R_A)$

6. Decreasing I_A decreases τ_{ind} until $\tau_{ind} = \tau_{load}$ at a higher speed ω

#Inserting a Resistor in Series with the Armature Circuit

1. Increasing R_A decreases $I_A = ((V_T - E_A)/R_A \uparrow)$

2. Decreasing I_A decreases $\tau_{ind} = (K\phi I_A \downarrow)$

3. decreasing τ_{ind} , makes $\tau_{ind} < \tau_{load}$ and the speed ω decreases

4. decreasing ω decreases $E_A = (K\phi\omega \downarrow)$

5. Decreasing E_A increases $I_A = ((V_T - E_A \downarrow)/R_A)$

6. Increasing I_A increases τ_{ind} until $\tau_{ind} = \tau_{load}$ at a lower speed ω

the internal generated voltage of a DC machine with its speed expressed in revolution per minute is given by

$$e_A = k' \phi n$$

the relationship between the speeds and internal generated voltages of the motor at two different conditions is thus

$$\frac{E_{A2}}{E_{A1}} = \frac{K' \phi n_2}{K' \phi n_1} \rightarrow n_2 = \frac{E_{A2}}{E_{A1}} n_1$$

The induced torque for any other load can be found from the fact $P_{conv} = E_A I_A = \tau_{ind} \omega \rightarrow$


$$\tau_{ind} = \frac{E_A I_A}{\omega}$$

the effective shunt field current of the motor is

$$I_F^* = I_F - \frac{\mathcal{F}_{AR}}{N_F}, \mathcal{F}_{AR} [\text{A. turns}]$$

#Transformers:

*Ideal transformer

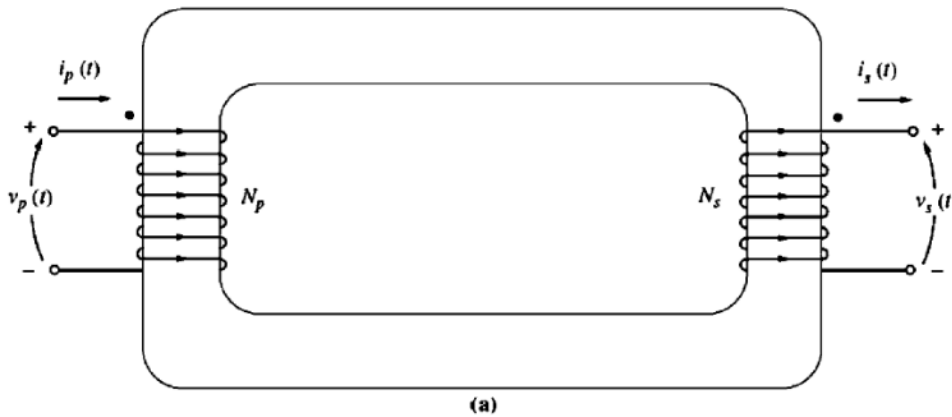

(a)
FIGURE 2-4
(a) Sketch of an ideal transformer.

* Faraday's law of induction


$$\varepsilon = -N \frac{\Delta\Phi_B}{\Delta t}$$

ε : induced emf, N : number of loops, $\Delta\Phi/\Delta t$: rate of change of flux with time
minus sign from lenz's law


* Lenz's Law


The *induced B field* in a loop of wire will **oppose the change in magnetic flux** through the loop.

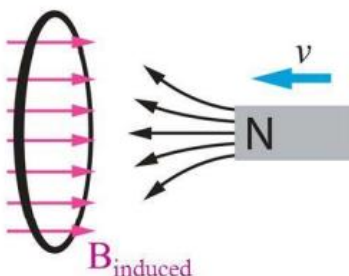If you try to **increase** the flux through a loop, the induced field will oppose that increase!



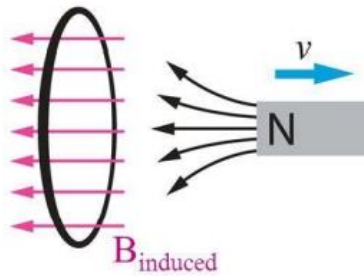If you try to **decrease** the flux through a loop, the induced field will replace that decrease!



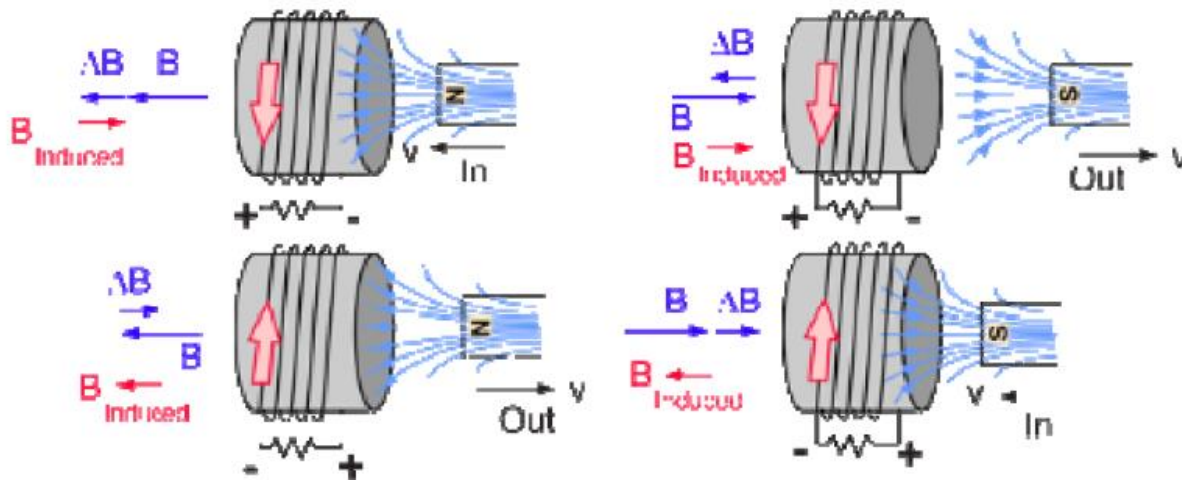

* Since the magnetomotive forces are equal in primary and secondary windings

$$\mathcal{F}_P = \Phi \mathcal{R} = \mathcal{F}_S \rightarrow N_P i_P = N_S i_S \rightarrow \frac{N_P}{N_S} = \frac{i_S}{i_P} = a$$

where a is the **transformer turns ratio**

* From faraday's laws

V is proportional to N ($V \propto N$)

$$\frac{V_P}{V_S} = \frac{N_P}{N_S} = a$$

$$* V_P i_P = V_S i_S \rightarrow S_{in} = S_{out}$$

$$* P_{in} = V_P i_P(\theta_P), * P_{out} = V_S i_S(\theta_S)$$

* since $V_p i_p = V_s i_s$ and since voltage and current angles are unaffected by an ideal transformer then $\theta_p = \theta_s$

* The primary and secondary windings of an ideal transformer have the same

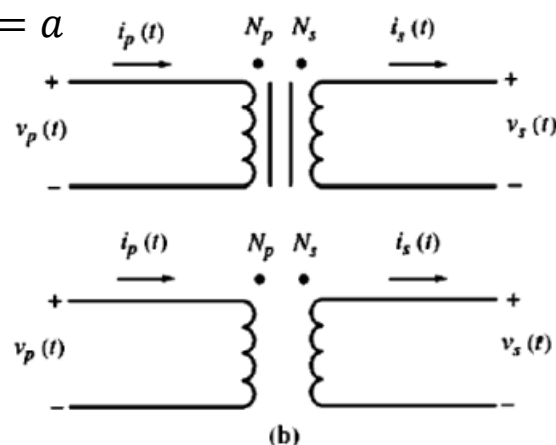


FIGURE 2-4
(b) Schematic symbols of a transformer.

power factor then $P_{in} = P_{out}$ and then $Q_{in} = Q_{out}$

#If $N_P < N_S \rightarrow V_P < V_S \rightarrow i_P > i_S$ (step – up transformer)

#If $N_P > N_S \rightarrow V_P > V_S \rightarrow i_P < i_S$ (step – down transformer)

* The impedance of a device or an element is defined as the ratio of the phasor Voltage across it to the phasor current flowing through it

$$Z_L = \frac{V_L}{I_L}$$

$$* Z'_L = \frac{V_P}{I_P} = \frac{aV_S}{I_S/a} = a^2 \frac{V_S}{I_S}$$

$$\rightarrow Z'_L = a^2 Z_L$$

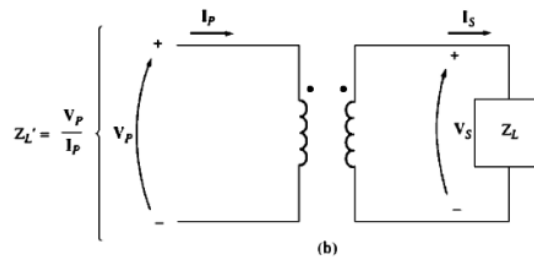
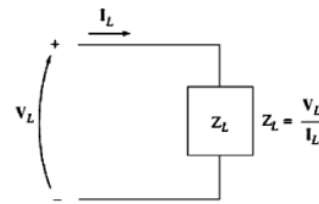


FIGURE 2-5 (a) Definition of impedance. (b) Impedance scaling through a transformer.

$$* I_{line} = \frac{V}{Z_{line} + Z_{load}}, V_{load} = I_{line} Z_{load}, P_{loss} = (I_{line})^2 R_{line}, Z_{eq} = Z_{line} + Z'_{load}$$

#Operation of real transformer

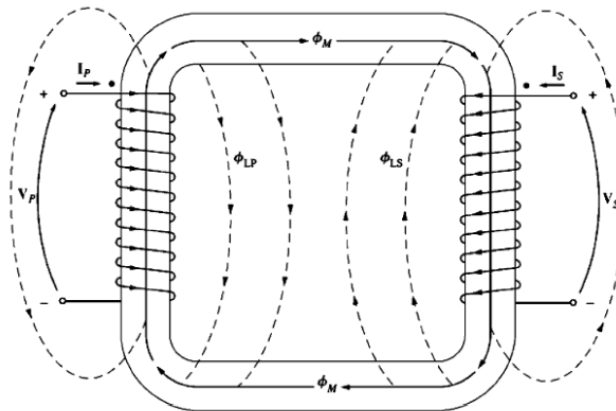


FIGURE 2-10 Mutual and leakage fluxes in a transformer core.

#The questions about this case will be concept questions

* The flux in the primary coil of the transformer can thus be divided into two components: a mutual flux, which remains in the core and links both windings, and a small leakage flux, which passes through the primary winding but returns through the air, bypassing the secondary winding:

$$\bar{\Phi}_P = \Phi_M + \Phi_{LP}$$

$\bar{\Phi}_P$: total average primary flux, Φ_M : flux component linking both primary and secondary coils,
 Φ_{LP} : primary leakage flux

* There is a similar division of flux in the secondary winding between mutual flux and leakage flux which passes through the secondary winding but returns through the air, by passing the primary winding:

$$\bar{\Phi}_S = \Phi_M + \Phi_{LS}$$

$\bar{\Phi}_S$: total average secondary flux, Φ_M : flux component linking both primary and secondary coils,
 Φ_{LS} : secondary leakage flux

* Since in a well designed transformer $\Phi_M \gg \Phi_{LP}$ and $\Phi_M \gg \Phi_{LS}$ the ratio of the total voltage on the primary of a transformer to the total voltage on the secondary of a transformer is approximately

* The smaller the leakage fluxes of the transformer are, the closer the total transformer voltage ratio approximates that of the ideal transformer

$$\frac{v_P(t)}{v_S(t)} = \frac{N_P}{N_S} = a$$

* *Open – circuit test:*

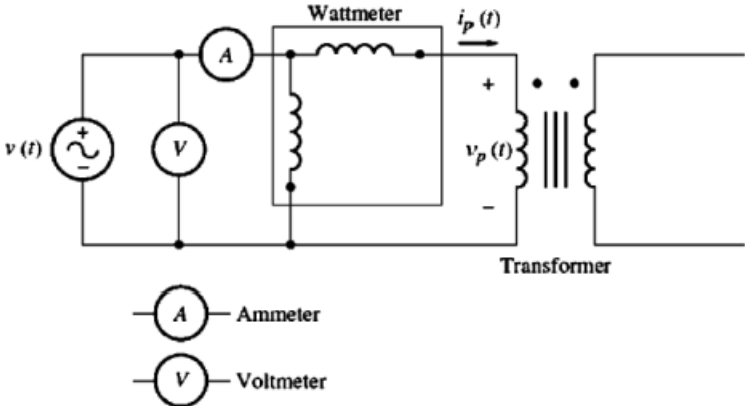


FIGURE 2-19
 Connection for transformer open-circuit test.

- The conductance of the core – loss resistor is given by

$$G_c = \frac{1}{R_c}$$

- The susceptance of the magnetizing inductor is given by

$$B_M = \frac{1}{X_M}$$

- Since these two elements are in parallel, their admittances add, and the total excitation admittance is

$$Y_E = G_c - jB_M$$

$$Y_E = \frac{1}{R_c} - j\frac{1}{X_M}$$

- the following relations can be obtained

$$|Y_E| = \frac{I_{oc}}{V_{oc}}$$

$$PF = \cos(\theta) = \frac{P_{oc}}{V_{oc}I_{oc}} \Rightarrow \theta = \cos^{-1}\left(\frac{P_{oc}}{V_{oc}I_{oc}}\right)$$

$$Y_E = \frac{I_{oc}}{V_{oc}} \angle -\theta \Rightarrow Y_E = \frac{I_{oc}}{V_{oc}} \angle -\cos^{-1}(PF)$$

$$R_c = \frac{1}{G_c} = \frac{1}{Y_E \cos(\theta)}$$

$$X_M = \frac{1}{B_M} = \frac{1}{Y_E \sin(\theta)}$$

* *Short – circuit test:*

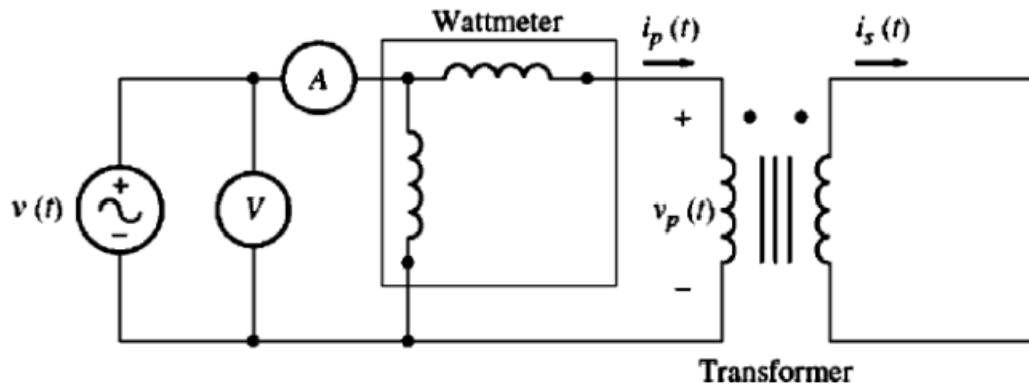


FIGURE 2-20
Connection for transformer short-circuit test.

◦ The magnitude of the series impedances referred to the primary side of the transformer is

$$|Z_{SE}| = \frac{V_{sc}}{I_{sc}}$$

◦ *The following relations can be obtained*

$$PF = \cos(\theta) = \frac{P_{sc}}{V_{sc}I_{sc}} \Rightarrow \theta = \cos^{-1}\left(\frac{P_{sc}}{V_{sc}I_{sc}}\right)$$


$$Z_{SE} = \frac{V_{sc} \angle 0}{I_{sc} \angle -\theta} = \frac{V_{sc}}{I_{sc}} \angle \theta$$

$$R_{eq} = Z_{SE} \cos(\theta)$$

$$X_{eq} = Z_{SE} \sin(\theta)$$

$$\underline{Z_{SE} = R_{eq} + jX_{eq} = (R_P + a^2R_S) + j(X_P + a^2X_S)}$$

* DC test:

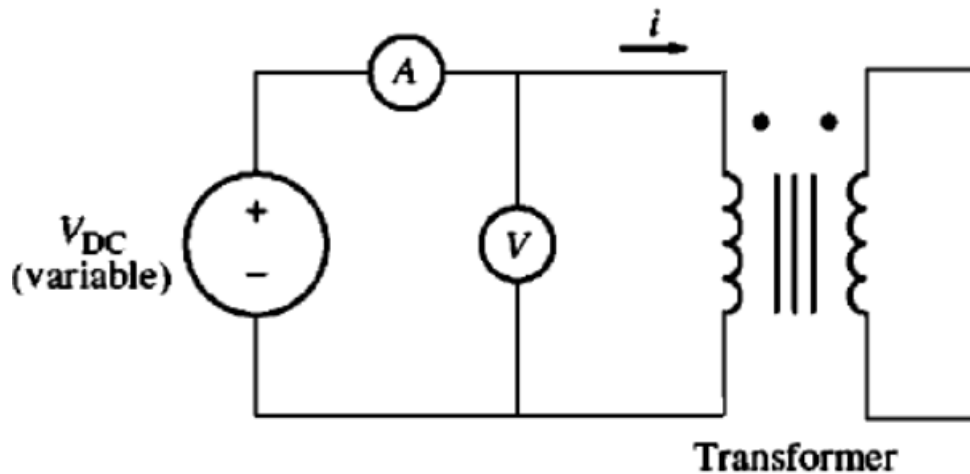

- Using Ohm's law and measurements of voltage and current, the internal resistor of the winding can be determined as

$$R = V / I$$

- It should be noted that this test can be done on both sides of the transformer
- Moreover, the DC power supply should be adjusted so that maximum DC current is not exceeded.
- **Note that the coil can handle a DC current that is certainly less than the rated AC current.**

* **Voltage regulation (VR)**

$$VR = \frac{V_{S.nl} - V_{S.fl}}{V_{S.fl}} \times 100\%$$

$$VR = \frac{V_P/a - V_{S.fl}}{V_{S.fl}} \times 100\%$$

$$\circ \frac{V_P}{a} = V_S + R_{eq}I_S + jX_{eq}I_S$$

* **Efficiency**

Transformers are also compared and judged on their efficiencies. The efficiency of a device is defined by the equation

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

$$\eta = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$$

To calculate the efficiency of a transformer at a given load, just add the losses the equation of efficiency such that

$$P_{out} = V_S I_S \cos\theta_S$$

$$\eta = \frac{V_S I_S \cos\theta_S}{P_{Cu} + P_{core} + V_S I_S \cos\theta_S} \times 100\%$$

$$P_{Cu} = (I_S)^2 R_{eq}$$

$$P_{core} = \frac{(V_P/a)^2}{R_C}$$

** In rotary machines, speed is measured in (radian per second [r/s])
or (revolution per minute [rpm])*

$$1[\text{rpm}] = \frac{\pi}{30} [\text{r/s}]$$

Where [r/s] < [rpm]

** In all motors and generators, electric power is measured in Watts [W]*

*On the other hand, mechanical power is measured either in watts [W]
or in Horsepower [hp]*

$$1[\text{hp}] = 746[\text{W}]$$

Where [hp] < [W]

** It should be noted that the mechanical power can be computed
from the torque and speed as:*

$$\text{Power [W]} = \text{Torque [N.m]} \times \text{speed [r/s]}$$

** Electrical power can be computed as:*

$$\text{—DC Machines} \rightarrow \text{Power [W]} = \text{current [A]} \times \text{voltage [V]}$$

$$\text{—AC Machines — } 1\theta^{(\text{one phase})} \rightarrow$$

$$\text{Active power [W]} = \text{current [A]} \times \text{voltage [V]} \times \cos\theta$$

$$\text{—AC Machines — } 3\theta \rightarrow$$

$$\text{Active power [W]} = \sqrt{3} \times \text{line current [A]} \times \text{line voltage [V]} \times \cos\theta$$

$$\text{Active power [W]} = 3 \times \text{phase current [A]} \times \text{phase voltage [V]} \times \cos\theta$$

Magnetic field

* The total flux in the core due to the current i in the winding is

$\Phi = BA = \mu \frac{NiA}{L_c}$, $N \rightarrow$ Num of turns, $i \rightarrow$ the current in the coil, $A \rightarrow$ the cross-sectional area of the magnetic field, $L_c \rightarrow$ the average path in which the mag field flows, $\mu \rightarrow$ permeability

Where Φ (magnetic field) in Webers [Web], B (magnetic field density) in Webers per square meter [Web/m²]

known as Tesla [T]

* *right hand rule: -four fingers in the direction of the current*

-the thumb in the direction of the magnetic field

-palm of the hand in the direction of the force

In the magnetic circuit:

* The reluctance of a magnetic circuit is the counterpart of electrical resistance, and its units are ampere – turns per weber

$\Phi = BA = \mu HA$ $\mathcal{F} \rightarrow$ magnetomotive force of circuit

$\Phi = \mu \left(\frac{Ni}{L_c} \right) A = Ni \left(\frac{\mu A}{L_c} \right)$ $\Phi \rightarrow$ flux of circuit, $\mathcal{R} \rightarrow$ reluctance

$\Phi = \mathcal{F} \left(\frac{\mu A}{L_c} \right) = \frac{\mathcal{F}}{\mathcal{R}}$ $H \rightarrow$ magnetic field intensity

$B = \mu H$

Linear DC Machine

* *the equation for the force on a wire in the presence of a magnetic field:*

$F = i(L \times B) \rightarrow F = iLB \sin \theta$

where $F \rightarrow$ force on wire, $i \rightarrow$ magnitude of current in wire, $B \rightarrow$ magnetic flux density vector
 $L \rightarrow$ length of wire. with direction of L defined to be in the direction of current flow

* the equation for the voltage induced on a wire moving in a magnetic field:

$$e_{ind} = (v \times B) \cdot L \rightarrow e_{ind} = (VB \sin \theta_1) L \cos \theta_2$$

where $e_{ind} \rightarrow$ voltage induced in wire, $v \rightarrow$ velocity of the wire, $B \rightarrow$ magnetic flux density vector, $L \rightarrow$ length of conductor in the magnetic field

* Kirchoff's voltage law for this machine


$$V_B - iR - e_{ind} = 0 \rightarrow V_B = e_{ind} + iR = 0$$

*Newton's law for the bar across the tracks:

$$F_{net} = ma$$

Linear DC Machine cases:

First case: (Ideal motor)

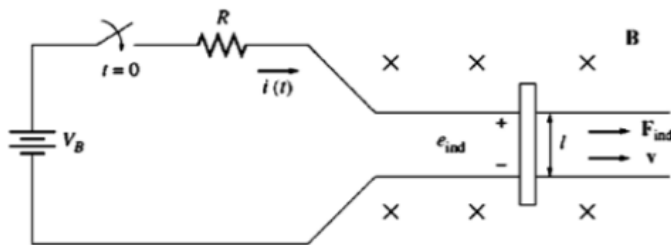

1. closing the switch produces a current flow $i = \frac{V_B}{R}$ (starting current)

2. the current flow produces an induced force on the bar given be

$$F_{ind} = iLB$$

3. The bar accelerates due to the induced force as $a = \frac{F_{ind}}{m} = \frac{\Delta v}{\Delta t}$


4. The bar moves to the right, producing an induced voltage $e_{ind} = vBL$ as it speeds up

5. This induced voltage reduces the current flow $i = (v_B - e_{ind} \uparrow)/R$

6. The induced force is thus decreased $F_{ind} = i \downarrow LB$ until eventually $F_{ind} = 0$ At that point. $e_{ind} = V_B$, $i = 0$, and the bar moves at a constant no – load speed

$v_{ss} = V_B/BL$ where $a = 0$ (note that $F_{ind} = 0$)

Second case: (real case of DC motor)

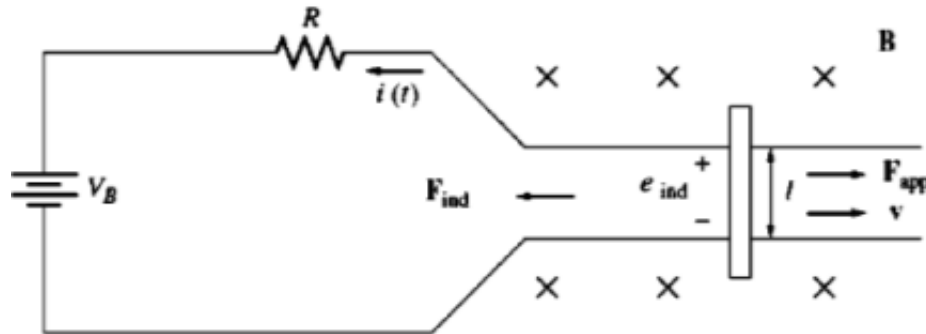

** if a force F_{load} is applied to the bar in OPPOSITE direction of motion hence the net force is $F_{net} = -F_{load}$ and the following events occur:*

1. The bar decelerates due to the load force as $a = F_{net}/m = \Delta v/\Delta t$ since $F_{net} < 0$
note that $F_{load} < F_{ind}$


2. The effect of this net force will reduce $e_{ind} = v \downarrow BL$ as the bar slows down

3. This induced voltage increases the current flow $i = (V_B - e_{ind} \downarrow)/R$

4. The induced force is thus increased $F = i \uparrow LB$ until $|F_{ind}| = |F_{load}|$ at a lower speed v

5. An amount of electric power equal to $e_{ind}i$ is now being converted to mechanical power equal to $F_{ind}v$, and the machine is acting as a motor.

Third case:

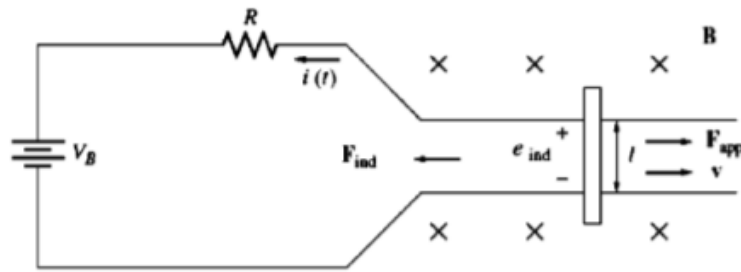


* If a force F_{app} is applied to the bar in the SAME direction of motion, hence the net force is $F_{net} = F_{app}$ and the following events occur:

1. The bar accelerates due to the load force as $a = F_{net}/m = \Delta v/\Delta t$ since $F_{net} > 0$
2. The effect of this net force will increase $e_{ind} = v \uparrow BL$ as the bar speeds up
3. This induced voltage reverses the direction of the current flow $i = (V_B - e_{ind})/R$ since $(V_B < e_{ind})$
4. The induced force is thus reverses its direction due to the reversed current $-F_{ind} = -iLB$ until $|F_{ind}| = |F_{app}|$. Note that $F_{net} = F_{app} - F_{ind}$ in this case
5. An amount of mechanical power equal to $F_{app}v$ is now being converted To electric power equal to $e_{ind}i$, and the machine is acting as a generator.

DC Machines-simple rotating loop

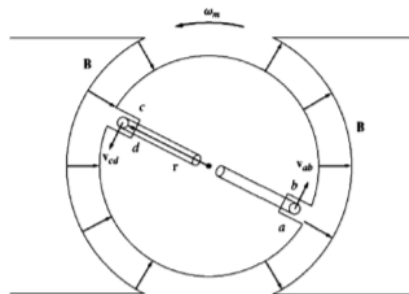- * If the rotor of this machine is rotated, a voltage will be induced in the wire loop.
- * To determine the total voltage e_{tot} on the loop, we need to examine each segment of the loop separately and sum all the resulting voltages. The voltage on each segment is given by



$$e_{ba} = (v \times B).L = \begin{cases} vBL & \text{positive into page under the pole face} \\ 0 & \text{beyond the pole edges} \end{cases} \dots(1)$$

$$e_{cb} = 0, \text{ because of thetas in sin and cos } \dots(2)$$


$$e_{dc} = (v \times B).L = \begin{cases} vBL & \text{positive out of page under the pole face} \\ 0 & \text{beyond the pole edges} \end{cases} \dots(3)$$

$$e_{ad} = 0, \text{ because of thetas in sin and cos } \dots(4)$$

The total induced voltage on the loop e_{ind} is given by:

$$e_{ind} = e_{ba} + e_{cb} + e_{dc} + e_{ad}$$
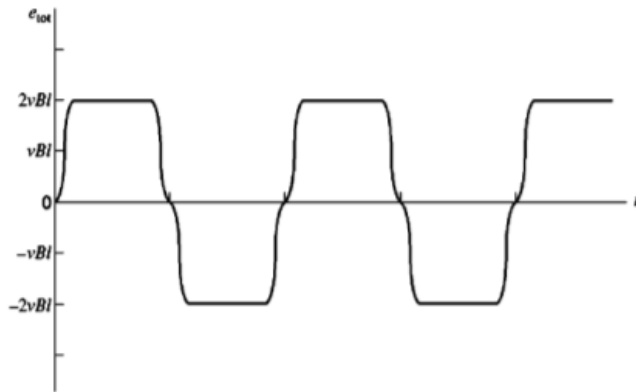
$$e_{ind} = \begin{cases} 2vBL & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \dots(5)$$



Given $v = r\omega$, $\Phi = A_p B$, and pole surface area of $A_p = \pi rL$, an alternative expression can be obtained.


$$e_{ind} = \begin{cases} 2r\omega BL & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases}$$

$$e_{ind} = \begin{cases} \frac{2}{\pi} A_p B \omega & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases}$$

$$e_{ind} = \begin{cases} \frac{2}{\pi} \Phi \omega & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \dots(6)$$

-This is for single loop (speed of rotor $\omega = \frac{V_B}{2rLB}$ when $V_B = e_{ind}$)

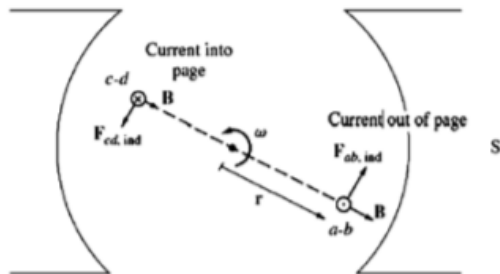* Suppose a battery is connected to the machine how the torque is developed inside it.(P11 in slides)



$$F_{ab} = i(L \times B) = iLB \text{ (tangent to direction of motion)...(7)}$$

The torque on the rotor caused by this force is

$$\tau_{ab} = rF \sin\theta = r(iLB) \sin 90^\circ = riLB \text{ CCW....(8)}$$

$$F_{bc} = i(L \times B) = 0 \text{ since } L \text{ is parallel to } B \text{....(9)}$$

$$\text{Therefore } \tau_{bc} = 0 \text{ (10)}$$

$$F_{cd} = i(L \times B) = iLB \text{ (tangent to direction of motion)(11)}$$

The torque on the rotor caused by this force is

$$\tau_{cd} = rF \sin\theta = r(iLB) \sin 90^\circ = riLB \text{ CCW....(12)}$$

$$F_{da} = i(L \times B) = 0 \text{ since } L \text{ is parallel to } B \text{....(13)}$$

$$\text{Therefore } \tau_{da} = 0 \text{ (14)}$$

* the resulting total induced torque on the loop is given by

$$\tau_{ind} = \tau_{ab} + \tau_{bc} + \tau_{cd} + \tau_{da}$$

$$\tau_{ind} = \begin{cases} 2riLB & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \text{....(15)}$$

By using $A_p \approx \pi rL$ and $\phi = A_p B$

$$\tau_{ind} = \begin{cases} \frac{2}{\pi} \phi i & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \text{....(16), } P = \tau \omega$$

this is in single loop if it's more than this $\frac{2}{\pi}$ will be represented as another constant(K)

Power flow and losses

* the copper losses for the armature and field windings are given by:

$$\text{Armature loss: } P_A = I_A^2 R_A$$

Where $P_A \rightarrow$ armature loss, $I_A \rightarrow$ armature current, $R_A \rightarrow$ armature resistance

$$\text{Field loss: } P_F = I_F^2 R_F$$


Where $P_F \rightarrow$ field circuit loss, $I_F \rightarrow$ field current, $R_F \rightarrow$ field resistance

* the brush losses it is given by the equation:

$$P_{BD} = V_{BD} I_A$$

where $P_{BD} \rightarrow$ brush drop loss, $V_{BD} \rightarrow$ brush voltage drop, $I_A \rightarrow$ armature current

Page(42 in slides)

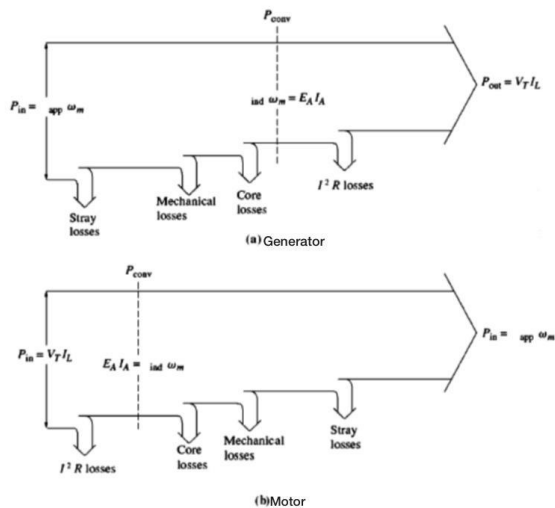

$$P_{conv} = \tau_{ind} \omega_m$$

$$P_{conv} = E_A I_A$$

* The efficiency of a DC machine is defined by the equation

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

$$\eta = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$$

DC Machines-Motors

* *the speed regulation (SR) of a motor is defined by*

$$SR = \frac{\omega_{nl} - \omega_{fl}}{\omega_{fl}} \times 100\% \quad (nl \rightarrow \text{no load}, fl \rightarrow \text{full load})$$

$$SR = \frac{n_{nl} - n_{fl}}{n_{fl}} \times 100\%$$

Separately Excited and Shunt DC Motors

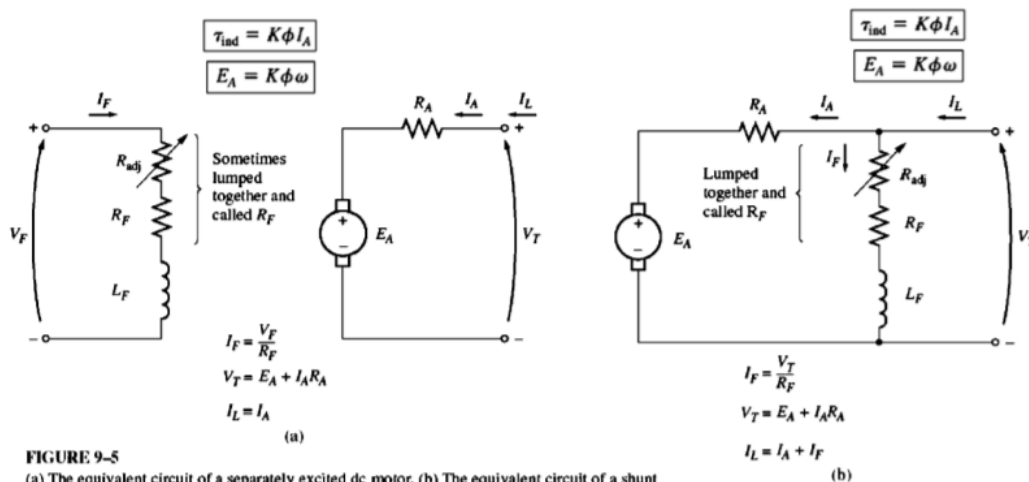


FIGURE 9-5
(a) The equivalent circuit of a separately excited dc motor. (b) The equivalent circuit of a shunt dc motor.

* *Speed of the motor* $\rightarrow \frac{E_A}{E_{A0}} = \frac{n}{n_0}$

#Changing the Field Resistor Control Method:

1. *Increasing R_F causes $I_F = (V_F/R_F \uparrow)$ to decrease.*
2. *Decreasing I_F decreases ϕ*
3. *Decreasing ϕ lowers $E_A = (K\phi \downarrow \omega)$.*
4. *Decreasing E_A increases $I_A = ((V_T - E_A \downarrow)/R_A)$*
5. *Increasing I_A increase $\tau_{ind} = (K\phi \downarrow I_A \uparrow)$, with the change in I_A dominant over the change in flux.*
6. *Increasing τ_{ind} makes $\tau_{ind} > \tau_{load}$, and the speed ω increases*
7. *Increasing ω increases $E_A = (K\phi\omega \uparrow)$ again.*

8. Increasing E_A decreases I_A

9. Decreasing I_A decreases τ_{ind} until $\tau_{ind} = \tau_{load}$ at a higher speed ω

#Changing the Armature Voltage Control Method

1. Increasing V_T increases $I_A = ((V_T \uparrow - E_A)/R_A)$

2. Increasing I_A increases $\tau_{ind} = (K\phi I_A \uparrow)$

3. Increasing τ_{ind} , makes $\tau_{ind} > \tau_{load}$ and the speed ω increases

4. Increasing ω increases $E_A = (K\phi\omega \uparrow)$

5. Increasing E_A decreases $I_A = ((V_T - E_A \uparrow)/R_A)$

6. Decreasing I_A decreases τ_{ind} until $\tau_{ind} = \tau_{load}$ at a higher speed ω

#Inserting a Resistor in Series with the Armature Circuit

1. Increasing R_A decreases $I_A = ((V_T - E_A)/R_A \uparrow)$

2. Decreasing I_A decreases $\tau_{ind} = (K\phi I_A \downarrow)$

3. decreasing τ_{ind} , makes $\tau_{ind} < \tau_{load}$ and the speed ω decreases

4. decreasing ω decreases $E_A = (K\phi\omega \downarrow)$

5. Decreasing E_A increases $I_A = ((V_T - E_A \downarrow)/R_A)$

6. Increasing I_A increases τ_{ind} until $\tau_{ind} = \tau_{load}$ at a lower speed ω

the internal generated voltage of a DC machine with its speed expressed in revolution per minute is given by

$$e_A = k' \phi n$$

the relationship between the speeds and internal generated voltages of the motor at two different conditions is thus

$$\frac{E_{A2}}{E_{A1}} = \frac{K' \phi n_2}{K' \phi n_1} \rightarrow n_2 = \frac{E_{A2}}{E_{A1}} n_1$$

The induced torque for any other load can be found from the fact $P_{conv} = E_A I_A = \tau_{ind} \omega \rightarrow$

$$\tau_{ind} = \frac{E_A I_A}{\omega}$$

the effective shunt field current of the motor is

$$I_F^* = I_F - \frac{\mathcal{F}_{AR}}{N_F}, \mathcal{F}_{AR} [A. \text{ turns}]$$

* If $E_{A1} = E_{A2}$ the equation of motor speed reduces as

$$1 = \frac{\Phi_2 n_2}{\Phi_1 n_1} \rightarrow n_1 = \frac{\Phi_1}{\Phi_2} n_2$$

Series DC Motors

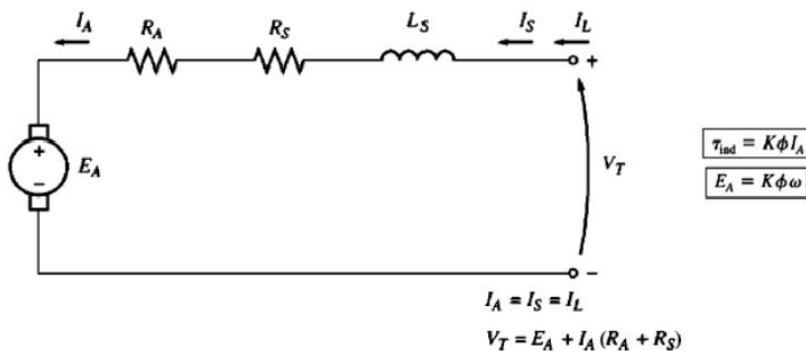


FIGURE 9-20
The equivalent circuit of a series dc motor.

* The output characteristic of series DC motors can be derived from the induced voltage and torque equations of the motor plus Kirchhoff's voltage law such as

$$\phi = c I_S = c I_A \text{ since } I_A = I_S \text{ then } \phi = c I_A$$

$$\text{Recall } \tau_{ind} = I_A K \phi = c K I_A^2 \Rightarrow \tau_{ind} \propto I_A^2$$

$$\text{Note that } I_A = \sqrt{\frac{\tau_{ind}}{cK}} \text{ and } \phi = c \sqrt{\frac{\tau_{ind}}{cK}} = \sqrt{\frac{c \tau_{ind}}{K}}$$


$$V_T = E_A + I_A(R_A + R_S) = K\phi\omega + I_A(R_A + R_S)$$

* The output characteristic of series DC motors can be derived from the induced voltage and torque equations of the motor plus Kirchhoff's voltage law such as

$$V_T = K \sqrt{\frac{c\tau_{ind}}{K}} \omega + \sqrt{\frac{\tau_{ind}}{cK}} (R_A + R_S) \Rightarrow \omega = \frac{V_T}{\sqrt{cK}} \frac{1}{\sqrt{\tau_{ind}}} - \frac{(R_A + R_S)}{cK}$$

#Transformers:

*Ideal transformer

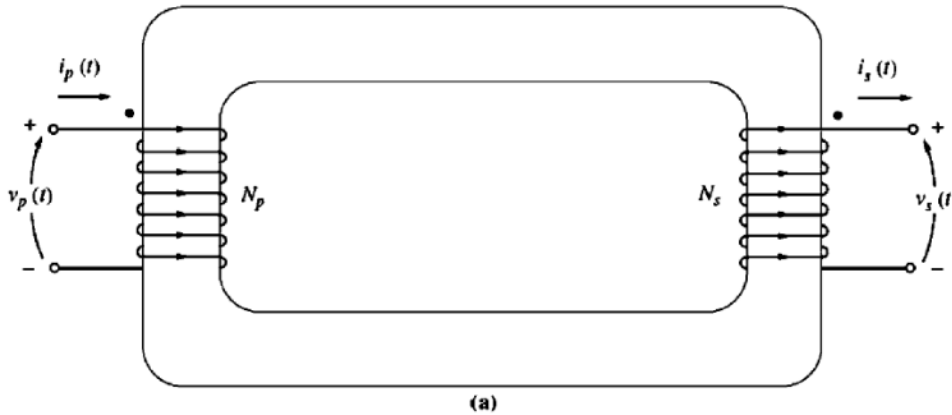

(a)
FIGURE 2-4
(a) Sketch of an ideal transformer.

* Faraday's law of induction


$$\varepsilon = -N \frac{\Delta\Phi_B}{\Delta t}$$

ε : induced emf, N : number of loops, $\Delta\Phi/\Delta t$: rate of change of flux with time
minus sign from lenz's law


* Lenz's Law


The induced B field in a loop of wire will **oppose the change in magnetic flux** through the loop.

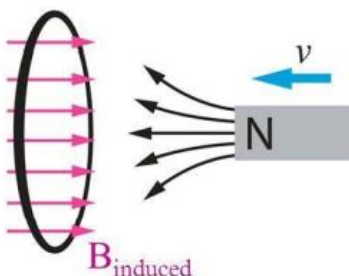If you try to **increase** the flux through a loop, the induced field will oppose that increase!



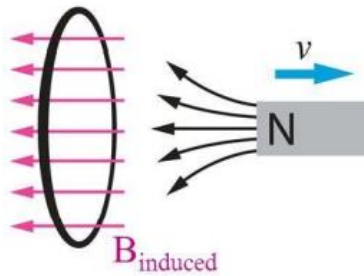If you try to **decrease** the flux through a loop, the induced field will replace that decrease!



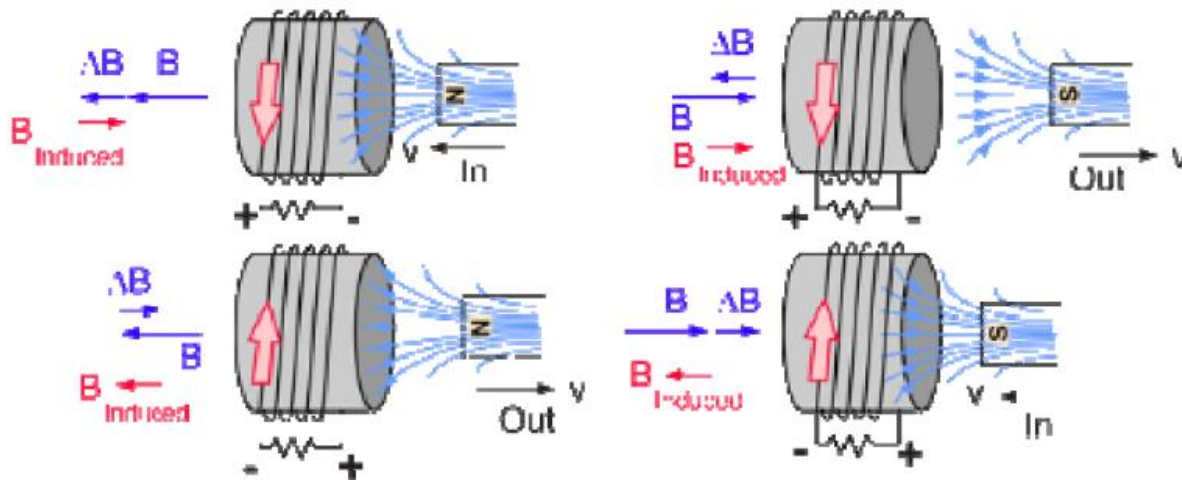

* Since the magnetomotive forces are equal in primary and secondary windings

$$\mathcal{F}_P = \Phi \mathcal{R} = \mathcal{F}_S \rightarrow N_P i_P = N_S i_S \rightarrow \frac{N_P}{N_S} = \frac{i_S}{i_P} = a$$

where a is the **transformer turns ratio**

* From faraday's laws

V is proportional to N ($V \propto N$)

$$\frac{V_P}{V_S} = \frac{N_P}{N_S} = a$$

$$* V_P i_P = V_S i_S \rightarrow S_{in} = S_{out}$$

$$* P_{in} = V_P i_P(\theta_P), * P_{out} = V_S i_S(\theta_S)$$

* since $V_P i_P = V_S i_S$ and since voltage and current angles are unaffected by an ideal transformer then $\theta_P = \theta_S$

* The primary and secondary windings of an ideal transformer have the same

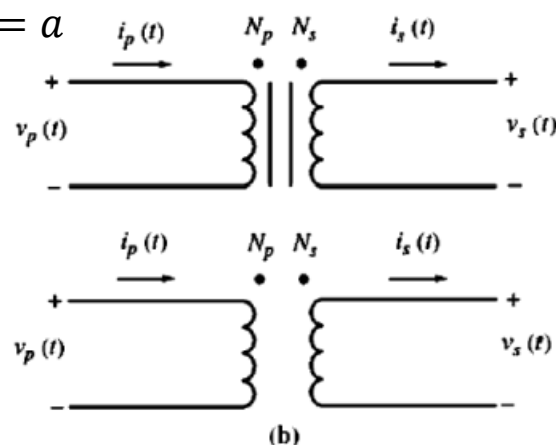


FIGURE 2-4

(b) Schematic symbols of a transformer.

power factor then $P_{in} = P_{out}$ and then $Q_{in} = Q_{out}$

#If $N_P < N_S \rightarrow V_P < V_S \rightarrow i_P > i_S$ (step – up transformer)

#If $N_P > N_S \rightarrow V_P > V_S \rightarrow i_P < i_S$ (step – down transformer)

* The impedance of a device or an element is defined as the ratio of the phasor Voltage across it to the phasor current flowing through it

$$Z_L = \frac{V_L}{I_L}$$

$$* Z'_L = \frac{V_P}{I_P} = \frac{aV_S}{I_S/a} = a^2 \frac{V_S}{I_S}$$

$$\rightarrow Z'_L = a^2 Z_L$$

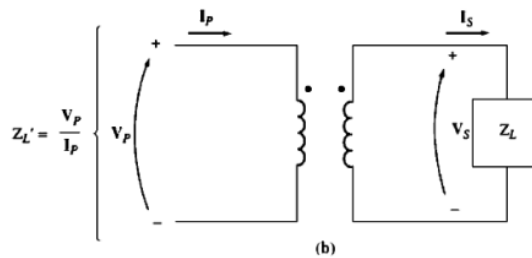
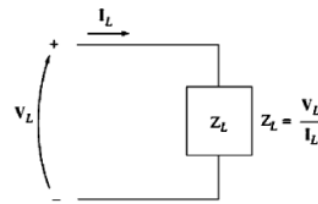


FIGURE 2-5 (a) Definition of impedance. (b) Impedance scaling through a transformer.

$$* I_{line} = \frac{V}{Z_{line} + Z_{load}}, V_{load} = I_{line} Z_{load}, P_{loss} = (I_{line})^2 R_{line}, Z_{eq} = Z_{line} + Z'_{load}$$

#Operation of real transformer

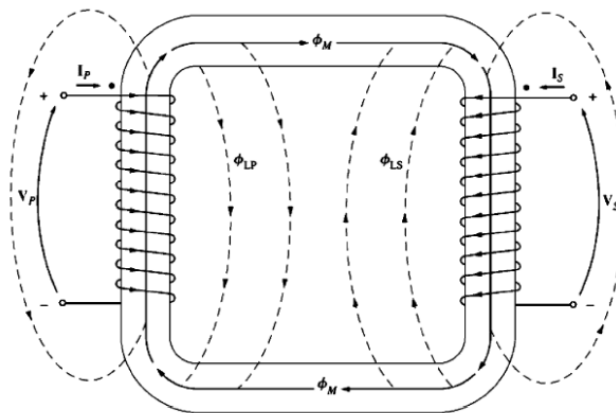


FIGURE 2-10 Mutual and leakage fluxes in a transformer core.

#The questions about this case will be concept questions

* The flux in the primary coil of the transformer can thus be divided into two components: a mutual flux, which remains in the core and links both windings, and a small leakage flux, which passes through the primary winding but returns through the air, bypassing the secondary winding:

$$\bar{\Phi}_P = \Phi_M + \Phi_{LP}$$

$\bar{\Phi}_P$: total average primary flux, Φ_M : flux component linking both primary and secondary coils,
 Φ_{LP} : primary leakage flux

* There is a similar division of flux in the secondary winding between mutual flux and leakage flux which passes through the secondary winding but returns through the air, by passing the primary winding:

$$\bar{\Phi}_S = \Phi_M + \Phi_{LS}$$

$\bar{\Phi}_S$: total average secondary flux, Φ_M : flux component linking both primary and secondary coils,
 Φ_{LS} : secondary leakage flux

* Since in a well designed transformer $\Phi_M \gg \Phi_{LP}$ and $\Phi_M \gg \Phi_{LS}$ the ratio of the total voltage on the primary of a transformer to the total voltage on the secondary of a transformer is approximately

* The smaller the leakage fluxes of the transformer are, the closer the total transformer voltage ratio approximates that of the ideal transformer

$$\frac{v_P(t)}{v_S(t)} = \frac{N_P}{N_S} = a$$

* *Open – circuit test:*

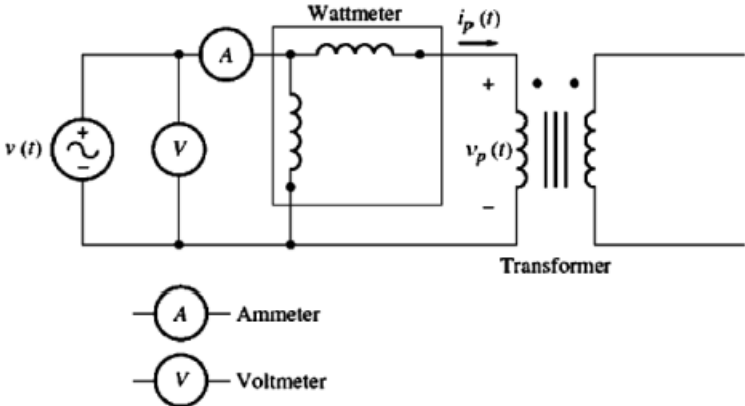


FIGURE 2-19
 Connection for transformer open-circuit test.

- The conductance of the core – loss resistor is given by

$$G_c = \frac{1}{R_c}$$

- The susceptance of the magnetizing inductor is given by

$$B_M = \frac{1}{X_M}$$

- Since these two elements are in parallel, their admittances add, and the total excitation admittance is

$$Y_E = G_c - jB_M$$

$$Y_E = \frac{1}{R_c} - j\frac{1}{X_M}$$

- the following relations can be obtained

$$|Y_E| = \frac{I_{oc}}{V_{oc}}$$

$$PF = \cos(\theta) = \frac{P_{oc}}{V_{oc}I_{oc}} \Rightarrow \theta = \cos^{-1}\left(\frac{P_{oc}}{V_{oc}I_{oc}}\right)$$

$$Y_E = \frac{I_{oc}}{V_{oc}} \angle -\theta \Rightarrow Y_E = \frac{I_{oc}}{V_{oc}} \angle -\cos^{-1}(PF)$$

$$R_c = \frac{1}{G_c} = \frac{1}{Y_E \cos(\theta)}$$

$$X_M = \frac{1}{B_M} = \frac{1}{Y_E \sin(\theta)}$$

* *Short – circuit test:*

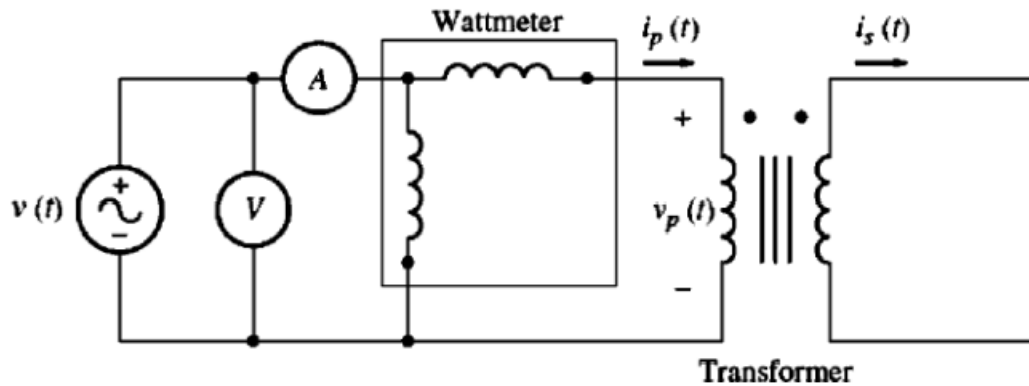


FIGURE 2-20
Connection for transformer short-circuit test.

◦ The magnitude of the series impedances referred to the primary side of the transformer is

$$|Z_{SE}| = \frac{V_{sc}}{I_{sc}}$$

◦ *The following relations can be obtained*

$$PF = \cos(\theta) = \frac{P_{sc}}{V_{sc}I_{sc}} \Rightarrow \theta = \cos^{-1}\left(\frac{P_{sc}}{V_{sc}I_{sc}}\right)$$


$$Z_{SE} = \frac{V_{sc} \angle 0}{I_{sc} \angle -\theta} = \frac{V_{sc}}{I_{sc}} \angle \theta$$

$$R_{eq} = Z_{SE} \cos(\theta)$$

$$X_{eq} = Z_{SE} \sin(\theta)$$

$$\underline{Z_{SE} = R_{eq} + jX_{eq} = (R_P + a^2R_S) + j(X_P + a^2X_S)}$$

* DC test:

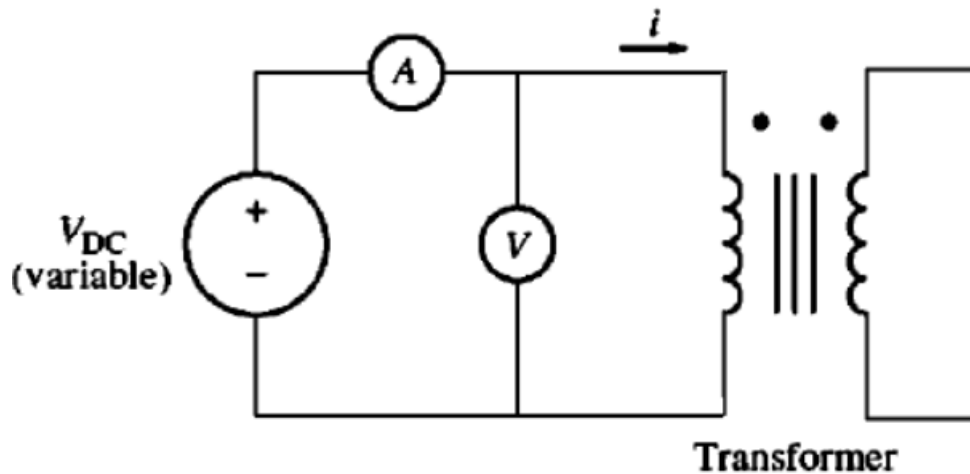

- Using Ohm's law and measurements of voltage and current, the internal resistor of the winding can be determined as

$$R = V / I$$

- It should be noted that this test can be done on both sides of the transformer
- Moreover, the DC power supply should be adjusted so that maximum DC current is not exceeded.
- **Note that the coil can handle a DC current that is certainly less than the rated AC current.**

* **Voltage regulation (VR)**

$$VR = \frac{V_{S.nl} - V_{S.fl}}{V_{S.fl}} \times 100\%$$

$$VR = \frac{V_P/a - V_{S.fl}}{V_{S.fl}} \times 100\%$$

$$\circ \frac{V_P}{a} = V_S + R_{eq}I_S + jX_{eq}I_S$$

* **Efficiency**

Transformers are also compared and judged on their efficiencies. The efficiency of a device is defined by the equation

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

$$\eta = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$$

To calculate the efficiency of a transformer at a given load, just add the losses the equation of efficiency such that


$$P_{out} = V_S I_S \cos\theta_S$$

$$\eta = \frac{V_S I_S \cos\theta_S}{P_{Cu} + P_{core} + V_S I_S \cos\theta_S} \times 100\%$$

$$P_{Cu} = (I_S)^2 R_{eq}$$

$$P_{core} = \frac{(V_P/a)^2}{R_C}$$

#Autotransformer:

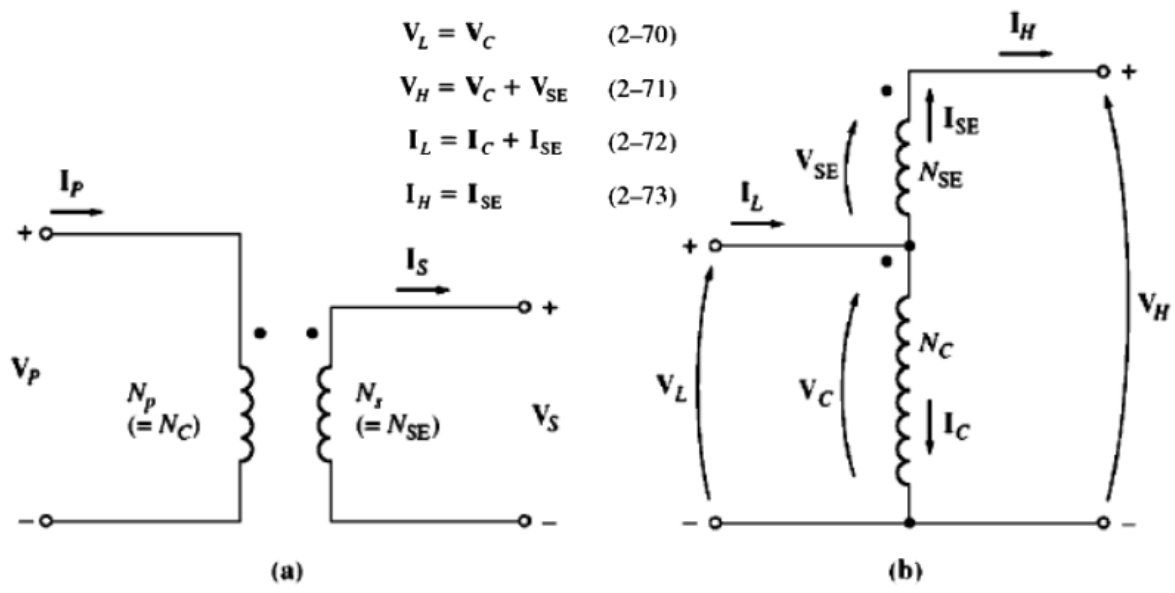


$$V_L = V_C \quad (2-70)$$

$$V_H = V_C + V_{SE} \quad (2-71)$$

$$I_L = I_C + I_{SE} \quad (2-72)$$

$$I_H = I_{SE} \quad (2-73)$$

FIGURE 2-32
A transformer with its windings (a) connected in the conventional manner and (b) reconnected as an autotransformer.

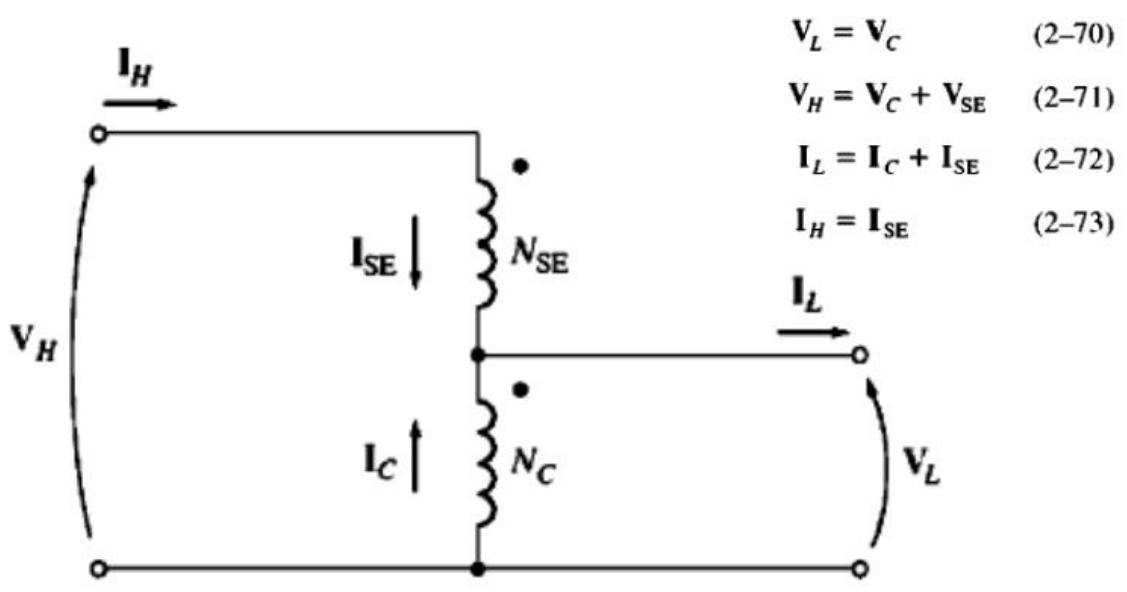

$$V_L = V_C \quad (2-70)$$

$$V_H = V_C + V_{SE} \quad (2-71)$$

$$I_L = I_C + I_{SE} \quad (2-72)$$

$$I_H = I_{SE} \quad (2-73)$$

FIGURE 2-33
A step-down autotransformer connection.

*Voltage relationship:

$$V_H = V_C + V_{SE} \text{ But } V_C/V_{SE} = N_C/N_{SE}, \text{ so } \rightarrow$$

$$V_H = V_C + \frac{N_{SE}}{N_C} V_C, \text{ noting that } V_L = V_C \text{ then we get } \rightarrow$$

$$V_H = V_L + \frac{N_{SE}}{N_C} V_L = \frac{N_{SE} + N_C}{N_C} V_L \rightarrow$$

$$\frac{V_L}{V_H} = \frac{N_C}{N_{SE} + N_C}$$

*Current relationship:

$$I_L = I_C + I_{SE}, \text{ also } I_C = (N_{SE}/N_C)I_{SE}, \text{ so } \rightarrow$$

$$I_L = \frac{N_{SE}}{N_C} I_{SE} + I_{SE}, \text{ Noting that } I_H = I_{SE}, \text{ then we get } \rightarrow$$

$$I_L = \frac{N_{SE}}{N_C} I_H + I_H = \frac{N_{SE} + N_C}{N_C} I_H \rightarrow$$

$$\frac{I_L}{I_H} = \frac{N_{SE} + N_C}{N_C}$$

*Apparent Power Rating Advantage

$$S_{in} = V_L I_L \text{ and } S_{out} = V_H I_H$$

$$S_{in} = S_{out} = S_{IO}$$

$$S_W = V_C I_C = V_{SE} I_{SE}$$

$$S_W = V_C I_C = V_L (I_L - I_H) = V_L I_L - V_L I_H$$

$$S_W = V_L I_L - V_L I_L \left(\frac{N_C}{N_{SE} + N_C} \right) = V_L I_L \left(1 - \frac{N_C}{N_{SE} + N_C} \right)$$

$$S_W = V_L I_L \left(\frac{N_{SE} + N_C - N_C}{N_{SE} + N_C} \right) = S_{IO} \left(\frac{N_{SE}}{N_{SE} + N_C} \right)$$

* Therefore, the ratio of the apparent power in the primary and secondary of the autotransformer to the apparent power actually traveling through its windings is

$$\frac{S_{IO}}{S_W} = \frac{N_{SE} + N_C}{N_{SE}} > 1$$

#Three-Phase Transformers (Connection)

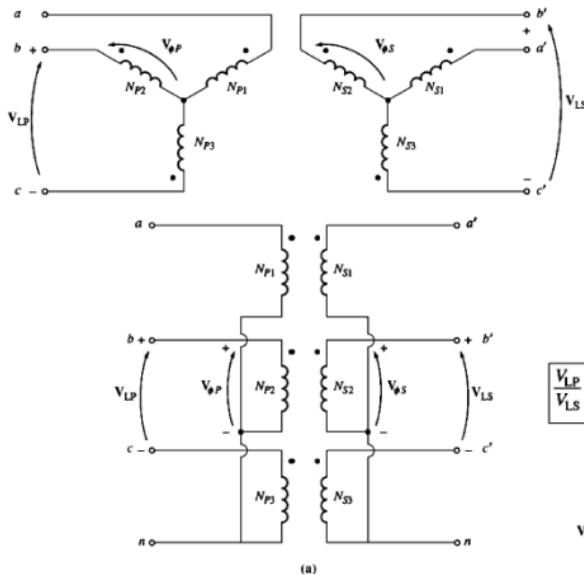


FIGURE 2-38
Three-phase transformer connections and wiring diagrams: (a) Y-Y

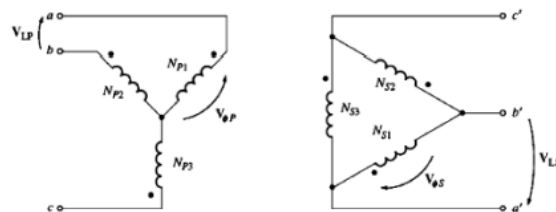


FIGURE 2-38
(b) Y-Delta (continued)

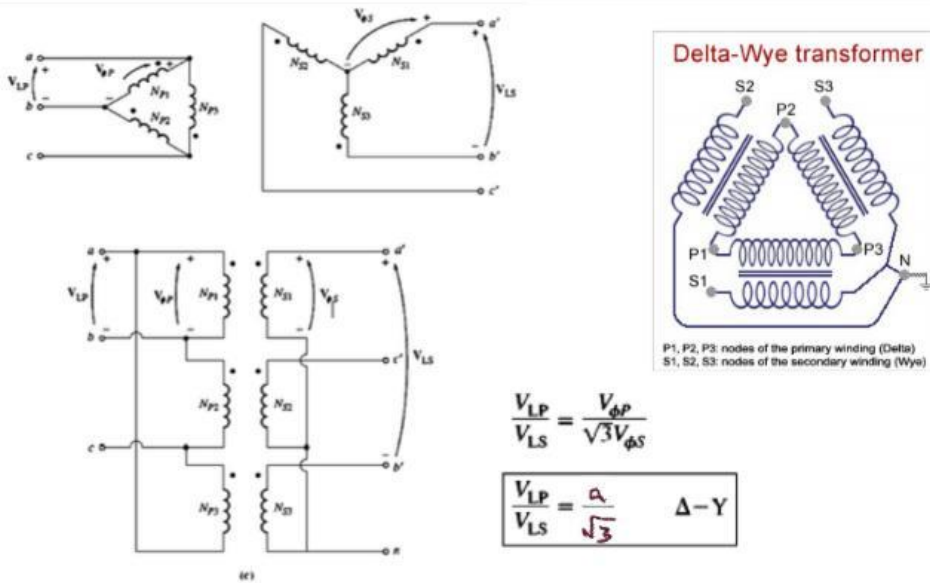


FIGURE 2-38
(c) Δ -Y (continued)

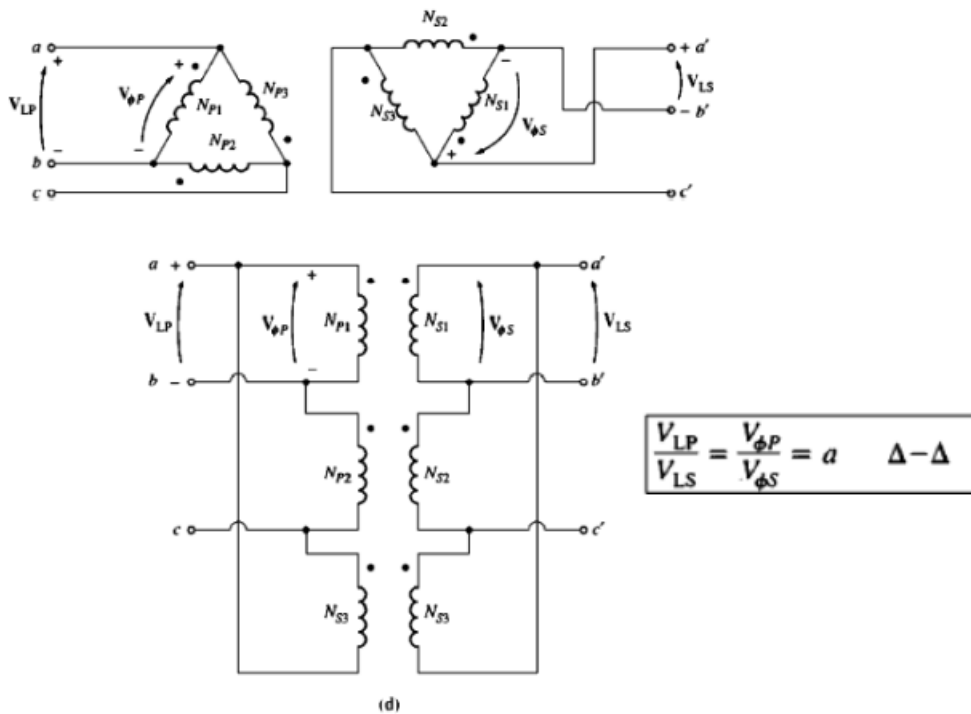


FIGURE 2-38
(d) Δ - Δ (concluded)

- * The impedance, voltage regulation, efficiency, and similar calculations for three – phase transformers are done on a per – phase basis, using exactly the same techniques already developed for single – phase transformers.

*Basic Concepts of Operation

The speed of the magnetic field's rotation is given by

$$n_{sync} = \frac{120f_e}{P}, f_e: \text{system frequency in hertz}, P: \text{num of poles}$$

The voltage induced in a given rotor bar is given by the equation

$$e_{ind} = (v \times B) \cdot l$$

v: the velocity of the bar relative to the magnetic field,

B: the magnetic flux density vector,

l: the length of conductor in the magnetic field

The induced torque in the machine is given by

$$\tau_{ind} = kB_R \times B_S$$

Note that $k = K/\mu$ and K is a constant dependent on the construction of the machine

In fact, the parameter k will not be constant since μ varies with the amount of magnetic saturation in the machine.

Two terms are commonly used to define the relative motion of the rotor and the magnetic fields

(1) One is slip speed, defined as the difference between synchronous speed and rotor speed:

$$n_{slip} = n_{sync} - n_m$$

n_{slip} : the slip speed of the machine, n_{sync} : the speed of the rotating magnetic fields,

n_m : the mechanical shaft speed of motor

(2) The other is term used to describe the relative motion is slip, which is the relative speed expressed on a percentage basis, and it is defined as

$$s = \frac{n_{slip}}{n_{sync}} \times 100\% \rightarrow s = \frac{n_{sync} - n_m}{n_{sync}} \times 100\% \rightarrow s = \frac{\omega_{sync} - \omega_m}{\omega_{sync}} \times 100\%$$

*If the rotor turns at synchronous speed $s = 0$, while if the rotor is stationary $s = 1$.

* It is possible to express the mechanical speed of the rotor shaft in terms of synchronous speed and slip.

By Solving the previous Equations for mechanical speed yields

$$n_m = (1 - s)n_{sync}$$

$$\omega_m = (1 - s)\omega_{sync}$$

* At $n_m = 0$ r/min the rotor frequency $f_r = f_e$ and the slip $s = 1$.

* At $n_m = n_{sync}$ the rotor frequency $f_r = 0$ Hz and the slip $s = 0$

* Based on the definition of the slip, the rotor frequency can be expressed as

$$f_r = sf_e$$

*From the previous equations:

$$f_r = \frac{n_{sync} - n_m}{n_{sync}} f_e, \text{ but } n_{sync} = 120f_e/P \text{ so } \rightarrow$$

$$f_r = (n_{sync} - n_m) \frac{P}{120f_e} f_e \rightarrow f_r = \frac{P}{120} (n_{sync} - n_m)$$

*Equivalent Circuit

—magnitude of the induced voltage at any slip will be given by the equation

$$E_R = sE_{RO}$$

—The frequency of the induced voltage at any slip will be given by the equation


$$f_r = sf_e$$

—The reactance of an induction motor rotor depends on the inductance of the rotor and the frequency of the voltage and current in the rotor. With a rotor

inductance of L_R , the rotor reactance is given by

$$X_R = \omega_r L_R = 2\pi f_r L_R \rightarrow X_R = 2\pi s f_e L_R = s(2\pi f_e L_R) = sX_{RO}$$

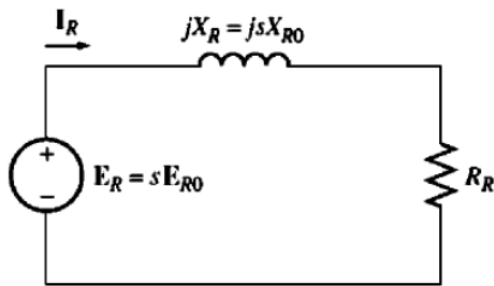Where X_{RO} is the blocked – rotor rotor reactance.



$$I_R = \frac{E_R}{R_R + jX_R}$$

$$I_R = \frac{E_R}{R_R + jsX_{R0}} \quad (7-12)$$

$$I_R = \frac{E_{R0}}{R_R/s + jX_{R0}} \quad (7-13)$$

FIGURE 7-9
The rotor circuit model of an induction motor.

$$Z_{R,eq} = R_R/s + jX_{R0}$$

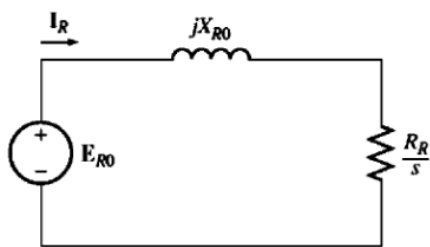


FIGURE 7-10
The rotor circuit model with all the frequency (slip) effects concentrated in resistor R_R .

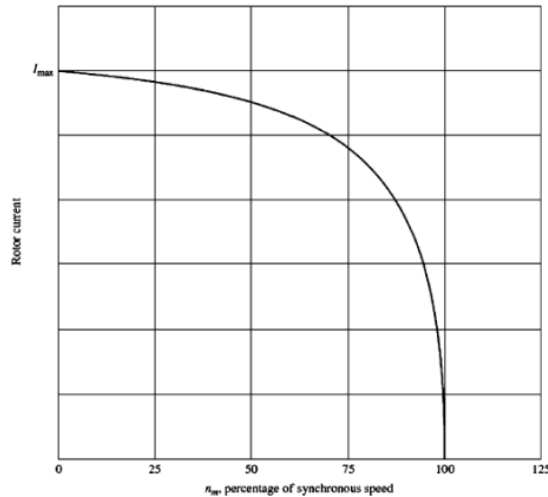


FIGURE 7-11
Rotor current as a function of rotor speed.

—In an ordinary transformer, the voltages, currents, and impedances on the secondary side of the device can be referred to the primary side by means of the turns ratio of the transformer:

$$V_P = V'_S = aV_S$$

$$I_P = I'_S = \frac{I_S}{a}$$

$$Z'_S = a^2Z_S$$

—If the effective turns ratio of an induction motor is a_{eff} , then the transformed rotor voltage becomes

$$E_1 = E'_R = a_{eff}E_{R0}$$

$$I_2 = \frac{I_R}{a_{eff}}$$

$$Z_2 = a^2_{eff} \left(\frac{R_R}{s} + jX_{RO} \right)$$

$$R_2 = a^2_{eff} R_R$$

$$X_2 = a^2_{eff} X_{RO}$$

—The efficiency of an AC machine is defined by the equation

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

$$\eta = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$$

$$P_{in} = \sqrt{3} V_T I_L \cos \theta$$

$$P_{out} = \tau_{load} \omega_m$$

- From the equivalent circuit of an induction motor and power flow diagram, the following relations can be obtained

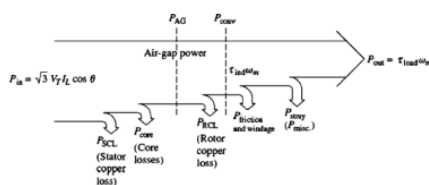


FIGURE 7-13
The power-flow diagram of an induction motor.

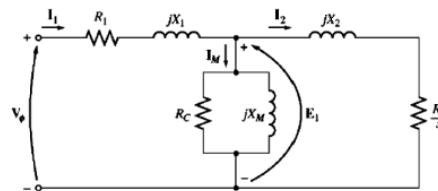


FIGURE 7-12
The per-phase equivalent circuit of an induction motor.

$$I_1 = \frac{V_\phi}{Z_{eq}} \quad (7-23)$$

where

$$Z_{eq} = R_1 + jX_1 + \frac{1}{G_C - jB_M + \frac{1}{V_2/s + jX_2}} \quad (7-24)$$

$$P_{SCL} = 3I_1^2 R_1$$

$$P_{core} = 3E_1^2 G_C$$

$$P_{AG} = P_{in} - P_{SCL} - P_{core}$$

$$P_{AG} = 3I_2^2 \frac{R_2}{s}$$

$$P_{RCL} = 3I_R^2 R_R$$

$$P_{RCL} = 3I_2^2 R_2$$

$$\begin{aligned} P_{conv} &= P_{AG} - P_{RCL} \\ &= 3I_2^2 \frac{R_2}{s} - 3I_2^2 R_2 \\ &= 3I_2^2 R_2 \left(\frac{1}{s} - 1 \right) \end{aligned}$$

$$P_{conv} = 3I_2^2 R_2 \left(\frac{1-s}{s} \right)$$

$$P_{RCL} = s P_{AG}$$

$$\begin{aligned} P_{conv} &= P_{AG} - P_{RCL} \\ &= P_{AG} - s P_{AG} \end{aligned}$$

$$P_{conv} = (1-s) P_{AG}$$

$$P_{out} = P_{conv} - P_{F\&W} - P_{misc}$$

$$\tau_{ind} = \frac{P_{conv}}{\omega_m}$$

$$\tau_{ind} = \frac{(1-s) P_{AG}}{(1-s) \omega_{sync}}$$

$$\tau_{ind} = \frac{P_{AG}}{\omega_{sync}}$$

Developed Torque

*Torque-Speed Characteristic

From utilizing the induction motor equivalent circuit and applying Thevenin theorem, the torque-speed characteristic curve can be obtained

$$\tau_{ind} = \frac{3V_{TH}^2 R_2 / s}{\omega_{sync} [(R_{TH} + R_2/s)^2 + (X_{TH} + X_2)^2]}$$

$$V_{TH} \approx V_{\phi} \frac{X_M}{X_1 + X_M}$$

$$R_{TH} \approx R_1 \left(\frac{X_M}{X_1 + X_M} \right)^2$$

$$X_{TH} \approx X_1$$

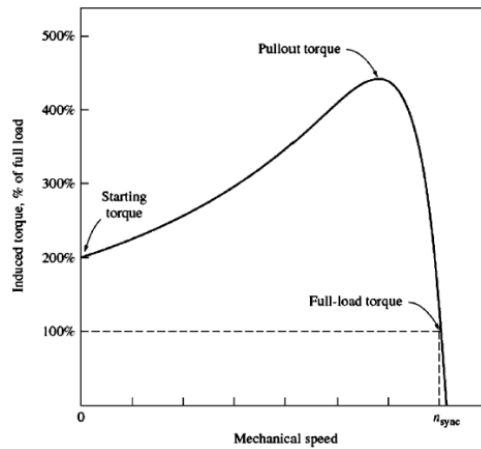


FIGURE 7-19 A typical induction motor torque-speed characteristic curve.

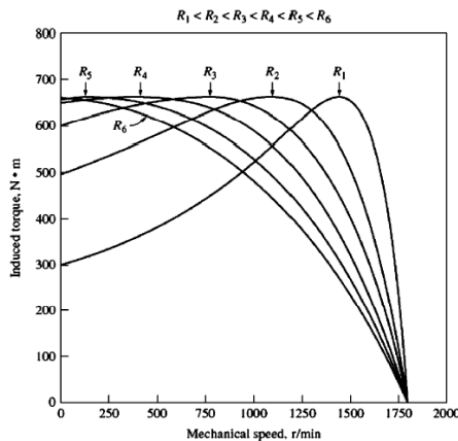


FIGURE 7-22 The effect of varying rotor resistance on the torque-speed characteristic of a wound-rotor induction motor.

$$s_{max} = \frac{R_2}{\sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}}$$

$$\tau_{max} = \frac{3V_{TH}^2}{2\omega_{sync} [R_{TH} + \sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}]}$$

Curves that represent the characteristics of induction motors

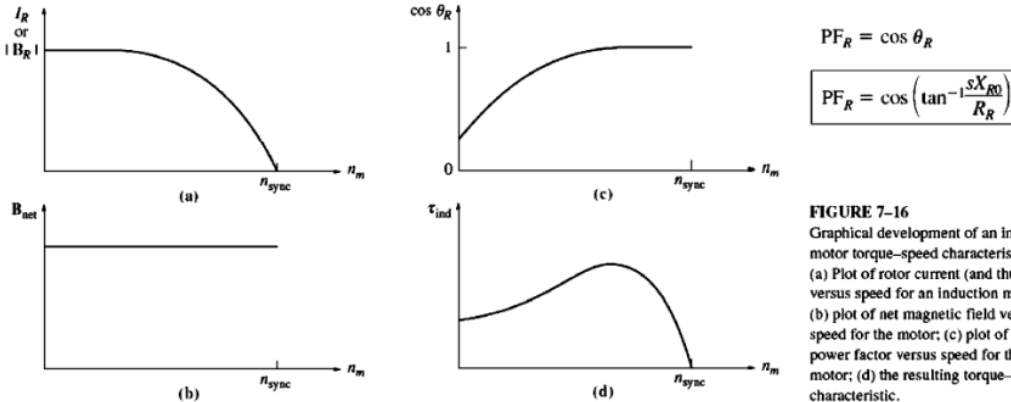


FIGURE 7-16
Graphical development of an induction motor torque–speed characteristic. (a) Plot of rotor current (and thus $|B_R|$) versus speed for an induction motor; (b) plot of net magnetic field versus speed for the motor; (c) plot of rotor power factor versus speed for the motor; (d) the resulting torque–speed characteristic.

*Generators

Separately Excited DC Generators

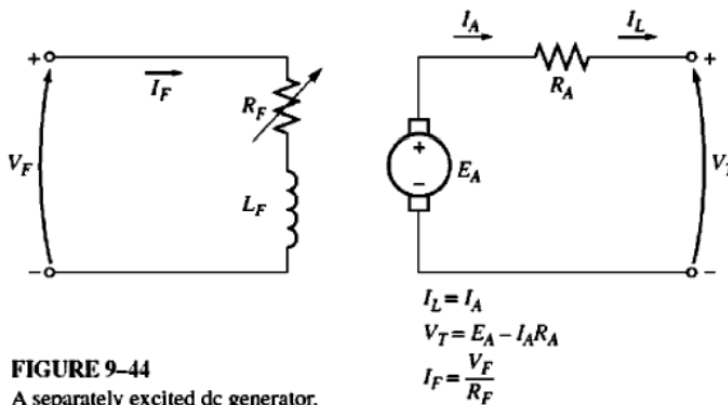


FIGURE 9-44
A separately excited dc generator.

For a constant speed $V_T = E_A - I_A R_A$ (9-41)

- ▶ Since the internal generated voltage E_A is given by the equation $E_A = K\phi\omega$, there are two possible ways to control the voltage of this generator:
 1. **Change the speed:** If ω increases, then $E_A = K\phi\omega$ increases, so $V_T = E_A - I_A R_A$ increases too.
 2. **Change the field current:** If R_F is decreased, then the field current increases ($I_F = V_F/R_F$). Therefore, the flux ϕ in the machine increases. As the flux rises, $E_A = K\phi\omega$ must rise too, so $V_T = E_A - I_A R_A$ increases.
- ▶ In many applications, the speed range of the prime mover is quite limited, so the terminal voltage is most commonly controlled by changing the field current.

—Voltage regulation (VR) is defined by the equation

$$VR = \frac{V_{nl} - V_{fl}}{V_{fl}} \times 100\%$$

—The total magnetomotive force in a separately excited generator is the field circuit magnetomotive force less the magnetomotive force due to armature reaction (AR):

$$\mathcal{F}_{net} = N_F I_F - \mathcal{F}_{AR}$$

—The equivalent field current of a separately excited DC generator is given by

$$I_F^* = I_F - \frac{\mathcal{F}_{AR}}{N_F}$$

—the difference between the speed of the magnetization curve and the real speed of the generator must be taken into account:

$$\frac{E_A}{E_{AO}} = \frac{n}{n_0}$$