



تقدم لجنة

ملخص لمادة:

آلات كهربائية

جزيل الشكر للطالب:




حمزة اسماعيل



* Electrical Machines :-

* Introduction to Electrical Machines :-

* Electromechanical energy converter

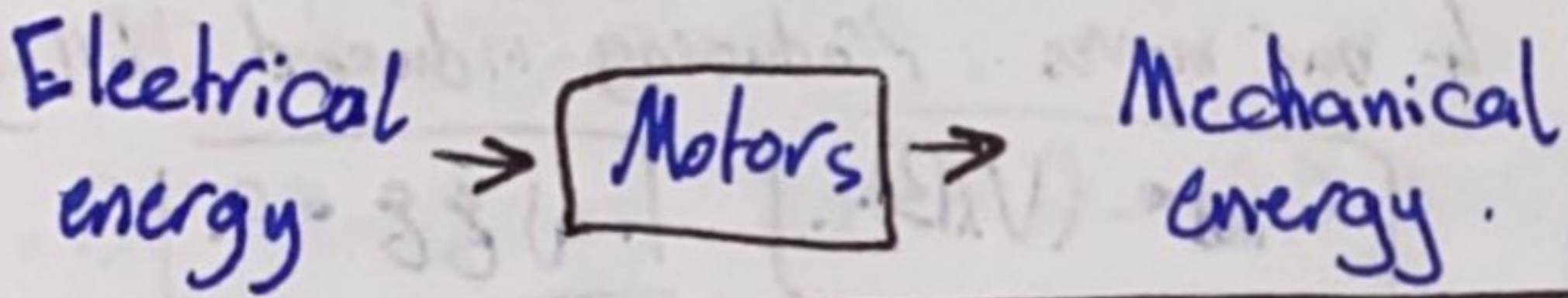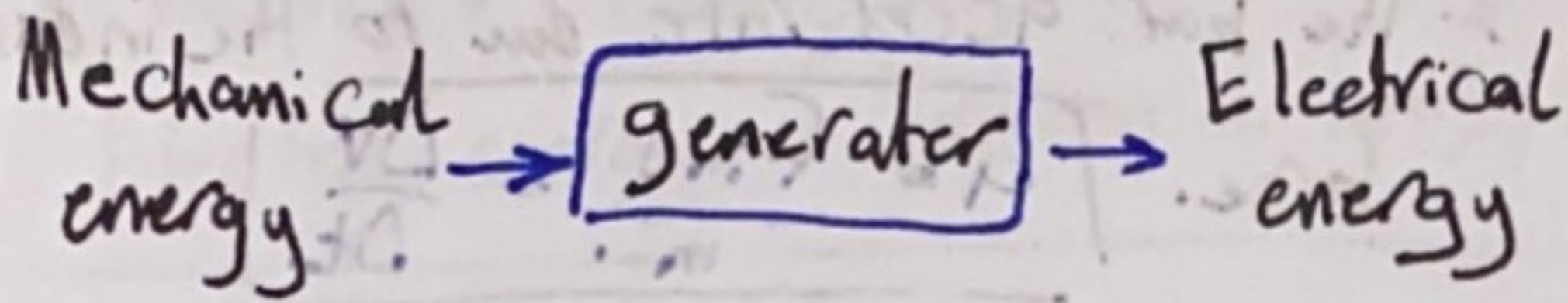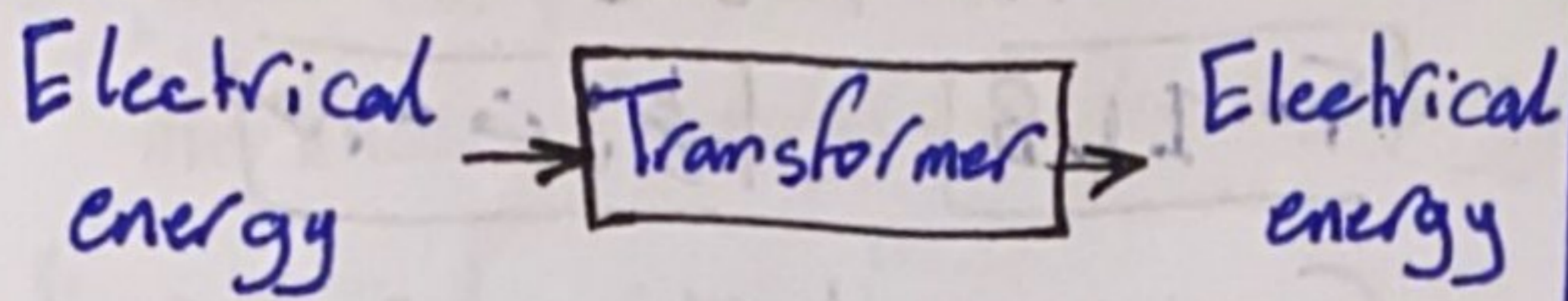

* Conversions :-

$$1 \text{ rpm} = \frac{2\pi \text{ (rad)}}{60 \text{ (sec)}} = \frac{\pi}{30} \text{ [r/s]}$$

$$1 \text{ [rpm]} = \frac{\pi}{30} \text{ [r/s]} \quad ; \quad 1 \text{ [r/s]} = \frac{30}{\pi} \text{ [rpm]}$$

$$1 \text{ hp} = 746 \text{ Watt}$$

* Electrical and Mechanical Power :-

1. Mechanical Power :-

$$\text{Power [W]} = \text{Torque [N.m]} * \text{Speed [r/s]}$$

2. Electrical Power :-

→ DC Machine :-

$$\text{Power [W]} = \text{Current [A]} * \text{Voltage [V]}$$

→ AC Machine : θ :-

$$\text{Active Power [W]} = \text{Current} * \text{Voltage} * \cos\theta$$

Power factor ←

→ AC Machine - 3ϕ :-

$$\text{Power [W]} = \sqrt{3} \text{ line Current [A]} * \text{line Voltage [V]} * \cos\theta$$

$$\text{Power [W]} = 3 * \text{Phase Current [A]} * \text{Phase Voltage [V]} * \cos\theta$$

$$V_L = \sqrt{3} V_P$$

$$I_L = \sqrt{3} I_P$$

* Principles how magnetic fields are used in these devices :-

1. Current carrying wire produces a magnetic field in area around it.
التيار الكهربي ينتج مجال مغناطيسي حوله

2. time changing magnetic field induced a Voltage in a coil of wire.
(basis of Transformer action)

تغير المجال المغناطيسي ينتج فرقاً كهربائياً على طرفي الملف

3. Current carrying wire in magnetic field has a force induced on it.
(basis of motor action)

التيار الكهربي في مجال مغناطيسي يتأثر بقوة


4. moving wire in a magnetic field has a Voltage induced in it.
(basis of generator action)

تحريك سلك في مجال مغناطيسي ينتج فرقاً كهربائياً

* Magnetic Circuits :-

$$\Phi = BA = \frac{\mu NI A}{L_c}$$

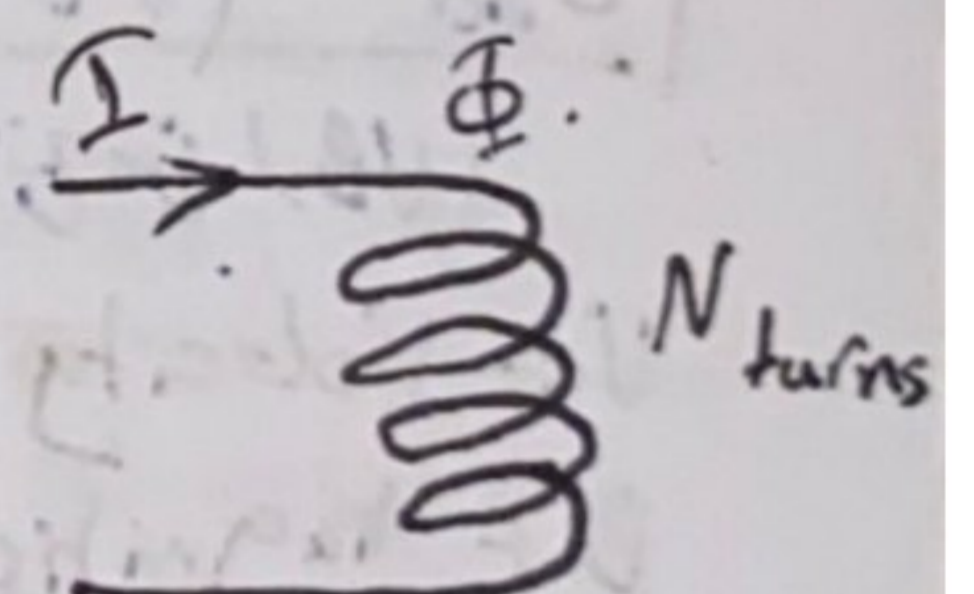↳ total flux (weber) magnetic field density (Tesla).
 μ : permeability



$$\Phi = BA = \mu H A$$

↳ magnetic field Intensity

$$\Phi = NI \left(\frac{\mu A}{L_c} \right) = \frac{F}{R}$$

↳ magnetomotive force
↳ Reluctance.

$$\Phi = \frac{F}{R}$$

↳ Magnetic Circuit.


$$I = \frac{V}{R}$$

↳ Electrical Circuit.

* Electrical Machines :-

* Introduction to Electrical Machines

* Linear DC Machine :-

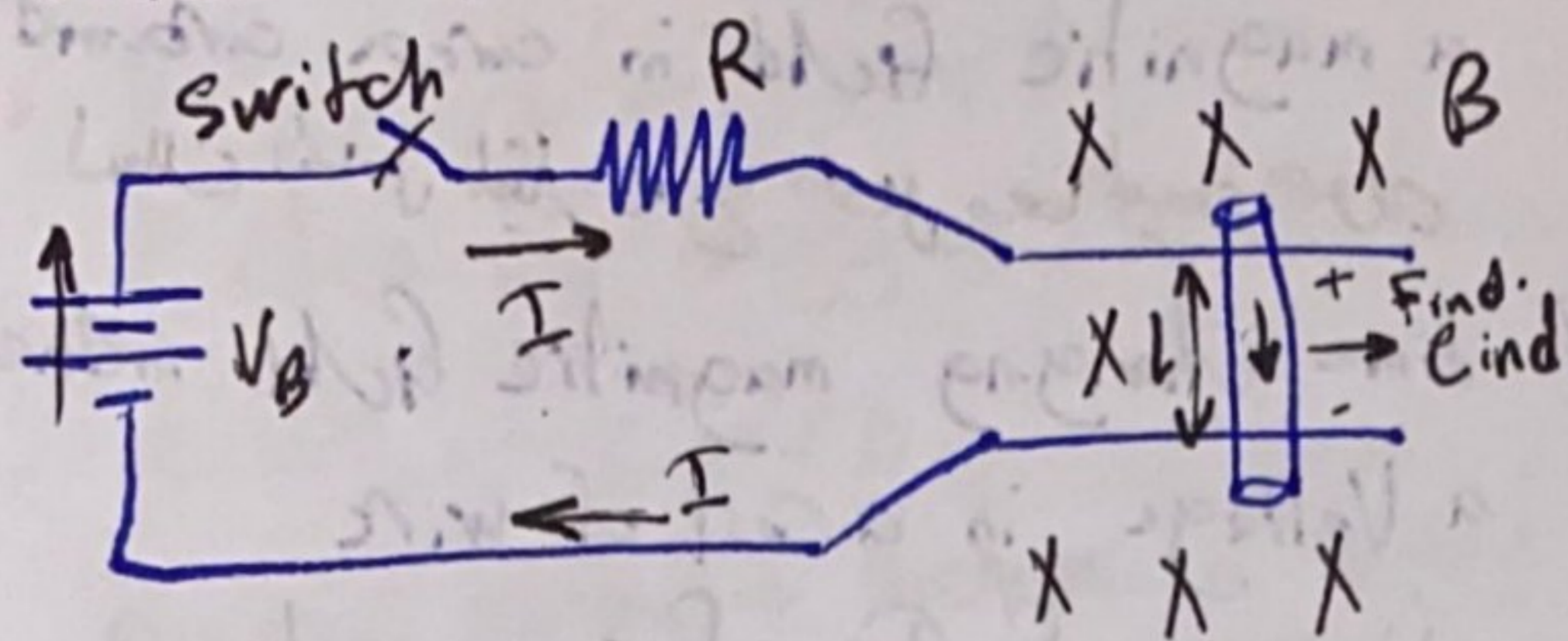


Linear DC Machine behavior :-

1. force on a wire.

$$F = I(L \times B)$$

$$F = I L B \sin \theta$$

force on wire
current
length

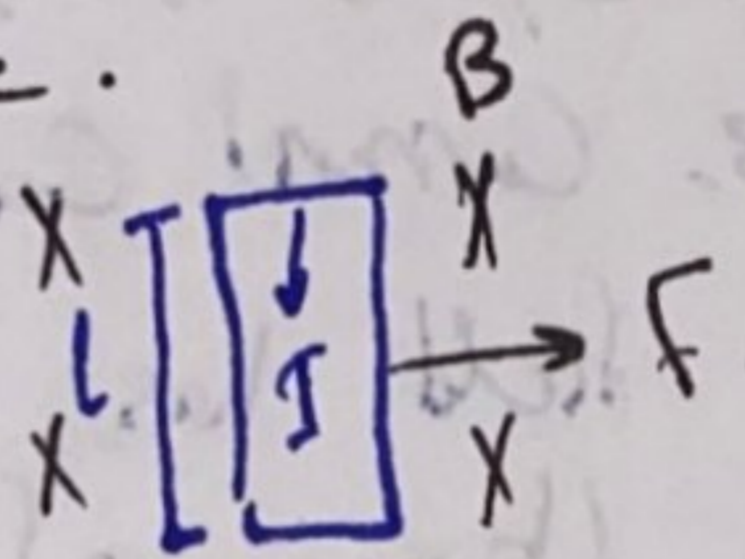

magnetic field density

2. Voltage induced on a wire moving in a magnetic field.

$$e_{ind} = (V \times B) \cdot L$$

$$e_{ind} = (VB \sin \theta_1) (L \cos \theta_2)$$


(VB) is velocity and (L) is length

V = Velocity of the wire.

B = Magnetic field density.

L = length of conductor

e_{ind} = Voltage induced in wire

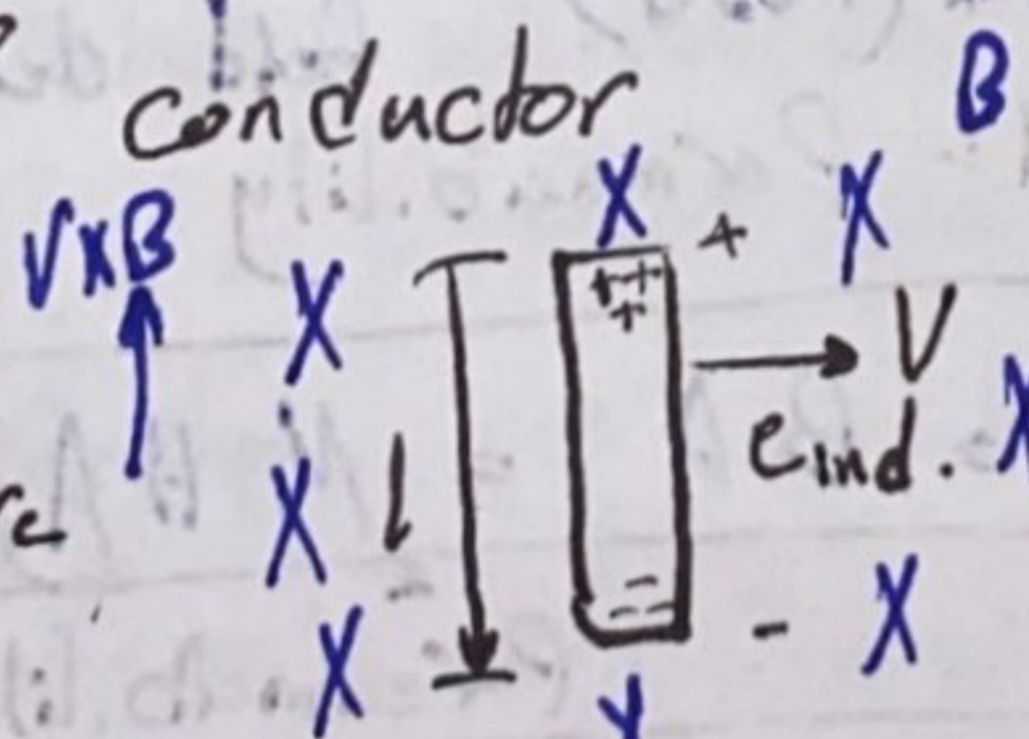

3. Kirchoff's Voltage Law

$$V_B - e_{ind} - IR = 0$$

$$V_B = e_{ind} + IR$$

4. Newton's Law for the bar

$$F_{net} = m a \rightarrow \text{acceleration}$$

mass

[2]

* Linear DC Machine :-

1. $I = \frac{V_B}{R}$ starting current
maximum current

2. Current flow produce an induced force

$$F = I L B \quad \int \vec{j} \times \vec{B} = \vec{F}$$


3. The bar accelerate due to the induced force.

$$a = \frac{F_{ind}}{m} = \frac{DV}{Dt}$$

4. bar moves, producing induced Voltage

$$e_{ind} = (V \times B) \cdot L \quad \int \vec{v} \times \vec{B} = \vec{e}$$

* Linear DC Machine :-

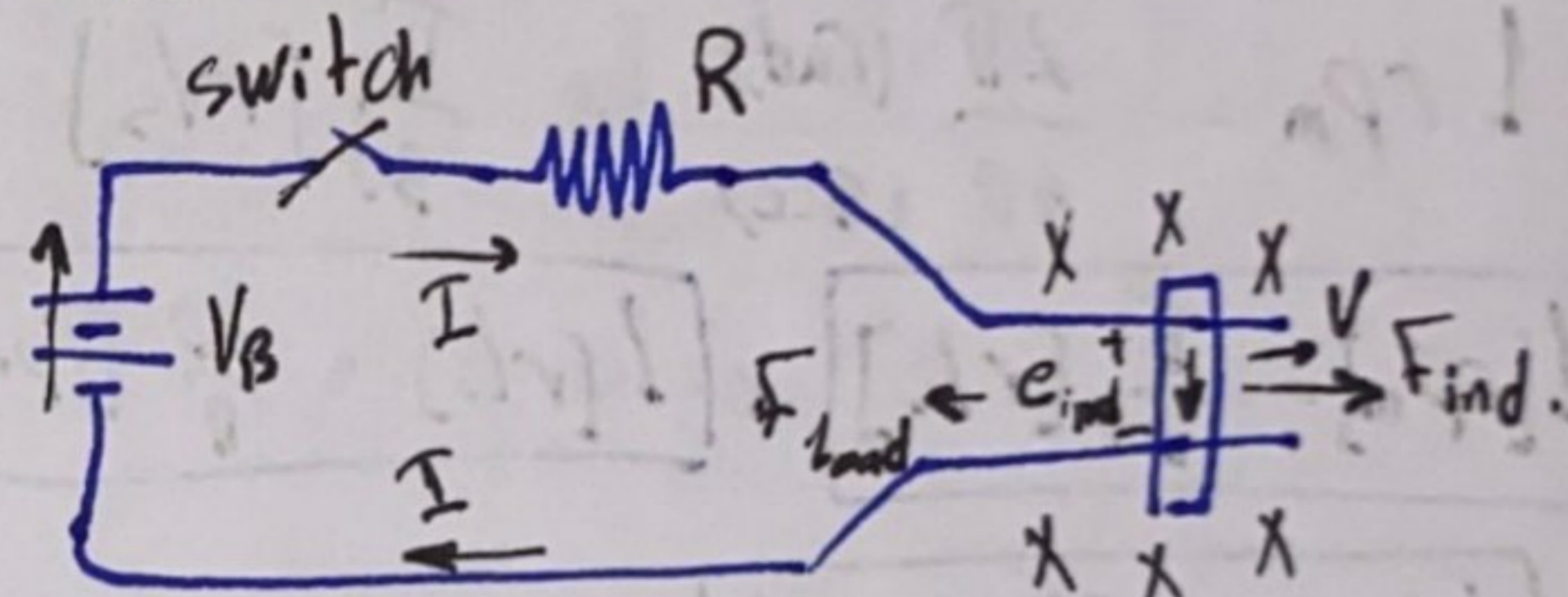

if we applied a force (F_{load}) to the bar in opposite direction of motion:

$$F_{net} = -F_{load} \quad \text{frictionless}$$

1. The bar decelerates due to the load force

$$a = \frac{F_{net}}{m} = \frac{DV}{Dt}$$

2. net force reduce induced Voltage

$$e_{ind} = V - BL \Rightarrow I = \frac{V_B - e_{ind}}{R}$$

but increase current.

3. Induced force increased

$$F_{ind} = I L B$$

in this case.

$$F_{net} = F_{ind} - F_{load}$$

4. Electrical Power = $e_{ind} \times I$.

converted to Mechanical Power

$$= F_{ind} \times V \quad \text{The Machine} \rightarrow \text{motor}$$

* Electrical Machines :-

* DC Machines :-

* DC Machines are :-

1. generators :- convert Mechanical energy \rightarrow Electric energy
2. motors :- convert Electric energy \rightarrow Mechanical energy

* DC Machines :-

- DC Machines have AC Voltages and Currents within them.
- DC Machines have a DC output only because \rightarrow a mechanism (commutator) exists that converts the internal AC Voltages to DC Voltages at terminals

* Simple Rotating Loop :-

- Simple Rotating loop \Rightarrow Single loop of wire rotating about a fixed axis.
- rotating part is called \Rightarrow rotor
- stationary part is called \Rightarrow stator.
- to easy calculation we assume:
 1. the magnetic field is perpendicular to the rotor surface every where.
 2. the flux is uniformly distributed (constant) every where.
- the Voltages in any real machine depend on the :-
 1. the flux in the machine.
 2. the speed of rotation.
 3. Constant representing (K) 3

* Total Voltages on the loop :-

$$E_{ind} = (V \times B) \cdot l$$

\rightarrow The Voltages on each segment

$$E_{ind} = 2VBl$$

\rightarrow Total Voltages on the loop.

$$E_{ind} = 2VBl = \frac{2}{\pi} \Phi \omega = k \Phi \omega$$

* Total Torque on the loop :-

$$F_{ind} = I(L \times B) \rightarrow \text{force induced.}$$

$$T_{ind} = r F_{ind} = r I L B$$

\rightarrow The Torque on each segment.

$$T_{ind} = 2r F_{ind} = 2r I L B$$

\rightarrow Total Torque on the loop.

$$T_{ind} = 2r I L B = \frac{2}{\pi} \Phi I = k \Phi I$$

- The torque in any real machine will depend on the :-

1. the Flux in the machine.
2. the Current in the machine.
3. Constant representing (K)

* Commutation Problems :-

1. Armature reaction.

the effect of the magnetic field set up by the armature current on the distribution of the flux under main poles.

- Armature reaction causes :-

1. Neutral plane shift.
2. Flux weakening.

2. $\frac{d\Phi}{dt}$ Voltages.

* Electrical Machines -

* DC Machines :-

* Power Flow and losses :-

1. Electrical or (copper) losses :-

the losses that occur in the armature and field windings.

Armature losses $P_A = I_A^2 R_A = I_A V_A$

Field losses $P_F = I_F^2 R_F = I_F V_F$

$P_{Elec} = P_A + P_F = I_A^2 R_A + I_F^2 R_F$

2. Brush losses :-

the power lost across the contact potential at the brushes.

Brush drop loss $P = V_{BD} I_A$

V_{BD} :- Brush Voltage drop.

I_A :- Current armature.

3. Core losses.

4. Mechanical losses.

1. Friction losses ضياع الاحتكاك

2. Windage losses ضياع الريح

Core and mechanical losses

$P_{tot} = P_{core} + P_{mech} = V I$
at no load

5. stray losses :-

$P_{stray} = 0.01 * P_{input}$

* Efficiency (η) :-

$\eta = \frac{P_{out}}{P_{in}} * 100\% = \frac{P_{in} - P_{loss}}{P_{in}} * 100\%$

4

* Types of DC Machines :-

1. Permanent Magnet :-

مغناطيس دائم عن طريق field circuit
منه لا يمر تيار R_f, V_f, I_f

2. Separately Excited :-

field circuit عبارة عن ملف كهربائي مستقل
عن تيار و يوجد معه مصدر جهد مستقل

3. Shunt DC Machine :-

field circuit عبارة عن ملف مرتبط على التوازي مع دائرة ال Armature

4. Series DC Machine :-

field circuit عبارة عن ملف مرتبط على التوالي مع دائرة ال Armature

* Speed Regulation (SR) :-

$SR = \frac{W_{NL} - W_{FL}}{W_{FL}} * 100\%$

$SR = \frac{n_{NL} - n_{FL}}{n_{FL}} * 100\%$


$W \rightarrow r/s$
 $n \rightarrow rpm$
 $NL \rightarrow no load$
 $FL \rightarrow full load$

⊕ SR \Rightarrow Motor's speed $\downarrow \rightarrow$ Load \uparrow

⊖ SR \Rightarrow Motor's speed $\uparrow \rightarrow$ Load \uparrow

* Separately Excited DC Motors :-

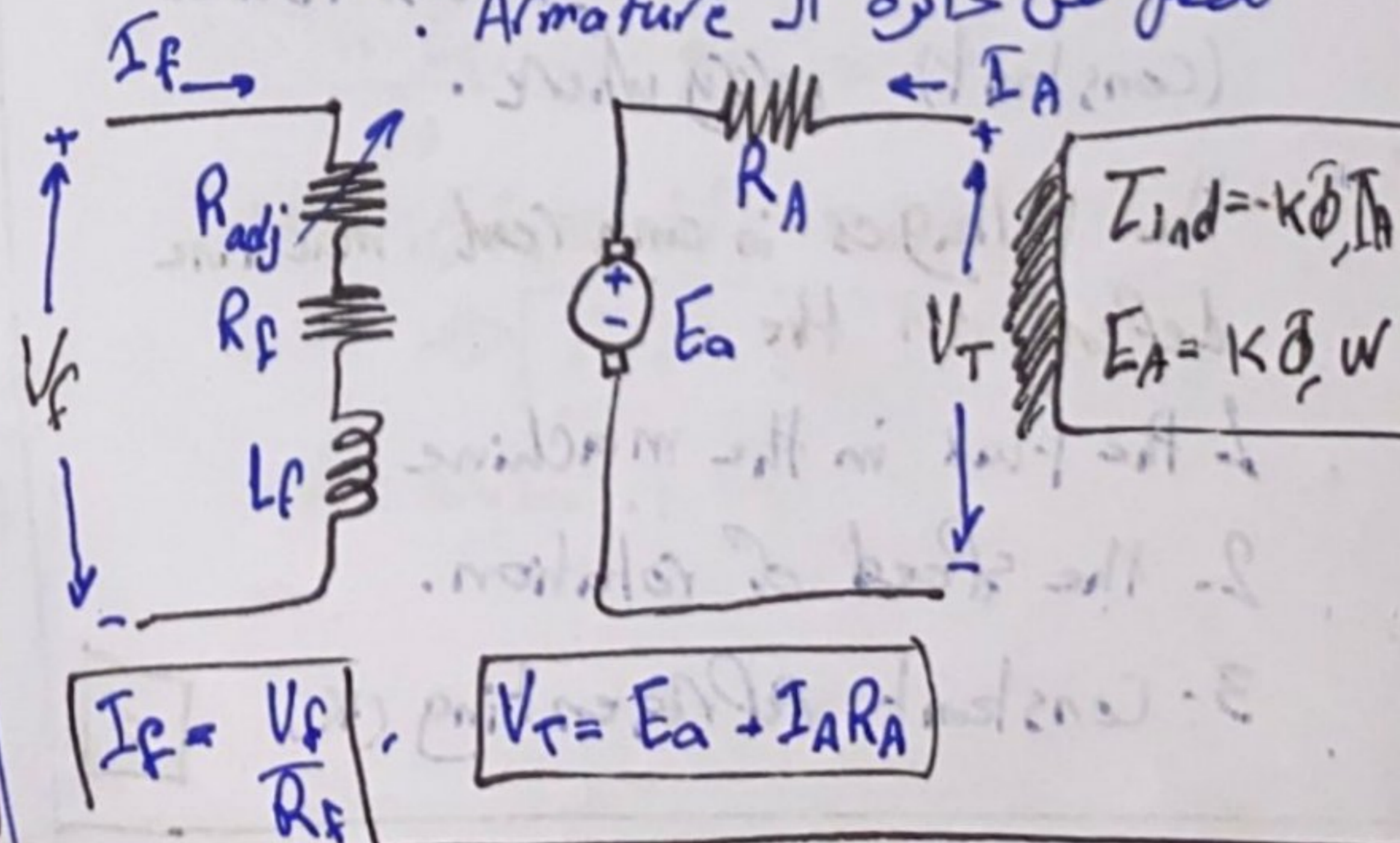دائرة ال field عبارة عن ملف مستقل عن تيار ال Armature



$I_f = \frac{V_f}{R_f}$


$V_T = E_a + I_a R_a$

* Electrical Machines :-

* DC Machines :-

* Shunt DC Motors :-

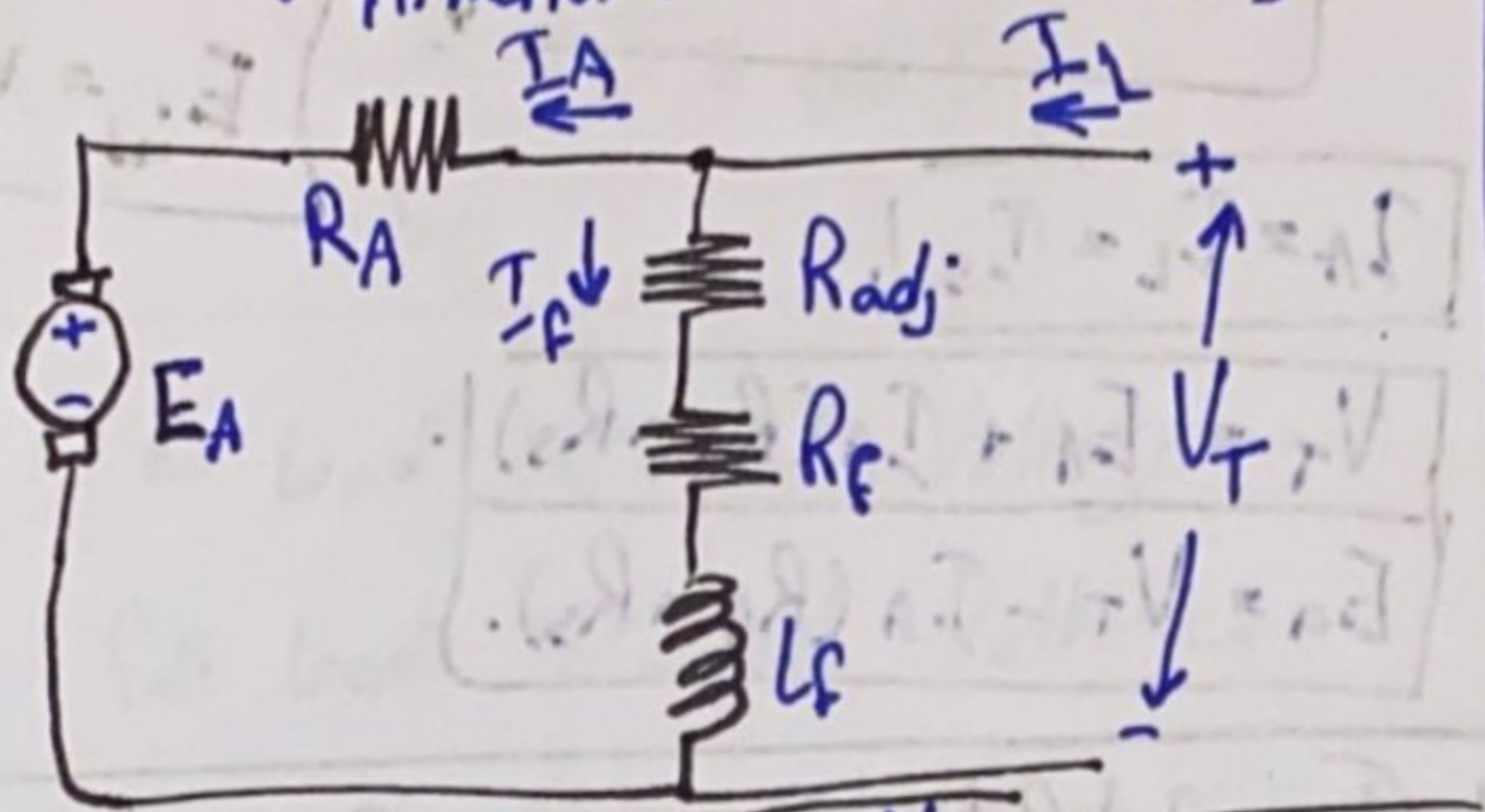موتور ذو مجال مغناطيسي مستقل عن دارة الجهد على التوازي مع دائرة الـ Armature



$$T_{ind} = k\Phi I_A$$

$$E_A = k\Phi \omega$$

$$I_f = \frac{V_f}{R_f}$$

$$I_L = I_A + I_f$$

$$V_T = E_A + I_A R_A$$

$$E_A = V_T - I_A R_A$$

* The Output of a separately excited and a shunt DC motors (W) :-

$$V_T = E_A + I_A R_A$$

$$E_A = k\Phi \omega$$

$$I_A = \frac{T_{ind}}{k\Phi}$$

$$V_T = k\Phi \omega + \frac{T_{ind} R_A}{k\Phi}$$

$$\omega = \frac{V_T}{k\Phi} - \frac{R_A}{(k\Phi)^2} T_{ind}$$

* Some of equations :-

$$E_A = k\Phi n$$

where $n \rightarrow \text{rpm}$

$$E_A = k\Phi \omega$$

where $\omega \rightarrow \text{r/s}$

$$\frac{E_{A2}}{E_{A1}} = \frac{k\Phi_2 n_2}{k\Phi_1 n_1}$$

$$\frac{E_{A2}}{E_{A1}} = \frac{k\Phi_2 \omega_2}{k\Phi_1 \omega_1}$$

DC motor with compensating windings

⇒ no armature reaction $\Phi = \text{const}$

$$\frac{E_{A2}}{E_{A1}} = \frac{n_2}{n_1}$$

$$\frac{E_{A2}}{E_{A1}} = \frac{\omega_2}{\omega_1}$$

* Some of equations :-

$$I_f^* = I_f - \frac{F_{AR}}{N_f}$$

→ magnetomotive force
→ number of turns.

↳ Current under effect of armature reaction (AR).

DC motor without compensating windings.

⇒ have an armature reaction

$$\Phi \neq \text{const}$$

$$I_f \rightarrow I_f^* \Rightarrow E_{A1} \rightarrow E_{A0}$$


$$P_{conv} = T_{ind} \omega = E_A I_A$$

$$T_{ind} = \frac{E_A I_A}{\omega}$$

$$W = \frac{E_A I_A}{T_{ind}}$$

* The Ways Which the speed of a separately excited and shunt DC motors can be controlled :-

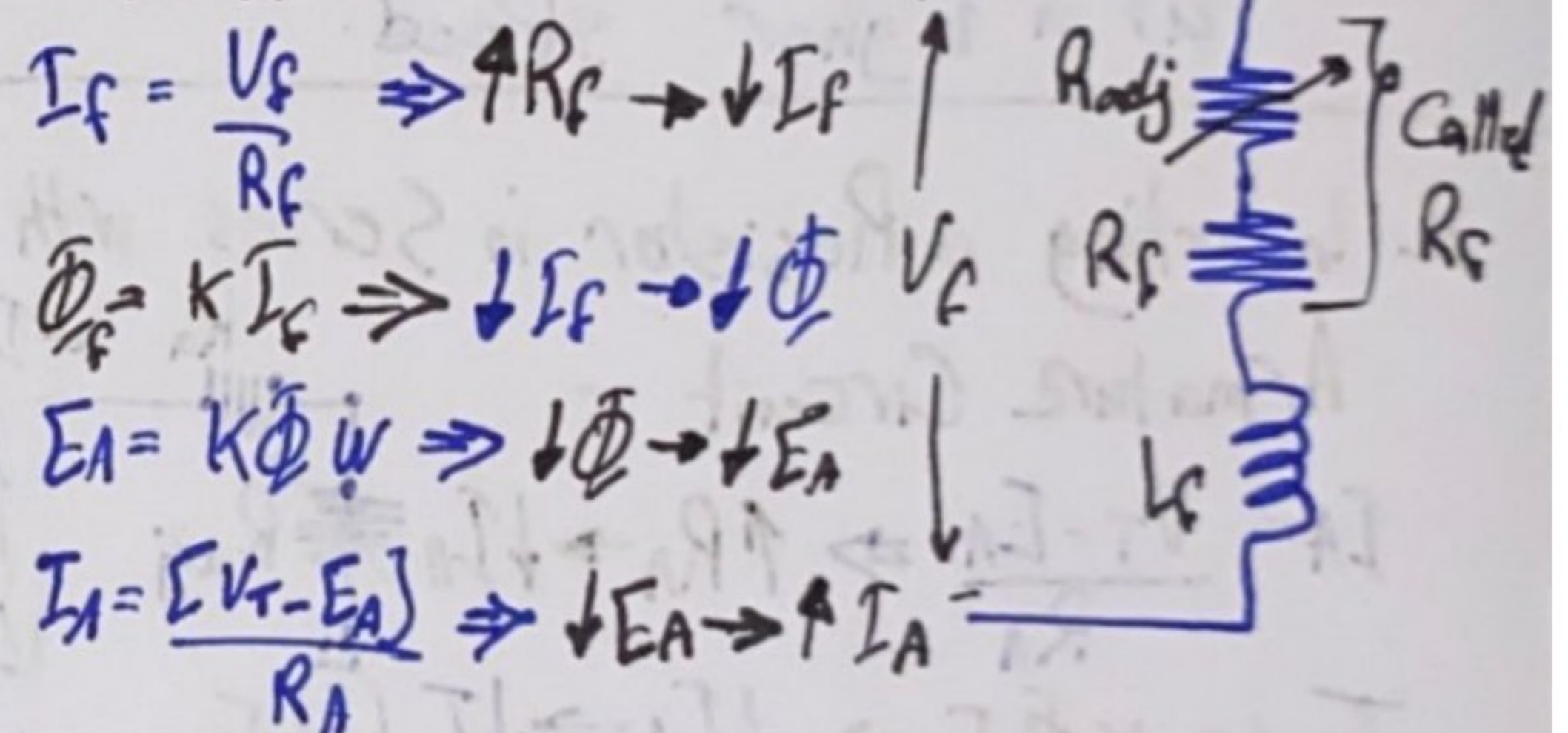1- Changing the field resistor control method :-



$$I_f = \frac{V_f}{R_f} \Rightarrow \uparrow R_f \rightarrow \downarrow I_f$$

$$\Phi \propto I_f \Rightarrow \downarrow I_f \rightarrow \downarrow \Phi$$

$$E_A = k\Phi \omega \Rightarrow \downarrow \Phi \rightarrow \downarrow E_A$$

$$I_A = \frac{V_T - E_A}{R_A} \Rightarrow \downarrow E_A \rightarrow \uparrow I_A$$

$$T_{ind} = k\Phi I_A \Rightarrow \uparrow I_A \rightarrow \uparrow T_{ind}$$

$$\uparrow T_{ind} \Rightarrow T_{ind} > T_{load} \Rightarrow \uparrow T_{ind} \rightarrow \uparrow \omega$$

$$E_A = k\Phi \omega \Rightarrow \uparrow \omega \rightarrow \uparrow E_A \text{ again.}$$

$$I_A = \frac{V_T - E_A}{R_A} \Rightarrow \uparrow E_A \rightarrow \downarrow I_A$$

$$T_{ind} = k\Phi I_A \Rightarrow \downarrow I_A \rightarrow \downarrow T_{ind}$$


until $T_{ind} = T_{load}$ at a higher speed.

* Electrical Machines :-

* DC Machines :-

* The Ways which the speed of a separately excited and shunt DC motors can be controlled :-

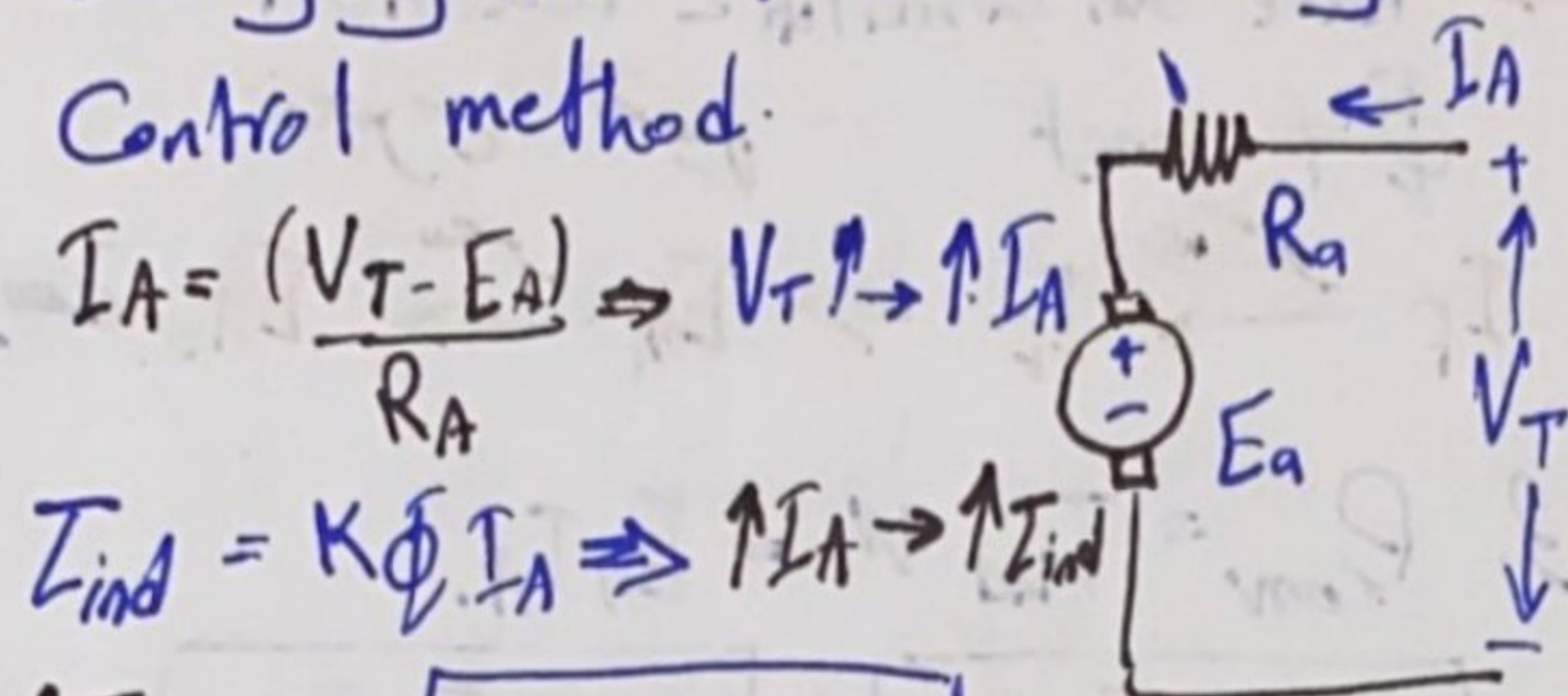2. Changing the Armature Voltage control method.



$$I_A = \frac{V_T - E_a}{R_a} \Rightarrow V_T \uparrow \Rightarrow \uparrow I_A$$

$$T_{ind} = K\Phi I_A \Rightarrow \uparrow I_A \Rightarrow \uparrow T_{ind}$$

$$\uparrow T_{ind} \Rightarrow \boxed{T_{ind} > T_{load}} \Rightarrow \uparrow T_{ind} \Rightarrow \uparrow W$$

$$E_a = K\Phi W \Rightarrow \uparrow W \Rightarrow \uparrow E_a$$


$$I_A = \frac{V_T - E_a}{R_a} \Rightarrow \uparrow E_a \Rightarrow \downarrow I_A$$

$$T_{ind} = K\Phi I_A \Rightarrow \downarrow I_A \Rightarrow \downarrow T_{ind}$$

$$\text{until } \boxed{T_{ind} = T_{load}}$$

at a higher speed.

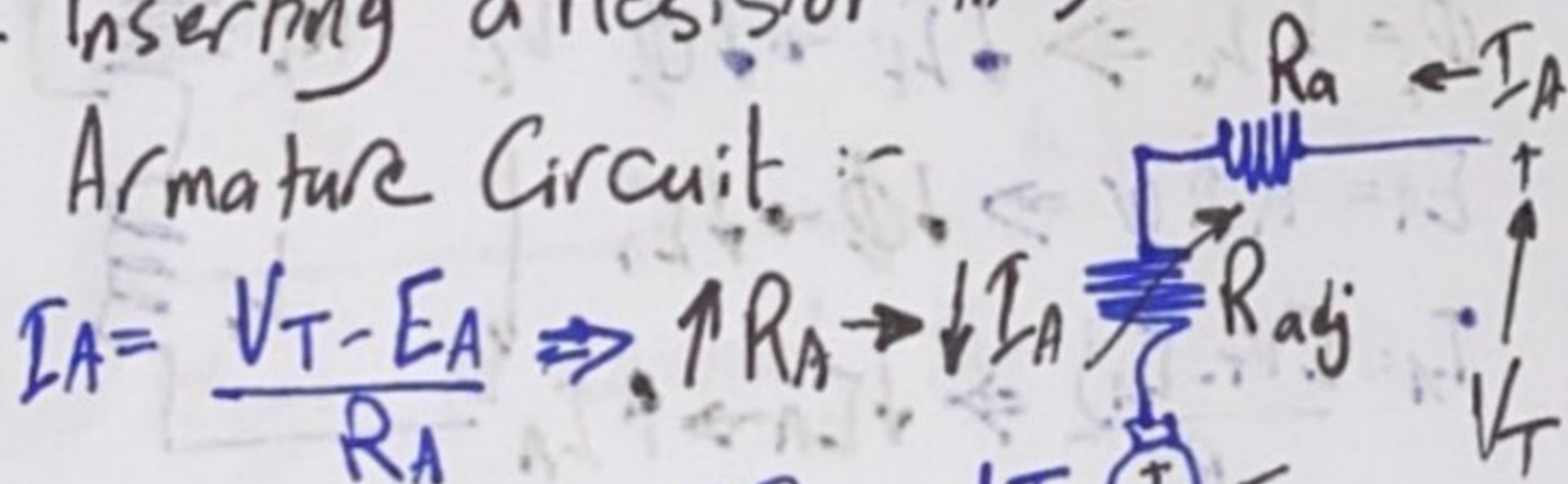3. Inserting a Resistor in Series with Armature Circuit :-



$$I_A = \frac{V_T - E_a}{R_a} \Rightarrow \uparrow R_a \Rightarrow \downarrow I_A$$

$$T_{ind} = K\Phi I_A \Rightarrow \downarrow I_A \Rightarrow \downarrow T_{ind}$$

$$\downarrow T_{ind} \Rightarrow \boxed{T_{ind} < T_{load}} \Rightarrow \downarrow W$$

$$E_a = K\Phi W \Rightarrow \downarrow W \Rightarrow \downarrow E_a$$

$$I_A = \frac{V_T - E_a}{R_a} \Rightarrow \downarrow E_a \Rightarrow \uparrow I_A$$


$$T_{ind} = K\Phi I_A \Rightarrow \uparrow I_A \Rightarrow \uparrow T_{ind}$$

$$\text{until } \boxed{T_{ind} = T_{load}}$$

at a lower speed.

* Series DC Motors :-

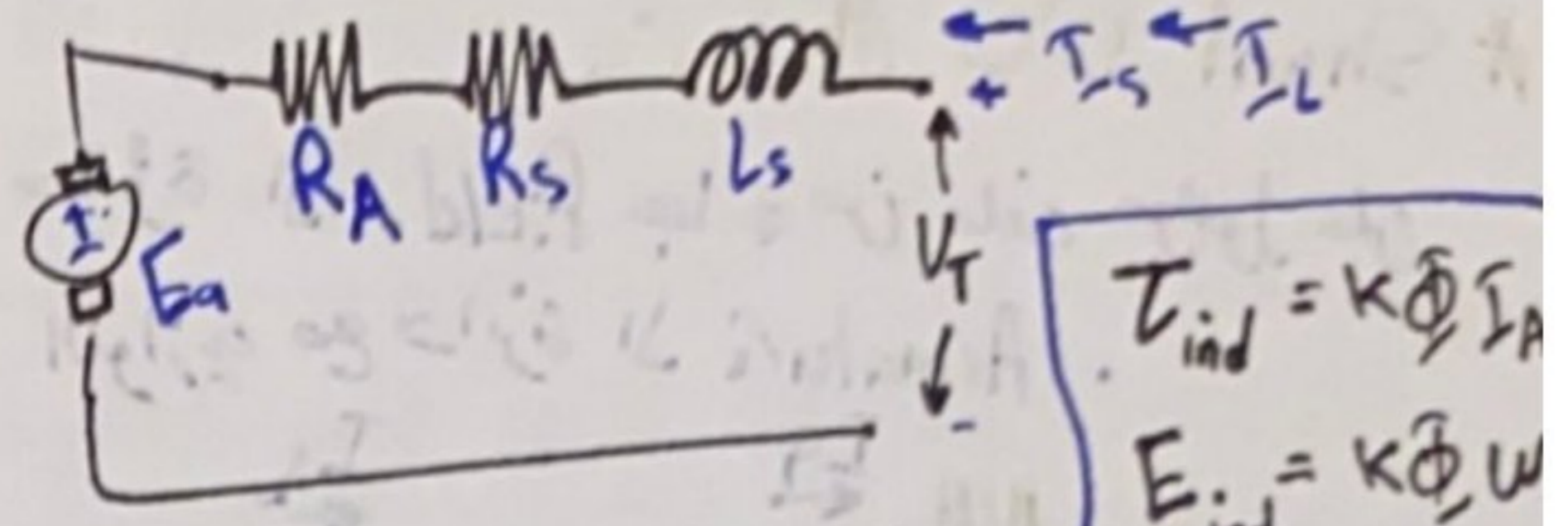دائرة ال field عبارة عن ملف يسري فيه التيار مع دائرة ال Armature



$$\begin{aligned} T_{ind} &= K\Phi I_A \\ E_{ind} &= K\Phi W \end{aligned}$$

$$I_A = I_L = I_s$$

$$V_T = E_a + I_A (R_A + R_s)$$

$$E_a = V_T - I_A (R_A + R_s)$$

* The Output of series DC motors :-

$$\Phi = C I_s = C I_A \quad I_s = I_A$$

$$T_{ind} = K\Phi I_A = CK I_A^2$$

$$T_{ind} \propto I_A^2 \rightarrow \text{series motor}$$

يعطي عزم عالي بنفس التيار

$$T_{ind} = CK I_A^2 \Rightarrow I_A = \sqrt{\frac{T_{ind}}{CK}}$$

$$\Phi = C \sqrt{\frac{T_{ind}}{CK}} = \sqrt{\frac{CT_{ind}}{K}}$$

$$V_T = E_a + I_A (R_A + R_s)$$

$$V_T = K\Phi W + I_A (R_A + R_s)$$

$$V_T = K \sqrt{\frac{CT_{ind}}{K}} W + \sqrt{\frac{T_{ind}}{CK}} (R_A + R_s)$$

$$\Rightarrow \boxed{W = \frac{V_T}{\sqrt{CK T_{ind}}} - \frac{R_A + R_s}{CK}}$$

* Electrical Machines :-

* DC Machines :-

* DC generators :-

* Voltage regulation (VR) :-


$$VR = \frac{V_{nl} - V_{FL}}{V_{FL}} \times 100\%$$

V_{nl} :- no load terminal Voltage.

V_{FL} :- full load terminal Voltage.

⊕ VR → drooping, ⊖ VR → rising.

* Separately Excited DC generators :-

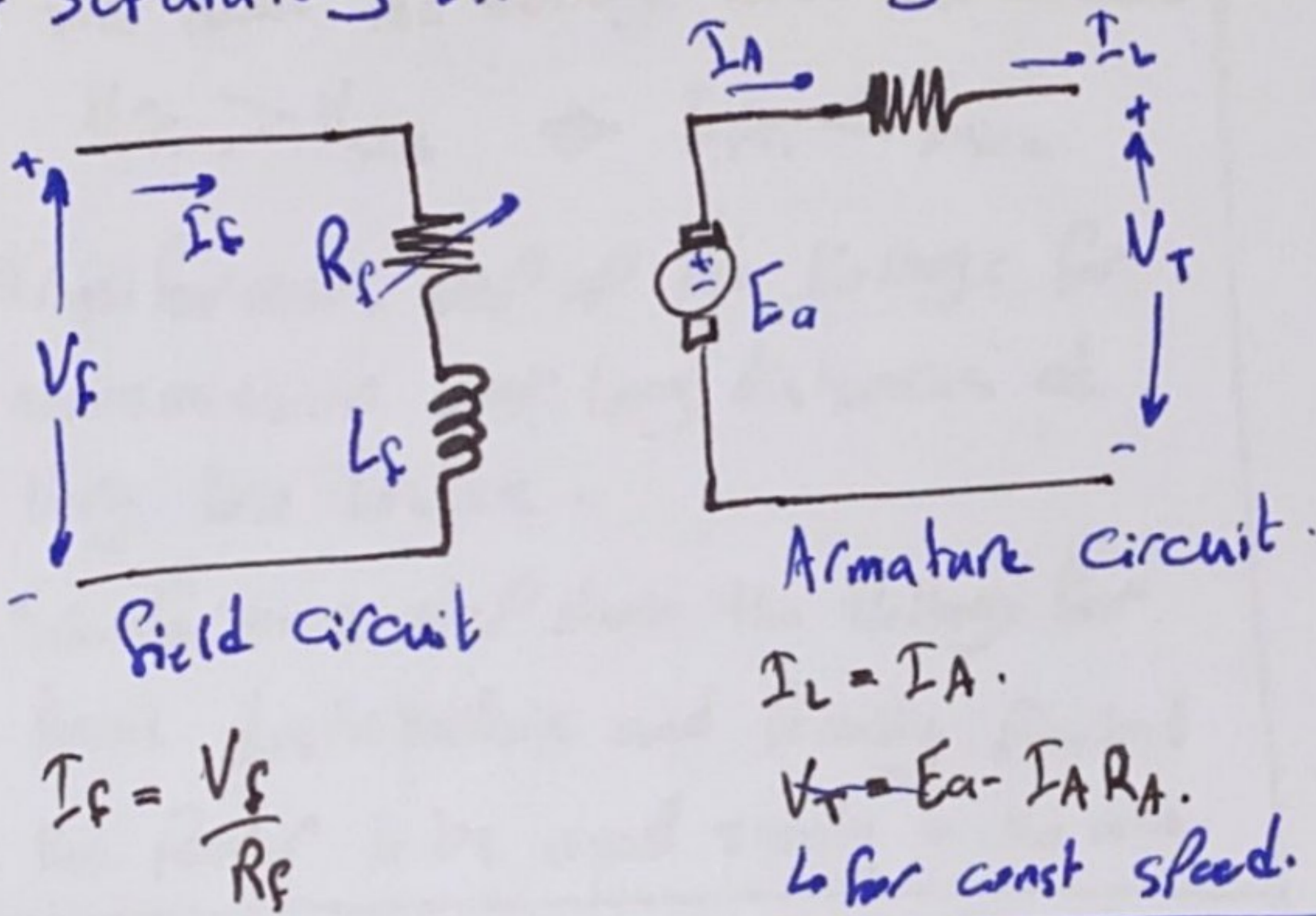

* The Ways to Control the Voltage of the generators :-

1. Change the speed (W) :-

$$W \uparrow \rightarrow \uparrow E_A = K \Phi W \uparrow$$

$$\uparrow V_T = E_A \uparrow - I_A R_A$$

2. Change the Field current (I_f) :-

$$\uparrow I_f = \frac{V_f}{R_f \downarrow} \rightarrow \uparrow \Phi = K I_f \uparrow$$

$$\uparrow E_A = K \Phi \uparrow W$$

$$\uparrow V_T = E_A \uparrow - I_A R_A$$

* Total magnetomotive force :-

$$F_{net} = N_f I_f - F_{AR}$$

no Armature reaction $F_{AR} = 0$.


$$F_{net} = N_f I_f$$

* Equivalent field ~~circuit~~ current :-

$$I_f^* = I_f - \frac{F_{AR}}{N_f}$$

* Electrical Machines :-

* The Transformers :-

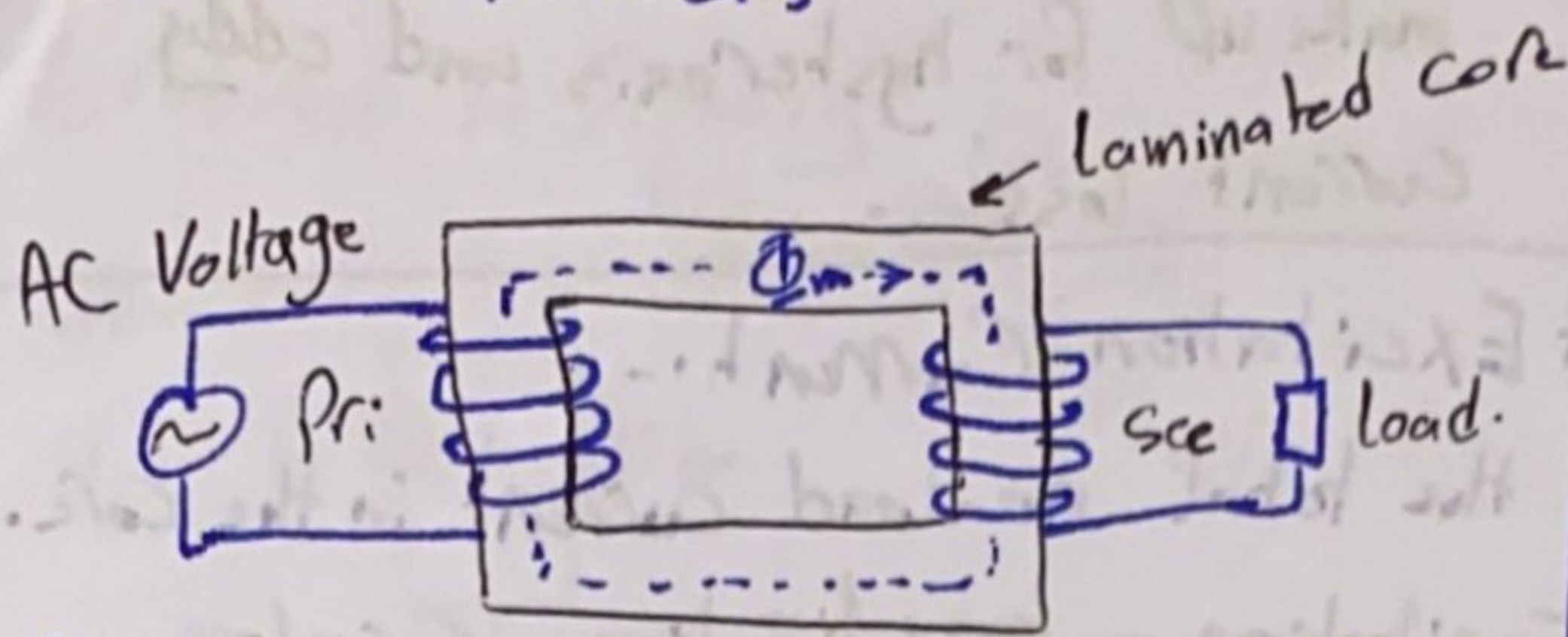

AC source \Rightarrow to have change in flux (Φ) in time.

* The Transformer :-

1. step up the voltage level of a circuit.

$$V_{sec} > V_{pri} \Rightarrow I_{sec} < I_{pri}$$

2. step down the voltage level of a circuit.


$$V_{pri} > V_{sec} \Rightarrow I_{pri} < I_{sec}$$

- Transformers step up the voltage for transmission over long distances at very low losses.

- Transformers step down the voltage for local distribution and finally permit the power to be used safely in homes.


* Types of cores :-

1. core form

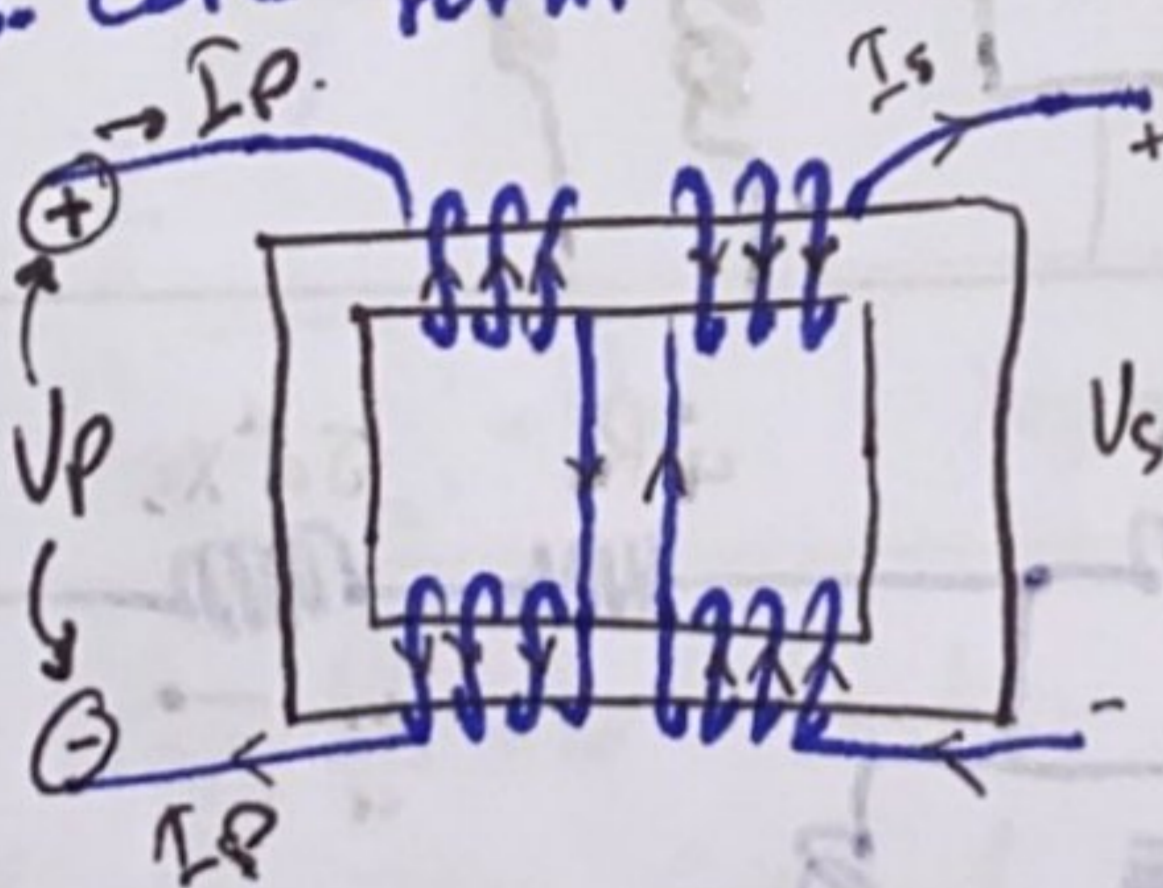

rectangular laminated piece of steel.

2. shell form :-

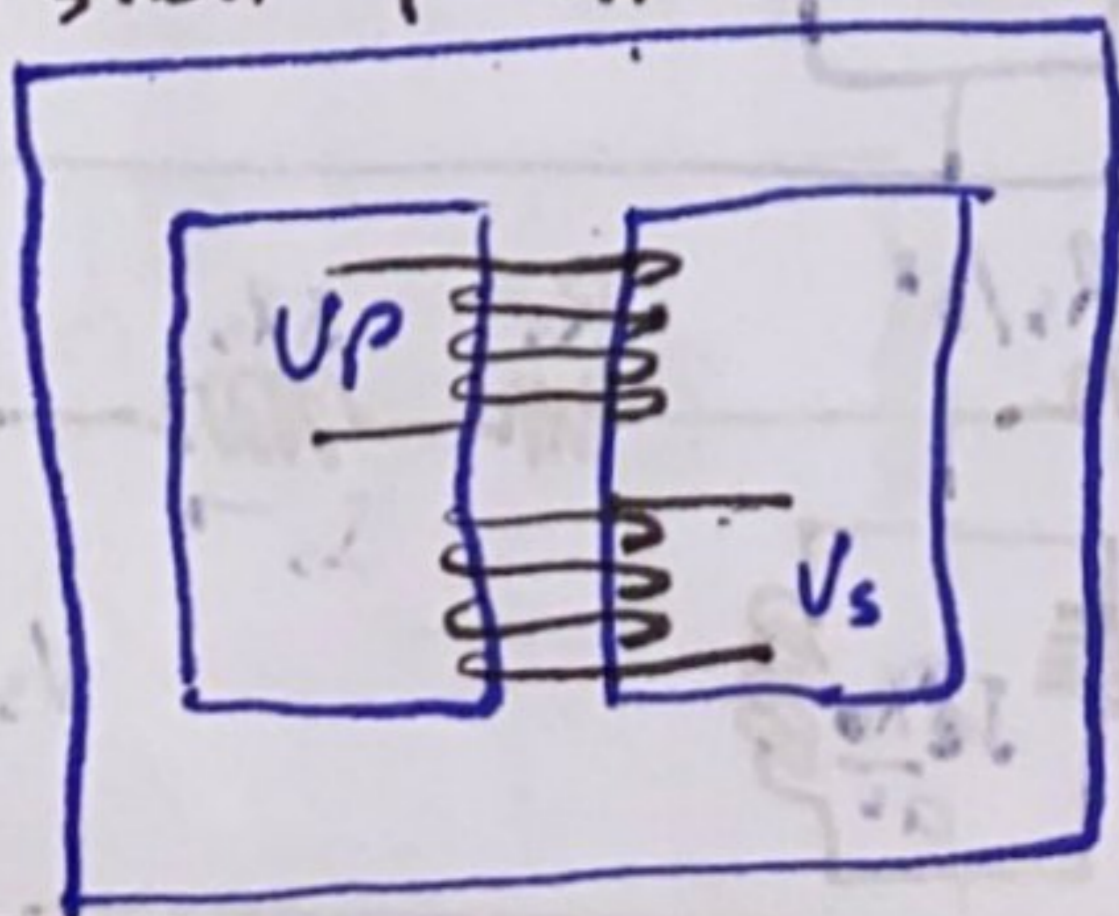

Three legged laminated core winding wrapped around the center leg

* Types of Transformers :-

1. Conventional $\begin{cases} \rightarrow 1\text{-Phase} \\ \rightarrow 3\text{-Phase} \end{cases}$

حازة ال Primary دائرة secondary

2. Auto transformer $\begin{cases} \rightarrow 1\text{-Phase} \\ \rightarrow 3\text{-Phase} \end{cases}$

Primary وال secondary دائرة مشتركة (الدارة)

each type have tapped type and variable type.

* The Ideal Transformer :-

have no losses $\Rightarrow \eta = 100\%$

$$P_{in} = P_{out} \Rightarrow V_p I_p = V_s I_s$$

\Rightarrow magnetomotive force are equal.

$$F_p = F_s \Rightarrow N_p I_p = N_s I_s$$

$$\Rightarrow \frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{I_s}{I_p} = a \rightarrow \text{transformer turns ratio}$$

\Rightarrow Power are equal.

$$P_{in} = P_{out}$$

$$V_p I_p \cos(\theta_p) = V_s I_s \cos(\theta_s)$$

$$\text{but } \theta_p = \theta_s \Rightarrow V_p I_p = V_s I_s$$

$$Q_{in} = Q_{out}$$

$$V_p I_p \sin(\theta_p) = V_s I_s \sin(\theta_s)$$

$$\text{but } (\theta_p = \theta_s) \Rightarrow V_p I_p = V_s I_s$$

$$P_{in} = P_{out} \quad , \quad Q_{in} = Q_{out}$$

$$\Rightarrow S_{in} = S_{out}$$

$$S_{in} = V_p I_p \cos(\theta_p) + j V_p I_p \sin(\theta_p)$$

$$S = P_{avg} (W) + j Q (VAR)$$

Complex Power (VA) average Power (W) reactive Power (VAR)

Electrical Machines :-

* The Transformers :-


* The Impedance (Z) :-

$$Z_L = \frac{V_L}{I_L} \quad Z_L := \text{load Impedance.}$$

$$Z_L' = a^2 Z_L$$

* Operation of Real Transformers :-

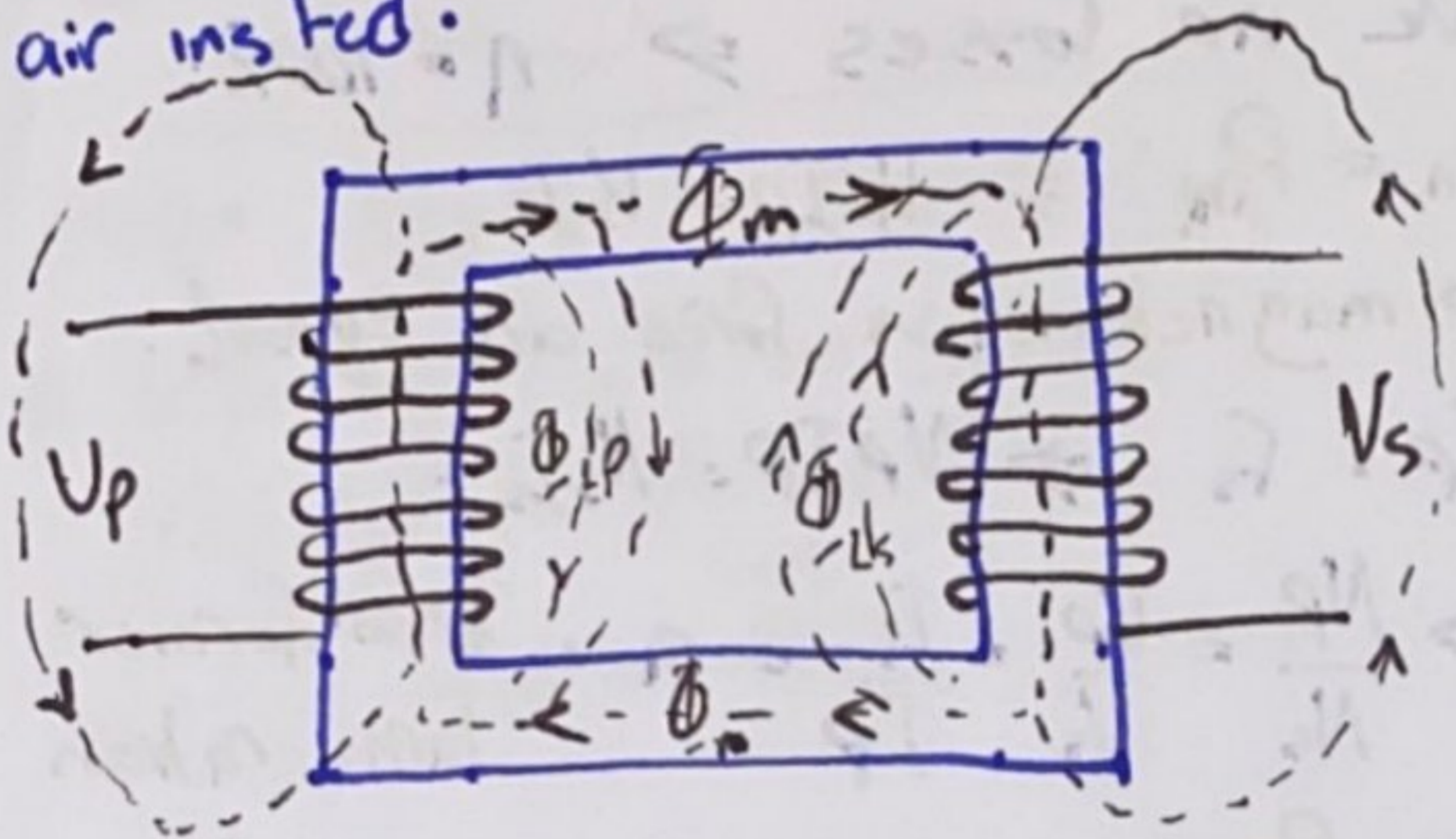Not all the flux produced in the primary coil also passes through the secondary coil. Some of the flux lines leave the iron core and pass through the air instead.



$$\Phi_p = \Phi_m + \Phi_{lp} \rightarrow \text{Leakage Flux.}$$

total Pri Flux mutual flux

$$\Phi_s = \Phi_m + \Phi_{ls}$$

$$\Phi_m \gg \Phi_{lp} \quad \Phi_m \gg \Phi_{ls}$$

$$\Rightarrow \frac{V_p(t)}{V_s(t)} = \frac{N_p}{N_s} = a \rightarrow \text{approximately}$$

* The Current flows in its Primary circ when the secondary circuit is open.

→ this current is required to produce flux in a real ferromagnetic core. and divided to two components :-

1. magnetization current :- required to produce the flux in the transformer core.

2

* Component of Current :-

2. Core-loss current :- required to make up for hysteresis and eddy current losses.

* Excitation Current :-

the total no-load current in the core.

$$\text{Excitation Current} = \text{magnetization Current} + \text{Core-loss Current.}$$

* Equivalent Circuit of a Transformer :-

* The losses :-

1. Copper losses ($I^2 R$)
Primary ($I_p^2 R_p$), Secondary ($I_s^2 R_s$).
Copper losses $\propto I^2$ winding.




2. Core losses (R_c)

① eddy current losses.

② hysteresis losses.

Core losses = Eddy current losses + hysteresis losses.


3. Leakage Flux (X_p, X_s) :-

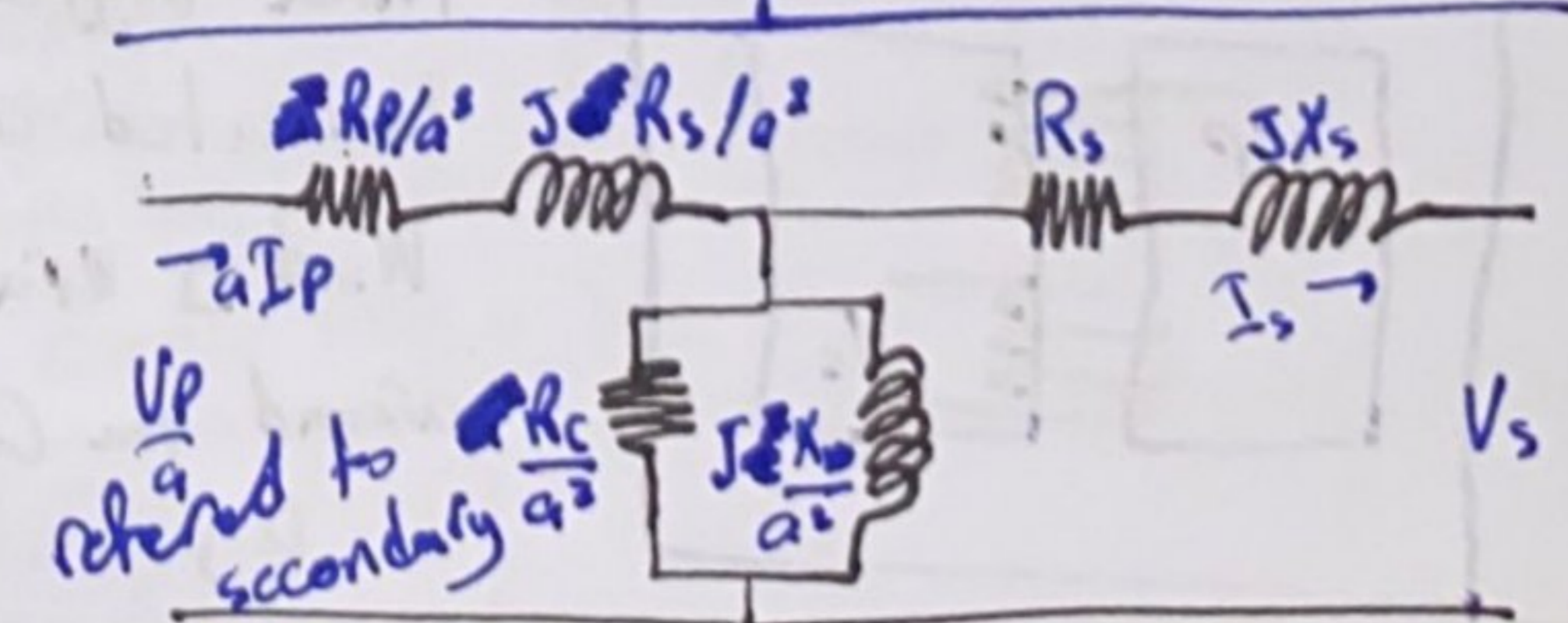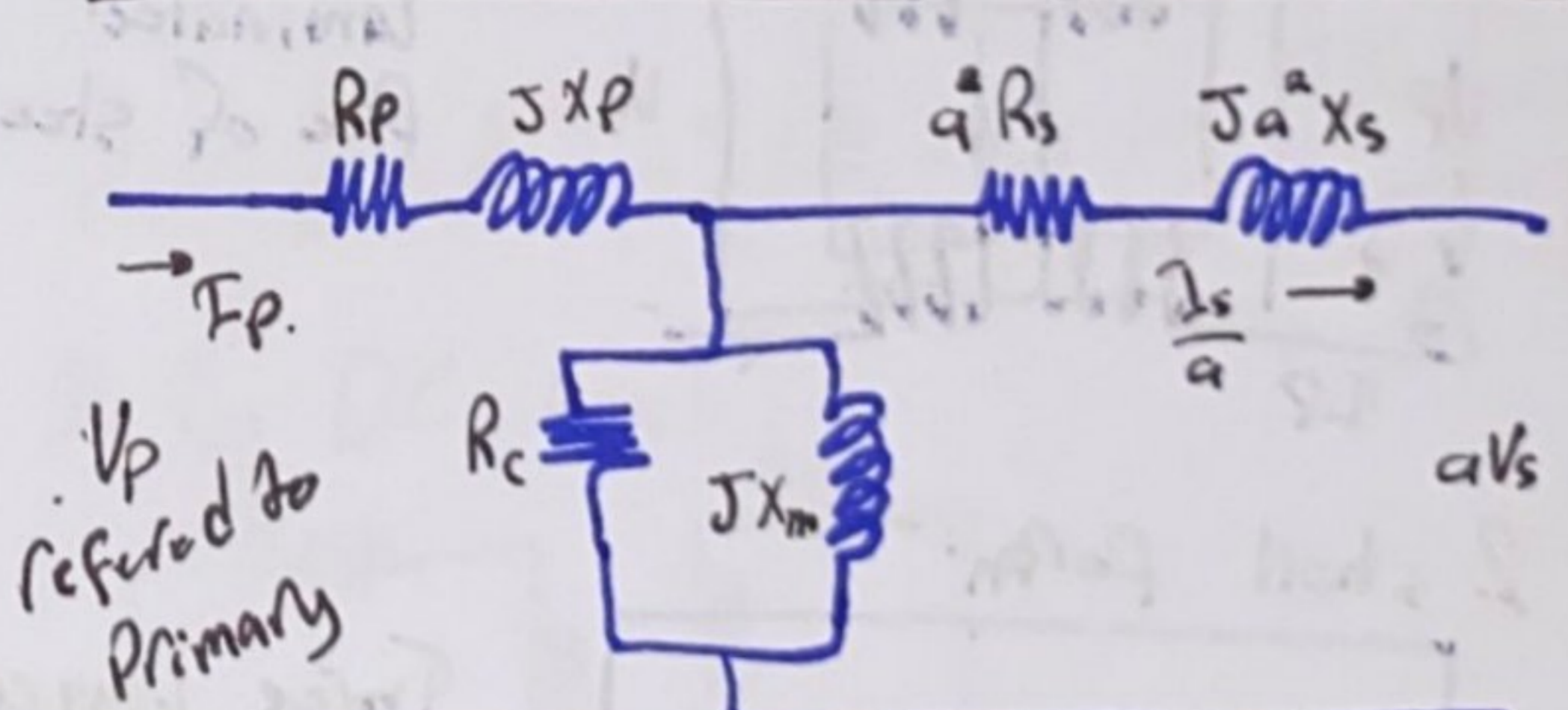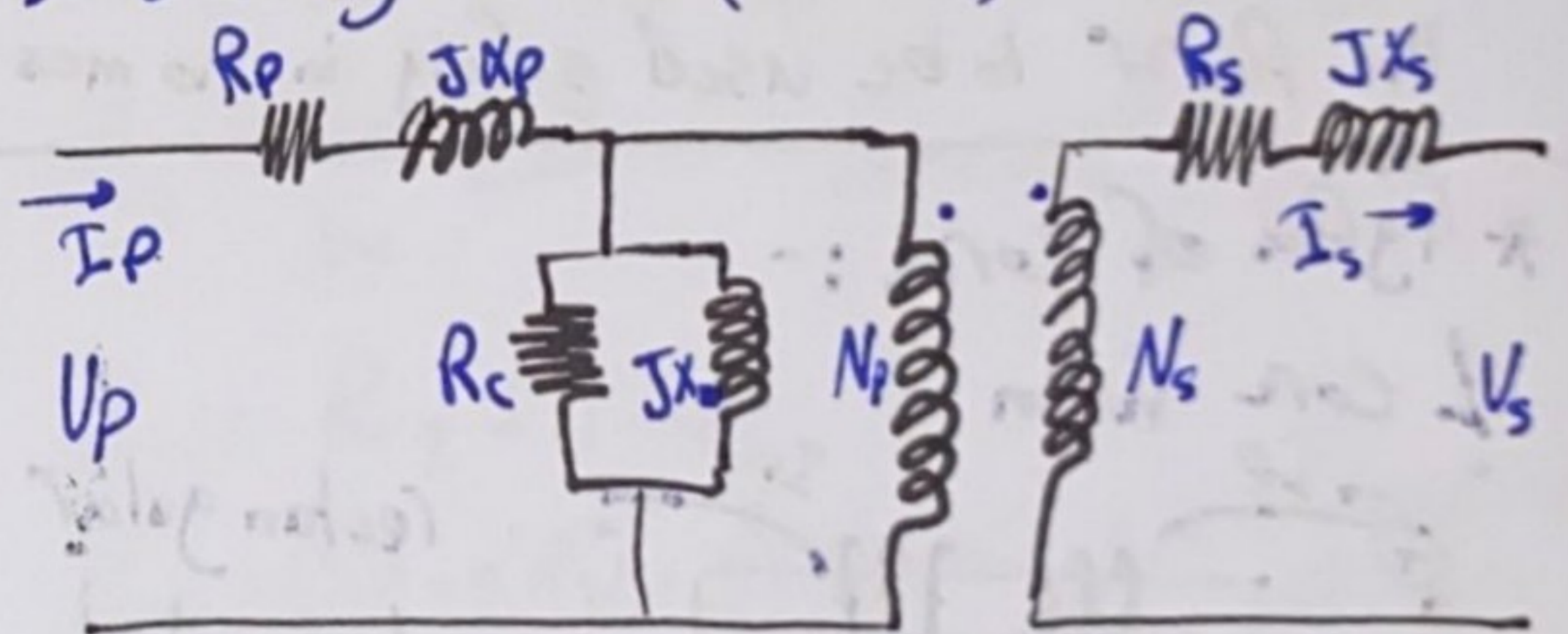

* Electrical Machines :-


* Approximate Equivalent Circuits :-

1. referred to Primary :-

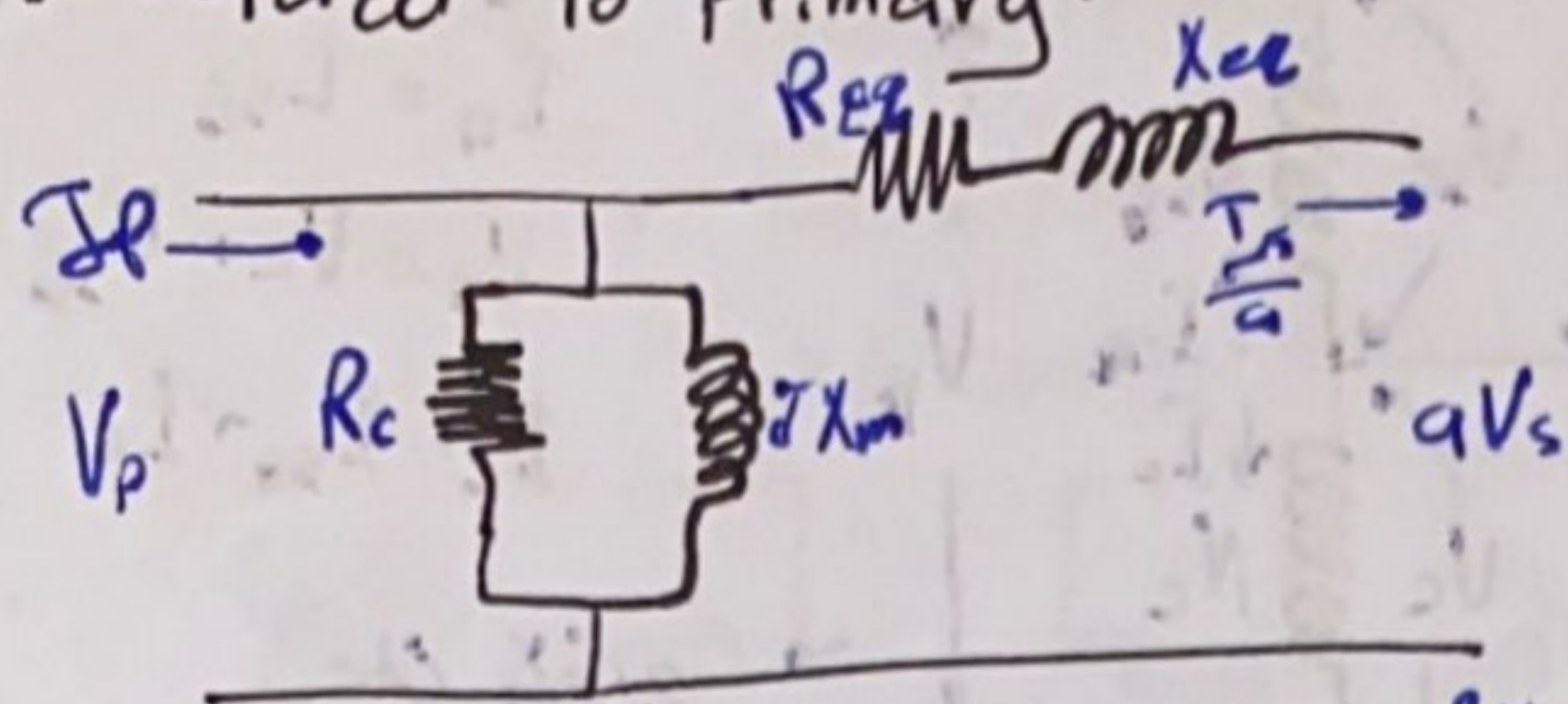

$$R_{eq} = R_p + a^2 R_s \quad X_{eq} = X_p + a^2 X_s$$


2. referred to secondary :-

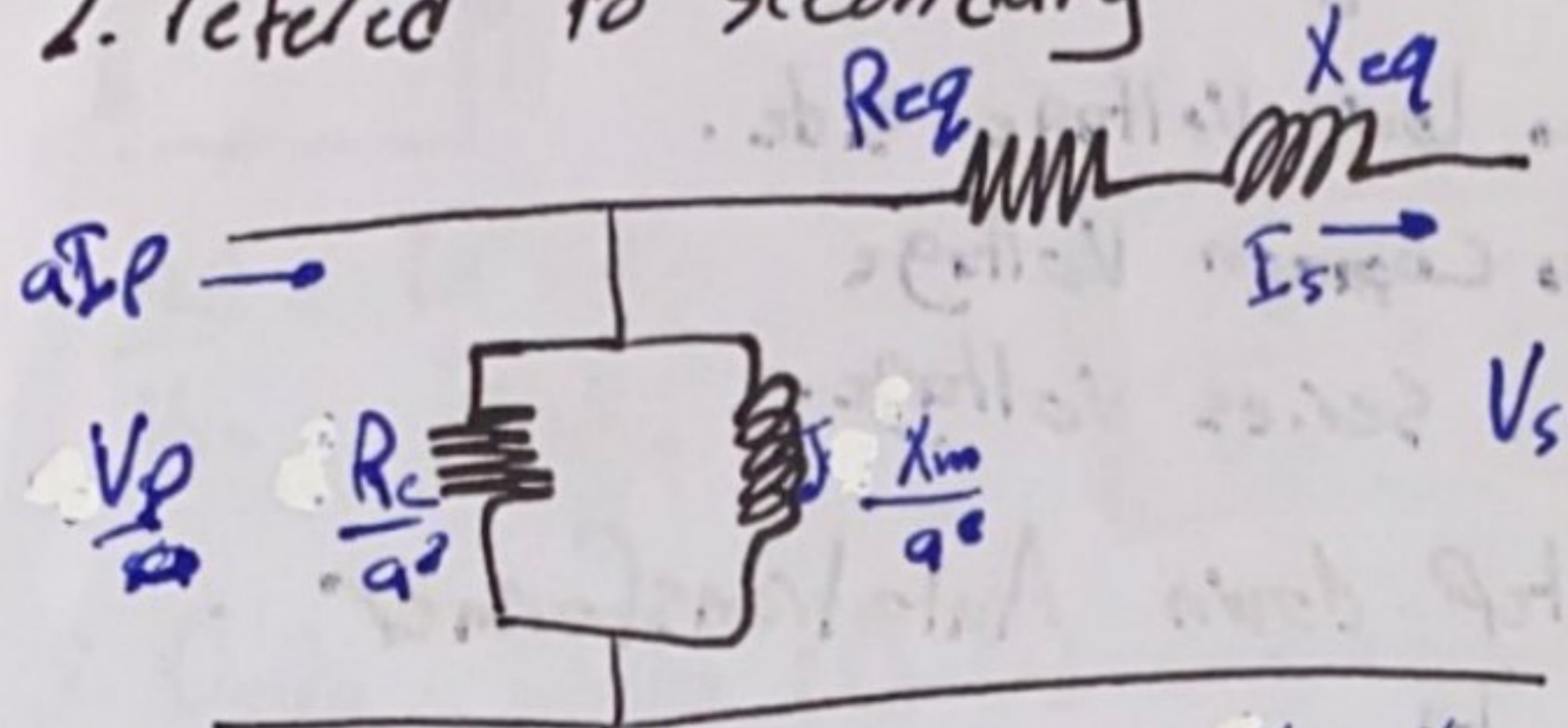

$$R_{eq} = \frac{R_p}{a^2} + R_s \quad X_{eq} = \frac{X_p}{a^2} + X_s$$


3. With no excitation branch

referred to Primary :-

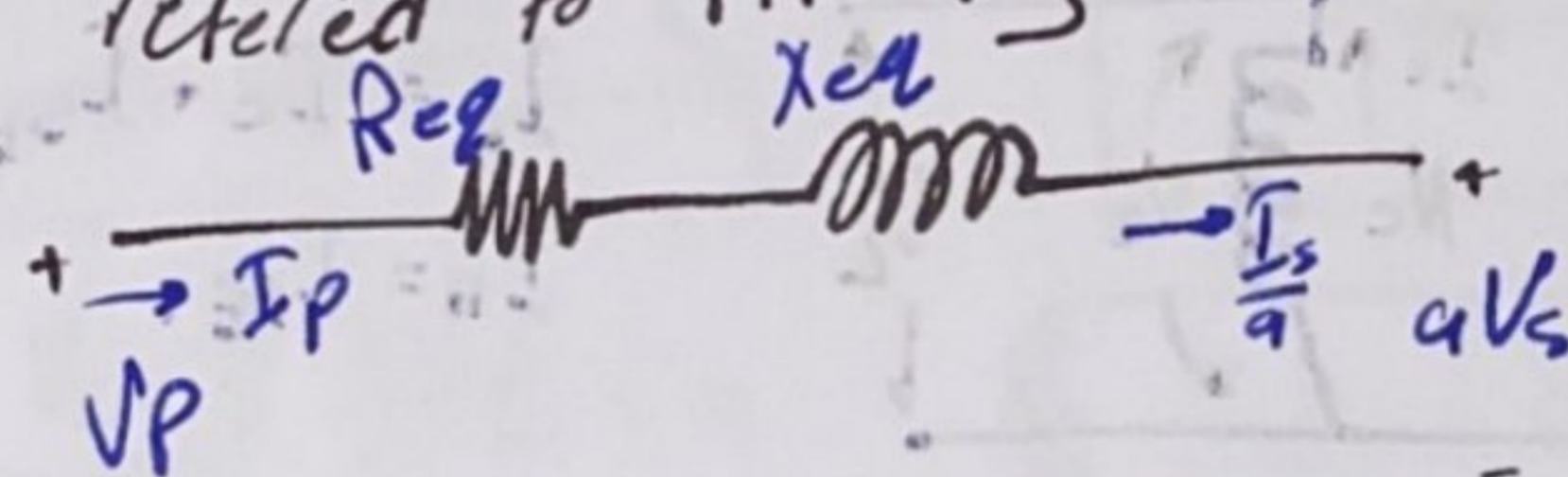

$$R_{eq} = R_p + a^2 R_s \quad X_{eq} = X_p + a^2 X_s$$

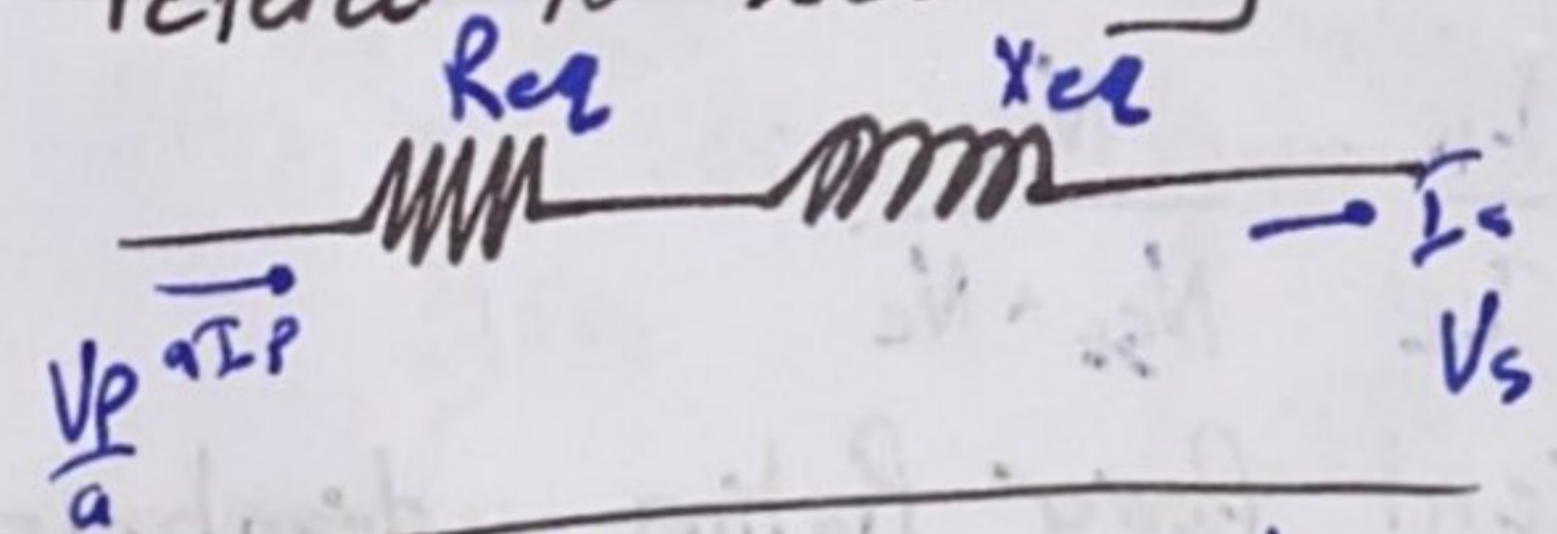4. With no excitation branch referred to secondary :-




$$R_{eq} = \frac{R_p}{a^2} + R_s \quad X_{eq} = \frac{X_p}{a^2} + X_s$$

* Transformer Test :-

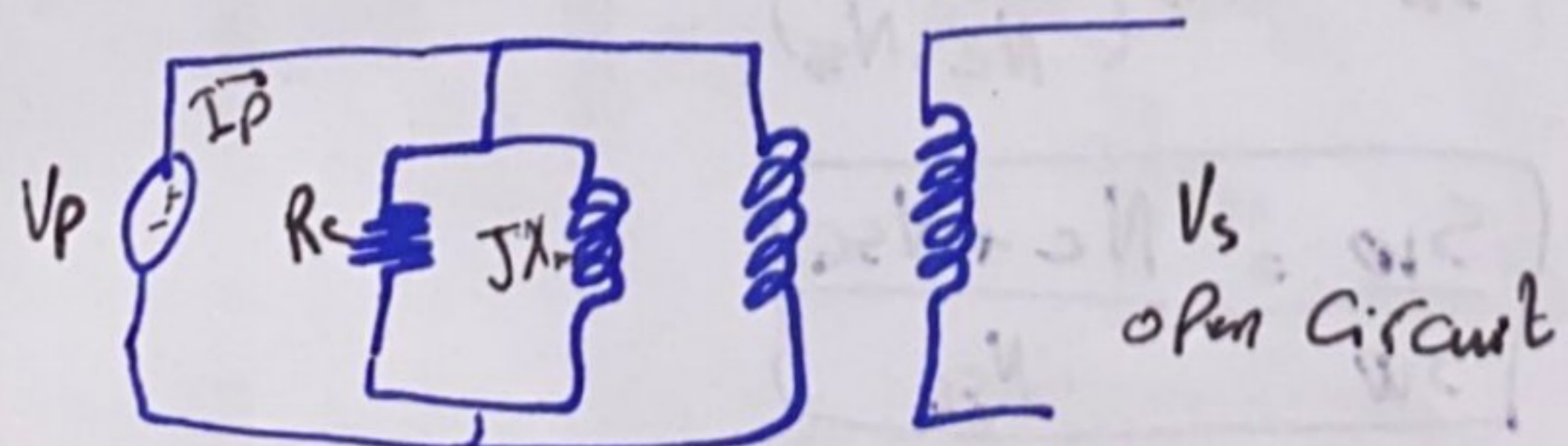1. The Open-Circuit test :- R_c, X_m

$R_p, R_s, X_p, X_s \Rightarrow$ referred



3

* Transformer test :-

1. Open-Circuit test :-

$$G_c = \frac{1}{R_c} \quad G = \text{Conductance}$$

$$B_m = \frac{1}{X_m} \quad B = \text{susceptance}$$

$$Y_E = \frac{1}{Z} \quad Y = \text{admittance}$$

$$Y_E = G_c - jB_m = \frac{1}{R_c} - j\frac{1}{X_m}$$


$$Y_E = \frac{I_{oc}}{V_{oc}} \angle -\theta \quad \theta = \cos^{-1}\left(\frac{P_{oc}}{V_{oc} I_{oc}}\right)$$

$$Y_E = |Y_E| \angle \alpha$$

$$G_c = |Y_E| \cos \alpha \Rightarrow \frac{1}{R_c} = \frac{1}{|Y_E| \cos \alpha}$$

$$B_m = |Y_E| \sin \alpha \Rightarrow \frac{1}{X_m} = \frac{1}{|Y_E| \sin \alpha}$$

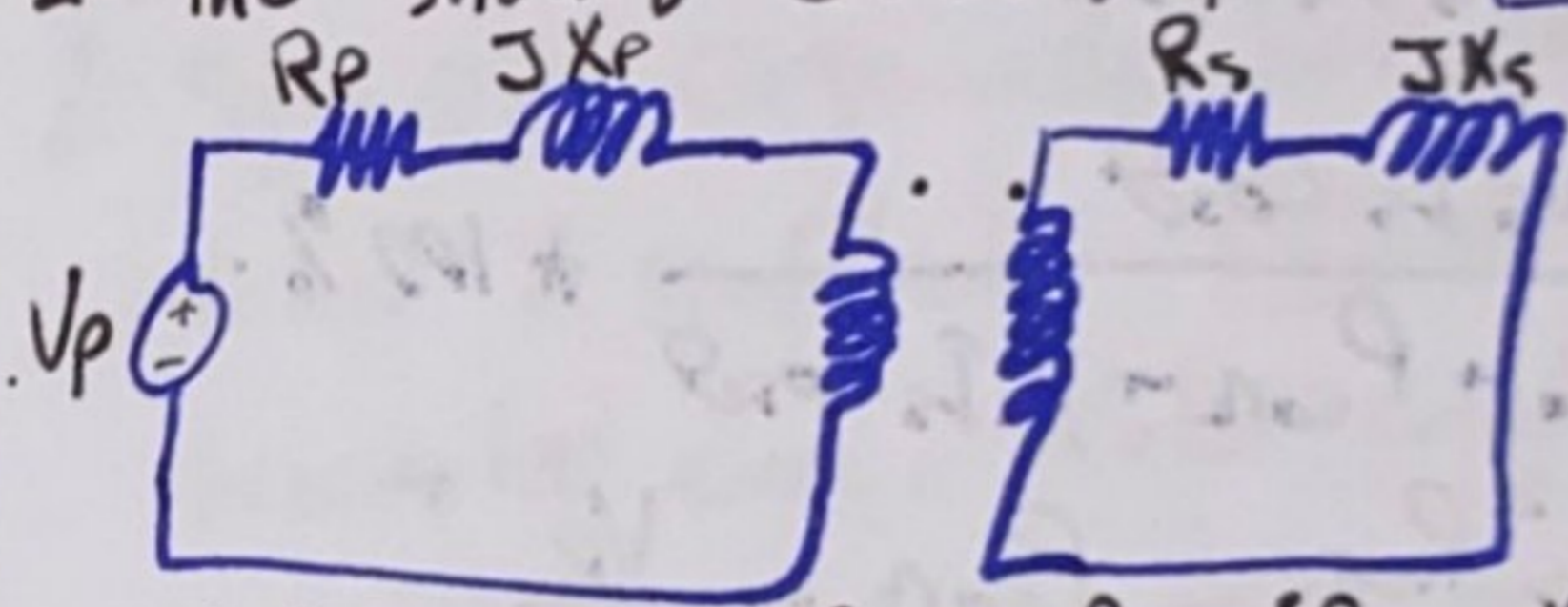2. The short-circuit test :- R_{eq}, X_{eq}



referred to Pri $\Rightarrow R_{eq} = R_p + a^2 R_s, X_{eq} = X_p + a^2 X_s$

referred to sec $\Rightarrow R_{eq} = \frac{R_p}{a^2} + R_s, X_{eq} = \frac{X_p}{a^2} + X_s$


$$Z_{sc} = \frac{V_{sc}}{I_{sc}} \angle \theta \quad \theta = \cos^{-1}\left(\frac{P_{sc}}{V_{sc} I_{sc}}\right)$$

$$Z_{sc} = R_{eq} + jX_{eq}$$

$$Z_{sc} = (R_p + a^2 R_s) + j(X_p + a^2 X_s) \rightarrow \text{referred to Primary}$$

$$Z_{sc} = \left(\frac{R_p}{a^2} + R_s\right) + j\left(\frac{X_p}{a^2} + X_s\right) \rightarrow \text{referred to secondary}$$

3. The DC test :-

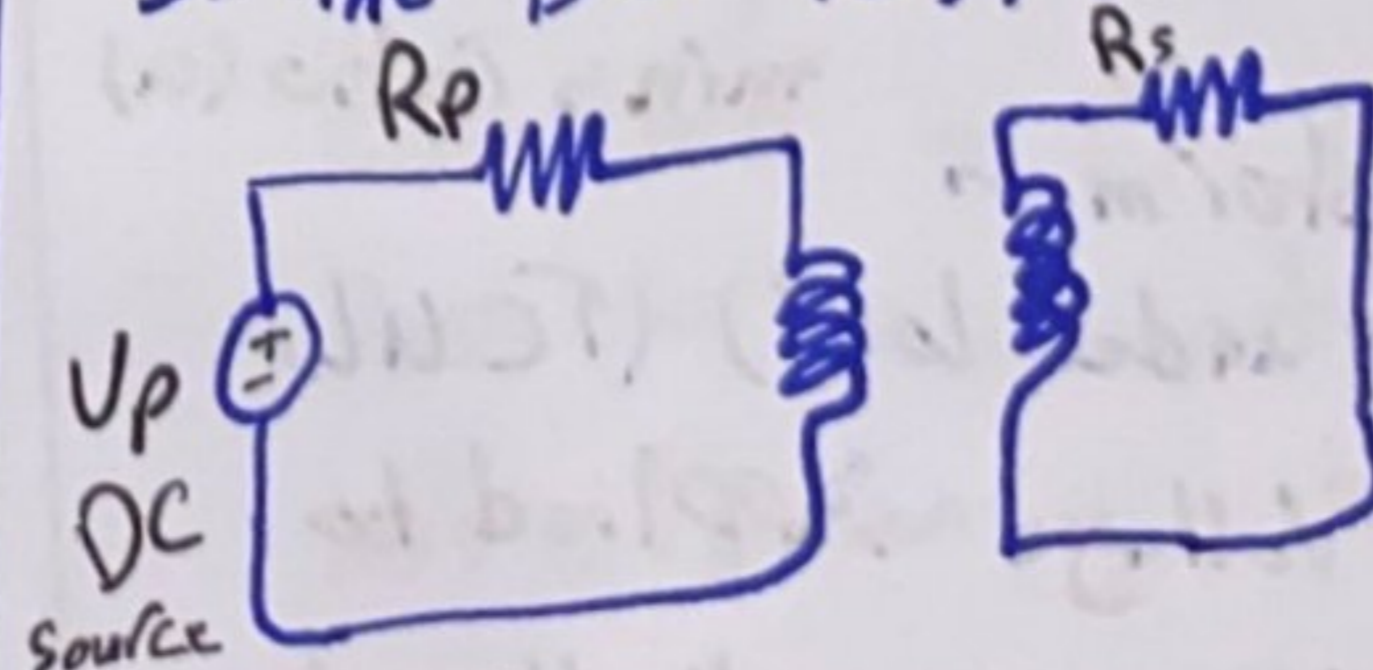

$$Z_{eq} = R_{eq} + jX_L$$

$$X_L = \omega L = 2\pi f L$$

$$f = 200 \Rightarrow X_L = 200$$

$$Z_{eq} = R_{eq}$$

* Electrical Machines :-

* Voltage regulation (VR) :-

$$VR = \frac{V_{s, nl} - V_{s, fl}}{V_{s, fl}} \times 100\%$$

$$a = \frac{V_p}{V_s} \Rightarrow V_s = \frac{V_p}{a}$$

$$VR = \frac{\frac{V_p}{a} - V_{s, fl}}{V_{s, fl}} \times 100\%$$

* Efficiency :-

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$= \frac{P_{out}}{P_{out} + P_{loss}} \times 100\% = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$$


$$P_{out} = V_s I_s \cos \phi$$

$$\eta = \frac{V_s I_s \cos \phi}{P_{cu} + P_{core} + V_s I_s \cos \phi} \times 100\%$$

$$P_{cu} = I_s^2 R_{eq} \quad P_{core} = \frac{V_p^2}{a^2 R_c}$$

* Transformer Taps :-

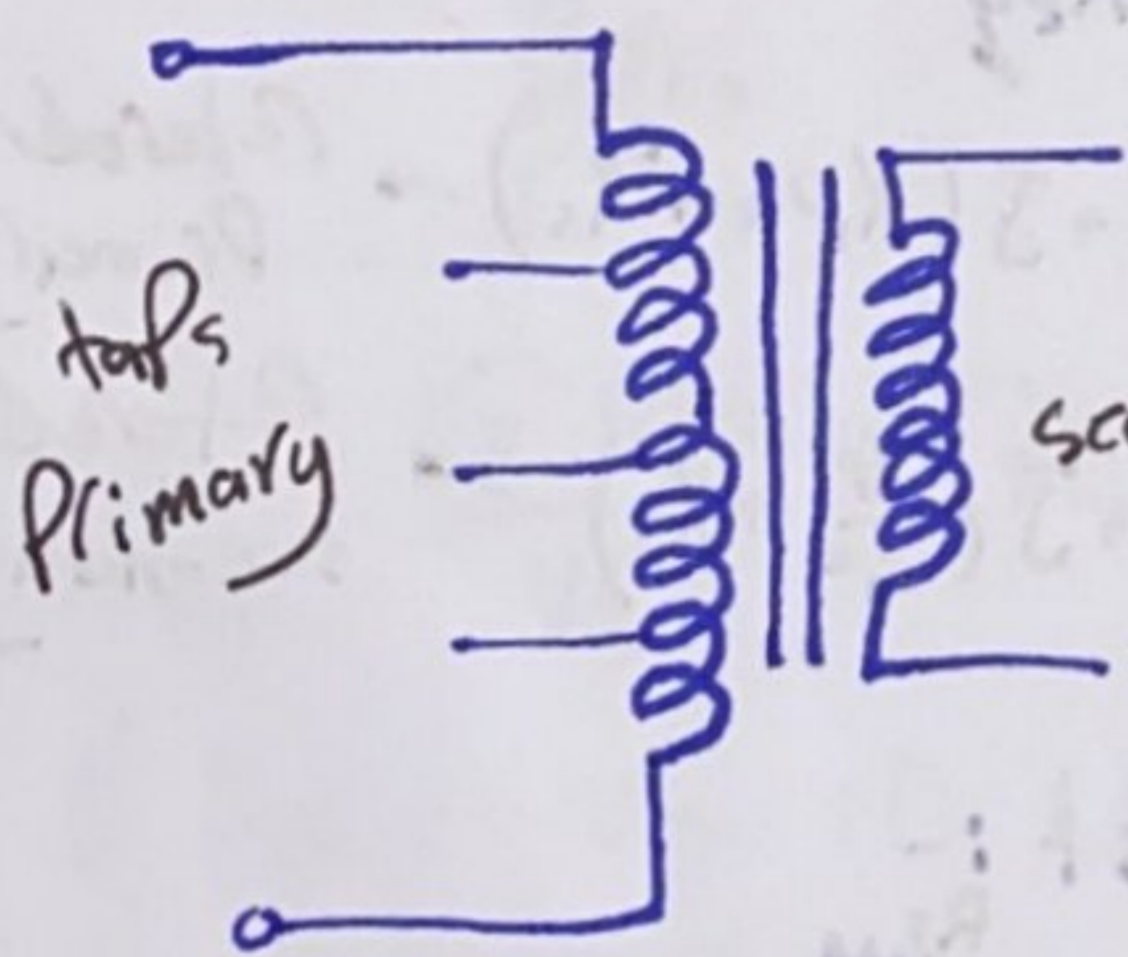اذا كاننا نريد ان نغير الجهد في الجهد
 Primary في الجهد في الجهد




We have a series of taps sec in winding to permit small change in the turns ratio (a)

special Transformer (tap changing under load) (TCUL)
 ⇒ Constant voltage supplied to loads which are constantly changing
 TCUL → Transformer with ability to change taps while power is connected

* The Auto-transformer :-

1. step-up Auto transformer :-

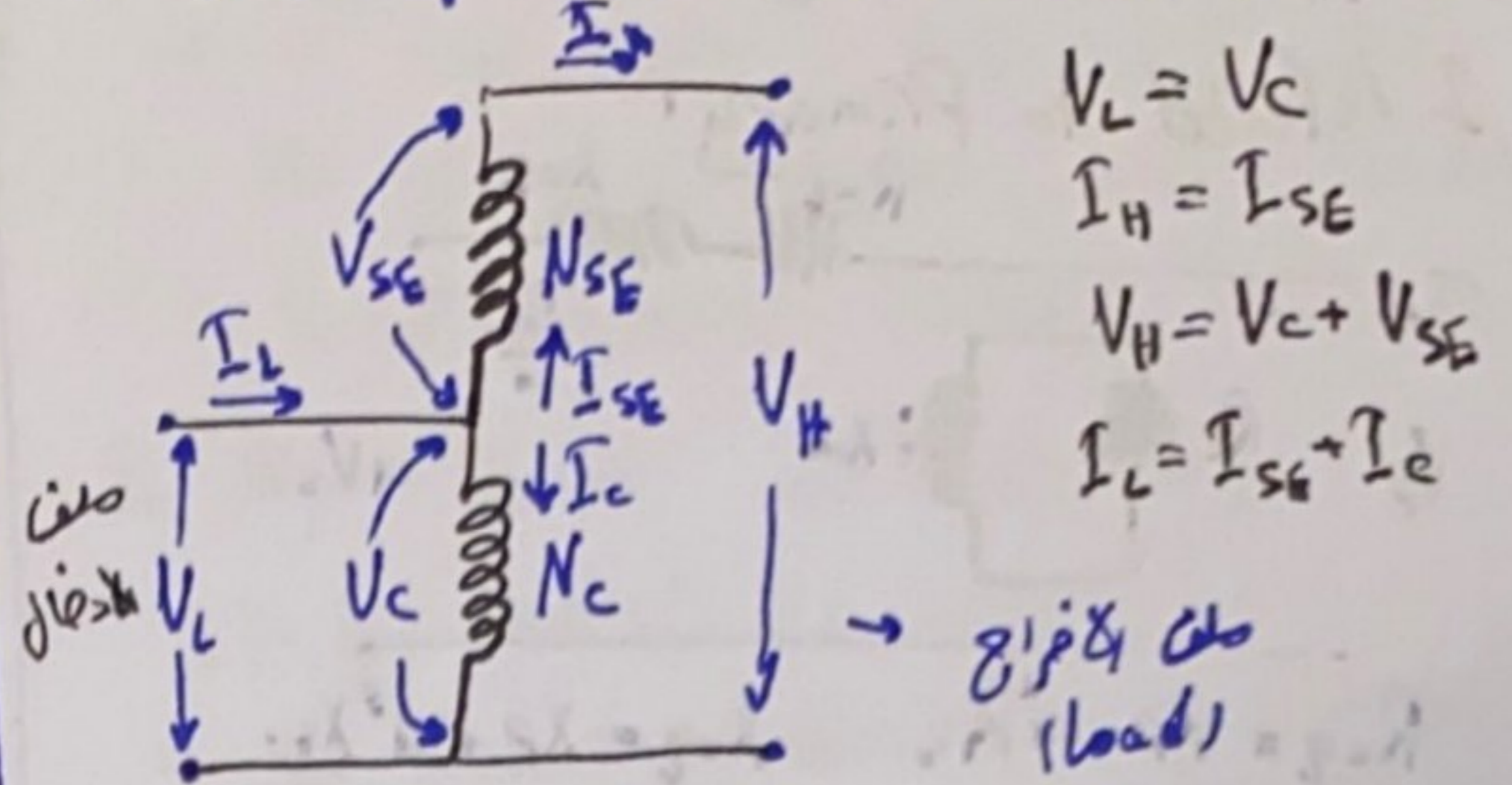

$$V_L = V_c$$

$$I_H = I_{se}$$

$$V_H = V_c + V_{se}$$

$$I_L = I_{se} + I_c$$


VH → high Voltage side

VL → low Voltage side.

Vc → Common Voltage

Vse → Series Voltage.

2. step-down Auto transformer :-

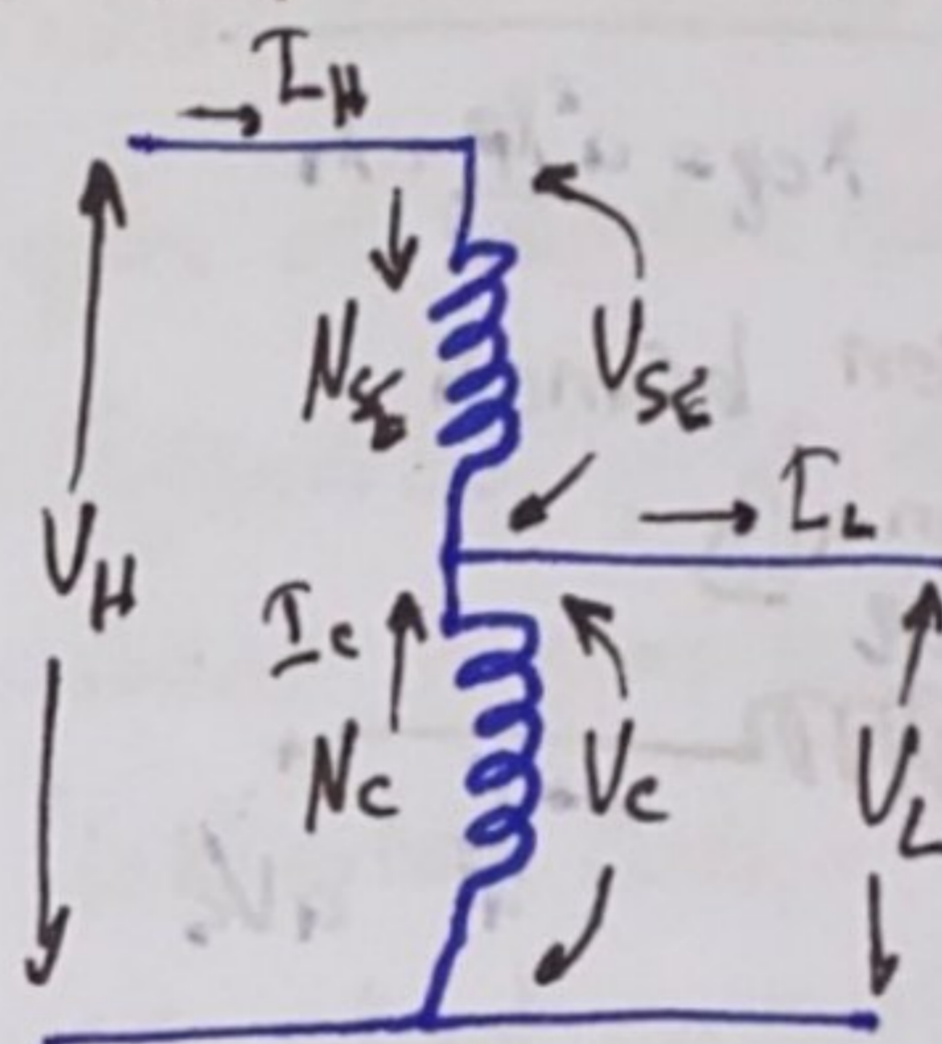

$$V_L = V_c$$

$$V_H = V_c + V_{se}$$

$$I_L = I_c + I_{se}$$

$$I_H = I_{se}$$

Voltage Relationship

Current Relationship

$$\frac{V_L}{V_H} = \frac{N_c}{N_{se} + N_c}$$

$$\frac{I_L}{I_H} = \frac{N_{se} + N_c}{N_c}$$

$$\frac{V_L}{V_H} = \frac{I_H}{I_L} = \frac{N_c}{N_{se} + N_c}$$

* Apparent Power Rating advantage.

$$S_{in} = V_L I_L \quad S_{out} = V_H I_H$$

$$S_{in} = S_{out} = S_{io} \rightarrow \text{Input output Power}$$

$$S_w = V_c I_c = V_{se} I_{se} \rightarrow \text{Winding Power.}$$

$$S_w = S_{io} \left(\frac{N_{se}}{N_c + N_{se}} \right)$$

$$\frac{S_{io}}{S_w} = \frac{N_c + N_{se}}{N_{se}}$$


* Electrical Machines:

* The Transformers:

* Three-Phase Transformers

* Connection for Three Phase Transformers:-


1. Wye-Wye (Y-Y) connection:-

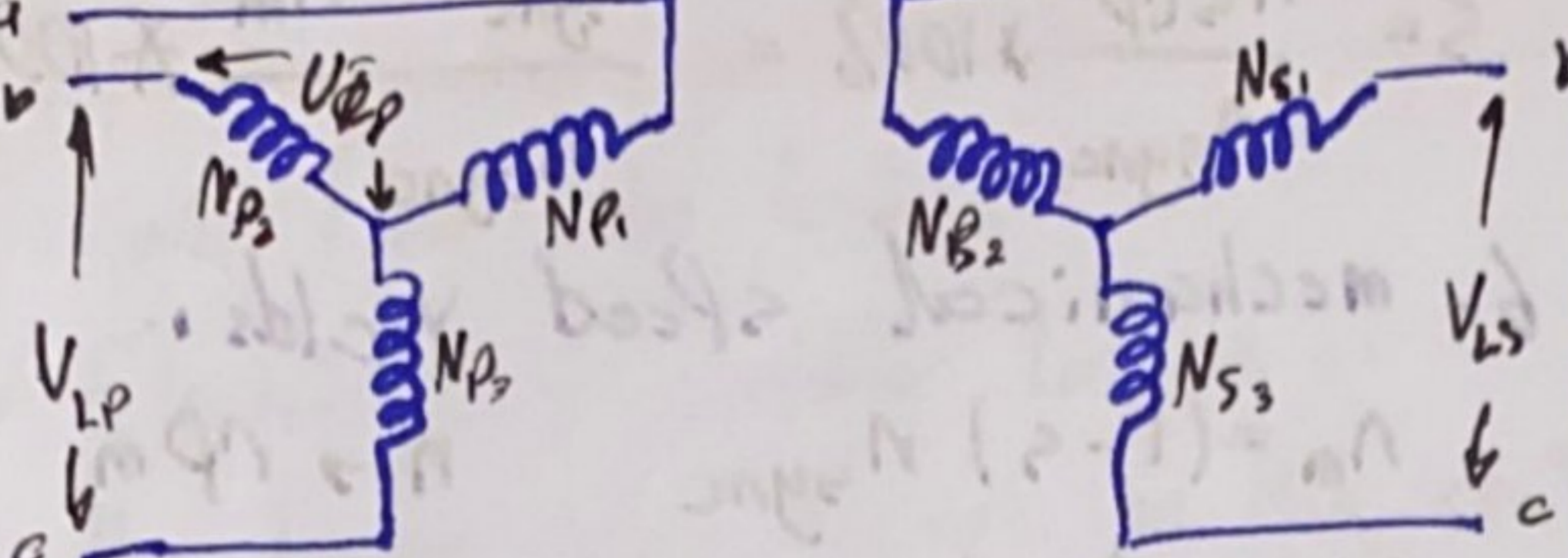

$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3} V_{\phi P}}{\sqrt{3} V_{\phi S}} = a$$

$$\frac{V_{LP}}{V_{LS}} = a$$


2. Delta-Delta (D-D) connection:-

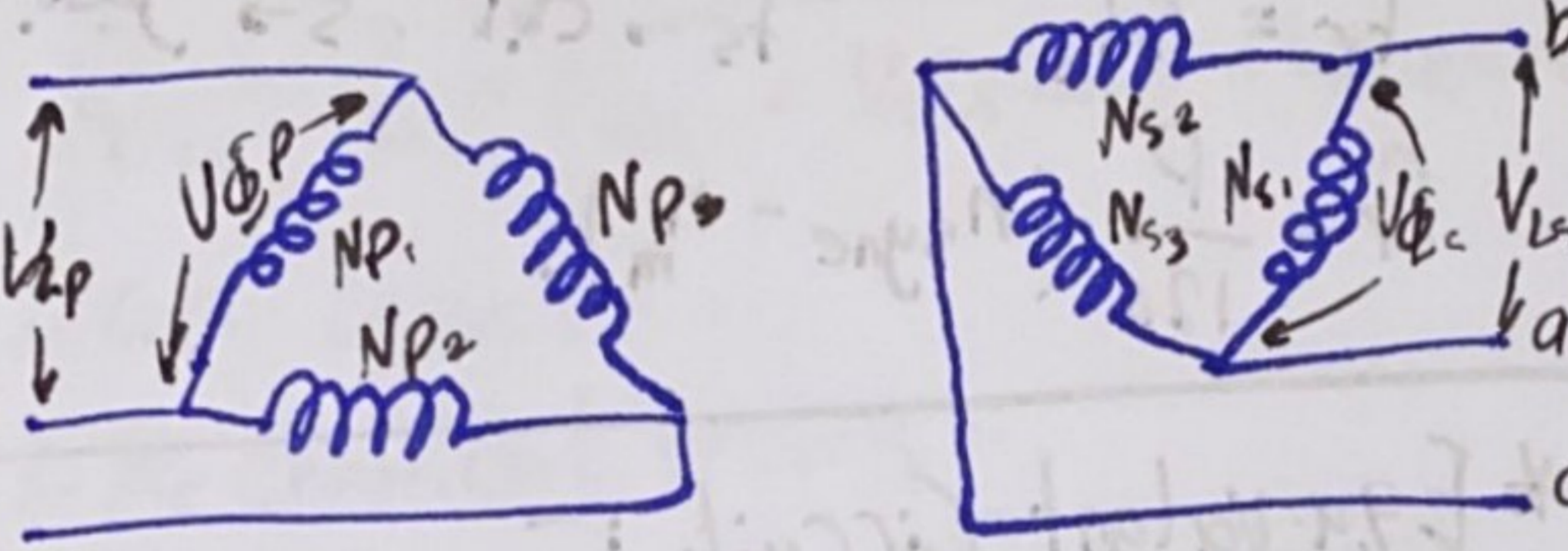

$$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{V_{\phi S}} = a$$

$$\frac{V_{LP}}{V_{LS}} = a$$


3. Wye-Delta (Y-D) connection:-

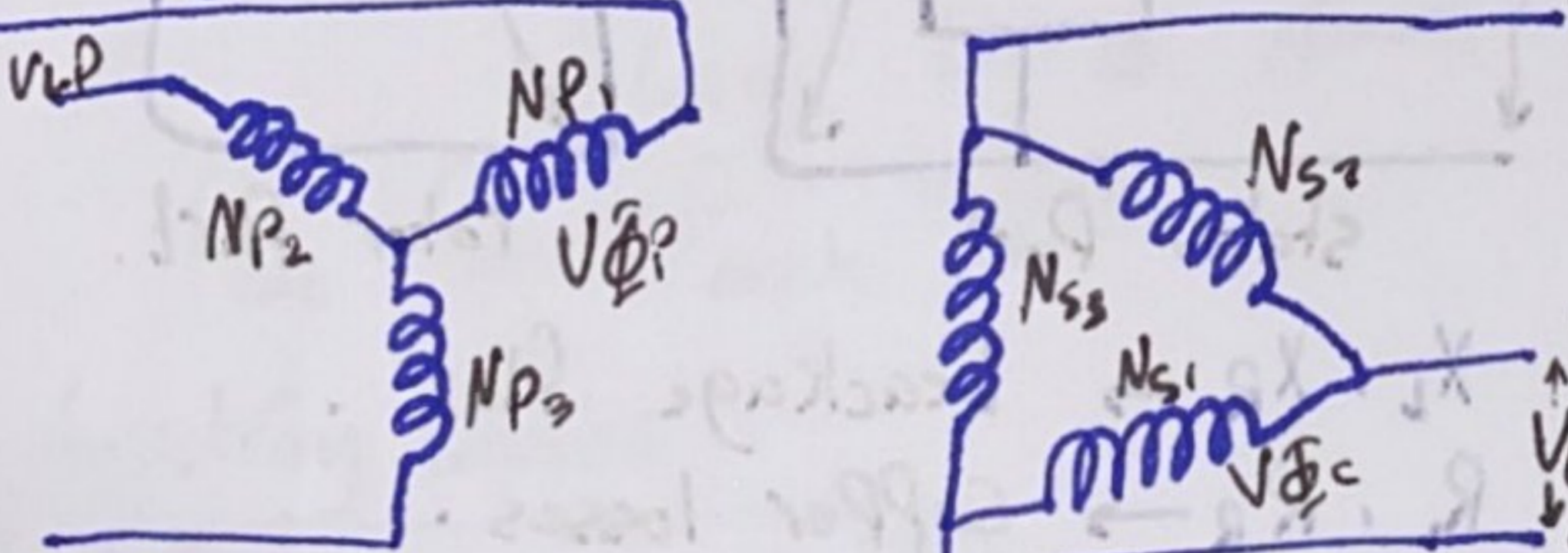

$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3} V_{\phi P}}{V_{\phi S}} = \sqrt{3} a$$

$$\frac{V_{LP}}{V_{LS}} = \sqrt{3} a$$

4. Delta-Wye (D-Y) connection:-

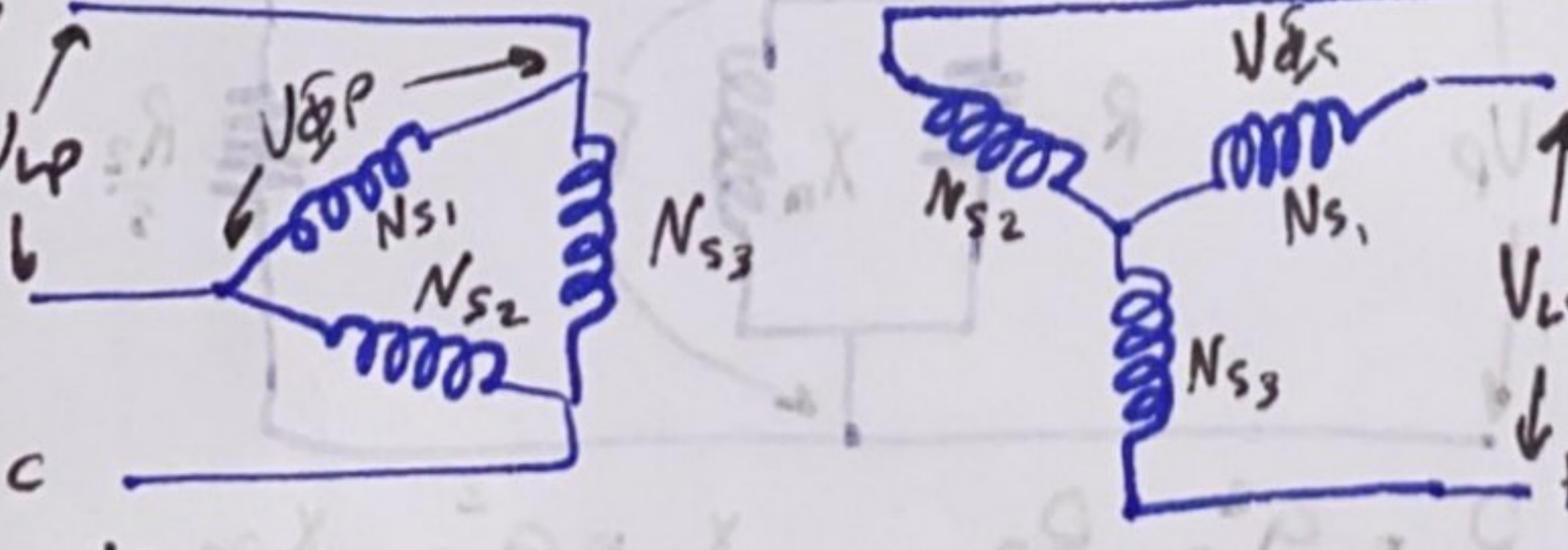

$$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{\sqrt{3} V_{\phi S}} = \frac{a}{\sqrt{3}}$$

$$\frac{V_{LP}}{V_{LS}} = \frac{a}{\sqrt{3}}$$

* Problems of connections:-


1. Wye-Wye (Y-Y) connection
 - a. If loads are unbalanced, then the voltages become unbalanced.
 - b. Third-harmonic voltages be large.
2. Wye-Delta and Delta-Wye (Y-D) and (D-Y) connection:-
 - a. the secondary voltage is shifted 30° relative to the primary voltage.
3. Delta-Delta (D-D) connection:-
 - a. has no phase shift and no problems.

* Induction Motors:-

* Types of Induction motors:-

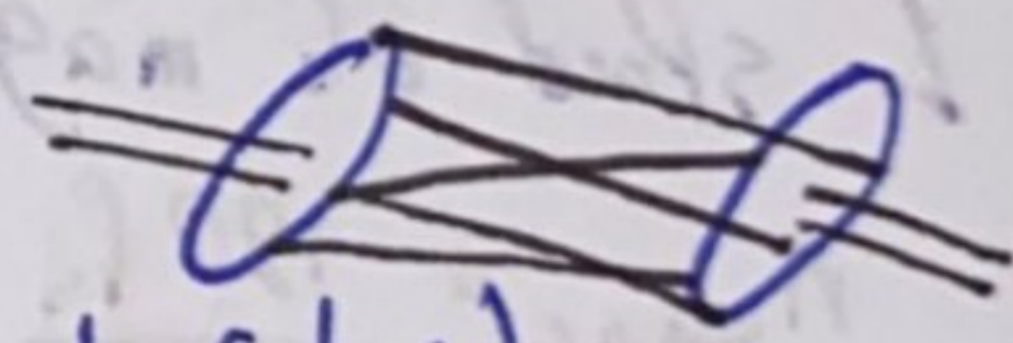1. Squirrel cage induction motors:-

- rotor is simplest, cylindrical laminated core, rotor conductors are short circuit with end rings, impossible to connect extra resistance, higher efficiency, low starting torque.



2. slip ring (wound rotor) induction motor:-

- rotor is wound, carbon brushes, cylindrical laminated core, starting the windings are connected to (Y) connected rheostat, possible to connect extra resistance, less efficiency, high starting torque, less starting current.

* Electrical Machines :-

* Induction Motors :-

* Rotor conductors are skewed because

1. to prevent the cogging phenomenon

مع ظاهرة cogging التي تحدث في المحرك عند بدء التشغيل
بسبب تفاعل المجال المغناطيسي بين الأجزاء الكهربية
في rotor و stator مما يؤدي إلى قفل المحرك في بعض المواضع

2. to avoid crawling phenomenon.

ظاهرة crawling التي تحدث في بعض المحركات الكهربائية
بسبب زيادة المقاومة في rotor

3. to increase rotor resistance

لزيادة سرعة الدوران في بعض المحركات
من خلال زيادة المقاومة في rotor
 $R_r = \frac{P_L}{P}$

4. to improve starting torque and starting power factor

5. increasing effective magnetic coupling between stator and rotor

* Basic Concepts of operation :-

1. speed of magnetic field's rotation

$$n_{sync} = \frac{120 f_s}{p}$$

$f_s \rightarrow$ system freq
 $p \rightarrow$ # of poles

2. Voltage induced in a rotor bar

$$E_{ind} = (V \times B_s) \cdot L$$

3. Induced torque in the machine

$$I_s \rightarrow B_s \quad I_r \rightarrow B_r$$

$$T_{ind} = k B_r \times B_s = k B_r B_s \sin \theta$$

$$\Sigma T = JX \Rightarrow T_{ind} - T_{load} = JX$$

6

* Basic concepts of operation :-

4. slip speed.

$$n_{slip} = n_{sync} - n_m$$

$n_{sync} \rightarrow$ سرعة دوران المجال المغناطيسي
 $n_m \rightarrow$ سرعة دوران shaft

5. slip :- $0 \leq s \leq 1$

$$s = \frac{n_{slip}}{n_{sync}} \times 100\% = \frac{n_{sync} - n_m}{n_{sync}} \times 100\%$$

6. mechanical speed yields.

$$n_m = (1-s) n_{sync}$$

$n \rightarrow$ rpm

$$\omega_m = (1-s) \omega_{sync}$$

$\omega \rightarrow$ r/s

$$n = \frac{\pi}{3} \omega, \quad \omega = \frac{3\pi}{\pi} n$$


7. rotor frequency :-

$$f_r = s f_s$$

$f_s \rightarrow$ C.V.V, $s \rightarrow$ تنغير

$$f_r = \frac{p}{120} (n_{sync} - n_m)$$

* Equivalent Circuit :-

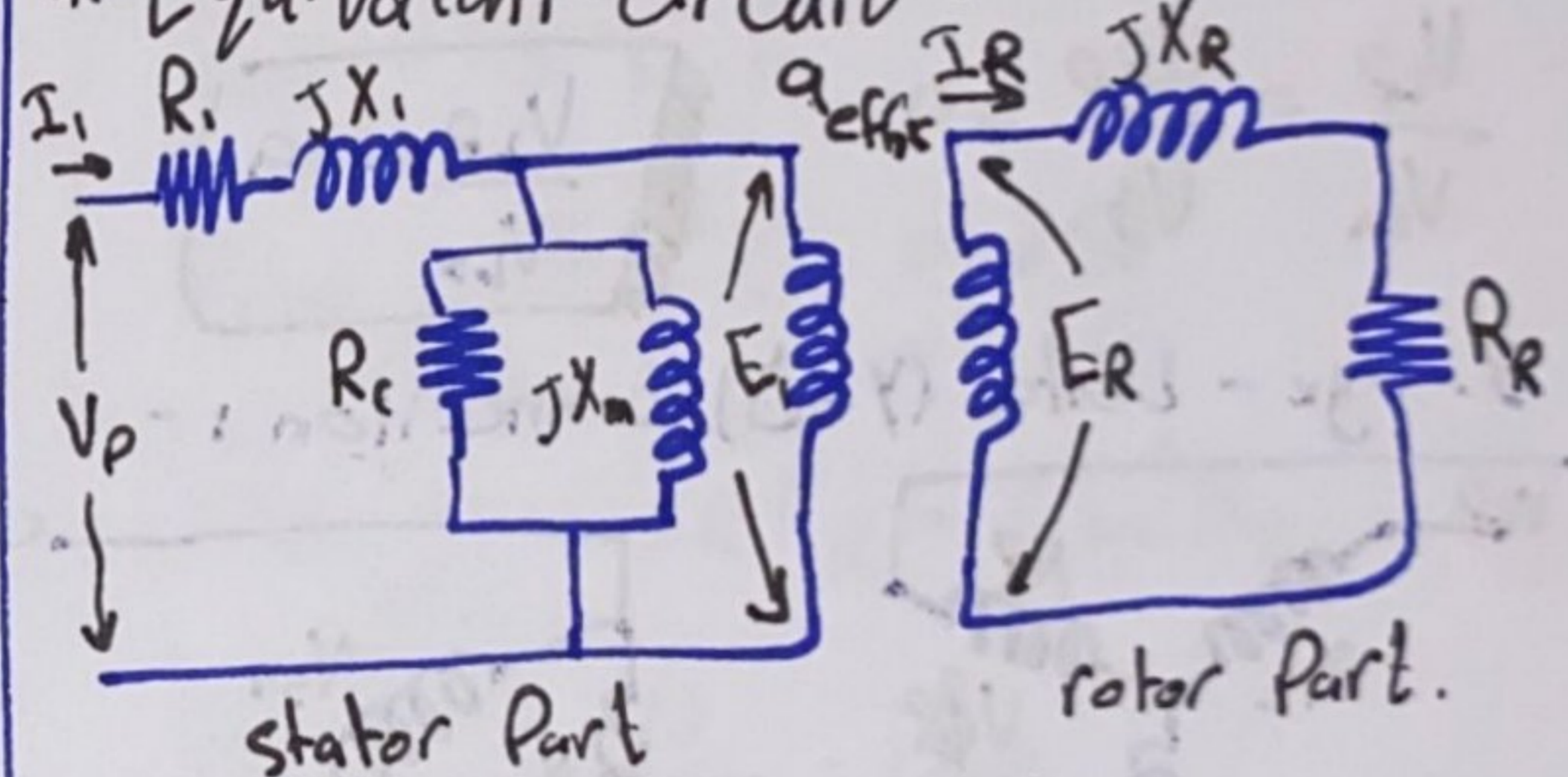


$X_1, X_r \rightarrow$ Leakage flux.

$R_1, R_r \rightarrow$ Copper losses.

$R_c \rightarrow$ core losses.

$X_m \rightarrow$ Magnetization losses.

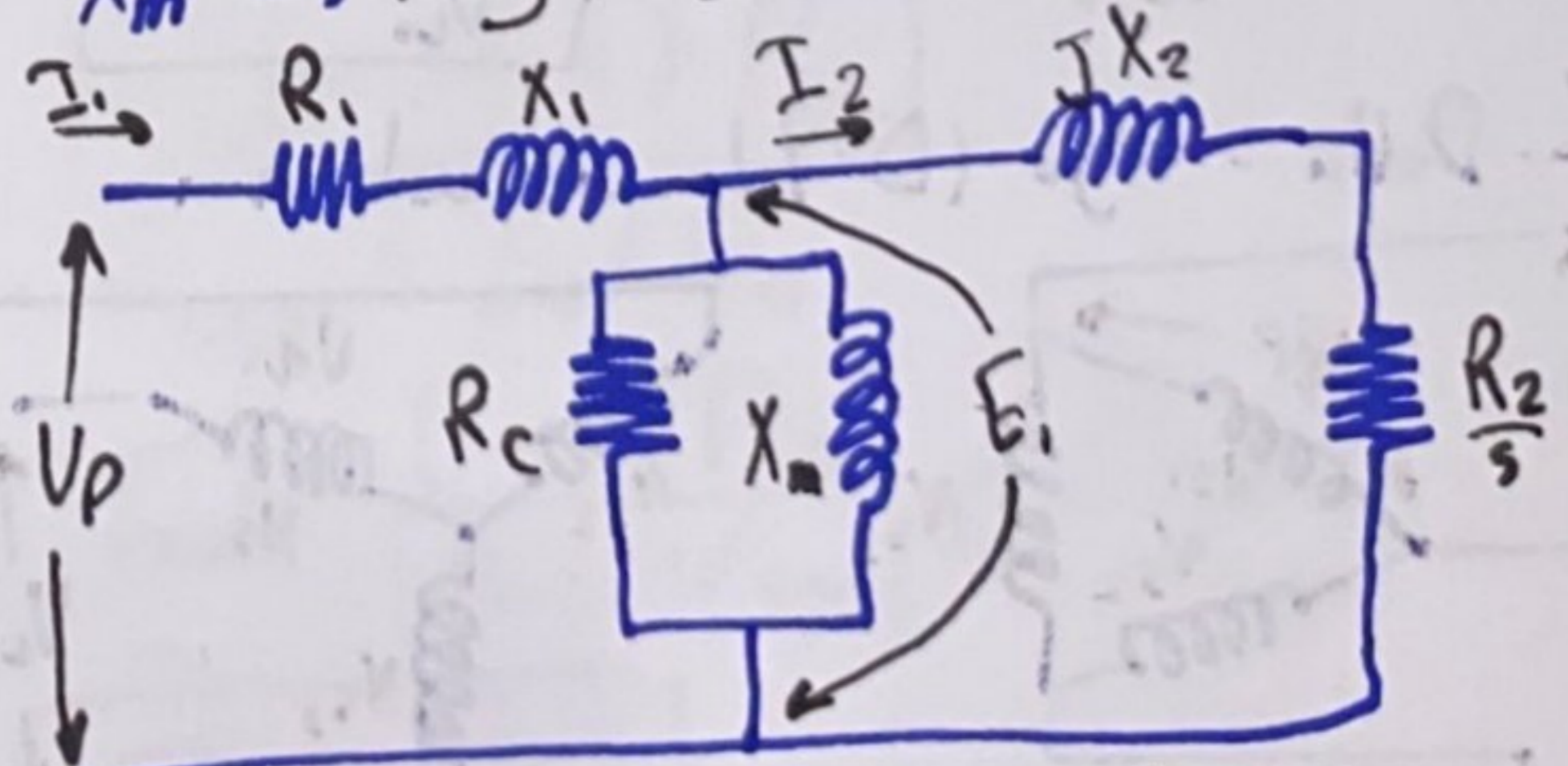

$$R_2 = a_{eff}^2 R_r$$

$$X_2 = a_{eff}^2 X_{r0}$$

$$E_r = s E_{r0}, \quad X_r = s X_{r0}, \quad I_2 = \frac{I_r}{a_{eff}}$$

* Electrical Machines :-

* Induction Motors :-

* The efficiency of an AC machine :-

$$\eta = \frac{P_{out}}{P_{in}} * 100\% = \frac{P_{in} - P_{loss}}{P_{in}} * 100\%$$

* Power flow and losses :-

1. Electrical or Copper losses :-

the losses that occur in the stator and rotor winding of the machine.

Stator losses $P_{scl} = V_s I_s \cos \phi$

Rotor losses $P_{rcL} = V_r I_r \cos \phi$

$$P_{Elec} = P_{scl} + P_{rcL} = V_s I_s \cos \phi + V_r I_r \cos \phi$$

2. Core losses .

3. Mechanical losses :-

1. Friction losses .

2. Winding losses .

core and mechanical losses


no load .

$$P_{tot} = P_{core} + P_{mech} = VI$$

4. stray losses :-

$$P_{stray} = 0.01 * P_{in}$$

* Power flow and losses :-

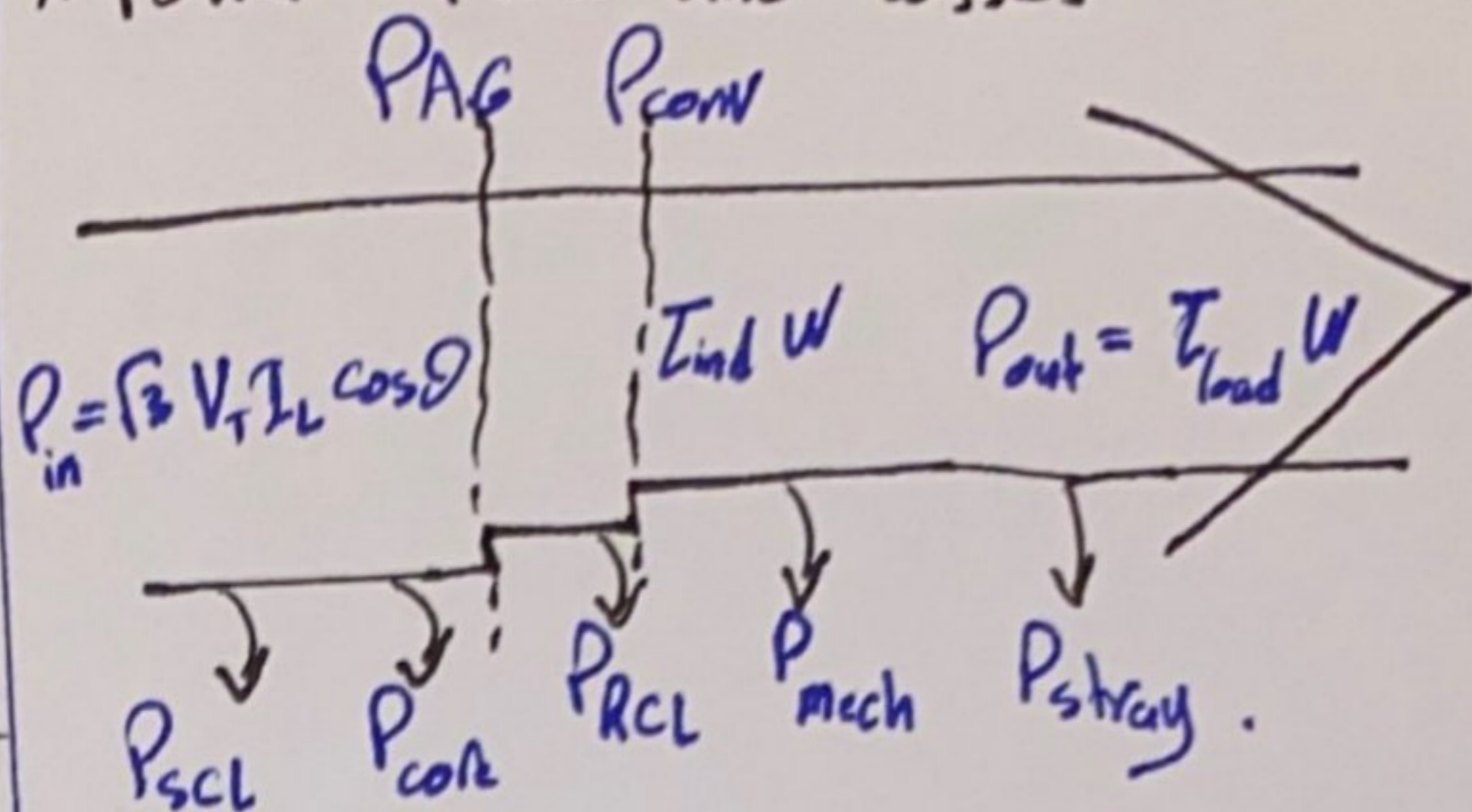

$$P_{in} = \sqrt{3} V_T I_L \cos \phi$$

$$P_{out} = T_{load} W_m$$

$$P_{scl} = I_1^2 R_1, \quad P_{rcL} = I_2^2 R_2$$

$$P_{AG} = P_{in} - P_{scl} - P_{core}$$

$$P_{conv} = P_{AG} - P_{rcL}$$

$$P_{out} = P_{in} - P_{scl} - P_{rcL} - P_{stray} - P_{mech} - P_{core}$$

$$P_{out} = P_{conv} - P_{stray} - P_{mech}$$

* Total power on 3-Phase Winding :-

$$P_{scl\ total} = 3 I_1^2 R_1$$

$$P_{core\ total} = 3 E_1^2 G_c = \frac{3 E_1^2}{R_c}$$

$$P_{rcL\ total} = 3 I_2^2 R_2$$

$$P_{AG} = P_{in} - P_{scl} - P_{core}$$

$$P_{AG} = 3 I_2^2 \frac{R_2}{s}$$

$$P_{conv} = 3 I_2^2 R_2 \left(\frac{1-s}{s} \right)$$

$$P_{conv} = (1-s) P_{AG}$$

$$P_{conv} = T_{ind} W_m$$

$$T_{ind} = \frac{(1-s) P_{AG}}{(1-s) W_{sync}} = \frac{P_{AG}}{W_{sync}}$$

$$T_{ind} = \frac{P_{AG}}{W_{sync}}$$