

Wires

Dr. Bassam Jamil

**Adopted from slides of the
textbook**

Outline


- ❑ Introduction
- ❑ Interconnect Modeling
 - Wire Resistance
 - Wire Capacitance
- ❑ Interconnect Impact
 - Wire RC Delay
 - Crosstalk
 - Wire Engineering
- ❑ Repeaters

Introduction

- ❑ Chips are mostly made of wires called *interconnect*
 - In stick diagram, wires set size
 - Transistors are little things under the wires
 - Many layers of wires
- ❑ Wires are as important as transistors
 - Speed
 - Power
 - Noise
- ❑ Alternating layers run orthogonally

Wire Geometry

 
- ❑ Pitch = $w + s$
- ❑ Aspect ratio: $AR = t/w$
 - Old processes had $AR \ll 1$
 - Modern processes have $AR \approx 2$
 - Pack in many skinny wires



Layer Stack


- ❑ Example of old process: AMI 0.6 μm process has 3 metal layers
 - M1 for within-cell routing
 - M2 for vertical routing between cells
 - M3 for horizontal routing between cells
- ❑ Modern processes use 6-10+ metal layers
 - M1: thin, narrow ($< 3\lambda$)
 - High density cells
 - Mid layers
 - Thicker and wider, (density vs. speed)
 - Top layers: thickest
 - For V_{DD} , GND, clk

Example

 

Intel 90 nm Stack

[Thompson02]

 


Intel 45 nm Stack

[Moon08]

Lumped Element Models

 - ❑ Wires are a distributed system
 - Approximate with lumped element models



- ❑ 3-segment π -model is accurate to 3% in simulation
- ❑ L-model needs 100 segments for same accuracy!
- ❑ Use single segment π -model for Elmore delay

Wire Resistance

□ $\rho = \text{resistivity } (\Omega \cdot \text{m})$


$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$

□ $R_{\square} = \text{sheet resistance } (\Omega/\square)$

– □ is a dimensionless unit(!)

□ Count number of squares

 – $R = R_{\square} * (\# \text{ of squares})$





Choice of Metals

- ❑ Until 180 nm generation, most wires were **aluminum**
- ❑ Contemporary processes normally use **copper**
 - Cu atoms diffuse into silicon and damage FETs
 - Must be surrounded by a diffusion barrier

Metal	Bulk resistivity ($\mu\Omega \cdot \text{cm}$)
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Titanium (Ti)	43.0

Contacts Resistance

  
- ❑ Contacts and vias also have 2-20 Ω
- ❑ Use many contacts for lower R
 - Many small contacts for current crowding around periphery



Copper Issues

- ❑ Copper must be surrounded by a lower-conductivity diffusion barrier which effectively reduces the wire cross-sectional area and increases resistance.
- ❑ Copper is also prone to *dishing* during polishing
- ❑ Effective resistance is higher
 
$$R = \frac{\rho}{(t - t_{\text{dish}} - t_{\text{barrier}})} \frac{l}{(w - 2t_{\text{barrier}})}$$



Cu Wire Example

- ❑ Compute the sheet resistance of a 0.22 μm thick Cu wire in a 65 nm process. The resistivity of thin film Cu is $2.2 \times 10^{-8} \Omega \cdot \text{m}$. Ignore dishing.


$$R_{\square} = \frac{2.2 \times 10^{-8} \Omega \cdot \text{m}}{0.22 \times 10^{-6} \text{ m}} = 0.10 \Omega/\square$$

- ❑ Find the total resistance if the wire is 0.125 μm wide and 1 mm long. Ignore the barrier layer.

$$R = (0.10 \Omega/\square) \frac{1000 \mu\text{m}}{0.125 \mu\text{m}} = 800 \Omega$$

Wire Capacitance

 - ❑ Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- ❑ $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$



Capacitance Trends


- ❑ Parallel plate equation: $C = \epsilon_{ox} A/d$
 - Wires are not parallel plates, but obey trends
 - Increasing area (W, t) increases capacitance
 - Increasing distance (s, h) decreases capacitance
- ❑ Dielectric constant
 - $\epsilon_{ox} = k\epsilon_0$
 - $\epsilon_0 = 8.85 \times 10^{-14}$ F/cm
 - $k = 3.9$ for SiO_2
- ❑ Processes are starting to use low-k dielectrics
 - $k \approx 3$ (or less) as dielectrics use air pockets

Capacitance Formula

- ❑ Capacitance of a line without neighbors can be approximated as


$$C_{tot} = \epsilon_{ox} l \left[\frac{w}{h} + 0.77 + 1.06 \left(\frac{w}{h} \right)^{0.25} + 1.06 \left(\frac{t}{h} \right)^{0.5} \right]$$

 - ❑ This empirical formula is accurate to 6% for $AR < 3.3$



M2 Capacitance Data

 - Typical dense wires have ~ 0.2 fF/ μm
 - Compare to 1-2 fF/ μm for gate capacitance



Diffusion & Polysilicon


- ❑ Diffusion capacitance is very high (1-2 fF/ μm)
 - Comparable to gate capacitance
 - Diffusion also has high resistance
 - Avoid using diffusion *runners* for wires!
- ❑ Polysilicon has lower C but high R
 - Use for transistor gates
 - Occasionally for very short wires between gates

Wire RC Delay Example

- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 1 mm wire. Assume :
 - Wire capacitance is 0.2 fF/ μm and resistance of the Cu Wire example (in earlier slide)
 - A unit-sized inverter has $R = 10 \text{ K}\Omega$ and $C = 0.1 \text{ fF}$.

$$t_{pd} = (1000 \Omega)(100 \text{ fF}) + (1000 + 800 \Omega)(100 + 0.6 \text{ fF}) = 281 \text{ ps}$$

 Intrinsic delay
(due to diffusion cap)
is ignored.



Wire Delay Example (2)

Find the RC flight time per mm^2 for a wire using the parameters from Example 6.3. Express the result in FO4/ mm^2 , if the FO4 inverter delay is 15 ps. What is the flight time to cross a 10 mm die?

SOLUTION: $R = 800 \Omega/\text{mm}$. $C = 0.2 \text{ pF}/\text{mm}$. The flight time is $RC/2 = 80 \text{ ps}/\text{mm}^2$, or $5.3 \text{ FO4}/\text{mm}^2$. The flight time across a 10 mm die is thus 530 FO4, which is dozens of clock cycles.


Lumped RC Network/Tree

$$\square R_{44} = R_1 + R_3 + R_4$$

$$\square R_{i4} = R_1 + R_3$$

$$\square R_{i2} = R_1$$
 
$$\square \tau_{Di} = r_1 (c_1 + c_2) \\ + (r_1 + r_3) (c_3 + c_4) \\ + (r_1 + r_3 + r_i) c_i$$



Wire Delay Example (3)


Example 6.5

Figure 6.15 models a gate driving wires to two destinations. The gate is represented as a voltage source with effective resistance R_1 . The two receivers are located at nodes 3 and 4. The wire to node 3 is long enough that it is represented with a pair of π -segments, while the wire to node 4 is represented with a single segment. Find the Elmore delay from input x to each receiver.

SOLUTION: The Elmore delays are

$$T_{D_3} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + R_1 C_4 \quad (6.18)$$
 
$$T_{D_4} = R_1 C_1 + R_1 (C_2 + C_3) + (R_1 + R_4) C_4$$



Wire Energy

- Estimate the energy per unit length to send a bit of information (one rising and one falling transition) in a CMOS process.

- $E = E_{C(\text{rising})} + E_{C(\text{falling})} +$
 $= \frac{1}{2} C V^2 + \frac{1}{2} C V^2$


- $E = (0.2 \text{ pF/mm})(1.0 \text{ V})^2 = 0.2 \text{ pJ/bit/mm}$
 $= 0.2 \text{ mW/Gbps/mm}$

Crosstalk

- ❑ A capacitor does not like to change its voltage instantaneously.
- ❑ A wire has high capacitance to its neighbor.
 - When the neighbor switches from 1- \rightarrow 0 or 0- \rightarrow 1, the wire tends to switch too.
 - Called capacitive *coupling* or *crosstalk*.
- ❑ Crosstalk effects
 - Noise on nonswitching wires
 - Increased delay on switching wires

Crosstalk Delay

 - ❑ Assume layers above and below on average are quiet
 - Second terminal of capacitor can be ignored
 - Model as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- ❑ Effective C_{adj} depends on behavior of neighbors
 - *Miller effect*




B	ΔV	$C_{\text{eff(A)}}$	MCF
Constant	V_{DD}	$C_{\text{gnd}} + C_{\text{adj}}$	1
Switching with A	0	C_{gnd}	0
Switching opposite A	$2V_{\text{DD}}$	$C_{\text{gnd}} + 2C_{\text{adj}}$	2

Crosstalk Noise

- ❑ Crosstalk causes noise on nonswitching wires
- ❑ If victim is floating:
 - model as capacitive voltage divider
 
$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$




Driven Victims

- Usually victim is driven by a gate that fights noise
 - Noise depends on relative resistances
 - Victim driver is in linear region, agg. in saturation
 - If sizes are same, $R_{\text{aggressor}} = 2-4 \times R_{\text{victim}}$


$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \frac{1}{1+k} \Delta V_{\text{aggressor}}$$
 
$$k = \frac{\tau_{\text{aggressor}}}{\tau_{\text{victim}}} = \frac{R_{\text{aggressor}} (C_{\text{gnd-a}} + C_{\text{adj}})}{R_{\text{victim}} (C_{\text{gnd-v}} + C_{\text{adj}})}$$



Coupling Waveforms

 - Simulated coupling for $C_{adj} = C_{victim}$





Noise Implications

- ❑ *So what* if we have noise?
- ❑ If the noise is **less than the noise margin**, nothing happens
- ❑ **Static CMOS** logic will eventually settle to correct output even if disturbed by large noise spikes
 - But glitches cause extra delay
 - Also cause extra power from false transitions
- ❑ **Dynamic logic never recovers** from glitches
- ❑ **Memories** and other sensitive circuits also can produce the wrong answer

Repeaters

  - ❑ R and C are proportional to
- ❑ RC delay is proportional to
 - Unacceptably great for long wires
- ❑ Break long wires into N shorter segments
 - Drive each one with an inverter or buffer



Repeater Design


- ❑ How many repeaters should we use?
- ❑ How large should each one be?
- ❑ Equivalent Circuit
 - Wire length l/N
 - Wire Capacitance $C_w * l/N$, Resistance $R_w * l/N$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W

Repeater Results

$$t_{pd} = N \left[\frac{R}{W} \left(C_w \frac{l}{N} + CW (1 + p_{inv}) \right) + R_w \frac{l}{N} \left(\frac{C_w}{2} \frac{l}{N} + CW \right) \right]$$

- Differentiate with respect to W and N. Set equal to 0, solve
 
$$\frac{l}{N} = \sqrt{\frac{2RC(1 + p_{inv})}{R_w C_w}}$$



$$\frac{t_{pd}}{l} = \left(2 + \sqrt{2(1 + p_{inv})} \right) \sqrt{RCR_w C_w} \approx 1.67 \sqrt{FO4 R_w C_w}$$

$$W = \sqrt{\frac{RC_w}{R_w C}}$$

Repeater Energy

- ❑ Energy / length $\approx 1.87C_w V_{DD}^2$
 - 87% premium over unrepeated wires
 - The extra power is consumed in the large repeaters
- ❑ If the repeaters are downsized for minimum EDP:
 - Energy premium is only 30%
 - Delay increases by 14% from min delay

Repeater Example

Example 6.10

Compute the delay per mm of a repeated wire in a 65 nm process. Assume the wire is on a middle routing layer and has 2x width, spacing, and height, so its resistance is 200 Ω /mm and capacitance is 0.2 pF/mm. The FO4 inverter delay is 15 ps. Also find the repeater spacing and driver size to achieve this delay and the energy per bit.

SOLUTION: Using EQ (6.29), the delay is
$$\frac{t_{pd}}{l} = \left(2 + \sqrt{2(1 + p_{inv})}\right) \sqrt{RCR_w C_w} \approx 1.67 \sqrt{FO4 R_w C_w}$$


$$t_{pd} = 1.67 \sqrt{(15 \text{ ps})(200 \text{ } \Omega/\text{mm})(0.2 \text{ pF}/\text{mm})} = 41 \text{ ps}/\text{mm} \quad (6.32)$$

This delay is achieved using a spacing of 0.45 mm between repeaters and an nMOS driver width of 18 μ m (180x unit size). The energy per bit is 0.4 pJ/mm.

$$\text{Energy / length} \approx 1.87 C_w V_{DD}^2$$

Skin Effect

 - At high frequency, current tends to flow near the surface of the conductor, and thus reducing the effective cross-sectional area of the thick conductor and raising resistance.
- Skin depth (δ) is the depth where the current falls off e^{-1} value. ($e^{-1} = 0.37$)



Therefore, the skin depth for a conductor is

$$\delta = \sqrt{\frac{2\rho}{\omega\mu}} \quad (6.14)$$

where μ is the magnetic permeability of the dielectric (normally the same as in free space, $4\pi \times 10^{-7}$ H/m). T

Therefore, the frequency associated with the edge can be approximated as

$$\omega = \frac{2\pi}{8.65 t_{rf}} \quad (6.15)$$

where t_{rf} is the average 20–80% rise/fall time.

Skin Depth Example

Determine the skin depth for a copper wire in a chip with 20 ps edge rates.

SOLUTION: According to EQ (6.15), the maximum frequency of interest is

$$\omega = \frac{2\pi}{8.65 \times 20 \text{ ps}} = 3.6 \times 10^{10} \text{ rad/s} = 5.8 \text{ GHz}$$