

## Electrical Circuit Lab

### Experiment Six: Step Response of AC Circuit

Student's Name:

ID:


Razan Monther Jaradat

1931783

#### 1- Transient RL Circuit

- a. Construct the following circuit.
- b. Measure the internal resistance of the inductor.

Element	Unit	Theoretical	Measured
R1	KΩ	1.2	1.19
R2	Ω	10	9.9
$R_{int}$	Ω		12.3
L	mH	1	
$\tau$	s	$8.264 \times 10^{-7}$	

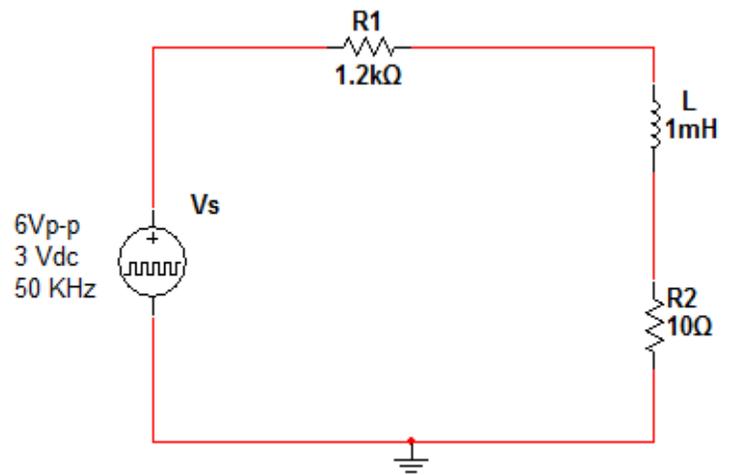

- c. Calculate the time constant  $\tau$ .

$$\tau = \frac{L}{R_{eq}} = \frac{1 \times 10^{-3}}{1200 + 10} = 8.264 \times 10^{-7} \text{ s}$$

- d. Draw the inductor current & evaluate it at  $t = \tau, 3\tau$  and  $5\tau$ .

At  $t = \tau$  :

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ 1 - e^{-\frac{t}{\tau}} \right] = \frac{6(1 - \frac{1}{e})}{1210} = 3.134 \text{ mA}$$

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ e^{-\frac{t}{\tau}} \right] = \frac{6(\frac{1}{e})}{1210} = 1.8242 \text{ mA}$$

At  $t = 3\tau$  :

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ 1 - e^{-\frac{3t}{\tau}} \right] = \frac{6(1 - \frac{1}{e^3})}{1210} = 4.712 \text{ mA}$$

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ e^{-\frac{3t}{\tau}} \right] = \frac{6(\frac{1}{e^3})}{1210} = 0.2469 \text{ mA}$$

At  $t = 5\tau$  :

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ 1 - e^{-\frac{5t}{\tau}} \right] = \frac{6(1 - \frac{1}{e^5})}{1210} = 4.925 \text{ mA}$$

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ e^{-\frac{5t}{\tau}} \right] = \frac{6(\frac{1}{e^5})}{1210} = 0.0334 \text{ mA}$$

## Electrical Circuit Lab

### Experiment Six: Step Response of AC Circuit

Student's Name:

ID:

- e. Draw the voltage source and inductor voltage in the same graph.

$$V_{pp} = 54 \text{ mV}$$


$$I_{pp} = \frac{V_{pp}}{R} = 5.4 \text{ mA}$$

#### 2- Transient RC Circuit

- a. Construct the following circuit.  
b. Calculate the time constant  $\tau$ .

c.  $\tau = R_{eq} \times C = 1210 \times 680 \times 10^{-9} = 8.228 \times 10^{-4} \text{ s}$

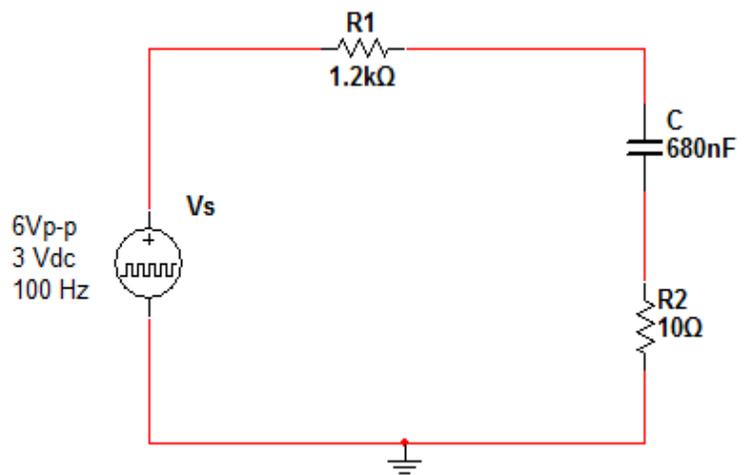- d. Draw the capacitor voltage & evaluate it at  $t = \tau, 3\tau$  and  $5\tau$ .



At  $t = \tau$  :

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ 1 - e^{-\frac{t}{\tau}} \right] = \frac{6(1 - \frac{1}{e})}{1210} = 3.134 \text{ mA}$$

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ e^{-\frac{t}{\tau}} \right] = \frac{6(\frac{1}{e})}{1210} = 1.8242 \text{ mA}$$

At  $t = 3\tau$  :

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ 1 - e^{-\frac{3t}{\tau}} \right] = \frac{6(1 - \frac{1}{e^3})}{1210} = 4.712 \text{ mA}$$

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ e^{-\frac{3t}{\tau}} \right] = \frac{6(\frac{1}{e^3})}{1210} = 0.2469 \text{ mA}$$

At  $t = 5\tau$  :

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ 1 - e^{-\frac{5t}{\tau}} \right] = \frac{6(1 - \frac{1}{e^5})}{1210} = 4.925 \text{ mA}$$

$$I(t) = \frac{V_s}{R_1 + R_2} \left[ e^{-\frac{5t}{\tau}} \right] = \frac{6(\frac{1}{e^5})}{1210} = 0.0334 \text{ mA}$$

# Electrical Circuit Lab

## Experiment Six: Step Response of AC Circuit

Student's Name:


ID:

- e. Draw the voltage source and capacitor current in the same graph.

$$\frac{V_{R2}}{R2} = IR_2 = I(t)$$

$$V_{R2} = 49.6 \text{ mA}$$

$$\frac{49.6}{10} = 4.96 \text{ mA}$$


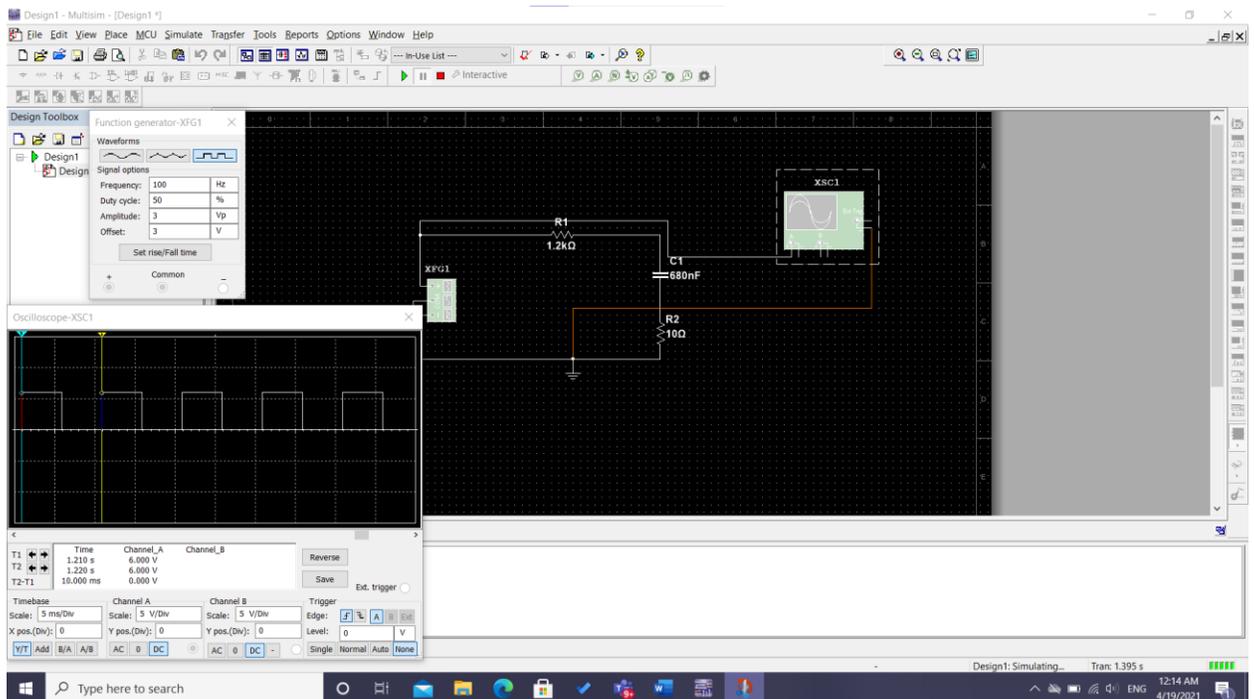


# Electrical Circuit Lab

## Experiment Six: Step Response of AC Circuit

Student's Name:

ID:

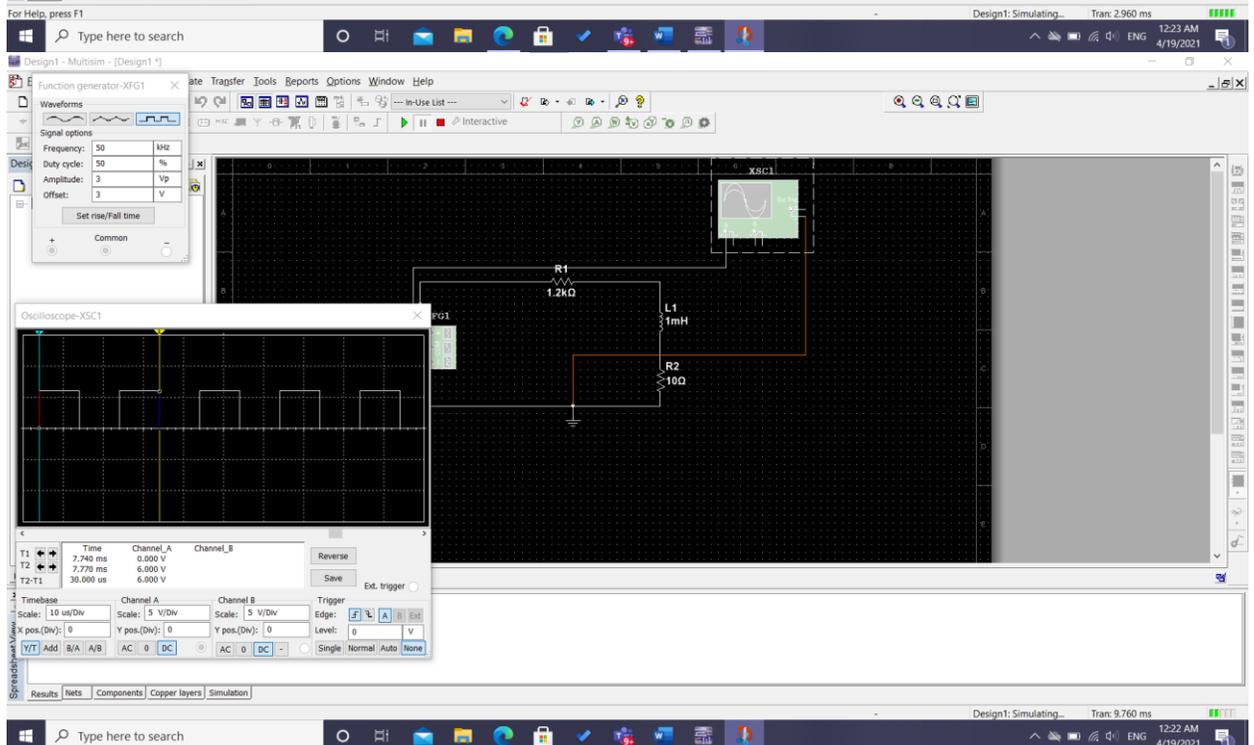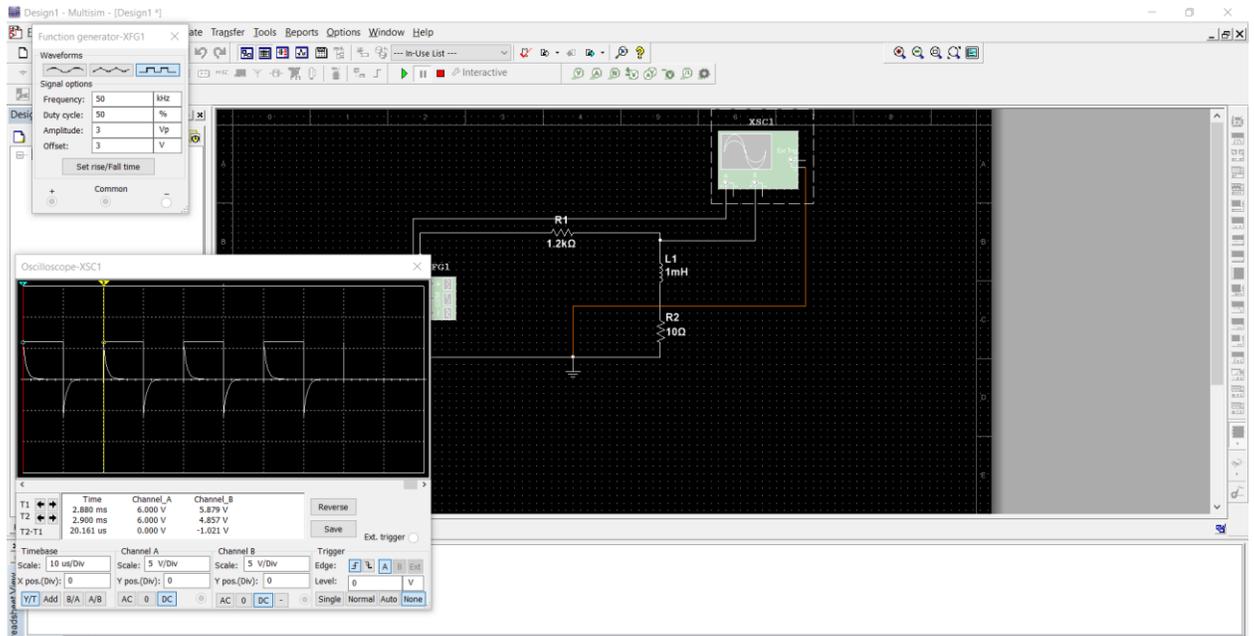

# Electrical Circuit Lab

## Experiment Six: Step Response of AC Circuit

Student's Name:

ID:

