

Name:

ID:

Razan Monther Jaradat.

1931783

- Construct the circuits shown below and answer the following questions.

A- RL Circuit


- 1- V_L [lag, Lead, In phase]with I_L ?

Lag

- 2- Find the magnitude of V_L , V_R and I_L ?

- 3- Find the phase shift between V_s and I_s ?

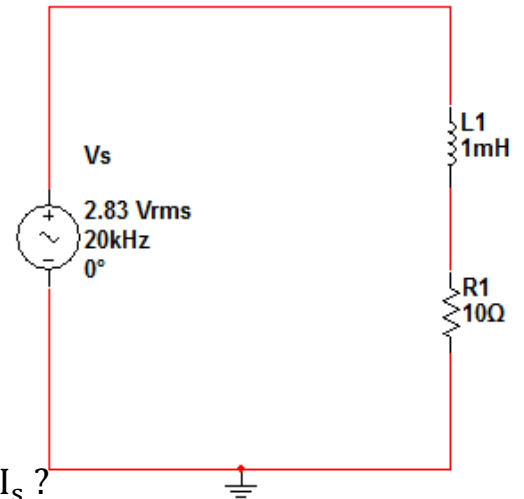- 4- Plot V_s and I_s on the same graph ?



$$V_p = V_{rms} \times \sqrt{2} = 2.83 \times \sqrt{2} = 4 \text{ V}$$

$$W = 2 \times \pi \times f = 2 \times \pi \times 20000 = 40000\pi, \quad W \times L = 40\pi$$

$$I_L = \frac{V_p}{\sqrt{R^2 + (WL)^2}} = 0.032 \text{ mA}$$


$$V_R = I_L \times R = 0.032 \times 10 = 0.32 \text{ V}$$

$$\theta = \tan^{-1} \left(\frac{40\pi}{10} \right) = 85.5^\circ$$

$$V_L = 0.032 * 125.66 = 4.02$$

Name:

ID:

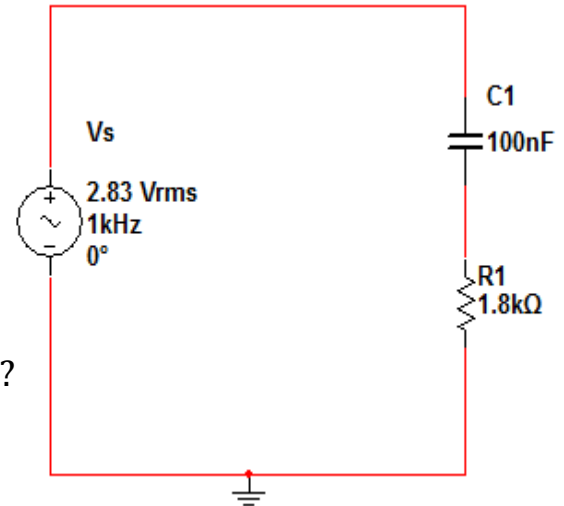B- RC Circuit1- V_C [lag, Lead, In phase]with I_C ?**Lead**2- Find the magnitude of V_C , V_R and I_C ?3- Find the phase shift between V_s and I_s ?4- Plot V_s and I_s on the same graph ?

$$V_p = V_{rms} \times \sqrt{2} = 2.83 \times \sqrt{2} = 4 V$$

$$W = 2 * \pi * f = 2000\pi$$

$$I_c = \frac{V_p}{\sqrt{R^2 + (1/WC)^2}} = 0.7 \mu A$$

$$\theta = \tan^{-1} \left(\frac{1}{1800 * 2000 * \pi * 100 * 10^{-9}} \right) = 89.4^\circ$$

Name:

ID:

