



تقدم لجنة EiCoM الاكاديمية

دفتر لمادة:

الات كهربائية

من شرح:

محمد ملاح

جزيل الشكر للطالب:

ليث تفاع



Introduction

By

Dr. Mohammad Salah

Mechatronics Engineering Department
The Hashemite University

Introduction

المركبات الكهربائية

محول كهربائي = تحويل
تحويل

▶ An **Electric Machine** is a general term for **electric motors** and **electric generators** and other **electromagnetic machines**.

تحويل كهربائي

▶ They are **electromechanical energy converters**: an **electric motor converts electricity to mechanical power** while an **electric generator converts mechanical power to electricity**.


تحويل كهربائي = تحويل
تحويل كهربائي ← تحويل

▶ **Electric machines, in the form of generators, produce virtually all electric power on Earth, and in the form of electric motors consume approximately 60% of all electric power produced.**

مولدات الكهرباء تنتج 100% من الطاقة الكهربائية
محركات الكهرباء تستهلك 60% من الطاقة الكهربائية

تحويل كهربائي = تحويل

Electrical Machines

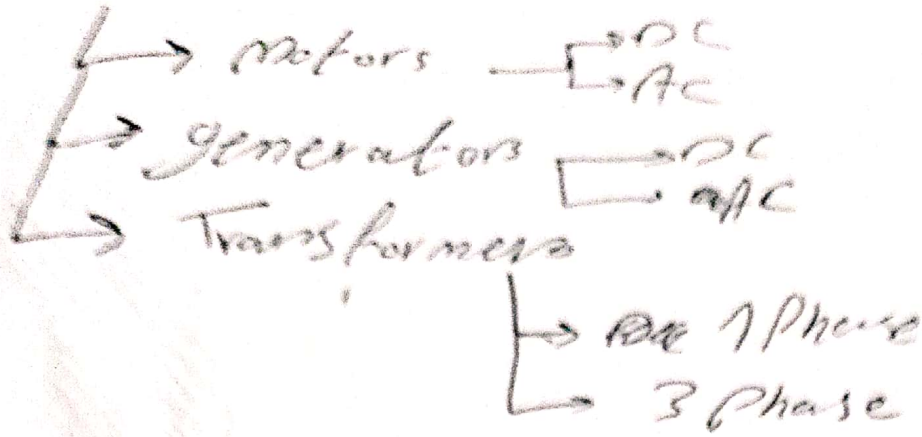

Transformers \Rightarrow $\begin{matrix} \text{در جریان ولتاژ کمتری} \\ \text{در ولتاژ ولتاژ بیشتری} \end{matrix}$

$$\begin{matrix} V_1 I_1 \\ \text{---} \\ 1 \end{matrix} \Rightarrow \begin{matrix} V_2 I_2 \\ \text{---} \\ 2 \end{matrix}$$


generators \Rightarrow $\begin{matrix} \text{در ولتاژ ولتاژ بیشتری} \\ \text{در جریان ولتاژ کمتری} \end{matrix}$

Motors \Rightarrow $\begin{matrix} \text{در ولتاژ ولتاژ کمتری} \\ \text{در جریان ولتاژ بیشتری} \end{matrix}$

در ولتاژ کمتری در جریان بیشتری


Asynchronous

Introduction

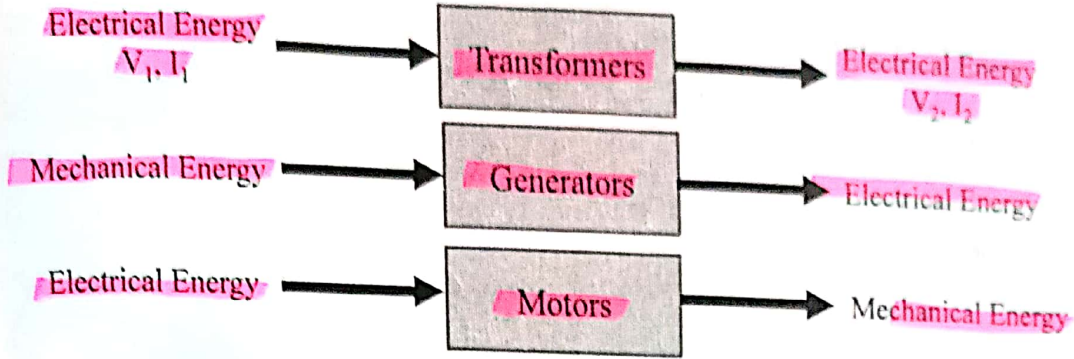

- ▶ The common variable in all machines is the magnetic field (Φ). $F \propto X$
- ▶ Without a magnetic field, machines CANNOT work.

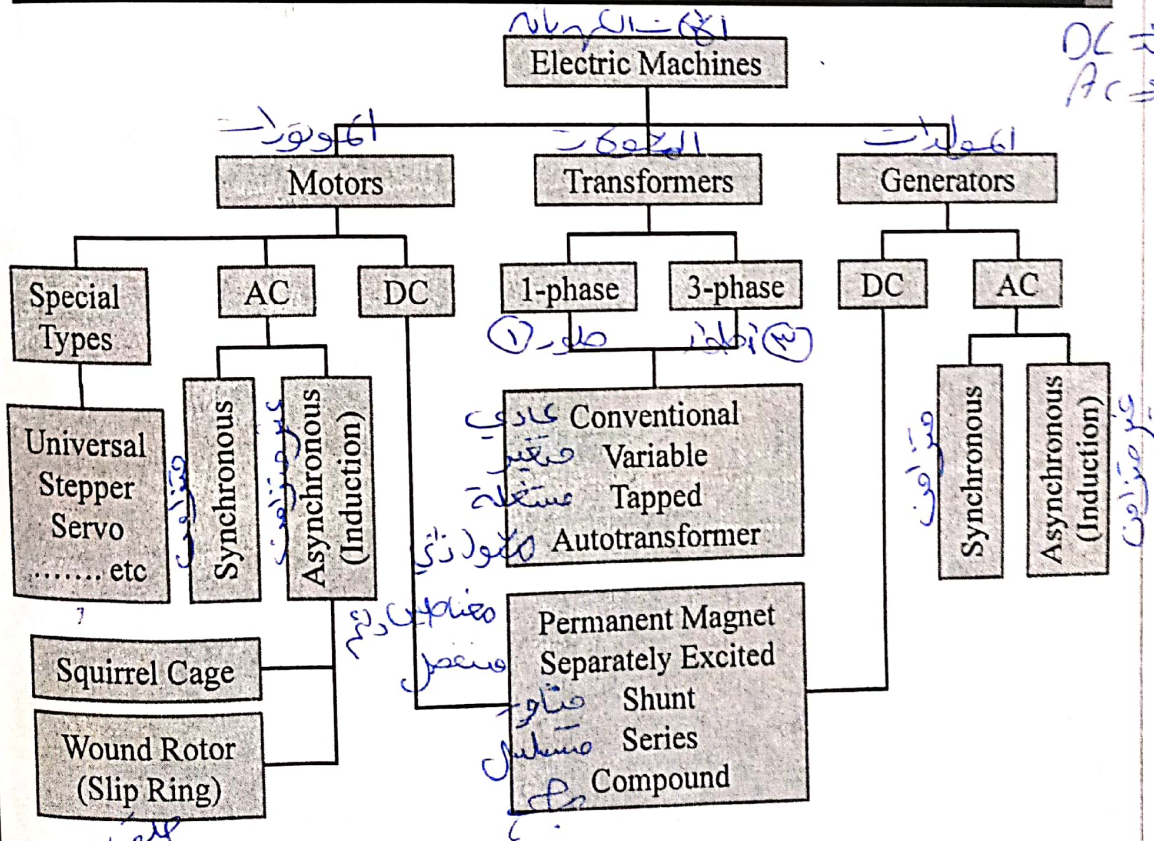المجال المغناطيسي المشترك في جميع الآلات هو الفيض Φ $F \propto X$



* تقاس السرعة بالسرديات في الحركات الدورانية

* لحائتي على الألة = اي حركتها حركة

فوتونات ومولات

تكون حركتها وبالعادة تكون على
الحركة دائرية وعشان تغير عنا صغير عننا
اما سرعة او مركز دوران

السرعة تقاس في أغلب المواضع في الحركات

(rpm) \Rightarrow revolution per minute


$$1 \text{ [rpm]} = \frac{\pi}{30} \text{ [r/s]}$$

(تقسيم الألفي)

$$1 \text{ r/s} = \frac{30}{\pi} \text{ rpm}$$

$$50 \text{ r/s} = \frac{30}{\pi} \times 50 = \frac{60 \times 30}{\pi} = X$$

$$X = \frac{1500}{\pi} \text{ rpm}$$

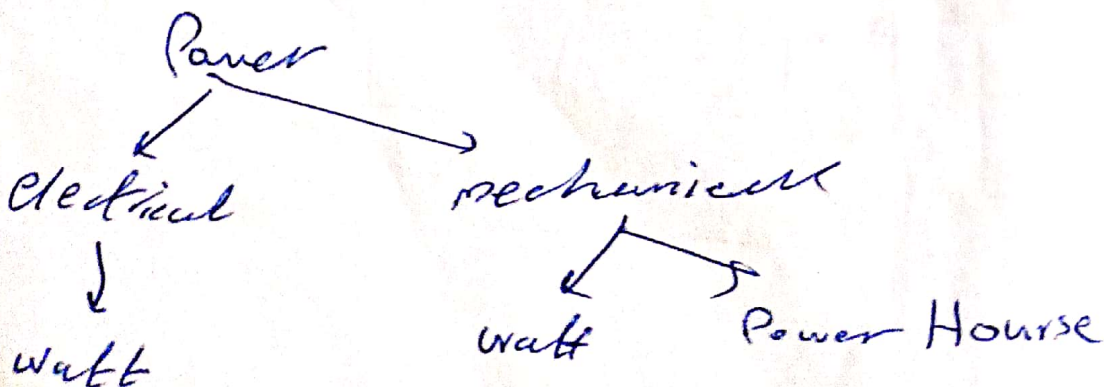

الآلات الدوارة

Introduction

- In rotary machines, speed is measured in radian per second [r/s] or revolution per minute [rpm] such that:

$$1 \text{ [rpm]} = 1 \left[\frac{\text{revolution}}{\text{minute}} \right] = 1 \left[\frac{2\pi \text{ [rad]}}{60 \text{ [sec]}} \right] = \frac{\pi}{30} \text{ [r/s]}$$

Example: Convert 50 [r/s] to [rpm]

$$1 \text{ [r/s]} = \frac{30}{\pi} \text{ [rpm]} \Rightarrow 50 \text{ [r/s]} = 50 \times \frac{30}{\pi} \text{ [rpm]} \\ = \frac{1500}{\pi} \text{ [rpm]} \\ \cong 477.5 \text{ [rpm]}$$

عدد الدورات في الدقيقة

القدرة الكهربائية تقاس بالواط أو الكيلو وات
القدرة الميكانيكية تقاس بالواط

Introduction

- In all motors and generators, electric power is measured in Watts [W].
- On the other hand, mechanical power is measured either in Watts [W] or Hours Power [hp] so that:

$$1 \text{ [hp]} = 746 \text{ [W]}$$

Example: Convert 5 [kW] to [hp]

$$5 \text{ [kW]} = 5000 \text{ [W]} = 5000 \times \frac{1}{746} \text{ [hp]} \\ \cong 6.7 \text{ [hp]}$$

1k = 1000

الطاقة الميكانيكية
HP
تقاس بالواط
تبع الـ 746

أقل بكثير من 5000
تقريباً 6.7

$$P = \int \tau \omega$$

\swarrow القدرة \downarrow العزم \searrow السرعة

$$P \Rightarrow [W] \begin{cases} \rightarrow \tau \rightarrow N \cdot m \\ \rightarrow \omega \rightarrow r/s \end{cases}$$

ازدبيك أخبر عن ال Power لوحة او watt
 كرم العزم يكون لوحة اكمالي سيوتت
 والسرعة بار r/s :

⊗ اذا كان عني ال r/s فانه لوحة او rpm
 كرم ال هولها ال r/s و اذا كنت
 ال r/s فانه لوحة نسبة كرم ال هولها ال
 N.M


لو رطل بيوتي
 ال P بلد
 HP بحسب
 لعين ديتل

DC Machine electrical Power
 القدرة الكهرطانية

$$P = I V$$

\downarrow w \downarrow A \downarrow v

AC machine electrical Power

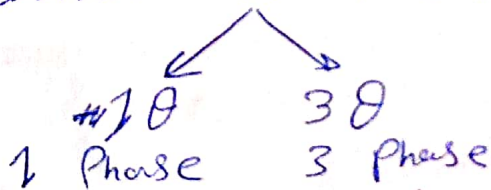

$$\text{Active Power} = I V \cos \theta$$

$$\text{Active Power} = \sqrt{3} I V \cos \theta$$

\downarrow line current \downarrow line voltage

OR

$$\text{Active Power} = 3 I V \cos \theta$$

\downarrow Phase current \downarrow Phase voltage

Intro

Mechanical Power = $T \cdot \omega$
 ↓ Torque ↓ Speed
 [N.m] [r/s]

الطاقة الميكانيكية = التورق × السرعة
 [N.m] ⇒ N.m (تورق)
 [r/s] ⇒ r/s (سرعة)

Power → DC machines
 $P = IV$
 → AC machines

↓ 1 phase ↓ 3 phase

Active Power = $I V \cos \theta$
 Active Power line = $\sqrt{3} I_L V_L \cos \theta$
 Active Power phase = $3 I_p V_p \cos \theta$

► It should be noted that the mechanical power can be computed from the torque and speed as:

Power [W] = Torque [N.m] × Speed [r/s]

► Moreover, electrical power can be computed as:

DC Machines ⇒ Power [W] = Current [A] × Voltage [V]

AC Machines - 1φ ⇒ Single Phase

Active Power [W] = Current [A] × Voltage [V] × cos(θ)

AC Machines - 3φ ⇒ Three Phase

Active Power [W] = $\sqrt{3}$ × Line Current [A] × Line Voltage [V] × cos(θ)

Active Power [W] = 3 × Phase Current [A] × Phase Voltage [V] × cos(θ)

الطاقة الكهربائية = التيار × الجهد


Introduction – Magnetic Circuits

► As mentioned before, machines cannot work without magnetic fields. Hence, studying magnetic circuits is an important topic to understand the basic principles of electric machines operation and characteristics.

► Magnetic fields are the fundamental mechanism by which energy is converted from one form to another in motors, generators, and transformers.

الطاقة الكهربائية

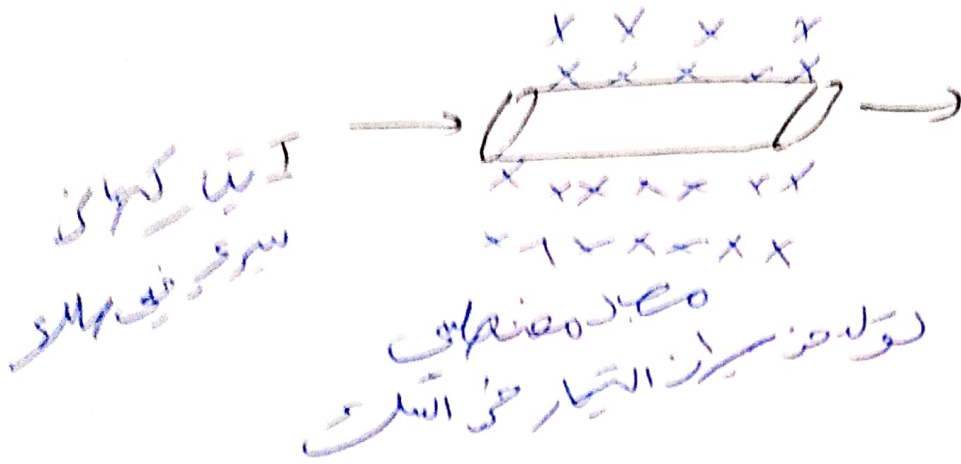1) إذا كان عذب سلك سريعاً بما يتناسب مع سرعة مرور هذا التيار
 في هذا السلك ربح ليد معاً معاً في كل من السلك
 وهذه طاقة من ظواهر الكهرومغناطيسية



2) إذا كان عذب مجال مغناطيسي يتغير مع الزمن ويولد تياراً
 من التيارات المتغيرة ذلك في كل الحالات
 في كل هذه الحالات (صباح على الامتحان)

3) إذا كان عذب تيار سري في سلك وهذا السلك سريع
 في مجال مغناطيسي متغير في كل الحالات
 قوة تيار التي تحرك السلك داخل هذا المجال
 (صباح على الامتحان)

4) إذا كان في سلك تياراً متغيراً في مجال مغناطيسي متغير
 ذلك في كل الحالات في كل هذه الحالات
 (صباح على الامتحان)

Introduction – Magnetic Circuits

Four basic principles describe how magnetic fields are used in these devices:

1. A current-carrying wire produces a magnetic field in the area around it.
2. A time-changing magnetic field induces a voltage in a coil of wire if it passes through that coil. (This is the basis of transformer action.)
3. A current-carrying wire in the presence of a magnetic field has a force induced on it. (This is the basis of motor action.)
4. A moving wire in the presence of a magnetic field has a voltage induced in it. (This is the basis of generator action.)

Introduction – Magnetic Circuits

تقوله القوة الدافعة
المغناطيسية
من حث في موصل
من حث في موصل
من حث في موصل
من حث في موصل
من حث في موصل
(F)

The total flux in the core due to the current i in the winding is

$$\phi = BA = \mu \frac{NiA}{l_c}$$

where ϕ is measured in Webers [Web] and B is measured in Webers per square meters [Web/m²] known as Tesla [T]

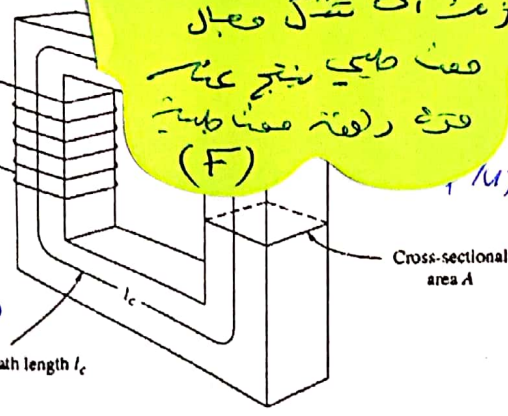


FIGURE 1-3 A simple magnetic core.

التيار هو
حلوله حث
مغناطيسي
تقوله الحث
كأنه يولد
قوة دافعة
مغناطيسية
(F)
التي هي
من حث في موصل
من حث في موصل
من حث في موصل
من حث في موصل
من حث في موصل

B: كثافة
الحث
المغناطيسي
N عدد
اللفات
i تيار
A مساحة
الطرف
Average
Path
μ
المغناطيسية
المادة
المغناطيسية
المغناطيسية

Tesla = web/m²
Permeability

F: Magnetomotive Force

Φ : Flux

R: reluctance of circuit.

μ : Magnetic Permeability of material

H: Magnetic Field Intensity

$$\begin{aligned}\Phi &= BA = \frac{\mu Ni A}{L_c} \\ \Phi &= \frac{F}{R} \\ B &= \frac{\mu Ni}{L_c}, B = \mu H \\ H &= \frac{Ni}{L_c} = \frac{F}{L_c} \\ F &= Ni \quad R = \frac{L_c}{\mu A}\end{aligned}$$

Introduction – Magnetic Circuits


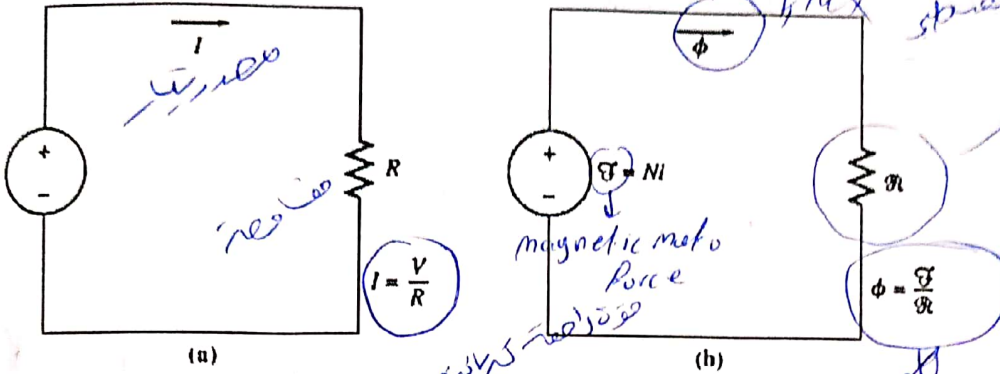


FIGURE 1-4 (a) A simple electric circuit. (b) The magnetic circuit analog to a transformer core.

The magnetic circuit model of magnetic behavior is often used in the design of electric machines and transformers to simplify the otherwise quite complex design process.

Introduction – Magnetic Circuits

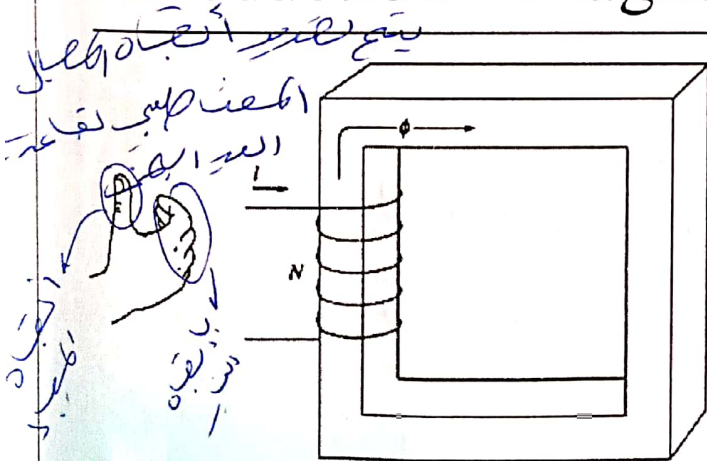

The reluctance of a magnetic circuit is the counterpart of electrical resistance, and its units are ampere-turns per weber

$$\phi = BA = \mu H A$$

$$\phi = \mu \left(\frac{Ni}{l_c} \right) A = Ni \left(\frac{\mu A}{l_c} \right)$$

$$\phi = \mathcal{F} \left(\frac{\mu A}{l_c} \right) = \frac{\mathcal{F}}{\mathcal{R}}$$

- \mathcal{F} = magnetomotive force of circuit
- ϕ = flux of circuit
- \mathcal{R} = reluctance of circuit
- μ = magnetic permeability of material
- H = magnetic field intensity

FIGURE 1-5 Determining the polarity of a magnetomotive force source in a magnetic circuit.

حسابات افعال المختلط بعد Core راي تبع
بالمختص حسابات الفرة المختلطة رايه تقريبي
ونسبة الاطراف 5%

وهو العلامة بار ال Permeability
كانها فعلية في صفت ثالثة بالتاكيد حساباتنا
ر؟ تكون $\pm 5\%$

الاجال المختلط ايجاد ابي اعتمدا عليه لغيره
ان الاجال ثابت ضمن ال Core المختلط
وهو الكلام غير صحيح والى في صفة
تتراوح بين 6000 الى 6000

كثير من ال Fraction هو يتبع الاجال المختلط
بمجرد ان ال Core
من فعلية في

سواء ال Core
سواء ال Core
سواء ال Core


الاجال يخرج للمصنوع Surrounding

وهو الاجال ابي برامته


leakage flux

الورد كثير في

المكانات
التي يكون فيها

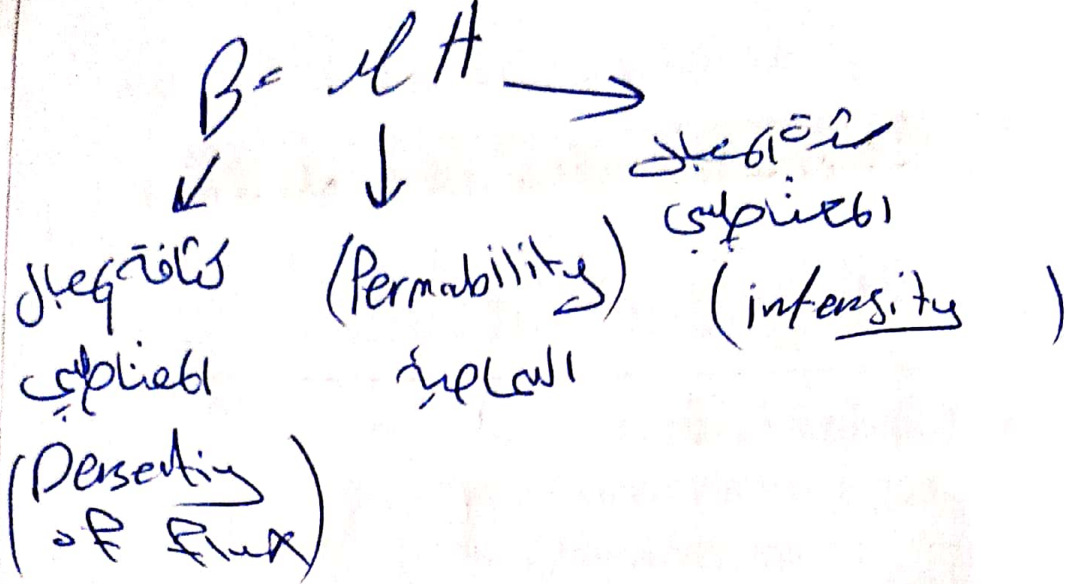


Ferromagnetic materials

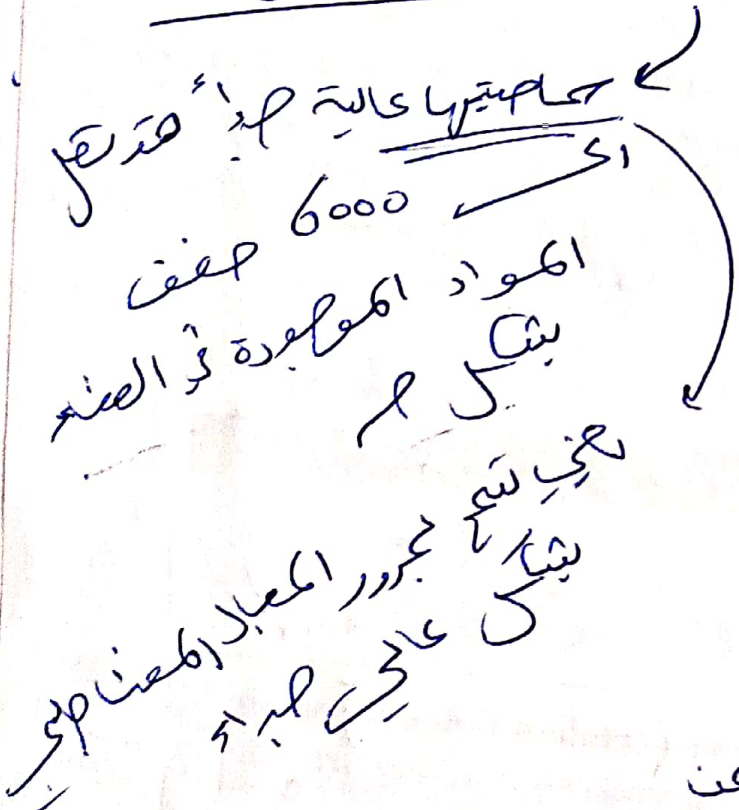

μ_0 \rightarrow الهواء
 Air

μ \rightarrow كان يفرض
 بأننا نأخذ نصف التفرع
 في الـ F (الفرق الدائري) المطلية
 في المادة

Introduction – Magnetic Circuits

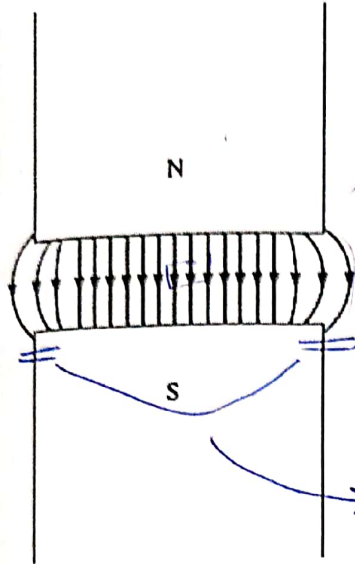

Fringing effect

توزيع القوة المغناطيسية لا يكون متساوياً في كل مكان (cross section Area) south or north

FIGURE 1-6

The fringing effect of a magnetic field at an air gap. Note the increased cross-sectional area of the air gap compared with the cross-sectional area of the metal.

لذلك كلما زاد عرض الفجوة كلما قلت كثافة خطوط المجال في الفجوة (cross section area) %5

Introduction –

Magnetic Behavior of Ferromagnetic Material.

- ▶ It was explained that the permeability of ferromagnetic materials is very high, up to 6000 times the permeability of free space.
- ▶ The permeability was assumed to be constant regardless of the magnetomotive force applied to the material.
- ▶ Although permeability is constant in free space, this most certainly is not true for iron and other ferromagnetic materials.
- ▶ Recall

$$B = \mu H$$

العلاقة بين B و H



والتي تسمى بـ B
والتي تسمى بـ H

لا تتغير مع زيادة القوة المغناطيسية
لكن في المواد المغناطيسية تتغير مع زيادة القوة المغناطيسية

* كل حازد الـ H زياد الـ B زياد الـ B انقل الـ H يعني
 يصح لها زيادة كبيرة بار H وزيادة طفيفة بار B
 وهاد دليل انو اصحابنا حلنا مرحلة اشباع

وهاد يعني انو اناعذب مع طفلة ثلثة والبعير
 صار عنده يفر فبما انو امير يفر فعيف
 الـ H نقل بالنتائج

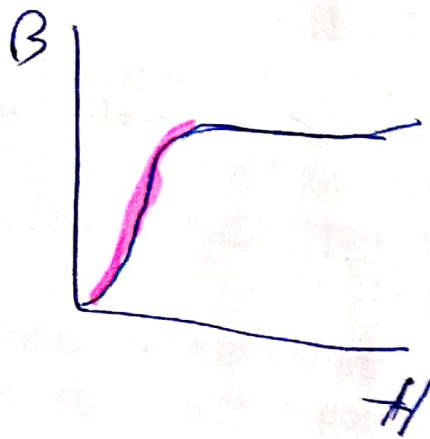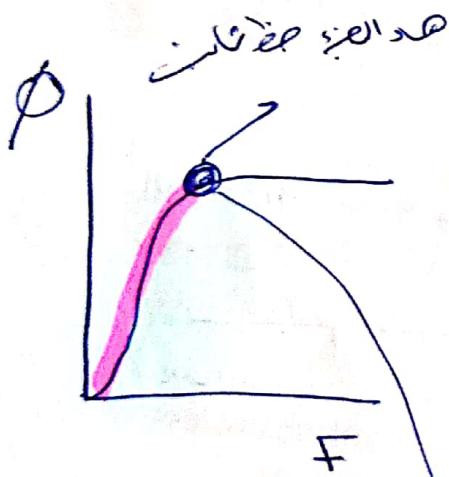↓
 جماعة اكدت لمرور المصالح بطنهم
 يستغل وينادي في هذه الاماكن
 ايضا لالة مشتغل عند الـ H
 ومنه لالة في اننا نقل اننا صار البرز



Magnitasion Curve
 صفة الـ H

نقطة العمل ونقطة الـ Knee
 وعند ص من حالة اشباع

Introduction –

Magnetic Behavior of Ferromagnetic Material

أجزاء الكيرفة
للصان المصنوع
والجزء

▶ Since real generators and motors depend on magnetic flux to produce voltage and torque, they are designed to produce as much flux as possible.

▶ As a result, most real machines operate near the knee of the magnetization curve, and the flux in their cores is not linearly related to the magnetomotive force producing it.

قل
مغناطيسية
التي

▶ This nonlinearity accounts for many of the strange behaviors of machines

المغناطيسية
من
التي

هنا عدم الخطية المعروفة باسم الآلة تتأثر
في العديد من السلوكيات الغير المتوقعة بالآلة


الآلة - التيار ثابت ذو السرعة الزاوية

Introduction – Linear DC Machine


أسهل
واستعمل
تتميز
DC
machines
ويتميز
ب
لغز الكيرفات
التي

A linear dc machine is about the simplest and easiest-to-understand version of a dc machine, yet it operates according to the same principles and exhibits the same behavior as real generators and motors. It thus serves as a good starting point in the study of machines.

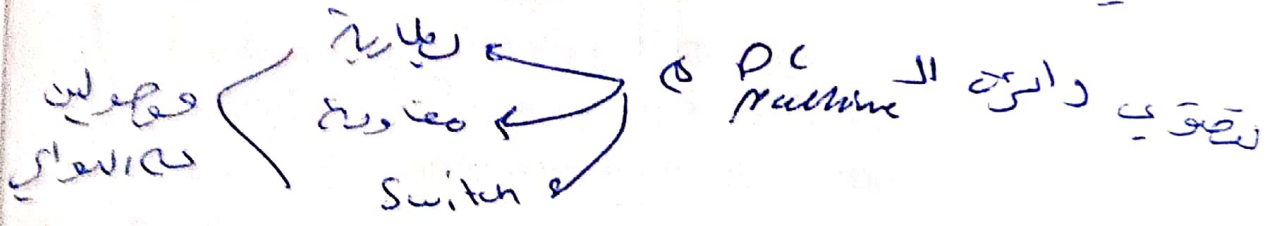كبريتا نفرت انوفار لا Rail بي بيوت در اعمله صنفه
 ثابت (unit or density magnetic) في اتر مكان كولين
 Distributed Perik
 هي السنة



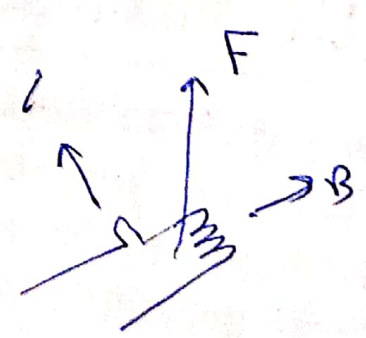بباردة صنفه با اتر امو Rail
 عباة عن بعة صنفه كمولها وصل
 صنفه صبي ثابت وصا بيوت
 في اتر اترتبات ثابت جزه لا حركت
 هي هذا Rail



$$F = I L B \sin \theta$$

بين B و I

Introduction – Linear DC Machine

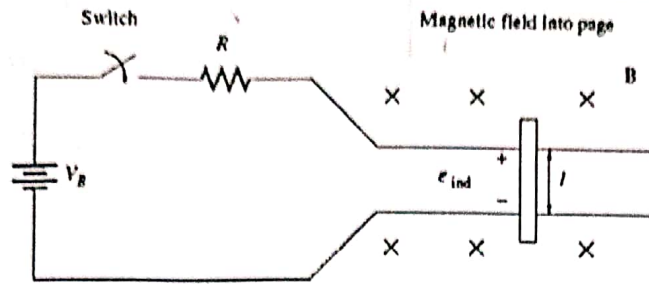


FIGURE 1-19 A linear dc machine. The magnetic field points into the page.

زي على اليمين
 لا لو انضكرك
 كتي صير يجر ك على
 في راي راي

A linear dc machine consists of a battery and a resistance connected through a switch to a pair of smooth, frictionless rails. Along the bed of this "railroad track" is a constant uniform-density magnetic field directed into the page. A bar of conducting metal is lying across the tracks.

طريقة اسعة الحديد

Introduction – Linear DC Machine

Linear DC machines' behavior can be determined from an application of four basic equations to the machine:

القوة المغناطيسية داخل Core سير لا تبد داخل مدار مغناطيسي لو انضكرك

1. The equation for the force on a wire in the presence of a magnetic field:

Concept 3

$$F = i(I \times B) \quad (1-43)$$

where **F** = force on wire

$$F = i L \times B \times \sin \theta$$

Cross Product

i = magnitude of current in wire

l = length of wire, with direction of **l** defined to be in the direction of current flow


B = magnetic flux density vector

Left Rule
 ↓

C: قوة مغناطيسية
 على
 C: القوة المغناطيسية

القوة المغناطيسية
 ال B يربطه ال y المربع
 F في ال y المربع

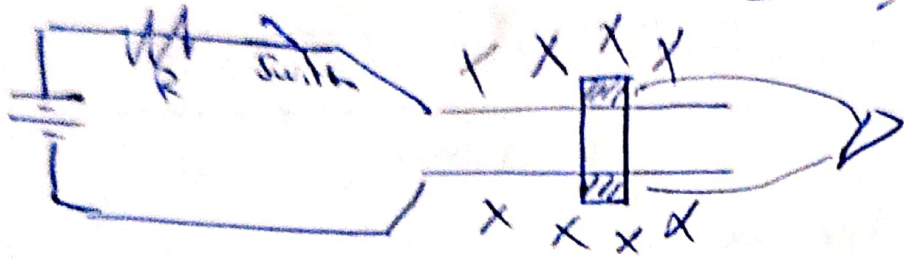بعض نہ اُطراف وہاں ان طرف اسری ہوتا ہے
 فہمنا صاف اور کے بساں اہستہ ایک سو
 فہمنا ہوتا ہے۔



اے طرف
 اسری ہوتا ہے
 ہوتا ہے

$$\begin{aligned}
 \mathcal{E}_{ind} &= (v \times B) \cdot L \\
 &= (v B \sin \theta) \cdot L \\
 &= (v B \sin \theta) L \cos \theta
 \end{aligned}$$

Introduction – Linear DC Machine

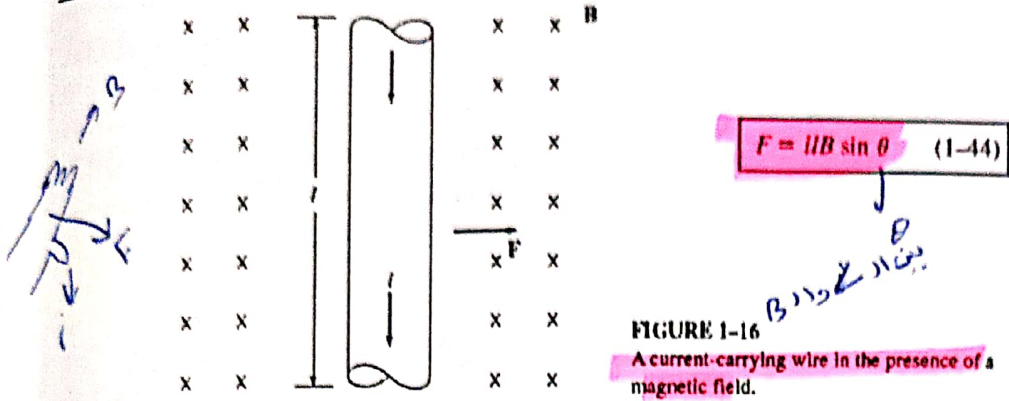


FIGURE 1-16 A current-carrying wire in the presence of a magnetic field.

where

i = magnitude of current in wire

l = length of wire, with direction of l defined to be in the direction of current flow

B = magnetic flux density vector

Introduction – Linear DC Machine

2. The equation for the voltage induced on a wire moving in a magnetic field:

$e_{induced}$ $e_{ind} = (v \times B) \cdot l$ (1-45)

where e_{ind} = voltage induced in wire

v = velocity of the wire

B = magnetic flux density vector

l = length of conductor in the magnetic field

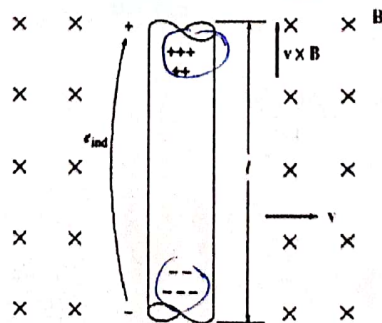


FIGURE 1-17 A conductor moving in the presence of a magnetic field.


Paradity

اذا كان حركتك فعل بترك حركته مع اتجاهه
المتجهات هي في
Concept 17

القارة ← خارج
المجال ← داخل

Introduction – Linear DC Machine

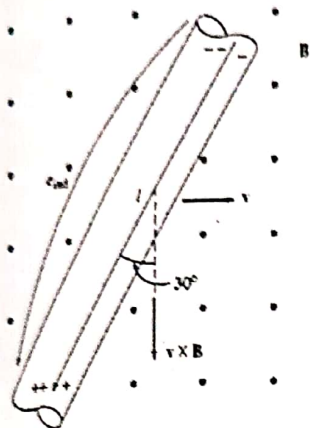Example 1.5 Figure 1-18 shows a conductor moving with a velocity of 10 m/s to the right in a magnetic field. The flux density is 0.5 T, out of the page, and the wire is 1.0 m in length, oriented as shown. What are the magnitude and polarity of the resulting induced voltage?



$$\begin{aligned}
 e_{ind} &= (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l} & (1-45) \\
 &= (vB \sin 90^\circ) l \cos 30^\circ \\
 &= (10.0 \text{ m/s})(0.5 \text{ T})(1.0 \text{ m}) \cos 30^\circ \\
 &= 4.33 \text{ V}
 \end{aligned}$$

زاوية بين \mathbf{v} و \mathbf{B} \rightarrow \sin
وساتج حاصل $\mathbf{v} \times \mathbf{B}$ \rightarrow \cos
Product

FIGURE 1-18
The conductor of Example 1-9.

قوة المحرك التي تتولد في الحرف
المتحرك
التي

Introduction – Linear DC Machine

سلك في الحرف عند دائرة كهربية متحركة

3. Kirchhoff's voltage law for this machine. From Figure 1-19 this law gives

$$\begin{aligned}
 V_B - iR - e_{ind} &= 0 \\
 V_B = e_{ind} + iR &= 0 & (1-46)
 \end{aligned}$$

4. Newton's law for the bar across the tracks:

$$\begin{aligned}
 F_{net} &= ma & (1-7) \\
 \sum F &= Ma
 \end{aligned}$$

سلك في الحرف متساوي الكتلة
المتساوي

الكتلة في كتلة السلك المتحرك

No load
On Bar

موتور
DC
مخبره

قضیة زوايا كاتونكل ازاوية تبلغ 90
 $\sin 90 = \cos 0 = 1$

Introduction - DC Machine


1. Closing the switch
2. The current flow in the bar given by $F_{ind} = I l B$
3. The bar accelerates due to the induced force as $a = F_{ind} / m = \Delta v / \Delta t$
4. The bar moves to the right, producing an induced voltage $e_{ind} = v B l$ as it speeds up
5. This induced voltage reduces the current flow $i = (V_B - e_{ind}) / R$
6. The induced force is thus decreased $F_{ind} = i l B$ until eventually $F_{ind} = 0$. At that point, $e_{ind} = V_B$, $i = 0$, and the bar moves at a constant no-load speed $v_{ss} = V_B / B l$ where $a = 0$ (note that $F_{ind} = 0$)

نقل الى
المحرك
كثافة التيار
عندما يكون
التيار
كله

$(V \times B) \cdot L$

صافي حمل
موتور
في
حيز
Bar

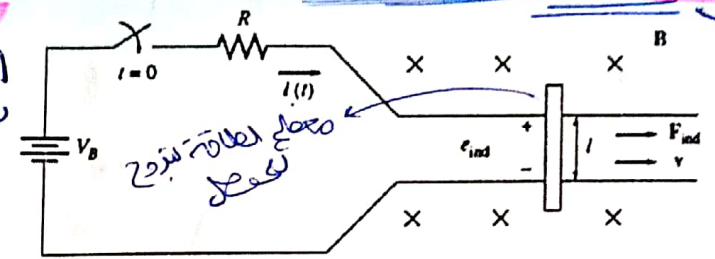الكثافة فون
سبب هي
FIGURE 1-20
Starting a linear dc machine.



$v_{no\ load} = v_{steady\ state}$

مطابقة ال e_{ind} مع V_B لكي يكون كيرتوف صفر في الزوجة التي
تقل ياتي في صلا F_{ind} وتقل بمرور الوقت الى ان
Electrical Machines (110405323) Dr. Mohammad Salah 28

دستور هي العملية ان F_{ind} صفر بعد صير $e_{ind} = V_B$
والتا e_{ind} في a ستا صفر بعد صير e_{ind} في V_B

Introduction - Linear DC Machine

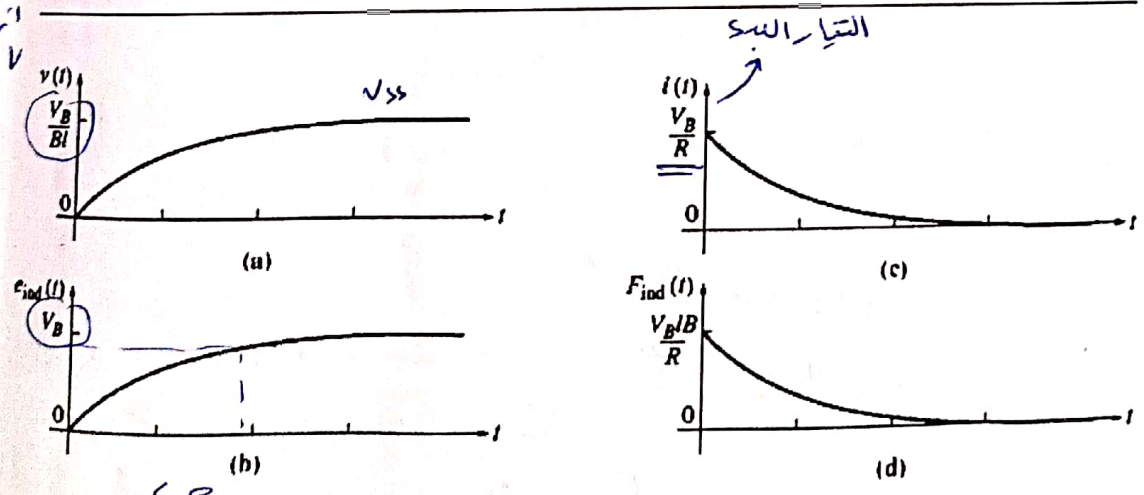


FIGURE 1-21
The linear dc machine on starting.
(a) Velocity $v(t)$ as a function of time;
(b) induced voltage $e_{ind}(t)$; (c) current $i(t)$;
(d) induced force $F_{ind}(t)$.

F
موتور
مع
تيار
تكون
نفس
استقر

حركة
عندما
تكون
التيار
صفر

Regions of DC machine's working
as a motor in Ideal conditions

في هذه الحالة الالة تتصرف كجهد
 يناسب انزما motor والالة تتصرف
 في نفسها الحالة السابقة بنفس الالة
 No load
 كما ينبغي عند الالة
 condition
 انما عا في حمل ميكانيكي سواء في احوال
 وصفت كبره منة ومضنا ليه
 في الحالة الالهية الحالية

Introduction – Linear DC M

If a force F_{load} is applied to the bar in the **OPPOSITE** direction net force is $F_{net} = -F_{load}$ and the following events occur:

1. The bar decelerates due to the load force as $a = F_{net}/m = \Delta v/$
 2. The effect of this net force will reduce $e_{ind} = v \downarrow BI$ as the bar slows down
 3. This induced voltage increases the current flow $i = (V_B - e_{ind} \downarrow) / R$
 4. The induced force is thus increased $F = i \uparrow IB$ until $|F_{ind}| = |F_{Load}|$ at a lower speed v .
- Note that $F_{net} = F_{ind} - F_{Load}$ in this case.

5. An amount of electric power equal to $e_{ind} i$ is now being converted to mechanical power equal to $F_{ind} v$, and the machine is acting as a **motor**.

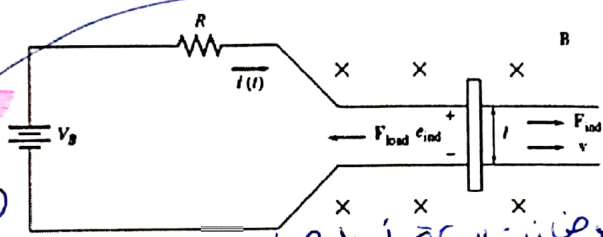


FIGURE 1-22 The linear dc machine as a motor.

Power conversion

تقلنا اننا صفا و لا عشان في
 صلب يتروح في R والقد
 تناقض الطارة في صفا في
 باحفا واه بعدت صفا في يتكول

بيننا تقريبا اننا صفا في
 كانه في باحفا في صفا في
 هاد الحفظ في الالة في شكل مستقر

Introduction – Linear DC Ma

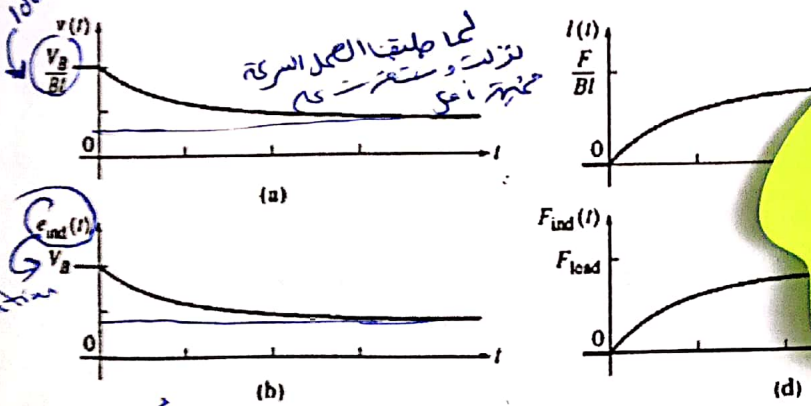


FIGURE 1-23 The linear dc machine operating at no-load conditions and then loaded as a motor. (a) Velocity $v(t)$ as a function of time; (b) Induced voltage $e_{ind}(t)$; (c) current $i(t)$; (d) induced force $F_{ind}(t)$.

No load
 كما ينبغي ان في الالة
 efficiency 100%
 No load ideal condition
 يعني ان في صفا في حمل ولا
 اتمت الالة في صفا في

كما طبقنا العمل
 في تقريبا في صفا في

Real case

لما في الالة في صفا في
 في اتمت الالة في صفا في

Introduction – Linear DC Machine

If a force F_{app} is applied to the bar in the SAME direction of motion, hence the net force is $F_{net} = F_{app}$ and the following events occur:

1. The bar accelerates due to the load force as $a = F_{net}/m = \Delta v / \Delta t$ since $F_{net} > 0$
2. The effect of this net force will increase $e_{ind} = v \uparrow Bl$ as the bar speeds up
3. This induced voltage reverses the direction of the current flow $i = (V_B - e_{ind}) / R$ since $(V_B < e_{ind})$
4. The induced force is thus reverses its direction due to the reversed current $-F_{ind} = -iBl$ until $|F_{ind}| = |F_{app}|$. Note that $F_{net} = F_{app} - F_{ind}$ in this case.
5. An amount of mechanical power equal to $F_{app} v$ is now being converted To electric power equal to $e_{ind} i$, and the machine is acting as a generator.

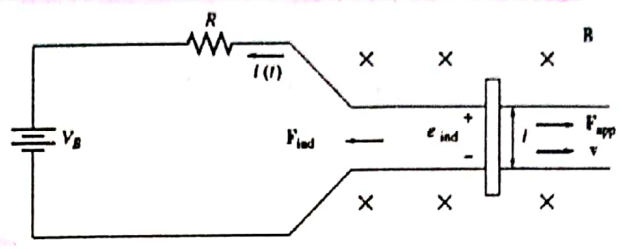


FIGURE 1-24 The linear dc machine as a generator.

Introduction – Linear DC Machine

Example 1.10 The linear dc machine shown in Figure 1-27a has a battery voltage of 120 V, an internal resistance of 0.3 Ω , and a magnetic flux density of 0.1 T. (a) What is this machine's maximum starting current? What is its steady-state velocity at no load? (b) Suppose that a 30-N force pointing to the right were applied to the bar. What would the steady-state speed be? How much power would the bar be producing or consuming? How much power would the battery be producing or consuming? Explain the difference between these two figures. Is this machine acting as a motor or as a generator? (c) Now suppose a 30-N force pointing to the left were applied to the bar. What would the new steady-state speed be? Is this machine a motor or a generator now? (d) Assume that a force pointing to the left is applied to the bar. Calculate speed of the bar as a function of the force for values from 0 N to 50 N in 10-N steps. Plot the velocity of the bar versus the applied force. (e) Assume that the bar is unloaded and that it suddenly runs into a region where the magnetic field is weakened to 0.08 T. How fast will the bar go now?

velocity \leftarrow Force \leftarrow N
motion

$\frac{V_B}{R}$

$\frac{V_B}{Bl}$

القوة
التي

0-10-20-30-40-50

تجاه اليمين
Consuming

إذا طبقنا قانون في انفس انقباض العضلة في بصر عند اره ففعلية
 والتاثير في تزداد القوة ويتاثير اره سابقه فلا تتركه وقوية التاثير
 في بصر السليم يعني تغير التوازن في الترتيب في ذلك انفس السليم
 (جلس)

فيما عند تيار سريع في فصل عننا هناك عننا في بصر عند
 Find كذا التاثير سلب والسالب فوله التاثير في التاثير في
 العملية له ما لو وصل حالة الاشارة يكون فيها $F_{app} = F_{ind}$
 في هذا الحل اره F_{ind} تقاومة اليد اليمنى بالعضلة الاولى كان على
 فون خارج القوس بالتاثير هاد يعني انفس الاشارة يحاول تسيار
 التغير القاه اليه بصر التغير يعني الكموال مع العين والهايز
 بالزيادة اره F_{app} في تادي لزيادة القوة بعد ان اكله راع
 لغير توازن بحيث تكون مجموع القوى على الكموال غير
 ساكن التاثير في تادي ما هي زيادة حركة سببها
 تكون في حيا انوسر كذا الكموال اذى وانقباض التاثير في عكس
 و في تغير القوة في عمل Generator

ان عند القدر الكهربي
 ان في F_{app} هو لها
 لقدر كهربائي

* حالة *

- اما في يعطين قوة او عزم حسب الحاجة
 يعني ان الكموال اعطيتو كهربيا و حاجي حتى تقاوم العزم
 الي يعطين اياه فلهذا فاعني شرا اف وهو اعطي كوما
 ثمان في هذا الكموال في تولد عزميا انقباض العكسي ثمان
 تقاوم اذ حركة و ثمان يعطينا هذا العزم بتاثير انوسر في تادي
 من الكموال و يتاثير في حسب التاثير ثمان زيادة العمل الكهربائي

في حالة المولد أثناء بعض الأوقات والالة تدور في اتجاه الحركة
للتيار (عكس) والتي تكون بالانتباه العلمي تدور في
المصدر وفي حال يكون عند سرعة دوران الالة
أكبر من سرعة دورات المحرك ويتكبر مصدر توليد
عكسي له لأنواع ما زدت الحركة من حيث
السرعة الأمامي أصبحت يزداد واتجاه الالة قيمة أكبر
من قيمة المصدر وتنعكس التيار وتكون عليه
Returning Power لا Power supply يعني آخر أنا سبغت البطارية
وتتأخر أنا سبغت الالة عن أساس أنها مولد
generator

DC Machines

By

Dr. Mohammad Salah

Mechatronics Engineering Department
The Hashemite University

Handwritten notes in Arabic: "هذا هو" (This is), "بسم الله" (In the name of God), "الحمد لله" (Praise be to God).


Handwritten notes in Arabic: "AC \Rightarrow commutating machinery", "Relative", "كانت في الماضي", "يكون AC", "DC".

DC Machines – Definition

Handwritten notes in Arabic: "فول" (Voltage), "مرك" (Current), "طاقة حركة" (Kinetic energy), "طاقة كهربائية" (Electrical energy), "طاقة ميكانيكية" (Mechanical energy).


- ▶ DC machines are generators that convert mechanical energy to DC electric energy and motors that convert DC electric energy to mechanical energy.
- ▶ Most DC machines are like AC machines in that they have AC voltages and currents within them. DC machines have a DC output only because a mechanism exists that converts the internal AC voltages to DC voltages at their terminals.
- ▶ Since this mechanism is called a commutator, DC machinery is also known as commutating machinery.

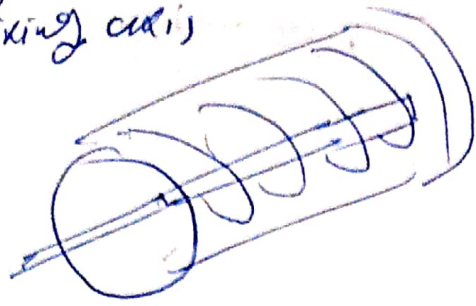أسهل أشكال المحركات الدوارة هو عبارة عن Loop تلف حولين
 Fixing axis



المحرك الدوار في آلة DC أو آلي
 آلة متحركة أو Rotor والحيز
 الثابت متحركة Stator

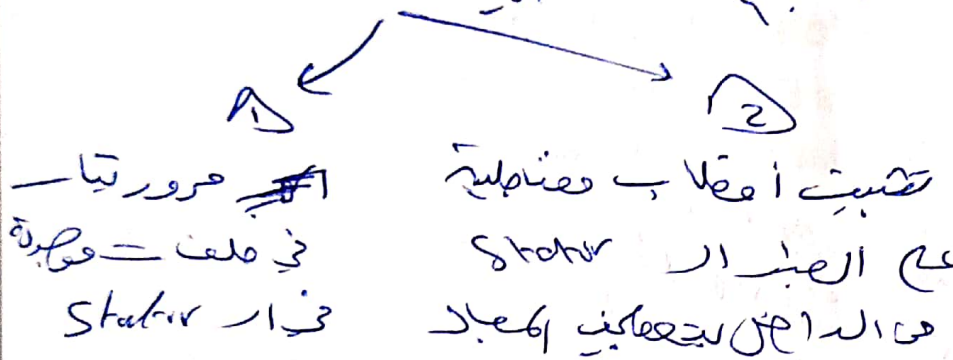هنا أيضا كغيرها أنو كل آلة كآلة يكون فيها مجال مغناطيسي
 لحتى تعمل والمجال المغناطيسي في رotor من متحركة الثابتة
 أي هي ال Stator ويتم ذلك عن طريق إما



يجب أن نعرض أنو هناك السلك في ال core ويصنع بالبركة
 والبركة هي ال core هو تشكيله مغلوط المجال وهذا ال
 مغلوط المجال المغلوط في ال Stator core

عند سرطين كآلة انقطع عن مكان التثبيت المغلوط = أي
 لا يتحرك لا DC machine

ألو يكون حيز في سطح المجال المغناطيسية متحركة في
 السطح الداخلي لل Rotor ويحرك ال Stator

منه المجال المغناطيسي قد يتحرك ثلثه من أول
 طرفه للقطب الآخر

لا يمكن على هذا الحيز غير دقيق والسداد من داني كتابت

DC Machines – Simple Rotating Loop

- ▶ The simplest possible rotating dc machine consists of a single loop of wire rotating about a fixed axis.
- ▶ The rotating part of this machine is called the **rotor**, and the stationary part is called the **stator**.
- ▶ The magnetic field for the machine is supplied by the magnetic north and south poles on the stator.
- ▶ Notice that the loop of rotor wire lies in a slot carved in a ferromagnetic core.
- ▶ The magnetic field is perpendicular to the rotor surface everywhere under the pole faces.
- ▶ The magnetic flux is uniformly distributed (constant) everywhere under the pole faces.

الجزء الثابت
الجزء المتحرك
المجال المغناطيسي
التيار الكهربائي
القوة الدافعة الكهربائية

DC Machines – Simple Rotating Loop

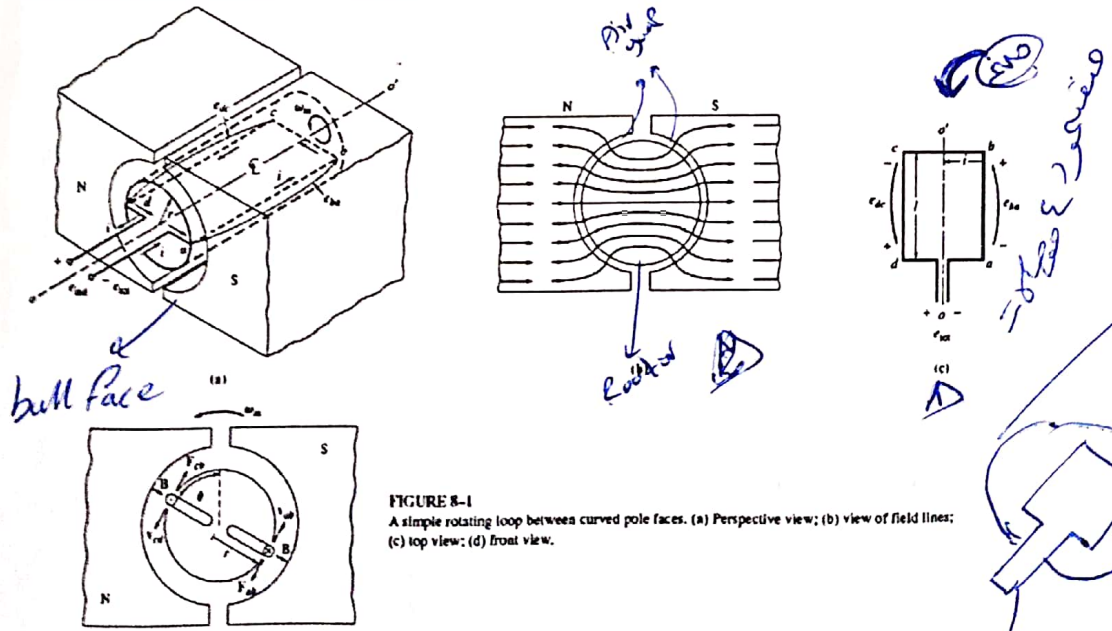


FIGURE 8-1
A simple rotating loop between curved pole faces. (a) Perspective view; (b) view of field lines; (c) top view; (d) front view.

المجال المغناطيسي
القوة الدافعة الكهربائية
التيار الكهربائي

القطب الشمالي
القطب الجنوبي
المجال المغناطيسي
القوة الدافعة الكهربائية
التيار الكهربائي

المجال المغناطيسي
القوة الدافعة الكهربائية
التيار الكهربائي

السؤال الرابع
 لا اله الا الله محمد بن عبد الله
 صواب

الحل: يكون في اربع نصوص في الـ 4 نقاط
 صحتها وصحة الادوات الحلال التي في الجمل
 التي في الجمل التي في الجمل التي في الجمل

Total E_{ind} , $2 \times$ $2 \times$ $2 \times$


$$E_{ind}^{Total} = E_{ba} + E_{cb} + E_{dc} + E_{ad}$$

$E_{ind} = \int_0^{2\pi} 2vBL$ under the pole faces
 beyond the pole edges

$$E_{ba} = \int_0^{2\pi} vBL + E_{cb} + E_{dc} = \int_0^{2\pi} vBL + E_{ad}$$

$$= \int_0^{2\pi} 2vBL$$

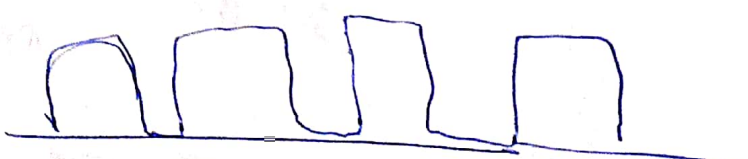Commutator
 يكون في 4 نصوص في الـ 4 نقاط
 يا اما كل نصيبا اما كل نصيب



Full wave Rectifier

DC Machines – Simple Rotating Loop

- ▶ If the rotor of this machine is rotated, a voltage will be induced in the wire loop.
- ▶ To determine the total voltage e_{tot} on the loop, we need to examine each segment of the loop separately and sum all the resulting voltages. The voltage on each segment is given by

$$e_{ca} = (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l} = \begin{cases} vBl & \text{positive into page under the pole face} \\ 0 & \text{beyond the pole edges} \end{cases} \quad (8-1)$$

$$e_{cb} = (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l} = \begin{cases} vBl & \text{positive out of page under the pole face} \\ 0 & \text{beyond the pole edges} \end{cases} \quad (8-3)$$

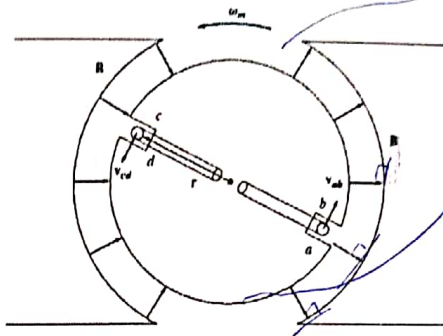


FIGURE 8-2 Derivation of an equation for the voltages induced in the loop.


طالع كاس و Tax e ind من ال poles
voltages

DC Machines – Simple Rotating Loop

The total induced voltage on the loop e_{ind} is given by

$$e_{ind} = e_{ba} + e_{cb} + e_{dc} + e_{ad}$$
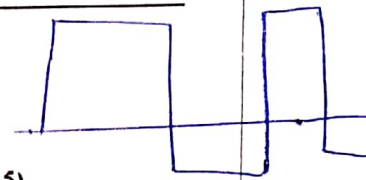
$$e_{ind} = \begin{cases} 2vBl & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \quad (8-5)$$



هذا الشكل

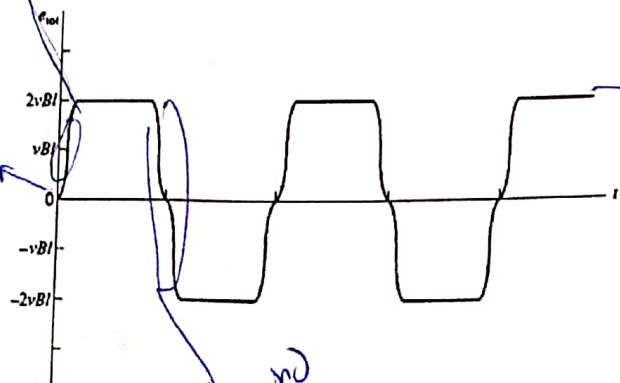


FIGURE 8-3 The output voltage of the loop.

الزمن الذي يكون فيه
در المنتصف بين
القطبين

الزمن الذي يكون فيه
القطب
الزمن الذي يكون فيه
القطب

التي هي
مجال مغناطيسي
مساوي
في كل مكان

مجال مغناطيسي
مساوي
في كل مكان

$$\frac{2\pi r L}{2} = \pi r L = A_p$$

integrated

$$E_{ind} = \int_0^{2\pi r L} 0$$

$$v = r\omega$$

$$B = \frac{\Phi}{A_p}$$

$$L = \frac{A_p}{\pi r}$$


$$2\pi r\omega \times \frac{\Phi}{A_p} \times \frac{A_p}{\pi r}$$

$$= \frac{2\pi\omega\Phi}{\pi r} = \boxed{\frac{2}{\pi}\omega\Phi}$$

$$E_{ind} = \int_0^{2\pi r L} \frac{2}{\pi}\omega\Phi$$

under pole
beyond pole

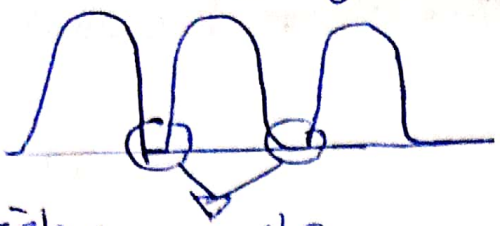
موجباته او voltage في حالة عمل المولد تكون $\sin \omega t$ و
 العزم العكسي



فان العزم العكسي يكون موجبا في
 كل دورة فترتها المولدة ووصول
 لمرحلة عاكسا فصال مضاعف
 بين القطب الاكبر والصغير

فترتها نصفه واد
 الكلايم عن طرفه اتي
 انموال Comutator


قطعة
 رخيصة مرفوعة على اطراف المولد

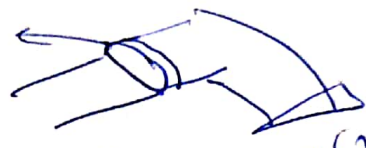

مفاتيح الالمكناي في حيز من ال Simple
 Rotating Loop

يكون اتصاله بالعالج الخارج عن طرفه ال brush

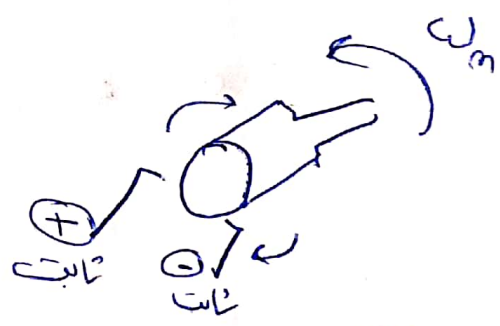عبارة عن صان مصنوعه
 من الكربون مقطوعة بنيزك
 على الامام حيث انفراد
Brushes ثابتات فالتحرك
 القمطين



عمرة الفتحه اكي مع
 العين على الجانبين وادب
 سبب في تلف فالسلك اكي على
 اليمين فتره يكون (+) وحرر
 (-) والعكس صحيح سبب بالهنا
 ال Comutator كانه على
 اليمين (-) بشكل راجع

لو تدركت $\sin \omega t$ يرضه معابر
 سبب في تلف الكوموتور يعني مع
 الاز كس وقت
 الساتر

$$\tau_{ind} = \tau_{ab} + \tau_{bc} + \tau_{cd} + \tau_{da}$$

$$F_{ab} = i(l \times B) = i l B$$

$$\tau_{ab} = r F \sin \theta = r (i l B) \sin 90 = r i l B$$

$$\tau_{bc} = 0 \Rightarrow \sin 0 = 0$$

$$\tau_{cd} = r F \sin \theta = r (i l B) \sin 90 = r i l B$$

$$\tau_{da} = 0 \Rightarrow \sin 0 = 0$$

$$\Rightarrow \tau_{ind} = r i l B + 0 + r i l B + 0 = 2 r i l B$$

by using $A_p = \pi r l$ & $A \cdot B = \phi$

$\tau_{ind} = \frac{2}{\lambda} \phi(i)$, under the pole faces
 0, beyond the pole edges

تحت القطب
 في القطب
 خارج القطب

DC Machines – Simple Rotating Loop

$$F_{cd} = i(l \times B) = ilB \text{ (tangent to direction of motion)} \quad (8-7)$$

The torque on the rotor caused by this force is

$$\begin{aligned} \tau_{cd} &= rF \sin \theta \\ &= r(ilB) \sin 90^\circ \\ &= rilB \quad \text{CCW} \end{aligned} \quad (8-8)$$

$$F_{bc} = i(l \times B) = 0 \text{ since } l \text{ is parallel to } B \quad (8-9)$$

Therefore,

$$\tau_{bc} = 0 \quad (8-10)$$

$$F_{da} = i(l \times B) = ilB \text{ (tangent to direction of motion)} \quad (8-11)$$


The torque on the rotor caused by this force is

$$\begin{aligned} \tau_{da} &= rF \sin \theta \\ &= r(ilB) \sin 90^\circ \\ &= rilB \quad \text{CCW} \end{aligned} \quad (8-12)$$

$$F_{ab} = i(l \times B) = 0 \text{ since } l \text{ is parallel to } B \quad (8-13)$$

Therefore,

$$\tau_{ab} = 0 \quad (8-14)$$

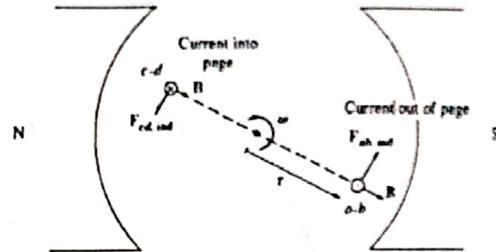

DC Machines – Simple Rotating Loop

The resulting total induced torque on the loop is given by

$$\tau_{ind} = \tau_{ab} + \tau_{bc} + \tau_{cd} + \tau_{da}$$

$$\tau_{ind} = \begin{cases} 2rilB & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \quad (8-15)$$

By using the facts that $A_p \approx \pi rl$ and $\phi = A_p B$, the torque expression can be reduced to

$$\tau_{ind} = \begin{cases} \frac{2}{\pi} \phi i & \text{under the pole faces} \\ 0 & \text{beyond the pole edges} \end{cases} \quad (8-16)$$

تعملي $1/100$ \Rightarrow $\left(\frac{p}{k}\right)$

أما إذا كان عددي
لوح أكثر من واحد
فيثبت k

← الصيغة الكلاسيكية الكهرومغناطيسية
يساري ثابت ϕ و ϕ و ϕ بالسرعة v و v
مع اللولبي الكلاسيكية بالسرعة v و v
مع ϕ و ϕ و ϕ و ϕ و ϕ و ϕ
بسرعة v و v و v و v و v و v

DC Machines – Simple Rotating Loop


العزم الناتج
بالإضافة إلى
دالة كلف
بشكل
التي يمر بها
ع راحة
ع
ع
ع

- ▶ The torque produced in the machine is the product of the flux in the machine and the current in the machine, times some quantity representing the mechanical construction of the machine (the percentage of the rotor covered by pole faces).
- ▶ In general, the torque in any real machine will depend on the same three factors:
 1. The flux in the machine
 2. The current in the machine
 3. A constant representing the construction of the machine

DC Machines – Simple Rotating Loop

قوة متحركة الدورات (مساحة الزاوية) مقادير

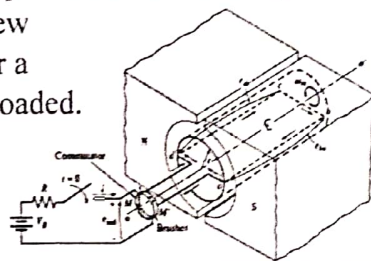Example 8.1 Given the system shown in Figure 8-6. The physical dimensions and characteristics of this machine are $r = 0.5\text{m}$, $R = 0.3\Omega$, $V_B = 120\text{V}$, $l = 1.0\text{m}$, $B = 0.25\text{T}$ (a) What happens when the switch is closed? (b) What is the machine's maximum starting current? What is its steady-state angular velocity at no load? (c) Suppose a load is attached to the loop, and the resulting load torque is $10\text{ N}\cdot\text{m}$. What would the new steady-state speed be? How much power is supplied to the shaft of the machine? How much power is being supplied by the battery? Is this machine a motor or a generator? (d) Suppose the machine is again unloaded, and a torque of $7.5\text{ N}\cdot\text{m}$ is applied to the shaft in the direction of rotation. What is the new steady-state speed? Is this machine now a motor or a generator? (e) Suppose the machine is running unloaded. What would the final steady-state speed of the rotor be if the flux density were reduced to 0.20 T ?



صورة
كمية
Power
رأية
الطاقة
ميكانيكية
ع
Mechanical
Power

فما فعلت حين انزلنا حرك
عنات اننا نجد حركنا

Maximum \rightarrow Starting Current

11 5 11

DC Machines – Simple Rotating Loop

(a) When the switch in Figure 8-6 is closed, a current will flow in the loop. Since the loop is initially stationary, $e_{ind} = 0$. Therefore, the current will be given by

كبير نسيف $i = \frac{V_B - e_{ind}}{R} = \frac{V_B}{R}$

This current flows through the rotor loop, producing a torque

$\tau_{ind} = \frac{2}{\pi} \phi i$ CCW

This induced torque produces an angular acceleration in a counterclockwise direction, so the rotor of the machine begins to turn. But as the rotor begins to turn, an induced voltage is produced in the motor, given by

$e_{ind} = \frac{2}{\pi} \phi \omega$

so the current i falls. As the current falls, $\tau_{ind} = (2/\pi)\phi i$ decreases, and the machine winds up in steady state with $\tau_{ind} = 0$, and the battery voltage $V_B = e_{ind}$. This is the same sort of starting behavior seen earlier in the linear dc machine.

تدريجياً
تقل
التيار
والتorque
حتى
يصير
صفر

هنا
يحدث
تغير
في
التيار
والتorque
حتى
يصير
صفر

DC Machines – Simple Rotating Loop

(b) At starting conditions, the machine's current is

$i = \frac{V_B}{R} = \frac{120 \text{ V}}{0.3 \Omega} = 400 \text{ A}$

At no-load steady-state conditions, the induced torque τ_{ind} must be zero. But $\tau_{ind} = 0$ implies that current i must equal zero, since $\tau_{ind} = (2/\pi)\phi i$, and the flux is nonzero. The fact that $i = 0 \text{ A}$ means that the battery voltage $V_B = e_{ind}$. Therefore, the speed of the rotor is

$V_B = e_{ind} = \frac{2}{\pi} \phi \omega$

$\omega = \frac{V_B}{(2/\pi)\phi} = \frac{V_B}{2rIB}$

$= \frac{120 \text{ V}}{2(0.5 \text{ m})(1.0 \text{ m})(0.25 \text{ T})} = 480 \text{ rad/s}$

السرعة الزاوية
Angular
velocity
OR
Rotor
speed

RPM
3000

بالتالي

480

التيار
يصير
صفر

DC Machines – Simple Rotating Loop

(c) If a load torque of $10 \text{ N} \cdot \text{m}$ is applied to the shaft of the machine, it will begin to slow down. But as ω decreases, $e_{ind} = (2/\pi)\phi\omega$ decreases and the rotor current increases $[i = (V_B - e_{ind})/R]$. As the rotor current increases, $|\tau_{ind}|$ increases too, until $|\tau_{ind}| = |\tau_{load}|$ at a lower speed ω .

At steady state, $|\tau_{load}| = |\tau_{ind}| = (2/\pi)\phi i$. Therefore,

By Kirchhoff's voltage law, $e_{ind} = V_B - iR$, so

$$e_{ind} = 120 \text{ V} - (40 \text{ A})(0.3 \Omega) = 108 \text{ V}$$

Finally, the speed of the shaft is

$$\omega = \frac{e_{ind}}{(2/\pi)\phi} = \frac{e_{ind}}{2rB}$$

$$= \frac{108 \text{ V}}{(2)(0.5 \text{ m})(1.0 \text{ m})(0.25 \text{ T})} = 432 \text{ rad/s}$$

The power supplied to the shaft is

$$P = \tau\omega$$

$$= (10 \text{ N} \cdot \text{m})(432 \text{ rad/s}) = 4320 \text{ W}$$

The power out of the battery is

$$P = V_B i = (120 \text{ V})(40 \text{ A}) = 4800 \text{ W}$$

This machine is operating as a motor, converting electric power to mechanical power.

السرعته تنخفض
تساويها مع التيار
السرعته تنخفض
التيار يزداد
السرعته تنخفض
التيار يزداد

السرعته تنخفض
التيار يزداد
السرعته تنخفض
التيار يزداد

السرعته تنخفض
التيار يزداد
السرعته تنخفض
التيار يزداد

المحرك
التيار يزداد
السرعته تنخفض
المحرك

التيار يزداد
السرعته تنخفض
التيار يزداد
السرعته تنخفض

DC Machines – Simple Rotating Loop

(d) If a torque is applied in the direction of motion, the rotor accelerates. As the speed increases, the internal voltage e_{ind} increases and exceeds V_B , so the current flows out of the top of the bar and into the battery. This machine is now a generator. This current causes an induced torque opposite to the direction of motion. The induced torque opposes the external applied torque, and eventually $|\tau_{load}| = |\tau_{ind}|$ at a higher speed ω .

The current in the rotor will be

$$i = \frac{\tau_{ind}}{(2/\pi)\phi} = \frac{\tau_{ind}}{2rB}$$

$$= \frac{7.5 \text{ N} \cdot \text{m}}{(2)(0.5 \text{ m})(1.0 \text{ m})(0.25 \text{ T})} = 30 \text{ A}$$

The induced voltage e_{ind} is

$$e_{ind} = V_B + iR$$

$$= 120 \text{ V} + (30 \text{ A})(0.3 \Omega)$$

$$= 129 \text{ V}$$

Finally, the speed of the shaft is

$$\omega = \frac{e_{ind}}{(2/\pi)\phi} = \frac{e_{ind}}{2rB}$$

$$= \frac{129 \text{ V}}{(2)(0.5 \text{ m})(1.0 \text{ m})(0.25 \text{ T})} = 516 \text{ rad/s}$$

التيار يزداد
السرعته تنخفض
التيار يزداد
السرعته تنخفض
التيار يزداد
السرعته تنخفض

التيار يزداد
السرعته تنخفض
التيار يزداد
السرعته تنخفض

التيار يزداد
السرعته تنخفض
التيار يزداد
السرعته تنخفض

التيار يزداد
السرعته تنخفض
التيار يزداد
السرعته تنخفض

التيار يزداد
السرعته تنخفض
التيار يزداد
السرعته تنخفض

5% كوتور، عي 20%

DC Machines – Simple Rotating Loop

(e) Since the machine is initially unloaded at the original conditions, the speed $\omega = 480$ rad/s. If the flux decreases, there is a transient. However, after the transient is over, the machine must again have zero torque, since there is still no load on its shaft. If $\tau_{ind} = 0$, then the current in the rotor must be zero, and $V_B = e_{ind}$. The shaft speed is thus

$$\omega = \frac{e_{ind}}{(2/\pi)\phi} = \frac{e_{ind}}{2rB}$$

$$= \frac{120 \text{ V}}{(2)(0.5 \text{ m})(1.0 \text{ m})(0.20 \text{ T})} = 600 \text{ rad/s}$$

0.25 T
↓
0.20 T

Notice that when the flux in the machine is decreased, its speed increases. This is the same behavior seen in the linear machine and the same way that real dc motors behave.

في حالة انخفاض التدفق في الآلة، تزداد السرعة ←

محمد صلاح

DC Machines – Operation



▶ DC Motor, How it works?

<https://www.youtube.com/watch?v=LAtPHANefQo&t=1s>

Commutator لا يفسد كل من
 تحويلات AC و DC
 صاعداً

Realitive

Armature هو الجزء الذي

DC machine بال

motor يعني هو نفس motor
 يعني!!

DC machine

$$\frac{L di}{dt}$$

Inductive kick


تلفظ الصدى

حسب قوانين الحث الـ Drop voltage

$\frac{L di}{dt}$ بلزوم تخير الدنيا وضرب بالحدية
 اها اذا كان في تخير في التيار

تأثير الارستور هو تأثير اتصال كصناعي لتأثير عن مرور التيار في الارستور عن توزيع مجال تحت القطب

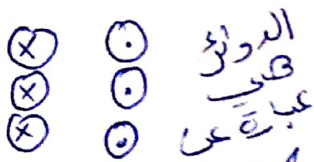لهم في توزيع كصناعي يتكون مستطيلة بكميات
 مع المطع



تلك عناء المتواضع
 السبب في ذلك
 كصناعي

لتحويل التيار = تحويل AC الى DC

DC Machines – Commutation Problems

- ▶ **Commutation** is the process of converting the AC voltages and currents in the rotor of a DC machine to DC voltages and currents at its terminals.
- ▶ It is the most critical part of the design and operation of any DC machine.
- ▶ The commutation process is not as simple in practice as it seems in theory, because two major effects occur in the real world to disturb it:

التيار في
محطة التحويل
مورد

1. Armature reaction

مناخات رقاب عملية
Commutation

2. $L \frac{di}{dt}$ voltages

رد فعل الحث

Inductive Kick



عادة الفجوات يتبدل الى القطب الايجابى عند
صفره الزوا يكون هي اذونات للبرش والمناخات

DC Machines – Commutation Problems

التيار في
محطة التحويل
مورد

Armature Reaction

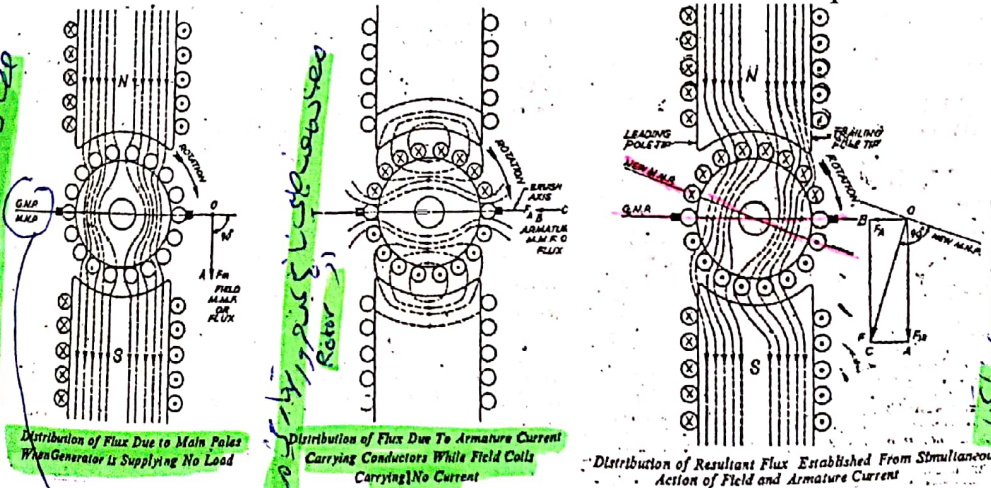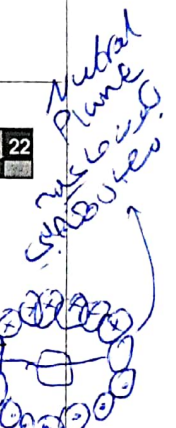It is the effect of the magnetic field set up by the armature current on the distribution of the flux under main poles




محطة التحويل
مورد

المناخات
التيار في
محطة التحويل
مورد

المناخات
التيار في
محطة التحويل
مورد

استوه المحب بصورتها الكنتاد بآرب الي تاتي في الكمال الكنتاد
 لما تتلاصق الفخيات مع الـ Commutator وتتغير مكانها
 Neutral Point في الـ Commutator من هذا الامتداد او الكنتاد الي
 تكون صفت عتوت في فعل الـ Primitive

* Neutral Plane Shifts

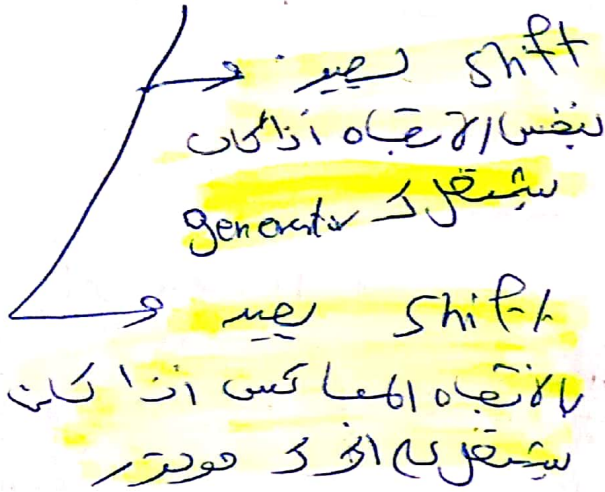

مع فتره الايام بتعلم مع فتره الايام بالتك في مستوى العمل مع الاله


يطلع وينزل بناء على الاصحاب

كهربائي عمارة كهربائية وياتي اليها
 وكان في صلب الحركة والنور

تأين لدراسه الهواء

~~بشكل~~
 النور هاد عمارة عن انتقال في نقطة الك اخرج
 من خلال البرطاد وكثير من الاكديان صاحبو حراة كالتة هاد
 ممكن تاري لدراسه الفخيات والاهالي في الـ Commutator

DC Machines – Commutation Problems

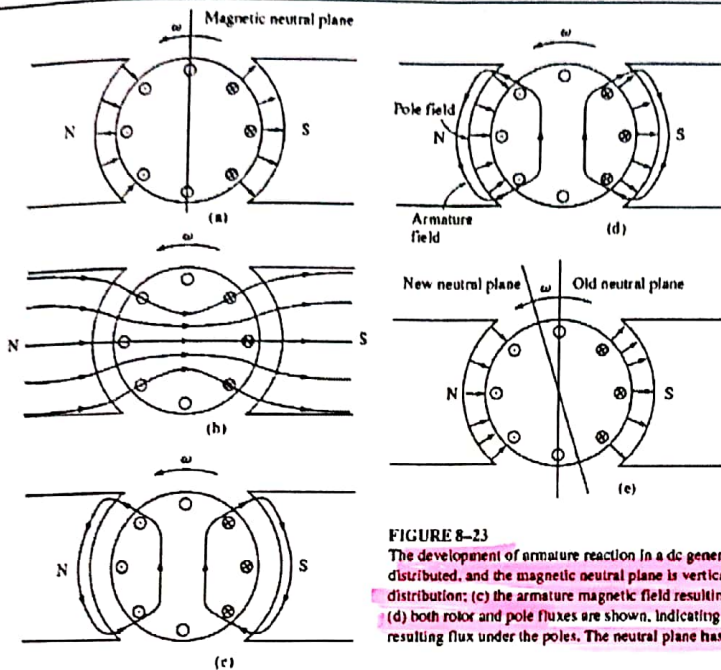

Armature Reaction causes two serious problems:

1. Neutral Plane Shift
2. Flux weakening

الخط المتعادل يبتعد عن القطب
في اتجاه دوران المحرك

FIGURE 8-23

The development of armature reaction in a dc generator. (a) Initially the pole flux is uniformly distributed, and the magnetic neutral plane is vertical; (b) the effect of the air gap on the pole flux distribution; (c) the armature magnetic field resulting when a load is connected to the machine; (d) both rotor and pole fluxes are shown, indicating points where they add and subtract; (e) the resulting flux under the poles. The neutral plane has shifted in the direction of motion.

DC Machines – Commutation Problems

- ▶ **Magnetic neutral plane** is defined as the plane within the machine where the **velocity of the rotor wires is exactly parallel to the magnetic flux lines**, so that e_{ind} in the conductors in the plane is exactly zero.
- ▶ In general, the **neutral-plane shifts in the direction of motion for a generator and opposite to the direction of motion for a motor.**
- ▶ Furthermore, **the amount of the shift depends on the amount of rotor current and hence on the load of the machine.**
- ▶ The end result is **arcing and sparking at the brushes** and this is a very serious problem

الخط المتعادل يبتعد عن القطب في اتجاه دوران المحرك

Flashover \rightarrow extreme
النور يكون كبير على هذه النوع
التي احترق او segments

الريود جنب الفجوات يكون فائز نتيجة اسرار
بسرعة الفجوات

هو هكذا اجزاء انقاسه هو انتقال التروان كما ان
الريود فهو غير الريود

كما يغير عند الريود لقطعتين نحاسيتين جنب بعض
بسرعة حرارية صاكنة نتيجة مرورها
فقدت او Flashover

بالموتورات \rightarrow تزيد السرعة والمخرج يزداد العمل (فوق عند ذلك العمل كما ينبغي
لن يزداد لكن المصنوع هو زيادة بهت التيار) توتب على زرد
انقاسه بغيره صفت اصاخي له بيان كمنظومة

DC Machines – Commutation Problems

- ▶ In extreme cases, the neutral-plane shift can even lead to flashover in the commutator segments near the brushes.
- ▶ The air near the brushes in a machine is normally ionized as a result of the sparking on the brushes.
- ▶ Flashover occurs when the voltage of adjacent commutator segments gets large enough to sustain an arc in the ionized air above them.
- ▶ If flashover occurs, the resulting arc can even melt the commutator's surface.



حالت ذرية نتيجة الحرارة على

صورة وضع صناعية (A)

DC Machines – Commutation Problems

تأثير كمية من التيار القادح من الموصل

- ▶ The effect of flux weakening is simply to reduce the voltage supplied by the generator for any given load.
- ▶ In motors, this effect increases the speed and then probably the load, resulting in more flux weakening.
- ▶ It is possible for some motors to reach a runaway condition.
- ▶ as a result of flux weakening, where the speed of the motor just keeps increasing until the machine is disconnected from the power line or until it destroys itself.

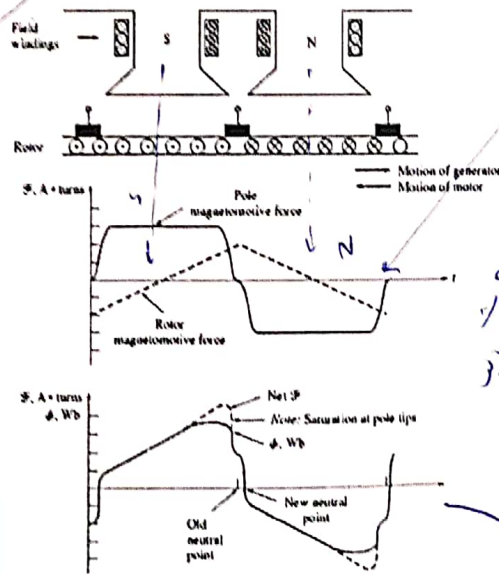


FIGURE 8-25 The flux and magnetomotive force under the pole faces in a dc machine. At those points where the magnetomotive forces subtract, the flux closely follows the net magnetomotive force in the iron; but at those points where the magnetomotive forces add, saturation limits the total flux present. Note also that the neutral point of the rotor has shifted.

السطح المستطع هو

العمود الوصل بين القطب والقطب

المغناطيسية
تتغير
بسبب التغير في المجال
المغناطيسي
S و N

في نقطة
مع بعض
شئ

حفظ

حفظ

يقولون ان
التيار القادح
يقلل من
المجال المغناطيسي
التيار القادح
يقلل من
المجال المغناطيسي

تتغير السرعة
التيار القادح
يقلل من
المجال المغناطيسي
P2
حالي

كيف ابر brushes ندها تهر. Started out ال segments ؟

ال Commutator عبارة عن segments (مقسمة مسطحة) والقطعة
يتلف حولها فإلحظة من قاي الاخطات مكان ال brush تكون ملامسة
Two segments و بهر كنب اتيار يتوزع على القطب و بهر كنب
القطب قاي $\frac{dI}{dt}$ (Inductive Kick) اكي قوا ال Drop voltage
و كويو م ا كني (Inductive Kick) قاي كني قاي متغير
القطب

Drop voltage
سقوط الجهد
Rotor $\omega = \omega_c$


DC Machines – Commutation Problems

- ▶ $L \frac{di}{dt}$ voltage that occurs in commutator segments being shorted out by the brushes, sometimes called **inductive kick**
- ▶ This voltage is relatively high and naturally causes sparking at the brushes of the machine, resulting in the same arcing problems that the neutral-plane shift causes.

سقوط الجهد في اقسام commutator

بالسرعة الزاوية

بتغير مستوى المحايد
Neutral Plane

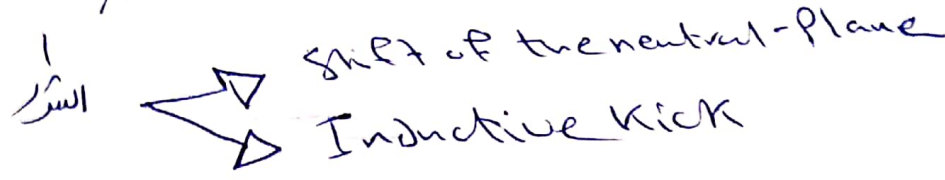

سبب
الشرارة
القضبان

DC Machines – Commutation Problems

Three approaches have been developed to partially or completely correct the problems of armature reaction and $L \frac{di}{dt}$ voltages:

- (1) Brush shifting
- (2) Commutating poles or interpoles
- (3) Compensating windings

أساليب
تصحيح
مشاكل
التي تحدث
بسبب
تفاعل
التيار
المتحرك
او
سقوط
الجهد

Shifting brushes

ایک فوٹو دیکھو
 انوار Mutual
 Phase
 سٹرڈ وینٹ ما انٹرویو
 سیرینڈیٹ

دیکھنا یہاں آف انڈر ایچ ایک سیرینڈیٹ ہے اس کے اگلے وینٹ
 اور segments ایک ہے جو کہ ایک سیرینڈیٹ ہے اس کے ساتھ
 ایک ہے = یہی ہے کہ ایک سیرینڈیٹ ہے اس کے ساتھ
 یہی ہے کہ ایک سیرینڈیٹ ہے اس کے ساتھ
 یہی ہے کہ ایک سیرینڈیٹ ہے اس کے ساتھ

Commutating Poles or Interpoles

تین وینٹس اور N & S یا ایک سیرینڈیٹ ہے اس کے ساتھ

ار N & S

یہ وہاں ہے اور وہاں ہے اس کے ساتھ
 ایک سیرینڈیٹ ہے اس کے ساتھ
 یہی ہے کہ ایک سیرینڈیٹ ہے اس کے ساتھ
 یہی ہے کہ ایک سیرینڈیٹ ہے اس کے ساتھ



من الممكن ان توقف السيار وكثيرا فحالت تزييد من سرعة او تايثير ضعف الجهد
 الامتصاص في الناسر عن الارض تزييد في الالة والاهامة كزييد
 Electrical Machines (110405323) Dr. Mohammad Salah 31

DC Machines – Commutation Problems

- ▶ **Shifting brushes** may stop the sparking but it actually aggravated the flux-weakening effect of the armature reaction in the machine. In addition, the neutral plane moves with every change in load, and the shift direction reverses when the machine goes from motor operation to generator operation.
- ▶ By about 1910, the brush-shifting approach to controlling sparking was already obsolete. Today, brush-shifting is only used in very small machines that always run as motors.

من الممكن ان
 تزييد من سرعة
 الجهد

فما تبعه انما هو بالالة =
 الصغيرة ان ستمتدز انما في اسات انما
 عولف مزل انما في اسات انما في اسات
 Electrical Machines (110405323) Dr. Mohammad Salah 32

DC Machines – Commutation Problems

- ▶ If the voltage in the wires undergoing commutation can be made zero, then there will be no sparking at the brushes.
- ▶ To accomplish this, small poles, called **commutating poles or interpoles**, are placed midway between the main poles.

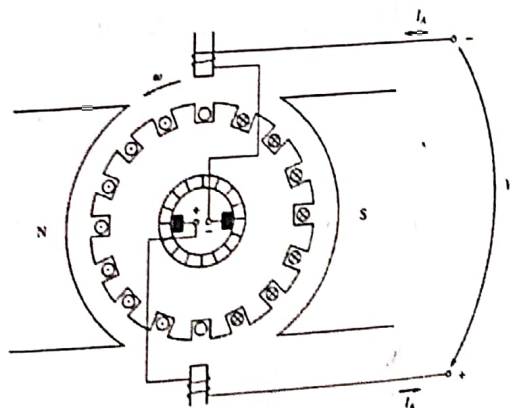


FIGURE 8-28
 A dc machine with interpoles.


من الممكن ان
 تزييد من سرعة
 الجهد

مشکل ضعف بولمان ابلیطیب کما یونینت انمار
 ملینت سبب کتتقی مع فلود
 Structure Reaction و magnetic field weakening


الات کبیرة واهمال کبیرة وخی کند - **Duty cycle**

یعنی شغل و ابلین
 شغل فاطلی

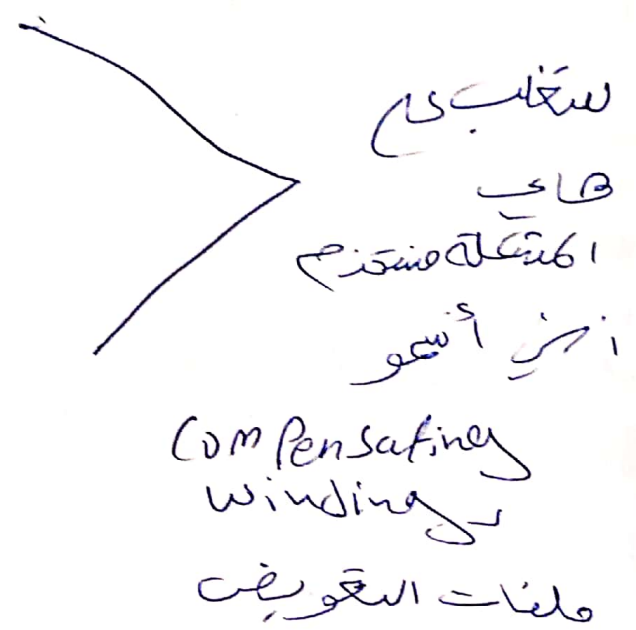فادالینت بعل تیای
 بد عادیة کبیرة کتت
 ممکن سبب ال Armature
 Reaction و weak magnetic
 field



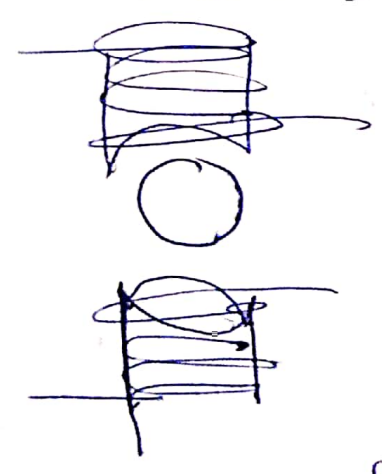تبعی مضر با ابلایب ای سبب یی وین الا قضا - ای بکورد
 هوزتة لکوهات ال Rotor



یکوتتقی Slots ملف
 علیها ملفات القویض
 تتولد فبال مضناطیبی تتعرض
 النقص ای حد او تبعل

Cancel للکمال المضناطیبی ای صاع - من ال Rotor فنبلی
 ابلع ال ای فوئلین اما یی فوالاب یعن الا قضا و تبع
 توصلی مع التواک لصب کما زاد العمل بزاد ال فبیرة ابلع

DC Machines – Commutation Problems

These commutating poles are located directly over the conductors being commutated. By providing a flux from the commutating poles, the voltage in the coils undergoing commutation can be exactly canceled. If the cancellation is exact, then there will be no sparking at the brushes.

▶ The use of commutating poles or interpoles is very common, because they correct the sparking problems of dc machines at a fairly low cost.

▶ They are almost always found in any dc machine of 1 hp or larger.

It is important to realize, though, that they do nothing for the flux distribution under the pole faces, so the flux-weakening problem is still present.

بالفردية
منه قريبا
التي تسمى
motor

أعلى
تدوير
التي تسمى
المحرك

توزيع المجال المغناطيسي سيضعف كفاية فهو قادر على توليد حل مشكلة ضعف المجال المغناطيسي

DC Machines – Commutation Problems

▶ For very heavy, severe duty cycle motors, the flux-weakening problem can be very serious.

▶ To completely cancel armature reaction and thus eliminate both neutral-plane shift and flux weakening, compensating windings are placed in slots carved in the faces of the poles parallel to the rotor conductors, to cancel the distorting effect of armature reaction.

▶ These windings are connected in series with the rotor windings, so that whenever the load changes in the rotor, the current in the compensating windings changes, too.

مخالف
التعويض

DC Machines – Commutation Problems

Compensating windings
 في دارة التحويل
 التي تلتحق بالقطب
 لكي تلغي التدفق
 الناتج عن التيار
 في الدارة

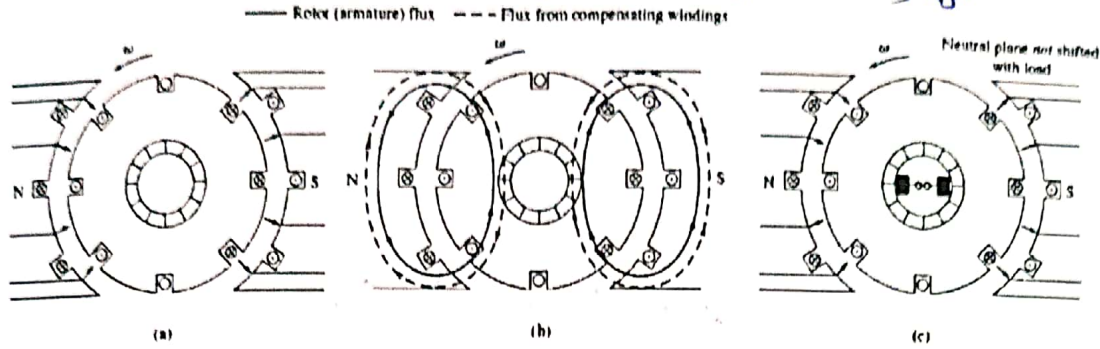


FIGURE 8-30
 The effect of compensating windings in a dc machine. (a) The pole flux in the machine; (b) the fluxes from the armature and compensating windings. Notice that they are equal and opposite; (c) the net flux in the machine, which is just the original pole flux.

عالية لأنها كالتالي تتغير مع حمل القطب يعني كالم
 في المحركات على الأقطاب - عملياً تحفظ
 DC Machines – Commutation Problems

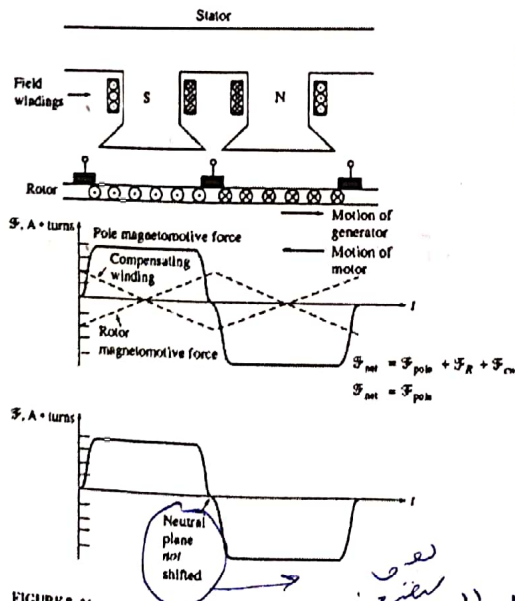


FIGURE 8-31
 The flux and magnetomotive forces in a dc machine with compensating windings.

The major disadvantage of compensating windings is that they are expensive, since they must be machined into the faces of the poles. Any motor that uses them must also have interpoles, since compensating windings do not cancel $L \frac{di}{dt}$ effects. Because of the expense of having both compensating windings and interpoles on such a machine, these windings are used only where the extremely severe nature of a motor's duty demands them.

صيانة
 ملف
 التعويض
 أي عيوب
 كالتالي
 لا يتحمل
 حمل
 الشحنة
 التوتيتو
 مع
 ال
 InterPoles

سبب كلفتها العالية جداً
 في دارة DC تتغير مع حمل القطب
 Duty Demand
 في المحركات على الأقطاب - عملياً تحفظ


كالتالي يتغير تيار
 تأثير
 Inductive
 kick

رأى في جميع الآلات كما في مبداء ديفيات من عملية التحويل

5 أقسام الخسائر الضياع

$I^2 R \Delta$ losses
Electric or copper losses
تنتج عن مرور تيار في
المكونات الداخلية
للمحاور (مخيمات نحاسية)

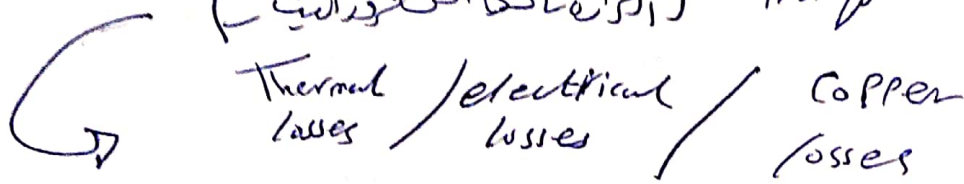كلما انخفضت أوقات الضياع في سبب حرارة والنفاس من مقتر
المواد التي يتبعها لتوصيل التيار والنفاس بعد حرارة عناء
هيك (تسبب Copper) (الحرارة ناتجة من مرور التيار)



Brush losses
الضياع = صدمة مع (Commutator) نقطة التماس التي تتغير
التيار والظبية في عليها صدمة يصير عليها
Drop voltage وقد اد Prop فوار Brush losses

Core losses
ضيات إحصاء المعنوية من ال Ferromagnetic المعبوية
داخل المحرك و مرور التيار داخلها بعد ضيات

ضيات ميكانيكية (احتكاك أو أي شيء آخر)

الضياع اشارة التوائسفة ← يتغير حسب تغير فجوة المحرك

DC Machines – Power Flow and Losses

- ▶ In all DC machines, there is always some loss associated with the operation.
- ▶ The losses that occur in DC machines can be divided into five basic categories:

1. Electrical or copper losses (I^2R losses)
2. Brush losses
3. Core losses
4. Mechanical losses
5. Stray load losses

الضخمة السارية

DC Machines – Power Flow and Losses

لأننا كان نحوي

- ▶ Electrical or copper losses are the losses that occur (in the armature and field windings of the machine.)
- ▶ The copper losses for the armature and field windings are given by

Permeant-
Magnetic
Field
motor

Armature loss:	$P_A = I_A^2 R_A$
Field loss:	$P_F = I_F^2 R_F$

(8-52)
(8-53)

الضخمة
تكون صمكة
فقط هي
صفت =
الأنشور

- where
- P_A = armature loss
 - P_F = field circuit loss
 - I_A = armature current
 - I_F = field current
 - R_A = armature resistance
 - R_F = field resistance

صفت
صفت
الضخمة
تكرارة
لحساب
الأنشور

الفقد = الفقد الناتج عن كسب الحديد = الفقد الناتج عن كسب الحديد (Core loss)

DC Machines – Power Flow and Losses

- ▶ **Brush losses** is the power lost across the contact potential at the brushes of the machine. It is given by the equation

$$P_{BD} = (V_{BD}) I_A \quad (8-54)$$

where P_{BD} = brush drop loss
 V_{BD} = brush voltage drop
 I_A = armature current

prop voltage on brush

- ▶ The reason that the brush losses are calculated in this manner is that the voltage drop across a set of brushes is approximately constant over a large range of armature currents. Unless otherwise specified, the brush voltage drop is usually assumed to be about 2 V.

نفسه شرط السرعة = يمكن اعتبار ثابت في نظامنا والى من الإقتصر

DC Machines – Power Flow and Losses

- ▶ **Core losses** are the **hysteresis losses** and **eddy current losses** occurring in the metal of the motor.

These losses vary as the square of the flux density (B^2) and for the rotor, as the 1.5th power of the speed of rotation ($n^{1.5}$).

- ▶ **Mechanical losses** are associated with mechanical effects and there are two basic types:

1. **Friction losses** are losses caused by the friction of the bearings in the machine.

2. **Windage losses** are caused by the friction between the moving parts of the machine and the air inside the motor's casing.

- ▶ These losses vary as the cube of the speed (n^3).

مع الهواء (Rotor) مع الهواء (Air gap) مع الهواء (Air gap)

← تناسب كمية صيفت ال ρ \approx تقريباً مع (ρ^2) ← Flux density
 ← تناسب كبرياء مع سرعة دوران الحركة
 للقوة ١٥

← تناسب الصفات الكمية متناسب كبرياء مع كتل
 السرعة دوران الحركة

DC Machines – Power Flow and Losses

- **Stray losses (or miscellaneous losses)** are losses that cannot be placed in one of the previous categories. No matter how carefully losses are accounted for, some always escape inclusion in one of the above categories.
- All such losses are lumped into **stray losses**. For most machines, stray losses are taken by convention to be 1% of full load input power.

1% of Input Power
في كامل الحمل

التي
لا
تحتسب
فيها

DC Machines – Power Flow and Losses

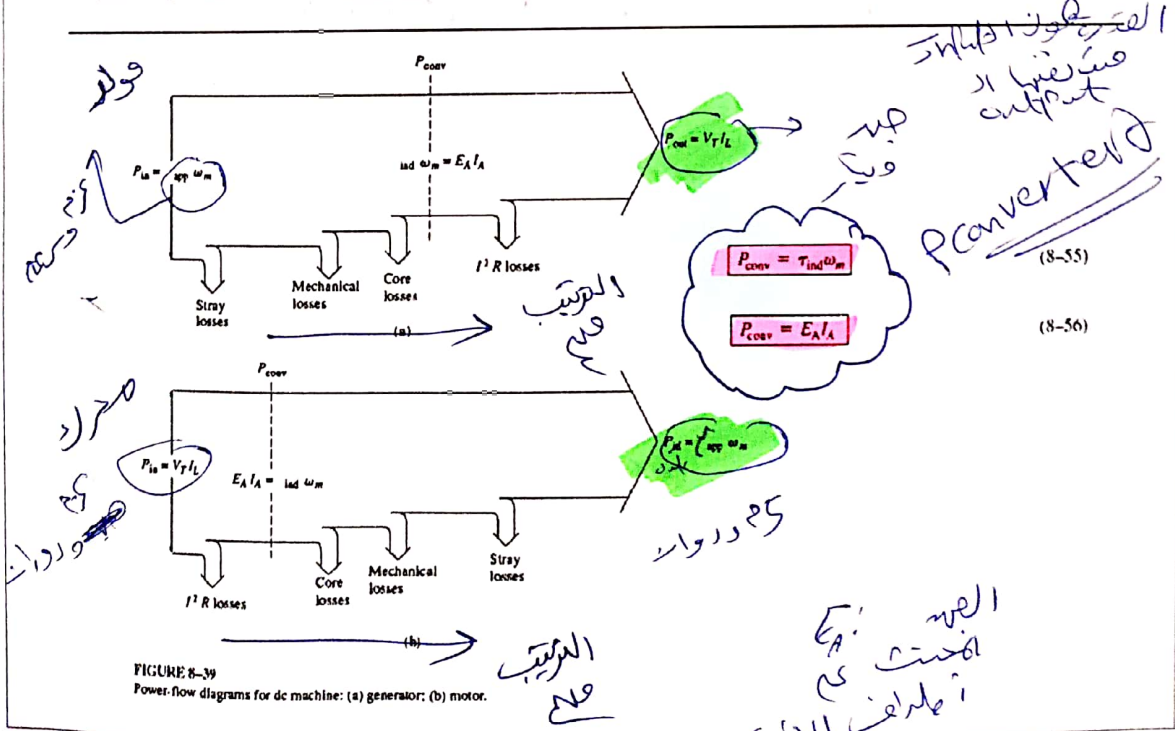


FIGURE 8-39 Power-flow diagrams for dc machine: (a) generator; (b) motor.

التي
تحتسب
فيها
output
P converted

$P_{conv} = T_{ind} \omega_m$
 $P_{conv} = E_A I_A$

التي
تحتسب
فيها
التي
تحتسب
فيها

التي
تحتسب
فيها

DC Machines – Power Flow and Losses

The efficiency of a DC machine is defined by the equation

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$


Handwritten notes: *الكفاءة* (efficiency), *قدرة الخارج* (output power), *قدرة الداخل* (input power)

$$\eta = \frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

	P_{in}	P_{out}
فولت	جهد	جهد
أمبير	تيار	تيار

DC Machines – Simple Rotating Loop

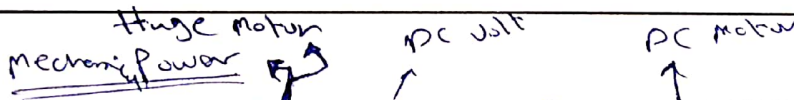

Example 9.8 (A 50 hp, 250 V, 1200 rpm shunt dc motor) has a rated armature current of 170 A and a rated field current of 5 A. When its rotor is blocked, an armature voltage of 10.2 V (exclusive of brushes) produces 170 A of current flow and a field voltage of 250 V produces a field current flow of 5 A. The brush voltage drop is assumed to be 2 V. At no load with the terminal voltage equal to 240 V, the armature current is equal to 13.2 A, the field current is 4.8 A, and the motor's speed is 1150 rpm.

- How much power is output from this motor at rated conditions?
- What is the motor's efficiency?


صفتي
جز
التيار
الارادي
تأثير
الحث
يكون
التيار
المتحرك
لا ينفصل
من
التيار
الارادي
التيار
المتحرك
لا ينفصل
من
التيار
الارادي

الكفاءة
Include all losses

أي
قدرة
للجهد
يكون
Full load
Rate Value
R. motor
1200
1150
شنت
DC
Motor
الكفاءة
التيار
المتحرك
لا ينفصل
من
التيار
الارادي

← كاشف الصواعق اطراف الكوفة السوية في نقل


DC Machines – Types

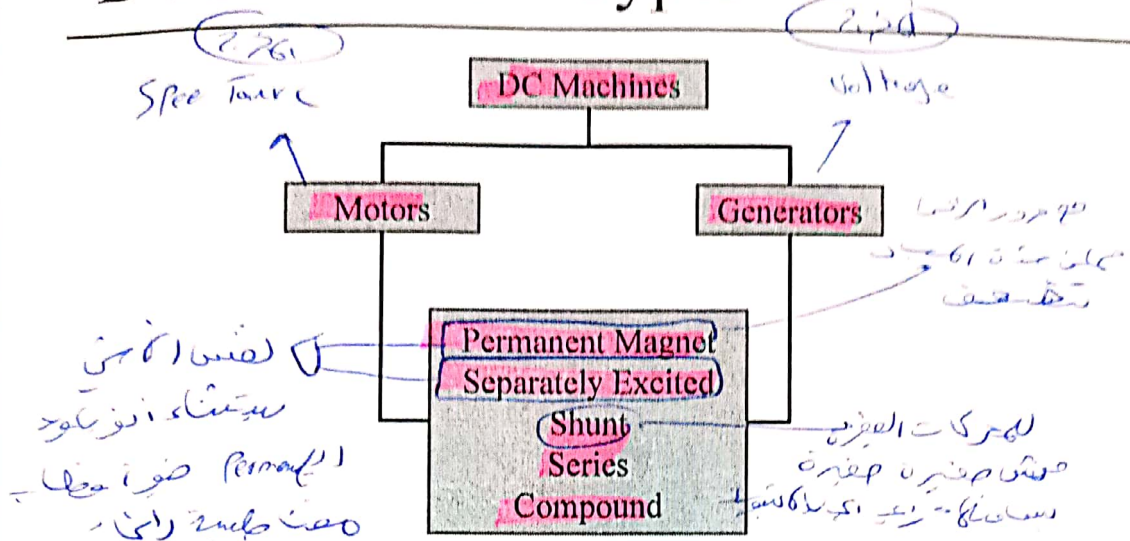

These various types of DC machines differ in their output (voltage-current) characteristics if they are generators or (speed-torque) characteristics if they are motors, and therefore in the applications to which they are suited.

DC Machines – Types

- ▶ In a **separately excited machine**, the field flux is derived from a separate power source.
- ▶ In a **shunt machine**, the field flux is derived by connecting the field circuit directly across the terminals of the armature.
- ▶ In a **series machine**, the field flux is produced by connecting the field circuit in series with the armature.
- ▶ In a **cumulatively compounded machine**, both a shunt and a series field are present, and their effects are additive.
- ▶ In a **differentially compounded machine**, both a shunt and a series field are present, but their effects are subtractive.

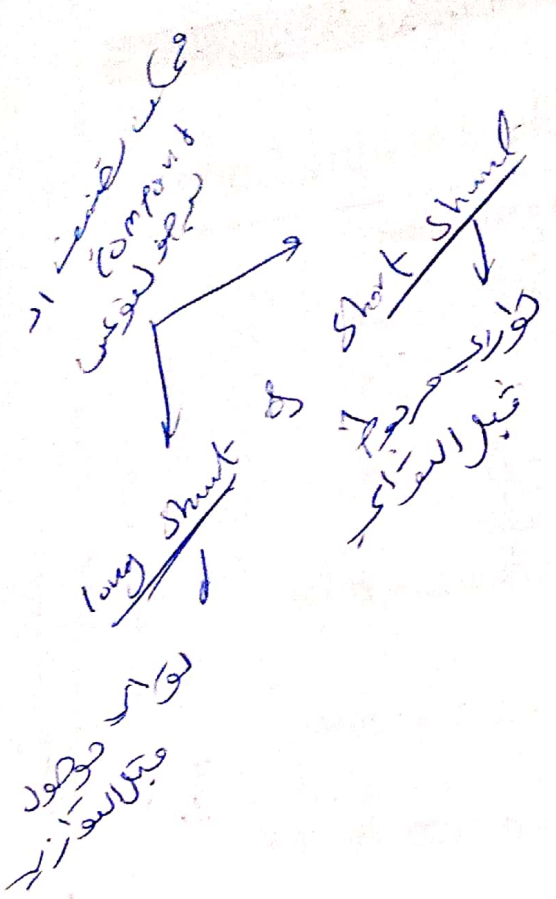


Shunt

المكافئ للتوازي مع التوازي

series

المكافئ للتوازي مع التوازي

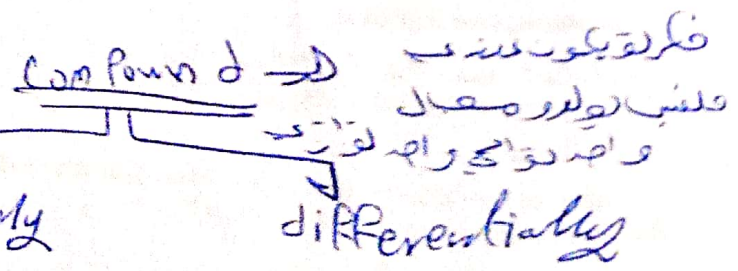

انما كان المكافئ التوازي
بعض التوازي والتوازي
بعض التوازي

لنا ك توازي المكافئ التوازي
والتوازي يعكس التوازي

DC Machines – Types



- ▶ Types of DC Motors - Classification of DC Motors
<https://www.youtube.com/watch?v=uth3248pzzqM>

DC Machines – Generators

- ▶ DC generators are compared by their voltages, power ratings, efficiencies, and voltage regulations.

- ▶ Voltage regulation (VR) is defined by the equation

$$VR = \frac{V_{nl} - V_{fl}}{V_{fl}} \times 100\%$$


- ▶ V_{nl} is the no-load terminal voltage of the generator and V_{fl} is the full-load terminal voltage of the generator

- ▶ It is a rough measure of the shape of the generator's voltage-current characteristic. A positive voltage regulation means a drooping characteristic, and a negative voltage regulation means a rising characteristic.

voltage regulation (Rough measure)

$$V_p = \frac{V_{nl} - V_{fl}}{V_{fl}}$$

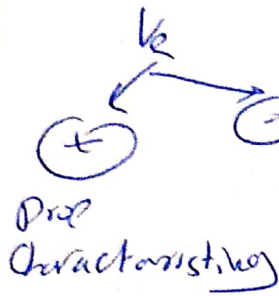مقياس تقديري
 بجعلناك حمل
 العولن والبريت
 الحاص بنا يكون كيف
 يكون بلكو



Rising Characteristic

العرضة بالتحمل

العرضة
 التي ينقص
 بالتحمل

$V_{nl} \Rightarrow$ صفر الحمل
 No load

nl: no load

$V_{fl} \Rightarrow$ الحمل
 Full load

FL: Full load

على السهل الحمل يعني بزيادة الحمل كبري يمكن يكون صيانة أو مقاومة
 أو مكثف أو مسمكة صفر كالتوضيح حوله يعني كبري
 يمكن يكون فولج براتاي يعني صفر كالتوضيح صفر
 Regulation

\Rightarrow Rising characteristic

وأي حمل يعني (مقاومة متغير) والبر
 Regulation \Rightarrow Prop characteristic

DC Machines – Generators

- ▶ All generators are driven by a source of mechanical power, which is usually called the **prime mover** of the generator.
- ▶ A prime mover for a DC generator may be a steam turbine, a diesel engine, or even an electric motor.
- ▶ Since the speed of the prime mover affects the output voltage of a generator, and since prime movers can vary widely in their speed characteristics, it is customary to compare the voltage regulation and output characteristics of different generators, assuming constant speed prime movers.
- ▶ DC generators are quite rare in modern power systems. Even DC power systems such as those in automobiles now use **AC generators plus rectifiers to produce DC power**.

DC Machines – Generators

Separately Excited DC Generators

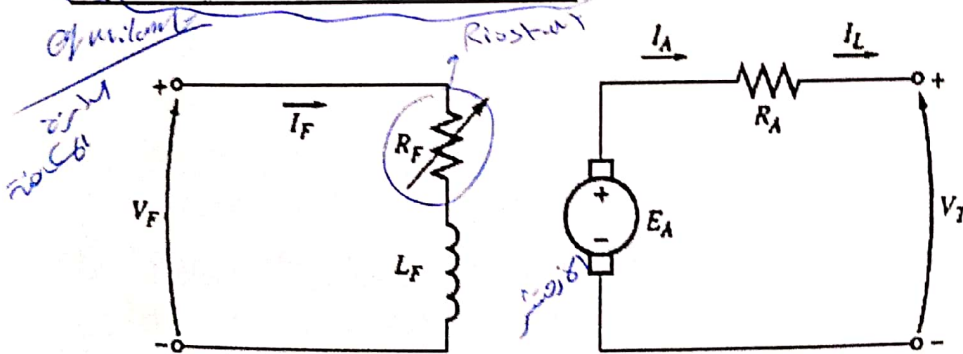


FIGURE 9-44
A separately excited dc generator.

$$I_L = I_A$$

$$V_T = E_A - I_A R_A$$

$$I_F = \frac{V_F}{R_F}$$

For a constant speed $V_T = E_A - I_A R_A$


(9-41)

Handwritten notes in Arabic: "السرعة ثابتة" (constant speed), "التيار في الحثية يساوي التيار في الحمل" (armature current equals load current), "توليد كهرطيسية" (electromagnetic induction), "تحويلها إلى تيار" (converting it to current).


Prm
Movers

تغير سكر كبير بالتالي الصفات والتغير
العدد والتغير والتغير
حاصل التغير
حاصل التغير

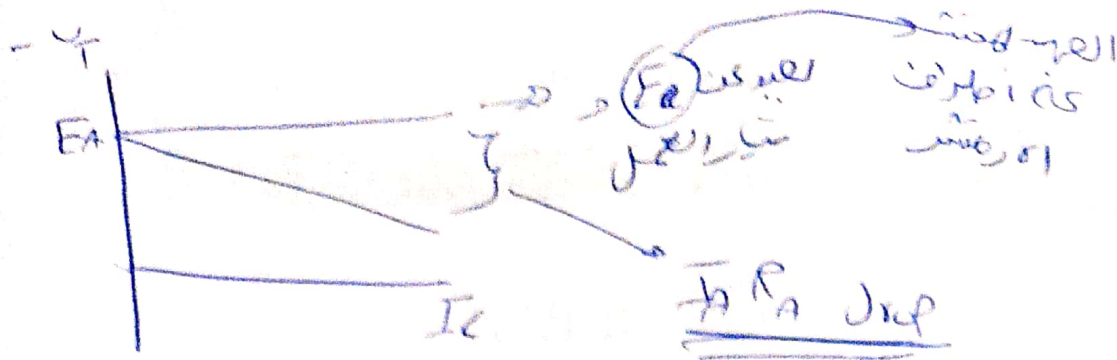حاصل التغير التغير والتغير والتغير
التغير والتغير والتغير
IF



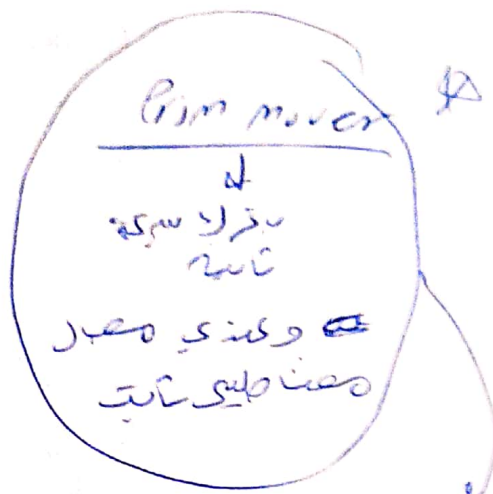V_t بتغير
 Voltage Terminal
 الجهد الداخلي $I_c R_a$ drop
 الجهد الداخلي $I_c R_a$ drop
 الجهد الداخلي $I_c R_a$ drop



Terminal Voltage E_a عند حالة الحمل $I_c R_a$ drop
 Voltage

Voltage drop $I_c R_a$ عند حالة الحمل $I_c R_a$ drop
 Voltage

Voltage drop $I_c R_a$ عند حالة الحمل $I_c R_a$ drop
 Voltage

Voltage drop $I_c R_a$ عند حالة الحمل $I_c R_a$ drop
 Voltage

Voltage drop $I_c R_a$ عند حالة الحمل $I_c R_a$ drop
 Voltage

زيادة الحمل الكهربائي لا تقى انز اعبر العمل كونه
 انقسام مقادير العمل

DC Machines – Generators

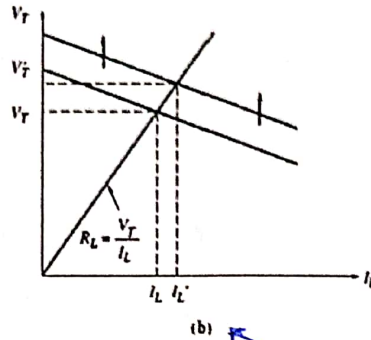
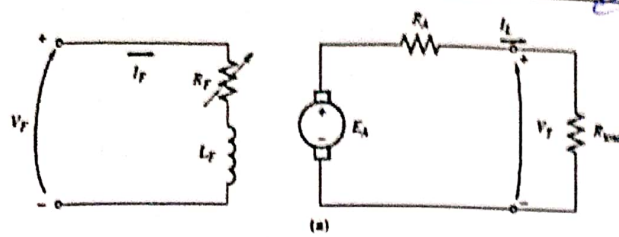


FIGURE 9-46 (a) A separately excited dc generator with a resistive load. (b) The effect of a decrease in field resistance on the output voltage of the generator.

equivalent circuit of DC generator

تغير في الجهد مع التغير في المقاومة

زيادة في المقاومة، تنخفض نسبة تقطع المقاومة لزيادة الجهد الكهربي بحيث لا يتغير العلاقة $E_A = k \Phi \omega$

فتكون الجهد الناتج يتناسب مع سرعة الدوران خاصة إذا كان الحمل ثابتاً
أيضا سرعة الدوران من ذلك إذا كان الحمل ثابتاً يتغير الجهد

DC Machines – Generators

- ▶ Because the internal generated voltage of a generator is a nonlinear function of its magnetomotive force, it is not possible to calculate simply the value of E_A to be expected from a given field current.
- ▶ The magnetization curve of the generator must be used to accurately calculate its output voltage for a given input voltage.
- ▶ In addition, if a machine has armature reaction, its flux will be reduced with each increase in load, causing E_A to decrease.
- ▶ The only way to accurately determine the output voltage in a machine with armature reaction is to use graphical analysis.

التيار الكهربي في الدائرة المغناطيسية يغير الجهد الناتج

التيار الكهربي في الدائرة المغناطيسية يغير الجهد الناتج
في حالة الحمل الثابت


أحد دوائر معالجة إشارات منفصلة يكون في ظلها غير مستمرة
بالتالي السلوك يكون Non-linear

Minimization curve ⇒ مبرمجيات
كالمتين

الكثيرة لتأثيرات
منه في حساب القيم
الخرج
Output voltage

قوة الدافع المغناطيسي في سلك الموصلات تكون حثية في شكلها
 القوة الدافع المغناطيسي في سلك الموصلات تكون حثية في شكلها

DC Machines – Generators

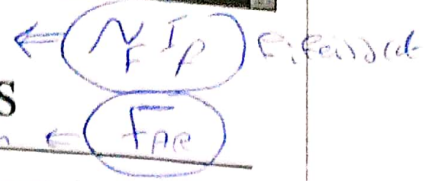

- The total magnetomotive force in a separately excited generator is the field circuit magnetomotive force less the magnetomotive force due to armature reaction (AR):

$$F_{net} = N_F I_F - F_{AR}$$

$F_{AR} = 0$
 is use same (combination) with binary

- As with DC motors, it is customary to define an **equivalent field current** that would produce the same output voltage as the combination of all the magnetomotive forces in the machine.
- The resulting voltage E_{A0} can then be determined by locating that equivalent field current on the magnetization curve.

DC Machines – Generators

Armature reaction
 Reactance
 Flux

- The equivalent field current of a separately excited DC generator is given by

$$I_F^* = I_F - \frac{F_{AR}}{N_F}$$

Equivalent field current

- Also, the difference between the speed of the magnetization curve and the real speed of the generator must be taken into account:

$$\frac{E_A}{E_{A0}} = \frac{n}{n_0}$$

نسبة السرعة بين السرعة الحقيقية والسرعة الاسمية
 عند السرعة الاسمية
 عند السرعة الحقيقية

DC Machines – Generators

Example 9.9 A separately excited dc generator is rated at 172kW, 430V, 400A, and 1800 r/min. It is shown in Figure 9-47 and its magnetization curve is shown in Figure 9-48. This machine has the following characteristics: $R_A=0.05 \Omega$, $R_F=20\Omega$, $R_{adj}=0$ to 300Ω , $V_F = 430V$, $N_F = 1000$ turns per pole (a) If the variable resistor R_{adj} in this generator's field circuit is adjusted to 63Ω and the generator's prime mover is driving it at 1600 r/min, what is this generator's no-load terminal voltage? (b) What would its voltage be if a 360-A load were connected to its terminals? Assume that the generator has compensating windings. (c) What would its voltage be if a 360-A load were connected to its terminals but the generator does not have compensating windings? Assume that its armature reaction at this load is 450 A·turns. (d) What adjustment could be made to the generator to restore its terminal voltage to the value found in part a? (e) How much field current would be needed to restore the terminal voltage to its no-load value? (Assume that the machine has compensating windings.) What is the required value for the resistor R_{adj} to accomplish this?

DC Machines – Generators

- (d) The voltage at the terminals of the generator has fallen, so to restore it to its original value, the voltage of the generator must be increased. This requires an increase in E_A , which implies that R_{adj} must be decreased to increase the field current of the generator.
- (e) For the terminal voltage to go back up to 382 V, the required value of E_A is

$$E_A = V_T + I_A R_A = 382 \text{ V} + (360 \text{ A})(0.05 \Omega) = 400 \text{ V}$$

To get a voltage E_A of 400 V at $n_n = 1600 \text{ r/min}$, the equivalent voltage at 1800 r/min would be

$$\frac{E_A}{E_{A0}} = \frac{n}{n_0} \quad (9-13)$$

$$E_{A0} = \frac{1800 \text{ r/min}}{1600 \text{ r/min}} 400 \text{ V} = 450 \text{ V}$$

From the magnetization curve, this voltage would require a field current of $I_F = 6.15 \text{ A}$. The field circuit resistance would have to be

$$R_F + R_{adj} = \frac{V_F}{I_F}$$

$$20 \Omega + R_{adj} = \frac{430 \text{ V}}{6.15 \text{ A}} = 69.9 \Omega$$

$$R_{adj} = 49.9 \Omega \approx 50 \Omega$$

DC Machines – Motors

- ▶ Today, induction motors with solid-state drive packages are the preferred choice over DC motors for most speed control applications. However, there are still some applications where dc motors are preferred.
- ▶ DC motors are often compared by their speed regulations.
- ▶ The speed regulation (SR) of a motor is defined by

$$SR = \frac{\omega_{nl} - \omega_{fl}}{\omega_{fl}} \times 100\%$$

$$SR = \frac{n_{nl} - n_{fl}}{n_{fl}} \times 100\%$$

DC Machines – Motors

- ▶ It is a rough measure of the shape of a motor's speed-torque characteristic. A (positive speed regulation) means that a motor's speed drops with increasing load, and a (negative speed regulation) means a motor's speed increases with increasing load.
- ▶ The magnitude of the speed regulation tells approximately how steep the slope of the torque- speed curve is.
- ▶ It is a rough measure of the shape of a motor's torque-speed characteristic. A positive speed regulation means that a motor's speed drops with increasing load, and a negative speed regulation means a motor's speed increases with increasing load.


DC Machines – Motors

- ▶ The magnitude of the speed regulation tells approximately how steep the slope of the torque- speed curve is.
- ▶ It should be noted that in order to get the maximum possible power per pound of weight out of a machine, most motors and generators are designed to operate near the saturation point on the magnetization curve (at the knee of the curve).
- ▶ This implies that a fairly large increase in field current is often necessary to get a small increase in E_A when operation is near full load.

نوع العزم المطلوب *
 العزم المطلوب

فی اغلب اکثر کت دایا در Speed Regulation
تفاوت فریبه بین سیکلر از ایا کیره
آورده

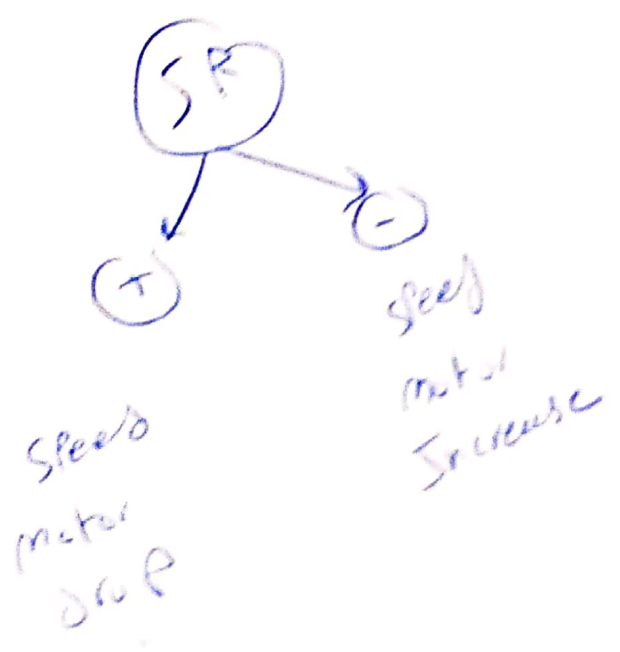سجلی معلومه تقریباً دین اکتفا نه منجای
اصفا رف عمل فوجا اکتفا از لقیف اکتفا



DC Machines – Motors

Separately Excited and Shunt DC Motors

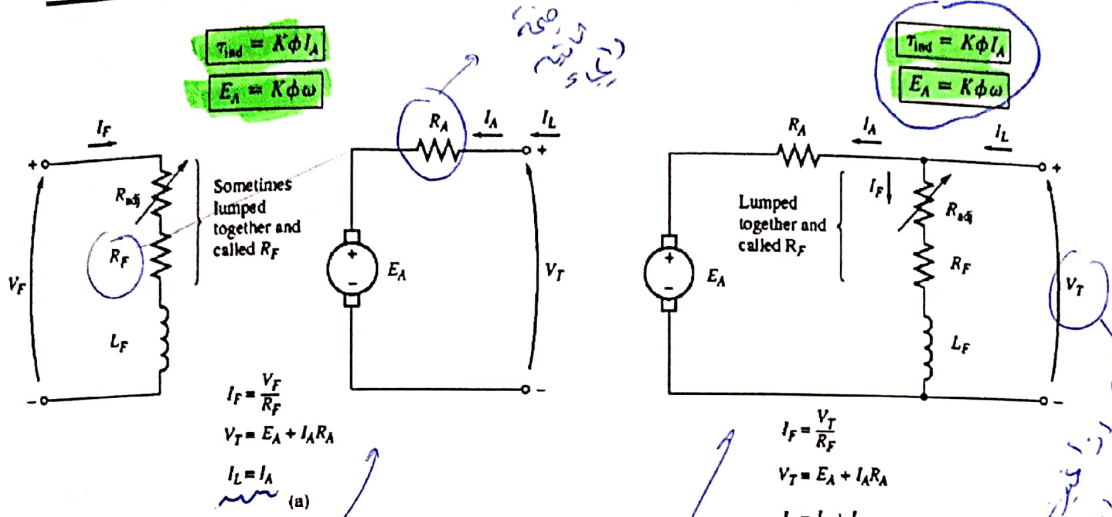


FIGURE 9-5 (a) The equivalent circuit of a separately excited dc motor. (b) The equivalent circuit of a shunt dc motor.

DC Machines – Motors

- The output characteristic of a separately excited and shunt DC motors can be derived from the induced voltage and torque equations of the motor plus Kirchhoff's voltage law as

$$V_T = E_A + I_A R_A$$

$$V_T = K\phi\omega + I_A R_A$$

$$V_T = K\phi\omega + \frac{\tau_{ind}}{K\phi} R_A \text{ where } \tau_{ind} = I_A K\phi$$

$$\Rightarrow \omega = \frac{V_T}{K\phi} - \frac{R_A}{(K\phi)^2} \tau_{ind}$$

Handwritten notes in Arabic: "هذا هو المخطط التفاضلي" (This is the differential characteristic), "منه نحصل على سرعة المحرك" (From it we get the motor speed), "في ظل حمل ثابت" (under constant load).

Handwritten notes in Arabic: "V_T ∝ سرعة المحرك" (V_T ∝ motor speed), "R_A ∝ سرعة المحرك" (R_A ∝ motor speed), "φ ∝ سرعة المحرك" (φ ∝ motor speed), "∴ V_T ∝ R_A ∝ φ ∝ ω" (∴ V_T ∝ R_A ∝ φ ∝ ω).

قولون ← اللوب مع بيتا -

بينبريتون ←

دلتا مع اللوب مع

التقاء التباين



المعز لا يكون داخل AR

الممول يكون خارج AR

DC Machines – Motors

It is important to realize that, in order for the speed of the motor to vary linearly with torque, the other terms in this expression must be constant as the load changes.

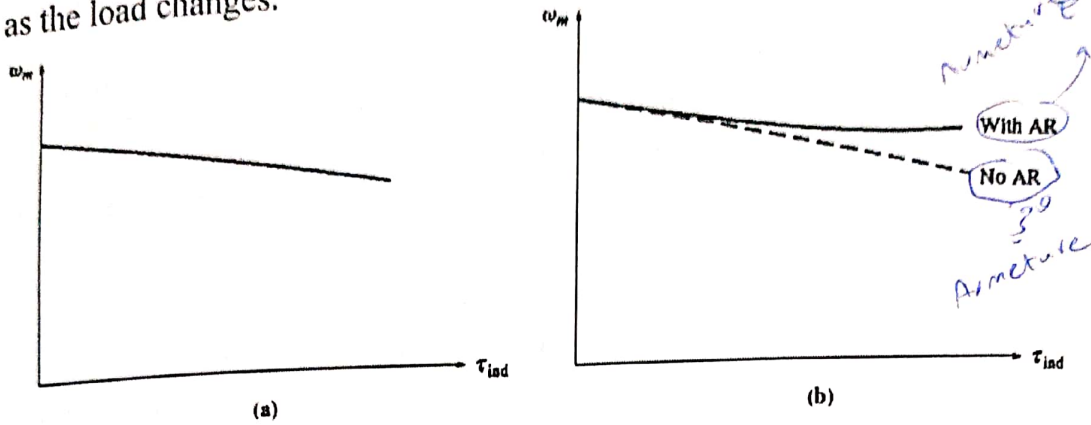


FIGURE 9-6 (a) Torque-speed characteristic of a shunt or separately excited dc motor with compensating windings to eliminate armature reaction. (b) Torque-speed characteristic of the motor with armature reaction present.

DC Machines – Motors

Example 9.1 A 50-hp, 250-V, 1200 r/min dc shunt motor with compensating windings has an armature resistance (including the brushes, compensating windings, and interpoles) of 0.06Ω . Its field circuit has a total resistance $R_{adj} + R_F$ of 50Ω , which produces a no-load speed of 1200 r/min. There are 1200 turns per pole on the shunt field winding (see Figure 9-7).

- (a) Find the speed of this motor when its input current is 100 A.
- (b) Find the speed of this motor when its input current is 200 A.
- (c) Find the speed of this motor when its input current is 300 A.
- (d) Plot the to torque-speed characteristic of this motor.

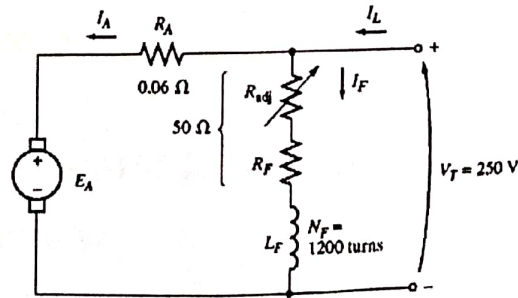


FIGURE 9-7 The shunt motor in Example 9-1.

$F \leq M$

No load \Rightarrow
 يكون في حد
 بعد لث

DC Machines – Motors

(b) At 200 A of load in Example 9-1, the motor's speed was $n = 1144$ r/min. In this example, the motor's speed is 1227 r/min. Notice that the speed of the motor with armature reaction is higher than the speed of the motor with no armature reaction. This relative increase in speed is due to the flux weakening in the machine with armature reaction.

(c)

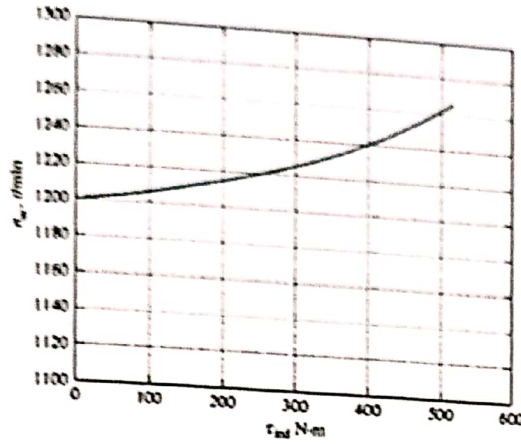


FIGURE 9-10 The torque-speed characteristic of the motor with armature reaction in Example 9-2.

DC Machines – Motors كيفية سيطرة السرعة

There are two common ways in which the speed of a separately excited and shunt DC motors can be controlled:

1. Adjusting the field resistance R_F (and thus the field flux) تغيير المقاومة الحثية R_F وبالتالي سيطرة التدفق الحثي
2. Adjusting the terminal voltage applied to the armature. تغيير الجهد الطرفي المطبق على المحرك V_t
3. Inserting a resistor in series with the armature circuit (the less common method of speed control). إدراج مقاومة في السلسلة مع دائرة المحرك (الطريقة الأقل شيوعاً لسيطرة السرعة)

تغيير المقاومة الحثية R_F وبالتالي سيطرة التدفق الحثي

تغيير الجهد الطرفي المطبق على المحرك V_t

DC Machines – Motors

Changing the Field Resistor Control Method

1. Increasing R_F causes $I_F (= V_F/R_F \uparrow)$ to decrease.
2. Decreasing I_F decreases ϕ .
3. Decreasing ϕ lowers $E_A (= K\phi\omega)$.
4. Decreasing E_A increases $I_A (= (V_T - E_A)/R_A)$
5. Increasing I_A increases $\tau_{ind} (= K\phi I_A \uparrow)$, with the change in I_A dominant over the change in flux.
6. Increasing τ_{ind} makes $\tau_{ind} > \tau_{load}$, and the speed ω increases.
7. Increasing ω increases $E_A (= K\phi\omega \uparrow)$ again.
8. Increasing E_A decreases I_A
9. Decreasing I_A decreases τ_{ind} until $\tau_{ind} = \tau_{load}$ at a higher speed ω

DC Machines – Motors

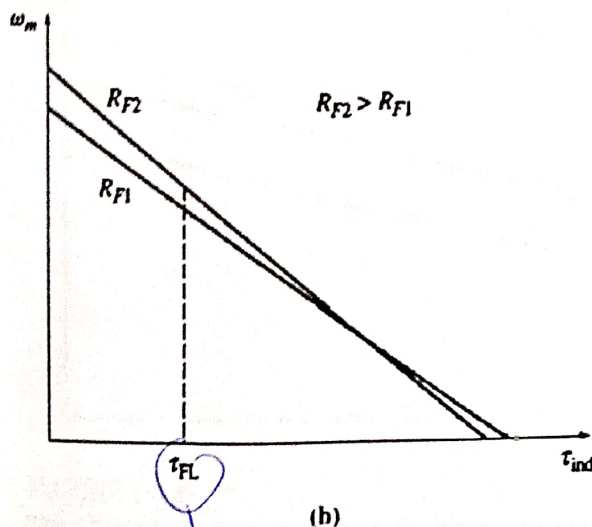


FIGURE 9-12

The effect of field resistance speed control on a shunt motor's torque-speed characteristic: (b) over the entire range from no-load to stall conditions.

تأثير تغيير المقاومة الحقلية على سرعة المحرك عند حمل ثابت

لقد تم تغيير المقاومة الحقلية من R_{F1} إلى R_{F2} حيث $R_{F2} > R_{F1}$ مما أدى إلى زيادة السرعة عند الحمل الثابت τ_{FL} .

زیادہ صحیح اور (R_F) کے تغیرات سے متعلقہ اثرات I_p

لے اگھادوہہ اگھادوہہ
 $R_F + R_{int}$

$$\Delta I_p = \frac{V_F}{R_{eff}}$$

لہذا نقص اور I_p کے ساتھ ساتھ اگھادوہہ کے تغیرات

ساتھ ہی اور R_{int} کے بڑھنا اور I_p کے بڑھنا اور I_A کے بڑھنا

الغیر ہا I_p کے بڑھنا اور R_{int} کے بڑھنا اور ϕ

الغیر ہا اور I_p کے بڑھنا اور R_{int} کے بڑھنا اور I_A کے بڑھنا اور ϕ

الغیر ہا اور I_p کے بڑھنا اور R_{int} کے بڑھنا اور I_A کے بڑھنا اور ϕ

I_p اور R_{int} کے بڑھنا اور I_A کے بڑھنا اور ϕ

$$I_{p1} = I_{p2} \text{ عند } R_{int} \text{ کے بڑھنا اور } \phi$$